

**American University of Beirut**  
Faculty of Engineering and Architecture  
Department of Electrical and Computer Engineering  
ELEG 042 - Analog Electronics  
Instructors: A. Kayssi and Z. Othman  
Quiz 1  
Thursday November 23, 2000

Closed Book  
Programmable Calculators Are Not Allowed.

**Time: 1.5 hours**

VERSION A

Name: \_\_\_\_\_ ID#: \_\_\_\_\_

- ▶ Provide your answer on the *computer card only*.
- ▶ Return the computer card attached to the question sheet.
- ▶ Use a pencil for marking your answers and ID number on the computer card.
- ▶ When using an eraser, make sure you erased well.
- ▶ On this sheet, write with a pen your name followed by your ID number.
- ▶ All questions are equally graded.
- ▶ *Only the computer card will be considered in grading.*

**PENALTY is FOUR to ONE**

1. What is the version of your question sheet? (This question is not graded.)
  - a) Version A
  - b) Version B
  - c) Version C
  - d) Version D
  - e) Version E

**Assume in all problems that:**  
 $|V_{BE}| = 0.7 \text{ V}$   
 $V_T = 25 \text{ mV}$   
 $\beta = 100$  unless otherwise specified  
Capacitors are very large  
Early effect is negligible unless otherwise specified

**In the circuit of Figure 1,  $R_B = 300\text{K}$ .**

2. Find the voltage gain  $v_o/v_i$ .

- a) -0.81      b) -0.97      c) -1.59      d) -2.34      e) -1.21

3. Find the input resistance  $R_i$  in  $\text{K}\Omega$ .

- a) 380.5      b) 175.8      c) 292.7      d) 339.6      e) 238.7

4. Find the current gain  $i_o/i_i$ .

- a) -41.2      b) -31.0      c) -35.4      d) -38.1      e) -33.0

**In the circuit of Figure 2, assume  $R_E = 0.5\text{K}$ .**

5. Find the voltage gain  $v_o/v_i$ .

- a) 0.900      b) 0.928      c) 0.952      d) 0.825      e) 0.943

6. Find  $R_{ib2}$  at the base of  $Q_2$  (in  $\text{K}\Omega$ .)

- a) 203.2      b) 253.9      c) 152.4      d) 101.6      e) 50.8

7. Find  $R_{ib1}$  at the base of  $Q_1$  (in  $\text{M}\Omega$ .)

- a) 16.39      b) 11.36      c) 21.74      d) 27.03      e) 6.17

8. Find the current gain  $i_o/i_i$ .

- a) 396.6      b) 220.1      c) 152.3      d) 94.3      e) 116.5

**In the circuit of Figure 3, assume  $V_{CC} = 12\text{V}$ .**

9. Find the voltage gain  $v_o/v_i$ .

- a) 95.2      b) 75.2      c) 35.3      d) 55.2      e) 115.2

10. Find the input resistance  $v_i/i_i$  in Ohms.

- a) 8.5      b) 27.3      c) 13.0      d) 17.6      e) 10.3

**In the circuit of Figure 4, assume  $I = 2.5\text{mA}$ .**

11. Find the differential voltage gain  $(v_{c1} - v_{c2})/v_d$ , when  $v_{B1} = +v_d/2$  and  $v_{B2} = -v_d/2$ .

- a) -9.9      b) -11.3      c) -12.4      d) -13.2      e) -11.9

12. Find the differential input resistance  $R_{id}$  in  $K\Omega$ .

- a) 26.5      b) 30.3      c) 22.7      d) 25.3      e) 24.2

13. Find the input bias current in microAmps when  $\beta_1=80$  and  $\beta_2=120$ .

- a) 12.88      b) 5.15      c) 10.31      d) 20.61      e) 8.24

14. Find the input offset current in microAmps when  $\beta_1=80$  and  $\beta_2=120$ .

- a) 4.08      b) 8.16      c) 5.10      d) 2.04      e) 3.26

15. A differential amplifier has a CMRR of 70 dB. The output voltage is 100 mV when the inputs are  $v_1 = 21.5$  mV and  $v_2 = 20$  mV. Find the differential gain of this amplifier.

- a) 66.4      b) 53.5      c) 58.6      d) 46.4      e) 63.9

In the circuit of Figure 5, the MOSFETs have  $V_t = 2.2V$  and  $\frac{1}{2} k'_n(W/L) = 1$  mA/V<sup>2</sup>. Neglect body effect and channel length modulation.

16. Find  $I_D$  in mA.

- a) 0.090      b) 0.0563      c) 0.116      d) 0.0730      e) 0.160

17. Find  $g_m$  for the MOSFETs in mA/V.

- a) 0.600      b) 0.540      c) 0.474      d) 0.800      e) 0.681

18. Find  $v_{o1}/v_s$ .

- a) -5.12      b) -5.68      c) -7.58      d) -4.49      e) -6.45

19. Find  $v_{o2}/v_s$ .

- a) 18.4      b) 29.3      c) 22.7      d) 40.4      e) 14.2

20. Find  $r_o$  in  $K\Omega$  for the MOSFETs given that channel length modulation for AC signals is not negligible and is modeled by  $\lambda = 0.1$  V<sup>-1</sup>.

- a) 62.5      b) 177.7      c) 137.0      d) 111.1      e) 86.2

21. Find  $R_o$  in  $K\Omega$ , given that channel length modulation for AC signals is not negligible and is modeled by  $\lambda = 0.1$  V<sup>-1</sup>.

- a) 16.9      b) 17.5      c) 16.2      d) 15.2      e) 18.0

