

American University of Beirut
 Department of Electrical and Computer Engineering
EECE 311 – Electronic Circuits
Spring 2008
Midterm – April 11, 2008
Open Book – 90 minutes

NAME: _____ ID Number: _____

Problem 1 [60 points]

Mark the answers for questions 1 to 15 below on the Scantron (computer) sheet.

Consider the circuit shown in Figure 1. Assume $V_{DD} = 2.5$ V. The MOSFET parameters are $k' = 200 \mu\text{A}/\text{V}^2$, $V_t = 0.5$ V, $(W/L)_1 = 20\mu\text{m} / 0.25\mu\text{m}$, and $(W/L)_2 = 10\mu\text{m} / 0.25\mu\text{m}$. Assume that the DC drain current of a MOSFET in SAT is given by $I_D \approx \frac{1}{2}k' \left(\frac{W}{L}\right)V_{ov}^2$.

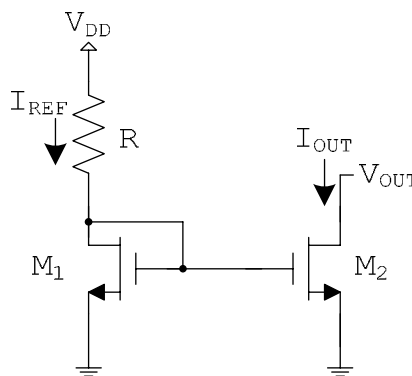


Figure 1

1. [4 points] Find the resistance R (in $\text{K}\Omega$) in the circuit if the current I_{REF} is $100 \mu\text{A}$.
 a) 6.02 **b) 18.88** c) 12.42 d) 9.21 e) 7.29
2. [4 points] Find the drain current of M_2 , I_{OUT} (in μA).
 a) 75 b) 100 c) 125 d) 150 **e) 50**
3. [4 points] Find the largest resistance (in $\text{K}\Omega$) that can be connected between the drain of M_2 and V_{DD} to maintain saturation region operation for M_2 .
 a) 15.38 b) 23.42 **c) 47.76** d) 31.51 e) 18.59
4. [4 points] Find the variation in I_{OUT} (in μA) when V_{OUT} increases from 1.5 to 2.5 V. At $L = 0.25 \mu\text{m}$, V_A is 10 V.
a) 5 b) 7.5 c) 10 d) 12.5 e) 15

5. [4 points] Repeat question 4, assuming that $(W/L)_2$ is changed from $10\mu\text{m} / 0.25\mu\text{m}$ to $40\mu\text{m} / 1\mu\text{m}$.

- a) 3.75 **b) 1.25** c) 1.88 d) 2.50 e) 3.13

6. [4 points] A P-channel MOSFET M_3 with $k' = 100 \mu\text{A}/\text{V}^2$, and $V_t = -0.6 \text{ V}$ is connected with MOSFET M_1 of question 1, as shown in Figure 2. Find $(W/L)_3$ if the current I_{REF} is $200 \mu\text{A}$ and $R = 4.5 \text{ K}\Omega$.

- a) 108.6 **b) 34.2** c) 46.9 d) 68.4 e) 20.5

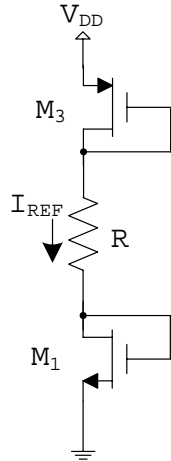


Figure 2

Consider the differential amplifier shown in Figure 3. The reference current is $I_{\text{REF}} = 240 \mu\text{A}$. Assume $V_{\text{DD}} = 2.5 \text{ V}$. The MOSFET parameters are as follows.

For NMOS:

$$k'_n = 200 \mu\text{A}/\text{V}^2, V_{\text{tn}} = 0.5 \text{ V}$$

$$(W/L)_1 = 20\mu\text{m} / 0.25\mu\text{m}$$

$$(W/L)_2 = 10\mu\text{m} / 0.25\mu\text{m}$$

$$(W/L)_4 = 10\mu\text{m} / 0.25\mu\text{m}$$

$$(W/L)_5 = 10\mu\text{m} / 0.25\mu\text{m}$$

For PMOS:

$$k'_p = 100 \mu\text{A}/\text{V}^2, V_{\text{tp}} = -0.6 \text{ V}$$

$$(W/L)_3 = 40\mu\text{m} / 0.25\mu\text{m}$$

$$(W/L)_6 = 10\mu\text{m} / 0.25\mu\text{m}$$

$$(W/L)_7 = 10\mu\text{m} / 0.25\mu\text{m}$$

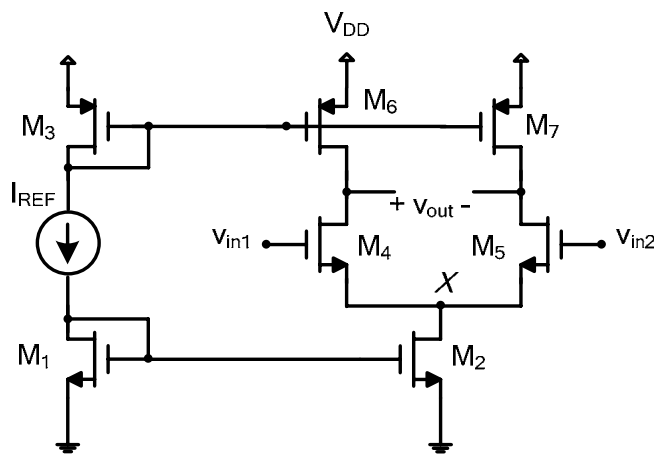


Figure 3

7. [4 points] Find the DC voltage (in mV) at node X when the two inputs are at 0.9 V.

- a) 258.6 b) 250.0 c) 277.5 d) 267.7 e) 288.2

8. [4 points] Find the total power dissipation (in mW) in the circuit.

- a) 0.90 b) 1.05 c) 1.20 d) 1.35 e) 0.75

Assume in the following that $V_{AN} = 10$ V, and $|V_{AP}| = 8$ V.

9. [4 points] Find the small-signal differential gain $v_{out}/(v_{in1} - v_{in2})$.

- a) -79.5 b) -72.6 c) -67.2 d) -62.9 e) -59.3

10. [4 points] Find the small-signal differential gain $v_{out}/(v_{in1} - v_{in2})$ when a 1000 K Ω resistor is connected across the v_{out} terminals.

- a) -53.9 b) -56.6 c) -67.5 d) -63.2 e) -59.6

11. [4 points] Find the small-signal common-mode gain when the output is taken *single-endedly* (at the drain of M_4 or M_5). In this case, $v_1 = v_2 = v_{icm}$.

- a) -2.8 b) -0.008 c) -0.08 d) -0.8 e) -1.8

12. [4 points] Find the small-signal common-mode gain when the output is taken differentially. In this case, $v_1 = v_2 = v_{icm}$.

- a) 0 b) 0.08 c) -0.08 d) -0.008 e) 0.008

Assume in the following two questions that when the input is common-mode, the DC voltage at the drains of M_4 and M_5 is 1.5 V.

13. [4 points] Find the maximum common-mode input voltage (in V) that maintains saturation-region operation for all MOSFETs in the circuit.

- a) 2.4 b) 2.0 c) 2.1 d) 2.2 e) 2.3

14. [4 points] Find the minimum common-mode input voltage (in V) that maintains saturation-region operation for all MOSFETs in the circuit.

- a) 0.86 b) 0.80 c) 0.82 d) 0.84 e) 0.77

15. [4 points] The two inputs are $v_{in1}(t) = 4.5 \sin(\omega t)$ mV and $v_{in2}(t) = 4.9 \sin(\omega t)$ mV. If the differential gain is 62 dB, and the CMRR is 50 dB, find the amplitude of the output voltage (in V).

- a) 0.52 b) 0.33 c) 0.37 d) 0.41 e) 0.47

Problem 2 [40 points]

Solve this problem on the answer booklet.

The common-emitter amplifier shown in Figure 4 is biased using $I_{REF} = 140 \mu\text{A}$, and has $V_{AN} = 10 \text{ V}$, $|V_{AP}| = 5 \text{ V}$, and large β . Q_2 and Q_3 are matched. In DC analysis, assume that the collector current in ACTIVE is given by $I_C \approx I_S e^{\frac{V_{BE}}{V_T}}$, where $V_T = 25 \text{ mV}$.

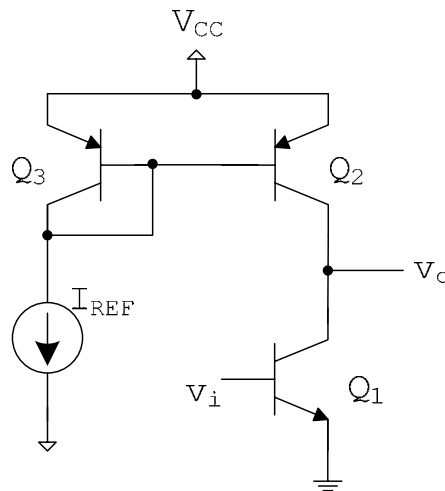


Figure 4

a) [5 points] Find the output resistance of the amplifier. Assume all transistors are an *internal part* of the amplifier.

The output resistance is $r_{o(Q1)} // r_{o(Q2)}$

Since Q_2 and Q_3 are matched, and β is very large: $I_{C1} = I_{C2} = I_{REF} = 140 \mu\text{A}$.

$$r_{o(Q1)} = V_{AN} / I_{C1} = 10 / 0.14 = 71.43 \text{ K}\Omega$$

$$r_{o(Q2)} = |V_{AP}| / I_{C1} = 5 / 0.14 = 35.71 \text{ K}\Omega$$

$$R_{out} = r_{o(Q1)} // r_{o(Q2)} = 71.43 // 35.71 = 23.81 \text{ K}\Omega$$

b) [5 points] Find the open-circuit voltage gain v_o/v_i .

The open circuit voltage gain v_o/v_i is $-g_{m1} R_{out}$

$$g_{m1} = I_{C1} / V_T = 0.14 / 25 = 5.6 \text{ mA/V}$$

$$v_o/v_i = -g_{m1} R_{out} = -5.6 \times 23.81 = -133.34 \text{ V/V}$$

Assume in the following that a signal source is connected to the input of the amplifier. It is a voltage source v_{sig} with a source resistance $R_{sig} = 25 \text{ K}\Omega$. Assume also that a $10 \text{ K}\Omega$ load resistor is connected from the output to ground. The signal source and the load do not affect the DC bias.

c) [4 points] Find the input resistance v_i/i_i of the amplifier if $\beta = 200$.

$$\text{The input resistance } v_i/i_i \text{ is } r_{\pi} = V_T / I_B = \beta V_T / I_C = 200 \times 25 / 0.14 = 35.71 \text{ K}\Omega$$

d) [4 points] Find the voltage gain v_o/v_{sig} .

The voltage gain is $-g_{m1} R'_L \times (\text{voltage divider ratio at input})$.

$$R'_L = R_{out} // R_L = 23.81 // 10 = 7.04 \text{ K}\Omega$$

The voltage divider ratio at the input is $r_\pi / (r_\pi + R_{sig}) = 35.71 / (35.71 + 25) = 0.5882$

The voltage gain $v_o/v_{sig} = -5.6 \times 7.04 \times 0.5882 = -23.19 \text{ V/V}$

Assume now that for Q_1 , $C_\pi = 25 \text{ fF}$, $C_\mu = 10 \text{ fF}$, and that a load capacitance $C_L = 40 \text{ fF}$ is connected from the output to ground. Neglect all other capacitances.

e) [5 points] Using Miller's theorem, and assuming that the input circuit determines the upper 3-dB frequency f_H , find the value of f_H .

The Miller constant K is $v_o/v_b = -g_{m1} R'_L = -5.6 \times 7.04 = -39.42$

We apply Miller's theorem to obtain the input capacitance:

The input capacitance is $C_{in} = C_\pi + (1 - K)C_\mu = 25 + (1 + 39.42) \times 10 = 429.2 \text{ fF}$

The resistance seen by this input capacitance is $r_\pi // R_{sig} = 35.71 // 25 = 14.71 \text{ K}\Omega$


The 3-dB frequency due to the input circuit is

$$f_H = 1/(2\pi C_{in} (r_\pi // R_{sig})) = 1/(2\pi \times 429.2 \text{ f} \times 14.71 \text{ K}) = 25.21 \text{ MHz}$$

f) [5 points] Based on the results of (d) and (e), show and *label* the Bode plot for the magnitude of the voltage gain (v_o/v_{sig}).

The low-frequency gain is -23.19 V/V , which corresponds to 27.3 dB

The 3-dB frequency is 25.21 MHz

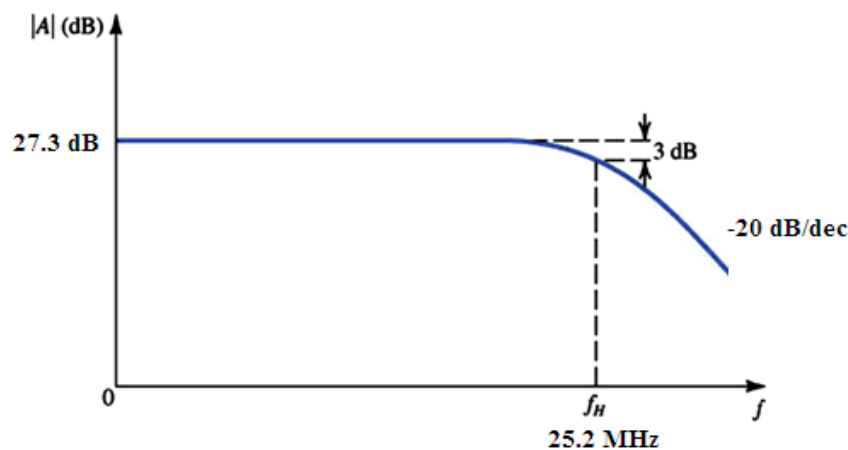

g) [12 points] Using the open-circuit time constants methods, find the resistance seen by each capacitor [3 points each], and estimate the value of f_H [3 points].

$$R(\text{seen by } C_\pi) = r_\pi // R_{sig} = 14.71 \text{ K}\Omega$$

$$R(\text{seen by } C_L) = R'_L = 7.04 \text{ K}\Omega$$

$$\begin{aligned} R(\text{seen by } C_\mu) &= (r_\pi // R_{sig}) + R'_L + g_{m1} R'_L (r_\pi // R_{sig}) && \text{frequently-used resistance calc.} \\ &= 14.71 + 7.04 + 5.6 \times 14.71 \times 7.04 \\ &= 601.7 \text{ K}\Omega \end{aligned}$$

$$f_H = 1/(2\pi(25\text{f} \times 14.71\text{K} + 40\text{f} \times 7.04\text{K} + 10\text{f} \times 601.7\text{K})) = 23.87 \text{ MHz}$$