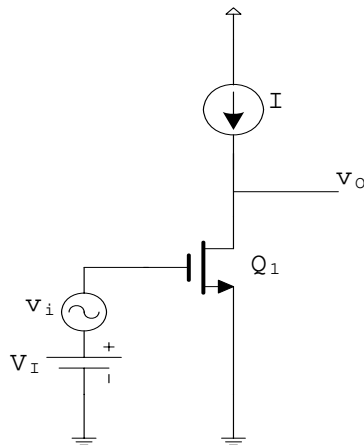


**American University of Beirut**  
 Department of Electrical and Computer Engineering  
**EECE 311 – Electronics II**  
 Fall 2005 – 2006 (Section 2)  
**Quiz 1 – Solution**


**Problem 1:**



a)  $I = \frac{1}{2} k'_n (W/L) (V_{GS} - V_{tn})^2$   
 $\Rightarrow 40 \mu = 0.5 (0.2m)(5)(V_I - 0.5)^2$   
 $\Rightarrow V_I = 0.5 + \sqrt{40\mu/0.5m} = 0.783 \text{ V}$

b)  $v_O = v_{DS} \Rightarrow v_{Omin} = v_{DSmin} = v_{GS} - V_{tn}$   
 Assuming  $v_{GS} = V_{GS}$  (DC value)  $\Rightarrow v_{Omin} = 0.783 - 0.5 = 0.283 \text{ V}$

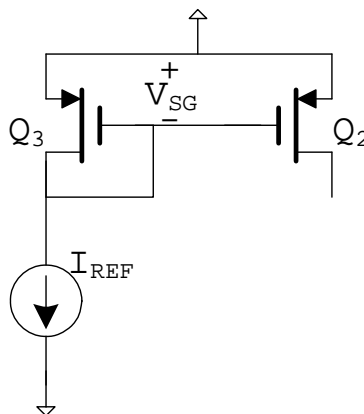c)  $g_m = I_D / (V_{OV}/2) = 40\mu / (0.283/2) = 0.283 \text{ mA/V}$   
 $r_o = V_A / I_D = (1/0.1) / 40\mu = 250 \text{ K}$   
 $\text{gain} = v_o / v_i = -g_m (r_o // R_o \text{ of current source}) = -0.283(100 // 250) = -20.2 \text{ V/V}$



d)  $I_D(Q2) = \frac{1}{2} k'_p (W/L) (V_{OV2})^2$   
 This current is equal to  $40\mu$   
 $\Rightarrow 40\mu = 0.5(0.08m)(W/L)(0.2)^2 \Rightarrow (W/L) = 25 \text{ for } Q_2$   
 $(W/L) = 25 \text{ for } Q_3$ , since  $Q_2$  and  $Q_3$  are matched.


e)  $V_{SG} = |V_{tp}| + |V_{OV2}| = 0.54 + 0.2 = 0.74 \text{ V}$

f) Output resistance is  $r_{o2} = V_{AP} / I_{D2} = (1/0.12) / 40\mu = 208.33 \text{ K}$

g) For Q2:  $|V_{DS}| \geq |V_{GS}| - |V_{tp}| \Rightarrow V_{DD} - V_O \geq 0.2 \text{ V} \Rightarrow V_{Omax} = V_{DD} - 0.2 \text{ V}$
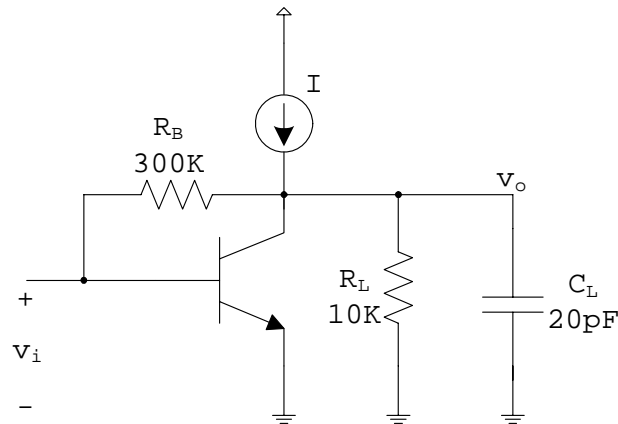
### Problem 2:


In this problem, there is an implicit assumption that the signal source (not shown) has a large source resistance, and that the source does not affect the DC bias.



a) DC analysis: current in 300K resistor =  $I_B$   
 KCL at collector:  $0.5 \text{ mA} = I_B + I_C + V_O/10\text{K}$   
 But  $V_O = 300\text{K} \times I_B + V_{BE} = 300\text{K} \times I_B + 0.7 \text{ V}$   
 $\Rightarrow 0.5 \text{ mA} = I_B + \beta I_B + (300\text{K} \times I_B + 0.7 \text{ V})/10\text{K}$   
 $\Rightarrow 0.5 \text{ mA} - 0.07 \text{ mA} = 91 I_B \Rightarrow I_B = 4.725 \text{ uA}$   
 $I_C = 60 I_B = 0.2835 \text{ mA}$   
 $V_O = 300\text{K} \times 4.725 \text{ uA} + 0.7 \text{ V} = 2.118 \text{ V}$

b) The Miller constant is the gain from base to collector without  $R_B$ , and is given by  $-g_m R'_L$  with  $R'_L = r_o(\text{BJT}) // R_o(\text{current source}) // R_L$   
 $r_o(\text{BJT}) = V_A/I_C = 80/0.2835\text{m} = 282.2 \text{ K}$   
 $R'_L = 282.2 \text{ K} // 100 \text{ K} // 10\text{K} = 8.807 \text{ K}$   
 $g_m = I_C/V_T = 0.2835\text{m}/25\text{m} = 11.34 \text{ mA/V}$   
 Miller's  $K = -g_m R'_L = -11.34 \times 8.807 = -99.87$   
 Equivalent resistance from base to ground due to  $R_B$ :  $R_1 = R_B/(1 - K) = 300\text{K}/(1+99.87) = 2.974 \text{ K}$   
 The input resistance is  $R_{in} = r_\pi // R_1$   
 $r_\pi = V_T/I_B = 25\text{m}/4.725\text{u} = 5.291 \text{ K}$   
 $R_{in} = 5.291 // 2.974 = 1.904 \text{ K}$

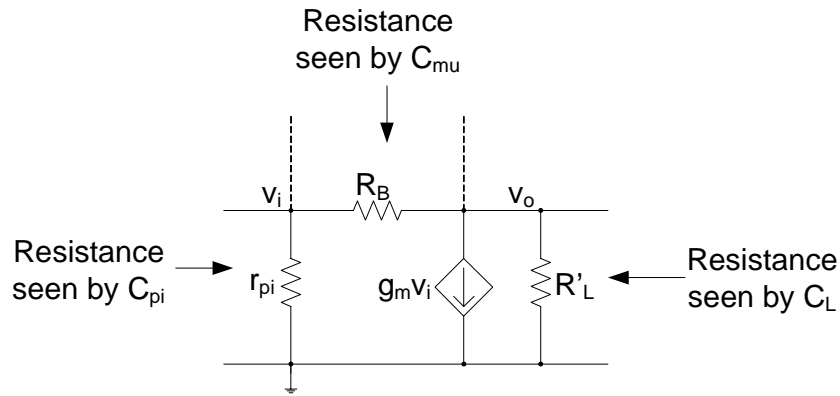c) The resistance seen by  $C_\pi$  is  $R_{in}$  (we can use the approximation from part (b)) =  $1.904 \text{ K}$ . The more accurate estimate is obtained as follows:  
 $i_{RB} = (v_i - v_o)/R_B = (1 - \text{gain})v_i/R_B \Rightarrow v_i/i_{RB} = R_B/(1 - \text{gain}) = 300\text{K}/(1 + 97) = 3.061 \text{ K}$  [note: the value of the voltage gain is found in part (d)]  
 Resistance seen by  $C_\pi$  is equal to:  $r_\pi // (v_i/i_{RB}) = 5.291 \text{ K} // 3.061 \text{ K} = 1.939 \text{ K}$



The resistance seen by  $C_L$  is equal to:

$R'_L // (\text{resistance due to controlled source}) // (R_B + r_\pi)$ :  
 $v_\pi = v_i = v_x r_\pi / (r_\pi + R_B) = v_x \times 5.291 / (5.291 + 300) = v_x / 57.7$   
 The controlled current source is therefore equivalent to a resistance equal to  $57.7 / g_m = 5.088 \text{ K}$

The resistance seen by  $C_L$  is therefore:  $8.807 // 5.088 // 305.29 = 3.191 \text{ K}$

The resistance seen by  $C_\mu$  is equal to:  $R_B // (R'_L + r_\pi + g_m \times r_\pi \times R'_L) = 300 \text{ K} // (8.807 \text{ K} + 5.291 \text{ K} + 11.34 \times 8.807 \times 5.291 \text{ K}) = 193.2 \text{ K}$ .


$\tau_H = 1.939 \text{ K} \times 1 \text{ pF} + 3.191 \text{ K} \times 20 \text{ pF} + 193.2 \text{ K} \times 1 \text{ pF} = 258.96 \text{ nsec}$

$f_H = 1 / (2\pi \tau_H) = 614.6 \text{ KHz}$


d) The low-frequency voltage gain is determined *without* using Miller's theorem. The current in  $R_B$  is  $(v_i - v_o) / R_B$ . This current is equal to  $g_m v_i + v_o / R'_L$ . Therefore:

$(1/R_B - g_m) v_i = v_o (1/R'_L + 1/R_B) \Rightarrow$  The voltage gain is  
 $v_o / v_i = (1/R_B - g_m) / (1/R'_L + 1/R_B) = (1 - g_m R_B) / (R_B / R'_L + 1)$   
 $= (1 - 11.34 \times 300) / (300 / 8.807 + 1) = -97 \text{ V/V}$  or  $39.74 \text{ dB}$

e) Asymptotic Bode Plot

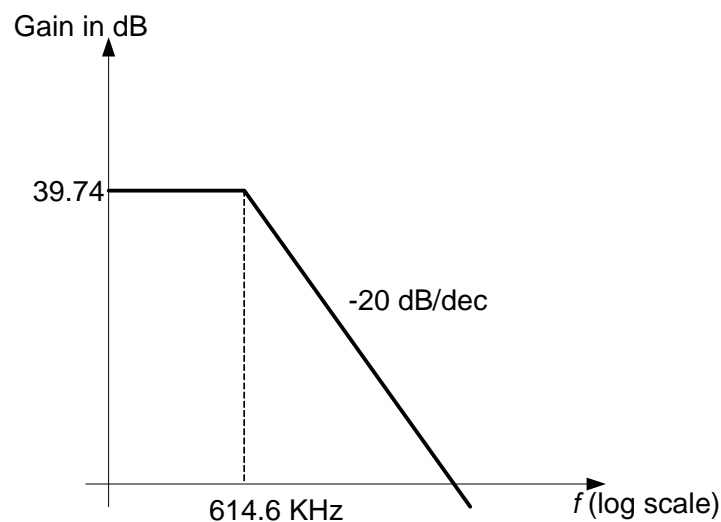

### Problem 3

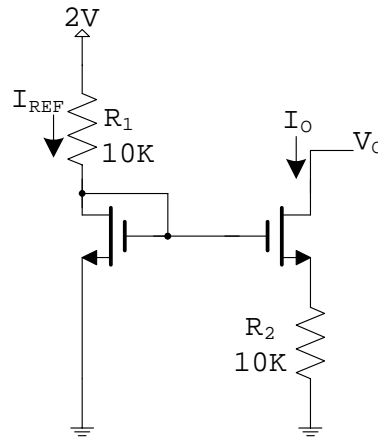

a)  $I_{REF} = (2 - V_{GS1})/10K = \frac{1}{2} k'_n (W/L) (V_{GS1} - V_{tn})^2 = (0.5)(0.2m)(10)(V_{GS1} - 0.4)^2$ .  
Solving the quadratic equation we get:  $V_{GS} = 0.753$  V (the other root is negative).  
 $I_{REF}$  is therefore  $(2 - 0.753)/10K = 0.1247$  mA


b)  $V_{GS2} = V_{GS1} - I_O \times R_2$  and  
 $I_O = \frac{1}{2} k'_n (W/L) (V_{GS2} - V_{tn})^2 = \frac{1}{2} k'_n (W/L) (V_{GS1} - I_O \times R_2 - V_{tn})^2$   
Therefore  $I_O = (0.5)(0.2m)(10)(0.753 - I_O \times 10K - 0.4)^2$   
 $\Rightarrow I_O = 20.86$  uA  
The value of  $V_{GS2}$  is  $0.753 - 20.86u \times 10K = 0.5444$  V

c) The minimum output voltage corresponds to  $V_{DS2} = V_{GS2} - V_{tn} \Rightarrow V_O - I_O R_2 = V_{GS2} - V_{tn} \Rightarrow V_{Omin} = 20.86u \times 10K + 0.5444 - 0.4 = 0.353$  V

d) The output resistance is given by  $r_{o2} + R_2 + g_{m2} r_{o2} R_2$   
 $r_{o2} = V_A/I_O = (1/0.08)/20.86u = 599.23$  K  
 $g_{m2} = I_O/(V_{OV}/2) = 20.86u/((0.5444-0.4)/2) = 0.289$  mA/V  
 $R_O$  is therefore equal to:  $10K + 599.23K + 599.23K \times 0.289m \times 10K = 2340.5$  K
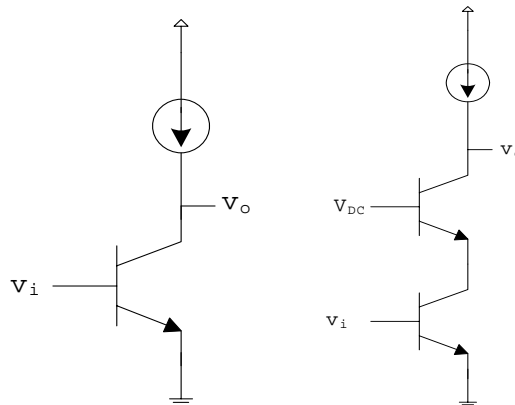
### Problem 4

*In this problem, there is an implicit assumption that the signal source (not shown) has a large source resistance.*



a) Using Miller's theorem, the time constant at the input of the circuit is given by

$\tau_H = r_\pi (C_\pi + C_\mu (1 + g_m r_o))$  since the only “load” is the output resistance of the BJT itself.

$$\tau_H = r_\pi (C_\pi + C_\mu (1 + g_m r_o)) = r_\pi C_\pi + r_\pi C_\mu + r_\pi C_\mu g_m r_o = r_\pi C_\pi + r_\pi C_\mu + \beta r_o C_\mu$$

The third term is much larger than the first two, and therefore  $\tau_H$  is approximately  $\beta r_o C_\mu$ .

$$f_H = 1/(2\pi \tau_H) = 1/(2\pi \beta r_o C_\mu)$$


b) The current source output resistance is approximately  $r_o$ . The output resistance of the amplifier becomes  $R_o \approx r_o/r_o = r_o/2$ . The open-circuit voltage gain becomes  $-g_m r_o/2 = -A_0/2$ . The 3-dB frequency becomes  $1/(2\pi \tau_H) = 1/(2\pi \beta(r_o/2)C_\mu) = 2 f_H$

c) The current source output resistance is approximately  $\beta r_o$ . The output resistance of the amplifier becomes  $R_o \approx \beta r_o/r_o \approx r_o$ . The open-circuit voltage gain becomes  $-g_m r_o = -A_0$ . The 3-dB frequency becomes  $1/(2\pi \tau_H) = 1/(2\pi \beta r_o C_\mu) = f_H$

d) For an unloaded cascode amplifier, the output resistance of the *unloaded* amplifier is given by  $\beta r_o$ . The output resistance of the amplifier becomes  $R_o \approx \beta r_o/r_o \approx r_o$ . The open-circuit voltage gain becomes (see Fig. 6.41 in textbook)  $-\beta A_0 r_o/(r_o + \beta r_o) \approx -A_0$ . The 3-dB frequency becomes  $1/(2\pi \tau_H) \approx 1/(2\pi r_o C_\mu) = \beta f_H$  (see Fig. 6.42 in textbook)

e) The output resistance of the amplifier becomes  $R_o \approx \beta r_o/\beta r_o = r_o/2$ . The open-circuit voltage gain becomes  $-\beta A_0 \beta r_o/(\beta r_o + \beta r_o) = -\beta A_0/2$ . The 3-dB frequency becomes  $1/(2\pi \tau_H) \approx 1/(2\pi (\beta r_o/2)C_\mu) = 2f_H$

### Problem 5

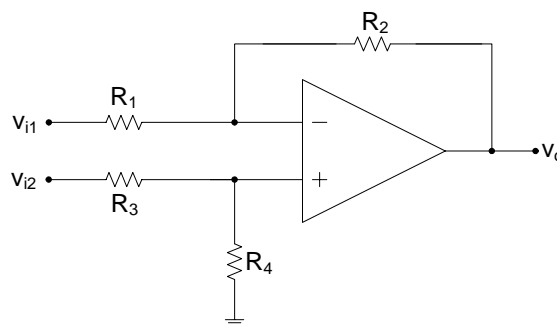

For the difference amplifier, the output voltage is given by:

$$v_o = \frac{-R_2}{R_1} v_{i1} + \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1}\right) v_{i2}$$

$$\Rightarrow v_o = -4.7v_{i1} + 4.674v_{i2} = A_{v1} v_{i1} + A_{v2} v_{i2} = A_d (v_{i1} - v_{i2}) + A_{cm} (v_{i1} + v_{i2})/2$$

$$\Rightarrow A_d = (A_{v1} - A_{v2})/2 = -4.687 \text{ V/V}$$

$$\text{and } A_{cm} = A_{v1} + A_{v2} = -0.026 \text{ V/V}$$

$$\Rightarrow \text{CMRR} = 20 \log|4.687/0.026| = 45.12 \text{ dB}$$