

# Experiment 5

## Diode Rectifier Circuits

### Objectives:

In this experiment you will learn how to:

- Measure and calculate all the characteristics of the half-wave rectifier.
- Measure, calculate, and compare the characteristics of full-wave rectifiers.
- Measure and calculate the characteristics of a rectifier with a capacitor filter.
- Design a rectifier circuit with a capacitor filter by proper choice of the transformer secondary voltage and the capacitance value.

### 1 Define a rectifier.

**A rectifier circuit converts an alternating input to a unidirectional output. This may be accomplished by using unidirectional devices, which allow the passage of current in one direction through the device but not in the opposite direction.**

**The most common types of unidirectional devices are semiconductor diodes.**

**Ideally, a diode behaves as a perfect switch. In the forward direction it has a zero resistance and zero offset voltage. In the reverse direction, it behaves as an open circuit.**

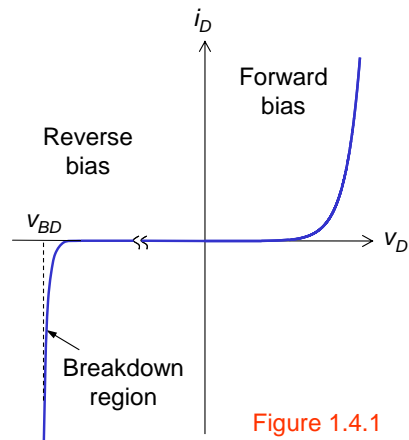


Figure 1.4.1

**The half-wave rectifier blocks the negative variations of the input; the output is approximately equal to the input when the input is positive, and is zero otherwise. In the full-wave rectifier, on the other hand, the output is approximately equal to the absolute value of the input.**

## **② What are the important characteristics of the rectifier?**

**The most important characteristics which must be specified for a rectifier circuit are:**

### **1. DC output voltage.**

*The DC output voltage  $V_{DC}$  is: (from the highest to the lowest) center-tapped full-wave rectifier, bridge full-wave rectifier (the output is always approximately equal to the absolute value of the input), and then half-wave rectifier (DC output is zero half of the time). The full wave-rectifiers have a greater DC output voltage than the half-wave rectifier.*

### **2. ripple-factor, defined as a ratio of the peak-to-peak ripple (voltage variation in the output) to the average voltage across the load.**

*The three circuits have approximately the same ripple peak-to-peak voltage. However, the bridge rectifier has a ripple peak-to-peak voltage  $V_{pp}$  slightly less due to the two diodes that are conducting at any time.*

### **3. Average and peak currents in each diode.**

*The average and peak currents in the rectifiers are the greatest in the half-wave rectifier, and they are approximately equal in both full-wave rectifiers since power used is relatively the same amount at the output resistance which is approximately  $= P = V_{2rms}^2 / R$ .*

**4. Peak inverse voltage (PIV) for each diode.**

*The descending order is by the value of the PIV is: center-tapped full-wave rectifier, half-wave rectifier where the PIV equals the peak input voltage; bridge rectifier (equals half that of the center-tap full-wave).*

**5. Percent regulation, defined as  $(V_L - V_o / V_o) \times 100$ , where  $V_0$  is the no-load voltage and  $V_L$  is the full-load voltage.**

*The percent regulation could be represented in the following descending order: the bridge full-wave rectifier, the half-wave rectifier and the center-tapped full-wave rectifier.*

**6. Transformer requirements, such as the secondary winding voltage and current ratings.**

*According to the current ratings, we have seen that the half-wave rectifier requires the greatest secondary current while the other two require only half of that value. Therefore, the magnetic polarization is strongest in the half-wave rectifier and the center-tap rectifier.*

**③ Notes:**

**It should be carefully noted that these characteristics, depend, in general, upon the type of load connected to the rectifier output, i.e., whether it is resistive, capacitive or inductive.**

**A transformer is used for stepping-down the input AC voltage. It is a device that transmits AC power from one circuit to another through magnetic coupling, often with no conductive connection. The transformation process obeys the relationships: and, where subscripts 1 and 2 refer to the primary and secondary sides, respectively.**

$$\frac{V_2}{V_1} = \frac{N_2}{N_1} \text{ and } \frac{I_2}{I_1} = \frac{N_1}{N_2}$$

**A capacitor can be connected *in parallel* at the output of the rectifier to smooth the voltage variations. An approximate**

**analysis for a full-wave rectifier with a capacitor filter gives the following:**

$$\text{PEAK-TO-PEAK RIPPLE VOLTAGE: } V_r \approx \frac{V_{2\max}}{2fR_L C}$$

$$\text{DC VOLTAGE: } V_{DC} \approx V_{2\max} - \frac{V_r}{2}$$

$$\text{DC CURRENT: } I_{DC} = \frac{V_{DC}}{R_L}.$$

**Where  $V_{2\max}$  is the peak AC input voltage (at the secondary of the transformer),  $R_L$  is the load resistance,  $C$  is the filter capacitance, and  $f$  is the frequency of the AC voltage.**

**④ Definition:** rectifier circuit converts an alternating, or bidirectional, current or voltage to a unidirectional one.

**Half-Wave Rectifier:**


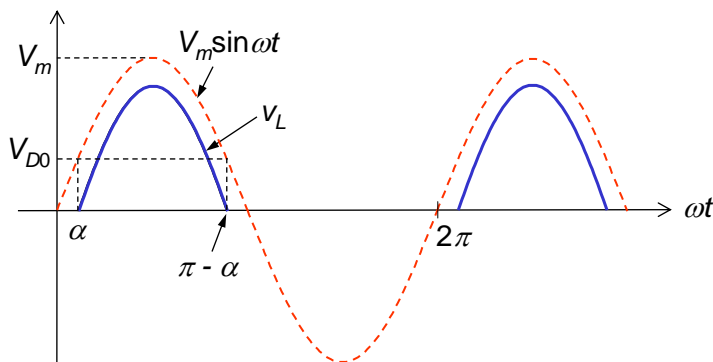



Figure 1.3.1

(b)

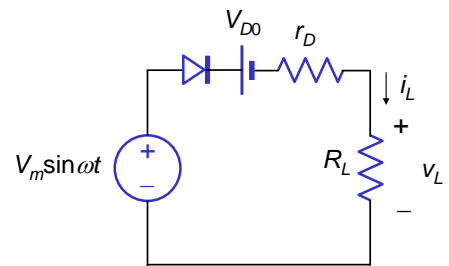


(a)

## Full- wave Rectifier:

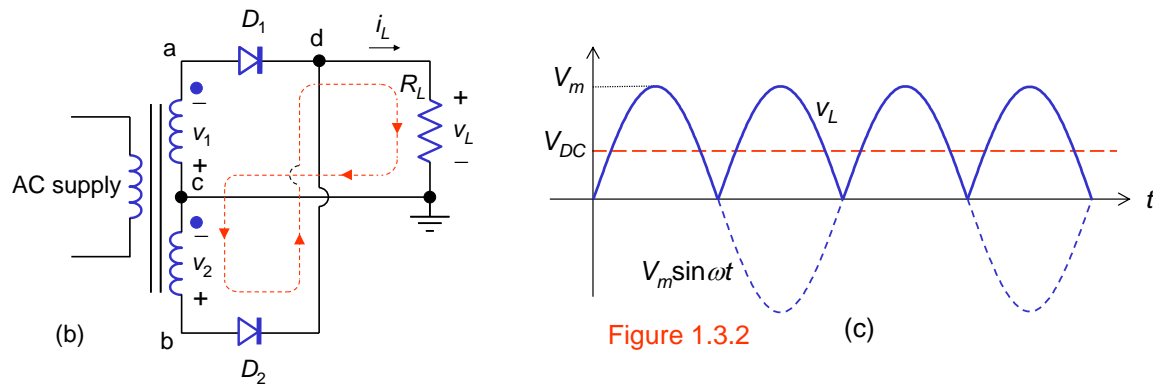

## Bridge Rectifier:

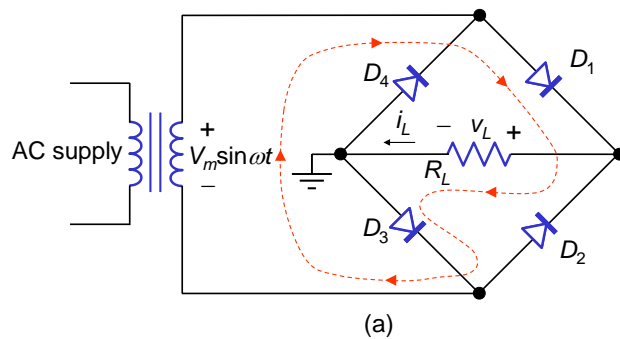

⑤ Under what conditions would each of the circuits be most advantageous?

**Full- wave rectifiers are most advantageous for applications that need power for small amounts of time.**

**Bridge- full- wave rectifiers are cheaper and easier to build than center-tapped ones.**

**Half- wave rectifier is advantageous for:**

- Applications such as charging a battery because this operation takes more time (twice the time of a full-wave rectifier).
- Simplicity and cheap cost.

### ⑥ Note:

For each of the circuits in Figs 1, 2, and 3 we adjust the load resistor to get  $I_{DC} = 50 \text{ mA}$  and we observe the output across the load on the *oscilloscope*.

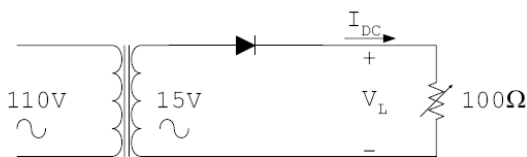


Fig. 1

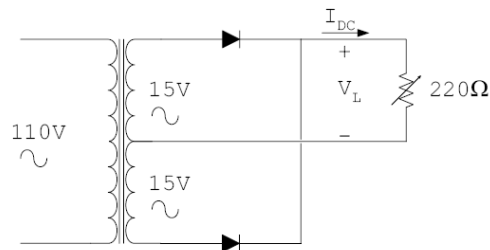


Fig. 2


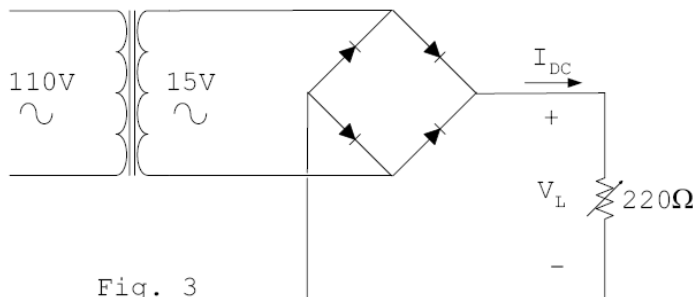


Fig. 3
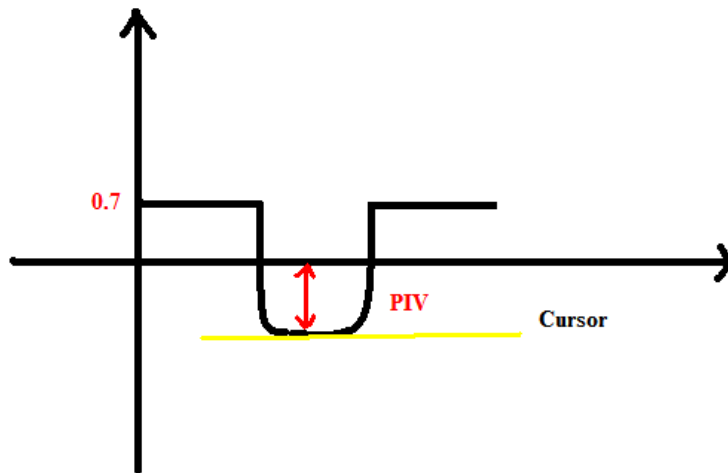
### ⑦ How do we find the different quantities mentioned in the Theory section?

- $V_{DC}$ : DC output voltage measured by the mean value on the oscilloscope screen
- $V_{ripple}$ : peak to peak value on the oscilloscope screen
- $I_{DC} = 50 \text{ mA}$  (given) determined by the digital multimeter
- $I_{peak} = V_{peak}/R$  (R found by adjusting the rheostat)
- **PIV**: peak inverse voltage. It could be calculated by the oscilloscope across the diode



- **By the oscilloscope place the horizontal cursor adjust the VOLT/DIV and SEC/DIV settings to get stable traces**

*Note:*  $V_r \ll V_{DC}$  so we need to amplify the ripple

**⑧ Does  $V_{DC}$  increase appreciably with  $C$  for all values of  $C$ ?  
Does  $V_r$  decrease appreciably with  $C$  for the values of  $C$  used in the experiment?**

**$V_{DC}$  increases exponentially as  $C$  increases.**

**$V_r$  decreases exponentially but not appreciably.**

**⑨ How does the presence of the capacitor affect the regulation of the circuit?**

**The presence of a capacitor in parallel with the load stabilizes and maintains the output voltage. Moreover, the presence of a capacitor decreases  $V_r$  and thus decreases the ripple voltage.**

## *How do we measure the DC open circuit voltage?*

- **Remove the resistor**
- **Measure the mean value across the output by the oscilloscope**

## **JOUJOU**

**For certain required ripple voltage and DC voltage/current at the load:**

**① ① *What should be the RMS voltage rating of the secondary of the transformer?***

**Using the formulas from the Theory section we have that:**

$$V_{DC} = V_{2\max} - V_r/2 \rightarrow V_{2\max} = V_{DC} + V_r/2$$

***What should be the value of the capacitor?***

$$V_r = \frac{V_{2\max}}{2fR_L C} \rightarrow C = \frac{V_{2\max}}{2fR_L V_r}$$



