

**American University of Beirut**

**ECE312 Lab**


**MyDAQ Assignment 3**

**Bilal Itani**

**20110\*\*\*\***

**Due on 23/12/2011**


## 1. Description of the hardware setup:

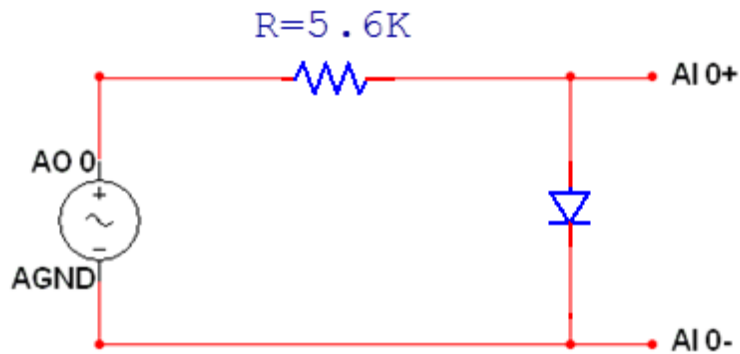

We use AO0 & AGND of the MyDAQ from which we can get the input voltage signal.

We use AI0+ & AI0- of the MyDAQ in order to plot the output voltage signal on the scope & measure the values needed.

Figure A-1: One diode clipping circuit

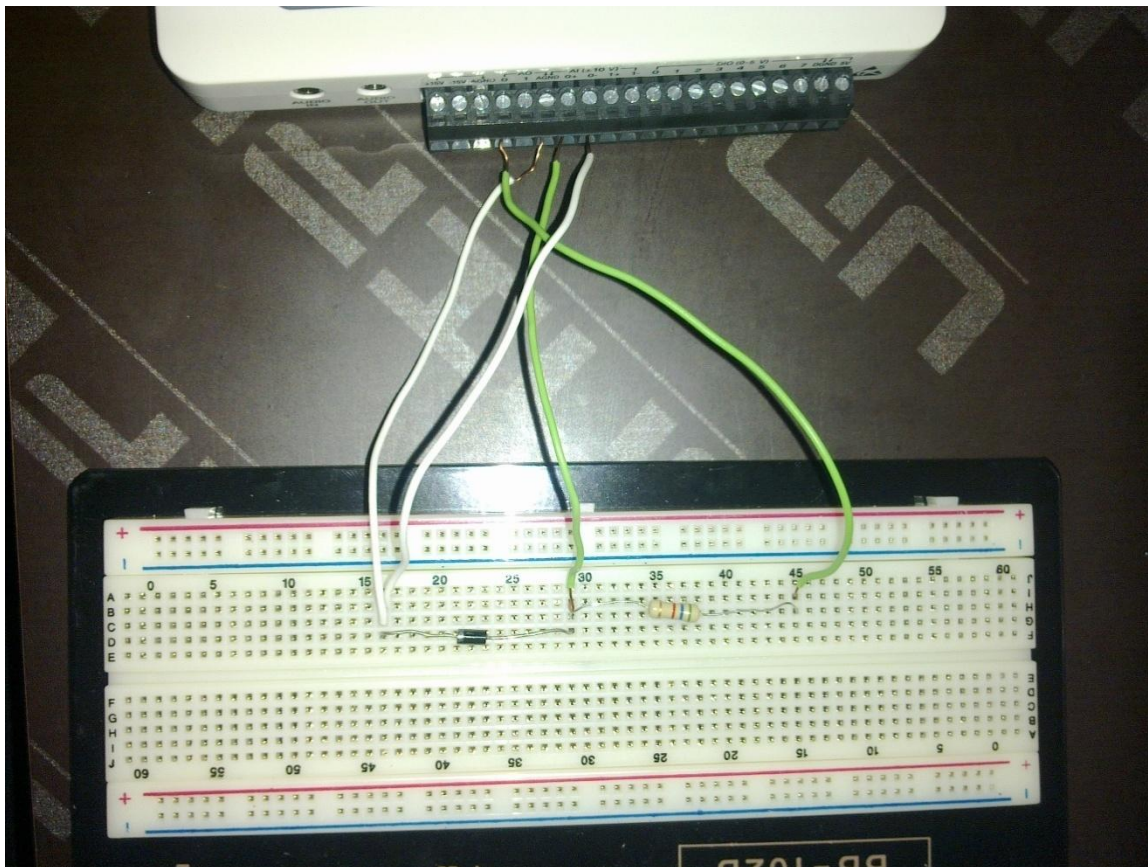


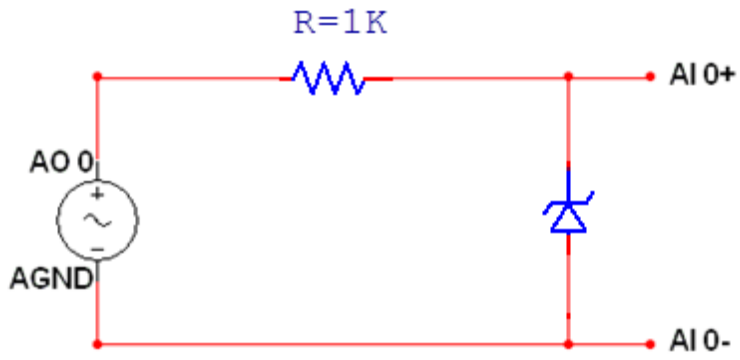


Figure A-2: One Zener clipping circuit

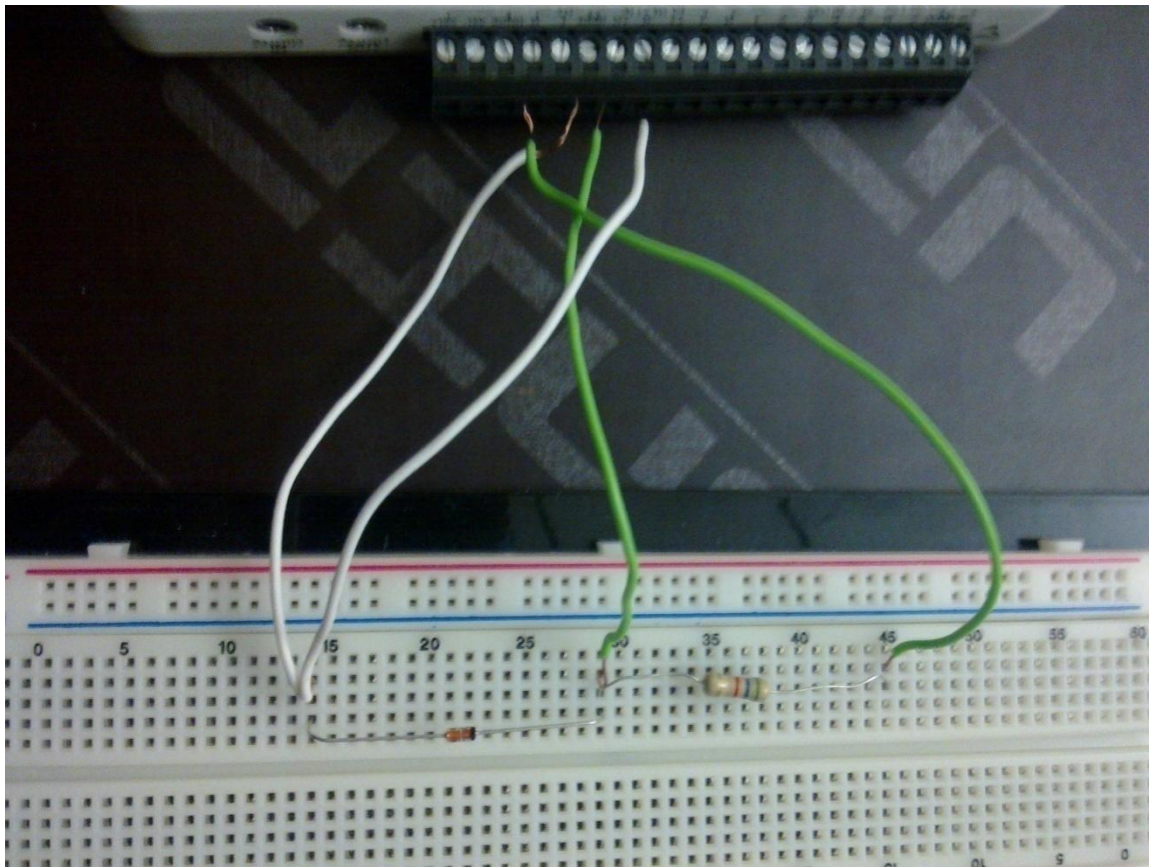


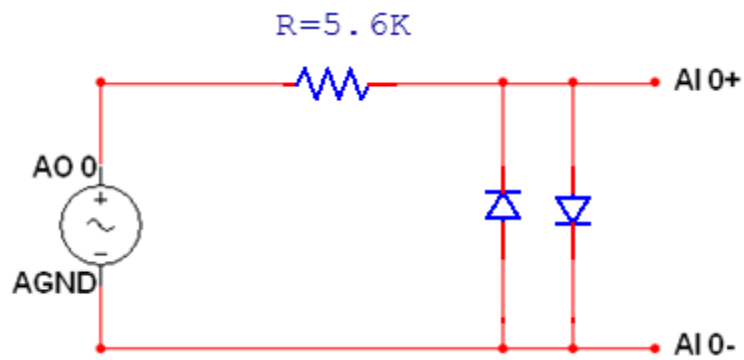


Figure A-3: Two diode clipping circuit

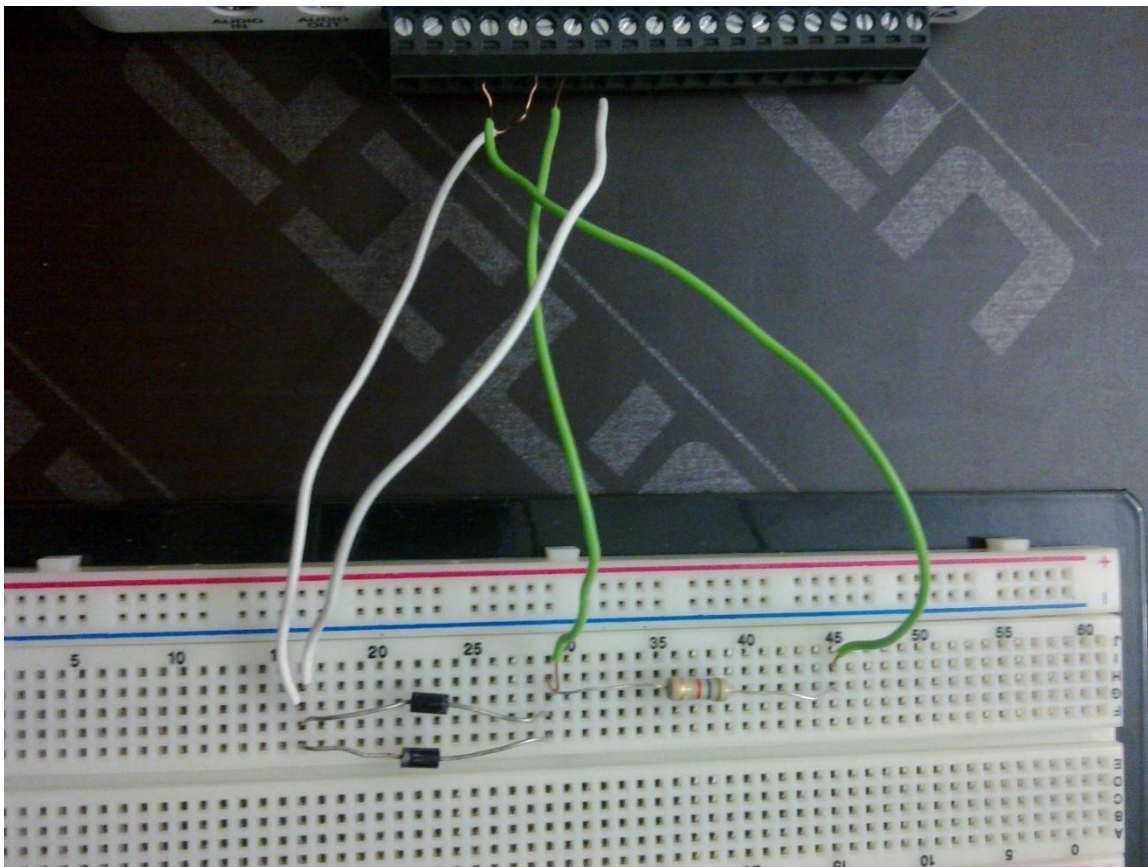


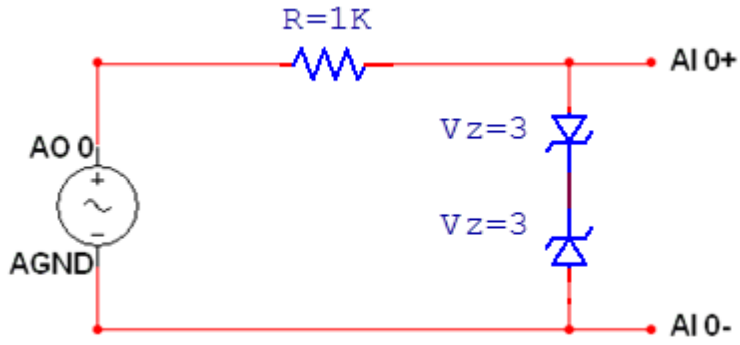


Figure A-4: Two Zener clipping circuit

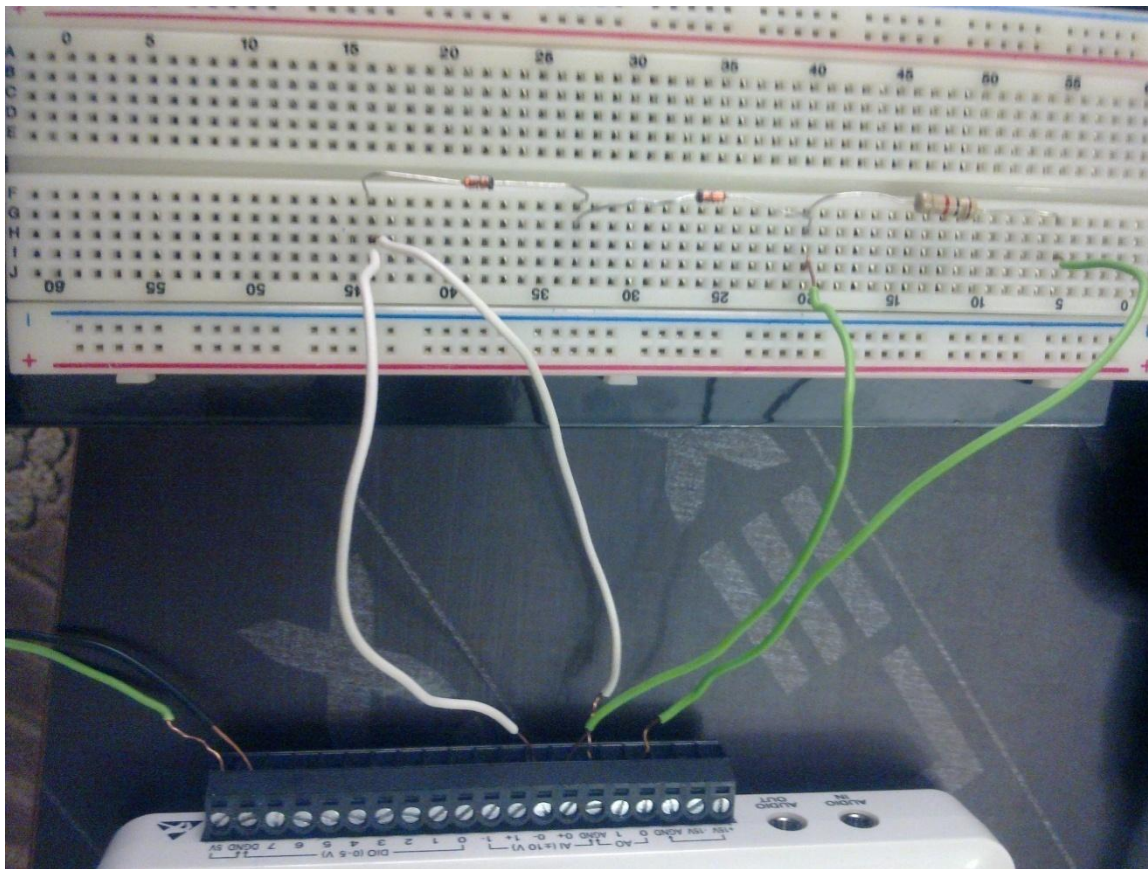

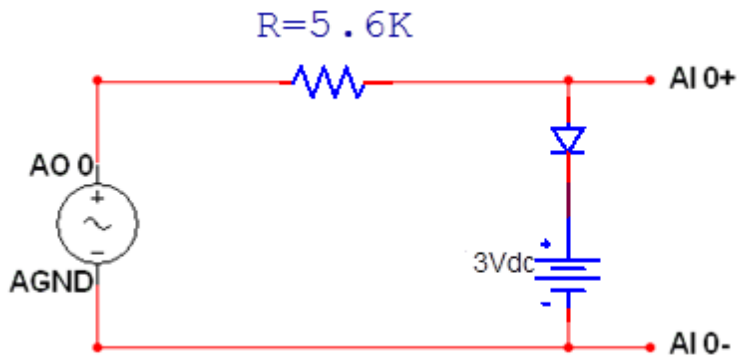


Figure A-5: Diode clipping with DC source



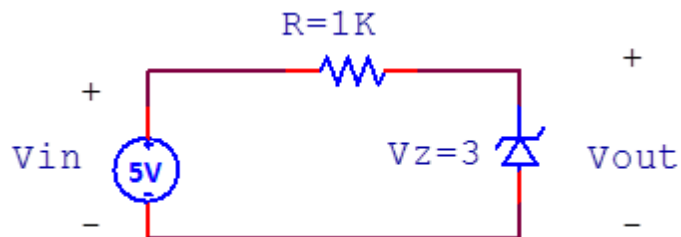


Figure B-1: Voltage regulator used as DC source


## 2. Description of the software setup:

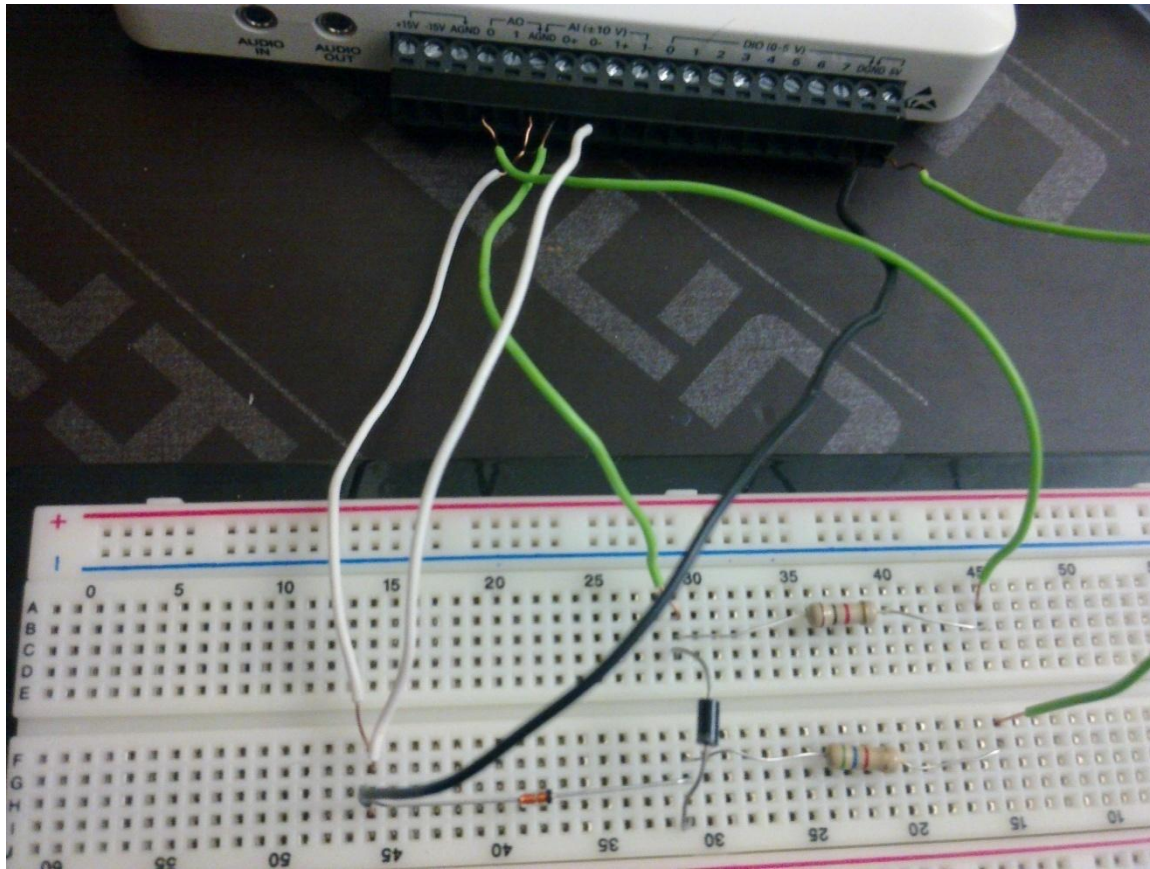

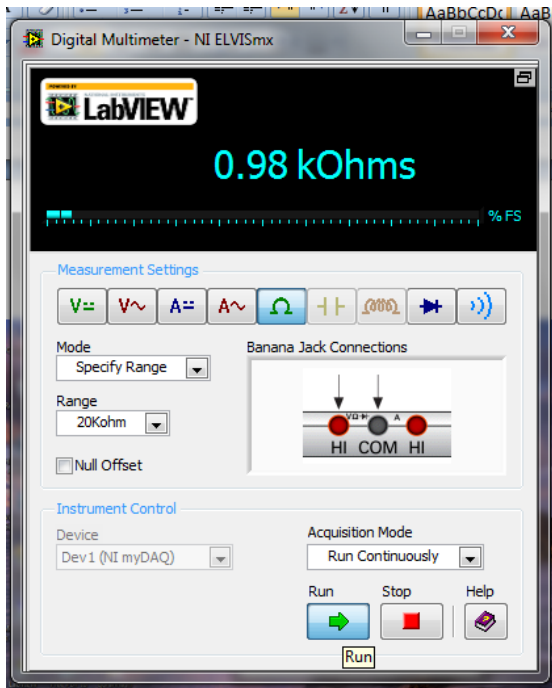
We will use the DMM to measure the resistance of the resistors that we will use in our circuits.



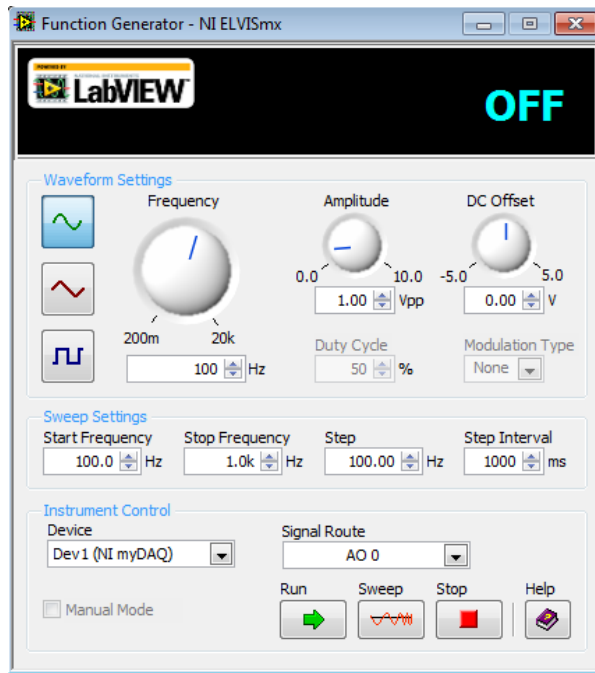We will also use the Function Generator to apply a sinusoidal input signal of specified frequency and pk-pk voltage ( $V_{pp}$ )



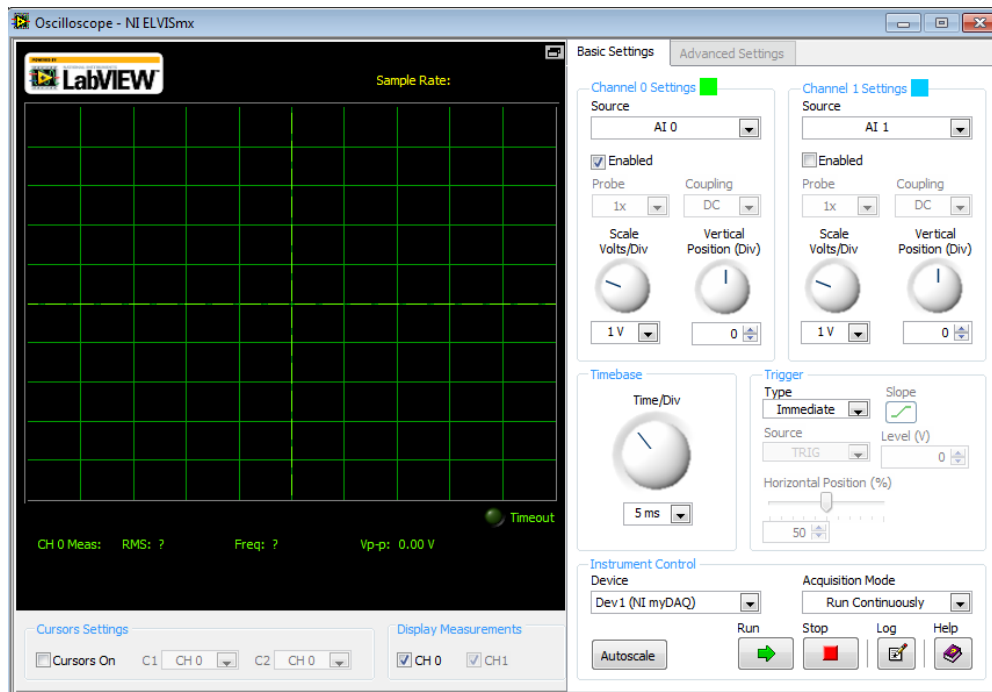
We will also use the scope, where the output signal is plotted, in order to measure the pk-pk output voltage, maximum output voltage, and minimum output voltage.






### 3. Testing:

#### Resistors Used:

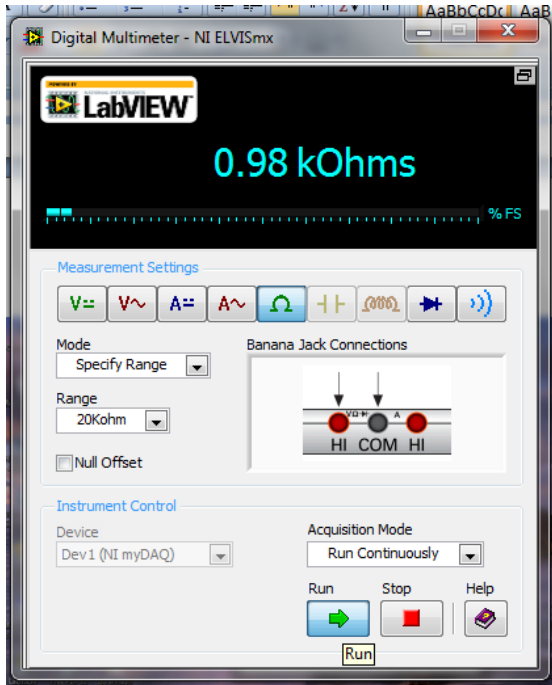


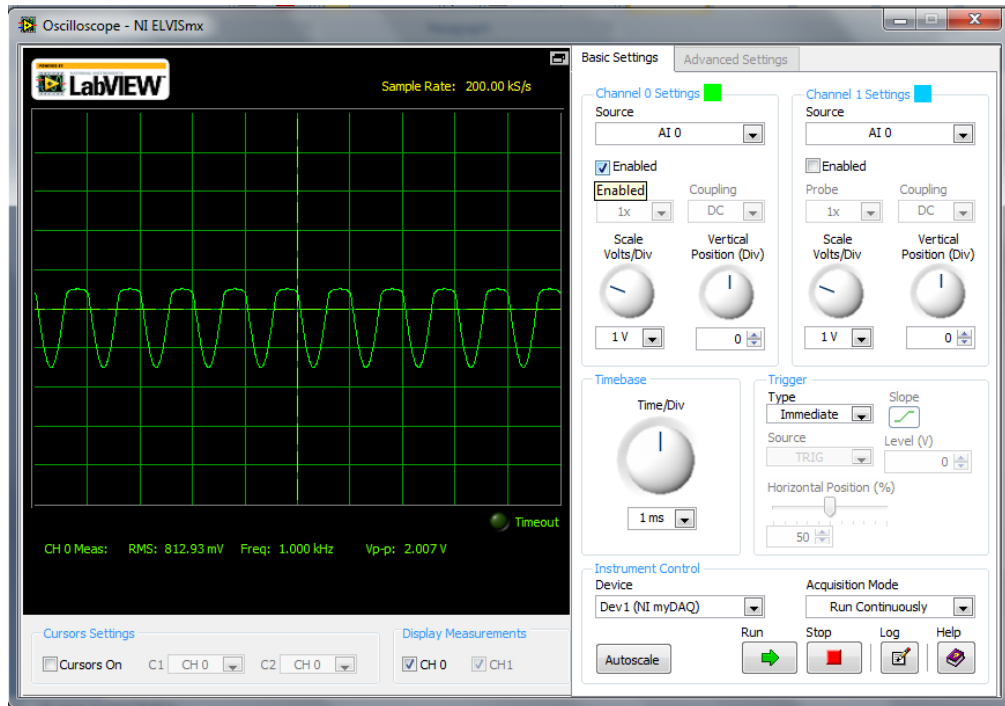For one diode clipping circuit (Figure A-1), apply a 2 V peak-to-peak, 1 KHz sinusoidal wave as input.




$V_{pk-pk} = 2.0V$   
 $V_{max} = 0.5V$   
 $V_{min} = -1.5V$

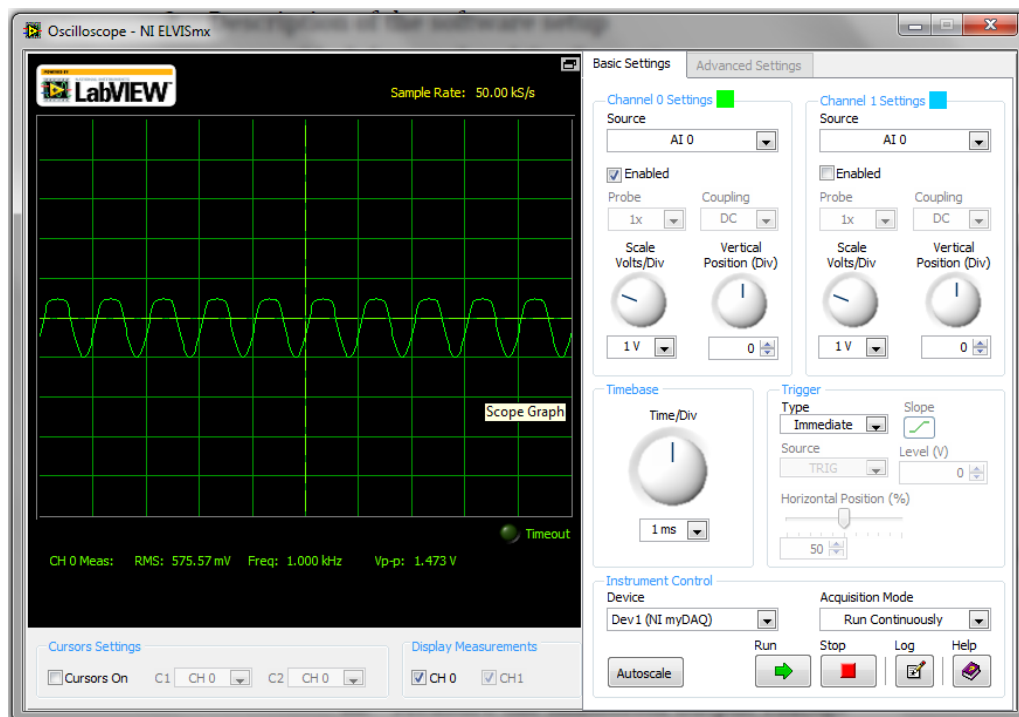For one diode clipping circuit (Figure A-1), apply a 3 V peak-to-peak, 1 KHz sinusoidal wave as input.




$V_{pk-pk} = 1.473V$   
 $V_{max} = 0.473V$   
 $V_{min} = -1.0V$

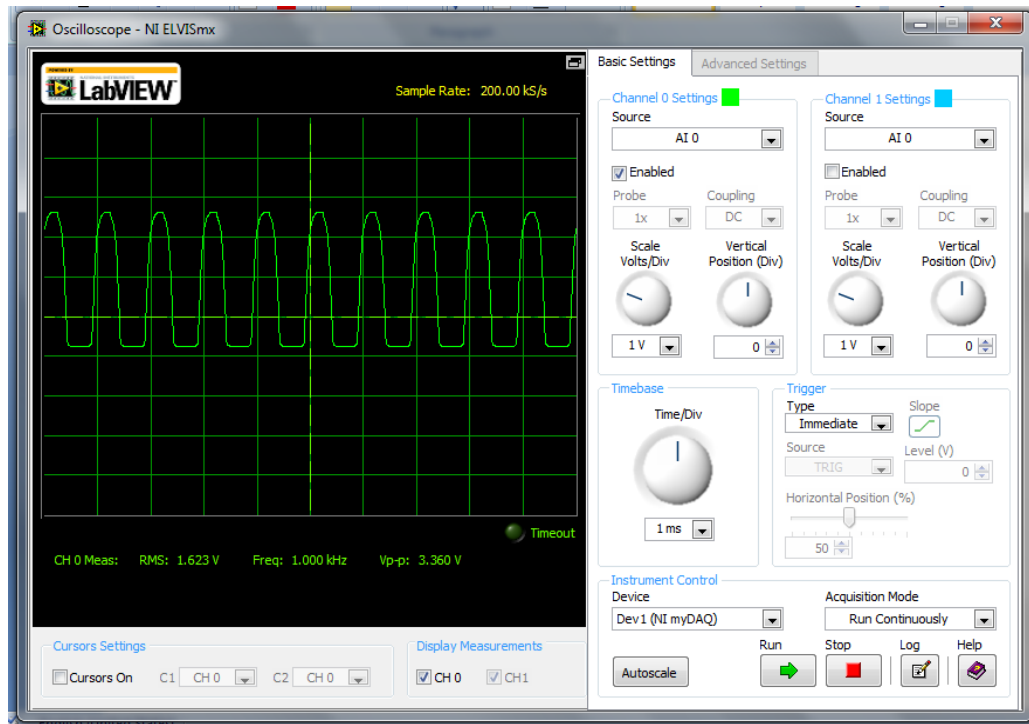For one Zener clipping circuit (Figure A-2), apply a 3 V peak-to-peak, 1 KHz sinusoidal wave as input.




$V_{pk-pk} = 3.36V$   
 $V_{max} = 2.56V$   
 $V_{min} = -0.8V$

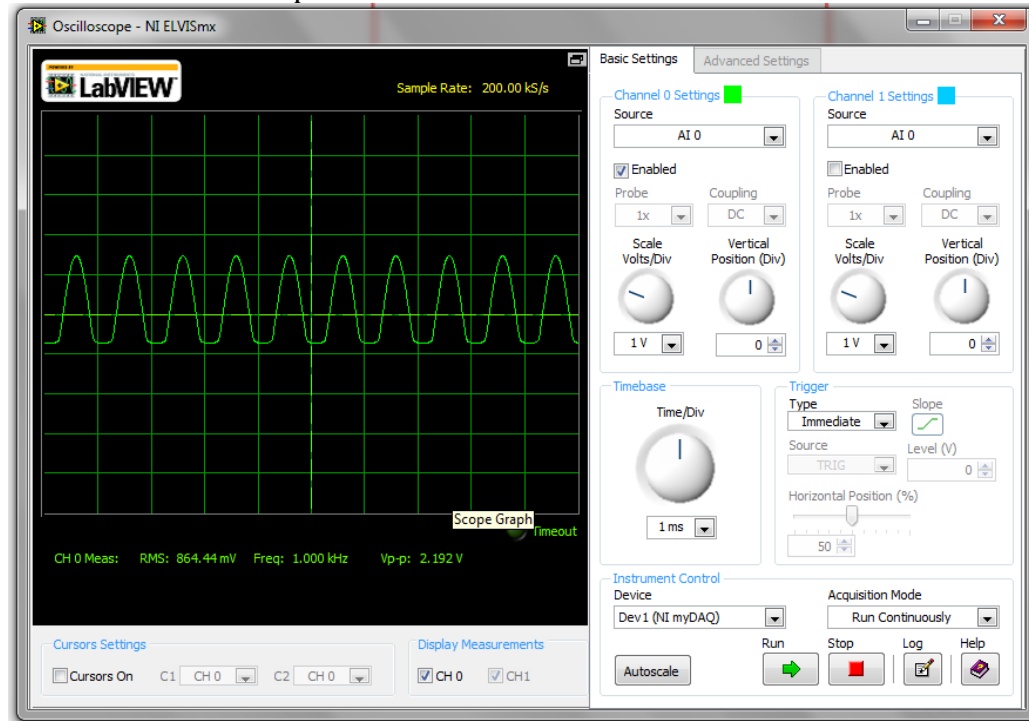For one Zener clipping circuit (Figure A-2), apply a 10 V peak-to-peak, 1 KHz sinusoidal wave as input.



$V_{pk-pk} = 2.192V$   
 $V_{max} = 1.4V$   
 $V_{min} = -0.792V$

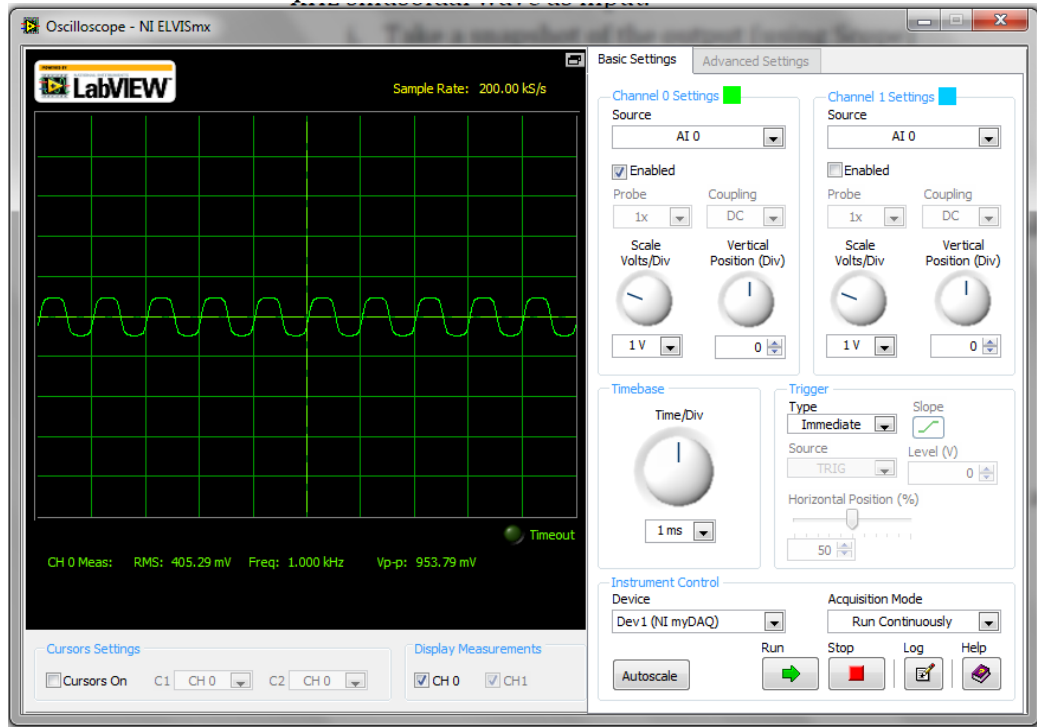For two diode clipping circuit (Figure A-3), apply a 2 V peak-to-peak, 1 KHz sinusoidal wave as input.




$V_{pk-pk} = 953.8\text{mV}$

$V_{max} = 476.9\text{mV}$

$V_{min} = -476.9\text{mV}$

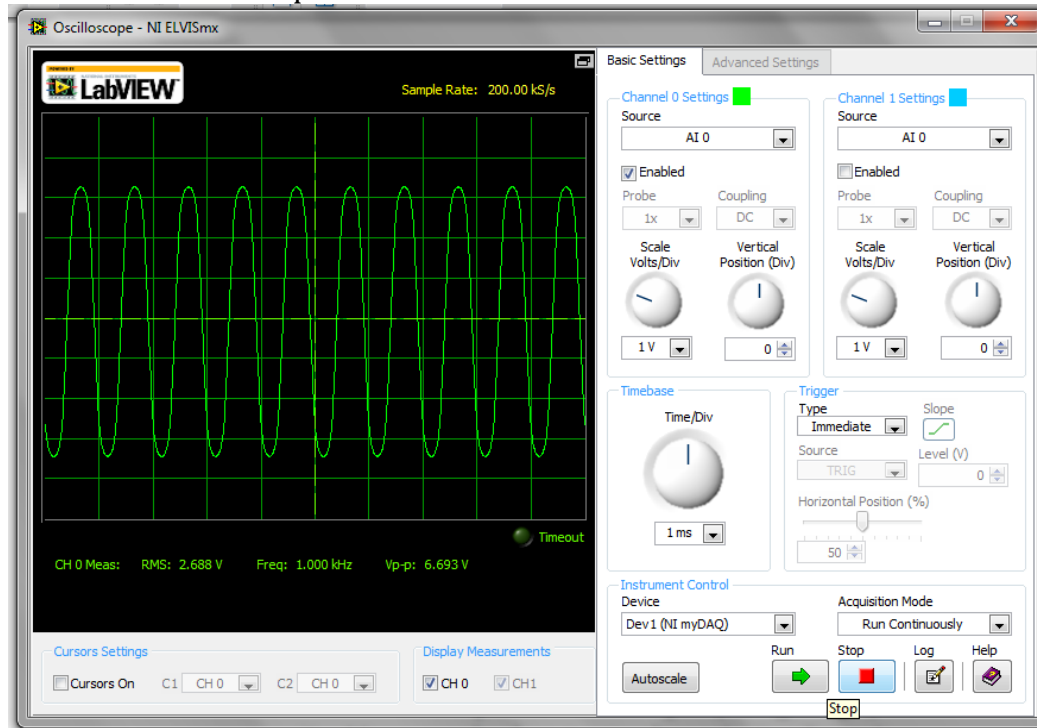For two Zener clipping circuit (Figure A-4), apply a 10 V peak-to-peak, 1 KHz sinusoidal wave as input.




$V_{pk-pk} = 6.693\text{V}$

$V_{max} = 3.347\text{V}$

$V_{min} = -3.347\text{V}$

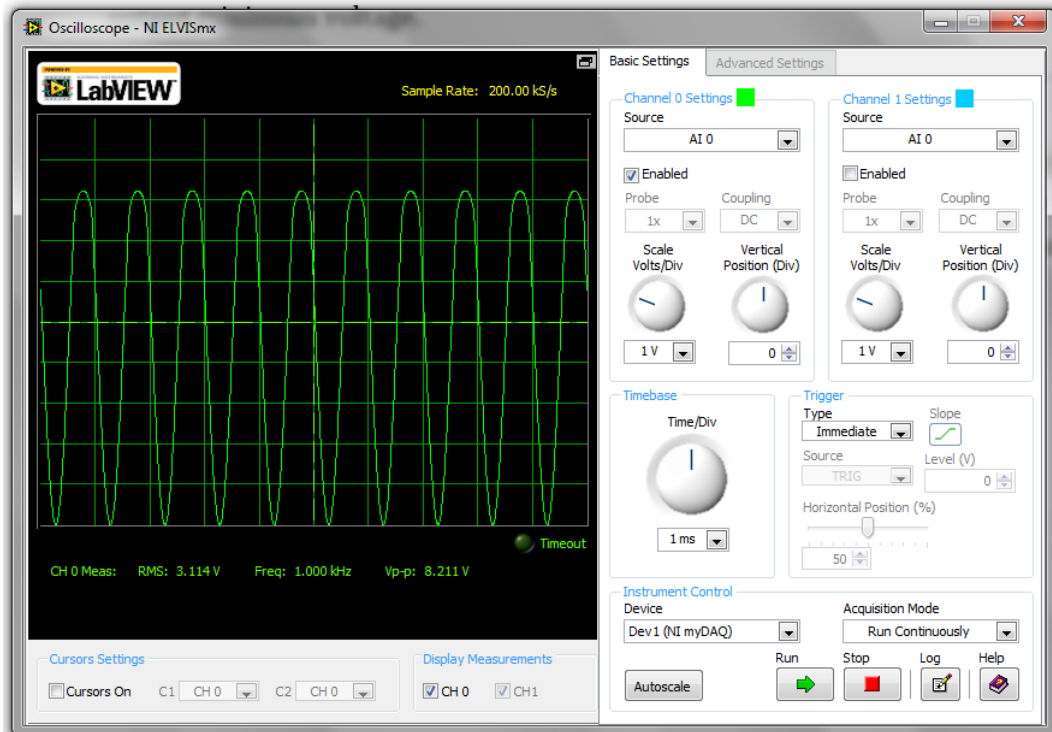For diode clipping circuit with DC source (Figure A-5), apply a 10 V peak-to-peak, 1 KHz sinusoidal wave as input.



Vpk-pk = 8.211V  
Vmax = 3.21V  
Vmin = -5.0V