

# Experiment 3: Voltage Dividers and Thévenin's Theorem

---

## Post-Lab Report

### I. Discussion on parts A and B

- Refer to the data of Table A.1. How does the load current vary with the load resistance  $R_L$ ? Explain why.

As the load current increase , the load resistor decrease, thus they are inversely proportional

- Refer to Table A.1. What is the effect on bleeder current  $I_1$  as the load current increases? Explain why.

as the load current increases , the bleeder current also decreases.

$$I = I_1 + I_L$$

When  $I_L$  increases ,  $I_1$  decreases to maintain  $I$  constant.

### Experiment 3: Voltage Dividers and Thévenin's Theorem

- What is the effect on the voltages  $V_A$  and  $V_B$  at the divider taps as the load current increases (Table A.1)? Explain why.

When  $I_L$  increases  $V_b$ ,  $V_a$  and  $(V_b - V_a)$  decreases.  $V_b - V_a = I_1 * R_a$ ;  $R_a$  is constant and  $I_1$  decreases. so  $V_b - V_a$  will decrease

- Compare the computed values in Table A.1 with the measured values. Explain any differences.

The values are almost the same; difference due to experimental error

- Compare the design values and the measured values of the circuit in Fig. B.1. Explain any differences.

The measurements were precise and accurate, where the error on measurements is almost negligible

## II. Discussion on parts C

- Compare the measured and theoretical values obtained for  $V_{TH}$  and  $R_{TH}$  of Fig. C.3. Explain any differences in the values of  $V_{TH}$  and  $R_{TH}$ .

There is no differences in the values they can be considered the same .

- With the  $2.2\text{ K}\Omega$  resistor in branch CD of Fig. C.3 opened; calculate  $V_{TH}$  and  $R_{TH}$  of the modified circuit. Explain any differences in the values of  $V_{TH}$  and  $R_{TH}$ .

We open-circuit the branch CD , so its obvious to obtain different values of  $V_{TH}$  and  $R_{TH}$

- In the Procedure of Part C,  $R_{TH}$  was derived by shorting the 15 V source in Fig. C.3 and measuring the resistance between A and B. In the statement of Thévenin's theorem,  $R_{TH}$  is derived from the current that flows when  $R_L$  is shorted. Verify the equivalence of these two methods.

### *Experiment 3: Voltage Dividers and Thévenin's Theorem*

% error = 0.176

Both methods are correct