

Voltage Dividers and Thévenin's Theorem


Objectives:

In this experiment you will learn how to:

- Determine analytically the effects of a load on the voltage relationships in a resistive voltage-divider circuit.
- Design a voltage divider which will meet specified voltage and current requirements.
- Investigate the operation of real voltage and current sources, and calculate and measure the Thévenin voltage and resistance of a circuit.

A. Voltage Divider Circuits

Circuit Diagrams

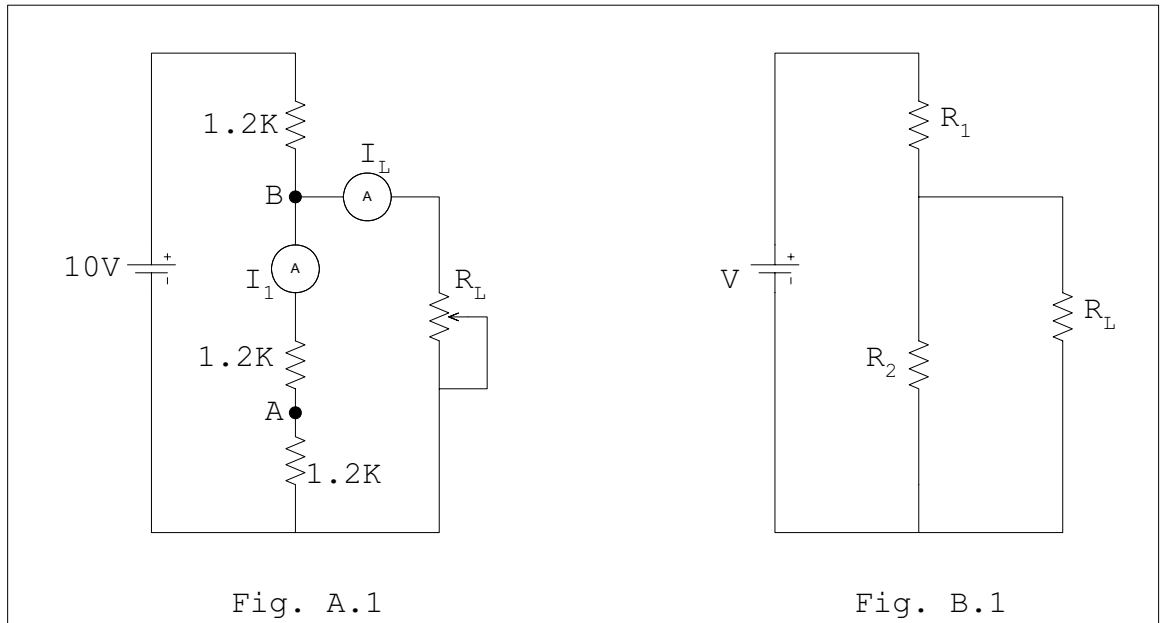

Procedure

- Connect the circuit of Fig. A.1. Maintain a *constant* voltage of 10V at the input.
- With zero load current, (i.e. rheostat open), measure the bleeder current I_1 (in mA) and record in Table A.1. Measure also and record the voltages V_B to ground, and V_A to ground.
- Connect the rheostat in the circuit and adjust it to draw 2 mA of load current while maintaining $V=10V$, measured. Measure and record the bleeder current and the voltages V_B and V_A . Open the load resistor R_L , but *do not vary* the setting of the arm. Measure and record the resistance to which it was set to draw 2 mA of load current. Reconnect R_L after this measurement.
- Repeat the previous step for conditions of 4 mA and 6 mA of load current.
- Compute and record in Table A.1, the bleeder current I_1 , the voltages V_B and V_A , and the load resistance R_L for each of the load conditions in the experiment. Show your computations.

TABLE A.1

Measured						Computed			
V (V)	I _L (mA)	I ₁ (mA)	V _B (V)	V _A (V)	R _L (Ω)	I ₁ (mA)	V _B (V)	V _A (V)	R _L (Ω)
10	0								
10	2								
10	4								
10	6								

B. Voltage Divider Design

Procedure

- Design a voltage-divider circuit, similar to that shown in Fig. B.1, for a 6-V regulated power supply which must feed a 3 mA load at 4.4V. The bleeder current should be 2 mA (approximately). Draw the circuit diagram, showing all values of voltage, current, and resistance. Show your computations.

Note

Ask your instructor to check your solution before you connect the circuit.

- Select the required resistors from your kit. If your kit does not contain a design-value resistor, adjust a potentiometer connected as a rheostat to the desired value, or make up the resistor from a combination (series, parallel) of the other resistors.
- Connect the circuit. Measure the required voltages and currents and record them in a table.

Discussion on Parts A and B

- Refer to the data of Table A.1. How does the load current vary with the load resistance R_L ? Explain why.
- Refer to Table A.1. What is the effect on bleeder current I_1 as the load current increases? Explain why.
- What is the effect on the voltages V_A and V_B at the divider taps as the load current increases (Table A.1)? Explain why.
- Compare the computed values in Table A.1 with the measured values. Explain any differences.
- Compare the design values and the measured values of the circuit in Fig. B.1. Explain any differences.

C. Thévenin's Theorem

Circuit Diagrams

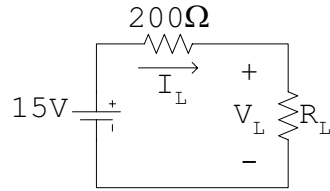


Fig. C.1

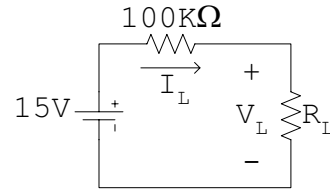


Fig. C.2

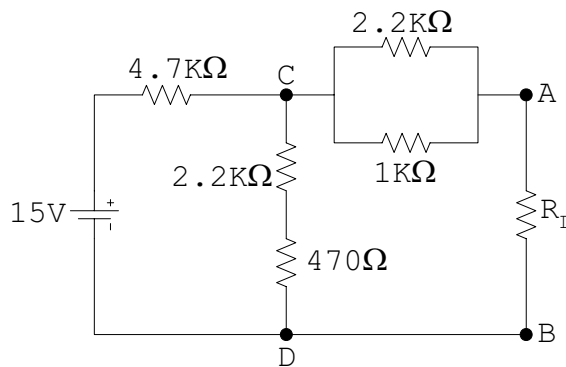


Fig. C.3

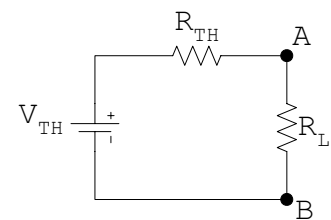


Fig. C.4

Procedure

- The resistor R_L in the circuits of Fig. C.1 and Fig. C.2 takes the values 100 K Ω , 56 K Ω , 22 K Ω , 5.6 K Ω , 2.2 K Ω , 1 K Ω , 560 Ω , 220 Ω , and 100 Ω . Measure each of the resistor values using the digital multimeter, then connect the circuit, and measure V_L in each case. Calculate the value of I_L and plot V_L vs. I_L for both circuits. For the circuit of Fig. C.2, transform the voltage source and the 100 K Ω resistor to an equivalent current source before plotting V_L vs. I_L .
- Calculate the Thévenin voltage V_{TH} and the Thévenin resistance R_{TH} for the circuit of Fig. C.3.
- With the Thévenin values just found, calculate the load voltage V_L across the load resistance across R_L , for $R_L = 1\text{ K}\Omega$ and $R_L = 4.7\text{ K}\Omega$ using the circuit of Fig. C.4.
- Connect the circuit of Fig. C.3 and measure the open-circuit voltage between points A and B of this circuit.

- With the 15 V source in Fig. C.3 replaced by a short-circuit, measure the resistance between the AB terminals with the digital multimeter.
- Connect the load resistances of 1 K Ω and 4.7 K Ω in turn in the circuit of Fig. C.3 and measure the corresponding load voltages.
- Find R_{TH} using the matched-load method; that is, use a 5 K Ω potentiometer as a variable resistance between the AB terminals of the circuit of Fig. C.3. Vary the resistance until load voltage drops to half of the measured V_{TH} (open-circuit voltage.) Then disconnect the load resistance and measure its resistance with the multimeter.

Discussion on Part C

- Over what range of values of R_L can the source of Fig. C.1 be considered to closely approximate an ideal voltage source? Over what range of values of R_L can the source of Fig. C.2 be considered to closely approximate an ideal current source? Convert the source in Fig. C.2 to an ideal current source in parallel with a source resistance using Norton's theorem; prove the equivalence by writing the circuit equations.
- Compare the measured and theoretical values obtained for V_{TH} and R_{TH} of Fig. C.3. Explain any differences in the values of V_{TH} and R_{TH} .
- With the 2.2 K Ω resistor in branch CD of Fig. C.3 opened, calculate V_{TH} and R_{TH} of the modified circuit. Explain any differences in the values of V_{TH} and R_{TH} .
- In the Procedure of Part C, R_{TH} was derived by shorting the 15 V source in Fig. C.3 and measuring the resistance between A and B. In the statement of Thévenin's theorem, R_{TH} is derived from the current that flows when R_L is shorted. Verify the equivalence of these two methods.