

Experiment 3

Voltage Dividers

And Thévenin's Theorem

In-Lab Report

Measure and record in the Table A.1 below, the bleeder current I_1 , the voltages V_B and V_A , and the load resistance R_L for each of the load conditions in the experiment 3 part A.

Measured Values					
V (V)	I_L (mA)	I_1 (mA)	V_B (V)	V_A (V)	R_L (Ω)
10	0	2.380	6.867	3.735	Infin
10	2	1.764	5.185	2.856	2591
10	4	1.158	3.512	1.947	875.6
10	6	0.572	1.802	1.012	292.7

TABLE A.1

After connecting the circuit of Fig. C.1, measure the open-circuit voltage between points A and B.

Open Circuit Voltage	5.459
----------------------	-------

With the 15 V source in Fig. C.1 replaced by a short-circuit, measure the resistance between the AB terminals with the digital multimeter.

Resistance AB	2375 ohm
---------------	----------

Matched-Load Method:

R_{TH}	2363
V_{TH}	2.73