

Experiment 10

Digital Design

In-Lab Report

Half Adder

Test the circuit you built by applying the different combinations and checking for the outputs.

A1	B1	S1	C1
0	0		
0	1		
1	0		
1	1		