

Experiment 10

Digital Design

In-Lab Report

Half Adder

Test the circuit you built by applying the different combinations and checking for the outputs.

A1	B1	S1	C1
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1