

# Experiment 6:

## LEDs and Zener Diodes

---

### Post-Lab Report

**A.**

- If  $V_S = 12\text{ V DC}$ , choose the series resistor to give 20 mA through the red LED. Draw the load line.

- In the circuit of Fig. 2, does the power dissipated in the reverse direction serve any useful purpose? How can it be eliminated?

**B.**

- Plot a curve of  $I_Z$  versus  $V_Z$ .

- Calculate the value of the Zener resistance  $r_Z$ .

- What is the minimum value of  $V_S$  required to get Zener diode breakdown?

- What is the value of the knee Zener voltage,  $V_{ZK}$ ? ; What is the value of knee Zener current,  $I_{ZK}$ ?

- Find the line regulation of the Zener diode.

- For what range of load resistors does the Zener diode regulate the load voltage? What is the load regulation of the Zener diode?

- How is the maximum current in a Zener diode determined?

- How is the minimum current in a Zener diode determined?

- Show that for a Zener voltage regulator, the value of the resistor R should be chosen using the equation:

$$R = \frac{V_{Smin} - V_{ZK} - r_Z I_{ZK}}{I_{ZK} + I_{LOADmax}}$$

