

# Experiment 5:

## Diode Rectifier Circuits

---

### Post-Lab Report

#### A. Rectifier Design Characteristics

- How is the current rating of the transformer secondary calculated?

$I_2 = I_1 \cdot (N_1/N_2)$  where:  $N_1$  &  $N_2$  are respectively the number of turns of the primary & secondary coil.  
 $I_1$  is the current rating of the transformer primary.

- Compare the three circuits for each of the characteristics 1 to 6 listed in the theory section. What is the regulation mainly due to?

\_DC output voltage VDC is the highest for center-tapped full-wave rectifier, lower for bridge full-wave rectifier ( $=|V_{in}|$ ), and the lowest for half-wave rectifier. The full wave-rectifiers have a greater VDC than the half-wave rectifier.

\_Ripple-factor: The three circuits have approximately the same ripple  $V_{pp}$ . The bridge rectifier has a ripple  $V_{pp}$  slightly less than the other due to the presence of two conducting diodes.

\_Average and peak currents in each diode.

The average and peak currents in the rectifiers are the greatest in the half-wave rectifier, and they are approximately equal in both full-wave rectifiers.

- Under what conditions would each of the circuits be most advantageous?

\_Full- wave rectifiers circuit is most advantageous for supplying power for small intervals of time.  
\_Bridge- full- wave rectifiers circuit is cheaper and easier to construct than center-tapped ones.  
\_Half- wave rectifier circuit is advantageous for charging purposes because charging takes more time and thus needs power for a large interval of time (the case where full-wave rectifier isn't advantageous).

## B. Full Wave Rectifier with Capacitor (Fig.4)

- Does  $V_{DC}$  increase appreciably with  $C$  for all values of  $C$ ?

$V_{DC}$  increases exponentially as the value of  $C$  increases.

- Does  $V_r$  decrease appreciably with  $C$  for the values of  $C$  used in the experiment?

$V_r$  decreases exponentially with the values of  $C$  but not appreciably

- Under what conditions are the approximate relations in the Theory section adequate for calculating  $V_r$  and  $V_{DC}$ ?

A capacitor must be connected in parallel to the rectifier output to smooth the voltage variations and thus the conditions for the approximate relations are valid.

- How does the presence of the capacitor affect the regulation of the circuit?

The presence of a capacitor connected in parallel with the load stabilizes and maintains the output voltage, decreases  $V_r$  and thus decreases the ripple voltage.

- What additional current rating of diodes must be considered for the capacitor filter?

The model of the diodes whether ideal, constant-voltage drop or piecewise-linear must be considered.

- For a certain required ripple voltage and DC voltage/current at the load: what should be the RMS voltage rating of the secondary of the transformer? what should be the value of the capacitor?

$$\begin{aligned}V_{2\max} &= V_{DC} + V_r/2 \\ V_r &= V_{2\max}/(2*f*RL*C) \\ C &= V_{2\max}/(2*f*RL*V_r)\end{aligned}$$