

Experiment 6

Op-Amp
Circuits I

Pre-Lab Report

Question 1:

Prove theoretically that for an ideal op-amp, the relation between the output voltage and the input voltage of the inverting amplifier shown in part A of this experiment is $V_o = -\frac{R_2}{R_1} V_I$.

For an ideal operational amplifier:

$V_p = V_n = 0$ in this case

Applying KCL on the negative inverting node:

$[(V_n - V_I)/R_1] + [(V_n - V_o)/R_2] = 0$ with $V_n = 0$

$-V_I/R_1 = V_o/R_2$

Thus, $V_o = -(R_2 \cdot V_I)/R_1$

$V_o = -V_I \cdot (R_2/R_1)$

Question 2:

Prove theoretically that for an ideal op-amp, the relation between the output voltage and the input voltage of the non-inverting amplifier shown in part B of this experiment is $V_o = \left(1 + \frac{R_2}{R_1}\right) V_I$.

For an ideal op-amp: $V_n = V_p = V_I$ as indicated in the figure

Applying KCL for the negative inverting node:

$V_I/R_1 + (V_I - V_o)/R_2 = 0$

$V_o = R_2(V_I/R_1) + V_I$

$V_o = V_I \cdot (1 + R_2/R_1)$

Question 3:

Prove theoretically that for an ideal op-amp, the relation between the output voltage and the input voltage of the unity gain non-inverting amplifier shown in part C of this experiment is **$V_o = V_i$** .

For an ideal operational amplifier: $V_p = V_n$

In this case: $V_p = V_1$ and $V_n = V_o$

Thus, by substitution: $V_1 = V_o$