

## Experiment 6

# Op-Amp Circuits I

### Pre-Lab Report

**Question 1:**

Prove theoretically that for an ideal op-amp, the relation between the output voltage and the input voltage of the inverting amplifier shown in part A of this experiment is  $V_o = -\frac{R_2}{R_1} V_I$ .

**Question 2:**

Prove theoretically that for an ideal op-amp, the relation between the output voltage and the input voltage of the non-inverting amplifier shown in part B of this experiment is  $V_o = \left(1 + \frac{R_2}{R_1}\right) V_I$ .

**Question 3:**

Prove theoretically that for an ideal op-amp, the relation between the output voltage and the input voltage of the unity gain non-inverting amplifier shown in part C of this experiment is  **$V_o = V_i$** .