

Experiment 7

Op-Amp Circuits II

In-Lab Report

Inverting Adder

Question 1:

Describe the signal that you placed on the input and the result you got.

Question 2:

Draw the non-inverting adder you have designed.

Integrator

Question 1:

<i>f (Hz) at input</i> <i>f (Hz) at input</i>	<i>f (Hz) at output</i>	<i>v_o (peak-to-peak in V)</i>
1000		
4000		
7000		
10000		

Table B-1

Question 2:

At what frequency does the output stop corresponding to the integral of the input?

Question 3:

Find out what causes the deterioration in the integration action of the op-amp.

Differentiator

Question 1:

<i>f (Hz) at input</i> <i>f (Hz) at input</i>	<i>f (Hz) at output</i>	<i>v_o (peak-to-peak in V)</i>
100		
400		
700		
1000		

Table C-1