

Experiment 7**Op-Amp
Circuits II****Pre-Lab Report****Question 1:**

Prove theoretically that the relation between V_o and the inputs of the inverting adder in part A of this experiment is given by:

$$v_o = -\left(\frac{R_4}{R_1}v_1 + \frac{R_4}{R_2}v_2 + \frac{R_4}{R_3}v_3\right)$$

Question 2:

Prove theoretically that the relation between V_o and V_i of the integrator in part B of this experiment is given by:

$$V_o = -\frac{1}{RC} \int V_i dt$$

Question 3:

Prove theoretically that the relation between V_o and V_i of the differentiator in part C of this experiment is given by:

$$V_o = -RC \frac{dV_i}{dt}$$