

Experiment 9

MOS

Transistor

In-Lab Report

MOSFET As Voltage-Controlled Resistor

Table 1.

$V_{GS} - V_T$ (Volts)	V_{DS} (Volt)	I_D (mA)
2	0.1	
2	0.15	
2	0.2	
2	0.25	
2	0.3	
3	0.1	
3	0.15	
3	0.2	
3	0.25	
3	0.3	
4	0.1	
4	0.15	
4	0.2	
4	0.25	
4	0.3	

MOSFET Logic Gate

Table 2.

In-1 (Logic)	In-2 (Logic)	Out (Logic)	V _{IN1} (Volts)	V _{IN2} (Volts)	V _{out} (Volts)
0	0	1	0.00	0.00	[]
0	1	[]	0.00	[]	[]
1	0	[]	[]	0.00	[]
1	1	[]	[]	[]	[]

Table 3.

V _{IN1} (Volts)	V _{out} (Volt)	MOSFET Region of Operation	Logical Value at output
0	[]	[]	[]
0.4	[]	[]	[]
0.8	[]	[]	[]
1.2	[]	[]	[]
1.6	[]	[]	[]
2.0	[]	[]	[]
2.4	[]	[]	[]
2.8	[]	[]	[]
3.2	[]	[]	[]
3.6	[]	[]	[]
4.0	[]	[]	[]
4.4	[]	[]	[]
4.8	[]	[]	[]