

Experiment 9


MOS

Transistor

Post-Lab Report

MOSFET As Voltage-Controlled Resistor

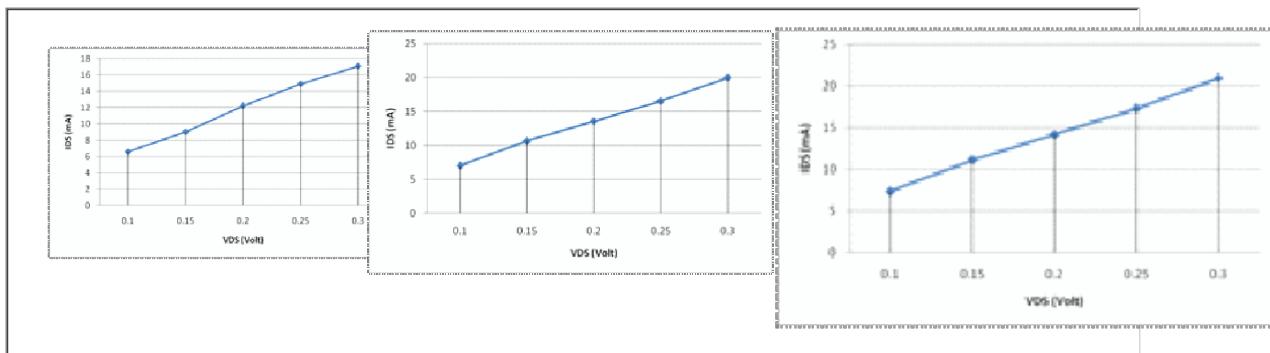Q1. For each value of $(V_{GS} - V_T)$ (2, 3, and 4 V), plot I_D versus V_{DS} . What kind of curve do you get? What is the slope for $(V_{GS} - V_T) = 2, 3, \text{ and } 4 \text{ V}$?



Q2. The inverse of the slope has units of V/A or Ohms. What is the resistance between drain and source of the MOSFET when $(V_{GS} - V_T) = 2, 3, \text{ and } 4 \text{ V}$? Complete TABLE 1.

Table 1.

$V_{GS} - V_T$ (Volts)	R_{DS} (Ohms)
2	[]
3	[]
4	[]

Q3. What are your conclusions?

Q4. In what region of operation is the MOSFET biased for the conditions described above? Can you explain why this region is called linear, or ohmic?

Q5. The current equation in the linear or ohmic region is given by:

$$I_D = \frac{k}{2} (2(V_{GS} - V_T)V_{DS} - V_{DS}^2)$$

How is this equation related to the voltage-controlled resistor behavior of the MOSFET that you have just seen? For what range of values of V_{DS} is the linear resistor approximation valid (i.e. the error in current values is less than 5%)? What is the value of R_{DS} that you get from the equation? How does it compare with the values of R_{DS} in TABLE B-2 (use the value of k calculated in part A)?

Q6. List some applications of a voltage-controlled resistor.

MOSFET Logic Gate

Q7. For this MOSFET gate, what are the values of high voltage (corresponding to logic 1) and the low voltage (corresponding to logic 0)? Note that when the two inputs are high, the output voltage is lower than the low value when only one input is high.

Q8. How is the value of the low voltage affected by the value of the 470 Ohm resistor? Would increasing this resistance make the output low value higher or lower?

Q9. Plot VOUT versus VIN1. Indicate at what value of the input voltage does the output switch states?

