

# EECE 310L: Electric Circuits Laboratory

## Experiment 10: MOS Transistors


Hussein Hazimeh

201100830

Hmh48@aub.edu.lb

Group 2

Tuesday, January 3, 2012

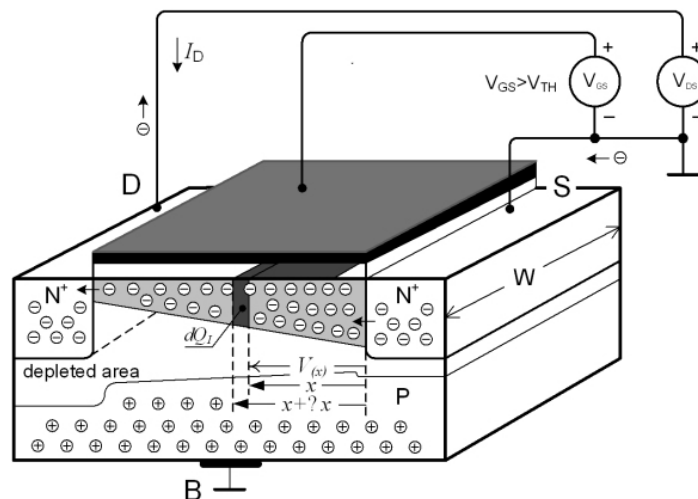

## Table of Contents

<b>I. Objectives</b>	<b>1</b>
<b>II. Lab Equipment Used</b>	<b>1</b>
<b>III. Lab tools Used</b>	<b>1</b>
<b>IV. Components Used</b>	<b>2</b>
<b>V. Experimental Procedure and Discussion</b>	<b>2-22</b>
<b>A. MOSFET Characteristics</b>	<b>2-5</b>
1. Circuit Diagrams	
2. Experimental Procedure	
3. Measurements and Results	
4. Discussions	
<b>B. MOSFET as a Voltage-Controlled Resistor</b>	<b>6-11</b>
1. Circuit Diagrams	
2. Experimental Procedure	
3. Measurements and Results	
4. Discussions	
<b>C. MOSFET as Logic Gate</b>	<b>12-14</b>
1. Circuit Diagrams	
2. Experimental Procedure	
3. Measurements and Results	
4. Discussions	

<b>D. MOSFET as an amplifier</b>	<b>15-19</b>
1. Circuit Diagrams	
2. Experimental Procedure	
3. Measurements and Results	
4. Discussions	
<b>E. MOSFET as a current source</b>	<b>19-22</b>
1. Circuit Diagrams	
2. Experimental Procedure	
3. Measurements and Results	
4. Discussions	
<b>VI. References</b>	<b>23</b>
<b>VII. Mistakes and Problems faced in the lab</b>	<b>23</b>

**List of Figures and Tables**

<b>Type</b>	<b>Title</b>	<b>Page</b>
Table	Resistors' Values	1
Table	Capacitor's Value	1
Circuit Diagram	MOSFET Characteristics	3
Tables	MOSFET Parameters	4-5
Circuit Diagram	MOSFET as VCR	6
Tables	Voltage and Current for Each $V_{GS}$	7-8
Graphs	I-V characteristics	8-9
Tables	Measured and Calculated Resistances	10-11
Circuit Diagram	NOR Circuits	12
Tables	Truth Table and Operating Regions	13
Graph	Circuit VTC	14
Circuit Diagrams	MOSFET as Amplifier	15
Tables	MOSFET biasing and Amplification Characteristics	17-18
Circuit Diagrams	MOSFET as a Current Source	19
Table	$V_{DS}$ and $i_{DS}$ as a Function of $R_{DS}$	20
Graphs	$V_{DS}$ and $i_{DS}$ as a Function of $R_{DS}$	21

## I. Objectives:

- Investigate the characteristics of the Metal-Oxide Field Effect Transistors.
- Study MOSFET's applications as:
  - Voltage-controlled resistor
  - Logic gate
  - Amplifier
  - Current source

## II. Lab Equipment Used:

- Function Generator (Agilent 33120A)
- Oscilloscope (Tektronix TDS220)
- DC Power Supply (Tektronix PS 280)
- Digital Multimeter (Fluke 45)
- Breadboard

## III. Lab Tools Used:

No soldering or connecting tools were basically used since the circuits were built as testing circuits on the breadboard.

#### IV. Components Used:

Resistors:

Theoretical Value ( $\Omega$ )	Measured Value ( $\Omega$ )	% Error
100	99.6	0.4
470	466.6	0.7
1000	1038	3.8
3300	3240	1.8
4700	4667	0.7
10000	9881	1.2
15000	14939	0.4

Capacitors:


Theoretical Value (uf)	Measured Value (uF)	% Error
10 (3 units)	NA	NA

MOSFETS: BS170 N-channel enhancement type MOSFET

#### VI. Experimental Procedure and Discussion

##### A. MOSFET Characteristics

A1. Circuit Diagrams:

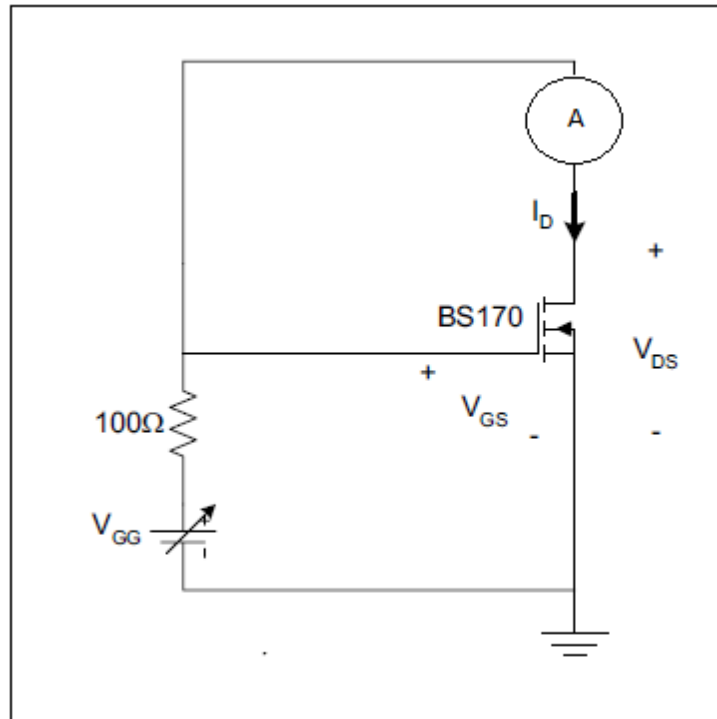

## A2. Detailed Experimental Procedure:

We setup the circuit shown above on the breadboard in which  $V_{GG}$  represents the master or the slave of the dc power supply. Since  $V_{GD} = 0$  V then the MOSFET is in the saturation region as long as the channel is enhanced (i.e.  $V_{GS} > V_T$ ). In this setup we are interested in finding the threshold voltage and the transconductance parameter of the MOSFET.

We start increasing  $V_{GG}$  from 0.5V to the value that gives a 10mA current in the digital multimeter and we record the corresponding value of  $V_{GS}$  (**and not  $V_{GG}$** ) using the voltmeter. Then we keep on increasing  $V_{GG}$  to read a current of 25mA

and record the value as before. Now, neglecting channel length modulation the

current in the drain (or the source) is given by:  $i_D = \frac{1}{2}k(V_{GS} - V_T)^2$ . Since the

transconductance parameter k is constant and independent of the current or  $V_{GS}$

then  $\frac{i_{D1}}{i_{D2}} = \frac{(V_{GS1} - V_T)^2}{(V_{GS2} - V_T)^2}$  (where  $i_{D1}$ ,  $i_{D2}$ ,  $V_{GS1}$ , and  $V_{GS2}$  are all known values). By

solving this equation we get the value of  $V_T$  and when we substitute  $V_T$  in either of

the two current equations we get k.

As to verify the values, we know that  $i_D = \frac{1}{2}k(V_{GS} - V_T)^2 \Rightarrow V_{GS} = \sqrt{\frac{2i_D}{k}} + V_T$ . So we

keep on increasing  $V_{GG}$  further to get a current of 40mA and we measure  $V_{GS}$  using

the voltmeter. The smaller the error between the measured  $V_{GS}$  and the

calculated one using the formula above, then the better are the values of the

parameters we got.

### A3. Measurements and Results:

Measure	
$I_D$	$V_{GS}$ (Volts)
10 mA	2.1122
25 mA	2.2785



Calculate		Units
K	<input type="text" value="0.244"/>	<input type="text" value="A/V^2"/>
V <sub>T</sub>	<input type="text" value="1.826"/>	<input type="text" value="V"/>


Calculated Vs Measured	
V <sub>GS</sub> Calculated (volts)	<input type="text" value="2.39"/>
V <sub>GS</sub> Measured (Volts)	<input type="text" value="2.42"/>

A4. Discussions:

The percent error between the calculated value of V<sub>GS</sub> and the measured one is 1.255% which is relatively small and proves that the values of the obtained parameters V<sub>T</sub> and k are accurate. This small error can be referred to the fact that we neglected channel length modulation and to measurement inaccuracies.

## B. MOSFET as a Voltage-Controlled Resistor

### B1. Circuit Diagrams:

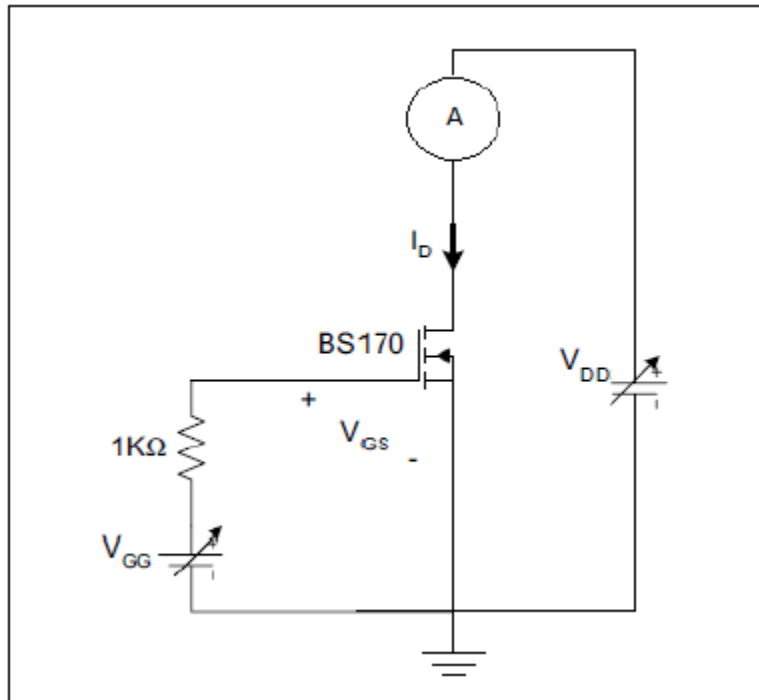

### B2. Detailed Experimental Procedure:

We build the circuit shown above in which the source is grounded and the gate and the source are connected to the master and slave of the power supply. As will be described later, the MOSFET is operating in the triode region (as long as  $V_{GG} > V_T$  and  $V_{GG} > V_{DD}$ ) where it acts as a resistor. To study the resistance of the MOSFET we should get the values of  $V_{DS}$  and  $i_D$  for each setup.

So we set  $V_{GG} = V_T + 2$  and we start increasing  $V_{DS}$  and recording the corresponding values of  $i_D$ . Then we repeat the same procedure for  $V_{GG} = V_T + 3$  and  $V_{GG} = V_T + 4$ .

**B3. Measurements and Results:**


$V_{GS} - V_T = 2$ Volts	
$V_{DS}$ (Volts)	$I_D$ (mA)
0.1	56.4
0.15	81.86
0.2	110.12
0.25	136.92
0.3	161.55



$V_{GS} - V_T = 3$ Volts	
$V_{DS}$ (Volts)	$I_D$ (mA)
0.1	77.5
0.15	94.53
0.2	136
0.25	164
0.3	197

$V_{GS} - V_T = 4 \text{ Volts}$	
$V_{DS}$ (Volts)	$I_D$ (mA)
0.1	81
0.15	103
0.2	156
0.25	174
0.3	226

B4. Discussions:

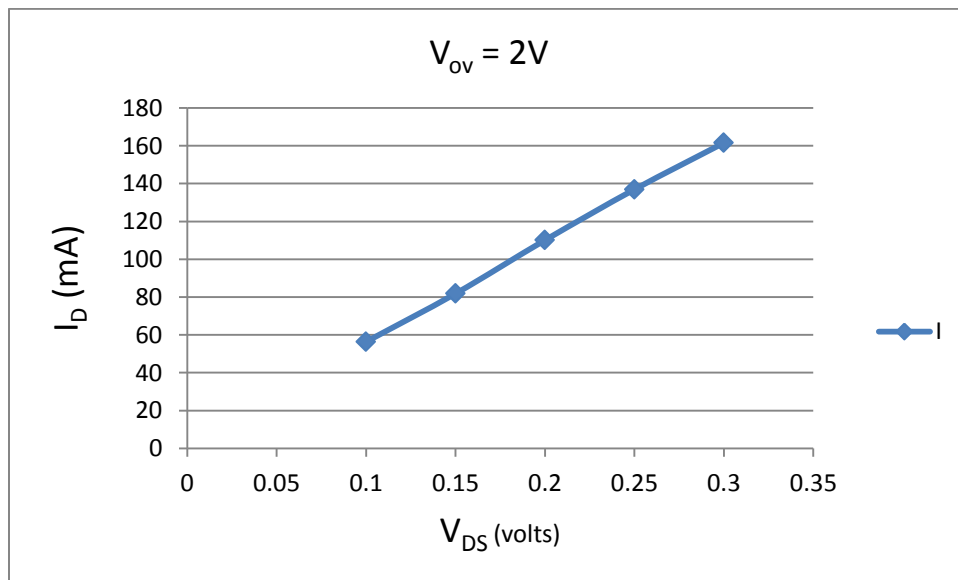- Below are the graphs of  $i_D$  versus  $V_{DS}$  for each  $V_{ov}$  (Plotted using Excel)



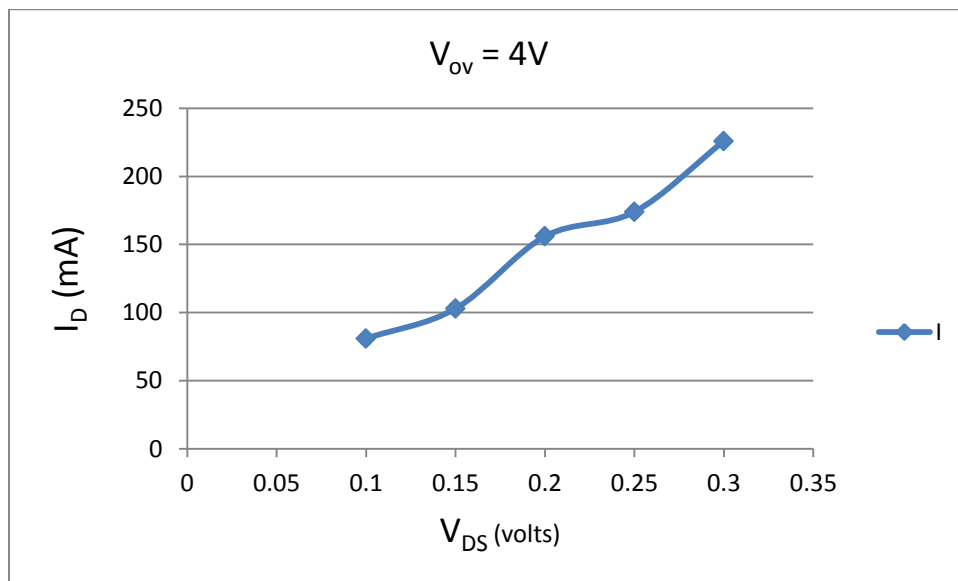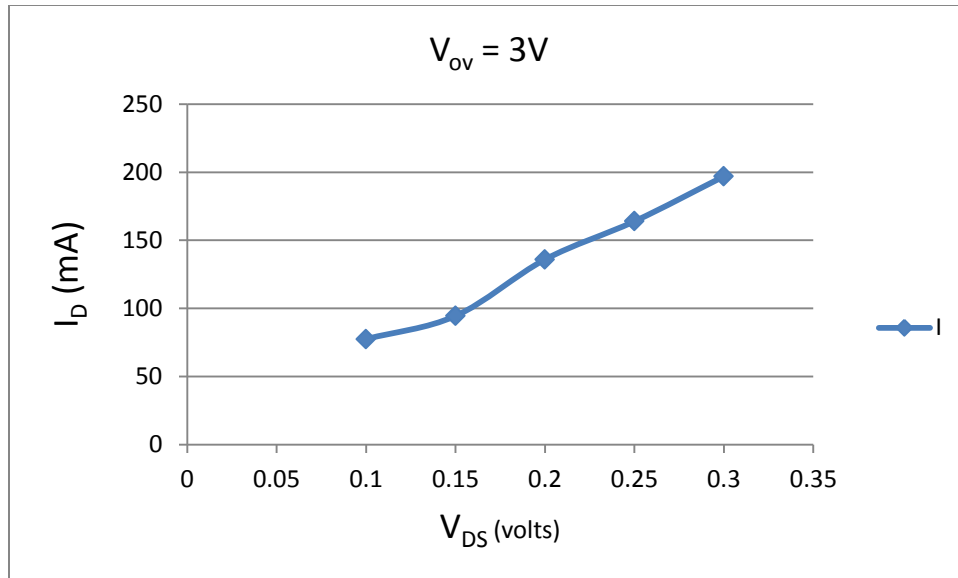

The graphs are linear. However, it seems that graphs 2 and 3 have remarkable measurement errors which lead to some fluctuations in them.

$V_{GS} - V_T$ (Volt)	Slope* (mA / V)	$R_{DS}$ (ohm)
2	530.72	1.884
3	616.94	1.621
4	722.00	1.385

\* The slopes are calculated using the least-square regression method (by Excel)

- The MOSFET is biased to operate in the triode region. This is obvious since  $V_{GS} > V_T$  and  $V_{GS} > V_{DS}$  for all the setups above. The triode region is also referred to as “linear” or “ohmic” since the relation between  $V_{DS}$  and  $i_D$  is linear in which the MOSFET acts as a resistor (i.e. the v-i relation satisfies ohm’s law  $V = Ri$ ).
- The i-v equation of the MOSFET in the triode region is given by:

$$i_D = \frac{1}{2} k (2(V_{GS} - V_T)V_{DS} - V_{DS}^2),$$

but since  $V_{DS}$  is too small then the term  $V_{DS}^2$  can

be neglected yielding  $i_D = k (V_{GS} - V_T)V_{DS} \Rightarrow R_{DS} = \frac{1}{k (V_{GS} - V_T)}$  which is a resistor

whose resistance is controlled by the value of  $V_{GS}$ .

The percent error in  $i_D$  after neglecting  $0.5V_{DS}^2$  should be less than 5% thus:

$$\left| \frac{i_{D1} - i_{D2}}{i_{D1}} \right| \leq 0.05 \Rightarrow \frac{k (V_{GS} - V_T)V_{DS}}{k((V_{GS} - V_T)V_{DS} - 0.5V_{DS}^2)} \leq 1.05$$

Eliminating  $k$  and  $V_{DS}$  we get  $\frac{(V_{GS} - V_T)}{(V_{GS} - V_T) - 0.5V_{DS}} \leq 1.05$  and thus

$$V_{DS} \leq \frac{2}{21}(V_{GS} - V_T) \text{ for the error in the current to be less than 5\%}$$


$V_{GS} - V_T$ (Volt)	$R_{DS}$ Calculated (ohm)	% Error
2	2.049	8.75
3	1.366	15.73
4	1.024	26.06

The error is large especially in the third case and this normal if we observe the non-linearity of the curve corresponding to  $V_{GS} - V_T = 4V$ . The latter maybe due to measurement errors as described before.

- Applications of MOSFETs in the linear region include:
  - Variable gain amplifiers where the gain is controlled by a variable voltage between the gate and the source.
  - Analog Filters

### C. MOSFET as Logic Gate

#### C1. Circuit Diagrams:

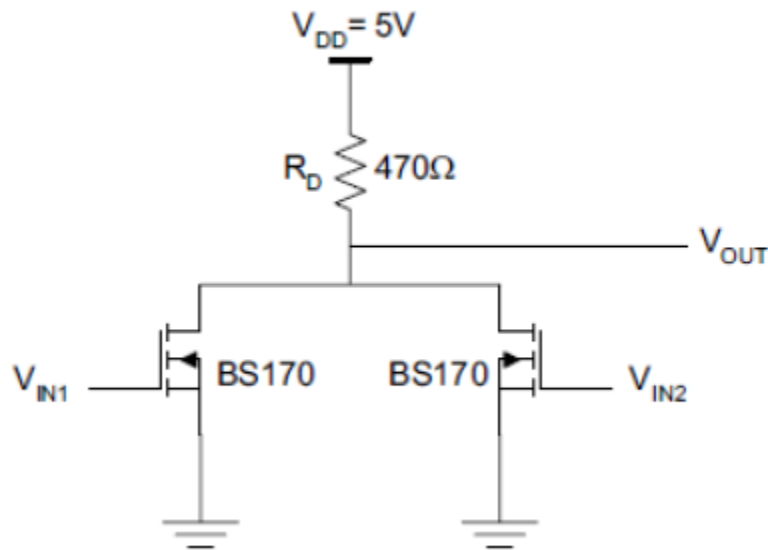

#### C2. Detailed Experimental Procedure:

We connect the circuit shown above where the gates of both MOSFETs are connected to the inputs and the output is across the common drain. Each MOSFET in the circuit will operate either in triode or cutoff regions which allows the MOSFET to operate as 2-input NOR gate. We will apply the 4 logic input combinations to verify that. After that, we set  $V_{in2}$  to 0 and we vary  $V_{in1}$  over several values to get the output values and deduce the corresponding regions of operation.



### C3. Measurements and Results:

IN1 (logic)	IN2(logic)	Out(logic)	$V_{IN1}$ (V)	$V_{IN2}$ (V)	$V_{out}$ (mV)
0	0	1	0.0	0.0	5200
0	1	0	0.0	5	10.2
1	0	0	5	0.0	10.2
1	1	0	5	5	1.4

$V_{IN1}$ (V)	$V_{out}$ (mV)	MOSFET Region (cutoff, Saturation, or Triode)	logic value at output (0,1, no)
0	4995	cutoff	1
0.4	4995	cutoff	1
2.0	2.34	saturation	no
4.8	12.53	triode	0

### C4. Discussions:

- As shown in the results, this MOSFET has a  $V_H = 5.2$  V and  $V_L = 10.2$  mV
- When at least one of the MOSFETs is operating in triode the output of the circuit would be logic 0. The MOSFET can be modeled by a resistor in the

triode region with resistance  $R_{DS} \ll R_D$ , thus  $R_D$  makes the logic 0 equivalent

to a very low output voltage due to the voltage divider  $V_o = \frac{R_{DS}}{R_{DS} + R_D} V_{DD}$


(This divider applies if exactly one MOSFET is in triode, however, if both

MOSFETs are in triode then  $V_o = \frac{R_{DS1} \parallel R_{DS2}}{(R_{DS1} \parallel R_{DS2}) + R_D} V_{DD}$  ). Increasing  $R_D$  would

make the denominator of the voltage dividers bigger and thus  $V_{OL}$  would

decrease, thus  $R_D$  and  $V_{OL}$  are inversely proportional. Note:  $R_D$  has no


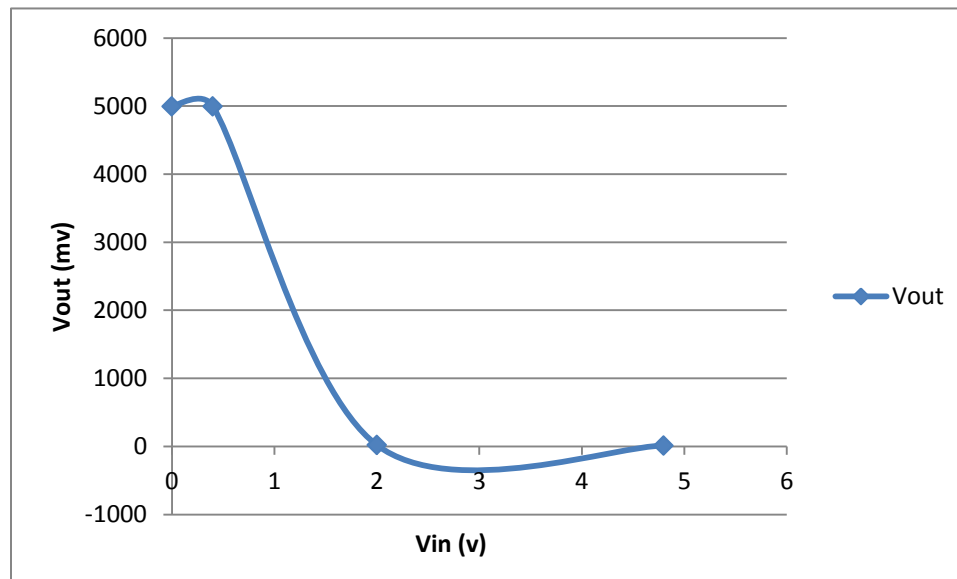
effect on the output when the MOSFETs are both in cutoff.



The above graph just shows the shape of the real graph due to the limited number of data points (We have 4 points only!). Graphically, the MOSFET changes from cutoff to saturation at  $V_{in1} \approx 0.4V$ , and it changes from saturation to triode at  $V_{in1} \approx 2V$ .

### D. MOSFET as an amplifier

#### D1. Circuit Diagrams:

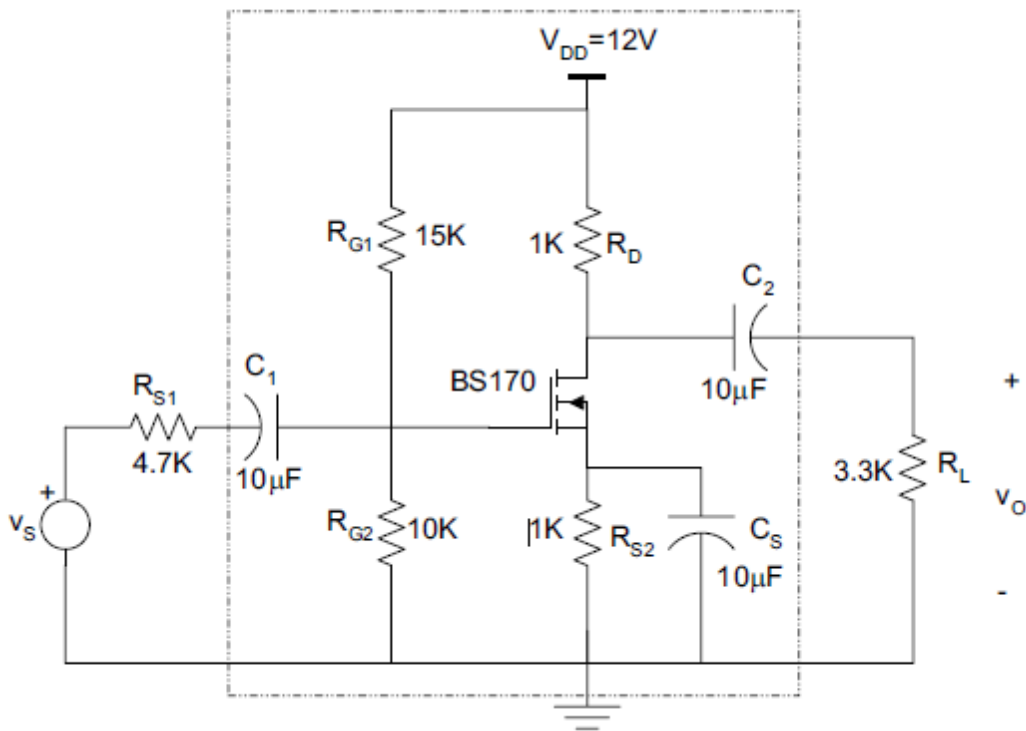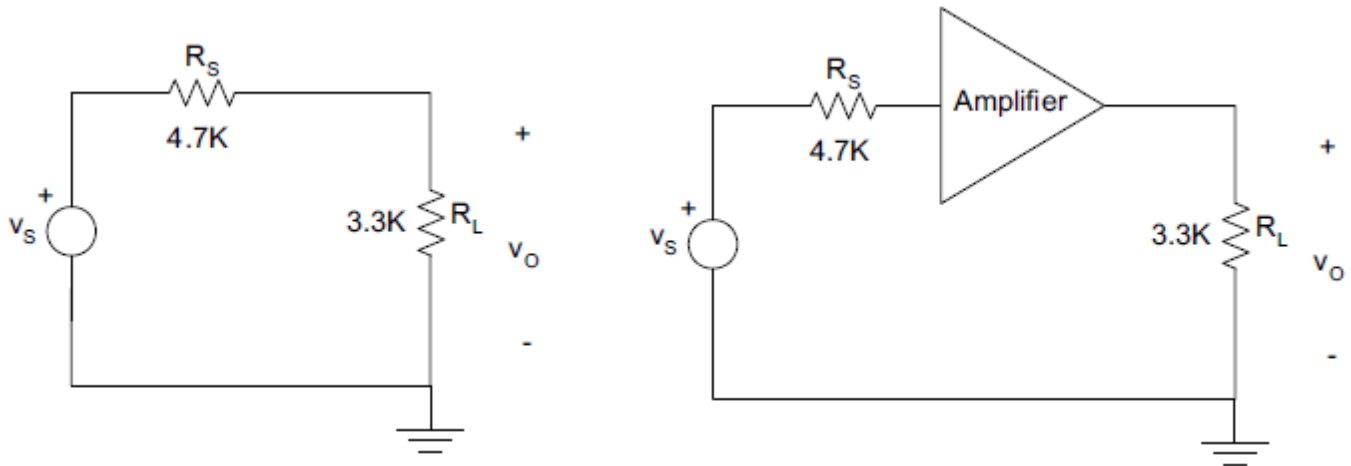

## D2. Detailed Experimental Procedure:

We connect the first circuit where the amplifier is not inserted and we should observe two important points:

- The voltage gain can't exceed 1 and thus the circuit acts as an attenuator.
- There is input signal frequency does not affect gain.

Then we connect the circuit with the MOSFET acting as an amplifier and capacitors to isolate the DC and AC components of the input and output. Note also that the MOSFET is biased to operate in the saturation region in order to avoid output signal distortion.

After that we measure the maximum value of the output in saturation, and we vary the frequency to relatively low and high frequencies to get the high and low cutoff frequencies where the amplitude is  $\frac{1}{\sqrt{2}}$  it's value at saturation.

## D3. Measurements and Results:

Perform DC analysis, thus

$$V_G = \frac{R_{G2}}{R_{G2} + R_{G1}} V_{DD} = \frac{10}{10 + 15} 12 = 4.8V$$

$$i_D = \frac{1}{2} k (V_{GS} - V_T)^2 \Rightarrow i_D = \frac{1}{2} k (V_G - R_{s2} i_D - V_T)^2$$

$$i_D = \frac{1}{2} (0.244)(4.8 - 1000i_D - 1.826)^2 \Rightarrow \boxed{i_{D1} = 2.8219 \text{ mA}} \text{ (accepted) } \text{ or } i_{D2} = 3.1342 \text{ mA (rejected)}$$

$$\boxed{V_{GS} = 4.8 - 2.8219 = 1.978 \text{ V}} > V_T \Rightarrow \text{Accepted}$$

$$\boxed{V_{DS} = 12 - 2 \times 2.8219 = 6.3562 \text{ V}}$$

Perform AC analysis, thus

$$g_m V_{gs} + V_O \left( \frac{1}{R_D} + \frac{1}{R_L} \right) = 0$$

$$\frac{V_O}{V_{gs}} = \frac{-g_m}{\frac{1}{R_D} + \frac{1}{R_L}} = -28.5 \text{ v/v}$$

$$\Rightarrow A_v = \frac{V_O}{V_{sig}} = \frac{V_O}{V_{gs}} \frac{V_{gs}}{V_{sig}} = -28.5 \times \frac{60}{107} = -15.98 \text{ v/v}$$

	Value
I <sub>D</sub> (DC) mA	<input type="text" value="3.48"/>
V <sub>GS</sub> (DC) Volts	<input type="text" value="1.22"/>
V <sub>DS</sub> (DC) Volts	<input type="text" value="5.1"/>

	Value
V <sub>S</sub> PK-PK (mV)	<input type="text" value="115"/>
V <sub>I</sub> PK-PK (mV)	<input type="text" value="64.8"/>
V <sub>O</sub> Pk-PK (mV)	<input type="text" value="960"/>
Phase Shift (V <sub>I</sub> , V <sub>O</sub> ) degrees	<input type="text" value="180"/>

For sure this measured value is wrong! Since V<sub>GS</sub> > V<sub>T</sub>. This was due the malfunctioning MOSFET.

Bandwidth Measurements	
$F_{low}$ (Hz)	430
$F_{High}$ (KHz)	180

#### D4. Discussions



- The error between the calculated and measured values is vast (reaches 50% for the gain!) and this is due to the malfunctioning MOSFET that we got.  
 Note: As indicated in the datasheet of the BS170 some MOSFETs may have a  $V_L$  as low as 0.8V and this may be the problem (When we measured  $V_T$  in the first part we did that on a different MOSFET).
- At low and high frequencies the capacitors in the circuit will affect the amplification bandwidth. At low frequencies, the capacitors will act as open circuits ( $Z_c = \frac{1}{j\omega C}$ ) and thus the signal source would be disconnected from the amplifier (i.e. the MOSFET) and the output would drop to values as low as zero. However, at high frequencies the capacitors would become short circuits and thus affecting the biasing of the MOSFET and taking it from the saturation region.

- When the amplitude of the signal becomes large if the MOSFET was connected, the biasing of the MOSFET will change at the extremities (or the high values) of the signals to cutoff and triode and thus the signal would be distorted. In order not to get distortion the two conditions  $V_{GS(\text{Total})} > V_T$  and

$$V_{DS(\text{Total})} > V_{GS(\text{Total})} - V_T .$$

### E. MOSFET as a current source

#### E1. Circuit Diagrams:

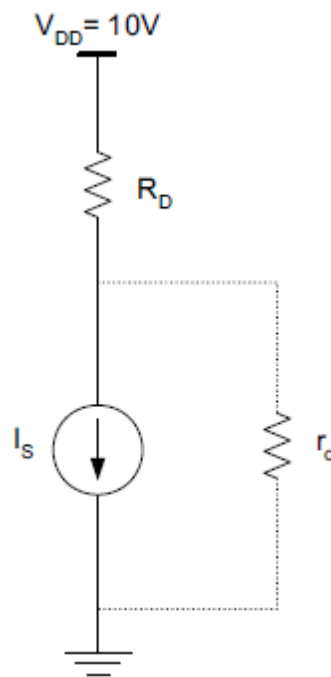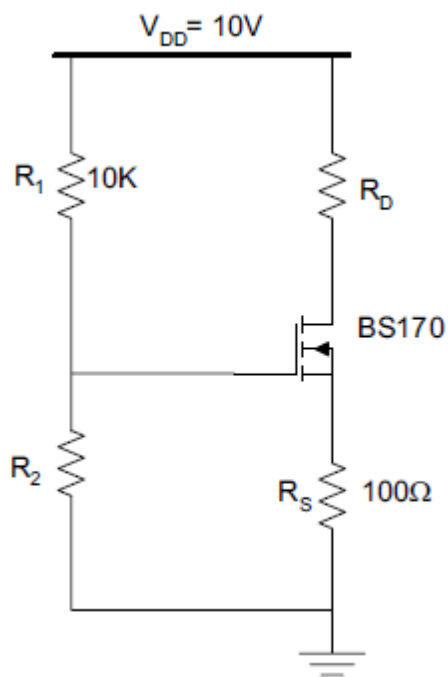

#### E2. Detailed Experimental Procedure:

Since the MOSFET is to be operated as a current source then it must be biased to the saturation region where the i-v relation is (neglecting channel length modulation):

$$i_D = \frac{1}{2} k (V_{GS} - V_T)^2$$

$$i_D = \frac{1}{2} k (V_G - R_s i_D - V_T)^2$$

$$10^{-2} = 0.122 (V_G - 1 - 1.826)^2 \quad (i_D \text{ is given as } 10\text{mA})$$

$$\Rightarrow V_G = 3.1123 \text{ but } V_G = \frac{R_2}{R_2 + 10K} 10$$

$$\therefore R_2 = 4.5186 K\Omega$$


So setup the above circuit with  $R_2 = 4.5 K \Omega$  and vary  $R_D$  from 0 to 1000 K  $\Omega$  while recording the drain current and drain to source voltage.

E3. Measurements and Results:


$R_D (\Omega)$	$I_D (mA)$	$V_{DS} (V)$
0	9.85	9.9
100	9.83	7.9
220	9.81	6.8
330	9.8	5.7
470	9.78	4.4
560	9.76	3.56
680	9.7	2.54
820	9.67	1.17
1000	9.63	0.25



E4. Discussions:

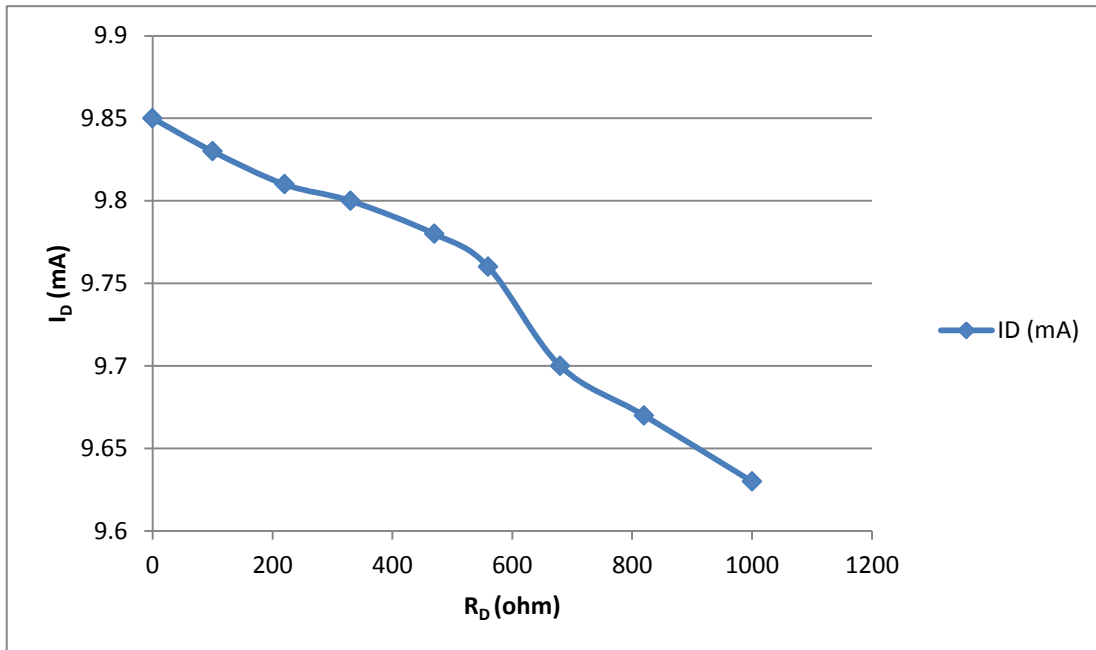

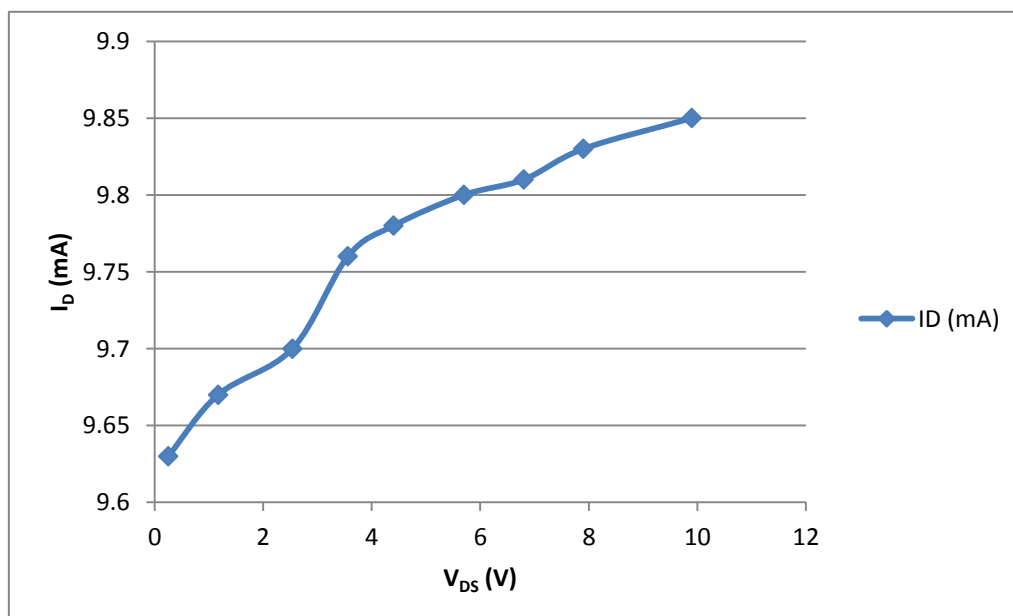- The region where  $I_D$  is constant can be approximated by the part of the curve with least value for the derivative; this  $I_D$  is constant between 220 and 560 ohms (The deviation is not given, so approximations are arbitrary).
- The value of  $I_D$  is about 9.78 mA.



- $I_D$  is approximately constant for the range 4.4-9.9 V.
- This range corresponds to the saturation region since  $I_D$  is independent of  $V_{DS}$  (The small variation is due to channel length modulation).
- $R_O = \frac{1}{\frac{\delta i_D}{\delta V_{DS}}} = \frac{1}{\text{slope}} = 7 k\Omega$  where  $R_O$  is the output resistance in saturation.

## VI- References:

- Sedra Smith – Microelectronic Circuits 6<sup>th</sup> Edition
- Lecture Notes

## VII- Mistakes and Problems faced in the lab:

We had initially a malfunctioning MOSFET, so the instructor replaced it with another malfunctioning one which wasted a lot of our time.

---

*“I HAVE NEITHER GIVEN NOR RECEIVED AID ON THIS REPORT NOR HAVE I CONCEALED ANY VIOLATION OF THE AUB STUDENT CODE OF CONDUCT.”*

14