

# Experiment 3:

## Voltage Dividers and Thevénin's Theorem

---

### In-Lab Report

#### A. Voltage divider circuits

Build the circuit and then record the measured values in the Table below, the bleeder current  $I_b$ , the voltages  $V_B$  and  $V_A$ , and the load resistance  $R_L$  for each of the load conditions in part A.

Measured Values					
V(V)	$I_L$ (mA)	$I_1$ (mA)	$V_B$ (V)	$V_A$ (V)	$R_L$ ( $\Omega$ )
10	0				
10	2				
10	4				
10	6				

#### B. Voltage Divider Design

Connect the circuit. Measure the required voltages and currents and record them in a table.

Measured Values	
$V_L$ (V)	
$I_L$ (mA)	
$I_{bleeder}$ (mA)	

#### C. Thevénin's Theorem

- Connect the circuit of Fig. C.3 and measure the open-circuit voltage between points A and B of this circuit.

Measured Value	
$V_{TH}$ (V)	

- With the 15 V source in Fig. C.3 replaced by a short -circuit, measure the resistance between the AB terminals with the digital multimeter.

*Experiment 3: Voltage Dividers and Thevénin's Theorem*

Measured Value	
$R_{TH}(\Omega)$	

- Connect the load resistances of  $1\text{ K}\Omega$  and  $4.7\text{ K}\Omega$  in turn in the circuit of Fig.C.3 and measure the corresponding load voltages.

Measured Values	
	$V_{load}(V)$
$1\text{ K}\Omega$	
$4.7\text{ K}\Omega$	

- Find  $R_{TH}$  using the matched-load method; that is, use a  $5\text{ K}\Omega$  potentiometer as a variable resistance between the AB terminals of the circuit of Fig. C.3. Vary the resistance until load voltage drops to half of the measured  $V_{TH}$  (open-circuit voltage.) Then disconnect the load resistance and measure its resistance with the multimeter.

Measured Value	
$R_{TH}(\Omega)$	