

**American University of Beirut  
Department of Electrical and Computer  
Engineering**

**EECE 210 – Electric Circuits  
Fall 2018 (November 9) – Quiz 2  
Version A**

**One A4 sheet with notes (no solutions)  
No Programmable Calculators  
No Wireless Devices**

**Only work written on this set of question  
sheets will be graded.**

**DURATION: 90 MINUTES**

***APPLY TIME MANAGEMENT!***

**TOTAL OF 100 POINTS**

**NUMBER OF PAGES: 9**


**NUMBER OF PROBLEMS: 8**

**NO QUESTIONS ASKED DURING THE QUIZ, EXCEPT FOR SIMPLE LOGISTICS  
SUCH AS EXTRA SCRATCH PAPER**

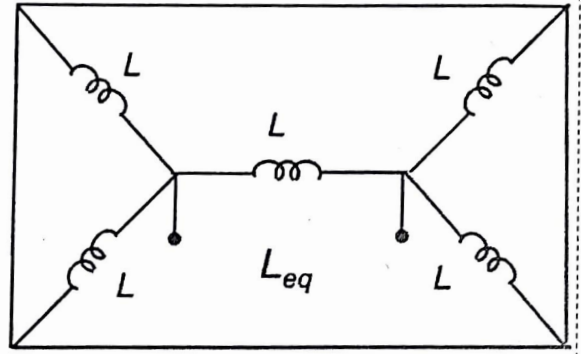**Problem 1** (5 pts)

Find  $L_{eq}$  in the circuit below, if  $L = 6\text{ H}$ . Circle the best answer.


- 3 H
- 4 H
- 6 H
- 1/3 H
- 1/4 H
- 1/6 H



**Problem 2** (10 pts)


A. (5 pts)  $V_T = 20\text{ V}$ , Find  $|V_{Th}|$  in the circuit without  $R$ . Circle the best answer.

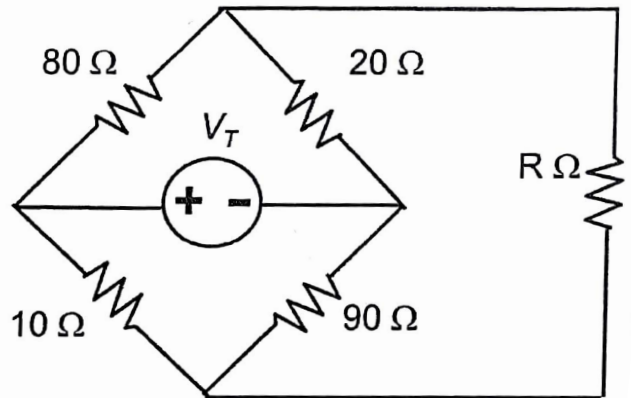- 1 V
- 7 V
- 10 V
- 14 V
- 20 V
- 25 V
- 28 V
- 40 V



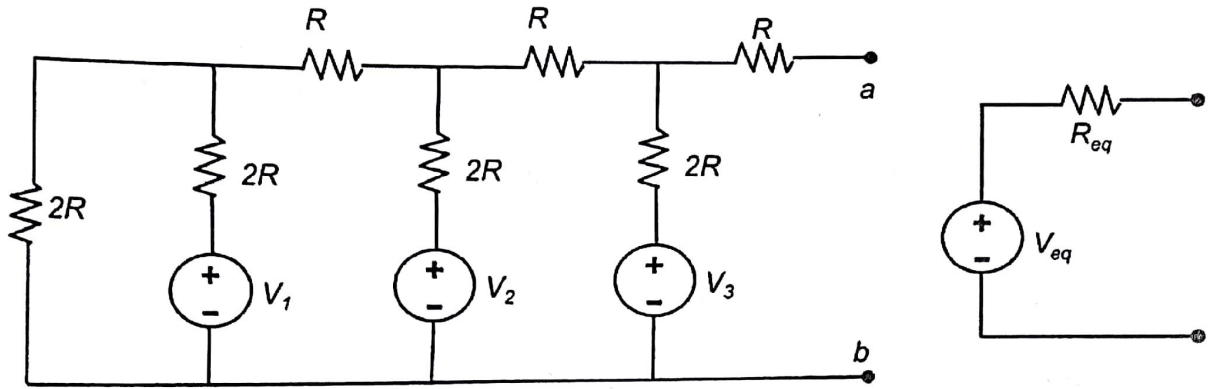B. (5 pts) Find the value of  $R$  for maximum power transfer.

- 10  $\Omega$
- 20  $\Omega$
- 25  $\Omega$
- 30  $\Omega$
- 35  $\Omega$
- 40  $\Omega$
- 50  $\Omega$
- 75  $\Omega$



**Problem 3 (5 pts)**


The circuit on the left hand side is replaced by an equivalent circuit as shown on the right. Use multiple source transformations to find an expression for  $V_{eq}$  in terms of  $R$ ,  $V_1$ ,  $V_2$ , and  $V_3$ :

- $V_1/2 + V_2/2 + V_3/2$
- $V_1/2 + V_2/4 + V_3/8$
- $V_1/8 + V_2/4 + V_3/2$
- $V_1/4 + V_2/2 + V_3$
- $V_1 + V_2 + V_3$
- $(V_1/8 + V_2/4 + V_3/2)/R$
- $(V_1/2 + V_2/2 + V_3/2)/R$
- $(V_1/2 + V_2/4 + V_3/8)/R$

**Problem 4 (15 pts)**

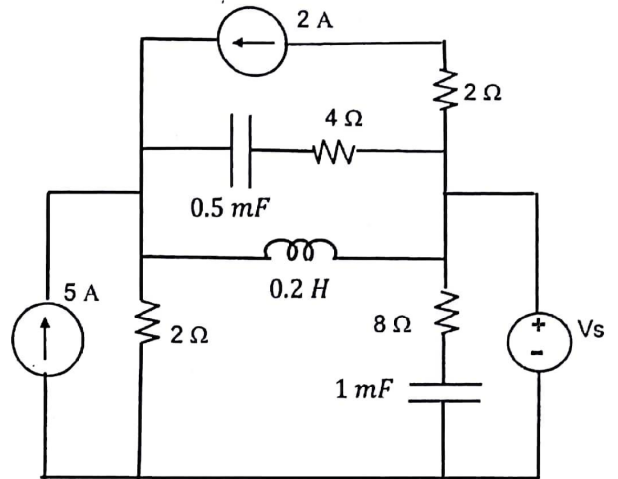A. (5 pts) The circuit is in DC steady state.  $V_s=80$  V. Find the energy stored in the  $1\text{mF}$  capacitance. Circle the best answer.

- 0 J,
- 0.8 J,
- 1.8 J,
- 3.2 J,
- 16.9 J,
- 17.7 J,
- 52.9 J,
- 54.7 J,
- 108.9 J,
- 112.1 J



B. (5 pts) Find the energy stored in the  $0.5\text{mF}$  capacitance. Circle the best answer.

- 0 J,
- 0.8 J,
- 1.8 J,
- 3.2 J,
- 16.9 J,
- 17.7 J,
- 52.9 J,
- 54.7 J,
- 108.9 J,
- 112.1 J


C. (5 pts) Find the energy stored in the inductance. Circle the best answer.

- 0 J,
- 0.8 J,
- 1.8 J,
- 3.2 J,
- 16.9 J,
- 17.7 J,
- 52.9 J,
- 54.7 J,
- 108.9 J,
- 112.1 J

### Problem 5 (15 pts)

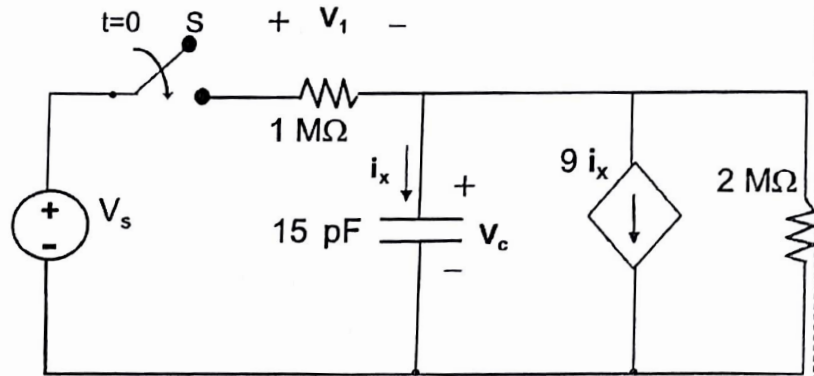- A. (5 pts) The switch has been open for a long time and closes at  $t=0$ .  $V_s=20$  V. Find  $v_1(0^+)$  (voltage over the  $1\text{ M}\Omega$  resistance). Circle the best answer.

- 0 V
- 6.7 V
- 16.7 V
- 20 V
- 26.7 V
- 50 V
- 66.7 V
- 80 V



- B. (5 pts) Find  $i_x(0^+)$ . Circle the best answer.

- 0 A
- 2.0  $\mu\text{A}$
- 5.0  $\mu\text{A}$
- 6.67  $\mu\text{A}$
- 8.0  $\mu\text{A}$
- 16.67  $\mu\text{A}$
- 20.0  $\mu\text{A}$
- 26.67  $\mu\text{A}$
- 50.0  $\mu\text{A}$
- 80.0  $\mu\text{A}$


- C. (5 pts) Find  $v_1(\infty)$  (voltage over the  $1\text{ M}\Omega$  resistance). Circle the best answer.

- 0 V
- 6.7 V
- 16.7 V
- 20 V
- 26.7 V
- 50 V
- 66.7 V
- 80 V

### Problem 6 (17 pts)

For the circuit below,  $V_s = 10V$ .

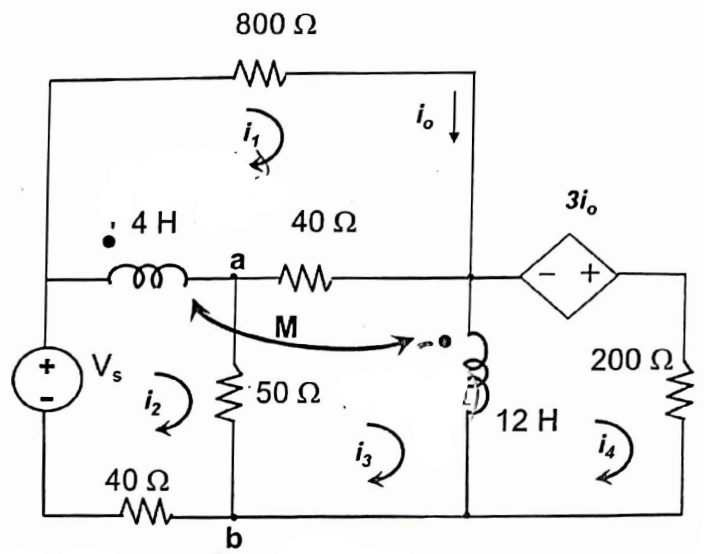- a) (8 pts) Write expressions for each mesh in the circuit in terms of the mesh currents,  $M$  and  $V_s$  (i.e. 4 expressions). Note to simplify each expression (group like variables).




b) (5 pts) Redraw the circuit for when  $t \rightarrow \infty$ ,

c) (4 pts) In the circuit of b), remove the  $50 \Omega$  resistor, and then find the Thevenin equivalent circuit with respect to terminals a-b.

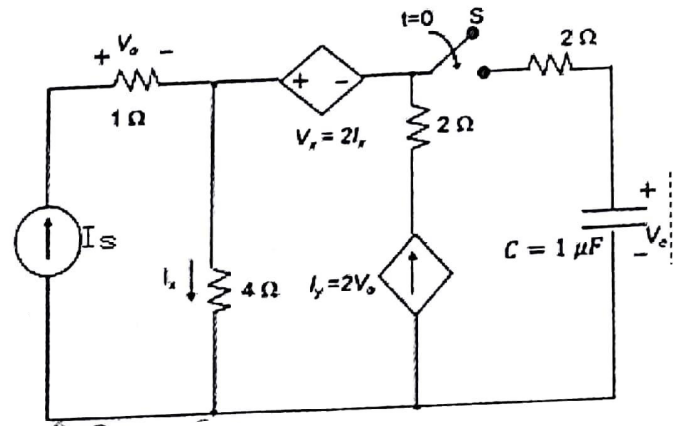• **Problem 7 (17 pts)**

$I_s = 5A$ . Find the voltage  $V_c(t)$  if the capacitor was uncharged before the switch is closed. (Hint: find the Thevenin or Norton equivalent circuit connected to the capacitance.)





• **Problem 8 (16 pts)**

Let  $V_1=8$  Volts. If you are told that for some value of  $V_2=M$  volts, the output voltage  $V_x=1$  Volts, Find  $V_x$  if the voltage  $V_2$  is doubled to  $2M$  volts.

