


EECE 370 Handout 2

Three-Phase Circuits – Appendix A

What are the advantages that *three-phase* ac power systems have over *single-phase* ac power systems?

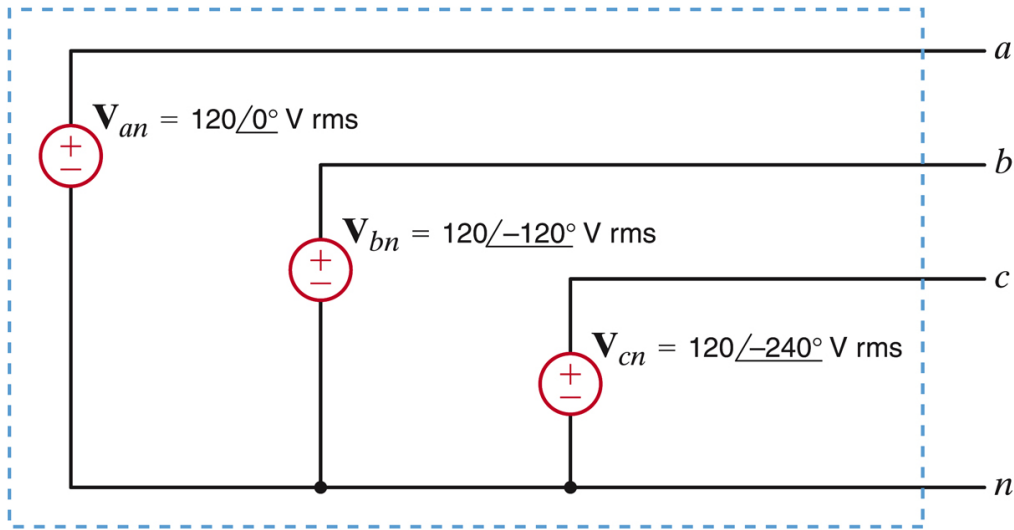1. More power per kilogram.
2. Instantaneous power is constant.
3. Induction motors start without special auxiliary starting windings.

Three-phase circuits are those in which the forcing function is a three-phase system of voltages



What are the conditions for a three-phase system of voltages to be *balanced*?

1-

2-


If the loads are such that the currents produced by the voltages are also balanced, the entire circuit is referred to as a balanced.

Example:

Find the expression of the instantaneous power in a three-phase circuit.


Three-Phase Connections

Balanced three-phase voltage source

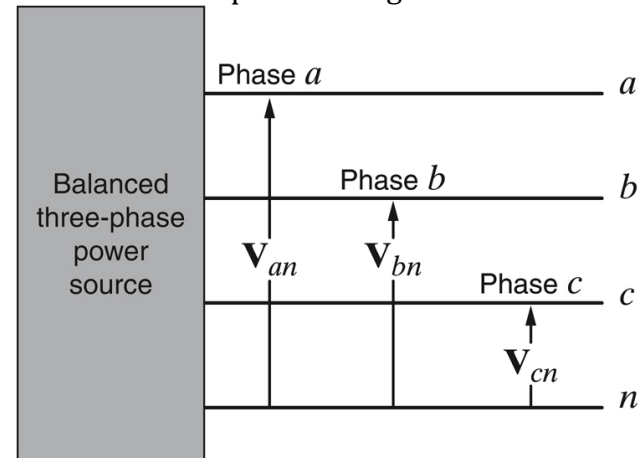


Line-to-neutral voltages

Y-connected loads

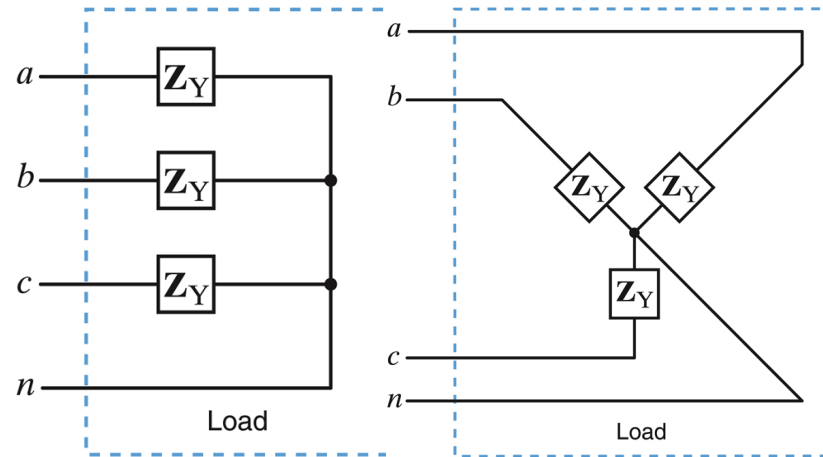


Δ -connected loads

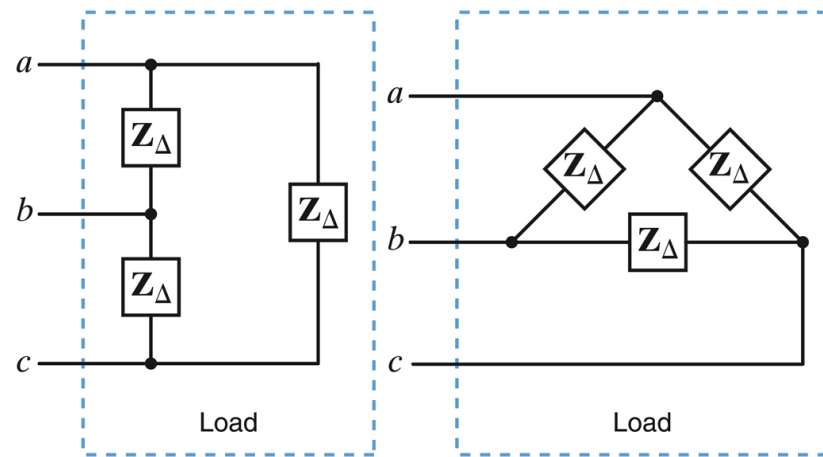

Source/Load Connections

**Balanced Y-Y Connection*

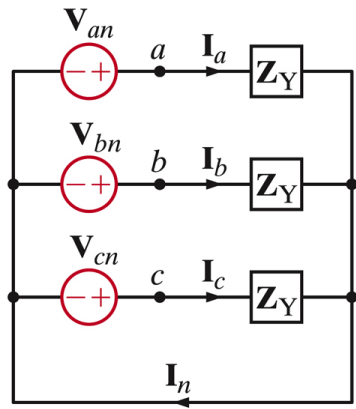

Example:

Positive sequence, balanced Y-Y three-phase circuit.



Source $V_\phi = 120$ Vrms. $\hat{Z}_{line} = 1 + j1 \Omega$. $\hat{Z}_Y = 20 + j10 \Omega$.

Determine the line currents.

Determine the phase voltages at the load.


Determine the line voltages at the load.

* Δ -connected Source

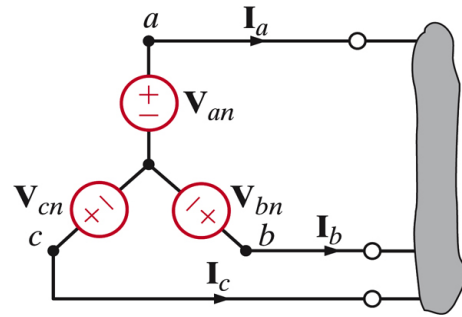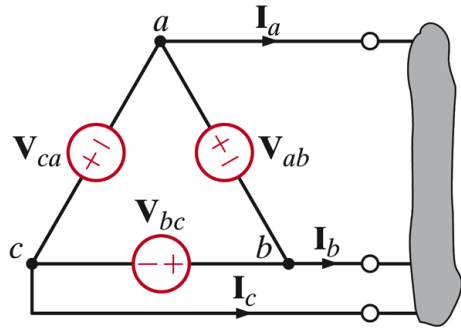


Example:

Determine the line voltages at the load.

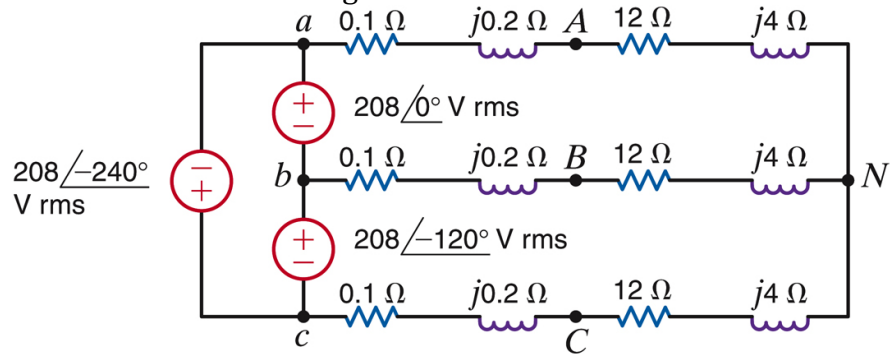

* Δ -connected Load

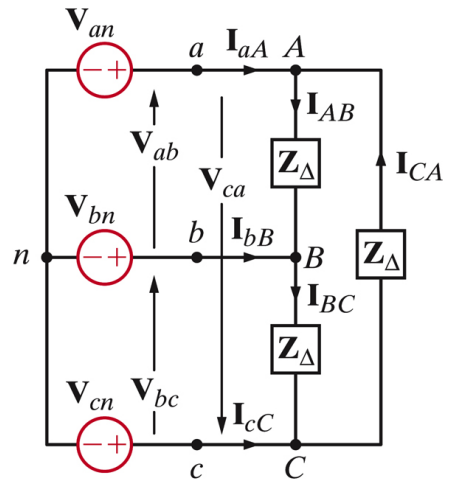

Example:

A delta-connected load consists of 10Ω resistance in series with 20 mH inductance. The source is Y-connected, abc sequence, 60 Hz , $\tilde{V}_{an} = 120\angle 30^\circ$ Vrms. Determine the line currents and the phase currents in the Δ -connected load.

Power Relationships

Per-phase real power:

Per-phase reactive power:



In terms of phase/line quantities

Total (three-phase) real power:

Total (three-phase) reactive power:

Total (three-phase) complex power:

Total (three-phase) apparent power:

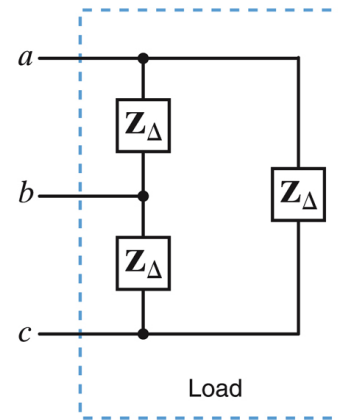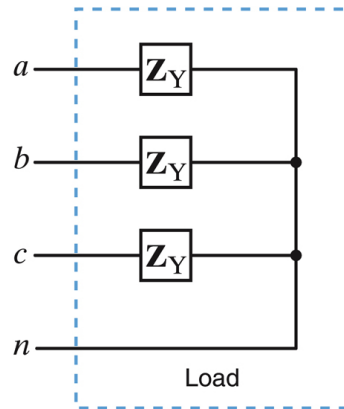

Example:

A three-phase balanced wye-delta system has a line voltage magnitude of 208 Vrms. The line impedance is negligible. The total real power absorbed by the load is 1200 W and the power factor angle of the load is 20° . Determine the magnitude of the line current and the value of the load impedance per phase in the delta.

Example:

The following balanced three-phase loads are served by a balanced three-phase source:

Load 1: 24 kW at PF = 0.6 lagging


Load 2: 10 kW at PF = 1

Load 3: 12 kVA at PF = 0.8 leading

The magnitude of the line voltage at the load is 208 Vrms, and the line impedance is $0.05 + j0.02 \Omega$.

- a) Determine the magnitude of the line current and the combined power factor at the load.
- b) Determine the magnitude of the line voltage and the power factor at the source.

Power Factor Correction

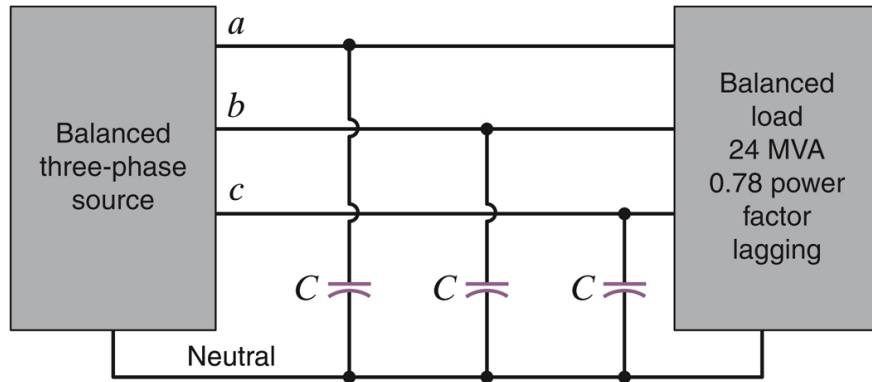

Example: in the previous diagram, $f = 60$ Hz, $V_L = 34.5$ kVrms, required PF = 0.9 lagging. Find C .