

EECE 370 – Quiz 1 – Fall 2011 – Problems

A 40 kVA, 480/4800 V, step-up transformer has the following equivalent circuit parameters:

$$R_p = 25 \text{ m}\Omega \quad X_p = 57.5 \text{ m}\Omega \quad (\text{Low-voltage side})$$

$$R_s = 2.5 \text{ }\Omega \quad X_s = 5.75 \text{ }\Omega \quad (\text{High-voltage side})$$

$$R_c = 500 \text{ }\Omega \quad X_M = 100 \text{ }\Omega \quad (\text{Low-voltage side})$$

Use the approximate equivalent circuit referred to the primary (low-voltage) side to answer the following two questions.

1. If the transformer is operating at full load with a power factor of 0.8 lagging, find the magnitude of the applied voltage to the primary winding (in V).

- a. 489.1 **
- b. 498.3
- c. 507.5
- d. 516.7
- e. 526.1

```
S=40*1E3
Rp=25E-3
Rs=2.5
Xp=57.5E-3
Xs=5.75
Rc=500
XM=100
```

```
Reqp=Rp+(480/4800)^2*Rs
Xeqp=Xp+(480/4800)^2*Xs
```

```
Ip=S/480
```

```
Vp=480+(Reqp+i*Xeqp)*Ip*(0.8-0.6i)
```

```
mag_Vp=abs(Vp)
```

2. If a voltage of 480 V is applied to the primary winding while the secondary winding is connected to a resistive load that draws the rated current, find the total losses (in W)?

- a. 9141.4
- b. 6016.4
- c. 3585.8
- d. 1849.7
- e. 808.0 **

```
Psc=Reqp*Ip.^2 + 480^2/Rc
```

3. A 75 kVA, 220/480-V single phase power transformer has a per-unit core-loss resistance (R_c) of 100 pu and a per-unit magnetizing reactance (X_m) of 80 pu. Find the excitation current (in A) when rated voltage is applied to the low-voltage winding.
- 2.2727 - j2.8409
 - 3.4091 - j4.2614 **
 - 4.5455 - j5.6818
 - 5.6818 - j7.1023
 - 6.8182 - j8.5227

$S=75*1E3$
 $R_c_pu=100$
 $X_m_pu=80$

$I_{ex_pu}=1/R_c_pu+1/(i*X_m_pu)$

$I_{ex}=I_{ex_pu}*S/220$

The following data were obtained when a 25-kVA, 2300/460 V, 50 Hz transformer was tested:

	Voltage (V)	Current (A)	Power (W)
Open-circuit test	460	1.5	550
Short-circuit test	108.7	10.87	750

Refer to this data for questions 4 and 5.

4. Find the magnetizing reactance (X_m) referred to the low voltage side (in Ω).
- 376.4
 - 404.5
 - 445.0
 - 507.8 **
 - 621.0

$V_{oc}=460$
 $I_{oc}=1.5$
 $P_{oc}=550$

$S_{oc}=V_{oc}*I_{oc}$
 $Q_{oc}=\sqrt{S_{oc}^2-P_{oc}^2}$
 $X_{mL}=V_{oc}^2./Q_{oc}$

5. Find the equivalent series resistance (R_{eq}) referred to the low voltage side (in $m\Omega$).
- 270.8
 - 253.9 **
 - 237.0
 - 220.0

e. 203.1

```
Vsc=108.7  
Isc=10.87  
Psc=750
```

```
ReH=Psc/Isc^2  
ReL=ReH*(460/2300)^2*1000
```

6. A 6.6 kVA, 440/220-V, 50 Hz step-down transformer has an equivalent series impedance of $3 + j4 \Omega$ referred to the primary (high-voltage) side. The transformer is operating at full load with a power factor of 0.6 leading. Determine the efficiency of the transformer (in %).
- a. 94.6
 - b. 92.1
 - c. 89.8
 - d. 87.6
 - e. 85.4 **

```
S=6.6*1E3  
I=S/440  
Pout=S*0.6  
Pin=Pout+3*I.^2  
eff=Pout./Pin*100
```

7. Fig. 1 shows a ferromagnetic core with a depth of 10 mm having a small air gap of 0.5 mm. The relative permeability of the core is 2000 and the coil has $N_T = 500$ turns and carries a current of $I = 1.5$ A. Other dimensions are shown in the figure. The fringing in the air gap increases its effective cross-sectional area by 5%. What is the magnetic flux density in the airgap?
- a. 1.422 T
 - b. 1.675 T **
 - c. 1.342 T
 - d. 1.257 T
 - e. 1.109 T

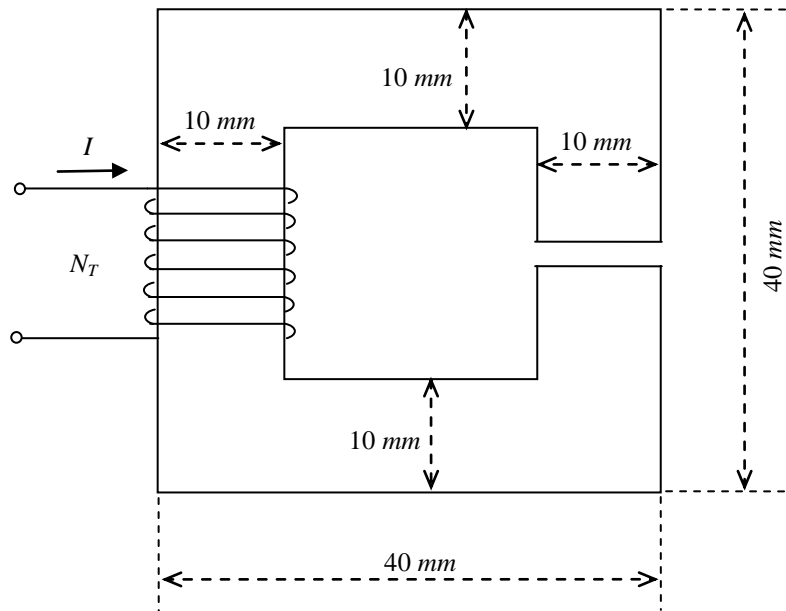


Fig. 1: Simple Ferromagnetic core

```

Ac=10E-3*10E-3
Ag=1.05*Ac
g=0.5*1E-3
lc=4*30E-3-g
u0=4*pi*1E-7
u=2000*u0
N=500
I=1.5

```

```

Phi=N*I./(lc./(u*Ac)+g/(u0*Ag))
Bg=Phi./Ag

```

8. Fig. 2 shows a non-uniform ferromagnetic core with dimensions as shown on the figure with the depth of the core being 50mm. The air gap width is $L_G = 0.5\text{mm}$. The relative permeability of the core is 3500 and the number of turns in each coil is $N_T = 200$ turns. The fringing in the air gap increases its effective cross-sectional area by 5%. What is the maximum current (I_{max}) that will keep the highest flux density in the core below a saturation level of 1.2T?

- a. 0.672 A
- b. 0.781 A
- c. **0.454 A** **
- d. 0.596 A
- e. 0.530 A

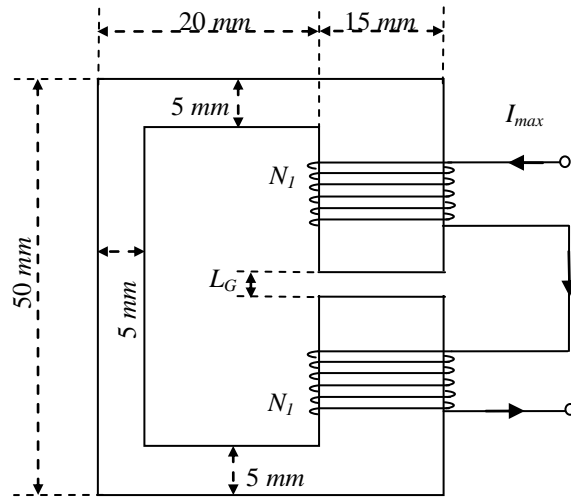


Fig. 2: Non-uniform core with two windings

$$u_0 = 4 \cdot \pi \cdot 10^{-7}$$

$$u = 3500 \cdot u_0$$

$$l_{c1} = ((50-5) + 2 \cdot ((20-2.5) + 7.5)) \cdot 10^{-3}$$

$$A_{c1} = 5 \cdot 10^{-3} \cdot 50 \cdot 10^{-3}$$

$$g = 0.5 \cdot 10^{-3}$$

$$l_{c2} = (50-5) \cdot 10^{-3} - g$$

$$A_{c2} = 15 \cdot 10^{-3} \cdot 50 \cdot 10^{-3}$$

$$A_g = 1.05 \cdot A_{c2}$$

$$N_1 = 200$$

$$B_1 = 1.2$$

$$\Phi = B_1 \cdot A_{c1}$$

$$I_{max} = (l_{c1} / (u \cdot A_{c1}) + l_{c2} / (u \cdot A_{c2}) + g / (u_0 \cdot A_g)) \cdot \Phi / (2 \cdot N_1)$$

Consider the one-line diagram of a balanced three phase system shown in Fig. 3. Load 1 is Y-connected and has a phase impedance is $Z_{\phi 1} = 4 \angle 35^\circ \Omega$, and Load 2 is Δ -connected and has a phase impedance of is $Z_{\phi 2} = 8 \angle 30^\circ \Omega$. The capacitor bank is Δ -connected and has a phase impedance of $Z_{\phi C} = 24 \angle -90^\circ \Omega$. This data will be used in the following two problems.

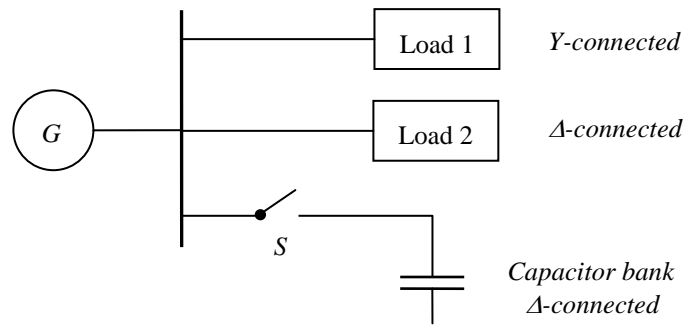


Fig. 3: Balanced three phase system

9. When switch S is open and the generator line voltage is 480 V, what are the active and reactive powers supplied by the generator?

- a. $122.01 + j76.24 \text{ kVA}$ **
- b. $113.69 + j71.44 \text{ kVA}$
- c. $91.20 + j56.99 \text{ kVA}$
- d. $128.61 + j80.37 \text{ kVA}$
- e. $84.99 + j53.40 \text{ kVA}$

$$Z_1=4$$

$$\theta_1=35^\circ$$

$$Z_2=8$$

$$\theta_2=30^\circ$$

$$Z_c=24$$

$$V_L=480$$

$$P_T=3 \cdot (V_L/\sqrt{3})^2 \cdot \cos(\theta_1) + 3 \cdot V_L^2 \cdot \cos(\theta_2)$$

$$Q_T=3 \cdot (V_L/\sqrt{3})^2 \cdot \sin(\theta_1) + 3 \cdot V_L^2 \cdot \sin(\theta_2)$$

$$S_T=(P_T + jQ_T) / 1000$$

10. When switch S is closed and the line current in Load 1, $I_{L1} = 68 \angle -35^\circ \text{ A}$, what is the reactive power supplied by the capacitor?

- a. 20.81 kVAr
- b. 27.74 kVAr **
- c. 41.62 kVAr
- d. 33.29 kVAr
- e. 23.78 kVAr

$$I_{L1}=68$$

$$V_L=\sqrt{3} \cdot I_{L1} \cdot Z_1$$

$$Q_c=3 \cdot V_L^2 \cdot \cos(\theta_c) / 1000$$