

(4)

1. a)

→ Length and area of air gap =

$$l_g = 0.1 \text{ cm} \quad a_g = 45 \times \frac{\pi}{180} \times 13.1 \times 20 = 205.8 \text{ cm}^2$$

→ Rotor

$$l_r = \frac{13 \times \cos 22.5 \times 2 + 26}{2} = 25 \text{ cm}$$

$$a_r = 13 \times 2 \sin 22.5 \times 2 \times 20 = 199 \text{ cm}^2 = 0.02 \text{ m}^2$$

→ Poles

$$l_p = 15 - 13 - 0.1 = 1.9 \text{ cm}$$

$$a_p \approx a_g = 13.1 \times 2 \sin 22.5^\circ \times 2 \times 20 = 200.5 \text{ cm}^2$$

→ Yoke

$$l_y \approx 15 \times \pi = 47.1 \text{ cm}$$

$$a_y = 0.5 \times 20 = 10 \text{ cm}^2$$

b) If the steel is unsaturated,

$$\mu_s = \frac{0.8}{100} = 8 \times 10^{-3} \text{ H/m} \quad \mu_0 = 4\pi \times 10^{-7} \text{ H/m}$$

calculate reluctances

$$R_g = \frac{1}{\mu_0} \times \frac{l_g}{a_g} = \frac{1}{4\pi} \times \frac{0.1 \times 10^{-2}}{205.8 \times 10^{-4}} = 38667 \text{ A/Wb}$$

$$R_r = \frac{1}{\mu_s} \times \frac{l_r}{a_r} = \frac{1}{8 \times 10^{-3}} \times \frac{25 \times 10^{-2}}{199 \times 10^{-4}} = 1570 \text{ A/Wb}$$

$$B_g = \frac{\phi}{a_g} = \frac{18.42 \times 10^{-4}}{205.8 \times 10^{-4}} = 0.0895 \text{ T}$$


flux densities:

$$\phi = \frac{E \times 2}{R_g} = \frac{150 \times 2}{108578} = 18.42 \times 10^{-4} \text{ Wb}$$

Machine flux = $R_c = 79134$

$$R_{og} = 2R_g + 2R_p + R_r + \frac{R_y}{2} = 108578 \text{ A/Wb}$$

c) Calculate equivalent reluctance =

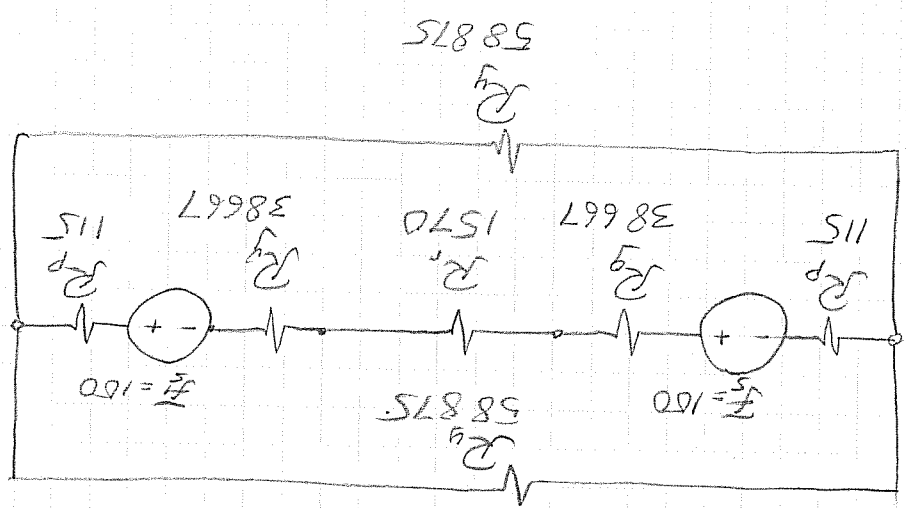

The magnetic circuit is:

$$E_s = 50 \times 2 = 100 \text{ A}$$

$$R_y = \frac{1}{\mu_0} \times \frac{1}{a_y} = \frac{1}{8 \times 10^{-3}} \times \frac{1}{47.1 \times 10^{-2}} = 58875 \text{ A/Wb}$$

$$R_p = \frac{1}{\mu_0} \times \frac{1}{a_p} = \frac{1}{8 \times 10^{-3}} \times \frac{1}{200.5 \times 10^{-2}} = 118 \text{ A/Wb}$$

$$I_{\max} = \frac{2 \times 50}{47.1 + 79.134 \times 16 \times 10^{-4}} = 1.74 \text{ A}$$

$$F_s = (F_y + R_c \phi_g) / 2 = NI_{\max} \Rightarrow$$

$$2 F_s = R_c \phi_g + F_y = 2 NI_{\max}$$

$$F_y = \phi_y \times R_y = 8 \times 10^{-4} \times 58.875 = 47.1 \text{ AT}$$

The required mmf across yoke is =

$$\phi_g = 2 \phi_y = 16 \times 10^{-4} \text{ Wb}$$

$$\phi_y = 0.8 \times 10 \times 10^{-4} = 8 \times 10^{-4} \text{ Wb}$$

at the knee of curve.

d) To obtain the maximum current we set the flux density in the yoke to 0.8 T


Flux density in the yoke is higher than the knee of the curve and hence, the yoke is saturated.

$$B_y = \frac{18.42 \times 10^{-4}}{2 \times 10 \times 10^{-4}} = 0.921 \text{ T}$$

$$B_p = \frac{205.8 \times 10^{-4}}{18.42 \times 10^{-4}} = 0.0895 \text{ T}$$

$$B_p = \frac{18.42 \times 10^{-4}}{199 \times 10^{-4}} = 0.0926 \text{ T}$$

2. a) The per-phase equivalent circuit:

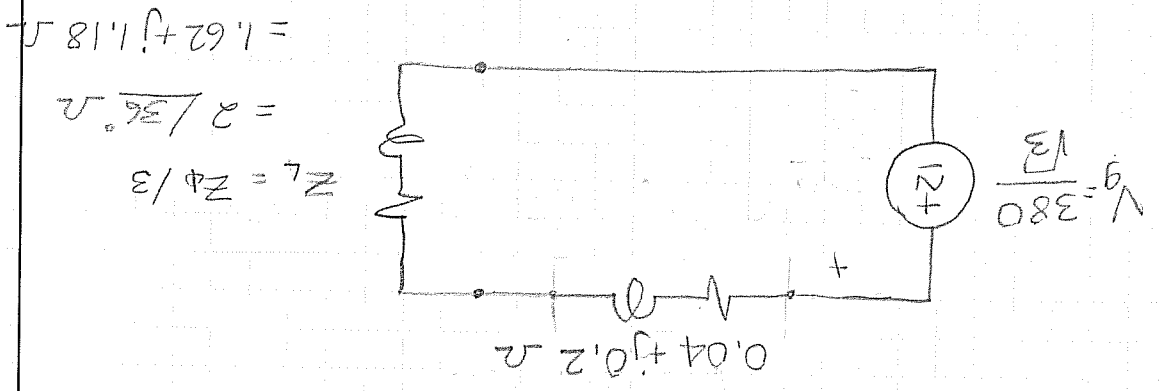

b) Current in transmission line:

First calculate load current or generator current:

$$I_L = V_g / (Z_L + Z_T) =$$

$$= \frac{380 \times \sqrt{3}}{1} \times \frac{(1.62 + j1.18) + (0.04 + j0.2)}{}$$

$$= 78.38 - j65.03 = 101.8 \angle -39.68^\circ$$

$$V_L = I_L Z_L = 101.8 \angle -39.68^\circ \times 2 \angle 36^\circ$$

$$= 203.6 \angle -3.68^\circ \text{ V}$$

$$|V_{\phi L}| = 203.6 \times \sqrt{3} = 352.6 \text{ V}$$

$$|\Delta V + I| = |219.4 - 203.6 \angle -3.68^\circ| = 20.8 \text{ V} = 9.48\%$$

$\Delta V = 47.5 \text{ V}$

$V_L = 352.6$

$I_L = 176.3$

$V_g = 380 \text{ V}$

7

c) Active and reactive power supplied to

the load =

$$P_L + jQ_L = 3V_L I_L^* = 3 \times 203.6 \sqrt{-3.69} \times (101.8 \sqrt{39.68})$$

$$= 62179 \sqrt{36}^\circ$$

$$= 50304 + j36548 \text{ VA}$$

Active and reactive power delivered by

generator =

$$P_G + jQ_G = 3V_G I_L^* = 3 \times 380 \sqrt{101.8 \sqrt{39.68}}$$

$$= 67005 \sqrt{39.68}^\circ$$


$$= 51569 + j42783 \text{ VA}$$

Active losses in the transmission lines =

$$P_{\text{losses}} = 51569 - 50304 = 1265 \text{ W}$$

$$PF_g = \frac{51569}{67005} = 0.77$$

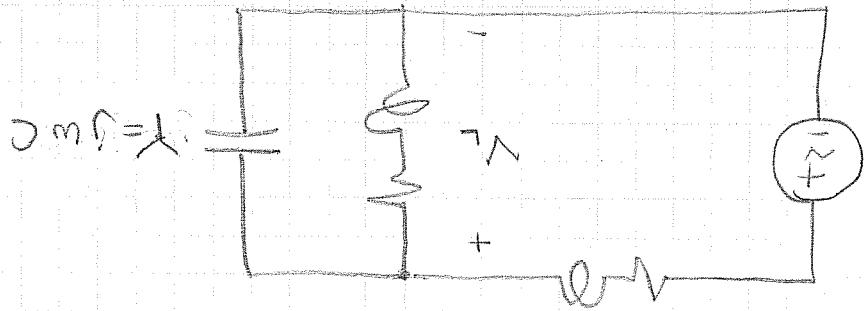The power factor of the load may be increased by adding a capacitor in parallel with the load. The size of the capacitor should be such that to provide reactive power be equal to that needed by the load:



The reactive power supplied by capacitor:

$$Q_c = 3V_L^2 = 3V_L^2 X_c$$

Let $Q_c = Q_L = 36548 \text{ VAR}$

$$\therefore X_c = Q_c = \frac{36548}{3V_L^2} = \frac{3 \times (203.6)^2}{36548} = 0.294 \Omega$$

$$C = \frac{1}{\omega X_c} = 9.35 \times 10^{-4} \text{ F} \approx 1 \text{ mF}$$

The new current is approximately given by:

$$I_L^{(n)} = I_L \cos \theta_L = 101.8 \times \cos 36^\circ = 82.4 \text{ A}$$

The new losses = $P_{\text{losses}}^{(n)} = 3I_L^2 R = 814 \text{ W}$

b) from the OC test we can calculate the components of excitation admittance:

$$Y_E = \frac{1}{R_c} - j \frac{1}{X_M}$$

$$Y_E = \frac{I_{oc}}{V_{oc}} \angle -\cos^{-1} PF_{oc}$$


$$PF_{oc} = \frac{127}{240 \times 1.07} = 0.495$$

$$Y_E = \frac{1.07}{240} \angle -\cos^{-1} 0.495 = 4.458 \angle -60.36^\circ$$


$$= (2.205 - j 3.875) \times 10^{-3} S$$

$$R_c = 453.5 \Omega$$

$$X_M = 258.1 \Omega$$

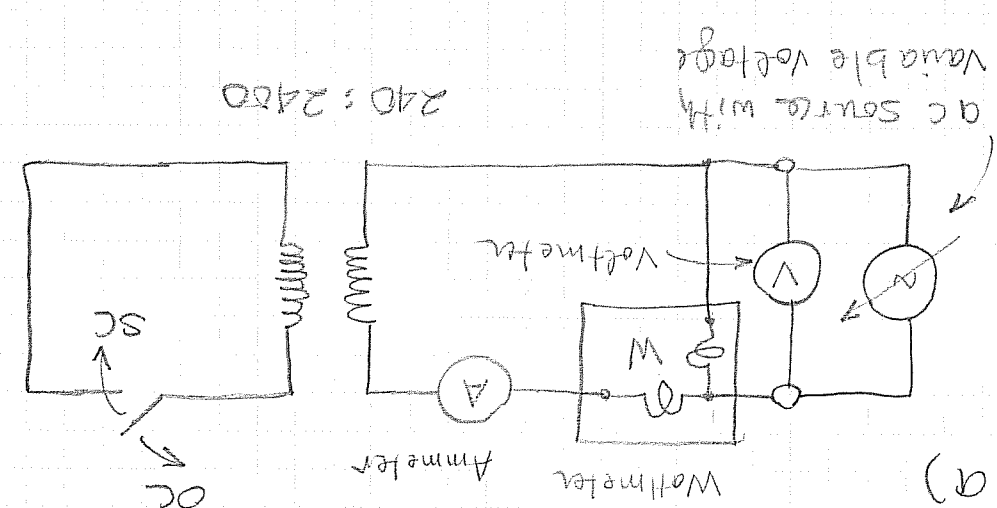

3. a)

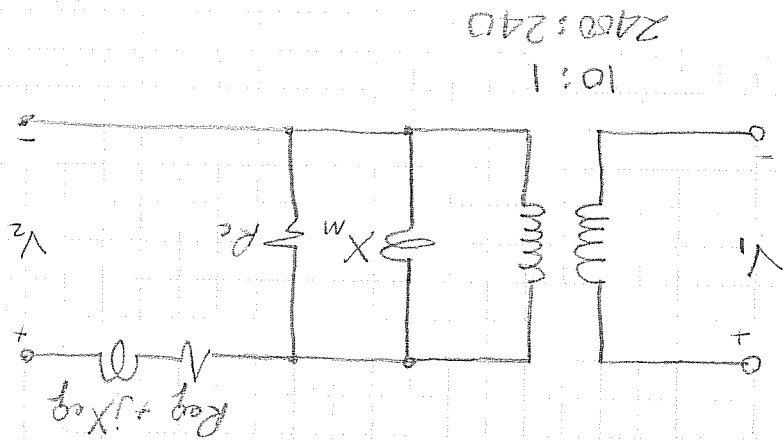

c)

referred to low voltage.

$$R_{0p} = 0.0408 \Omega \quad X_{0p} = 0.0555 \Omega$$

$$= 0.0408 + j0.0555 \Omega$$

$$= 0.06894 / +53.68^\circ$$

$$\therefore Z_{eq} = \frac{5.75}{83.4} / +65^\circ = 0.06894 / +53.68^\circ$$

$$PF_{sc} = \frac{P_{sc}}{V_{sc} I_{sc}} = 0.592$$

$$Z_{eq} = R_{0p} + jX_{0p} = \frac{V_{sc}}{I_{sc}} / -65^\circ = PF_{sc}$$

by the short circuit test:

The series impedance is essentially given

a)

Transformer efficiency at full load:

The full load current on low voltage is:

$$I_{2,fl} = \frac{20000}{240} / -31.79^\circ \text{ A}$$

$$V_{2,fl} = 240 \text{ V}$$

The transformer losses are:

$$P_{losses} = (I_{2,fl})^2 R_{eq} + \frac{V_{2,fl}^2}{R_c} = 283 + 127$$

$$= 410 \text{ W}$$

$$\eta = \frac{240 \times 83.3 \times 0.85}{240 \times 83.3 \times 0.85 + 410} = \frac{16993}{16993 + 410}$$

$$= 97.6\%$$

Voltage regulation is given by =

$$V_{2,nl} = \frac{q}{V_1}$$

$$\frac{q}{V_1} = V_{2,fl} + I_{2,fl} \times (R_{eq} + jX_{eq})$$

$$= 240 + (83.3 / -31.79^\circ) (0.06894 / 53.68^\circ)$$

$$= 240 + 5.7 / 21.9^\circ =$$

$$= 245.3 + j 2.13 = 245.3 / 0.5^\circ$$

$$0.2\%$$

(1)
4.

$$V_R = \frac{245.3 - 240}{240} = 0.022 = 2.2\%$$

a) Eddy currents flow in magnetic cores subjected to a time-varying flux. The flow of these current cause losses that are proportional to the path followed by these currents. These losses can be reduced by laminating the core along the path of the flux.

b) The excitation current has two components, the core loss current and magnetization current. The core loss current is in phase with the applied voltage and is modelled by a resistance in parallel with the source. The magnetization current lags the voltage by 90° and is thus modelled by an inductance in parallel with the magnetizing inductance, in parallel with the source.