

Corrections to PROBLEMS of Chapter 2 Sedra & Smith

Chapter 2 - Problems

2.1

The minimum number of pins required by dual-op-amp is 8. Each op-amp has 2 input terminals (4 pins) and one output terminal (2 pins). Another 2 pins are required for power.

Similarly, the minimum number of pins required by quad-op-amp is 14:

$$4 \times 2 + 4 \times 1 + 2 = 14$$

2.2

Refer to Fig. P2.2. $V_+ = V \frac{1K\Omega}{1M\Omega + 1K\Omega} = \frac{4}{1001} V$
 $V_o = A V_+ \Rightarrow A = \frac{4}{4/1001} = 1001$

2.3

The voltage at the positive input has to be $-3.000V$.

$$V_+ = -3.020V, A = \frac{V_o}{(V_+ - V_-)} = \frac{-2}{-3.020 - (-3)} = 100$$

2.4

#	V_1	V_2	$\frac{V_o}{V_1 - V_2}$	V_o	V_o/V_1
1	0.00	0.00	0.00	0.00	-
2	1.00	1.00	0.00	0.00	-
3	⊖ 1.00	⊕ 1.00	⊕ 1.00	1.00	
4	1.00	1.10	0.10	10.1	10.1
5	2.01	2.00	-0.01	-0.99	99
6	1.99	2.00	0.01	1.00	100
7	5.10	⊖ 5.10	⊕ 10.20	-5.10	

experiments 4, 5, 6 show that the gain is

approximately $100 V/V$. The missing entry for experiment #3 can be predicted as follows:

$$\textcircled{b} V_o = \frac{V_o}{A} = \frac{1.00}{100} = 0.01V$$

$$\textcircled{a} V_+ = V_2 - V_1 = 1.00 - 0.01 = 0.99V$$


The missing entries for experiment #7:

$$\textcircled{d} V_+ = \frac{-5.10}{100} = -0.051V$$

$$\textcircled{c} V_2 = V_+ + V_1 = 5.10 - 0.051 = 5.049V$$

All the results seem to be reasonable.

2.5

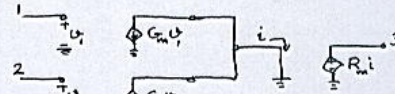

$$A = G_m R_m = 100 \times 10^{-3} \times 10^6 = 100,000 V/V$$

2.6

$$V_{CM} = 1V \sin(2\pi 60)t = \frac{1}{2}(V_1 + V_2)$$

$$V_d = 0.01 \sin(2\pi 1000)t = V_1 - V_2$$

$$V_1 = V_{CM} - V_d/2 = \sin(120\pi t) - 0.005 \sin(2000\pi t)$$

$$V_2 = V_{CM} + V_d/2 = \sin(120\pi t) + 0.005 \sin(2000\pi t)$$

2.7

$$V_d = R(G_{m2} V_2 - G_{m1} V_1) \text{ Refer to Fig. 2.4.}$$

$$V_o = V_3 = \mu V_d = \mu R(G_{m2} V_2 - G_{m1} V_1)$$

$$V_o = \mu R(G_{m1} V_2 + \frac{1}{2} \Delta G_m V_2 - G_{m1} V_1 + \frac{1}{2} \Delta G_m V_1)$$

$$V_o = \mu R G_m \underbrace{(V_2 - V_1)}_{V_{Id}} + \frac{1}{2} \mu R \Delta G_m \underbrace{(V_1 + V_2)}_{2V_{ICM}}$$

we have $V_o = A_d V_{Id} + A_{CM} V_{ICM}$
 $\Rightarrow A_d = \mu R G_m, A_{CM} = \mu R \Delta G_m$
 $CMRR = 20 \log \left| \frac{A_d}{A_{CM}} \right| = 20 \log \frac{G_m}{\Delta G_m}$

cont.

$$20 \log_{10} A_d = 80 \text{ dB} \Rightarrow A_d = 10^4$$

$$\frac{A_{cm}}{A_d} = \frac{\Delta G_m}{G_m} \Rightarrow A_{cm} = 10^4 \times \frac{0.1}{100} = 10$$

$$\text{CMRR} = 20 \log \frac{G_m}{\Delta G_m} = 20 \log \frac{1}{0.1/100} = 60$$

2.8


circuit	v_o/v_i (V/V)	R_{in} (k Ω)	
a	$-\frac{100}{10} = -10$	10	
b	-10	10	
c	-10	10	virtual ground
d	-10	10	no current in 10k Ω

2.9

closed loop gain = -1 V/V . for $v_i = 5 \text{ V} \Rightarrow v_o = -5 \text{ V}$
 Gain would be in the range of $-\frac{0.95}{1.05}$ to $-\frac{1.05}{0.95}$: $-0.9 < G < -1.1$
 for $v_i = 5 \Rightarrow -4 \text{ V} < v_o < -5.5 \text{ V}$

2.10

There are four possibilities:

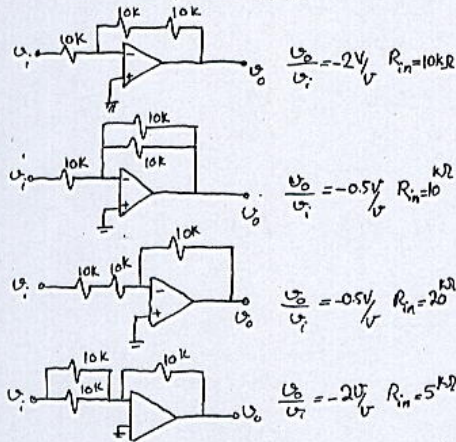

2.11

- a. $G = 1 \text{ V/V}$ b. $G = 10 \text{ V/V}$
 c. $G = 0.1 \text{ V/V}$ d. $G = 100 \text{ V/V}$
 e. $G = 10 \text{ V/V}$


2.12

- a. $G = -1 \text{ V/V} = -\frac{R_2}{R_1} \Rightarrow R_1 = R_2 = 10 \text{ k}\Omega$
 b. $G = -2 \text{ V/V} = -\frac{R_2}{R_1} \Rightarrow R_1 = 10 \text{ k}\Omega, R_2 = 20 \text{ k}\Omega$
 c. $G = -0.5 \text{ V/V} = -\frac{R_2}{R_1} \Rightarrow R_1 = 20 \text{ k}\Omega, R_2 = 10 \text{ k}\Omega$
 d. $G = -100 \text{ V/V} = -\frac{R_2}{R_1} \Rightarrow R_1 = 10 \text{ k}\Omega, R_2 = 1 \text{ M}\Omega$

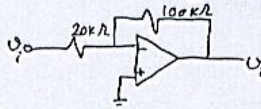2.13

$$\frac{v_o}{v_i} = -5 = -\frac{R_2}{R_1} \Rightarrow R_2 = 5R_1$$

$$R_1 + R_2 = 120 \text{ k}\Omega \Rightarrow 5R_1 + R_1 = 120 \text{ k}\Omega \Rightarrow R_1 = 20 \text{ k}\Omega \Rightarrow R_2 = 100 \text{ k}\Omega$$



2.14

$$20 \log |G| = 26 \text{ dB} \Rightarrow G = 19.95 \text{ V/V} = \frac{v_o}{v_i} = -\frac{R_2}{R_1}$$

$$\Rightarrow R_2 = 19.95 R_1 < 10 \text{ M}\Omega$$

For largest possible input resistance, select $R_2 = 10 \text{ M}\Omega \Rightarrow R_1 \approx 500 \text{ k}\Omega$
 $R_{in} = 500 \text{ k}\Omega$

2.15

$$G = \frac{v_o}{v_i} = -\frac{R_2}{R_1} = -\frac{100}{10} = -10$$

$v_{low} = -10 \text{ V}$, $v_{high} = 0$, $v_{avg} = -5 \text{ V}$

2.16


$$\frac{U_o}{U_i} = -\frac{R_2}{R_1} \Rightarrow U_o = -1 \times \frac{10 \text{ k}\Omega}{1 \text{ k}\Omega} = 10 \text{ V}$$

$$i_2 = \frac{U_o}{2 \text{ k}\Omega} = 5 \text{ mA}$$

$$i_1 = i_3 = \frac{U_o}{10 \text{ k}\Omega} = 1 \text{ mA}$$

$$i_4 = i_2 - i_3 = 4 \text{ mA}$$

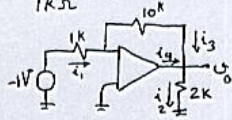This additional current comes from the output of the opamp.



2.19

$$U_i = -\frac{U_o}{A} = -\frac{U_o}{200}$$


$$\frac{U_o}{U_i} = 50 \text{ V/V}$$

$$U_i - \left(-\frac{U_o}{A}\right) = \frac{\left(-\frac{U_o}{A} - U_o\right)}{100 \text{ k}\Omega} \Rightarrow R_1 = 100 \text{ k}\Omega \times \frac{\frac{U_o}{200} - \frac{U_o}{50}}{-\frac{U_o}{200} - U_o}$$

$$\Rightarrow R_1 = 100 \text{ k}\Omega \times \frac{3}{201} = 1.49 \text{ k}\Omega$$

$$\text{Shunt Resistor } R_a: R_a \parallel 2 \text{ k}\Omega = 1.49 \text{ k}\Omega$$
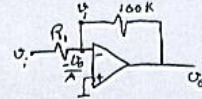
$$\frac{R_a \times 2}{R_a + 2} = 1.49 \Rightarrow R_a = 5.84 \text{ k}\Omega$$



2.17

$$|\text{Gain}| = \frac{R_2}{R_1} = \frac{R_2 (1+x/100)}{R_1 (1+x/100)} \approx \frac{R_2}{R_1} (1 \pm \frac{2x}{100})$$

$\Rightarrow 2x\%$ is the tolerance on the closed loop gain (G).

$$G = -100 \text{ V/V}, x = 5 \Rightarrow -110 < G < -90$$

$$\text{or more precisely: } -100 \times \frac{105}{95} < G < -100 \times \frac{95}{105}$$

$$-110.5 < G < -90.5$$

2.18

$$G = \frac{U_o}{U_i} = -\frac{R_2}{R_1} \Rightarrow \frac{R_2}{R_1} = \frac{5}{15}$$

$$U_1 = 0 \text{ V}, U_2 = U_o = 5 \text{ V}$$

$$\text{For } \pm 1\% \text{ on } R_1, R_2: R_1 = 15 \pm 0.15 \text{ k}\Omega$$


$$R_2 = 5 \pm 0.05 \text{ k}\Omega$$

$$U_o = U_i \frac{R_2}{R_1} = 15 \frac{R_2}{R_1} \Rightarrow 15 \times \frac{4.95}{15.15} \text{ V} < U_o < 15 \times \frac{5.05}{14.85}$$

$$\Rightarrow 4.9 \text{ V} < U_o < 5.1 \text{ V}$$

$$\text{For } U_i = -15 \pm 0.15 \text{ V } \frac{14.85 \times 4.95}{15.15} < U_o < \frac{15.15 \times 5.05}{14.85}$$
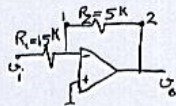
$$\Rightarrow 4.85 \text{ V} < U_o < 5.15 \text{ V}$$



2.20

a)

$$\frac{U_o}{U_i} = -\frac{R_2}{R_1} \Rightarrow -100 \text{ V/V} = -\frac{R_2}{1 \text{ k}\Omega} \Rightarrow R_2 = 100 \text{ k}\Omega$$


$$\text{b) } A = 1000 \text{ V/V}$$

$$U_i = -\frac{U_o}{A}$$

$$\frac{U_i - U_i}{R_1} = \frac{U_i - U_o}{R_2}$$

$$\frac{U_o}{U_i} = \frac{-R_2/R_1}{1 + (1 + R_2/R_1)/A} = \frac{-100}{1 + \frac{101}{1000}} = -90.8 \text{ V/V}$$
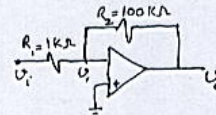
$$\Rightarrow \frac{U_o}{U_i} = 90.8 \text{ V/V}$$



c) Assume $R'_1 = R_x \parallel R_1$ when $R_1 = 1 \text{ k}\Omega$

$$\frac{U_o}{U_i} = 700 \text{ V/V}$$

$$\frac{U_i - U_i}{R'_1} = \frac{U_i - U_o}{R_2} \Rightarrow R'_1 = R_2 \times \left(\frac{U_o}{U_i} - 1\right) \left(\frac{-U_i - U_o}{U_i - U_o}\right)$$

$$R'_1 = \frac{1 - 0.1}{1.001} = 0.899 \text{ k}\Omega = \frac{R_1 R_x}{R_1 + R_x} = \frac{R_x}{1 + R_x}$$

$$\Rightarrow R_x = 8.9 \text{ k}\Omega \approx 8.87 \text{ k}\Omega \pm 1\%$$

2.21

Voltage of the inverting input terminal

Cont.

will vary from $\frac{-10V}{1000}$ to $\frac{+10V}{1000}$. Thus the virtual ground will depart from the ideal voltage of zero by a maximum of $\pm 10mV$.


2.22

a) For $A = \infty$: $V_i = 0$

$$V_o = -i_i R_f$$

$$R_m = \frac{V_o}{i_i} = -R_f$$

$$R_{in} = \frac{V_i}{i_i} = 0$$

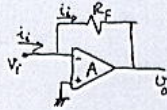

b) For $A = \text{finite}$: $V_i = -\frac{V_o}{A}$, $V_o = V_i - i_i R_f$

$$\rightarrow V_o = -\frac{V_o}{A} - i_i R_f \rightarrow R_m = \frac{V_o}{i_i} = -\frac{R_f}{1 + \frac{1}{A}}$$


$$R_{in} = \frac{V_i}{i_i} = \frac{R_f}{1 + A}$$

2.23

$$V_o = -A V_i = V_i - i_i R_2$$

$$i_i R_2 = (1 + A) V_i$$

$$V_i = \frac{i_i R_2}{1 + A}$$

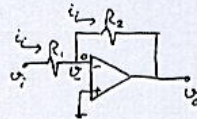

Now: $V_i = i_i R_1 + V_i = i_i R_1 + \frac{i_i R_2}{1 + A}$

$$R_{in} = \frac{V_i}{i_i} = R_1 + \frac{R_2}{1 + A}$$

2.24


$$G = \frac{-R_2/R_1}{1 + \frac{R_2/R_1}{A}}$$

$$\text{Gain Error } \epsilon = \left(1 + \frac{R_2}{R_1}\right) \times 100$$

$\frac{\epsilon}{A}$	0.1%	1%	10%
	1000 $\left(1 + \frac{R_2}{R_1}\right)$	100 $\left(1 + \frac{R_2}{R_1}\right)$	10 $\left(1 + \frac{R_2}{R_1}\right)$

Gain with R_{1a} :
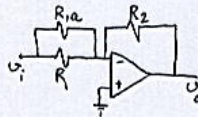
$$G \approx \frac{R_2}{R_1} \left(1 + \frac{R_1}{R_{1a}}\right)$$



where we have neglected the effect of R_{1a} on

the error on the denominator. To restore the gain to its nominal value of R_2/R_1 we use:

$$\frac{R_1}{R_{1a}} = \frac{1 + R_2/R_1}{A} = \frac{\epsilon}{100} \rightarrow R_{1a} = \frac{100 R_1}{\epsilon}$$

$\frac{\epsilon}{R_{1a}}$	0.1%	1%	10%
	1000 R_1	100 R_1	10 R_1

2.25

$$R'_i = R_1 \parallel R_2 \quad G' = \frac{-R_2/R'_i}{1 + \frac{R_2/R'_i}{A}}$$

$$G = \frac{-R_2}{R_1}$$

In order for $G' = G$: $G = \frac{-R_2/R'_i}{1 + \frac{R_2/R'_i}{A}} = \frac{-R_2}{R_1}$

$$R'_i = \frac{R_1 R_2}{R_1 + R_2}$$

$$\Rightarrow \frac{R_1 + R_2}{R_1 R_2} = \frac{1}{R_1} \left(1 + \frac{1 + R_2 (R_1 + R_2)}{A R_1 R_2}\right)$$

$$(R_1 + R_2) A = A R_2 + R_2 + \frac{R_2}{R_1} (R_1 + R_2)$$

$$R_1 A = R_2 + G R_1 + G R_2$$

$$\frac{R_2}{R_1} = \frac{A - G}{1 + G}$$

2.26

$$G = \frac{-R_2/R_1}{1 + \frac{R_2/R_1}{A}} \quad G_{\text{nominal}} = \frac{-R_2}{R_1}$$

$$\epsilon = \left| \frac{G - G_{\text{nominal}}}{G_{\text{nominal}}} \right| = \left| \frac{G}{G_{\text{nominal}}} - 1 \right|$$

$$\epsilon = \left| \frac{1}{1 + \frac{R_2/R_1}{A}} - 1 \right| = \left| \frac{-1 + R_2/R_1}{1 + \frac{R_2/R_1}{A}} \right| = \frac{1}{1 + \frac{R_2}{R_1} + 1}$$

which can be rearranged to yield:

$$\frac{A}{1 + \frac{R_2}{R_1}} + 1 = \frac{1}{\epsilon} \Rightarrow A = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{1}{\epsilon} - 1\right)$$

$$\text{or } A = \left(1 - G_{\text{nominal}}\right) \left(\frac{1}{\epsilon} - 1\right)$$

For $G_{\text{nominal}} = -100 \mu V$ and $\epsilon = 0.1\% = 0.001$

$$A = (1 + 100) \left(\frac{1}{0.001} - 1\right) = 909 \mu V$$

This is the minimum required value for A .

2.27

$$|G| = \frac{R_2/R_1}{1 + \frac{R_2}{R_1}} \quad A \rightarrow A(1 - \frac{x}{100})$$

$$|G'| = \frac{R_2/R_1}{1 + \frac{R_2/R_1}{A(1 - \frac{x}{100})}}$$

$$\text{For } |G'| = |G| (1 - \frac{x}{100k})$$

$$\frac{R_2/R_1}{1 + \frac{R_2/R_1}{A(1 - \frac{x}{100})}} = \frac{R_2/R_1}{1 + \frac{R_2/R_1}{A}} (1 - \frac{x}{100k})$$

$$1 + \frac{R_2/R_1}{A(1 - \frac{x}{100})} = (1 + \frac{R_2/R_1}{A}) (1 - \frac{x}{100k})$$

$$1 - \frac{x}{100k} + \frac{1 + R_2/R_1}{A} \frac{1 - x/100k}{1 - x/100} = 1 + \frac{R_2/R_1}{A}$$

$$\frac{1 + R_2/R_1}{A} \frac{1 - x/100k - 1 + x/100}{1 - x/100} = \frac{x}{100k}$$

$$A = \frac{1 + k}{1 - \frac{x}{100}} (1 + R_2/R_1) = \frac{(k-1)}{1 - \frac{x}{100}} (1 + \frac{R_2}{R_1})$$

$$\text{For } \frac{R_2}{R_1} = 100 \quad x = 50 \quad k = 100: A = \frac{99}{0.5} \times 101 = 19998$$

$$A \approx 2 \times 10^4 V/V$$

Thus for $A = 2 \times 10^4 V/V$, a reduction of 50% results in only 0.5% reduction of the closed loop gain whose nominal value is $\frac{R_2}{R_1} (100)$.

2.28

From the results of example 2.2, the gain of the circuit in fig. 2.8 is given by:

$$\frac{V_o}{V_i} = -\frac{R_2}{R_1} (1 + \frac{R_4}{R_2} + \frac{R_4}{R_3})$$

$$\text{For } R_1 = R_2 = R_4 = 1M\Omega \Rightarrow \frac{V_o}{V_i} = -(1 + 1 + \frac{1}{R_3})$$

$$a) \frac{V_o}{V_i} = -10 V/V \Rightarrow 10 = 2 + \frac{1}{R_3} \Rightarrow R_3 = \frac{1}{8} M\Omega = 125 k\Omega$$

$$b) \frac{V_o}{V_i} = -100 V/V \Rightarrow 100 = 2 + \frac{1}{R_3} \Rightarrow R_3 = \frac{1}{98} M\Omega = 10.2 k\Omega$$

$$c) \frac{V_o}{V_i} = -2 V/V \Rightarrow 2 = 2 + \frac{1}{R_3} \Rightarrow R_3 = \infty: \text{eliminate } R_3.$$

2.29

$$R_2/R_1 = 1000, R_2 = 100k\Omega \Rightarrow R_1 = 100\Omega$$

a) $R_{in} = R_1 = 100\Omega$

b) $\frac{V_o}{V_i} = -\frac{R_2}{R_1} (1 + \frac{R_4}{R_2} + \frac{R_4}{R_3}) = -1000$

If $R_2 = R_1 = R_4 = 100k \Rightarrow R_3 = \frac{100k}{1000-2} \approx 100\Omega$

$R_{in} = R_1 = 100k\Omega$

2.30

$V_x = 0 - i_1 R_2, i_1 = \frac{V_i}{R_1} \Rightarrow V_x = -\frac{V_i R_2}{R_1}$

$\frac{V_x}{V_i} = -\frac{R_2}{R_1}$

$V_x = V_o \frac{R_2 || R_3}{R_2 || R_3 + R_4} = V_o \frac{R_2 R_3}{R_2 R_3 + R_1 R_3 + R_1 R_2}$

$\frac{V_o}{V_x} = \frac{R_2 R_3 + R_2 R_4 + R_3 R_4}{R_2 R_3} = 1 + \frac{R_4}{R_3} + \frac{R_4}{R_2}$

$\frac{V_o/V_x}{V_i/V_x} = \frac{V_o}{V_i} = \frac{(1 + R_4/R_3 + R_4/R_2)}{-R_1/R_2}$

$\frac{V_o}{V_i} = -\frac{R_2}{R_1} (1 + \frac{R_4}{R_3} + \frac{R_4}{R_2})$

2.31

a) $R_1 = R$

$R_2 = R || R + \frac{R}{2} = \frac{R}{2} + \frac{R}{2} = R$

$R_3 = R_2 || R + \frac{R}{2} = R || R + \frac{R}{2} = R$

$R_4 = R_3 || R + \frac{R}{2} = R || R + \frac{R}{2} = R$

b) $V_i = RI = RI_1 \Rightarrow I_1 = I$


$I_2 = I + I = 2I \Rightarrow V_1 + 2I \times \frac{R}{2} = RI_2$

$RI + RI = RI_2 \Rightarrow I_2 = 2I$

$I_3 = I_2 + I_2 = 4I \Rightarrow V_2 + 4I \times \frac{R}{2} = RI_3$

$R \times 2I + 4I \times \frac{R}{2} = RI_3 \Rightarrow I_3 = 4I, I_4 = -(4I + 4I)$

$I_4 = -8I$

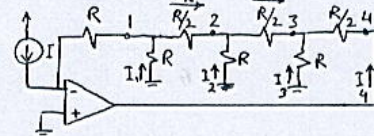

Cont.

$$\begin{aligned} \text{c) } V_1 &= I_1 R = IR \\ V_2 &= I_2 R = 2IR \\ V_3 &= -I_3 R = -4IR \\ V_4 &= -I_3 R + I_4 R_2 = -4IR - 8I \frac{R}{2} = -8IR \end{aligned}$$


2.32

$$\begin{aligned} \text{a) } I_1 &= \frac{1V}{10k\Omega} = 0.1 \text{ mA} \\ I_2 &= 0.1 \text{ mA}, \quad I_2 \times 10k\Omega = I_3 \times 100\Omega \Rightarrow I_3 = 10^{-4} \text{ A} \\ V_x &= 10 \text{ mA} \times 100\Omega = 1V \end{aligned}$$


$$\begin{aligned} \text{b) } V_x &= R_L I_L + V_0, \quad I_L = I_2 + I_3 = 10.1 \text{ mA} \\ 1V &= R_L \times 10.1 \text{ mA} + V_0 \\ R_L &= \frac{1 - V_0}{10.1} \Rightarrow R_{L \max} = \frac{1 - V_0 \min}{10.1} = \frac{14}{10.1} \\ R_{L \max} &= \end{aligned}$$

$$\begin{aligned} \text{c) } 100\Omega \leq R_L \leq 1k\Omega \\ I_L \text{ stays fixed at } 10.1 \text{ mA} \\ V_0 &= V_x - R_L I_L = 1 - R_L \times 10.1 \Rightarrow -9.1 \leq V_0 \leq -0.01 \text{ V} \end{aligned}$$

2.33
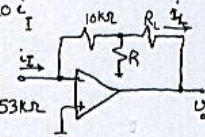
$$\begin{aligned} \text{a) } \frac{i_L}{i_I} = 20 \Rightarrow i_L = 20 i_I \\ -10k\Omega \times i_I = R(i_I - i_L) \\ R = \frac{10k\Omega \times i_I}{20i_I - i_I} = 0.53k\Omega \end{aligned}$$


$$\begin{aligned} \text{b) } R_L &= 1k\Omega, \quad -12 \leq V_0 \leq 12 \text{ V} \\ V_0 &= R_L i_L + 10k\Omega \times i_I = i_L (1k\Omega \times \frac{i_L}{10k\Omega} + 10k\Omega) \\ V_0 &= i_L (1 \times 20 + 10) = 30 i_L \\ i_I &= \frac{V_0}{30} \Rightarrow \frac{-12}{30} \leq i_I \leq \frac{12}{30} \Rightarrow -0.4 \leq i_I \leq 0.4 \text{ mA} \end{aligned}$$
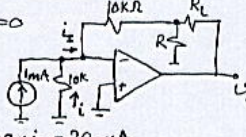
$$\begin{aligned} \text{c) } R_I &= \frac{V_I}{i_I} = \frac{0}{i_I} = 0 \\ V_0 &= 0 \Rightarrow i_I = 0 \\ \Rightarrow i_I &= 1 \text{ mA} \\ \text{From part a: } i_L &= 20 \times i_I = 20 \text{ mA} \end{aligned}$$


2.34

$$R_2 \gg R_3, \text{ if we ignore the current across } R_2: V_A = \frac{V_0 R_3}{R_3 + R_4}$$

$$\frac{V_I}{R_1} = \frac{0 - V_A}{R_2} \Rightarrow V_A = -\frac{R_2 V_I}{R_1}$$

$$V_0 \frac{R_3}{R_3 + R_4} = -\frac{R_2}{R_1} V_I \Rightarrow \frac{V_0}{V_I} = -\frac{R_2}{R_1} \left(1 + \frac{R_4}{R_3}\right)$$

Now if we recalculate V_A considering that there is a voltage divider between R_4 and $R_3 \parallel R_2$:

$$V_A = V_0 \frac{R_3 \parallel R_2}{R_4 + R_3 \parallel R_2} = \frac{V_0 R_3 R_2}{R_4 (R_3 + R_2) + R_3 R_2}$$

$$V_A = V_0 \frac{R_3 R_2}{R_3 R_2 + R_2 R_4 + R_3 R_4}$$

$$V_A = V_0 \frac{1}{\frac{R_4}{R_3} + \frac{R_4}{R_2} + 1}$$

$$V_A = -\frac{R_2}{R_1} V_I \Rightarrow \frac{V_0}{V_I} = -\frac{R_2}{R_1} \left(\frac{R_4}{R_2} + \frac{R_4}{R_3} + 1\right)$$

same as example 2.2.

2.35

$$R_I = 100k\Omega, \quad -10 \leq \frac{V_0}{V_I} \leq -1 \frac{V_0}{V_I}$$

$$R_I = R_1 = 100k\Omega$$

$$\frac{V_0}{V_I} = -\frac{R_2}{R_1} \left(\frac{R_4}{R_3} + \frac{R_4}{R_2} + 1\right)$$

$$R_4 = 0 \Rightarrow \frac{V_0}{V_I} = -\frac{R_2}{R_1} = -1 \Rightarrow R_2 = 100k\Omega$$

$$R_4 = 10k\Omega \Rightarrow \frac{V_0}{V_I} = -10 = -1 \times \left(\frac{10k\Omega}{R_3} + \frac{10k\Omega}{100k\Omega} + 1\right)$$

$$+10 = \left(\frac{10}{R_3} + 1.1\right) \Rightarrow R_3 = 1.12k\Omega$$

$$\text{Potentiometer in the middle: } \frac{V_0}{V_I} = -1 \left(\frac{5}{5+R_3} + \frac{5}{100} + 1\right)$$

$$\frac{V_0}{V_I} = -1.87 \frac{V_0}{V_I}$$


2.36

According to eq. 2.7:

$$U_o = -\left(\frac{R_F}{R_1} U_1 + \frac{R_F}{R_2} U_2 + \frac{R_F}{R_3} U_3\right)$$

$$U_o = -\left(\frac{50k}{100k} U_1 + \frac{50k}{100k} U_2 + \frac{50k}{100k} U_3\right)$$
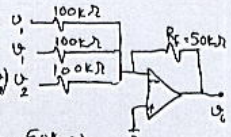
$$U_o = -(U_1 + \frac{U_2}{2}) \quad U_1 = 3, U_2 = -3 \Rightarrow U_o = -1.5V$$



2.37

we choose the weighted summer configuration

$$U_o = -\left[4U_1 + \frac{U_2}{3}\right]$$


$$i_1 = \frac{U_1}{R_1} \quad i_2 = \frac{U_2}{R_2}$$

$$i_1, i_2 \leq 0.1 \text{ mA for } U_1, U_2 = 1V$$

$$R_1, R_2 \geq 10k\Omega$$

$$\frac{R_F}{R_1} = 4, \text{ if } R_1 = 10k\Omega \Rightarrow R_F = 40k\Omega$$
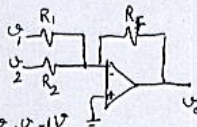
$$\frac{R_F}{R_2} = \frac{1}{3} \Rightarrow R_2 = 120k\Omega$$



2.38

$$U_o = -(2U_1 + 4U_2 + 8U_3)$$

$$R_1, R_2, R_3 \geq 10k\Omega$$

$$\frac{R_F}{R_1} = 2, \frac{R_F}{R_2} = 4, \frac{R_F}{R_3} = 8$$

$$R_3 = 10k\Omega \Rightarrow R_F = 80k\Omega$$

$$R_2 = 20k\Omega$$

$$R_1 = 40k\Omega$$

2.39

$$a) U_o = -(U_1 + 2U_2 + 3U_3)$$


$$\frac{R_F}{R_1} = 1 \Rightarrow R_1 = 10k\Omega, \frac{R_F}{R_2} = 2 \Rightarrow R_2 = 5k\Omega$$

$$\frac{R_F}{R_3} = 3 \Rightarrow R_3 = \frac{10}{3} k\Omega$$

$$R_{I1} = 10k\Omega$$

$$R_{I2} = 5k\Omega$$

$$R_{I3} = 3.3k\Omega$$

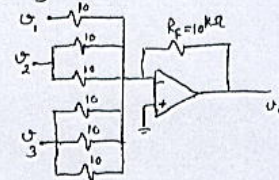

$$b) U_o = -(U_1 + U_2 + 2U_3 + 2U_4)$$

$$\frac{R_F}{R_1} = 1 \Rightarrow R_1 = 10k\Omega$$

$$\frac{R_F}{R_2} = 1 \Rightarrow R_2 = 10k\Omega$$

$$\frac{R_F}{R_3} = 2 \Rightarrow R_3 = \frac{10}{2} k\Omega$$

$$\frac{R_F}{R_4} = 2 \Rightarrow R_4 = \frac{10}{2} k\Omega$$

$$R_{I1} = R_{I2} = 10k\Omega$$

$$R_{I3} = R_{I4} = 5k\Omega$$



$$c) U_o = -(U_1 + 5U_2)$$

$$R_1 = 10k\Omega$$

$$R_2 = \frac{10k}{5}$$

$$R_{I1} = 10k\Omega$$


$$R_{I2} = 2k\Omega$$

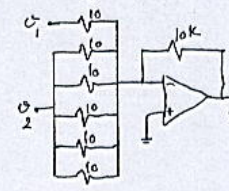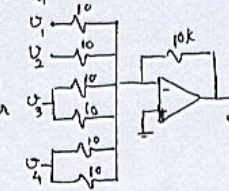

$$d) U_o = -6U_1$$

$$R_1 = 10k\Omega$$

$$R_{F1} = \frac{10}{6} k\Omega$$

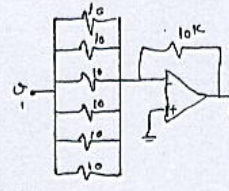

Suggested configurations:

$$U_o = -(2U_1 + 2U_2 + 2U_3)$$

$$U_o = -(3U_1 + 3U_2)$$

$$U_o = -(3U_1 + 3U_2)$$

$$U_o = -(3U_1 + 3U_2)$$

$$U_o = -(3U_1 + 3U_2)$$

$$U_o = -(3U_1 + 3U_2)$$

$$U_o = -(3U_1 + 3U_2)$$

$$U_o = -(3U_1 + 3U_2)$$

$$U_o = -(3U_1 + 3U_2)$$

$$U_o = -(3U_1 + 3U_2)$$

$$U_o = -(3U_1 + 3U_2)$$

$$U_o = -(3U_1 + 3U_2)$$

$$U_o = -(3U_1 + 3U_2)$$

$$U_o = -(3U_1 + 3U_2)$$

$$U_o = -(3U_1 + 3U_2)$$

$$U_o = -(3U_1 + 3U_2)$$

$$U_o = -(3U_1 + 3U_2)$$

$$U_o = -(3U_1 + 3U_2)$$

$$U_o = -(3U_1 + 3U_2)$$

$$U_o = -(3U_1 + 3U_2)$$

$$U_o = -(3U_1 + 3U_2)$$

$$U_o = -(3U_1 + 3U_2)$$

$$U_o = -(3U_1 + 3U_2)$$

$$U_o = -(3U_1 + 3U_2)$$


$$U_o = -(3U_1 + 3U_2)$$

$$U_o = -(3U_1 + 3U_2)$$

$$U_o = -(3U_1 + 3U_2)$$

$$U_o = -(3U_1 + 3U_2)$$

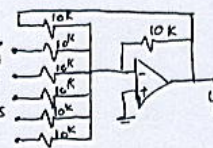In order to have coefficient = 0.5, connect one of the input resistors to U_1 . $\frac{U_o}{U_1} = 0.5$



2.40

The output signal should be:



$$U_o = -5 \sin \omega t - 5$$

if we assume: $U_1 = 5 \sin \omega t$
 $U_2 = 2V$ } $U_o = -U_1 + 2.5U_2$

In a weighted summer configuration:

$$\frac{R_F}{R_1} = +1 \quad \frac{R_F}{R_2} = 2.5$$
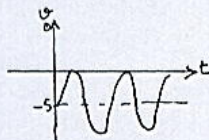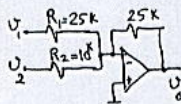
$$R_2 = 10k\Omega \Rightarrow R_F = 25k\Omega = R_1$$



2.41

$U_o = U_1 + 2U_2 - 3U_3 - 4U_4$: Consider Fig. 2.11.

According to eq. 2.8 for a weighted summer circuit:

$$U_o = U_1 \frac{R_F}{R_1} \frac{R_c}{R_b} + U_2 \frac{R_F}{R_2} \frac{R_c}{R_b} - U_3 \frac{R_c}{R_3} - U_4 \frac{R_c}{R_4}$$


$$\frac{R_F}{R_1} \frac{R_c}{R_b} = 1, \quad \frac{R_F}{R_2} \frac{R_c}{R_b} = 1, \quad \frac{R_c}{R_3} = 3, \quad \frac{R_c}{R_4} = 4$$

assume:

$$R_4 = 10k\Omega \Rightarrow R_c = 40k\Omega \Rightarrow R_3 = \frac{40}{3} = 13.3k\Omega$$

$$\frac{R_F}{R_1} \times \frac{40}{10} = 1 \quad \frac{R_F}{R_2} \times \frac{40}{10} = 1$$
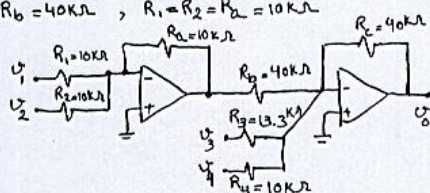
$$R_b = 40k\Omega, \quad R_1 = R_2 = R_a = 10k\Omega$$



2.42

$$U_1 = 3 \sin(2\pi \times 60t) + 0.01 \sin(2\pi \times 1000t)$$

$$U_2 = 3 \sin(2\pi \times 60t) - 0.01 \sin(2\pi \times 1000t)$$

we want to have: $U_o = 10U_1 - 10U_2$


we use the circuit in Fig. 2.11.

According to Eq. 2.8:

$$U_o = U_1 \frac{R_a}{R_1} \frac{R_c}{R_b} - U_2 \frac{R_c}{R_2}$$

$$\frac{R_a}{R_1} \frac{R_c}{R_b} = 10, \quad \frac{R_c}{R_2} = 10, \quad \text{if } R_2 = 10k\Omega \Rightarrow R_c = 100k\Omega$$
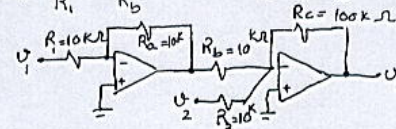
$$\Rightarrow \frac{R_a}{R_1} \times \frac{100k\Omega}{R_b} = 10 \Rightarrow R_a = R_1 = R_b = 10k\Omega$$



$$U_o = 10U_1 - 10U_2 = 10 \times 0.02 \sin(2\pi \times 1000t)$$

$$U_o = 0.2 \sin(2\pi \times 1000t) \quad -0.2 \leq U_o \leq 0.2V$$

2.43

This is a weighted summer circuit:

$$U_o = -\left(\frac{R_F}{R_0} U_a + \frac{R_F}{R_1} U_1 + \frac{R_F}{R_2} U_2 + \frac{R_F}{R_3} U_3\right)$$

we may write: $U_a = 5U \times a_0$, $U_1 = 5U \times a_1$

$$U_2 = 5U \times a_2, \quad U_3 = 5U \times a_3$$

$$U_o = -R_F \left(\frac{5U}{80k} a_0 + \frac{5U}{40k} a_1 + \frac{5U}{20k} a_2 + \frac{5U}{10k} a_3\right)$$

$$U_o = -R_F \left(\frac{a_0}{16} + \frac{a_1}{8} + \frac{a_2}{4} + \frac{a_3}{2}\right)$$

$$U_o = -\frac{R_F}{16} (2a_0 + 2a_1 + 2a_2 + 2a_3)$$

$$-12 \leq U_o \leq 0 \Rightarrow \frac{R_F}{16} (2 \times 1 + 2 \times 1 + 2 \times 1 + 2 \times 1) =$$

$$= \frac{15 R_F}{16} = 12 \quad \text{when } a_0 = a_1 = a_2 = a_3 = 1 \text{ we have the peak value at } U_o.$$

$$\Rightarrow R_F = 12.8k\Omega$$

2.44


$$a) \frac{U_o}{U_1} = 1 = 1 + \frac{R_2}{R_1} \Rightarrow R_2 = 0, R_1 = 10k\Omega$$

$$b) \frac{U_o}{U_1} = 2 = 1 + \frac{R_2}{R_1} \Rightarrow R_1 = R_2 = 10k\Omega$$

Cont.

c) $\frac{U_o}{U_i} = 101 \Rightarrow U_o = 101 U_i \Rightarrow 1 + \frac{R_2}{R_1} = 101 \Rightarrow R_2 = 100 R_1 = 100 \text{ k}\Omega$
 d) $\frac{U_o}{U_i} = 100 \Rightarrow U_o = 100 U_i \Rightarrow 1 + \frac{R_2}{R_1} = 100 \Rightarrow R_2 = 99 R_1 = 990 \text{ k}\Omega$

2.45

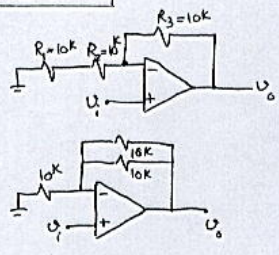

short-circuit R_2 :
 $\frac{U_o}{U_i} = 2$
 short-circuit R_3 :
 $\frac{U_o}{U_i} = 1$

2.46

$U_+ = U_- = V = R \cdot i$, $i = 100 \mu\text{A}$ when $V = 10 \text{ V}$
 $\Rightarrow R = \frac{10}{0.1 \text{ mA}} = 100 \text{ k}\Omega$

As indicated, i only depends on R and V and the meter resistance does not affect i .

2.47

Refer to the circuit in P2.47:

a) using superposition, we first set $U_1 = U_2 = \dots = 0$
 The output voltage that results in response to $U_{N1}, U_{N2}, \dots, U_{Nn}$ is:

$$U_{ON} = -\left[\frac{R_F}{R_{N1}} U_{N1} + \frac{R_F}{R_{N2}} U_{N2} + \dots + \frac{R_F}{R_{Nn}} U_{Nn} \right]$$


Then we set $U_{N1} = U_{N2} = \dots = 0$, then:

$$R_N = R_{N1} \parallel R_{N2} \parallel R_{N3} \parallel \dots \parallel R_{Nn}$$

The circuit simplifies to:

$$U_{OP} = \left(1 + \frac{R_F}{R_N}\right) \times$$
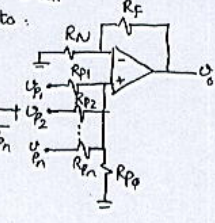
$$\left(U_{P1} \frac{Y_{RP1}}{R_{P1} + \frac{1}{R_{P2}} + \dots + \frac{1}{R_{Pn}}} + U_{P2} \frac{Y_{RP2}}{R_{P2} + \frac{1}{R_{P1}} + \dots + \frac{1}{R_{Pn}}} + \dots + U_{Pn} \frac{Y_{RPn}}{R_{Pn} + \frac{1}{R_{P1}} + \dots + \frac{1}{R_{P2}}} \right)$$



$$U_{OP} = \left(1 + \frac{R_F}{R_N}\right) \left(U_{P1} \frac{R_F}{R_{P1}} + U_{P2} \frac{R_F}{R_{P2}} + \dots + \frac{R_F}{R_{Pn}} U_{Pn} \right)$$


where: $R_P = R_{P1} \parallel R_{P2} \parallel \dots \parallel R_{Pn}$

when all inputs are present:

$$U_o = U_{ON} + U_{OP} = -\left(\frac{R_F}{R_{N1}} U_{N1} + \frac{R_F}{R_{N2}} U_{N2} + \dots \right) + \left(1 + \frac{R_F}{R_N}\right) \left(\frac{R_F}{R_{P1}} U_{P1} + \frac{R_F}{R_{P2}} U_{P2} + \dots \right)$$

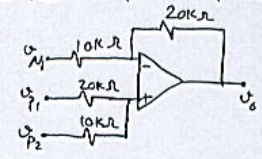b) $U_o = -2 U_{N1} + U_{P1} + 2 U_{P2}$
 $\frac{R_F}{R_N} = 2 \Rightarrow R_N = 10 \text{ k}\Omega \Rightarrow R_F = 20 \text{ k}\Omega$
 $\left(1 + \frac{R_F}{R_N}\right) \left(\frac{R_F}{R_{P1}} \right) = 1 \Rightarrow 3 \frac{R_F}{R_{P1}} = 1 \Rightarrow R_{P2} = \frac{R_{P1}}{2}$
 $\left(1 + \frac{R_F}{R_N}\right) \left(\frac{R_F}{R_{P2}} \right) = 2 \Rightarrow 3 \frac{R_F}{R_{P2}} = 2 \Rightarrow R_{P2} = \frac{3 R_{P1}}{2}$
 where $R_P = \frac{R_{P1} \cdot R_{P2}}{R_{P1} + R_{P2}}$ (ignoring R_{Pn})

Note that if the results from the last 2 constraints differ, we would use an additional resistor connected from the positive input to ground. (R_{Pn})



2.48

$$U_o = U_{I1} + 3 U_{I2} - 2 (U_{I3} + 3 U_{I4})$$

Refer to P2.47.
 $\frac{R_F}{R_{N3}} = 2$ if $R_{N3} = 10 \text{ k}\Omega \Rightarrow R_F = 20 \text{ k}\Omega$

$$\frac{R_F}{R_{N4}} = 6 \Rightarrow R_{N4} = \frac{20}{6} = 3.3 \text{ k}\Omega$$

$$R_N = R_{N3} \parallel R_{N4} = 10 \text{ k} \parallel 3.3 \text{ k} = 2.48 \text{ k}\Omega$$

$$\left(1 + \frac{R_F}{R_N}\right) \frac{R_P}{R_{P1}} = 1 \Rightarrow \left(1 + \frac{20}{2.48}\right) \frac{R_P}{R_{P1}} = 1 \Rightarrow 9.06 R_P = R_{P1}$$

$$R_P = R_{P1} \parallel R_{P2} \parallel R_{P3} \Rightarrow R_P = \frac{1}{\frac{1}{R_{P1}} + \frac{1}{R_{P2}} + \frac{1}{R_{P3}}}$$

$$\left(1 + \frac{R_F}{R_N}\right) \frac{R_P}{R_{P2}} = 3 \Rightarrow 9.06 \frac{R_P}{R_{P2}} = 3 \Rightarrow R_{P2} = 3 R_P$$

$$R_{P1} \parallel R_{P2} = \frac{9 \times 3 R_P}{9+3} = 2.25 R_P, R_P = 2.25 R_P \parallel R_{P3}$$


Cont.

$$2.25 R_p + R_{p0} = 2.25 R_{p0} \Rightarrow R_{p0} = 1.8 R_p$$

$$\text{if } R_p = 10 \text{ k}\Omega \Rightarrow R_{p0} = 18 \text{ k}\Omega$$

$$R_{p1} = 9 \times 10 \text{ k} = 90 \text{ k}\Omega$$
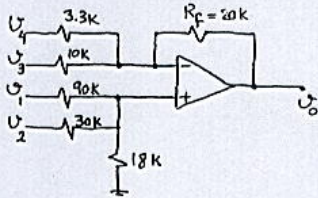
$$R_{p2} = 3 \times 10 \text{ k} = 30 \text{ k}\Omega$$



2.49

$$U_+ = U \frac{R_4}{R_3 + R_4} = U$$

$$\frac{U_o}{R_1} = \frac{U_2 - U_+}{R_2} \Rightarrow U_o = U_+ \left(1 + \frac{R_2}{R_1}\right)$$

from the two above equations:

$$\frac{U_o}{U_+} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) = \frac{1 + R_2/R_1}{1 + R_3/R_4}$$

2.50

Refer to Fig. 2.50. Setting $U_2 = 0$, we obtain the output component due to U_1 as:

$$U_{o1} = -20U$$

Setting $U_1 = 0$, we obtain the output component due to U_2 as:

$$U_{o2} = U_2 \left(1 + \frac{20R}{R}\right) \left(\frac{20R}{20R + R}\right) = 20U_2$$

The total output voltage is:

$$U_o = U_{o1} + U_{o2} = 20(U_2 - U_1)$$

$$\text{For } U_1 = 10 \sin 2\pi \times 60t - 0.1 \sin(2\pi \times 1000t)$$

$$U_2 = 10 \sin 2\pi \times 60t + 0.1 \sin(2\pi \times 1000t)$$

$$U_o = 4 \sin(2\pi \times 1000t)$$

2.51

$$\frac{U_o}{U_i} = 1 + \frac{R_2}{R_1} = 1 + \frac{(1-x)}{x} = 1 + \frac{1}{x} - 1 = \frac{1}{x}$$

$$0 < x < 1 \Rightarrow 1 \leq \frac{U_o}{U_i} < \infty$$

if we add a resistor on the ground path:

$$\frac{U_o}{U_i} = 1 + \frac{(1-x) \times 10 \text{ k}}{x \times 10 \text{ k} + R}$$


Gain_{max} = 21 when

$$x=0 \Rightarrow 21 = 1 + \frac{10 \text{ k}}{R}$$

$$\Rightarrow R = \frac{10 \text{ k}}{20} = 0.5 \text{ k}\Omega$$



2.52

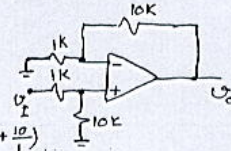

$$U_o = U \frac{10}{1 + 10} \left(1 + \frac{10}{1}\right)$$

$$U_o = 10U$$


2.53

a) Source is connected directly:

$$U_o = 10 \times \frac{1}{101} = 0.099 \text{ V}$$

$$i_L = \frac{U_o}{1 \text{ k}} = \frac{0.099}{1 \text{ k}} = 0.099 \text{ mA}$$

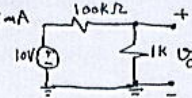current supplied by the source is 0.099 mA.




b) inserting a buffer

$$U_o = 10 \text{ V}$$


$$i_L = \frac{10 \text{ V}}{1 \text{ k}} = 10 \text{ mA}$$

current supplied by the source is 0.

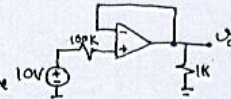The load current i_L comes from the power supply of the op-amp.



2.54

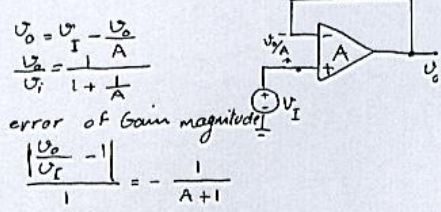

$$V_o = V_i - \frac{V_o}{A}$$

$$\frac{V_o}{V_i} = \frac{1}{1 + \frac{1}{A}}$$

error of Gain magnitude

$$\left| \frac{V_o}{V_i} - 1 \right| = -\frac{1}{A+1}$$

A (V/V)	1000	100	10
$\frac{V_o}{V_i}$ (V/V)	0.999	0.990	0.909
Gain Error	-0.1%	-1%	-9.1%

2.55

for an inverting amplifier:

$$R_i = R_1, G = -\frac{R_2}{R_1}$$

for a non-inverting amplifier:

$$R_i = \infty, G = 1 + \frac{R_2}{R_1}$$

Case	Gain ^{1/V}	R _{in}	R ₁	R ₂
a	-10	10K	10K	100K
b	-1	100K	100K	100K
c	-2	50K	50K	100K
d	+1	∞	10K	10K
e	+2	∞	10K	10K
f	+11	∞	10K	100K
g	-0.5	10K	10K	5K

2.56

$$A = 50 \text{ V/V}, 1 + \frac{R_2}{R_1} = 10 \text{ V/V}$$


$$\text{if } R_1 = 10 \text{ k}\Omega \Rightarrow R_2 = 90 \text{ k}\Omega$$

According to Eq. 2.11: $G = \frac{V_o}{V_i} = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{1}{A}}$

$$G = \frac{1 + \frac{90}{10}}{1 + \frac{1}{50}} = \frac{10}{1.2} = 8.33 \text{ V/V}$$

In order to compensate the gain drop,

we can shunt a resistor with R_1 .

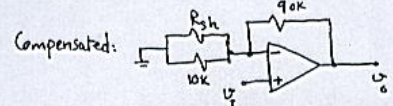

$$R_{sh}: 10 = \frac{1 + \left(\frac{90}{10} + \frac{90}{R_{sh}}\right)}{1 + \frac{1}{1 + \frac{90}{10} + \frac{90}{R_{sh}}}}$$

$$10 \times (50 R_{sh} + 90 R_{sh} + 900) = 50 \times (10 R_{sh} + 90 R_{sh} + 900)$$

$$100 R_{sh} = 3600 \Rightarrow R_{sh} = 36 \text{ k}\Omega$$

if A = 100 then:

$$G_{\text{uncompensated}} = \frac{1 + \frac{90}{10}}{1 + \frac{1}{100}} = \frac{10}{1.1} = 9.09 \text{ V/V}$$

$$G_{\text{compensated}} = \frac{1 + \frac{90}{10} + \frac{90}{36}}{1 + \frac{1}{100}} = \frac{12.5}{1.125} = 11.1 \text{ V/V}$$

2.57

$$G = \frac{G_0}{1 + \frac{G_0}{A}}, \frac{G_0 - G}{G_0} \times 100 = \frac{G_0/A \times 100}{1 + \frac{G_0}{A}}$$

or $\frac{1 + \frac{G_0}{A}}{\frac{G_0}{A}} \geq \frac{100}{x} \Rightarrow \frac{A}{G_0} \geq \frac{100}{x} - 1$

$$\Rightarrow A \geq G_0 F \text{ where } F = \frac{100}{x} - 1 \approx \frac{100}{x}$$

x	0.01	0.1	1	10
F	10 ⁴	10 ³	10 ²	10

Thus for:

x = 0.01: G_0 (V/V) | 1 | 10 | 10² | 10³ | 10⁴

A (V/V) | 10⁴ | 10⁵ | 10⁶ | 10⁷ | 10⁸

Too high to be practical

x = 0.1: G_0 (V/V) | 1 | 10 | 10² | 10³ | 10⁴

A (V/V) | 10³ | 10⁴ | 10⁵ | 10⁶ | 10⁷

x = 1: G_0 (V/V) | 1 | 10 | 10² | 10³ | 10⁴

A (V/V) | 10² | 10³ | 10⁴ | 10⁵ | 10⁶

x = 10: G_0 (V/V) | 1 | 10 | 10² | 10³ | 10⁴

A (V/V) | 10 | 10² | 10³ | 10⁴ | 10⁵

2.58

for non-inverting amplifier, Eq. 2.11:

$$G = \frac{G_0}{1 + \frac{G_0}{A}}, \quad E = \frac{G_0 - G}{G_0} \times 100$$

for inverting amplifier, Eq. 2.5:

$$G = \frac{G_0}{1 + \frac{1 - G_0}{A}}, \quad E = \frac{G_0 - G}{G_0} \times 100$$

Case	$G_0 (V/V)$	$A (V/V)$	$G (V/V)$	$e\%$
a	-1	10	-0.83	16
b	1	10	0.91	9
c	-1	100	-0.98	2
d	10	10	5	50
e	-10	100	-9	10
f	-10	1000	-9.89	1.1
g	+1	2	0.67	33

2.59

Refer to Fig. P2.59, when potentiometer is set to the bottom:

$$V_0 = V_+ = -15 + \frac{30 \times 20}{20 + 100 + 20} = -10.714 \text{ V}$$

$$\text{when set to the top: } V_0 = -15 + \frac{30 \times 120}{20 + 100 + 20} = 10.714 \text{ V}$$

$$\Rightarrow -10.714 \leq V_0 \leq +10.714$$

$$\text{pot has 20 turn, each turn: } \Delta V_0 = \frac{2 \times 10.714}{20} = 1.071 \text{ V}$$

2.60

Refer to Fig. 2.16. Notice that similar to eq. 2.15 we have: $\frac{R_{41}}{R_3} = \frac{R_2}{R_1} = \frac{100}{10}$. therefore according to 2.16:

$$V_0 = \frac{R_2}{R_1} V_{Id} \Rightarrow A = \frac{R_2}{R_1} = 10 \text{ V/V}$$

According to 2.20: $R_{id} = 2R_1 = 20 \text{ k}\Omega$

If $\frac{R_2}{R_1}$, $\frac{R_4}{R_3}$ were different by $i\%$:

$$\frac{R_2}{R_1} = 0.99 \frac{R_4}{R_3}$$

Refer to eq. 2.19: $A_{cm} = \frac{R_4}{R_1 + R_3} \left(1 - \frac{R_2}{R_1} \frac{R_3}{R_4}\right)$

$$A_{cm} = \frac{100}{100 + 10} (1 - 0.99) = 0.009$$

CMRR = $20 \log \frac{|A_d|}{|A_{cm}|}$, so let's calculate A_d

$A_d = \frac{V_0}{V_{Id}}$ if we apply superposition:

$$V_{01} = -\frac{R_2}{R_1} V_{I1}, \quad V_{02} = V_{I2} \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1}\right)$$

$$V_0 = V_{02} + V_{01} = V_{I2} \frac{R_4/R_3}{1 + R_4/R_3} \left(1 + \frac{R_2}{R_1}\right) - \frac{R_2}{R_1} V_{I1}$$

Replace $\frac{R_2}{R_1} = 0.99 \frac{R_4}{R_3} \Rightarrow \frac{R_2}{R_1} = 0.99 \times \frac{100}{10} = 9.9$

$$V_0 = V_{I2} \frac{10}{1 + 10} (1 + 9.9) - V_{I1} 9.9 = 9.9 (V_{I2} - V_{I1})$$

$$\frac{V_0}{V_{Id}} = 9.9 = A_d \Rightarrow \text{CMRR} = 20 \log \frac{9.9}{0.009} = 60.8$$

CMRR = 60.8

2.61

If we assume $R_3 = R_1$, $R_4 = R_2$, then

eq. 2.20: $R_{id} = 2R_1 \Rightarrow R_1 = \frac{20}{2} = 10 \text{ k}\Omega$

(Refer to Fig. 2.16)

a) $A_d = \frac{R_2}{R_1} = 1 \text{ V/V} \Rightarrow R_2 = 10 \text{ k}\Omega$
 $R_1 = R_2 = R_3 = R_4 = 10 \text{ k}\Omega$

b) $A_d = \frac{R_2}{R_1} = 2 \text{ V/V} \Rightarrow R_2 = 20 \text{ k}\Omega = R_4$
 $R_1 = R_3 = 10 \text{ k}\Omega$

c) $A_d = \frac{R_2}{R_1} = 100 \text{ V/V} \Rightarrow R_2 = 1 \text{ M}\Omega = R_4$
 $R_1 = R_3 = 10 \text{ k}\Omega$

d) $A_d = \frac{R_2}{R_1} = 0.5 \text{ V/V} \Rightarrow R_2 = 5 \text{ k}\Omega = R_4$
 $R_1 = R_3 = 10 \text{ k}\Omega$

2.62


Refer to Fig. P2.62:

Cont.


Considering that $U_- = U_+$:

$$U_1 + \frac{U_o - U_1}{2} = \frac{U_2}{2} \Rightarrow U_o = U_2 - U_1$$
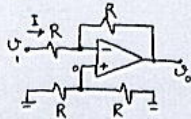
$$U_1 \text{ only: } R_I = \frac{U_1}{I} = R$$



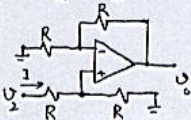
$$U_2 \text{ only: } R_I = \frac{U_2}{I} = 2R$$



U_3 between 2 terminals.

$$R_I = \frac{U}{I} = 2R$$


$$U_+ = U_- = 0$$

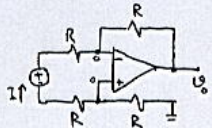

U_3 connected to both U_1 & U_2 :

$$R_I = \frac{U}{I} = R$$

$$U_+ = U_- = \frac{U_3}{2}$$

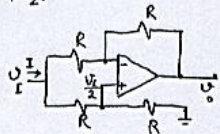


2.63

$$U_+ = U_{CM} \frac{R_4}{R_3 + R_4}$$

$$U_- = U_-$$

$$i_2 = \frac{U_{CM}}{R_3 + R_4}$$

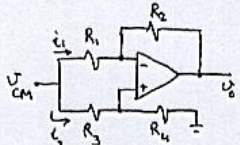

$$i_1 = \frac{U_{CM}}{R_1} - \frac{U_{CM} R_4}{R_3 + R_4} \cdot \frac{1}{R_1} = \frac{U_{CM}}{R_1} \frac{R_3}{R_3 + R_4}$$

$$i = i_1 + i_2 = \frac{U_{CM}}{R_1} \frac{R_3}{R_3 + R_4} + \frac{U_{CM}}{R_3 + R_4}$$

$$\frac{1}{R_I} = \frac{i}{U_{CM}} = \frac{1}{R_1} \frac{1}{\frac{R_4}{R_3} + 1} + \frac{1}{R_3 + R_4}$$

if we replace $\frac{R_4}{R_3}$ with $\frac{R_2}{R_1}$: $(\frac{R_4}{R_3} = \frac{R_2}{R_1})$

$$\frac{1}{R_I} = \frac{1}{R_1 + R_2} + \frac{1}{R_3 + R_4} \Rightarrow R_I = (R_1 + R_2) \parallel (R_3 + R_4)$$

2.64


In order to have an ideal differential amp:

$$\frac{R_5 + R_1}{R_2} = \frac{R_5 + R_3}{R_4}$$

$$\frac{R_5/R_1 + 1}{R_2/R_1} = \frac{R_5/R_3 + 1}{R_4/R_3}$$

$$\text{Since } \frac{R_2}{R_1} = \frac{R_4}{R_3} :$$
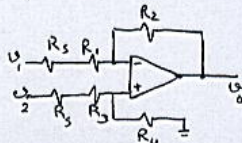
$$\frac{R_5}{R_1} + 1 = \frac{R_5}{R_3} + 1 \Rightarrow R_1 = R_3 \Rightarrow R_2 = R_4$$



2.65

Refer to eq. 2.19 and Fig. P2.62:

$$A_{CM} = \frac{U_o}{U_{CM}} = \frac{R_4}{R_3 + R_4} \left(1 - \frac{R_2}{R_1} \frac{R_3}{R_4} \right)$$

The worst case is when A_{CM} has its maximum value.

$$A_{CM} = \frac{1}{\frac{R_3}{R_4} + 1} \left(1 - \frac{R_2}{R_1} \frac{R_3}{R_4} \right)$$

Max $A_{CM} \Rightarrow R_2$ has to be at its minimum value and also $\frac{R_4}{R_3} R_2$ has to be minimum.

$$\frac{100-x}{100+x} \frac{R_3}{R_4} \leq \frac{100+x}{100-x} \frac{R_2}{R_1} \leq \frac{100+x}{100-x}$$

$$\text{so if } \frac{R_3}{R_4} = \frac{100-x}{100+x} \neq \frac{R_2}{R_1} = \frac{100-x}{100+x}$$

$$A_{CM \text{ Max}} = \frac{1}{\frac{100-x}{100+x} + 1} \left(1 - \frac{100-x}{100+x} \frac{100-x}{100+x} \right)$$

$$A_{CM \text{ Max}} = \frac{1}{200} \frac{(100+x)^2 - (100-x)^2}{100+x} = \frac{2x}{100+x} \approx \frac{x}{50}$$

x	0.1	1	5
$A_{CM \text{ Max}}$	0.002	0.02	0.1

$CMRR = 20 \log \left| \frac{A_d}{A_{CM}} \right|$. Now we have to calculate

A_d based on values we chose for $R_1 - R_4$

that gave us $A_{CM \text{ Max}}$.

$$R_2 = R_3 = 100 - x \quad R_1 = R_4 = 100 + x$$

$U_o = U_{o1} + U_{o2}$ by applying superposition

$$U_o = -\frac{R_2}{R_1} U_1 + U_2 \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1} \right)$$

$$U_o = -\frac{100-x}{100+x} U_1 + U_2 \frac{100+x}{200} \left(1 + \frac{100-x}{100+x} \right)$$

$$U_o = \frac{100-x}{100+x} U_1 + U_2$$

if we consider $\frac{100-x}{100+x} \leq 1 \Rightarrow \frac{U_o}{U_d} \leq 1$ Cont.

$$CMRR = 20 \log \frac{A_d}{A_{cm}} = 20 \log \frac{1}{\frac{1}{750}} = 20 \log \frac{750}{1}$$

x	0.1	1	5
CMRR	54db	34db	20db

2.66

Refer to Fig. 2.16 and eq. 2.19:

$$A_{cm} = \frac{R_4}{R_3 + R_4} \left(1 - \frac{R_2}{R_1} \frac{R_3}{R_4} \right)$$

In order to calculate A_d , we use superposition principle:

$$v_o = v_{o1} + v_{o2} = -\frac{R_2}{R_1} v_1 + v_2 \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1} \right)$$

$$\text{then replace } v_1 = v_{cm} - \frac{v_d}{2}$$

$$v_2 = v_{cm} + \frac{v_d}{2}$$

$$v_o = -\frac{R_2}{R_1} v_{cm} + \frac{R_2}{R_1} v_{cm} \frac{1}{2} + v_{cm} \frac{1 + R_2/R_1}{1 + R_3/R_4} + \frac{v_d}{2} \frac{1 + R_2/R_1}{1 + R_3/R_4}$$

$$v_o = \frac{R_2}{2R_1} \left[1 + \frac{R_2/R_1 + 1}{R_3/R_4 + 1} \right] v_d + \frac{R_2}{R_1} \left[1 + \frac{R_2/R_1 + 1}{R_3/R_4 + 1} \right] v_{cm}$$

$$CMRR = 20 \log \left| \frac{A_d}{A_{cm}} \right| = 20 \log \left| \frac{\frac{R_2}{2R_1} \left[1 + \frac{R_2/R_1 + 1}{R_3/R_4 + 1} \right]}{\frac{R_2}{R_1} \left[1 + \frac{R_2/R_1 + 1}{R_3/R_4 + 1} \right]} \right|$$

$$CMRR = 20 \log \left| \frac{\frac{1}{2} \frac{R_2}{R_1} \left[2 + \frac{R_2}{R_1} + \frac{R_3}{R_4} + \frac{R_2 R_3}{R_1 R_4} \right]}{1 - \frac{R_2}{R_1} \frac{R_3}{R_4}} \right|$$

$$CMRR = 20 \log \left| \frac{1 + \frac{1}{2} \frac{R_2}{R_1} + \frac{1}{2} \frac{R_2 R_3}{R_1 R_4}}{\frac{R_2}{R_1} - \frac{R_3}{R_4}} \right|$$

for worst case, or minimum CMRR we have to maximize the denominator, which means:

$$R_1 = R_m (1 + \epsilon) \quad R_3 = R_n (1 - \epsilon)$$

$$R_2 = R_m (1 - \epsilon) \quad R_4 = R_n (1 + \epsilon)$$

$$\text{also: } \frac{R_2 R_3}{R_1 R_4} = \frac{R_m R_n}{R_m R_n} = K$$

$$CMRR = 20 \log \left| K \frac{1 + \frac{1}{2K} \frac{1+\epsilon}{1-\epsilon} + \frac{1}{2K} \frac{1-\epsilon}{1+\epsilon}}{\frac{1+\epsilon}{1-\epsilon} - \frac{1-\epsilon}{1+\epsilon}} \right|$$

$$CMRR = 20 \log \left| K \frac{(1-\epsilon^2) + (1+\epsilon^2)}{4\epsilon} \right| = 20 \log \left| \frac{K+1}{4\epsilon} \right|$$

for $\epsilon^2 \ll 1$.

$$\text{if } K = A_d \text{ ideal} = 100, \epsilon = 0.01$$

$$CMRR = 20 \log \frac{101}{0.04} = 68 \text{db}$$

2.67

$$A_d = 100$$

we assume $\frac{R_2}{R_1} = \frac{R_4}{R_3}$ then $A_d = \frac{R_2}{R_1} = K$

$$K < 100$$

$$R_{id} = 2R_1 = 20 \text{K}\Omega \rightarrow R_1 = 10 \text{K}\Omega$$

$$CMRR = 80 \text{db} = 20 \log \frac{A_d}{A_{cm}} \Rightarrow \frac{A_d}{A_{cm}} = 10^4$$

$$\Rightarrow A_{cm} = 0.01$$

$$A_d = 100 = \frac{R_2}{R_1} \Rightarrow R_2 = 1 \text{M}\Omega$$

Refer to p. 2.66: $CMRR = 20 \log \frac{K+1}{4\epsilon}$

$$CMRR = 10^4$$

$$\Rightarrow \epsilon = 10^{-2} \times 0.25$$

We assumed earlier $\frac{R_2}{R_1} = \frac{R_4}{R_3}$ then

$$\frac{R_2}{R_1} < 100 \Rightarrow \text{if } R_3 = 10 \text{K}\Omega \pm \epsilon$$

$$\Rightarrow R_4 = 1 \text{M}\Omega \pm \epsilon \quad \epsilon = 0.25\%$$

$$R_2 = 1 \text{M}\Omega \pm \epsilon$$

$$R_1 = 10 \text{K}\Omega \pm \epsilon$$

2.68

Refer to Fig. 2.68 and Eq. 2.19:

$$A_{cm} = \frac{R_4}{R_3 + R_4} \left(1 - \frac{R_2}{R_1} \frac{R_3}{R_4} \right) = \frac{100}{100+100} \left(1 - \frac{100 \cdot 100}{100 \cdot 100} \right)$$

$$A_{cm} = 0$$

Refer to 2.17: $\frac{R_2}{R_1} = \frac{R_4}{R_3}$

$$\Rightarrow A_d = \frac{R_2}{R_1} = 1$$

b) Since $A_{cm} = 0$,

then if we apply v_{cm} to V_{i1} and V_{i2} , $v_o = 0$.

$$\text{Therefore, } V_A = v_{cm} \frac{100}{100+100}$$

$$V_A = \frac{v_{cm}}{2}$$

Similarly, $V_B = \frac{v_{cm}}{2}$


We know $V_A = V_B$ and $-2.5 \leq v_{cm} \leq 2.5$

$$\Rightarrow -5 \leq v_{cm} \leq 5$$

c) we apply the

superposition

principle to calculate

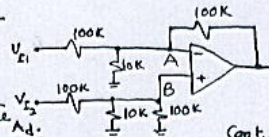

Cont.

v_{o1} is the output voltage when $v_{I2} = 0$

v_{o2} is the output voltage when $v_{I1} = 0$


$$v_o = v_{o1} + v_{o2}$$

$$v_{o1} = -\frac{R_2}{R_1} v_{I1} = -v_{I1}$$

$$v_{o2} = v_{I2} \frac{100k \parallel 110k}{100k \parallel 110k + 100} \left(1 + \frac{100k}{100k \parallel 110k}\right)$$

$$v_{o2} = v_{I2} \cdot 1 \Rightarrow v_o = v_{o1} + v_{o2} = -v_{I1} + v_{I2} \Rightarrow A_d = 1$$

Now we calculate A_{cm} :

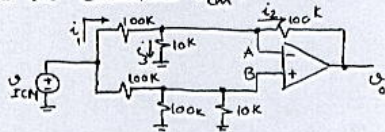

$$v_B = v_{ICM} \frac{100k \parallel 10k}{100k \parallel 110k + 100k}, \quad v_A = v_B$$

$$i_1 = \frac{v_{ICM} - v_A}{100k}$$

$$v_o = v_A - 100k \cdot i_2 \quad \text{and} \quad i_2 = i_1 - i_3 = i_1 - \frac{v_A}{10k}$$

$$v_o = v_A - 100k \cdot i_1 + 10 \cdot v_A$$

$$v_o = v_A - v_{ICM} + v_A + 10 \cdot v_A$$

$$v_A = v_B \Rightarrow v_o = v_{ICM} \left(-1 + 12 \frac{100k \parallel 110k}{100k \parallel 110k + 100}\right)$$

Now we calculate v_{ICM} range:

$$-25 \leq v_B \leq 2.5 \Rightarrow -25 \leq v_{ICM} \times \frac{100k \parallel 110k}{100k \parallel 110k + 100k} < 2.5$$

$$-30 \leq v_{ICM} \leq 30 \text{ V}$$

2.69

Refer to Fig. P2.69; we use superposition:

$$v_o = v_{o1} + v_{o2}$$

$$\text{calculate } v_{o1}: v_+ = \frac{\beta v_{o1}}{2} = v_-$$

$$\frac{v_+ - \beta v_{o1}}{2} = \frac{\beta v_{o1} - v_o}{2} \Rightarrow v_{o1} = \frac{v_+}{\beta - 1}$$

Calculate v_{o2} :

$$v_- = \frac{v_{o2}}{2} = v_+ \Rightarrow v_- - \frac{v_{o2}}{2} = \frac{v_{o2}}{2} - \beta v_{o2}$$

$$\Rightarrow v_{o2} = \frac{v_+}{1 - \beta}$$

$$v_o = v_{o1} + v_{o2} = \frac{v_+}{\beta - 1} + \frac{v_+}{1 - \beta} = \frac{1}{1 - \beta} (v_+ - v_+)$$

$$A_d = \frac{v_o}{v_+ - v_-} = \frac{1}{1 - \beta}$$


$$A_d = 10 \Rightarrow \beta = 0.9 = \frac{R_5}{R_5 + R_6}$$

$$R_{id} = 2R = 2M\Omega \Rightarrow R = 1M\Omega$$

$$R_5 + R_6 \leq \frac{R}{100} \Rightarrow R_5 + R_6 \leq 10k\Omega$$

$$R_5 = 6.8k\Omega \quad R_6 = 680\Omega \Rightarrow \beta = \frac{6.8}{6.8 + 0.68} \approx 0.9$$

2.70

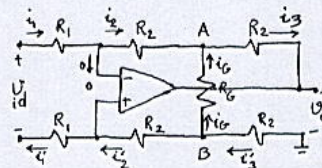

$v_+ = v_-$ so we can consider v_+, v_- a virtual short:

$$i_1 = v_{id} / 2R_1 \Rightarrow i_2 = \frac{v_{id}}{2R_1}$$

$$i_1 = i_2 = \frac{v_{id}}{2R_1}$$

$$\text{then: } i_2 R_2 + v_{AB} + i_3 R_2 = 0 \Rightarrow v_{AB} = -\frac{v_{id} R_2}{R_1}$$

$$i_3 = \frac{v_{id}}{R_6} \times \frac{R_2}{R_1}$$

$$i_3 = i_2 + i_6 = \frac{v_{id}}{2R_1} + \frac{v_{id}}{R_6} \frac{R_2}{R_1}$$

$$i_3 = i_6 + i_2 = i_3$$

$$\Rightarrow v_o = -[i_3 R_2 + v_{BA} + i_3 R_2]$$


$$v_o = -[2i_3 R_2 + v_{BA}]$$

$$v_o = -\left[2 \frac{v_{id} R_2}{2R_1} + 2v_{id} \frac{R_2}{R_1} \frac{R_2}{R_6} + \frac{v_{id} R_2}{R_1}\right]$$


$$\frac{v_o}{v_{id}} = A_d = -2 \frac{R_2}{R_1} \left[1 + \frac{R_2}{R_6}\right]$$

2.71

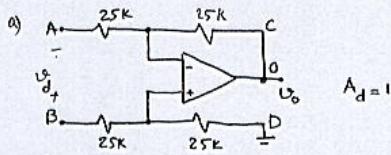
a) Refer to Eq. 2.17: $A_d = \frac{R_2}{R_1} = 1$. Connect C and D together. Cont.



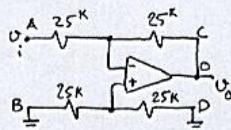b) $\frac{V_o}{V_i} = -1 \frac{V}{V}$
 i)




ii) $\frac{V_o}{V_i} = +1 \frac{V}{V}$

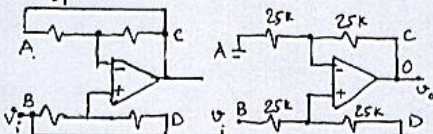


The circuit on the left ideally has infinite input resistances.

iii) $\frac{V_o}{V_i} = +2 \frac{V}{V}$

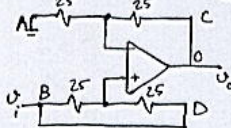


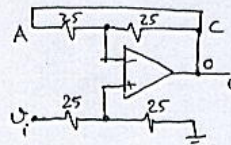iv) $\frac{V_o}{V_i} = +\frac{1}{2} \frac{V}{V}$

$V_+ = \frac{V_i}{2} = V_0$
 $= 7 \frac{V_o}{V_i} = \frac{1}{2}$



2.72

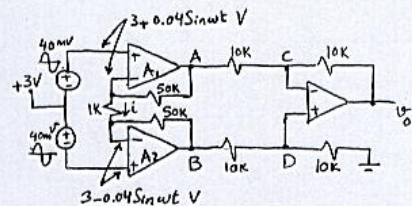

$i = \frac{3 + 0.04 \sin \omega t - (3 - 0.04 \sin \omega t)}{1k} = 0.08 \sin \omega t, \text{ mA}$

$V_A = 3 + 0.04 \sin \omega t + 50k \times i = 3 + 4.04 \sin \omega t, \text{ V}$

$V_B = 3 - 0.04 \sin \omega t - 50k \times i = 3 - 4.04 \sin \omega t, \text{ V}$

$V_C = V_0 = \frac{1}{2} V_B = 1.5 - 2.02 \sin \omega t, \text{ V}$

$V_o = V_C - V_A = -8.08 \sin \omega t, \text{ V}$

2.73

Refer to Fig. 2.20.a.

The gain of the first stage is: $(1 + \frac{R_2}{R_1}) = 101$

If the opamps of the first stage saturate at $\pm 14 \text{ V}$: $-14 \leq V_1 \leq +14 \text{ V} \Rightarrow -14 \leq 101 V_{icm} \leq +14$

$\Rightarrow -0.14 \leq V_{icm} \leq 0.14$

As explained in the text, the disadvantage of circuit in Fig. 2.20.a is that V_{icm} is amplified by a gain equal to $V_{id}(1 + \frac{R_2}{R_1})$ in the first stage and therefore a very small V_{icm} range is acceptable to avoid saturation.

b) In Fig. 2.20.b, when V_{icm} is applied, V_+ for both A_1 & A_2 is the same and therefore no current flows through $2R_1$. This means V_{01} & V_{02} at the output of A_1 and A_2 is the same as V_{icm} .

$-14 \leq V_o \leq 14 \Rightarrow -14 \leq V_{icm} \leq 14$

This circuit allows for bigger range of V_{icm} .

2.74

$V_{i1} = V_{cm} - V_d/2$

$V_{i2} = V_{cm} + V_d/2$

Refer to Fig. 2.20.a.

output of the first stage: $(1 + \frac{R_2}{R_1})(V_{cm} - \frac{V_d}{2})$

$V_{o1} = (1 + \frac{R_2}{R_1})(V_{cm} - \frac{V_d}{2})$

$V_{o2} = (1 + \frac{R_2}{R_1})(V_{cm} + \frac{V_d}{2})$

$V_{o2} - V_{o1} = (1 + \frac{R_2}{R_1}) V_d \Rightarrow A_d(\omega) = 1 + \frac{R_2}{R_1}$

$\frac{V_{o2} + V_{o1}}{2} = (1 + \frac{R_2}{R_1}) V_{cm} \Rightarrow A_{cm}(\omega) = 1 + \frac{R_2}{R_1}$

$\text{CMRR} = 20 \log \left| \frac{A_d}{A_{cm}} \right| = 0 \text{ (First stage)}$

Now consider Fig. 2.20.b

$V_{o1} = V_{i1} + R_2 \times \frac{(V_{i1} - V_{i2})}{2R_1}$

$V_{o1} = V_{cm} - V_d/2 + \frac{R_2}{2R_1} (-V_d)$

Cont.

$$v_{o1} = v_{cm} - \frac{v_d}{2} \left(1 + \frac{R_2}{R_1}\right)$$

$$v_{o2} = v_{i2} - R_2 \times \frac{v_{i1} - v_{i2}}{2} = v_{cm} + \frac{v_d}{2} + R_2 \frac{v_d}{2R_1}$$

$$v_{o2} = v_{cm} + \frac{v_d}{2} \left(1 + \frac{2R_2}{R_1}\right)$$

$$v_{o2} - v_{o1} = v_d \left(1 + \frac{R_2}{R_1}\right) \Rightarrow A_{d(1)} = 1 + \frac{R_2}{R_1}$$

$$\frac{v_{o2} + v_{o1}}{2} = v_{cm} \Rightarrow A_{cm(1)} = 1$$

$$CMRR = 20 \log \left| \frac{A_d}{A_{cm}} \right| = 20 \log \left(1 + \frac{R_2}{R_1}\right)$$

In 2.20.b, the common mode voltage is not amplified and it is only propagated to the outputs of the first stage.

2.75

Refer to eq. 2.22:

$$A_d = \frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1}\right) = \frac{100k}{100k} \left(1 + \frac{100k}{5k}\right) = 21 \frac{V}{V}$$

$$A_{cm} = 0$$

$$CMRR = 20 \log \left| \frac{A_d}{A_{cm}} \right| = \infty$$

If all resistors are $\pm 1\%$:

$$A_d \approx 21$$

In order to calculate A_{cm} , apply v_{cm} to both inputs and note that v_{cm} will appear at both output terminals of the first stage.

Now we can evaluate v_o by analyzing the second stage as was done in problem 2.65.

In P2.65 we showed that if each 100k resistor has $\pm x\%$ tolerance, A_{cm} of the differential amplifier is:

$$A_{cm} = \frac{v_o}{v_{cm}} = \frac{x}{50}$$

$$x = 1 \Rightarrow A_{cm} = \frac{1}{50} = 0.02$$

$$CMRR = 20 \log \frac{21}{0.02} = 60 \text{ dB}$$

$$\text{If } 2R_1 = 1k\Omega : A_d = \frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1}\right) = 201 \frac{V}{V}$$

$$A_{cm} = 0.02 \text{ unchanged}$$

$$CMRR = 20 \log \frac{201}{0.02} = 80 \text{ dB}$$

Conclusion: large CMRR can be achieved by

having relatively large A_d in the first stage.

2.76

$A_{d(2)}$ of the second stage is $\frac{R_4}{R_3} = 0.5$

$$R_4 = 100k\Omega, R_3 = 200k\Omega$$

We use a series configuration of R_F and R_1 (pot): $R_1 = 100k \text{ pot}$ (Fixed)

$$\text{Minimum gain} = 0.5 \left(1 + \frac{R_2}{R_1}\right) = 0.5 \left(1 + \frac{R_2}{100k + R_1}\right)$$

$$1 \leq A_d \leq 100 \Rightarrow 1 = 0.5 \left(1 + \frac{2R_2 R_1}{R_1 + 100k}\right)$$

$$\Rightarrow R_1 + 100 = 2R_2 \quad (1)$$

$$\text{Maximum gain} = 100 = 0.5 \left(1 + \frac{R_2}{R_1/2}\right) \Rightarrow$$

$$2R_2 = 199R_1 \quad (2)$$





$$(1), (2) \Rightarrow R_1 = 0.505k\Omega \approx 0.5k\Omega$$

$$R_2 = 50.25k\Omega \approx 50k\Omega$$

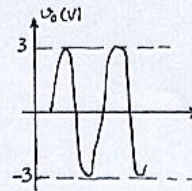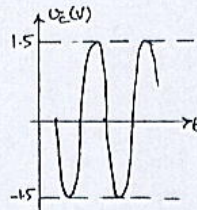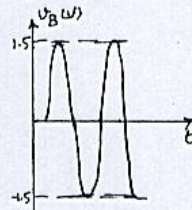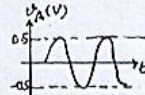2.77

$$a) \frac{v_B}{v_A} = 1 + \frac{20}{10} = 3 \frac{V}{V}, \quad \frac{v_C}{v_A} = -\frac{30}{10} = -3 \frac{V}{V}$$

$$b) v_o = v_B - v_C = 6 \frac{V}{V} \Rightarrow \frac{v_o}{v_A} = 6 \frac{V}{V}$$



c) v_B and v_C can be $\pm 14V$ or 28V P-P.

$$-28 \leq v_o \leq 28 \text{ or } 56 \text{ P-P.}$$


$$v_{rms} = 19.8 \text{ V} = \frac{28}{\sqrt{2}}$$

2.78

Refer to Fig. P.2.78.a.
 Since the inputs of the op-amp don't draw any current, V_1 appears across R_1 .

$$i_o = \frac{V_1}{R_1}$$

Fig. P.2.78.B

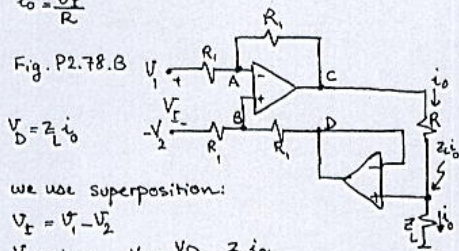

$$V_D = Z_L i_o$$

we use superposition:

$$V_1 = V_1 - V_2$$

$$V_1 \text{ only: } V_B = \frac{V_D}{2} = \frac{Z_L i_o}{2}$$

$$\frac{V_1 - \frac{Z_L i_o}{2}}{R_1} = \frac{\frac{Z_L i_o}{2} - i_o(Z_L + R_1)}{R_1}$$

$$\rightarrow V_1 = i_o R_1 \Rightarrow i_o = \frac{V_1}{R_1}$$

Now if only $(-V_2)$ is applied:

$$V_B = \frac{-V_2 + Z_L i_o}{2}, \quad V_A = \frac{i_o Z_L (R_1 + Z_L)}{2}$$

$$V_A = V_B \Rightarrow -V_2 + Z_L i_o = i_o Z_L R_1 + i_o Z_L^2$$

$$-V_2 = i_o Z_L R_1 \Rightarrow i_o = \frac{-V_2}{R_1}$$

The total current due to both sources is:

$$i_o = i_{o1} + i_{o2} = \frac{V_1}{R_1} - \frac{V_2}{R_1} = \frac{V_1 - V_2}{R_1}$$

The circuit in Figure P.2.78(a) has ideally infinite input resistance, and it requires that both terminals of Z_L be available, while the other circuit has finite input resistance with one side of Z_L grounded.

2.79

A_o	f_b (Hz)	f_c (Hz)	eq. 2.28:
10^5	10^2	10^7	$\omega_c = A_o \omega_b$
10^6	1	10^6	$\Rightarrow f_c = A_o f_b$
10^5	10^3	10^8	
10^7	10^1	10^6	
2×10^5	10	2×10^6	

2.80

$$\text{Eq. 2.25: } A = \frac{A_o}{1 + j\omega/\omega_b} \Rightarrow |A| = \frac{|A_o|}{\sqrt{1 + (\frac{f}{f_b})^2}}$$

$$A_o = 86 \text{ dB}, \quad A = 40 \text{ dB @ } f = 100 \text{ kHz}$$

$$20 \log \sqrt{1 + (\frac{f}{f_b})^2} = 20 \log |A| = 20 \log A_o - 20 \log |A|$$


$$= 86 - 40 = 46 \text{ dB}$$

$$1 + (\frac{100 \text{ kHz}}{f_b})^2 = (199.5)^2 \Rightarrow f_b = 0.501 \text{ kHz}$$

$$f_b = 501 \text{ Hz}$$

$$f_c = A_o f_b = 1.995 \times 10^4 \times 501 = 9.998 \text{ MHz} \approx 10 \text{ MHz}$$

2.81

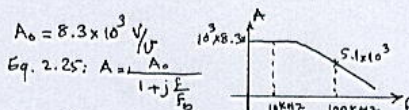

$$\text{Eq. 2.25: } A = \frac{A_o}{1 + j\frac{f}{f_b}}$$

$$f_c = A_o f_b$$

$$5.1 \times 10^3 = \frac{8.3 \times 10^3}{\sqrt{1 + (\frac{100 \text{ kHz}}{f_b})^2}} \Rightarrow 1 + (\frac{100 \text{ kHz}}{f_b})^2 = 2.65$$

$$f_b = 60.7 \text{ kHz}$$

$$f_c = A_o f_b = 8.3 \times 10^3 \times 60.7 = 503 \text{ MHz}$$

2.82

we have:

$$A_o = 20 \text{ dB} + A_{(db)} \quad 20 \text{ dB} = 20 \log 10 \Rightarrow A_o = 10 \text{ V/V}$$

$$\text{a) } A_o = 10 \times 3 \times 10^5 = 3 \times 10^6 \text{ Hz V/V}$$

$$A = \frac{A_o}{1 + j\frac{f}{f_b}} \Rightarrow |1 + j\frac{f}{f_b}| = \frac{A_o}{A} = 10 \Rightarrow \frac{6 \times 10^2}{f_b} = \sqrt{99}$$

$$\Rightarrow f_b = 60.3 \text{ Hz}$$

$$f_c = A_o f_b = 3 \times 10^6 \times 60.3 = 180.9 \text{ MHz}$$

$$\text{b) } A = 50 \times 10^5 \text{ V/V} \Rightarrow A_o = 10 \times 50 \times 10^5 = 50 \times 10^6 \text{ V/V}$$

$$|1 + j\frac{f}{f_b}| = \frac{A_o}{A} = 10 \Rightarrow \frac{10^8}{f_b} = \sqrt{99} \Rightarrow f_b = 1 \text{ Hz}$$

$$f_c = A_o f_b = 50 \text{ MHz}$$

$$\text{c) } A = 1500 \text{ V/V} \Rightarrow A_o = 15000 \text{ V/V}$$

Cont.

$$\left|1 + \frac{jf}{f_b}\right| = 10 \Rightarrow \frac{0.1 \times 10^6}{f_b} = \sqrt{99} \Rightarrow f_b = 10 \text{ kHz}$$

$$f_c = 15000 \times 10^6 = 150 \text{ MHz}$$

d) $A_0 = 10 \times 100 = 1000 \text{ V/V}$

$$\left|1 + \frac{jf}{f_b}\right| = 10 \Rightarrow \frac{0.1 \times 10^6}{f_b} = \sqrt{99} \Rightarrow f_b = 10 \text{ MHz}$$

$$f_c = 1000 \times 10^6 = 1000 \text{ MHz}$$

e) $A_0 = 25 \text{ V/V} \times 10 = 25 \times 10^4 \text{ V/V}$

$$\left|1 + \frac{jf}{f_b}\right| = 10 \Rightarrow \frac{25 \times 10^4}{f_b} = \sqrt{99} \Rightarrow f_b = 2.51 \text{ MHz}$$

$$f_c = A_0 f_b = 25 \times 10^4 \times 2.51 \times 10^3 = 627.5 \text{ MHz}$$

2.83

$$G_{nom} = -\frac{R_2}{R_1} = -20 \quad A_0 = 10^4 \text{ V/V} \quad f_b = 10^6 \text{ Hz}$$

Eq. 2.35: $\omega_{2dB} = \frac{\omega_b}{1 + R_2/R_1} = \frac{2\pi \times 10^6}{1 + 20} = 2\pi \times 47.6 \text{ kHz}$

$$f_{3dB} = 47.6 \text{ kHz}$$

Eq. 2.34: $\frac{V_o}{V_i} \approx \frac{-R_2/R_1}{1 + \frac{s}{\omega_b(1 + R_2/R_1)}} = \frac{-20}{1 + \frac{s}{2\pi \times 10^6}}$

$$F = 0.1 f_{3dB} \Rightarrow \left|\frac{V_o}{V_i}\right| = \frac{-20}{\sqrt{1 + (0.1)^2}} = -19.9 \text{ V/V}$$

$$F = 10 f_{3dB} \Rightarrow \left|\frac{V_o}{V_i}\right| = \frac{-20}{\sqrt{1 + 100}} = -1.99 \text{ V/V}$$

2.84

$$1 + \frac{R_2}{R_1} = 100 \text{ V/V}, \quad f_c = 20 \text{ MHz}$$

$$f_{3dB} = \frac{f_c}{1 + \frac{R_2}{R_1}} = 200 \text{ kHz}$$

$$G_{mid} = \frac{100}{1 + j f/f_{3dB}} \Rightarrow \varphi = -\tan^{-1} \frac{f}{f_{3dB}}$$

$$\varphi = -6^\circ \Rightarrow f = f_{3dB} \times \tan 6^\circ = 21 \text{ kHz}$$

$$\varphi = -84^\circ \Rightarrow f = f_{3dB} \times \tan 84^\circ = 1.9 \text{ MHz}$$

2.85

a) $-\frac{R_2}{R_1} = -100 \text{ V/V}, \quad f_{3dB} = 100 \text{ kHz}$

Eq. 2.35: $\omega_c = \omega_{3dB} (1 + \frac{R_2}{R_1}) \Rightarrow f_c = 100 \times 101 = 10.1 \text{ MHz}$

b) $1 + \frac{R_2}{R_1} = 100 \text{ V/V} \quad f_{3dB} = 100 \text{ kHz}$

$$f_c = f_{3dB} (1 + \frac{R_2}{R_1}) = 10 \text{ MHz}$$

c) $1 + \frac{R_2}{R_1} = 2 \text{ V/V} \quad f_{3dB} = 10 \text{ MHz}$

$$f_c = 10 \text{ MHz} \times 2 = 20 \text{ MHz}$$

d) $-\frac{R_2}{R_1} = -2 \text{ V/V} \quad f_{3dB} = 10 \text{ MHz}$

$$f_c = 10 \text{ MHz} (1 + 2) = 30 \text{ MHz}$$

e) $-\frac{R_2}{R_1} = -1000 \text{ V/V} \quad f_{3dB} = 20 \text{ kHz}$

$$f_c = 20 \text{ kHz} (1 + 1000) = 20.02 \text{ MHz}$$

f) $1 + \frac{R_2}{R_1} = 1 \text{ V/V} \quad f_{3dB} = 1 \text{ MHz}$

$$f_c = 1 \text{ MHz} \times 1 = 1 \text{ MHz}$$

g) $-\frac{R_2}{R_1} = -1 \quad f_{3dB} = 1 \text{ MHz}$

$$f_c = 1 \text{ MHz} (1 + 1) = 2 \text{ MHz}$$

2.86

$$1 + \frac{R_2}{R_1} = 100 \text{ V/V} \quad f_{3dB} = 8 \text{ kHz}$$

$$f_c = 8 \times 100 = 800 \text{ kHz}$$

$$\text{For } f_{3dB} = 20 \text{ kHz} : G_0 = \frac{800}{20} = 40 \text{ V/V}$$

2.87

$$f_{3dB} = f_c = 1 \text{ MHz}$$

$$|G| = \frac{1}{\sqrt{1 + \left(\frac{f}{f_{3dB}}\right)^2}} = \frac{1}{\sqrt{1 + f^2}} \quad f \text{ in MHz}$$

$$|G| = 0.99 \Rightarrow f = 0.142 \text{ MHz}$$

The follower behaves like a low-pass STC circuit with a time constant $\tau = \frac{1}{\omega_{3dB}}$

Thus: $\tau = \frac{1}{2\pi \times 10^6} = \frac{1}{2\pi} \mu\text{s}$

$$t_r = 2.2\tau = 0.35 \mu\text{s} \quad (\text{Refer to Appendix F})$$

a) $-\frac{R_2}{R_1} = -100 \text{ V/V}, \quad f_{3dB} = 100 \text{ kHz}$

Eq. 2.35: $\omega_c = \omega_{3dB} (1 + \frac{R_2}{R_1}) \Rightarrow f_c = 100 \times 101 = 10.1 \text{ MHz}$

2.88

$$1 + \frac{R_2}{R_1} = 10 \text{ V/V} \quad A_1 = 1 \text{KR} \quad R_2 = 9 \text{KR}$$

If we consider 5% the time that it takes for the output voltage to reach 99% of its final value, then: $5\tau = 100 \text{ns} \Rightarrow \tau = 20 \text{ns}$

$$\tau = \frac{1}{\omega_{3db}} \Rightarrow \omega_{3db} = 50 \times 10^6 \Rightarrow f_{3db} = 7.96 \text{MHz}$$

$$f_c = \left(1 + \frac{R_2}{R_1}\right) f_{3db} = 10 \times 7.96 = 79.6 \text{MHz}$$

2.89

a) Assume two identical stages, each with a gain function:

$$G = \frac{G_0}{1 + j\frac{\omega}{\omega_1}} = \frac{G_0}{1 + j\frac{f}{f_1}}$$

$$G = \frac{G_0}{\sqrt{1 + \left(\frac{f}{f_1}\right)^2}}$$

Overall gain of the cascade is $\frac{G_0^2}{1 + \left(\frac{f}{f_1}\right)^2}$

The gain will drop by 3db when:

$$1 + \left(\frac{f_{3db}}{f_1}\right)^2 = \sqrt{2}, \text{ Note } 3\text{db} = 20 \log \sqrt{2}$$

$$f_{3db} = f_1 \sqrt{\sqrt{2} - 1}$$

b) $40 \text{db} = 20 \log G_0 \Rightarrow G_0 = 100 = 1 + \frac{R_2}{R_1}$

$$f_{3db} = \frac{f_c}{1 + \frac{R_2}{R_1}} = \frac{1 \text{MHz}}{100} = 10 \text{kHz}$$

c) Each stage should have 20db gain or

$$1 + \frac{R_2}{R_1} = 10 \text{ and therefore a 3db frequency of: } f_1 = \frac{10^6}{10} = 10^5 \text{ Hz}$$

$$\text{The overall } f_{3db} = 10^5 \sqrt{\sqrt{2} - 1} = 64.35 \text{ kHz}$$

which is 6 times greater than the bandwidth achieved using single op-amp. (case b above)

2.90

$f_c = 100 \times 5 = 500 \text{MHz}$. if single op-amp is used.

with op-amp that has only $f_c = 40 \text{MHz}$, the possible closed loop gain at 5MHz is:

$$A_f \frac{40}{5} = 8 \text{ V/V}$$

To obtain an overall gain of 100, three such amplifiers cascaded, would be required.

Now, if each of the 3 stages, has a low-frequency (d) closed loop gain K , then its 3db frequency will be $\frac{40}{K} \text{MHz}$. Thus for each stage the closed loop gain is: $|G| = \frac{K}{\sqrt{1 + \left(\frac{f}{\frac{40}{K}}\right)^2}}$

which at $f = 5 \text{MHz}$ becomes:

$$|G_{5\text{MHz}}| = \frac{K}{\sqrt{1 + \left(\frac{5}{\frac{40}{K}}\right)^2}}$$

The overall gain of 100: $100 = \left[\frac{K}{\sqrt{1 + \left(\frac{5}{\frac{40}{K}}\right)^2}} \right]^3$

$$K = 5.7$$

Thus for each cascade stage: $f_{3db} = \frac{40}{5.7}$
 $f_{3db} = 7 \text{MHz}$

The 3db frequency of the overall amplifiers, f_1 , can be calculated as:

$$\left[\frac{5.7}{\sqrt{1 + \left(\frac{5}{7}\right)^2}} \right]^3 = \frac{(5.7)^3}{\sqrt{2}} \Rightarrow f_1 = 3.6 \text{MHz}$$

2.91

$$a) \frac{R_2}{R_1} = K \quad f_{3db} = \frac{f_c}{1 + \frac{R_2}{R_1}} = \frac{f_c}{1+K}$$

$$\text{GBP} = \text{Gain} \times f_{3db}$$

$$\text{GBP} = K \frac{f_c}{1+K}$$

$$b) 1 + \frac{R_2}{R_1} = K \quad f_{3db} = \frac{f_c}{K}$$

$$\text{GBP} = K \frac{f_c}{K} = f_c$$

The non-inverting amplifier realizes a higher GBP and it's independent of K .

2.92

To find f_{3db} we use superposition:


Set $V_2 = 0$

Now using Thevenin's Theorem to simplify the input circuit results in:



Cont.
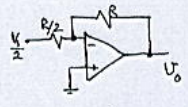
$$\frac{V_o}{V_i} = \frac{-R/R_{12}}{1 + \frac{R/R_{12}}{w_e}}$$



which gives:

$$\frac{V_o}{V_i} = \frac{-1}{1 + 5/(w_e/3)}$$

Thevenin's equivalent

$$f_{3dB} = \frac{f_{\omega}}{3}$$


Similar results can be obtained for $\frac{V_o}{V_a}$.

2.93

The peak value of the largest possible sine wave that can be applied at the input without output clipping is: $\frac{\pm 12V}{100} = 0.12V = 120mV$
 rms value = $\frac{120}{\sqrt{2}} = 85mV$

2.94

a) $R_L = 1k\Omega$

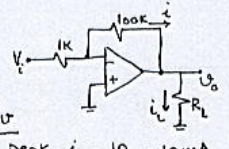

for $V_{omax} = 10V$: $V_p = \frac{10}{100}$
 $V_p = 0.1V$
 when output is at its peak, $i_L = \frac{10}{1k} = 10mA$
 $i = \frac{10}{100k} = 0.1mA$. therefore $i_o = 10 + 0.1 = 10.1mA$
 is well under $i_{omax} = 20mA$.

b) $R_L = 100\Omega$


If output is at its peak: $i_L = \frac{10V}{0.1} = 100mA$
 which exceeds $i_{omax} = 20mA$. Therefore V_o cannot go as high as $10V$. instead:
 $20mA = \frac{V_o}{100\Omega} + \frac{V_o}{100k} \Rightarrow V_o = \frac{20}{10.01} = 2V$
 $V_p = \frac{2}{100} = 0.02V = 20mV$

c) $R_L = ?$ $i_{o,max} = 20mA = \frac{10V}{R_{min}} + \frac{10V}{100k}$
 $20 \cdot 0.1 = \frac{10}{R_{min}} \Rightarrow R_{min} = 502\Omega$

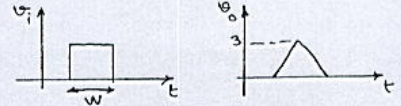
2.95

The output is triangular with the slew rate

of $20V/\mu s$. In order to reach $3V$, it takes $\frac{3}{20} \mu s = 0.15 \mu s = 150ns$.
 Therefore the minimum pulse width is $150ns$.



2.96

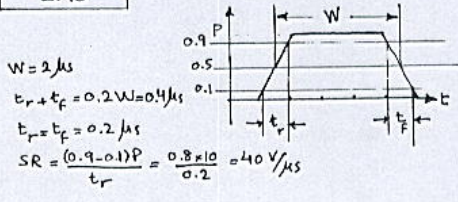

2.97

Slope of the triangle wave = $\frac{20V}{T/2} = SR$
 Thus $\frac{20}{T} \times 2 = 10V/\mu s$
 $\Rightarrow T = 4\mu s$ or $f = \frac{1}{T} = 250kHz$
 For a sine wave $V_o = V_o \sin(2\pi \times 250 \times 10^3 t)$
 $\frac{dV_o}{dt} = 2\pi \times 250 \times 10^3 V_o = SR$
 $\Rightarrow V_o = \frac{10 \times 10^6}{2\pi \times 10^3 \times 250} = 6.37V$

2.98

$V_o = 10 \sin \omega t \Rightarrow \frac{dV_o}{dt} = 10\omega \cos \omega t \Rightarrow \left. \frac{dV_o}{dt} \right|_{max} = 10\omega$
 The highest frequency at which this $\left. \frac{dV_o}{dt} \right|_{max}$ output is possible is that for which:
 $\left. \frac{dV_o}{dt} \right|_{max} = SR \Rightarrow 10\omega_{max} = 60 \times 10^6 \Rightarrow \omega_{max} = 6 \times 10^6$
 $\Rightarrow f_{max} = 45.5 kHz$.

2.99

a) $V_i = 0.5$, $V_o = 10 \times 0.5 = 5V$
 Cond.

Output distortion will be due to slew rate limitation and will occur at the frequency

for which $\left. \frac{dV_o}{dt} \right|_{\max} = SR$

$$\omega_{\max} \times 5 = \frac{1}{10^{-8}} = 2 \times 10^8 \text{ rad/s} \Rightarrow f_{\max} = 31.8 \text{ kHz}$$

b) The output will distort at the value of

V_i that results in $\left. \frac{dV_o}{dt} \right|_{\max} = SR$.

$$V_o = 10 V_i \sin 2\pi \times 20 \times 10^3 t$$

$$\left. \frac{dV_o}{dt} \right|_{\max} = 10 V_i \times 2\pi \times 20 \times 10^3$$

$$\text{Thus } V_i = \frac{1/10^{-6}}{10 \times 2\pi \times 20 \times 10^3} = 0.795 \text{ V}$$

c) $V_i = 50 \text{ mV}$ $V_o = 500 \text{ mV} = 0.5 \text{ V}$

Slew rate begins at the frequency for which $\omega \times 0.5 = SR$

$$\text{which gives } \omega = \frac{1/10^{-6}}{0.5} = 2 \times 10^6 \text{ rad/s or } f = 318 \text{ kHz}$$

However the small signal 3db frequency is

$$f_{3db} = \frac{f_0}{1 + \frac{R_2}{R_1}} = \frac{2 \times 10^6}{10} = 200 \text{ kHz}$$

Thus the useful frequency range is limited at 200 kHz.

d) for $f = 5 \text{ kHz}$, the slew rate limitation

occurs at the value of V_i given by

$$\omega \times 10 V_i = SR \Rightarrow V_i = \frac{1/10^{-6}}{2\pi \times 5 \times 10^3 \times 10} = 318 \text{ V}$$

Such an input voltage, however would ideally result in an output of 318V which exceeds

V_{omax} . Thus $V_{i\text{max}} = \frac{V_{\text{omax}}}{10} = 1 \text{ V peak}$.

2.100

$$V_o = V_{os} \left(1 + \frac{R_2}{R_1}\right) \Rightarrow -0.3 = V_{os} \left(1 + \frac{100}{1}\right) \approx 3 \text{ mV}$$

2.101

$$V_{os} = \pm 2 \text{ mV}$$

$$V_o = 0.01 \sin \omega t \times 200 + V_{os} \times 200 = 2 \sin \omega t \pm 0.4 \text{ V}$$

2.102

Output DC offset, $V_{os} = 3 \text{ mV} \times 1000 = 3 \text{ V}$

Therefore the maximum amplitude of an input


sinusoid is the one that results in an output peak amplitude of $13.3 = 10 \text{ V} \Rightarrow V_i = \frac{10}{1000} = 10 \text{ mV}$

If the amplifier is capacity coupled, then:

$$V_{i\text{max}} = \frac{13}{1000} = 13 \text{ mV}$$

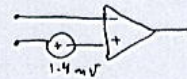2.103

$$V_{os} = \frac{1.4}{100} = 1.4 \text{ mV}$$



2.104

$$a) I_B = (I_{B1} + I_{B2})/2$$

open input:

$$V_o = V_i + R_2 I_{B1} = V_{os} + R_2 I_{B1}$$

$$9.31 = V_{os} + 10000 I_{B1} \quad (1)$$

input connected to ground:

$$V_o = V_i + R_2 \left(I_{B1} + \frac{V_{os}}{R_1} \right) = V_{os} \left(1 + \frac{R_2}{R_1} \right) + R_2 I_{B1}$$

$$9.09 = V_{os} \times 101 + 10000 I_{B1} \quad (2)$$

$$(1), (2) \Rightarrow 100 V_{os} = -0.22 \Rightarrow V_{os} = -2.2 \text{ mV}$$

$$\Rightarrow I_{B1} = 930 \text{ nA}$$

$$I_B \approx I_{B1} = 930 \text{ nA}$$

$$b) V_{os} = -2.2 \text{ mV}$$

c) In this case, since

R_1 is too large, we may

ignore V_{os} compare to



the voltage drop across R_1 .

$R_1 = 10 \text{ M}\Omega$


$V_{os} \ll R_1 I_B$, Also Eq. 2.46 holds: $R_3 = R_1 \parallel R_2$

therefore from Eq. 2.47: $V_o = I_{os} \times R_2 \Rightarrow I_{os} = \frac{-0.8}{10^4}$

$$I_{os} = -80 \text{ nA}$$

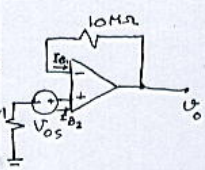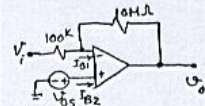

2.105

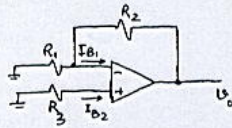


$R_2 = 100k\Omega$
 $R_1 = \frac{100k\Omega}{9}$
 $R_3 = 5k\Omega$
 $I_{B1} = 1 \pm 0.05 \mu A, V_{os} = 0$
 $I_{B2} = 1 \mp 0.05 \mu A$
 From Eq. 2.45: $V_o = -I_{B2}R_2 + R_2(I_{B1} - I_{B2}\frac{R_2}{R_1})$
 For $I_{B1} = 1.05 \mu A, I_{B2} = 0.95 \mu A$
 $V_o = -0.95 \times 5 + 100(1.05 - 0.95 \times \frac{5}{100} \times 9) = 57.5 mV$

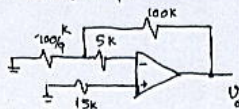
b) For $I_{B1} = 0.95 \mu A, I_{B2} = 1.05 \mu A$
 $V_o = -1.05 \times 5 + 100(0.95 - 1.05 \times \frac{5}{100} \times 9) = 42.5 mV$
 $\Rightarrow 42.5 mV \leftarrow V_o \leftarrow 57.5 mV$

From the discussion in the text we know that to minimize the DC output voltage resulting from the input bias current, we should make the total DC resistance in the inputs of the op-amp equal. Currently, the negative input sees a resistance of $R_1 \parallel R_2 = \frac{100}{9} \parallel 100 = 10k\Omega$ while the positive input terminal sees $5k\Omega$ source resistance. Therefore we should add $5k\Omega$ series resistor to the positive input terminal to make the effective resistance $5k\Omega + 5k\Omega = 10k\Omega$. The resulting V_o can be found as follows:
 $V_o = -I_{B2} \times 10 + 100(I_{B1} - I_{B2} \frac{10}{100}) = (I_{B1} - I_{B2}) \times 100$
 $V_o = I_{os} \times 100 = \pm 0.1 \times 100 = \pm 10 mV$
 $V_o = \pm 10 mV$

If the signal source resistance is $15k\Omega$, then the resistances can be equalized by adding a $5k\Omega$ resistor in series with the negative input load of the op-amp.



2.106

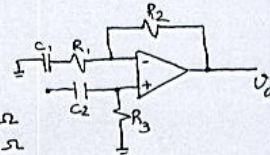

$R_2 = R_3 = 100k\Omega$
 $1 + \frac{R_2}{R_1} = 200$
 $R_1 = \frac{100k}{199} = 502\Omega$
 $\approx 500\Omega$
 $\frac{1}{R_1 C_1} = 2\pi \times 100 \Rightarrow C_1 = \frac{1}{500 \times 2\pi \times 100} = 3.18 \mu F$
 $\frac{1}{R_3 C_2} = 2\pi \times 10 \Rightarrow C_2 = \frac{1}{100 \times 2\pi \times 10} = 0.16 \mu F$

2.107

The output component due to V_{os} is:


$V_{o1} = V_{os} (1 + \frac{1M}{10k})$
 $V_{o1} = 4(1+100) = 404 mV$

The output component due to I_B or input bias current is:

$I_{B1} = I_B + \frac{I_{os}}{2}, I_{B2} = I_B - \frac{I_{os}}{2}$
 $I_{B1} = 0.3 + \frac{0.05}{2} = 0.325 \mu A, I_{B2} = 0.275 \mu A$
 $V_p = -I_{B2} \times (10k \parallel 1M)$
 $V_p = -2.72 mV$
 $V_{o2} = V_p + (1M) \times (I_{B1} + \frac{V_p}{10k})$
 $V_{o2} = 50 mV$

The worst case (largest) DC offset voltage at the output is $404 + 50 = 454 mV$

2.108

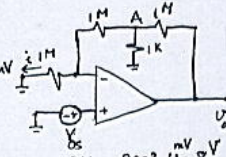

$V_p = V_{os} \Rightarrow V_o = 2V_{os} = 8 mV$
 $i = \frac{V_{os}}{1M} = V_{os} (\mu A)$
 $V_o = V_p + 1M \times (i + \frac{V_o}{1k})$
 $V_o = 2V_{os} + 1M (\frac{V_{os}}{1M} + \frac{2V_{os}}{1k}) = 2003V_{os} = 2003 \times 4 = 8 V$
 $V_o = 8V$

Cont.


for capacitively coupled input:

$$V_+ = V_- = V_{os}$$

$$V_A = V_{os}$$

$$V_o = V_A + 1M \times \frac{V_{os}}{1k}$$

$$V_o = 1001 V_{os} = \pm 21.004V$$

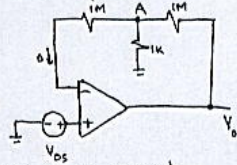


for capacitively coupled 1k to ground:

$$V_+ = V_- = V_{os}$$

$$V_A = 2V_{os}$$

$$V_o = 3V_{os} = \pm 2mV$$

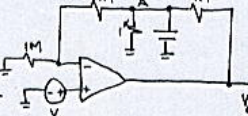

This is much smaller than capacitively coupled in V_{os} case.

2.109

At $0^\circ C$, we expect $\pm 10 \times 25 \times 1000^\mu = \pm 250mV$
 At $75^\circ C$, we expect $\pm 10 \times 50 \times 1000^\mu = \pm 500mV$
 We expect these quantities to have opposite polarities.

2.110

$$100 = 1 + \frac{R_2}{R_1} \Rightarrow R_1 = 10.1k\Omega$$

$$a) V_o = 100 \times 10^{-9} \times 1 \times 10^6 = 0.1V$$

b) largest output offset is:

$$V_o = 1mV \times 100 + 0.1V = 200mV = 0.2V$$


c) for bias current compensation we connect

a resistor R_3 in series with the positive input terminal of the op-amp, with: $R_3 = R_1 \parallel R_2$

$$I_{os} = \frac{100}{10} = 10nA \quad R_3 = 10k \parallel 11M = 10k\Omega$$

The offset current alone results in an output offset voltage of $I_{os} \times R_2 = 10 \times 10^{-9} \times 1 \times 10^6 = 10mV$


$$d) V_o = 100mV + 10mV = 110mV$$

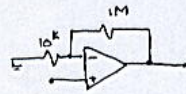

2.111

$$R_3 = R_1 \parallel R_2 = 9.9k\Omega$$

(Refer to 2.46)

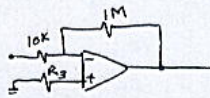


$$V_o = I_{os} R_2 \quad \text{Eq. 2.47}$$

$$V_o = 0.21 = I_{os} \times 1M \Rightarrow I_{os} = 0.21 \mu A$$

$$\text{If } V_{os} = 1mV$$

$$V_+ = -I_{B2} R_3 + V_{os}$$

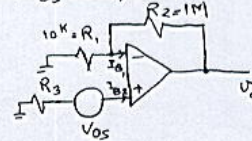

$$I_{B1} = \frac{R_2 I_{B2} + V_{os}}{R_1} + \frac{0.21 + R_2 I_{B2} + V_{os}}{R_2}$$

$$I_{B1} = R_3 I_{B2} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + V_{os} \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\frac{1}{R_3} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow I_{B1} - I_{B2} = \pm V_{os} \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\Rightarrow I_{os} = \pm \frac{1mV}{9.9k} = \pm 0.1 \mu A$$

If we apply the same current as I_{os} to the other end of R_3 , then it will cancel out the offset current effect on the output. $\pm 0.1 \mu A$

Now if we use $\pm 15V$ supplies:

2.112

$$\frac{V_o}{V_i} = \frac{-1}{sCR} = \frac{-1}{j\omega CR} = \frac{1}{-j\omega \times 10 \times 10^{-9} \times 100 \times 10^3}$$

$$\frac{V_o}{V_i} = \frac{-10^3}{j\omega}$$

$$a) \frac{V_o}{V_i} = 1 \Rightarrow \omega = \frac{10^3}{10} = 100 \text{ rad/s} \Rightarrow f = 15.9 \text{ Hz}$$

b) $\frac{1}{j}$ indicates 90° lag, but since it's $\frac{-1}{j}$, it results in output leading the input by 90°

c) $\frac{V_o}{V_i} = \frac{-10^3}{j\omega}$ if frequency is lowered by a factor of 10, then the output would increase by a factor of 10.


Cont.

d) The phase does not change and the output still leads the input by 90°

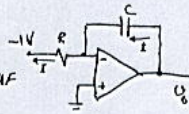2.113

$$R_{in} = R = 100k\Omega$$

$$CR = 15 \Rightarrow C = \frac{1}{100 \times 10^3} = 10nF$$




with a $-1V$ dc input applied, the capacitor charges with a constant current:

$I = \frac{1V}{R} = 0.01mA$ and its voltage rises linearly:

$$V_o(t) = -10 + \frac{1}{C} \int_0^t I dt = -10 + \frac{I}{C} t = -10 + \frac{t}{RC}$$

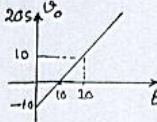the voltage reaches $0V$ at $t = 10RC = 10s$ and it reaches $10V$ at $t = 20s$



2.114

$|T| = \frac{1}{\omega RC}$ If $|T| = 100 \frac{V}{V}$ for $f = 1kHz$, then for $|T| = 1 \frac{V}{V}$, f has to be $1^k \times 100 = 100k Hz$.

$$\text{Also } RC = \frac{1}{\omega \cdot T} = \frac{1}{2\pi \times 1^k \times 100} = 1.59 \mu s$$

2.115



$R_{in} = R$, Thus $R = 100k\Omega$.

$$|T| = \frac{1}{\omega RC} = 1 \text{ at } \omega = \frac{1}{RC}$$

$$\omega = 1000 = \frac{1}{RC} \Rightarrow C = \frac{1}{1000 \times 10^3} = 10nF$$

with a $2V$ - $2ms$ pulse at the input, the output falls linearly until $t=2ms$ at which $V_o = V_i$, $V_o = \frac{-I}{C} t = \frac{-2}{RC} t = -2t$ Volts where t in ms

$$\text{Thus } V_i = -4V$$

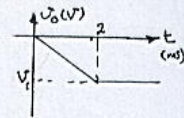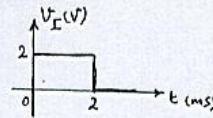

with $V_i = 2 \sin 1000t$ applied at the input,

$$V_o(t) = 2 \times \frac{1}{1000 \times 10^3} \sin(1000t + 90^\circ)$$

$$V_o(t) = 2 \sin(1000t + 90^\circ)$$

2.116



$$R_{in} = R = 20k\Omega$$

$$|T| = \frac{1}{\omega RC} = 1 \text{ at } \omega = 2\pi \times 10^4 \text{ Hz} \Rightarrow C = \frac{1}{2\pi \times 10^4 \times 20^k} = 0.796 nF$$

Refer to discussion in page 110:

$\frac{V_o}{V_i} = \frac{R_F/R}{1 + sCR_F}$ and the finite dc gain is $\frac{-R_F}{R}$. There fore for 40db gain or equivalently $100 \frac{V}{V}$ we have: $\frac{-R_F}{R} = -100 \frac{V}{V}$
 $\Rightarrow R_F = 100 \times 20k = 2M\Omega$

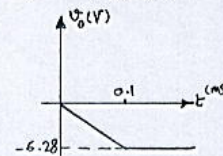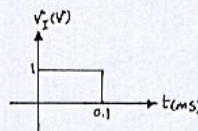The corner frequency $\frac{1}{C R_F}$ is: $\frac{1}{0.796 \times 2^M} = 628$ Hz



a) when no R_F

$$V_o(t) = \frac{1}{RC} \int_0^t 1 \cdot dt = -62.8t \quad 0 \leq t \leq 0.1ms$$


$$V_o(0.1) = -6.28V$$

b) with R_F : $V_o(t) = V_o(\infty) (1 - e^{-t/CR_F})$

(Refer to pg. 112)


$$V_o(\infty) = -I \times R_F = -\frac{1V}{20k} \times 2^M = -100V$$

$$V_o(t) = -100(1 - e^{-t/1.5})$$

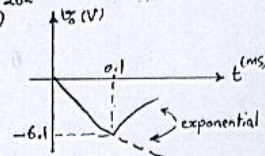

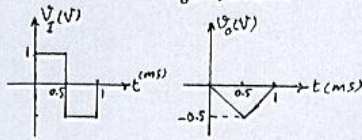2.117

For $0 \leq t \leq 0.5 \text{ ms}$: $V_o(t) = V_o(0) - \frac{1}{RC} \int_0^t V_i dt$
 $V_o(t) = 0 - \frac{t}{RC} = -\frac{t}{1 \text{ ms}}$
 $V_o(0.5) = -0.5 \text{ V}$



For $0.5 \leq t \leq 1 \text{ ms}$: $V_o(t) = V_o(0.5) - \frac{1}{RC} \int_{0.5}^t -1 dt$
 $V_o(t) = -0.5 + \frac{1}{RC} (t - 0.5)$
 $V_o(1 \text{ ms}) = -0.5 + 0.5 = 0 \text{ V}$

Another way of thinking about this circuit is as follows:


for $0 \leq t \leq 0.5 \text{ ms}$ a current $I = \frac{V_i}{R}$ flows through R and C in the direction indicated on the diagram. At time t we write:

$I \cdot t = -C \frac{dV_o(t)}{dt} \Rightarrow V_o(t) = -\frac{I}{C} t = -\frac{1}{RC} t$

which indicates that the output voltage is linearly decreased, reaching -0.5 V at $t = 0.5 \text{ ms}$.

Then for $0.5 \leq t \leq 1 \text{ ms}$, the current flows in the opposite direction and V_o rises linearly reaching 0 V at $t = 1 \text{ ms}$.

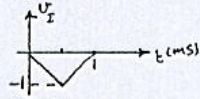For $V_i = \pm 2 \text{ V}$: we obtain the following waveform: (assuming time constant is the same)




If RC is also doubled, then the waveform becomes the same as the first case where $V_i = \pm 1 \text{ V}$ and $RC = 1 \text{ ms}$.

2.118

Each pulse lowers the output voltage by:

$\Delta V_o = \frac{1}{RC} \int_0^{10 \text{ ms}} 1 \cdot dt = \frac{10 \text{ ms}}{RC} = \frac{10 \text{ ms}}{1 \text{ ms}} = 10 \text{ mV}$

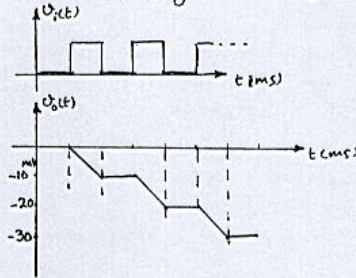Therefore a total of 100 pulses are required to cause a change of 1 V in $V_o(t)$.



2.119

Refer to Fig. P2.119.

$\frac{V_o}{V_i} = -\frac{Z_2}{Z_1} = -\frac{Y_1}{Y_2} = -\frac{1/R_1}{1/R_2 + sC} = -\frac{R_2/R_1}{1 + sCR_2}$

which is an STC LP circuit with a dc gain of $-\frac{R_2}{R_1}$ and a 3-dB frequency $\omega_0 = \frac{1}{CR_2}$.


The input resistance equal to R_1 . So for:

$R_1 = 1 \text{ k} \Rightarrow R_1 = 1 \text{ k}\Omega$ and for dc gain of 20 dB


$10 : \frac{R_2}{R_1} = 10 \Rightarrow R_2 = 10 \text{ k}\Omega$

for 3dB frequency of 4 kHz: $\omega_0 = 2\pi f + \times 10^3 = \frac{1}{CR_2}$
 $\Rightarrow C \approx 4 \text{ nF}$

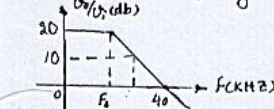the unity gain frequency is (0dB) is 40 kHz




2.120

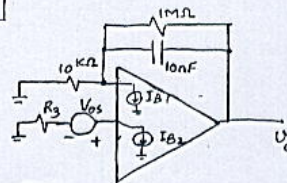

Cont.

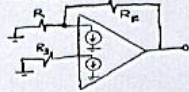a) To compensate for the effect of dc bias current I_B , we can consider the following model



Similar to the discussion leading to equation (2.16) we have: $R_3 = R \parallel R_F = 10k\Omega \parallel 1M\Omega \Rightarrow R_3 = 9.9k\Omega$

(b) As discussed in Section 2.3.2 the dc output voltage of the integrator when the input is grounded is: $V_o = V_{os} (1 + \frac{R_F}{R}) + I_{os} R_F$
 $V_o = 3mV (1 + \frac{1M\Omega}{10k\Omega}) + 10nA \times 1M\Omega = 0.303V + 0.01V$
 $V_o = 0.313V$

2.121

$$\frac{V_o}{V_i} = -sRC = -s \times 0.01 \times 10^{-6} \times 10 \times 10^3 = -10^{-4} s$$

$$\frac{V_o}{V_i}(j\omega) = -j\omega \times 10^{-4} \Rightarrow \left| \frac{V_o}{V_i} \right| = \omega \times 10^{-4} \Rightarrow$$

$$\left| \frac{V_o}{V_i} \right| = 1 \text{ when } \omega = 10^4 \text{ Rad/s or } f = 1.59 \text{ KHz}$$

For an input 10 times this frequency, the output will be 10 times as large as the input: 10V peak-to-peak. The (-j) indicates that the output lags the input by 90°. Thus $V_o(t) = -5 \sin(10^5 t + 90^\circ) \text{ Volts}$

2.122


$$V_o = -RC \frac{dV_i}{dt}$$

therefore:




for $0 \leq t \leq 0.5$:

$$V_o = -1mS \times \frac{1V}{0.5ms} = -2V$$

and $V_o = 0$ otherwise

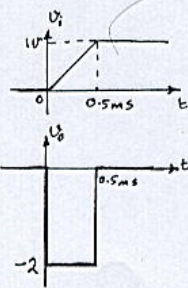

2.123

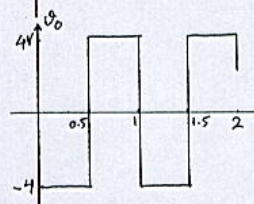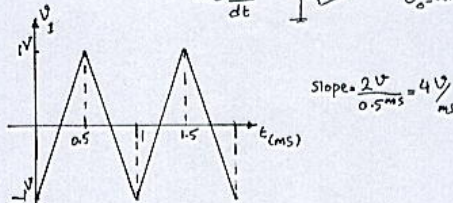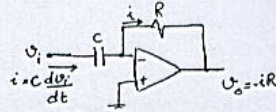

$$C \frac{dV_i}{dt} = 0.1 \times 10^{-6} \times \frac{4}{10^{-3}} = 0.4 \text{ mA}$$

Thus the peak value of the output square wave is $0.4 \text{ mA} \times 10^4 \Omega = 4V$. The frequency of the output is the same as the input (1KHz).

The average value of the output is 0.

To increase the value of the output to 10V, R has to be increased to $\frac{10}{4} = 2.5$, i.e. $25k\Omega$.

When a 1-KHz, 1V peak input sine wave is applied

$$V_i = \sin(2\pi \times 1000 t)$$

a sinusoidal signal appears at the output.

It can be determined by one of the following methods:


$$V_o(t) = -RC \frac{dV_i}{dt} = -0.1 \times 10^{-6} \times 10 \times 10^3 \frac{dV_i}{dt} = -10^{-3} \frac{dV_i}{dt}$$

$$V_o(t) = -10^{-3} \times 2\pi \times 1000 \times \cos(2\pi \times 1000 t)$$

$$V_o(t) = -2\pi \cos(2\pi \times 1000 t)$$

Thus the peak amplitude is 6.28V and the negative peaks occur at $t = 0, \frac{2\pi}{2\pi \times 1000}, \dots$

Cont.

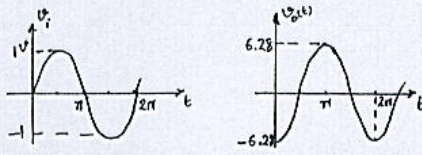

b) $\frac{V_o}{V_i} = -sRC \Rightarrow \frac{V_o}{V_i}(j\omega) = -j\omega RC \Rightarrow V_o(t) = -j\omega RC V_i(t)$

the output is inverted and has 90° phase shift, due to $(-j)$ factor.

$V_o(t) = -(\omega RC) \times 1 \sin(2\pi \times 1000t + 90^\circ)$

$V_o(t) = -6.28 \sin(2\pi \times 1000t + 90^\circ)$

$V_o(t) = -6.28 \cos(2\pi \times 1000t)$

Same as before.

c) The peaks of the output waveform are equal to $RC \times$ (maximum slope of input wave). Since the maximum slope occurs at the zero crossings, its value is $2\pi \times 1000$. Thus the peak output $= 2\pi \times 1000 \times RC = 6.28V$

The negative peak occurs at $\omega t = 0, 2\pi, \dots$

2.124


$RC = 10^{-3}$ when $C = 10^{-7}F \Rightarrow R = 100k\Omega$

$\frac{V_o}{V_i} = -sRC \Rightarrow \frac{V_o}{V_i}(j\omega) = -j\omega RC \quad \phi = -90^\circ$
always

$|\frac{V_o}{V_i}| = 1 \Rightarrow \omega = \frac{1}{RC} \Rightarrow$ Gain is 10 times the unity

gain, when the frequency is 10 times the unity gain frequency. Similarly for $\omega = \frac{1}{10} \frac{1}{RC}$, gain is

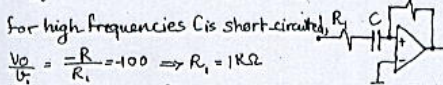$0.1 \times V_o$. (For $\omega = 10 \text{krad/s}$, gain $= 10 \times V_o$)



For high frequencies C is short-circuited, $\frac{V_o}{V_i} = -\frac{R}{R_1} = -100 \Rightarrow R_1 = 1k\Omega$

$\frac{V_o}{V_i} = \frac{-RCs}{R_1Cs + 1} = \frac{-10s}{10^{-5}s + 1} \Rightarrow \omega_{3dB} = 100 \text{krad/s}$ or $f = 15.9 \text{kHz}$

For unity gain: $|10^{-3}| = |10^{-5}s + 1| \Rightarrow \omega = 1.01 \text{krad/s}$

if $\omega = 10.1 \text{krad/s}$: $|\frac{V_o}{V_i}| = \frac{10.1}{1.01} = 10, \quad \phi = -95.7^\circ$

2.125

Refer to Fig. p2.125:

$\frac{V_o}{V_i} = -\frac{Z_2}{Z_1} = -\frac{R_2}{R_1 + \frac{1}{sC}} = \frac{-(\frac{R_2}{R_1})s}{s + \frac{1}{R_1C}}$ which is the

transfer function of an STC HP filter with a high frequency gain $K = -\frac{R_2}{R_1}$ and a

3-dB frequency $\omega_0 = \frac{1}{R_1C}$

The high-frequency input impedance approaches R_1 (as $\frac{1}{j\omega C}$ becomes negligibly small) So we can select $R_1 = 10k\Omega$

To obtain a high-frequency gain of 40db


(i.e. 100): $\frac{R_2}{R_1} = 100 \Rightarrow R_2 = 1M\Omega$.

For a 3-dB frequency of 1000 Hz:

$\frac{1}{R_1C} = 2\pi \times 1000 \Rightarrow C = 15.9 \text{nF}$

from the Bode diagram below, we see that

$|\frac{V_o}{V_i}|$ reduces to unity at $f = 0.01 f_0 = 10 \text{Hz}$

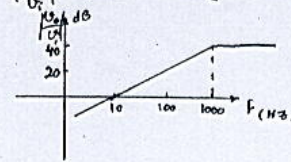

2.126

Refer to the circuit in Fig. P2.126:

$\frac{V_o}{V_i} = -\frac{Z_2}{Z_1} = -\frac{1}{Z_1 Z_2} = -\frac{1}{(R_1 + \frac{1}{sC_1})(\frac{1}{R_2} + sC_2)}$

$\frac{V_o}{V_i} = -\frac{R_2/R_1}{(1 + \frac{1}{R_1 C_1 s})(1 + sR_2 C_2)}$

$\frac{V_o}{V_i}(j\omega) = \frac{-R_2/R_1}{(1 + \frac{1}{j\omega R_1 C_1})(1 + j\omega R_2 C_2)} = \frac{-R_2/R_1}{(1 + \frac{j\omega}{\omega_1})(1 + j\omega/\omega_2)}$

where $\omega_1 = \frac{1}{R_1 C_1}$, $\omega_2 = \frac{1}{R_2 C_2}$

a) for $\omega \ll \omega_1 \ll \omega_2$

$\frac{V_o}{V_i}(j\omega) \approx \frac{-R_2/R_1}{(1 + \frac{j\omega}{\omega_1})} \approx \frac{-R_2/R_1}{\omega/\omega_1} = j \frac{R_2}{R_1} \frac{\omega}{\omega_1}$

Cont.


b) for $\omega_1 \ll \omega \ll \omega_2$

$$\frac{U_o}{U_i}(j\omega) \approx \frac{-R_2}{R_1}$$

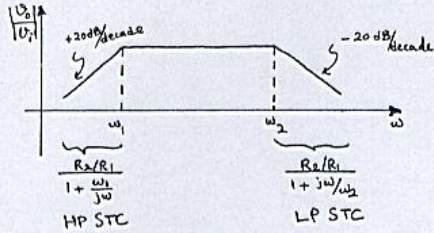c) for $\omega \gg \omega_2$ and $\omega_2 \gg \omega_1$:

$$\frac{U_o}{U_i}(j\omega) \approx \frac{-R_2/R_1}{1 + j\omega/\omega_2} \approx \frac{-R_2/R_1}{j\omega/\omega_2} = j \left(\frac{R_2}{R_1} \right) \left(\frac{\omega_2}{\omega} \right)$$

from the results of a), b) and c) we can draw the Bode-plot:



Design: $\frac{R_2}{R_1} = 1000$ (60dB gain in the mid-frequency range)

$$R_{in} \text{ for } \omega \gg \omega_1 = R_1 = 1 \text{ k}\Omega \Rightarrow R_2 = 1 \text{ M}\Omega$$

$$f_1 = 100 \text{ Hz} \Rightarrow \omega_1 = 2\pi \times 100 = \frac{1}{R_1 C_1} \Rightarrow C_1 = 1.59 \mu\text{F}$$

$$f_2 = 10 \text{ kHz} \Rightarrow \omega_2 = 2\pi \times 10 \times 10^3 = \frac{1}{R_2 C_2} \Rightarrow C_2 = 15.9 \text{ pF}$$