

## CHAPTER 12 - PROBLEMS

12.1

$$T(s) = \frac{\omega_0}{s + \omega_0} \quad T(j\omega) = \frac{\omega_0}{j\omega + \omega_0}$$

$$|T(j\omega)| = \frac{\omega_0}{\sqrt{\omega_0^2 + \omega^2}}$$

$$\phi(\omega) \triangleq \tan^{-1} \left[ \frac{\text{Im}(T(j\omega))}{\text{Re}(T(j\omega))} \right]$$

$$= -\tan^{-1} \omega/\omega_0$$

$$G = 20 \log_{10} |T(j\omega)|$$

$$A = -20 \log_{10} |T(j\omega)|$$

$\omega$	$ T(j\omega) $ [V/V]	G [dB]	A [dB]	$\phi$ °
0	1	0	0	0
0.5 $\omega_0$	0.8944	-0.97	0.97	-26.57
$\omega_0$	0.7071	-3.01	3.01	-45.0
2 $\omega_0$	0.4472	-6.99	6.99	-63.43
5 $\omega_0$	0.1961	-14.1	14.1	-78.69
10 $\omega_0$	0.0995	-20.0	20.0	-84.29
100 $\omega_0$	0.010	-40.0	40.0	-89.43

12.2

$$T(s) = \frac{1}{(s+1)(s^2+s+1)}$$

$$= \frac{1}{s^3 + 2s^2 + 2s + 1}$$

$$T(j\omega) = \left[ j(2\omega - \omega^3) + (1 - 2\omega^2) \right]^{-1}$$

$$\begin{aligned} |T(j\omega)| &= \left[ (2\omega - \omega^3)^2 + (1 - 2\omega^2)^2 \right]^{-1/2} \\ &= \left[ 4\omega^2 - 4\omega^4 + \omega^6 + 1 - 4\omega^2 + 4\omega^4 \right]^{-1/2} \\ &= \left[ 1 + \omega^6 \right]^{-1/2} \\ &= \frac{1}{\sqrt{1 + \omega^6}} \end{aligned}$$

For Phase Angle:

$$\begin{aligned} \phi(\omega) &= \tan^{-1} \left[ \frac{\text{Im}[T(j\omega)]}{\text{Re}[T(j\omega)]} \right] \\ &= -\tan^{-1} \left[ \frac{2\omega - \omega^3}{1 - 2\omega^2} \right] \end{aligned}$$

For  $\omega = 0.1$ :

$$\begin{aligned} |T(j\omega)| &= (1 + 0.1^6)^{-1/2} \approx \underline{\underline{1}} \\ \phi(\omega) &= -11.5^\circ = \underline{\underline{-0.20 \text{ rad}}} \end{aligned}$$

For  $\omega = 1 \text{ rad/s}$ :

$$\begin{aligned} |T(j\omega)| &= (1 + 1^6)^{-1/2} = 1/\sqrt{2} = \underline{\underline{0.7}} \\ \phi &= -\tan^{-1}(1/-1) = -135^\circ = \underline{\underline{2.356}} \end{aligned}$$

Note:  $G = -3 \text{ dB}$

$$\begin{aligned} \text{Also: } \tan^{-1}(-1) &= -45^\circ \text{ or } -135^\circ \\ \tan^{-1}(-1/1) &= -45^\circ \\ \tan^{-1}(1/-1) &= -135^\circ \end{aligned}$$

For  $\omega = 10 \text{ rad/s}$ :

$$\begin{aligned} |T(j\omega)| &= (1 + 10^6)^{-1/2} = \underline{\underline{0.001}} \\ \phi &= -\tan^{-1} \left[ \frac{2(10) - 10^3}{1 - 2(10^2)} \right] \end{aligned}$$

CONT.

$$\begin{aligned}
 &= -\tan^{-1} \left[ \frac{-980}{-199} \right] \\
 &= - \left[ 180^\circ + \tan^{-1} \left( \frac{980}{199} \right) \right] \\
 &= -258.5^\circ \\
 &= \underline{\underline{4.512 \text{ rad}}}
 \end{aligned}$$

Now consider an input of  $A \sin \omega t$  to  $T(s)$ . The output is then given by:


$$A |T(j\omega)| \sin(\omega t + \phi(\omega))$$

Using this result, the output to each of the following inputs will be:

INPUT	OUTPUT
$2 \sin(0.1t)$	$2 \sin(0.1t - 0.2)$ i.e. $2 \times 1 = 2$
$2 \sin(1t)$	$\sqrt{2} \sin(t - 2.356)$ i.e. $2 \times \frac{1}{\sqrt{2}} = \sqrt{2}$
$2 \sin(10t)$	$2 \times 10^{-3} \sin(10t - 4.512)$

12.3

12.4

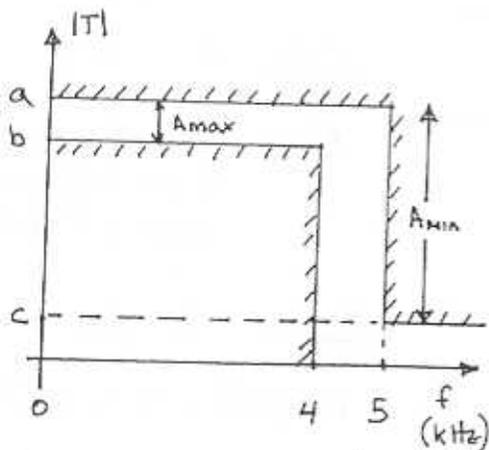

Note  $|T|$  is shown in a linear scale but  $A_{max}$  and  $A_{min}$  are in dB

From the problem


$$\frac{a}{b} = 1.1, \quad c = 0.1\% a \text{ or } \frac{c}{a} = 0.001$$

$$\begin{aligned}
 A_{max} &= 20 \log_{10} a - 20 \log_{10} b \\
 &= 20 \log_{10} \frac{a}{b} \\
 &= 20 \log_{10} (1.1) \\
 &= \underline{\underline{0.83 \text{ dB}}}
 \end{aligned}$$

$$\begin{aligned}
 A_{min} &= 20 \log_{10} a - 20 \log_{10} c \\
 &= 20 \log_{10} \left( \frac{a}{c} \right) \\
 &= 20 \log_{10} (0.001) \\
 &= \underline{\underline{60 \text{ dB}}}
 \end{aligned}$$

$$\text{Selectivity} = \frac{\omega_s}{\omega_p} = \frac{2\pi 5}{2\pi 4} = \underline{\underline{1.25}}$$

12.5

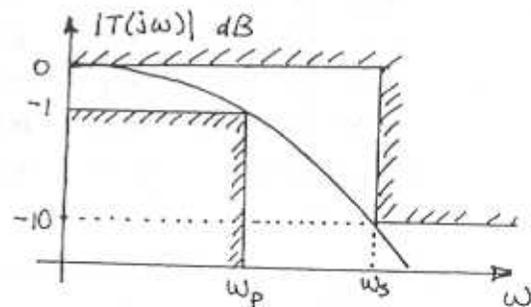

$$\begin{aligned}
 T(s) &= \frac{k}{1+s\tau} \\
 &= \frac{1}{1+s}
 \end{aligned}$$

If  $\tau=1s$  & the DC gain = 1 then  $\underline{\underline{k=1}}$

$$|T(j\omega)| = \frac{1}{\sqrt{1+\omega^2}}$$

At the passband edge :

CONT.

$$|T(j\omega_p)| = \frac{1}{\sqrt{1+\omega_p^2}} = 10^{-1/20}$$

$$\therefore \omega_p = \underline{0.5088 \text{ rad/s}}$$

At the stopband edge:

$$|T(j\omega_s)| = \frac{1}{\sqrt{1+\omega_s^2}} = 10^{-10/20}$$


$$\therefore \omega_s = \underline{3 \text{ rad/s}}$$

$$\text{Selectivity} = \frac{\omega_s}{\omega_p} = \frac{3}{0.5088} = \underline{5.9}$$

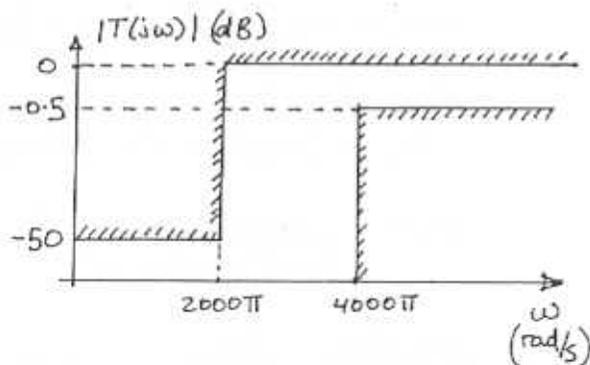12.6

Passband is defined by:  $f \geq 2 \text{ kHz}$   
 $\Rightarrow \omega_p = 2\pi(2000) \text{ rad/s}$

Stopband is defined by:  $f \leq 1 \text{ kHz}$   
 $\Rightarrow \omega_s = 2\pi(1000) \text{ rad/s}$




Note we assumed a maximum transmission of 0 dB.

12.7


Passband:  $f \in \{[0, 10 \text{ kHz}] \cup [20 \text{ kHz}, \infty]\}$

Stopband:  $f \in [12 \text{ kHz}, 16 \text{ kHz}]$
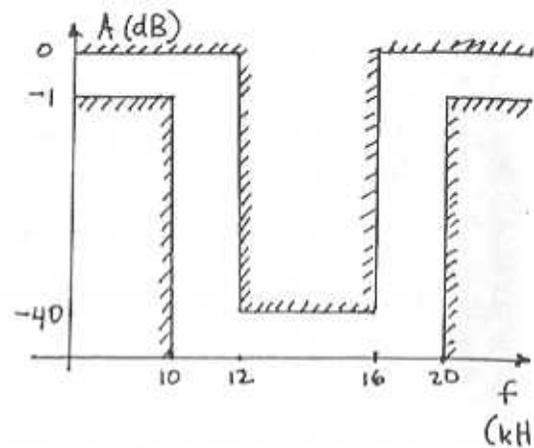
$$A_{\max} = 1 \text{ dB}, \quad A_{\min} = 40 \text{ dB}$$



12.8

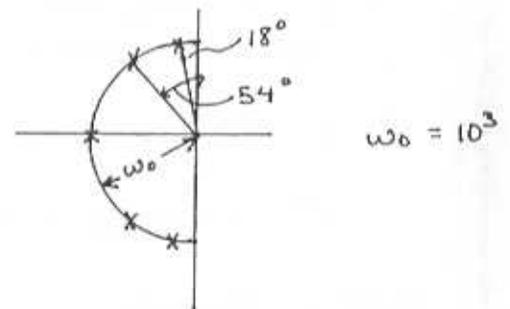

Poles at  $18^\circ$ :

$$\begin{aligned} P_1 &= \omega_0 (-\cos(90^\circ - 18^\circ) \pm j \sin(90^\circ - 18^\circ)) \\ &= \omega_0 (-\cos 72^\circ \pm j \sin 72^\circ) \\ &= \omega_0 (-0.309 \pm j 0.951) \end{aligned}$$

Poles at  $54^\circ$ :

$$\begin{aligned} P_2 &= \omega_0 (-\cos 36^\circ \pm j \sin 36^\circ) \\ &= \omega_0 (-0.809 \pm j 0.588) \end{aligned}$$

Poles on Real Axis

$$P_3 = -\omega_0$$

CONT.

Note: Given a pair of poles

$$P_i = \omega_0 (-\cos \alpha \pm j \sin \alpha),$$

introduces a second order term as follows:

$$\begin{aligned} & (s + \omega_0 \cos \alpha - j \omega_0 \sin \alpha)(s + \omega_0 \cos \alpha + j \omega_0 \sin \alpha) \\ &= s^2 + s(\omega_0 \cos \alpha - j \omega_0 \sin \alpha + \omega_0 \cos \alpha + j \omega_0 \sin \alpha) \\ & \quad + \omega_0^2 [\cos^2 \alpha + j \cos \alpha \sin \alpha - j \cos \alpha \sin \alpha + \sin^2 \alpha] \\ &= s^2 + s(2\omega_0 \cos \alpha) + \omega_0^2 \end{aligned}$$

So for  $P_1$  we get a term:

$$\begin{aligned} s^2 + s(2\omega_0 \cdot 0.309) + \omega_0^2 \\ = s^2 + 0.618\omega_0 s + \omega_0^2 \end{aligned}$$

For  $P_2$  we get:

$$s^2 + 1.618\omega_0 s + \omega_0^2$$

For  $P_3$ :  $(s + \omega_0)$

∴ The denominator of  $T(s)$  is given by

$$D(s) = \frac{(s + \omega_0)(s^2 + 0.618\omega_0 s + \omega_0^2) \times (s^2 + 1.618\omega_0 s + \omega_0^2)}{(s^2 + 1.618\omega_0 s + \omega_0^2)}$$

Case (a) - If all the zeros are @  $\infty$ , the numerator is a constant

$$|T(0)| = \frac{k}{\omega_0^5} = 1 \quad \text{for unity gain at DC}$$

$$\therefore k = \omega_0^5$$

$$T(s) = \frac{k}{D(s)} = \frac{\omega_0^5}{D(s)}$$

where  $D(s)$  is given above.

Case (b) - For all zeros at 0, the numerator is given by  $k s^5$

$$A s = j\omega \quad |T(s \rightarrow j\omega)| = \frac{k}{1} = 1$$

$$\therefore T(s) = \frac{s^5}{D(s)}$$

12.9

Poles at  $-1$  and  $-0.5 \pm j0.8$  gives a denominator:

$$\begin{aligned} D(s) &= (s+1)(s+0.5-j0.8)(s+0.5+j0.8) \\ &= (s+1)(s^2 + 2(0.5)s + 0.5^2 + 0.8^2) \\ &= (s+1)(s^2 + s + 0.89) \end{aligned}$$

Zeros at  $\infty$  and  $\pm j2$  give a numerator:

$$N(s) = k(s+j2)(s-j2) = k(s^2+4)$$

Note there is one zero at  $\infty$  because Degree( $D(s)$ ) - Degree( $N(s)$ ) = 1

$$T(s) = \frac{k(s^2+4)}{(s+1)(s^2+s+0.89)}$$

$$|T(j0)| = \frac{k(4)}{0.89} = 1 \quad \therefore \text{DC gain} = 1$$

$$\Rightarrow k = 0.2225$$

$$\therefore T(s) = \frac{0.2225(s^2+4)}{(s+1)(s^2+s+0.89)}$$

12.10

Numerator is given by

$$a_7 (s-0) (s^2 + (10^3)^2) (s^2 + (3 \times 10^3)^2) \times (s^2 + (6 \times 10^3)^2)$$

$$= a_7 s (s^2 + 10^6) (s^2 + 9 \times 10^6) (s^2 + 36 \times 10^6)$$


Degree of Numerator  $\triangleq M = 7$

Degree of Denominator  $\triangleq N$


Given that there is one zero at  $\infty$ :

$$N - M = 1 \Rightarrow \underline{N = 8}$$
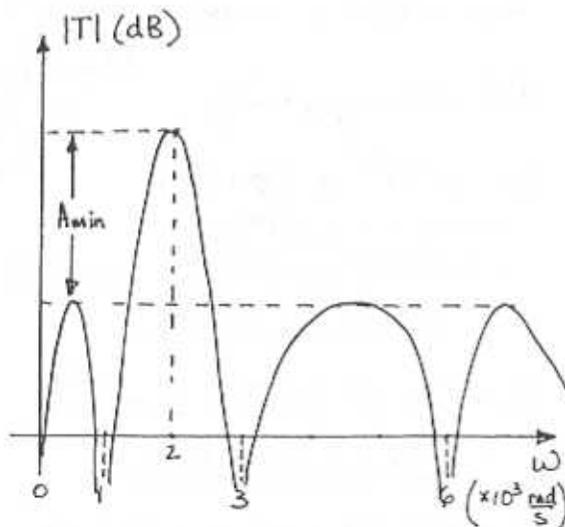
$$\therefore T(s) = \frac{a_7 s (s^2 + 10^6) (s^2 + 9 \times 10^6) (s^2 + 36 \times 10^6)}{s^8 + b_7 s^7 + b_6 s^6 + \dots + b_0}$$



12.11

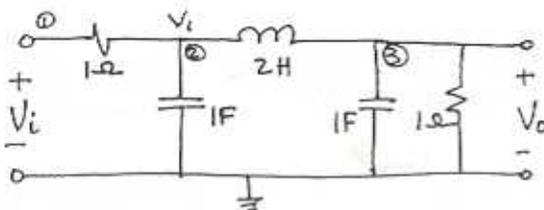

The easiest way to solve the circuit is to use nodal analysis at nodes ①, ②, ③

At node ③  $\sum I = 0$

$$\frac{V_0}{1} + \frac{V_0}{1/s} + \frac{V_0 - V_1}{2s} = 0$$

$$\therefore V_1 = V_0 (2s^2 + 2s + 1) \quad \text{Eq. (a)}$$

At node ②  $\sum I = 0$

$$\frac{V_1 - V_i}{1} + \frac{V_1}{1/s} + \frac{V_1 - V_0}{2s} = 0$$

$$\therefore V_1 (2s^2 + 2s + 1) = V_0 + 2sV_i \quad \text{Eq. (b)}$$

(a)  $\rightarrow$  (b)

$$V_0 (2s^2 + 2s + 1)^2 = V_0 + 2sV_i$$

$$V_0 (4s^4 + s^3(4+4) + s^2(2+4+2) + s(2+2) + 1) = V_0 + 2sV_i$$

$$\frac{V_0(s)}{V_i(s)} \triangleq T(s) = \frac{2s}{4s^4 + 8s^3 + 8s^2 + 4s}$$

$$T(s) = \frac{0.5}{s^3 + 2s^2 + 2s + 1}$$

Poles are given by:

$$s^3 + 2s^2 + 2s + 1 = 0$$

$$(s+1)(s^2 + s + 1) = 0$$

$$\therefore \text{Poles are } s = \underline{-1} \text{ and}$$

$$s = \underline{-\frac{1}{2} \pm j\frac{\sqrt{3}}{2}}$$

12.12

$$A_{\max} = 1 \text{ dB}, \quad A_{\min} = 20 \text{ dB}, \quad \omega_s/\omega_p = 1.3$$

Using:

$$A(\omega_s) = 10 \log \left[ 1 + \epsilon^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right] \quad \text{Eq. (12.15)}$$

$$= A_{\min}$$

CONT

$$\epsilon = [10^{10} - 1]^{1/2} = 0.5088$$

$$A_{min} = 10 \log \left[ 1 + \epsilon^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right]$$

$$10^{A_{min}/10} - 1 = \epsilon^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N}$$

$$\log \left( 10^{A_{min}/10} - 1 \right) = \log \left( \epsilon^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right)$$

$$N = \frac{\log \left[ \left( 10^{A_{min}/10} - 1 \right) / \epsilon^2 \right]}{2 \log \left( \omega_s / \omega_p \right)}$$

$$= 11.3 \Rightarrow \text{choose } \underline{N=12}$$

The actual value of stopband attenuation can be calculated using the integer value of N:

$$A(\omega_s) = 10 \log \left[ 1 + \epsilon^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right]; N=12$$

$$= \underline{\underline{27.35 \text{ dB}}} \text{ actual attenuation}$$

If the stopband specs are to be met exactly we need to find  $A_{max}$ .

Eq. 12.15 can be rearranged to give

$$\epsilon^2 = \frac{10^{A_{min}/10} - 1}{\left( \omega_s / \omega_p \right)^{2N}} \quad \begin{matrix} A_{min} = 20 \\ N = 12 \end{matrix}$$

$$= 0.1824$$

$$\therefore A_{max} = 10 \log (1 + \epsilon^2)$$

$$= \underline{\underline{0.73 \text{ dB}}}$$

12.13

$$N=7, A_{max}=3 \text{ dB}$$

We want attenuation at

$$\omega = 1.6 \omega_p \text{ or } \frac{\omega}{\omega_p} = 1.6$$

$$\epsilon = \sqrt{10^{A_{max}/10} - 1} = 0.998$$

$$A(\omega) = 10 \log \left[ 1 + \epsilon^2 \left( \frac{\omega}{\omega_p} \right)^{2N} \right]$$

$$= 10 \log \left[ 1 + 0.998^2 (1.6)^{14} \right]$$


$$= \underline{\underline{28.56 \text{ dB}}}$$

12.14

$$\omega_p = 10^3 \text{ rad/s}, N=5$$

$$A_{max} = 1 \text{ dB} \Rightarrow \epsilon = 0.5088$$

Find solution graphically

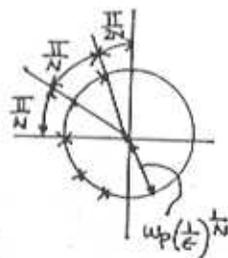

$$P_1 = \omega_p \left( \frac{1}{\epsilon} \right)^{1/N} \angle \left( \frac{\pi}{2} + \frac{\pi}{2N} \right)$$

$$= 873.59 \angle \left( \frac{6\pi}{10} \right)$$

$$= 873.59 \left[ \cos \left( \frac{6\pi}{10} \right) \pm j \sin \left( \frac{6\pi}{10} \right) \right]$$

$$= \underline{\underline{-269.96 \pm j 830.84}}$$

$$P_2 = 873.59 \angle \left[ \frac{\pi}{2} + \frac{\pi}{2N} + \frac{\pi}{N} \right]$$

$$= \underline{\underline{-706.75 \pm j 513.49}}$$

$$P_3 = 873.59 \angle \pi = \underline{\underline{-873.59}}$$

12.15

$$f_p = 10 \text{ kHz} \quad \frac{\omega_s}{\omega_p} = 1.5 \quad A_{min} = 15 \text{ dB}$$

$$f_s = 15 \text{ kHz} \quad \omega_p \quad A_{max} = 2 \text{ dB}$$

$$\epsilon^2 = 10^{A_{max}/10} - 1 \Rightarrow \epsilon = 0.76478$$

CONT.

Manipulation Eq. (12.15) we get:


$$N = \frac{\log \left[ \left( 10^{A_{\min}/10} - 1 \right) / \epsilon^2 \right]}{2 \log (\omega_s / \omega_p)} = 4.88$$

∴ Use  $N=5$

Finding natural modes graphically :-

$$\text{radius} = \omega_p \left( \frac{1}{\epsilon} \right)^{1/N} \triangleq \omega_0$$

$$\omega_0 = 6.629 \times 10^4$$

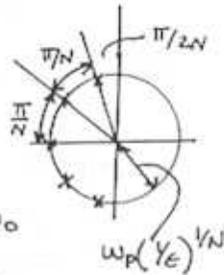

$$P_1 = \omega_0 \angle \left( \frac{\pi}{2} + \frac{\pi}{2N} \right) = \omega_0 \angle \left( \frac{6\pi}{10} \right)$$

$$= \omega_0 \left( \cos \left( \frac{6\pi}{10} \right) \pm j \sin \left( \frac{6\pi}{10} \right) \right)$$

$$= \underline{\underline{\omega_0 (-0.309 \pm j0.951)}}$$

$$P_2 = \omega_0 \left( \cos \frac{8\pi}{10} \pm j \sin \frac{8\pi}{10} \right)$$

$$= \underline{\underline{\omega_0 (-0.809 \pm j0.588)}}$$

$$P_3 = \omega_0 (\cos \pi \pm j \sin \pi) = \underline{\underline{-\omega_0}}$$

Given a natural mode  $-\alpha \pm j\beta$ , the following term results

$$\begin{aligned} & (s + \alpha + j\beta)(s + \alpha - j\beta) \\ &= s^2 + 2\alpha s + \alpha^2 + \beta^2 \\ &= \underline{\underline{s^2 + 2\text{Re}[P]s + |P|^2}} \end{aligned}$$

Also, note that for a Butterworth, all natural modes have a magnitude of  $\omega_0$ .

$$P_1 \text{ yields: } s^2 + 0.618\omega_0 s + \omega_0^2$$

$$P_2 \text{ yields: } s^2 + 1.618\omega_0 s + \omega_0^2$$

$$P_3 \text{ yields: } s + \omega_0$$

$$\begin{aligned} \therefore T(s) &= \frac{k}{(s + \omega_0)(s^2 + 0.618\omega_0 s + \omega_0^2)} \\ &\times \frac{1}{s^2 + 1.618\omega_0 s + \omega_0^2} \end{aligned}$$

For unity dc gain

$$|T(j0)| = \frac{k}{\omega_0^3} = 1 \Rightarrow k = \omega_0^3$$


$$\begin{aligned} \therefore T(s) &= \frac{\omega_0^3}{(s + \omega_0)(s^2 + 0.618\omega_0 s + \omega_0^2)} \times \\ &\frac{1}{(s^2 + 1.618\omega_0 s + \omega_0^2)} \end{aligned}$$

For attenuation at 20 kHz use Eq. (12.15) with  $\frac{\omega_s}{\omega_p} = \frac{20}{10} = 2$

$$A(\omega_s) = 10 \log \left[ 1 + \epsilon^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right]$$

$$= \underline{\underline{27.8 \text{ dB}}}$$

12.16

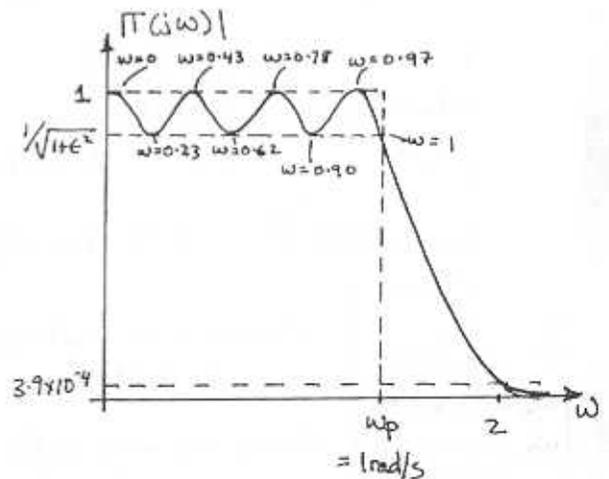

$$\text{Given } A_{\max} = 1 \text{ dB} \Rightarrow \epsilon = 0.5088$$

CONT.

Using Eq 12.18

$$|T(j\omega)| = \left[ 1 + \epsilon^2 \cos^2 \left( N \cos^{-1} \left( \frac{\omega}{\omega_p} \right) \right) \right]^{-1/2}$$

for  $\omega \leq \omega_p$

If  $|T(j\omega)| = 1$

$$1 = 1 + \epsilon^2 \cos^2 \left( N \cos^{-1} \left( \frac{\omega}{\omega_p} \right) \right) \quad \omega_p = 1$$

$$N \cos^{-1} \left( \frac{\omega}{1} \right) = \cos^{-1}(0)$$

$$\cos^{-1}(\omega) = \frac{2i+1}{2N} \pi$$

$\omega$ 's repeat after this value

$$\therefore \omega_i = \cos \left[ \frac{2i+1}{2N} \pi \right] \quad i=0, 1, \dots, \frac{N-1}{2}$$

$\omega_0 = 0.9749$	$\omega$ values at which
$\omega_1 = 0.7818$	$ T =1$
$\omega_2 = 0.4339$	note $\omega_4 = -0.4339$
$\omega_3 = 0$	$= -\omega_2!$

If  $|T| = \sqrt{1+\epsilon^2}$ , then

$$\sqrt{1+\epsilon^2} = \left[ 1 + \epsilon^2 \cos^2 \left( N \cos^{-1} \left( \frac{\omega}{\omega_p} \right) \right) \right]^{-1/2}$$

$$1 = \cos \left( N \cos^{-1} \left( \frac{\omega}{\omega_p} \right) \right)$$

$$N \cos^{-1} \left( \frac{\omega}{\omega_p} \right) = \cos^{-1}(0)$$

$$= i\pi \quad i=0, 1, 2, \dots$$

$$\omega_i = \cos \left[ \frac{i\pi}{N} \right] \quad i=0, 1, 2, \dots, \frac{N}{2}$$

$\omega_0 = 1.0$	$\omega$ values at which
$\omega_1 = 0.9010$	$ T  = (1+\epsilon^2)^{-1/2}$
$\omega_2 = 0.6235$	Note $\omega_4 = -0.2252$
$\omega_3 = 0.2252$	$= -\omega_3!$

To find  $|T(j2)|$  use Eq (12.19)  
since  $\omega > \omega_p$

$$|T(j\omega)| = \left[ 1 + \epsilon^2 \cosh^2 \left( N \cosh^{-1} \left( \frac{\omega}{\omega_p} \right) \right) \right]^{-1/2}$$

$$= \left[ 1 + 0.5088^2 \cosh^2 \left( 7 \cosh^{-1} 2 \right) \right]^{-1/2}$$

$$= \underline{\underline{3.898 \times 10^{-4} \text{ V/V}}}$$

$$|T|_{dB} = \underline{\underline{-68.2 \text{ dB}}}$$

For roll-off consider

$$T(s) = \frac{k}{s^2 + b_1 s^4 + \dots + b_n}$$

for  $\omega \gg \omega_p \quad |T(j\omega)| \approx \frac{k}{\omega^2}$

$\therefore$  Roll-off is  $\frac{1}{2}$  or  $20 \log(1/2^2)$   
per octave =  $\underline{\underline{-42 \text{ dB/octave}}}$ .

12.17


$$\omega_s/\omega_p = 2 \quad A_{max} = 1 \text{ dB} \Rightarrow \epsilon = \sqrt{10^{\frac{A_{max}}{10}} - 1} = 0.5088$$

$$|T_B| = \left[ 1 + \epsilon^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right]^{-1/2}$$

$$|T_C| = \left[ 1 + \epsilon^2 \cosh^2 \left( N \cosh^{-1} \left[ \frac{\omega_s}{\omega_p} \right] \right) \right]^{-1/2}$$

$$|T_B| = 6.13 \times 10^{-2} \Rightarrow \underline{\underline{-24.3 \text{ dB}}}$$

$$|T_C| = 5.43 \times 10^{-3} \Rightarrow \underline{\underline{-45.3 \text{ dB}}}$$

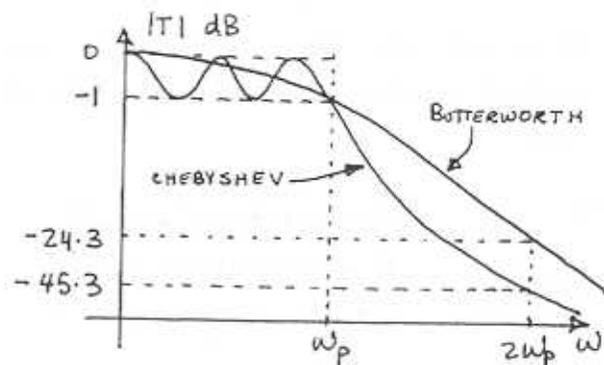

12.18

$$f_p = 3.4 \text{ kHz} \quad A_{\max} = 1 \text{ dB} \Rightarrow \epsilon = 0.5088$$

$$f_s = 4 \text{ kHz} \quad A_{\min} = 35 \text{ dB}$$

$$\omega_s/\omega_p = 1.176$$

Using Eq (12.22) :

$$A(\omega_s) = 10 \log \left[ 1 + \epsilon^2 \cosh^2 \left( N \cosh^{-1} \left( \frac{\omega_s}{\omega_p} \right) \right) \right]$$

∴ trying different values for N

N	A(ω <sub>s</sub> )	} ∴ Use <u>N=10</u>
8	28.8 dB	
9	33.9 dB	
10	38.98 dB	

$$\text{Excess attenuation} = 39 - 35 = \underline{4 \text{ dB}}$$

Poles are given by:

$$P_k = -\omega_p \sin \left( \frac{2k-1}{N} \cdot \frac{\pi}{2} \right) \sinh \left( \frac{1}{N} \sinh^{-1} \left( \frac{1}{\epsilon} \right) \right) + j \omega_p \cos \left( \frac{2k-1}{N} \cdot \frac{\pi}{2} \right) \cosh \left( \frac{1}{N} \sinh^{-1} \left( \frac{1}{\epsilon} \right) \right)$$

for k = 1, 2, ..., N.

$$\text{Since } \epsilon = 0.5088 \text{ and } N = 10$$

$$\sinh \left( \frac{1}{N} \sinh^{-1} \left( \frac{1}{\epsilon} \right) \right) = 0.1433$$

$$\cosh \left( \frac{1}{N} \sinh^{-1} \left( \frac{1}{\epsilon} \right) \right) = 1.010$$

$$\therefore P_1 = \omega_p \left[ -0.1433 \sin \left( \frac{\pi}{20} \right) + j 1.010 \cos \left( \frac{\pi}{20} \right) \right]$$

$$= \omega_p (-0.0224 + j 0.9978)$$

$$P_2 = \omega_p (-0.0650 + j 0.900)$$

$$P_3 = \omega_p (-0.1013 + j 0.7143)$$

$$P_4 = \omega_p (-0.1277 + j 0.4586)$$

$$P_5 = \omega_p (-0.1415 + j 0.1580)$$

Now it should be realized that the remaining poles are complex conjugates of the above.

Pole-pair  $P_1$  &  $P_1^*$  give a factor:

$$s^2 + 2(0.0224)\omega_p s + \omega_p^2(0.0224^2 + 0.9978^2)$$

$$= \underline{s^2 + 0.0448\omega_p s + 1.023\omega_p^2}$$

i.e. this factor is from  $(s - P_1)(s - P_1^*)$

$$P_2 \text{ yields: } \underline{s^2 + 0.130\omega_p s + 0.902\omega_p^2}$$

$$P_3 \text{ yields: } \underline{s^2 + 0.203\omega_p s + 0.721\omega_p^2}$$

$$P_4 \text{ yields: } \underline{s^2 + 0.265\omega_p s + 0.476\omega_p^2}$$

$$P_5 \text{ yields: } \underline{s^2 + 0.283\omega_p s + 0.212\omega_p^2}$$

Now  $T(s)$  is given by

$$T(s) = \frac{k \omega_p^{10}}{\epsilon 2^9 (s - P_1)(s - P_1^*) \dots (s - P_5)(s - P_5^*)}$$


where the second order terms of the denominator are given above.

k is the dc gain

∴ we want the dc gain to be


$$k = \frac{1}{1 + \epsilon^2} = \underline{0.8913}$$
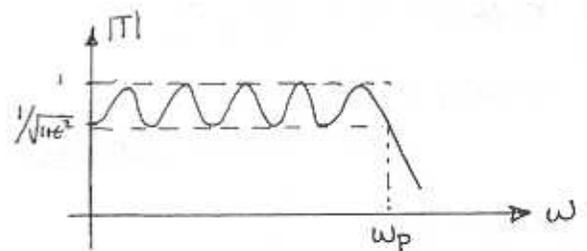
$$\omega_p = \underline{2\pi \times 3400}$$



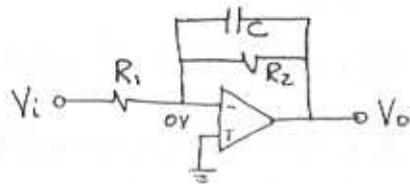12.19

$$f_0 = 10 \text{ kHz} \quad \text{DC gain} = 10 \quad R_{in} = 10 \text{ k}\Omega$$



$$R_{in} = R_1 = \underline{10 \text{ k}\Omega}$$

$$\text{DC gain} = -R_2/R_1 = -10$$

$$R_2 = 10R_1 = \underline{100 \text{ k}\Omega}$$


$$R_2 C = 1/\omega_0$$

$$C = \frac{1}{\omega_0 R_2} = \frac{1}{2\pi \cdot 10^4 \times 100 \times 10^3}$$

$$= \underline{0.159 \text{ nF}}$$

12.20

$$f_0 = 100 \text{ kHz} \quad R_i(\infty) = 100 \text{ k}\Omega \quad |T(\infty)| = 1$$

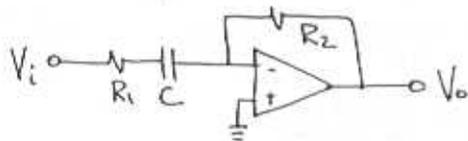

$$R_i(\infty) = R_1 = \underline{100 \text{ k}\Omega}$$

$$|T(\infty)| = R_2/R_1 = 1$$

$$R_2 = R_1 = \underline{100 \text{ k}\Omega}$$


$$C R_1 = 1/\omega_0$$

$$C = \frac{1}{\omega_0 R_1} = \frac{1}{2\pi \cdot 100 \times 10^3 \times 100 \times 10^3}$$

$$= \underline{15.9 \text{ nF}}$$

12.21

Use general first-order circuit:

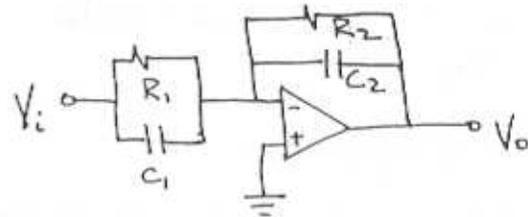

-Zero at 1 kHz; Pole at 100 kHz  
 $-|T(0)| = 1$ ;  $R_i(0) = 1 \text{ k}\Omega$

$$\text{Thus: } R_i(\text{DC}) = R_1 = \underline{1 \text{ k}\Omega}$$

$$T(\text{DC}) = -R_2/R_1 = -1$$

$$R_2 = R_1 = \underline{1 \text{ k}\Omega}$$

For a pole at 100 kHz

$$C_2 R_2 = \frac{1}{\omega_0} \Rightarrow C_2 = \frac{1}{2\pi f_0 R_2}$$

$$= \underline{1.59 \text{ nF}}$$

For the circuit  $T(s) = \frac{a_1 s + a_0}{s + \omega_0}$ Thus the zero at  $-a_0/a_1 = -2\pi \cdot 10^3$ 


$$C_1 R_1 = a_0/a_1$$

$$C_1 = \frac{1}{2\pi \cdot 10^3 R_1}$$


$$= \underline{159 \text{ nF}}$$

$$\text{High freq gain} = -\frac{C_1}{C_2} = \underline{-100}$$

$$= \underline{40 \text{ dB}}$$

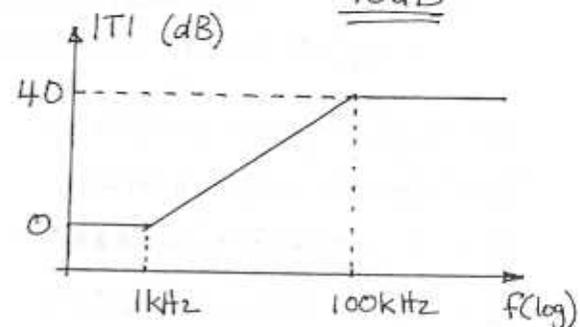

12.22

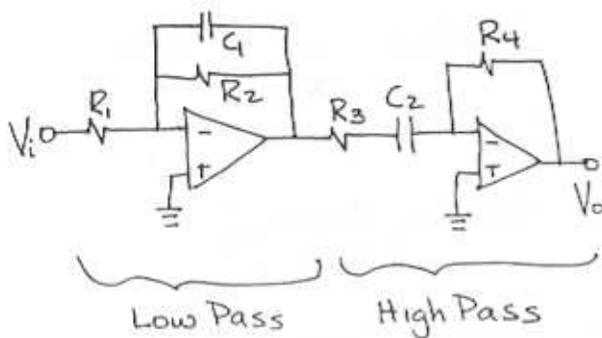

gain =  $10^{12/20} = 3.98 \approx 4$   
 want  $R_i = R_1$  large  
 $\therefore R_1 = \underline{100k\Omega}$

Total gain =  $A_{LP} A_{HP} = 4$

$A_{LP} = -R_2/R_1 \Rightarrow R_2 = -A_{LP} R_1$  and  
 $R_2 \leq 100k\Omega$

$\therefore$  make  $A_{LP} = -1$   $A_{HP} = -4$   
 $R_2 = \underline{100k\Omega}$

$R_2 C_1 = \frac{1}{\omega_{9LP}}$


$C_1 = \frac{1}{2\pi f_{0,LP} R_2} = \frac{1}{2\pi (10 \times 10^3) 100 \times 10^3}$   
 $= \underline{0.159 nF}$

$A_{HP} = -R_4/R_3 = -4$  } make  $R_4 = \underline{100k\Omega}$   
 $R_4 = 4R_3$  }  $R_3 = \underline{25k\Omega}$

now  $R_3 C_2 = 1/\omega_{0,HP}$

$C_2 = \frac{1}{2\pi f_{0,HP} R_3}$   
 $= \frac{1}{2\pi (100 \times 10^3) 25 \times 10^3}$   
 $= \underline{63.7 nF}$

12.23

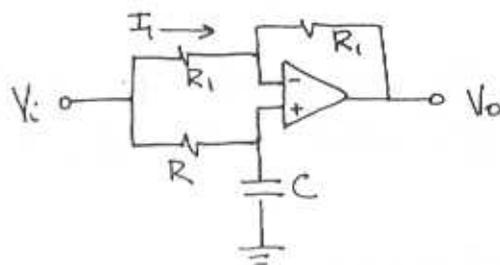

At +ve terminal

$V_+ = \frac{V_{sc}}{1/s\tau + R_1} V_i$   
 $= \frac{1}{1+s\tau} V_i$   $\tau = RC$

$V_- = V_+$  due to virtual short between terminals.

$\therefore I_1 = (V_i - \frac{1}{1+s\tau} V_i) \frac{1}{R_1}$

$V_o = V_- - I_1 R_1$   
 $= \frac{V_i}{1+s\tau} - (V_i - \frac{V_i}{1+s\tau}) \frac{R_1}{R_1}$

$\frac{V_o}{V_i} = \frac{1 - (1+s\tau) + 1}{1+s\tau} = \frac{1-s\tau}{1+s\tau}$   
 $= \frac{\omega_0 - s}{\omega_0 + s}$   $\omega_0 = \frac{1}{\tau}$

$= \underline{\underline{\frac{s - \omega_0}{s + \omega_0} = T(s)}}$

$T(s) = -\frac{j\omega - \omega_0}{j\omega + \omega_0}$

$\phi(\omega) = 180^\circ + \tan^{-1}\left(\frac{\omega}{-\omega_0}\right) - \tan^{-1}\left(\frac{\omega}{\omega_0}\right)$   
 $= 360^\circ - 2 \tan^{-1}\left(\frac{\omega}{\omega_0}\right)$   $\begin{matrix} 0^\circ \tan^{-1}\left(\frac{\omega}{-\omega_0}\right) \\ = 180^\circ - \tan^{-1}\left(\frac{\omega}{\omega_0}\right) \end{matrix}$   
 $= -2 \tan^{-1}(\omega/\omega_0)$

Now this equation can be rearranged:

$\frac{\omega}{\omega_0} = \tan(-\phi/2) \Leftrightarrow \omega_0 = \frac{1}{2} = \frac{1}{RC}$

$RC\omega = \tan(-\phi/2)$


CONT.

$$\therefore R = \frac{\tan(-\phi/2)}{c\omega} = 10^4 \tan(\phi/2)$$

$$\phi = -30^\circ, -60^\circ, -90^\circ, -120^\circ, -150^\circ$$

$$R = 2.68k\Omega, 5.77k\Omega, 10k\Omega, 17.32k\Omega, 37.32k\Omega$$

12.24

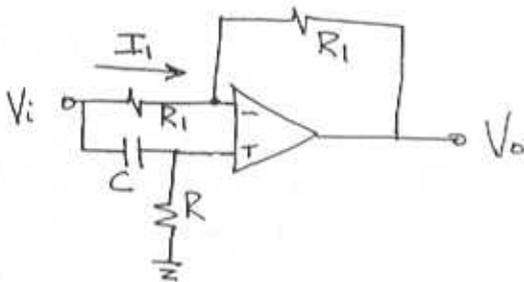

$$V_+ = \frac{R}{R + 1/sC} V_i = \frac{s}{s + \omega_0} V_i$$

where  $\omega_0 = \frac{1}{RC}$

$$I_1 = \frac{V_i - (s/s + \omega_0)V_i}{R_i}$$

$$V_o = \frac{s}{s + \omega_0} V_i - I_1 R_i$$

$$= \frac{s}{s + \omega_0} V_i - V_i \left(1 - \frac{s}{s + \omega_0}\right)$$

$$\frac{V_o}{V_i} = \frac{2s - s - \omega_0}{s + \omega_0} = \frac{s - \omega_0}{s + \omega_0}$$

Now:

$$\phi(\omega) = \tan^{-1}\left(\frac{\omega}{-\omega_0}\right) - \tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

$$= 180 - \tan^{-1}\left(\frac{\omega}{\omega_0}\right) - \tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

$$= 180 - 2 \tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

Clearly  $\phi(0) = 180^\circ$  &  $\phi(\omega \rightarrow \infty) = 0^\circ$

12.25

Low Pass  $\omega_0 = 10^3$  rad/s

$$Q = 1$$

$$\text{DC gain} = 1$$

$$T(s) = \frac{a_0}{s^2 + s\frac{\omega_0}{Q} + \omega_0^2}$$

$$T(0) = a_0/\omega_0^2 = 1$$

$$a_0 = \omega_0^2 = 10^6$$

$$\therefore T(s) = \frac{10^6}{s^2 + 10^3 s + 10^6}$$

$$\omega_{\max} = \omega_0 \sqrt{1 - 1/2Q^2}$$

$$= \frac{\omega_0}{\sqrt{2}}$$

$$= 0.707 \text{ rad/s}$$

$$|T_{\max}| = \frac{|a_0| Q}{\omega_0^2 \sqrt{1 - 1/4Q^2}} \leftarrow a_0 = \omega_0^2$$

$$= \frac{10^6 |1|}{10^6 \sqrt{3/4}}$$

$$= 2/\sqrt{3}$$

$$= 1.15 \text{ V/V}$$

$$= 1.21 \text{ dB}$$


12.26

$$\omega_p = 1 \text{ rad/s}$$

$$A_{\max} = 3 \text{ dB}$$

There are many Q-values which may be used

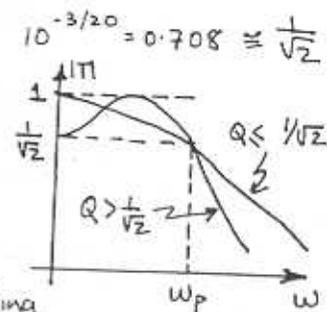$Q \leq 1/\sqrt{2}$  - no peaking  
 $Q > 1/\sqrt{2}$  - peaking



CONT.

Solution 1  $Q \leq \frac{1}{\sqrt{2}}$

For  $Q = \frac{1}{\sqrt{2}}$  the response is maximally flat. Because this is desirable, use:  $Q = \frac{1}{\sqrt{2}}$

$$T(s) = \frac{a_0}{s^2 + s\omega_0/\sqrt{2} + \omega_0^2}$$

$$|T(0)| = \frac{a_0}{\omega_0^2} = 1$$

$$\underline{a_0 = \omega_0^2}$$

$$|T(j\omega)|^2 = \frac{\omega_0^4}{(\omega_0^2 - \omega^2)^2 + 2\omega_0^2\omega^2} = \left(\frac{1}{\sqrt{2}}\right)^2$$

$$\omega_0 = 1 \text{ rad/s}$$

$$\therefore \underline{T_1(s) = \frac{1}{s^2 + \sqrt{2}s + 1}}$$

Solution 2  $Q > \frac{1}{\sqrt{2}}$

From the figure:  $|T(0)| = \frac{1}{\sqrt{2}} = \frac{a_0}{\omega_0^2}$

$$\therefore \underline{a_0 = \omega_0^2/\sqrt{2}}$$

$$\text{Now } |T|_{\max} = \frac{|a_0|Q}{\omega_0^2\sqrt{1 - 1/4Q^2}} = 1$$

$$\frac{Q}{\sqrt{2}\sqrt{1 - 1/4Q^2}} = 1$$

$$Q = \sqrt{2}\sqrt{1 - 1/4Q^2}$$

$$\therefore Q^2 = 2\left(1 - \frac{1}{4Q^2}\right)$$

$$= 2 - \frac{1}{2Q^2}$$

$$Q^4 - 2Q^2 + \frac{1}{2} = 0$$

Solving for  $Q^2$  gives:-

$$Q^2 = 1 \pm \frac{1}{\sqrt{2}}$$

ASIDE:

$$\therefore Q > \frac{1}{\sqrt{2}}$$

$$Q^2 > \frac{1}{2}$$

$$4Q^2 > 2$$

$$\frac{1}{4Q^2} < \frac{1}{2}$$

$$\therefore 1 - \frac{1}{4Q^2} > \frac{1}{2}$$

$$\therefore \left|1 - \frac{1}{4Q^2}\right| = 1 - \frac{1}{4Q^2}$$

$$\Rightarrow Q = 0.5412 \text{ or } 1.3066$$

$$\therefore Q > \frac{1}{\sqrt{2}} \text{ use } \underline{Q = 1.3066}$$

Now at the passband edge

$$|T(j1)| = \frac{1}{\sqrt{2}}$$

$$|T(j1)|^2 = \frac{(\omega_0^2/\sqrt{2})^2}{(\omega_0^2 - 1)^2 + \frac{\omega_0^2}{Q^2}} = \frac{1}{2}$$

$$\frac{\omega_0^4}{2} = \frac{1}{2} \left[ \omega_0^4 - 2\omega_0^2 + 1 + \frac{\omega_0^2}{Q^2} \right]$$

$$\omega_0^2(2 - 1/Q^2) = 1$$

$$\underline{\omega_0 = 0.841}$$

$$\therefore T_2(s) = \frac{\omega_0^2/\sqrt{2}}{s^2 + \omega_0/Qs + \omega_0^2}$$

$$= \frac{0.5}{s^2 + 0.644s + 0.707}$$

If  $\omega_s = 2$


$$|T_1(j2)| = 0.242 \quad |T_2(j2)| = 0.1414$$

$$\therefore \underline{A_{\min,1} = -12.3\text{dB}} \quad \underline{A_{\min,2} = -17\text{dB}}$$

12.27

$V_2$  lags  $V_1$  by  $120^\circ$

$V_3$  lags  $V_2$  by  $120^\circ$

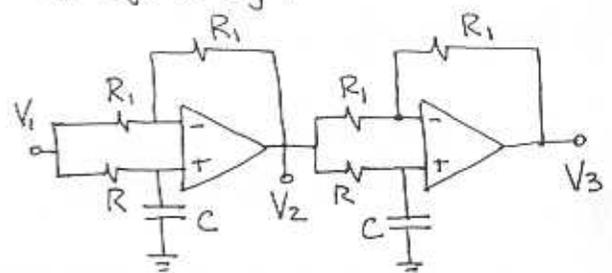

$$\omega = 2\pi 60 \text{ rad/s} \quad \& \quad C = 1 \mu\text{F}$$

$$T(s) = \frac{s - \omega_0}{s + \omega_0} \quad \omega_0 = \frac{1}{RC}$$

CONT.

$$\phi(\omega) = 180^\circ + \tan^{-1}\left(\frac{\omega}{-\omega_0}\right) - \tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

$$\text{Sub: } \tan\left(\frac{\omega}{-\omega_0}\right) = 180 - \tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

$$\Rightarrow \phi(\omega) = -2 \tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

Now  $\phi = -120^\circ$  at  $\omega = 2\pi 60$

$$-120 = -2 \tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$


$$-60 = -\tan^{-1}\left(2\pi 60 \times R \times 10^{-6}\right)$$

$$\underline{R = 4.59 \text{ k}\Omega}$$

$R_1$  can be arbitrarily chosen

$$\text{use } \underline{R_1 = 10 \text{ k}\Omega}$$

12.28

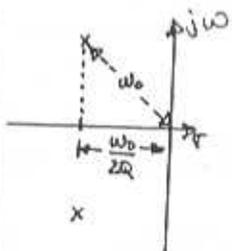

Natural Modes:

$$-\frac{1}{2} \pm j\frac{\sqrt{3}}{2}$$

$$\omega_0 = \sqrt{\left(\frac{1}{2}\right)^2 + \left(\frac{\sqrt{3}}{2}\right)^2}$$

$$= \underline{1.0}$$

$$\frac{\omega_0}{2Q} = \frac{1}{2} \Rightarrow \frac{\omega_0}{Q} = 1$$

$$T(s) = \frac{a_2 s^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2} = \frac{a_2 s^2}{s^2 + s + 1}$$

$$|T(j\infty)| = a_2 = 1$$

$$\therefore \underline{T(s) = \frac{s^2}{s^2 + s + 1}}$$

12.29

For a 2nd-order bandpass

$$T(s) = \frac{a_1 s}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$$T(j\omega) = \frac{j\omega a_1}{(\omega_0^2 - \omega^2) + j\frac{\omega\omega_0}{Q}}$$

$$|T(j\omega)| = \frac{a_1 \omega}{\left[ (\omega_0^2 - \omega^2)^2 + \frac{\omega^2 \omega_0^2}{Q^2} \right]^{1/2}}$$

Part (a):

$$|T(j\omega_1)| = |T(j\omega_2)|$$

$$\frac{a_1 \omega_1}{\sqrt{(\omega_0^2 - \omega_1^2)^2 + \left(\frac{\omega_1 \omega_0}{Q}\right)^2}} = \frac{a_1 \omega_2}{\sqrt{(\omega_0^2 - \omega_2^2)^2 + \left(\frac{\omega_2 \omega_0}{Q}\right)^2}}$$

$$\omega_1^2 \left[ (\omega_0^2 - \omega_2^2)^2 + \left(\frac{\omega_2 \omega_0}{Q}\right)^2 \right] = \omega_2^2 \left[ (\omega_0^2 - \omega_1^2)^2 + \left(\frac{\omega_1 \omega_0}{Q}\right)^2 \right]$$

$$\omega_1^2 (\omega_0^4 - 2\omega_0^2 \omega_2^2 + \omega_2^4) =$$

$$\omega_2^2 (\omega_0^4 - 2\omega_0^2 \omega_1^2 + \omega_1^4)$$

$$\omega_1^2 \omega_0^4 + \omega_1^2 \omega_2^4 = \omega_2^2 \omega_0^4 + \omega_2^2 \omega_1^4$$

$$\omega_0^4 (\omega_1^2 - \omega_2^2) = \omega_2^2 \omega_1^4 - \omega_1^2 \omega_2^4$$

$$\omega_0^4 (\omega_1^2 - \omega_2^2) = \omega_2^2 \omega_1^2 (\omega_1^2 - \omega_2^2)$$

$$\omega_0^4 = \omega_1^2 \omega_2^2$$

$$\underline{\underline{\omega_0^2 = \omega_1 \omega_2 \text{ Q.E.D.}}}$$

CONT.

For Fig. 12.4:  $\omega_{p1} = 8100 \text{ rad/s}$   
 $\omega_{p2} = 10000 \text{ rad/s}$   
 $A_{\max} = 1 \text{ dB}$

$$\omega_0^2 = (8100)(10000)$$

$$\omega_0 = \underline{9000 \text{ rad/s}}$$

$$|T(j\omega_{p1})| = |T(j\omega_{p2})| = 10^{-1/20} = \underline{0.8913}$$

$$|T(j\omega_0)| = \frac{\omega_0 a_1}{\sqrt{(\omega_0^2 - \omega_0^2)^2 + \left(\frac{\omega_0^2}{Q}\right)^2}} = 1$$

$$\Rightarrow \frac{\omega_0 a_1}{\omega_0^2 / Q} = 1$$

$$\therefore \frac{Q a_1}{\omega_0} = 1 \Rightarrow a_1 = \frac{\omega_0}{Q}$$

$$|T(j\omega_{p1})|^2 = |T(j0.9\omega_0)|^2 = 0.8913^2$$

$$\frac{(\omega_0/Q)^2 (0.9\omega_0)^2}{(\omega_0^2 - (0.9\omega_0)^2)^2 + \left(\frac{0.9\omega_0}{Q}\right)^2} = 0.8913^2$$

$$\left(\frac{\omega_0}{Q} (0.9\omega_0)\right)^2 = 0.8913^2 \left[ (\omega_0^2 - (0.9\omega_0)^2)^2 + \left(\frac{0.9\omega_0}{Q}\right)^2 \right]$$

$$\frac{0.81\omega_0^4}{Q^2} = 0.8913^2 \left[ \omega_0^4 (1-0.81)^2 + \frac{0.81\omega_0^4}{Q^2} \right]$$

$$\frac{0.81\omega_0^4}{Q^2} (1-0.8913^2) = 0.8913^2 \omega_0^4 \times (1-0.81)^2$$

sub  $\omega_0 = 9000$  gives

$$\underline{Q = 2.41}$$

$$\text{Now } a_1 = \frac{\omega_0}{Q} = 0.415 \omega_0$$

$$\therefore T(s) = \frac{0.415 \omega_0 s}{s^2 + 0.415 \omega_0 s + \omega_0^2}$$

If  $\omega_{s1} = 3000 \text{ rad/s}$

$$|T(j3000)| = \frac{0.415 \omega_0 (3000)}{\sqrt{(\omega_0^2 - 3000^2)^2 + (\omega_0 \cdot 3000 \cdot 0.415)^2}}$$

$$= 0.1537$$

$$\therefore A_{\min} = -20 \log(0.1537)$$

$$= \underline{16.3 \text{ dB}}$$

Now  $\omega_{s1}$  and  $\omega_{s2}$  are geometrically symmetrical about  $\omega_0$ :

$$\omega_{s1} \omega_{s2} = \omega_0^2$$

$$\omega_{s2} = \frac{9000^2}{3000}$$

$$= \underline{27000 \text{ rad/s}}$$

### 12.30

From exercise 12.15

$$Q = \frac{\omega_0}{\text{BW} \sqrt{10^{A/10} - 1}} \quad \begin{cases} \omega_0 = 2\pi(60) \\ \text{BW} = 2\pi(6) \\ A = 20 \text{ dB} \end{cases}$$

$$= \underline{1.005}$$

$$T(s) = a_2 \frac{s^2 + \omega_0^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$$|T(0)| = \frac{a_2 \omega_0^2}{\omega_0^2} = 1 \leftarrow \text{DC Gain}$$

CONT.

$$\underline{a_2 = 1}$$

$$T(s) = \frac{s^2 + (2\pi 60)^2}{s^2 + s \frac{2\pi 60}{1.005} + (2\pi 60)^2}$$

$$\underline{\underline{T(s) = \frac{s + 1.421 \times 10^5}{s^2 + 375.15s + 1.421 \times 10^5}}}$$

12.32

$$T(s) = \frac{s^2 - s \omega_0/Q' + \omega_0^2}{s^2 + s \omega_0/Q_0 + \omega_0^2} a_2$$


$$\text{Zero } Q < \text{ Pole } Q \Rightarrow Q' < Q_0$$

At  $\omega = \omega_0$ :

$$|T| = \frac{a_2 \omega_0^2/Q'}{\omega_0^2/Q_0} = \frac{a_2 Q_0}{Q'} > a_2$$

If  $Q' > Q_0$

$$|T(j\omega_0)| = \frac{a_2 Q_0}{Q'} < a_2$$

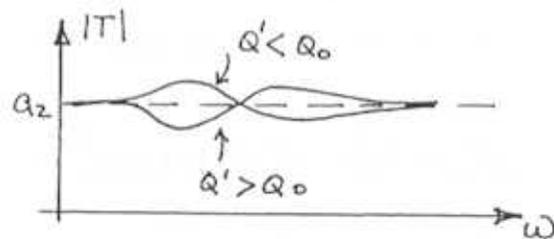

12.31


FOR ALL PASS:

$$T(s) = a_2 \frac{s^2 - s \omega_0/Q + \omega_0^2}{s^2 + s \omega_0/Q + \omega_0^2}$$

If zero frequency < pole frequency


$$T(s) = a_2 \frac{s^2 - s \omega_n/Q + \omega_n^2}{s^2 + s \omega_0/Q + \omega_0^2} \quad \omega_n < \omega_0$$

At DC:  $|T| = a_2 \frac{\omega_n^2}{\omega_0^2}$  where  $\frac{\omega_n^2}{\omega_0^2} < 1$

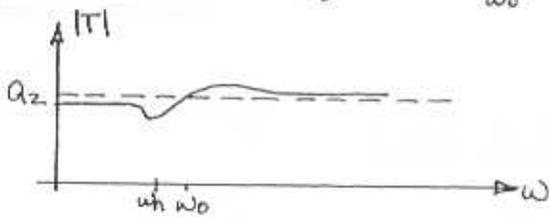

If zero frequency > pole frequency then  $\omega_n > \omega_0$

At DC:  $|T| = a_2 \omega_n^2/\omega_0^2$  where  $\frac{\omega_n^2}{\omega_0^2} > 1$

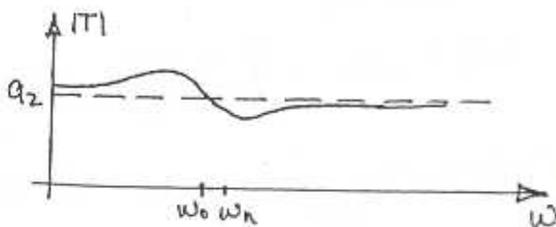

12.33

$$\omega_0 = 10^4 \text{ rad/s}, \quad Q = 2, \quad R = 10 \text{ k}\Omega$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow \omega_0^2 = \frac{1}{LC} \Leftrightarrow L = \frac{R^2 C}{Q^2} = \frac{Q^2}{R^2 C^2}$$

$$C = \frac{Q}{R \omega_0} = \underline{\underline{20 \text{ nF}}}$$

$$L = \frac{1}{C \omega_0^2} = \underline{\underline{500 \text{ mH}}}$$

12.34

$$\omega_0 = \sqrt{LC}$$


$$\begin{aligned} \text{If } L' &= 1.01L \\ \omega_0' &= (1.01LC)^{-1/2} \\ &= 0.9950 \frac{1}{\sqrt{LC}} \\ &= 0.9950 \omega_0 \end{aligned}$$

$$\therefore \underline{\underline{\Delta\omega_0 = -0.5\%}}$$

$$\begin{aligned} \text{If } C' &= 1.01C \\ \omega_0' &= 0.9950 \omega_0 \\ \Delta\omega_0' &= -0.5\% \end{aligned}$$

Changing R has no effect on  $\omega_0$

12.35

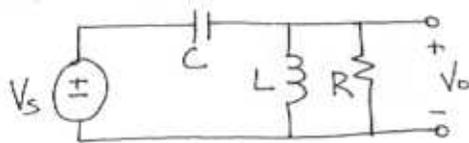

Use voltage divider rule:

$$V_o = \frac{Z_{RL}}{Z_{RL} + Z_C} V_s$$

$$\frac{V_o}{V_s} = \frac{\left(\frac{1}{R} + \frac{1}{sL}\right)^{-1}}{\left(\frac{1}{R} + \frac{1}{sL}\right)^{-1} + \frac{1}{sC}}$$

$$= \frac{sC}{\left(\frac{1}{sC} + \frac{1}{R}\right) + sC}$$

$$\therefore \underline{\underline{T(s) = \frac{V_o(s)}{V_s(s)} = \frac{s^2}{s^2 + s/RC + 1/L^2}}}$$

12.36

$$\text{Low Pass: } \omega_0 = 10^5, C = 0.1 \mu\text{F} \\ Q = 1/\sqrt{2}$$

$$Q = \omega_0 CR$$

$$R = \frac{Q}{\omega_0 C}$$

$$= \frac{1}{\sqrt{2} \times 10^5 \times 0.1 \times 10^{-6}}$$


$$= \underline{\underline{70.7 \Omega}}$$

$$\omega_0 = \sqrt{LC}$$

$$L = \frac{1}{\omega_0^2 C}$$

$$= \underline{\underline{1 \text{ mH}}}$$

12.37

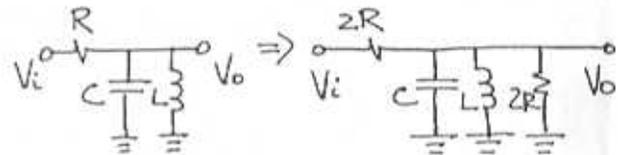


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q = \omega_0 CR \\ A_{mid} = 1$$

$$\omega_0 = \sqrt{LC}$$

$$\begin{aligned} Q &= \omega_0 C (2R \parallel 2R) \\ &= \omega_0 CR \\ A_{mid} &= \frac{2R}{2R + 2R} = 1/2 \end{aligned}$$

12.38

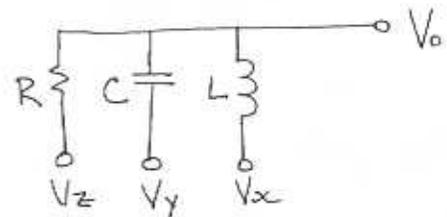

$$\left. \frac{V_o}{V_z} \right|_{V_y = V_x = 0} = T_{BP}(s)$$

$$\left. \frac{V_o}{V_y} \right|_{V_x = V_z = 0} = T_{HP}(s)$$

CONT.


$$\left. \frac{V_o}{V_x} \right|_{V_y=V_z=0} = T_{LP}(s)$$

Using superposition

$$\begin{aligned} V_o &= \frac{V_o}{V_x} V_x + \frac{V_o}{V_y} V_y + \frac{V_o}{V_z} V_z \\ &= T_{LP} V_x + T_{HP} V_y + T_{BP} V_z \\ &= \frac{\frac{1}{LC} V_x + s^2 V_y + \frac{s}{RC} V_z}{s^2 + s/RC + 1/LC} \end{aligned}$$

$$\begin{aligned} \therefore V_o &= V_x \frac{1/LC}{s^2 + s/RC + 1/LC} + \\ &V_y \frac{s^2}{s^2 + s/RC + 1/LC} + \\ &V_z \frac{s/RC}{s^2 + s/RC + 1/LC} \end{aligned}$$

12.39

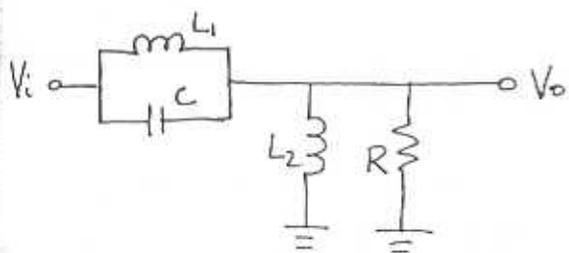

From Eq 12.46

$$T(s) = \frac{s^2 + 1/LC}{s^2 + s(1/RC) + \frac{1}{(L_1 \parallel L_2)C}}$$

Required notch  $\omega_n^2 = \frac{1}{L_1 C} = (0.9\omega_0)^2$

but:

$$\omega_0^2 = \frac{1}{(L_1 \parallel L_2)C} \quad \text{where } L_1 \parallel L_2 = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2}}$$

$$= \frac{L_1 + L_2}{L_1 L_2 C} = \frac{L_1 L_2}{L_1 + L_2}$$

$$= \frac{L_1 + L_2}{L_2} (0.9\omega_0)^2$$

$$1 = \left( \frac{L_1}{L_2} + 1 \right) 0.9^2$$

$$\therefore L_1/L_2 = \frac{1}{0.9^2} - 1 = \underline{\underline{0.2346}}$$

For  $\omega \ll \omega_0$ :-

$$|T| \cong \frac{1/L_1 C}{1/(L_1 \parallel L_2)C} = \frac{L_2}{L_1 + L_2}$$

i.e. inductors dominate!

For  $\omega \gg \omega_0$   $L_1$  &  $L_2$  are "open"  
C is shorted

$$\underline{\underline{|T| \cong 1}}$$

12.40

$$L = C_4 R_1 R_3 R_5 / R_2$$

Choose  $\underline{\underline{R_1 = R_2 = R_3 = R_5 = 10k\Omega}}$

$$\therefore L = C_4 \times 10^8$$


For:

$$L = 10H = C_4 \times 10^8 \Rightarrow \underline{\underline{C_4 = 100nF}}$$

$$L = 1H \Rightarrow \underline{\underline{C_4 = 10nF}}$$

$$L = 0.1H \Rightarrow \underline{\underline{C_4 = 1nF}}$$

12.41

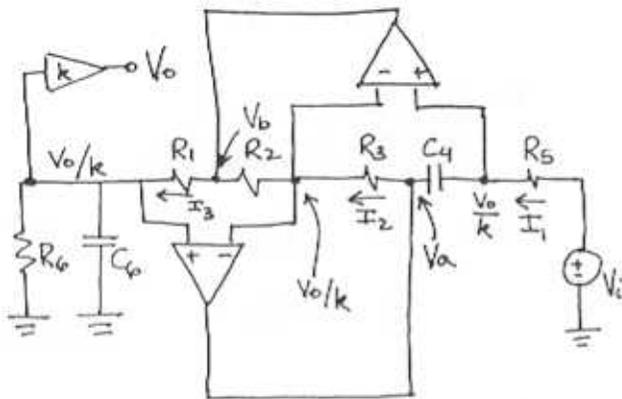

Because of the virtual short at opamp input terminals, the voltages are:  $V_o/k$

$$I_1 = \frac{V_i - V_o/k}{R_5}$$

$$\begin{aligned} V_a &= V_o/k - I_1 / sC_4 \\ &= V_o/k - \frac{V_i - V_o/k}{sC_4 R_5} \\ &= \frac{V_o (sC_4 R_5 + 1) - kV_i}{sC_4 R_5 k} \end{aligned}$$

$$\begin{aligned} I_2 &= \frac{V_a - V_o/k}{R_3} \\ &= \frac{V_i}{sC_4 R_3 R_5} + \frac{V_o/k}{sC_4 R_3 R_5} \end{aligned}$$

$$\begin{aligned} V_b &= \frac{V_o}{k} - I_2 R_2 \\ &= \frac{V_o}{k} - \frac{V_o/k - V_i}{sC_4 R_3 R_5 / R_2} \end{aligned}$$

$$I_3 = \frac{V_b - V_o/k}{R_1} = \frac{V_i - V_o/k}{sC_4 R_1 R_3 R_5 / R_2}$$

Now,  $I_3$  flows only into  $R_6$  &  $C_6$  since for ideal opamps,  $R_{in} = \infty$ !

$$\therefore \frac{V_o}{k} = I_3 \left( R_6 \parallel \frac{1}{sC_6} \right)$$

$$\text{Let } L \triangleq \frac{R_1 R_3 R_5 C_4}{R_2}$$

$$\text{So: } I_3 = \frac{V_i - V_o/k}{sL}$$

$$V_o/k = I_3 \left( R_6 \parallel \frac{1}{sC_6} \right)$$

$$\begin{aligned} \frac{V_o}{k} &= \frac{V_i - V_o/k}{sL} \cdot \frac{1}{1/R_6 + sC_6} \\ &= \frac{V_i - V_o/k}{sL/R_6 + s^2 LC_6} \end{aligned}$$

$$V_o/k \left( 1 + sL/R_6 + s^2 LC_6 \right) = V_i$$

$$\frac{V_o}{V_i} = \frac{k/LC_6}{s^2 + \frac{s}{R_6 C_6} + \frac{1}{LC_6}}$$

$$\text{Recall } L = R_1 R_3 R_5 C_4 / R_2$$


$$\therefore \frac{V_o}{V_i} = \frac{kR_2}{C_4 R_1 R_3 R_5} \cdot \frac{1}{s^2 + \frac{s}{R_6 C_6} + \frac{R_2}{C_6 C_4 R_1 R_3 R_5}}$$

12.42

$$A_{\max} = 10 \log(1 + \epsilon^2) = 3 \text{ dB}$$

$$\therefore \epsilon = 0.998 \cong 1$$

$$\omega_0 = \omega_p = 10^4$$

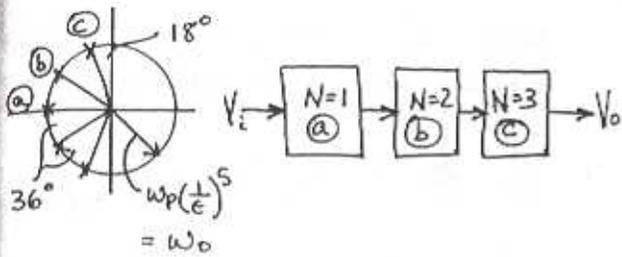

For circuit (a) use fig 12.13(a)

$$\text{DC Gain} = 1 = R_2/R_1 \Rightarrow R_1 = R_2 = 10 \text{ k}\Omega$$


$$CR_2 = 1/\omega_0 \Rightarrow C = 1/R_2 \omega_0 = \frac{1}{10^4 \cdot 10^4} = 10 \text{ nF}$$

For circuit (b) use Fig. 12.22(a)

$$\omega_0 = 10^4 \text{ rad/s}$$

$$\frac{\omega_0}{2Q} = \omega_0 \cos 36^\circ$$
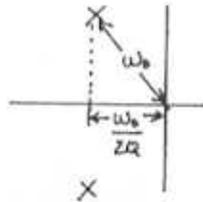
$$Q = \frac{1}{2 \cos 36^\circ} = 0.618$$



From Table 12.1

$$T(s) = \frac{k R_2}{C_4 C_6 R_1 R_3 R_5} \frac{R_2}{s^2 + s/C_6 R_6 + \frac{R_2}{C_4 C_4 R_1 R_3 R_5}}$$

$$\omega_0^2 = \frac{R_2}{C_4 C_6 R_1 R_3 R_5} \quad \text{Let } R_1 = R_3 = R_5 = R_2 = R$$

$$C_4 = C_6 = C$$

$$\omega_0^2 = \frac{1}{R^2 C^2} \quad \text{USE } C_4 = C_6 = 100 \text{ nF}$$

$$\therefore R = \frac{1}{\omega_0 C} \Rightarrow R_1 = R_2 = R_3 = R_5 = 1 \text{ k}\Omega$$

Now using:

$$\frac{\omega_0}{Q} = \frac{1}{C_6 R_6} \quad \& \quad Q = 0.618$$

$$R_6 = \frac{Q}{C_6 \omega_0} = 618 \Omega$$

For circuit (c) use Fig 12.22 (a)

$\omega_0 = 10^4$  which is the same as for circuit (b).

$$\therefore C_4 = C_6 = 100 \text{ nF}$$

$$R_1 = R_2 = R_3 = R_5 = 1 \text{ k}\Omega$$

$$\text{Now: } Q = \frac{1}{2 \cos 72^\circ} = 1.618$$

$$R_6 = Q/\omega_0 C_6 = 1.618 \text{ k}\Omega$$

12.43

$$f_0 = 4 \text{ kHz} \quad f_N = 5 \text{ kHz} \quad Q = 10$$

now  $C_4 = 10 \text{ nF}$  and  $k = 1 \equiv \text{dc gain}$

$$\omega_0 = [C_4 (C_{61} + C_{62}) R_1 R_3 R_5 / R_2]^{-1/2}$$

$$C_{61} + C_{62} = C_6$$

Choose  $C_4 = C_6 = 10 \text{ nF}$  &

$$R_1 = R_3 = R_5 = R_2 = R$$

$$\therefore \omega_0 = (C_4 C_6 R^2)^{-1/2}$$

$$R = \frac{1}{\omega_0 C_4}$$

$$\Rightarrow R_1 = R_3 = R_5 = R_2 = 3.979 \text{ k}\Omega$$

$$\omega_N = (C_4 C_{61} R^2)^{-1/2}$$

$$C_{61} = \frac{1}{\omega_N^2 R^2 C_4} \Rightarrow C_{61} = 6.4 \text{ nF}$$

$$\& \quad C_{62} = 3.6 \text{ nF}$$

$$Q = R_6 \sqrt{\frac{C_{61} + C_{62}}{C_4}} \cdot \frac{R_2}{R_1 R_3 R_5}$$

$$= R_6 \sqrt{\frac{1}{R^2}} = R_6/R_1 \Rightarrow R_6 = 39.79 \text{ k}\Omega$$

12.44

From Fig. 12.16 (g)  $\phi = 180^\circ$  at  $f_0$ !

∴ Use  $f_0 = 1\text{kHz}$   $Q = 1$

$$\omega_0^2 = \frac{R_2}{C_4 C_6 R_1 R_3 R_5} \quad \begin{matrix} \text{Let} \\ C = C_4 = C_6 = 1\text{nF} \\ R_1 = R_3 = R_5 = R_2 = R \end{matrix}$$

$$= \frac{1}{C^2 R^2}$$

$$R = \frac{1}{\omega_0 C} = \underline{159.16\text{ k}\Omega} = R_1 = R_3 = R_5 = R_2$$

$$\frac{\omega_0}{Q} = \frac{1}{R_6 C_6} \Rightarrow R_6 = \frac{Q}{C_6 \omega_0} = \frac{1}{10^{-9} 2\pi 10^3}$$

$$\therefore \underline{R_6 = 159.16\text{ k}\Omega}$$

$$V_a = V_2 - I_1 R_1 = V_2 (1 + s C_6 R_1)$$

$$I_2 = (V_a - V_2) \frac{1}{R_2} = \frac{s C_6 R_1}{R_2} V_2$$

$$V_b = V_2 - I_2 R_3 = V_2 - \frac{s C_6 R_1 R_3}{R_2} V_2$$

$$I_3 = (V_b - V_2) s C_4 = -\frac{s^2 C_4 C_6 R_1 R_3}{R_2} V_2$$

Now the voltage source sees an input impedance given by:

$$Z_{in} = -V_2 / I_3 = \frac{R_2}{s^2 C_4 C_6 R_1 R_3}$$


As required.

$$\text{for } s = j\omega \Rightarrow s^2 = -\omega^2$$

$$Z_{in}(j\omega) = \frac{-R_2}{C_4 C_6 R_1 R_3} \cdot \frac{1}{\omega^2}$$

$$= -R(\omega) \quad \text{i.e. A PURE NEGATIVE RESISTANCE!}$$

12.45

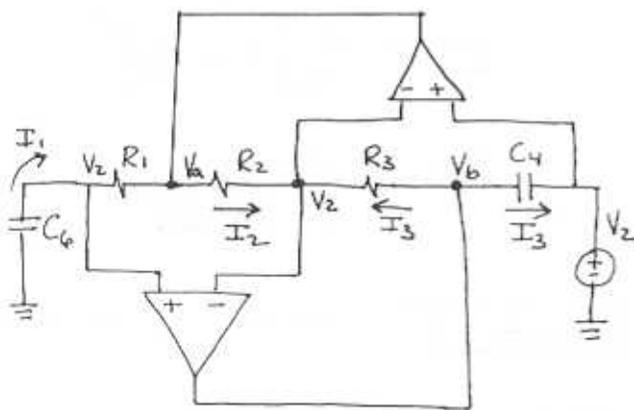

Because of virtual short at opamp input terminals all nodes are at  $V_2$ !

$$I_1 = -s C_6 V_2$$

Since no current goes into the opamp input terminals we have:

12.46

For LPN: See Table 12.1 & Fig. 12.22 (e)

$$T(s) = k \frac{C_{e1}}{C_{e1} + C_{e2}} \cdot \frac{s^2 + \frac{R_2}{C_4 C_6 R_1 R_3 R_5}}{s^2 + s / C_6 R_6 + \frac{R_2}{C_4 (C_{e1} + C_{e2}) R_1 R_3 R_5}}$$

At DC  $\rightarrow s = 0$

$$T(0) = k \frac{C_{e1}}{C_{e1} + C_{e2}} \cdot \frac{R_2 / C_4 C_6 R_1 R_3 R_5}{R_2 / C_4 (C_{e1} + C_{e2}) R_1 R_3 R_5}$$

CONT.

$$\Rightarrow T(0) = k \triangleq \text{DC Gain!}$$

Note that  $C_{01} + C_{02}$  is the total capacitance across  $R_0$

$$\therefore C_0 = C_{01} + C_{02}$$

$$\frac{\omega_n^2}{\omega_0^2} = \frac{R_2 / C_4 C_{01} R_1 R_3 R_5}{R_2 / C_4 (C_{01} + C_{02}) R_1 R_3 R_5}$$

$$= \frac{C_{01}}{C_{01} + C_{02}}$$

$$\frac{\omega_n^2}{\omega_0^2} = \frac{C_{01}}{C_0}$$

$$\therefore C_{01} = C_0 \left( \frac{\omega_n}{\omega_0} \right)^2 = C \left( \frac{\omega_n}{\omega_0} \right)^2$$

Clearly from  $T(s)$  above:

$$\omega_n^2 = R_2 / C_4 C_{01} R_1 R_3 R_5$$

$$\Rightarrow \omega_n = \sqrt{\frac{R_2}{C_4 C_{01} R_1 R_3 R_5}}$$

$$\omega_0^2 = R_2 / C_4 C_0 R_1 R_3 R_5$$

$$\Rightarrow \omega_0 = \sqrt{\frac{R_2}{C_4 (C_{01} + C_{02}) R_1 R_3 R_5}}$$

12.47

For HPN: See Table 12.1 & Fig 11.22(f)

$$T(s) = k \frac{s^2 + (R_2 / C_4 C_0 R_1 R_3 R_5)}{s^2 + s / C_4 R_4 + \left( \frac{R_2}{C_4 C_0 R_1 R_3} \right) \left( \frac{1}{R_{S1}} + \frac{1}{R_{S2}} \right)}$$

clearly:  $\omega_n = \sqrt{\frac{R_2}{C_4 C_0 R_1 R_3 R_5}}$

$$\omega_0 = \sqrt{\frac{R_2}{C_4 C_0 R_1 R_3} \left( \frac{1}{R_{S1}} + \frac{1}{R_{S2}} \right)}$$

At high frequencies  $s \rightarrow \infty$

$$T(\infty) = k \triangleq \text{high freq gain.}$$

Observe that the equivalent resistance at the two terminal of  $A_1$  is:

$$\frac{1}{R_S} = \frac{1}{R_{S1}} + \frac{1}{R_{S2}} \quad \text{AND}$$

for the resonator (table 12.1)

$$R_S = 1/\omega_0 C \Rightarrow \frac{1}{R_S} = \omega_0 C$$

$$\frac{\omega_0^2}{\omega_n^2} = \frac{R_2 / C_4 C_0 R_1 R_3 R_5}{R_2 / C_4 C_0 R_1 R_3 R_{S1}} \Rightarrow R_{S1} = R_5 \frac{\omega_0^2}{\omega_n^2}$$

$$\text{Now } \frac{1}{R_S} = \frac{1}{R_5 \frac{\omega_0^2}{\omega_n^2}} + \frac{1}{R_{S2}}$$

$$\frac{1}{R_{S2}} = \frac{1}{R_5} \left[ 1 - \frac{\omega_n^2}{\omega_0^2} \right]$$

$$R_{S2} = \frac{R_5}{1 - \omega_n^2 / \omega_0^2}$$

12.48

$$T(s) = \frac{0.4508 (s^2 + 1.6996)}{(s + 0.7294)(s^2 + 0.2786s + 1.0504)}$$

PART (a) Replace  $s$  with  $s/\omega_p$

$$T(s) = \frac{0.4508 (s^2/\omega_p^2 + 1.6996)}{\left( \frac{s}{\omega_p} + 0.7294 \right) \left( \frac{s^2}{\omega_p^2} + \frac{0.2786s}{\omega_p} + 1.0504 \right)}$$

CONT.

$$T(s) = \frac{0.4508 \omega_p (s^2 + 1.6996 \omega_p^2)}{(s + 0.7294 \omega_p)(s^2 + 0.2786 \omega_p s + 1.0504 \omega_p^2)}$$

$$\text{sub } \omega_p = 10^4 \text{ rad/s}$$

$$T(s) = \frac{4508 (s^2 + 1.6996 \times 10^8)}{(s + 7294)(s^2 + 2786s + 1.0504 \times 10^8)}$$

Part (b)

First decompose  $T(s)$  into 1st- and 2nd-order sections with unity DC gain!

$$T_1(s) = \frac{k_1}{s + 7294} \quad T_1(0) = \frac{k_1}{7294} = 1$$

$$\Rightarrow \underline{k_1 = 7294}$$

$$\text{Now } k_1 k_2 = 4508 \Rightarrow \underline{k_2 = 0.6180}$$

$$\therefore T_2(s) = \frac{0.6180 (s^2 + 1.6996 \times 10^8)}{s^2 + 2786s + 1.0504 \times 10^8}$$

As a check:

$$T_2(0) = \frac{0.6180 (1.6996 \times 10^8)}{1.0504 \times 10^8} = 1.000$$

As EXPECTED!

$$\therefore T(s) = T_1(s) \cdot T_2(s)$$

For first-order section use Fig 12.13(a)

$$\omega_0 = 7294 \text{ rad/s} \quad \text{DC Gain} = 1$$

$$\text{Let } \underline{C = 10 \text{ nF}}$$

$$R_1 = R_2 = \frac{1}{\omega_0 C} \Rightarrow \underline{R_1 = R_2 = 13.71 \text{ k}\Omega}$$

For second-order section

$$\omega_n^2 = 1.6996 \times 10^8 \Rightarrow \omega_n = 13.037 \times 10^3$$

$$\omega_0^2 = 1.0504 \times 10^8 \Rightarrow \omega_0 = 10.249 \times 10^3$$

$$\frac{\omega_0}{Q} = 2786 \Rightarrow Q = 3.6787$$

For LPN use table 12.1 and Fig 12.22(e)

Make  $R_1 = R_2 = R_3 = R_5 = R$  and

$$C = \underline{C_4 = C_6 = 10 \text{ nF}}$$

$$R = \frac{1}{\omega_0 C} = \underline{9.757 \text{ k}\Omega} = R_1 = R_2 = R_3 = R_5$$

$$\omega_n^2 = \frac{1}{C R^2 C_{61}} \Rightarrow \underline{C_{61} = 6.18 \text{ nF}}$$

$$C_{62} = C - C_{61} = \underline{3.82 \text{ nF}}$$

$$Q = R_6 \sqrt{\frac{C_6}{C_4} \frac{R_2}{R_1 R_3 R_5}} = \frac{R_6}{\sqrt{R^2}}$$

$$= \frac{R_6}{R}$$

$$\therefore R_6 = RQ = (9.757 \times 10^3)(3.6787)$$

$$= \underline{35.89 \text{ k}\Omega}$$

12.49

$$f_0 = 1 \text{ kHz}$$

The 3dB bandwidth for a 2<sup>nd</sup> order filter is given by:

$$B = \omega_0 / Q \Rightarrow Q = \frac{2\pi 10^3}{2\pi 50} = \underline{20}$$

Choose  $C = 10 \text{ nF}$

$$R = \frac{1}{\omega_0 C} = \underline{15.92 \text{ k}\Omega}$$

$$\text{Use } \underline{R_1 = R_f = 10 \text{ k}\Omega}$$

CONT.

$$\frac{R_3}{R_2} = 2Q - 1 = 39$$


choose  $R_2 = 10k\Omega$   $R_3 = 390k\Omega$

$$\text{Now } T(s) = \frac{-k\omega_0 s}{s^2 + s\frac{\omega_0}{Q} + \omega_0^2}$$

$$\Rightarrow |T(j\omega_0)| = \frac{k\omega_0^2}{\omega_0^2/Q} = kQ$$

but  $k = 2 - 1/Q = 1.95$

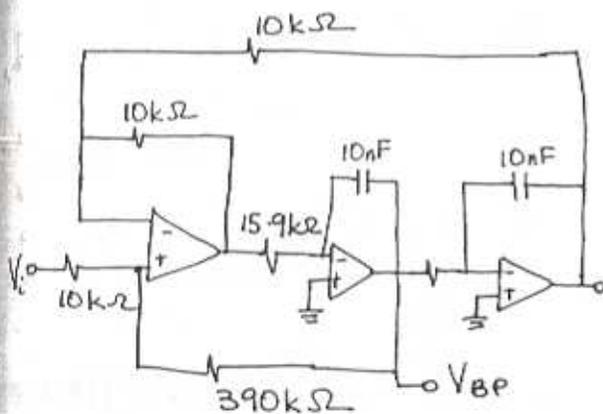$\therefore$  Centre-freq gain =  $kQ = 39$



Part (b) -  $\omega_0 = 10^4$  rad/s  $Q = 2$  Flat Gain = 10

choose  $C = 10nF \Rightarrow R = \frac{1}{\omega_0 C} = 10k\Omega$

choose  $R_F = R_1 = 10k\Omega$

$$\frac{R_3}{R_2} = 2Q - 1 = 3 \Rightarrow R_2 = 10k\Omega$$

$$R_3 = 30k\Omega$$

Now  $k = 2 - 1/Q = 1.5$

$\therefore$  Flat Gain = 10 =  $(1.5) \frac{R_F}{R_H}$

$\therefore \frac{R_H}{R_F} = 0.15$

choose  $R_F = 100k\Omega$

$$R_H = R_L = 15k\Omega$$

$$R_B = QR_H = 30k\Omega$$

12.51

Note  $\omega_n$  does not depend on  $R$  or  $C$   
From eq. 12.67:

$$\frac{R_H}{R_L} = \left(\frac{\omega_n}{\omega_0}\right)^2$$

$\therefore \omega_n = \omega_0 \sqrt{\frac{R_H}{R_L}}$  Nominally  $R_H = R_L \pm 1\%$

Thus:

$$\omega_n' = \omega_0 \sqrt{\frac{1.01}{0.99}} = 1.01\omega_0$$

$$\omega_n'' = \omega_0 \sqrt{\frac{0.99}{1.01}} = 0.99\omega_0$$

$\therefore \omega_n$  can deviate from  $\omega_0$   
by  $\pm 1\%$

12.50

$$R_L = R_H = R_B/Q \Rightarrow R_B = QR_H$$

$$R_L = R_H$$

Using Eq 12.66:

$$\frac{V_o}{V_i} = -k \frac{\frac{R_F}{R_H} s^2 - s\left(\frac{R_F}{R_B}\right)\omega_0 + \left(\frac{R_F}{R_L}\right)\omega_0^2}{s^2 + s\frac{\omega_0}{Q} + \omega_0^2}$$

$$= -k \frac{R_F}{R_H} \frac{s^2 - \frac{\omega_0}{Q}s + \omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

Flat Gain =  $-k \frac{R_F}{R_H}$

12.52

Use Tow Thomas to realize a LPN  
(Fig 12.26)

$$\omega_0 = 10^4 \quad \omega_n = 1.2\omega_0 \quad Q = 10 \quad |G_{\text{pin}}| = 1$$

$$C = 10 \text{ nF} \quad r = 20 \text{ k}\Omega$$

$$R = \frac{1}{\omega_0 C} = \underline{\underline{10 \text{ k}\Omega}}$$

from Eq. 16 (e):

$$\text{DC Gain} = a_2 \frac{\omega_n^2}{\omega_0^2} = 1$$

$$a_2 \frac{1.2^2 \omega_0^2}{\omega_0^2} = 1$$

$$a_2 = \frac{1}{1.2^2} = \text{HF Gain}$$

$$C_1 = C a_2 = \frac{10 \times 10^{-9}}{1.2^2} = \underline{\underline{6.94 \text{ nF}}}$$

$$R_2 = \frac{R (\omega_0 / \omega_n)^2}{\text{HF Gain}} = R \left(\frac{1}{1.2}\right)^2 \times (1.2)^2$$

$$= R = \underline{\underline{10 \text{ k}\Omega}}$$

$$\underline{\underline{R_1 = R_3 = \infty}}$$

12.53

For all pass:

$$T(s) = \frac{-s^2 \left(\frac{C_1}{C}\right) + s \frac{1}{C} \left(\frac{1}{R_1} - \frac{r}{RR_3}\right) + \frac{1}{C^2 RR_2}}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$$\omega_z^2 = \frac{1}{C^2 RR_2} \cdot \frac{C}{C_1} \Rightarrow \underline{\underline{\omega_z = \frac{1}{C \sqrt{RR_2}} \sqrt{\frac{C}{C_1}}}}$$

$$Q_z = \frac{\omega_z}{\frac{1}{C} \left(\frac{1}{R_1} - \frac{r}{RR_3}\right) \frac{C}{C_1}}$$

$$Q_z = \frac{\sqrt{\frac{1}{C^2 RR_2} \frac{C}{C_1}}}{\frac{1}{C} \left(\frac{1}{R_1} - \frac{r}{RR_3}\right) \left(\frac{C}{C_1}\right)} = \frac{1}{\sqrt{RR_2} \left(\frac{1}{R_1} - \frac{r}{RR_3}\right) \sqrt{\frac{C}{C_1}}}$$

For All Pass  $R_1 \rightarrow \infty$

To adjust  $Q_z$ , trim  $r$  or  $R_2$   
(independent of  $\omega_z$ !)

Now  $\omega_0 = \frac{1}{CR}$  so do not trim  $R$  or  $C$ !

Note if we trim  $R_2$  or  $C_1$  to adjust  $\omega_z$ , this will also affect  $Q_z$ . So the options are:

For  $\omega_z$ : (a) trim  $R_2$  AND ( $r$  or  $R_3$ ) to maintain the value of  $Q_z$   
OR

(b) trim  $C_1$ , and  $r$  or  $R_3$

Prefer not to trim a capacitor so use (a)!

12.54

$$T(s) = \frac{0.4508 (s^2 + 1.6996)}{(s + 0.7294)(s^2 + 0.2786s + 1.0504)}$$

Part (a) Replace  $s$  with  $s/\omega_p$   
 $\omega_p = 10^4 \text{ rad/s}$ .

$$T(s) = \frac{0.4508 (s^2/\omega_p^2 + 1.6996)}{\left(\frac{s}{\omega_p} + 0.7294\right) \left(\frac{s^2}{\omega_p^2} + \frac{0.2786s}{\omega_p} + 1.0504\right)}$$

CONT.

$$T(s) = \frac{0.4508 \omega_p (s^2 + 1.6996 \omega_p^2)}{(s + 0.7294 \omega_p)(s^2 + 0.2786 \omega_p s + 1.0504 \omega_p^2)}$$

$$= \frac{4508 (s^2 + 1.6996 \times 10^8)}{(s + 7294)(s^2 + 2786s + 1.0504 \times 10^8)}$$

For FIRST ORDER SECTION use Fig 12.13(g)

$$\omega_0 = 7294 \quad \text{DC gain} = 1$$

choose  $C = 10 \text{ nF}$

$$R_1 = R_2 = \frac{1}{\omega_0 C} \Rightarrow R_1 = R_2 = 13.71 \text{ k}\Omega$$

For SECOND ORDER SECTION - use Fig 12.26

$$\omega_n^2 = 1.6996 \times 10^8 \Rightarrow \omega_n = 13.037 \times 10^3$$

$$\omega_0^2 = 1.0504 \times 10^8 \Rightarrow \omega_0 = 10.249 \times 10^3$$

$$\frac{\omega_0}{Q} = 2786 \Rightarrow Q = 3.6787$$

DC gain = 1

For Tow Thomas LPN use table 12.2

choose  $C = 10 \text{ nF}$

$$R = \frac{1}{\omega_0 C} = \frac{1}{10.249 \times 10^3 \times 10 \times 10^{-9}}$$

$$= 9.757 \text{ k}\Omega$$

choose  $r = 20 \text{ k}\Omega$

Now from Fig 12.16 (e):

$$T(0) = a_2 \frac{\omega_n^2}{\omega_0^2} = 1 \Rightarrow a_2 = \frac{\omega_0^2}{\omega_n^2} = 0.618$$


$\therefore$  HF gain =  $a_2 = 0.618$

$$C_1 = C \times \text{HF gain} \Rightarrow C_1 = 6.18 \text{ nF}$$

$$R_2 = R \left( \frac{\omega_0}{\omega_n} \right)^2$$

$$R_2 = 0.618 R \Rightarrow R_2 = 6.03 \text{ k}\Omega$$
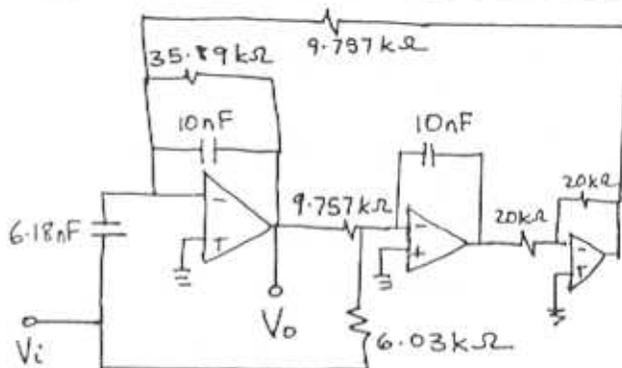
$$R_1 = R_3 = \infty \quad QR = 35.89 \text{ k}\Omega$$



12.55

Make  $C_1 = C_2 = 1 \text{ nF} = C$

$$\omega_0 = \frac{1}{\sqrt{C_1 C_2 R_3 R_4}} \quad Q = \left[ \frac{C_1 C_2 R_3 R_4}{R_3} \left( \frac{1}{C_1} + \frac{1}{C_2} \right) \right]^{-1}$$

$$\text{Let } R_3 = R \quad m = 4Q^2 = 4/2 = 2$$

$$R_4 = \frac{R}{m}$$

$$\therefore \omega_0 = \frac{1}{\sqrt{C^2 R^3/2}} = \frac{\sqrt{2}}{RC} = 10^4$$

$$\Rightarrow R = \frac{\sqrt{2}}{10^4 \cdot 10^{-9}} = 141.42 \text{ k}\Omega$$

$$R_3 = 141.4 \text{ k}\Omega$$

$$R_4 = \frac{R_3}{2} \Rightarrow R_4 = 70.7 \text{ k}\Omega$$

12.56

For Fig 12.2B (a)

$$t(s) = \frac{s^2 + s \left( \frac{1}{C_1} + \frac{1}{C_2} \right) \frac{1}{R_3} + \frac{1}{C_1 C_2 R_3 R_4}}{s^2 + s \left( \frac{1}{C_1 R_3} + \frac{1}{C_1 R_4} + \frac{1}{C_2 R_3} \right) + \frac{1}{C_1 C_2 R_3 R_4}}$$

But  $C_1 = C_2 = C$  &  $R_3 = R_4 = R$ ,  $RC = \tau$ 

$$\begin{aligned} \therefore t(s) &= \frac{s^2 + s^2/RC + 1/R^2 C^2}{s^2 + s^3/RC + 1/R^2 C^2} \\ &= \frac{s^2 + s^2/\tau + 1/\tau^2}{s^2 + s^3/\tau + 1/\tau^2} \end{aligned}$$

Zeros defined by  $\omega_z = 1/\tau$   
 $Q_z = \frac{1}{2}$  $\Rightarrow$  Double Root at  $s = -1/\tau$ Poles of  $t(s)$  are given by the quadratic formula:

$$s = \frac{-3}{2\tau} \pm \frac{\sqrt{5}}{2\tau} = \frac{-3 \pm \sqrt{5}}{2\tau}$$


i.e. two roots on the negative real axis

If the network is placed in the negative feedback path of an ideal amplifier ( $A = \infty$ ) then the poles are given by the zeros of  $t(s)$ :

Closed loop poles:

$$s = -1/\tau \quad (\text{multiplicity} = 2)$$

12.57

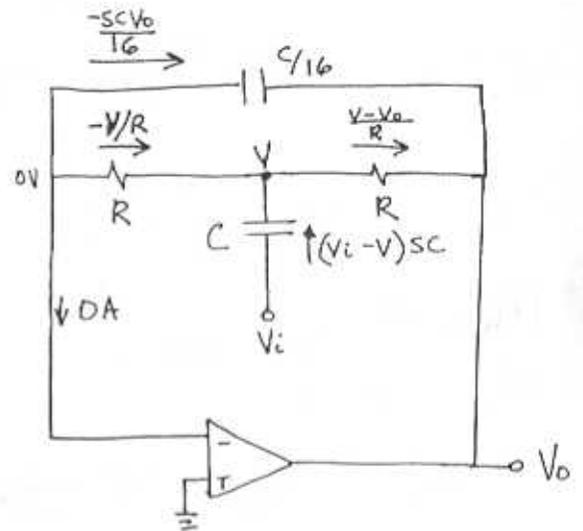Note first  $-\frac{sCV_o}{16} = -\frac{V}{R}$ 

$$V = -\frac{sCRV_o}{16}$$

 $\sum I$  at  $V$ 

$$-\frac{V}{R} + sC(V_i - V) - \frac{V - V_o}{R} = 0$$

$$\frac{sCV_o R}{R 16} + sCV_i + s^2 \frac{C^2 R V_o}{16} + \frac{sCV_o}{16} + \frac{V_o}{R} = 0$$

mult by:  $16R$  and let  $RC = \tau$ 

$$s\tau V_o + 16\tau V_i s + s^2 \tau^2 V_o + s\tau V_o + 16V_o = 0$$

$$V_o [s^2 \tau^2 + s \times 2\tau + 16] = -16s\tau V_i$$

$$\therefore \frac{V_o}{V_i} = -\frac{16s\tau}{s^2 \tau^2 + 2\tau s + 16}$$

$$\therefore T(s) = \frac{s 16/RC}{s^2 + s^2/RC + 16/RC^2}$$

CONT.

$$\text{Let } \omega_0^2 = \frac{16}{(RC)^2} \Rightarrow \omega_0 = \frac{4}{RC}$$


$$\frac{\omega_0}{Q} = \frac{2}{RC} \Rightarrow Q = \frac{RC\omega_0}{2} = \underline{\underline{2}}$$

$$\therefore \frac{V_o}{V_i} = \frac{-4\omega_0 s}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$$\left. \begin{aligned} |T|_{s=0} &= 0 \\ |T|_{s=\infty} &= 0 \end{aligned} \right\} \text{Bandpass}$$

$$|T(j\omega_0)| = 4/1/2 = 8 \frac{V}{V} \text{ CENTRE FREQ GAIN}$$

12.5B

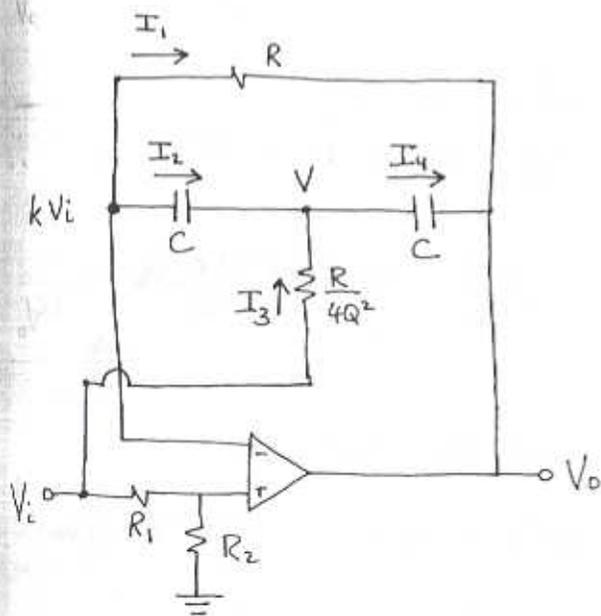

$$RC = 2Q/\omega_0$$

$$k = \frac{R_2}{R_1 + R_2}$$

$$V_{+ve} = V_{-ve} = kV_i \text{ due to virtual short}$$

$$I_1 = -I_2$$

$$\frac{kV_i - V_o}{R} = \frac{V - kV_i}{1} (sC)$$

$$V = \frac{1}{sCR} (kV_i - V_o + sCRkV_i)$$

$$\sum I \text{ at } V = 0$$

$$I_2 + I_3 - I_4 = 0$$

$$sC(kV_i - V) + \frac{4Q^2}{R}(V_i - V) - sC(V - V_o) = 0$$

$$sC(kV_i - \frac{kV_i}{sCR} + \frac{V_o}{sCR} - kV_i)$$

$$+ \frac{4Q^2}{R}(V_i - \frac{kV_i}{sCR} + \frac{V_o}{sCR} - kV_i)$$

$$- sC(\frac{kV_i}{sCR} - \frac{V_o}{sCR} + kV_i - V_o) = 0$$

$\Rightarrow$

$$-\frac{kV_i}{R} + \frac{V_o}{R}$$

$$+ \frac{4Q^2}{R}(V_i - \frac{kV_i}{sCR} + \frac{V_o}{sCR} - kV_i)$$

$$- \frac{sC}{R}(\frac{kV_i}{sC} - \frac{V_o}{sC} + kRV_i - V_oR)$$

$= 0$

$$\Rightarrow \text{SUB } CR = \frac{2Q}{\omega_0} \quad \& \quad R = \frac{2Q}{C\omega_0}$$

$$\begin{aligned} & -kV_i + V_o \\ & + 4Q^2 V_i - \frac{2Q^2 kV_i \omega_0}{s \& R} + \frac{V_o \omega_0 4Q^2}{s \& R} - 4Q^2 kV_i \\ & - kV_i + V_o - s k \frac{2Q}{\omega_0} V_i + s V_o \frac{2Q}{\omega_0} = 0 \end{aligned}$$

$$V_o \left[ 1 + \frac{2Q\omega_0}{s} + 1 + \frac{2Qs}{\omega_0} \right]$$

$$= V_i \left[ k - 4Q^2 + \frac{2kQ\omega_0}{s} + 4Q^2k + k + \frac{2kQs}{\omega_0} \right]$$

$$\Rightarrow V_o \left[ s^2 \frac{2Q}{\omega_0} + 2s + 2Q\omega_0 \right] = V_i \left[ s^2 \frac{2kQ}{\omega_0} + s(4Q^2k - 4Q^2 + 2k) + 2kQ\omega_0 \right]$$

$$\Rightarrow \frac{V_o}{V_i} = \frac{s^2 \frac{2kQ}{\omega_0} + s(4Q^2k - 4Q^2 + 2k) + 2kQ\omega_0}{s^2 \frac{2Q}{\omega_0} + 2s + 2Q\omega_0}$$

$$= k \frac{s^2 + s \frac{\omega_0}{Q} (2Q^2 - \frac{2Q^2}{k} + 1) + \omega_0^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

Recall  $k = \frac{R_2}{R_1 + R_2}$  and  $\frac{1}{k} = 1 + \frac{R_1}{R_2}$

$$\Rightarrow \frac{V_o}{V_i} = \left( \frac{R_2}{R_1 + R_2} \right) \frac{s^2 + s \frac{\omega_0}{Q} \left( 1 - \frac{R_1}{R_2} \cdot 2Q^2 \right) + \omega_0^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$$\therefore T(s) = \frac{R_2}{R_1 + R_2} \frac{s^2 + s \frac{\omega_0}{Q} \left( 1 - \frac{2Q^2 R_1}{R_2} \right) + \omega_0^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

For All Pass

we want  $T(s) \propto \frac{s^2 + \frac{\omega_0}{Q}(-1)s + \omega_0^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$

$$\Rightarrow 1 - \frac{2Q^2 R_1}{R_2} = -1$$

$$2Q^2 \frac{R_1}{R_2} = 2$$

$$\frac{R_1}{R_2} = \frac{1}{Q^2}$$

$$\therefore \frac{R_2}{R_1} = Q^2 \quad \& \quad \frac{R_2}{R_1 + R_2} = \frac{R_2/R_1}{1 + R_2/R_1}$$

$$= \frac{Q^2}{1 + Q^2}$$


For Notch :

$$1 - 2Q^2 \frac{R_1}{R_2} = 0$$

$$\frac{R_1}{R_2} = \frac{1}{2Q^2}$$

$$\frac{R_2}{R_1} = 2Q^2 \quad \& \quad \frac{R_2}{R_1 + R_2} = \frac{2Q^2}{1 + 2Q^2}$$

12.59

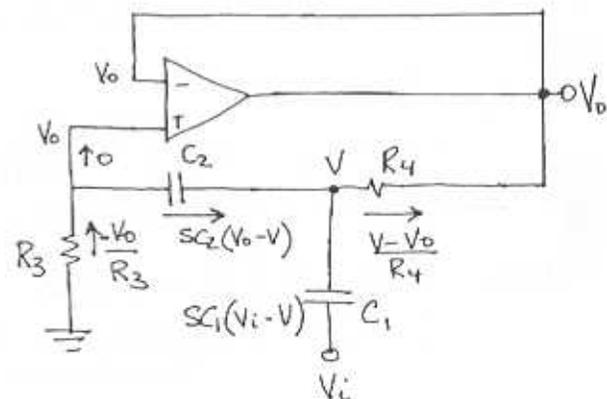

∵ No current can't flow into +ve terminal

$$-\frac{V_o}{R_3} = sC_2(V_o - V)$$

$$V = V_o \left( 1 + \frac{1}{sC_2 R_3} \right)$$

CONT.

$$\sum I @ V = 0$$

$$-\frac{V_o}{R_3} + \frac{V_i - V}{1} s C_1 = \frac{V - V_o}{R_4}$$

$$V_o \left[ -\frac{1}{R_3} + \frac{1}{R_4} \right] + V \left[ -s C_1 - \frac{1}{R_4} \right] = -s C_1 V_i$$

$$V_o [R_4 - R_3] + V [s C_1 R_3 R_4 + R_3] = \frac{1}{s} s C_1 R_3 R_4 V_i$$

$$V_o (R_4 - R_3) + V_o \left( 1 + \frac{1}{s C_1 R_3} \right) (s C_1 R_3 R_4 + R_3) = s C_1 R_3 R_4 V_i$$

$$V_o \left( R_4 - R_3 + s C_1 R_3 R_4 + R_3 + \frac{C_1}{C_2} R_4 + \frac{1}{s C_2} \right)$$

$$= s C_1 R_3 R_4 V_i$$

$$V_o \left( s^2 C_1 C_2 R_3 R_4 + s C_1 R_4 + s C_2 R_4 + 1 \right) = s^2 C_1 R_3 R_4 C_2 V_i$$

$$\therefore \frac{V_o}{V_i} = \frac{s^2 C_1 C_2 R_3 R_4}{s^2 C_1 C_2 R_3 R_4 + s C_1 R_4 + s C_2 R_4 + 1}$$

$$= \frac{s^2}{s^2 + s \left( \frac{1}{C_1 R_3} + \frac{1}{C_1 R_4} \right) + \frac{1}{C_1 C_2 R_3 R_4}}$$

Note  $|T(0)| = 0$  }  $\therefore$  High Pass  
 $|T(\infty)| = 1$  } High Freq Gain =  $\frac{1}{V}$

3dB frag =  $10^3$  rad/s,  $Q = \frac{1}{\sqrt{2}}$  for max flat.

$$\therefore \omega_0 = 10^3 \frac{\text{rad}}{\text{s}} \quad C_1 = C_2 = 10 \text{ nF}$$

clearly  $\omega_0^2 = \frac{1}{C_1 C_2 R_3 R_4}$  and

$$\frac{\omega_0}{Q} = \frac{1}{C_2 R_3} + \frac{1}{C_1 R_4} = \frac{C_1 + C_2}{C_1 C_2 R_3}$$

$$= \frac{2C}{C^2 R_3} = \frac{2}{C R_3} = \sqrt{2} \times 10^3$$

$$R_3 = \frac{2}{10 \times 10^{-9} \times 10^3 \times \sqrt{2}}$$

$$\underline{R_3 = 141.4 \text{ k}\Omega}$$

$$R_4 = \frac{1}{\omega_0^2 C_1 C_2 R_3} \Rightarrow \underline{R_4 = 70.7 \text{ k}\Omega}$$

12.60

$$A_{\text{max}} = 3 \text{ dB}$$

$$\epsilon = \left( 10^{3/10} - 1 \right)^{-1/2} \approx 1$$

$$\omega_0 = \omega_p \left( \frac{1}{\epsilon} \right)^{1/N} = \omega_p = 2\pi 5000 = 10^4 \pi$$

$$Q_1 = \frac{1}{2 \cos 36} = 0.618$$

$$Q_2 = \frac{1}{2 \cos 72} =$$

For first order section:

$$\omega_0 = 10^4 \pi \quad \text{dc gain} = 1$$

From 12.13 (a)


$$\underline{R_1 = R_2 = 10 \text{ k}\Omega}$$

$$C = \frac{1}{\omega_0 R_2} = \frac{1}{10^4 \pi 10^4} = \underline{3.18 \text{ nF}}$$

Second-Order Section  $Q = 0.618$ :

from 12.34 (c):  $m = 4Q^2 = 1.528$


CONT.

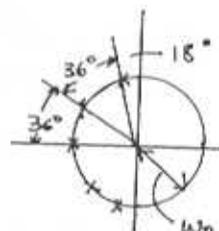

$$RC = \frac{2Q}{\omega_0} \quad \text{let } R_1 = R_2 = 10k\Omega$$

$$C = \frac{2Q}{\omega_0 R} \Rightarrow C_4 = C = 3.93nF$$

$$C_3 = \frac{C}{m} = 2.57nF$$

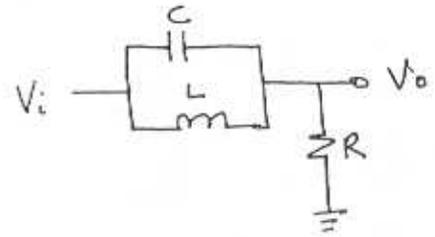

this is the same as Fig 12.18(e)

Second Order Section  $Q = 1.618$ :

$$C = \frac{2Q}{\omega_0 R} \quad m = 4Q^2 = 10.472$$

$$= 10.3nF \Rightarrow R_1 = R_2 = 10k\Omega$$

$$C_4 = C = 10.3nF$$

$$C_3 = \frac{C}{m} = 0.984nF$$

12.61

For a bandpass filter

$$T(s) = \frac{\omega_0/Q s}{s^2 + s\omega_0/Q + \omega_0^2}$$


centre freq. gain = 1

complementary transfer function:

$$T'(s) = 1 - T$$

$$= \frac{s^2 + \omega_0^2}{s^2 + s\omega_0/Q + \omega_0^2} \equiv \text{NOTCH!}$$

From Fig 12.18(d)

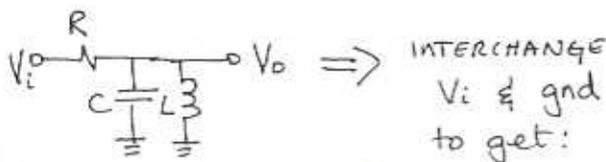

INTERCHANGE  
Vi & gnd  
to get:

12.62

for Fig 12.18(d):

$$T(s) = \frac{s/R}{s^2 + s/R + 1/LC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad Q = R\sqrt{\frac{C}{L}}$$

FOR  $\omega_0$

$$\frac{\partial \omega_0}{\partial L} = \frac{\partial (LC)^{-1/2}}{\partial L} = -\frac{1}{2} L^{-3/2} C^{-1/2} = -\frac{\omega_0}{2L}$$

$$\frac{\partial \omega_0}{\partial C} = -\frac{\omega_0}{2C}$$

$$\frac{\partial \omega_0}{\partial R} = 0$$

$$\therefore S_L^{\omega_0} = \frac{\partial \omega_0}{\partial L} \frac{L}{\omega_0} = -\frac{1}{2}$$

$$S_C^{\omega_0} = \frac{\partial \omega_0}{\partial C} \times \frac{C}{\omega_0} = -\frac{1}{2}$$

$$S_R^{\omega_0} = \frac{\partial \omega_0}{\partial R} \frac{R}{\omega_0} = 0$$

FOR Q

$$\frac{\partial Q}{\partial L} = \frac{R\sqrt{C}}{L\sqrt{L}} \left(-\frac{1}{2}\right)$$

$$\frac{\partial Q}{\partial C} = \frac{1}{2} \frac{R}{\sqrt{LC}} = \frac{1}{2} \frac{R\sqrt{C}}{C\sqrt{L}} = \frac{Q}{2C}$$

$$\frac{\partial Q}{\partial R} = \sqrt{C/L} = \frac{R}{R} \sqrt{C/L} = Q/R$$

CONT.

$$S_L^Q = \frac{-Q}{2L} \cdot \frac{L}{Q} = \underline{\underline{-\frac{1}{2}}}$$

$$S_C^Q = \frac{Q}{2C} \cdot \frac{C}{Q} = \underline{\underline{\frac{1}{2}}}$$

$$S_R^Q = \frac{Q}{R} \cdot \frac{R}{Q} = \underline{\underline{1}}$$

Part (d)  $y = u^n$

$$S_x^y = \frac{\partial y}{\partial x} \cdot \frac{x}{y} = \frac{\partial (u^n)}{\partial x} \cdot \frac{x}{u^n}$$

$$= n u^{n-1} \frac{\partial u}{\partial x} \cdot \frac{x}{u^n}$$

$$= n \frac{\partial u}{\partial x} \frac{x}{u} = \underline{\underline{n S_x^u}}$$

Part (e)  $y = f_1(u)$   $u = f_2(x)$

$$S_x^y = \frac{\partial y}{\partial x} \frac{x}{y} = \frac{\partial f_1(u)}{\partial x} \frac{x}{f_1(u)}$$

$$= \frac{\partial f_1(u)}{\partial u} \frac{\partial u}{\partial x} \cdot \frac{x}{f_1(u)}$$

$$= \frac{\partial f_1}{\partial u} \cdot \frac{\partial f_2}{\partial x} \cdot \frac{x}{f_1} \cdot \frac{u}{u}$$

But  $u = f_2$

$$\therefore S_x^y = \frac{\partial f_1}{\partial u} \cdot \frac{\partial f_2}{\partial x} \cdot \frac{x}{f_1} \cdot \frac{u}{f_2}$$

$$= \frac{\partial f_1}{\partial u} \cdot \frac{u}{f_1} \cdot \frac{\partial f_2}{\partial x} \frac{x}{f_2}$$

$$= S_u^{f_1} \cdot S_x^{f_2}$$

$$= \underline{\underline{S_u^y S_x^u}}$$

12.64

Since the characteristic equation of Fig. 12-33(b) is the same as for Fig. 12-29 the poles are given by Eq. 12-86:

$$s^2 + s \frac{\omega_0}{Q} \left[ 1 + \frac{2Q^2}{A+1} \right] + \omega_0^2 = 0$$

This is because 12-33(b) is based on the complementary transform of 12-29 and hence the pole

12.63

$y = uv$

$$S_x^y = \frac{\partial (uv)}{\partial x} \frac{x}{uv}$$

$$= v \frac{\partial u}{\partial x} \frac{x}{uv} + u \frac{\partial v}{\partial x} \frac{x}{uv}$$

$$= \frac{\partial u}{\partial x} \frac{x}{u} + \frac{\partial v}{\partial x} \frac{x}{v}$$

$$= \underline{\underline{S_x^u + S_x^v}}$$

Part (b)  $y = u/v$

$$S_x^y = \frac{\partial y}{\partial x} \cdot \frac{x}{y} = \frac{\partial (u/v)}{\partial x} \frac{xv}{u}$$

$$= \frac{1}{v} \frac{\partial u}{\partial x} \frac{xv}{u} + \frac{-u}{v^2} \frac{\partial v}{\partial x} \cdot \frac{xv}{u}$$

$$= \frac{\partial u}{\partial x} \frac{x}{u} - \frac{\partial v}{\partial x} \frac{x}{v}$$

$$= \underline{\underline{S_x^u - S_x^v}}$$

Part (c)  $y = ku$

$$S_x^y = \frac{\partial y}{\partial x} \cdot \frac{x}{y} = \frac{\partial (ku)}{\partial x} \frac{x}{ku}$$

$$= k \frac{\partial u}{\partial x} \frac{x}{ku}$$

$$= \frac{\partial u}{\partial x} \frac{x}{u}$$

$$= \underline{\underline{S_x^u}}$$

locations are preserved!  
Now the actual  $w_0$  and  $Q$  are given by:

$$w_{0,a} = w_0 \quad \text{and} \quad Q_a = \frac{Q}{1 + \frac{2Q^2}{A+1}}$$

Thus from Ex. 12.3

$$S_A^{w_{0,a}} = \underline{\underline{0}}$$

$$S_A^{Q_a} = \frac{A}{A+1} \frac{2Q^2/(A+1)}{1 + 2Q^2/(A+1)}$$

$$\therefore S_A^{Q_a} \approx \underline{\underline{\frac{2Q^2}{A}}}$$

12.65

If  $R_1 = R_2$ , then from (12.77) & (12.78)

$$w_0 = \frac{1}{\sqrt{C_3 C_4 R_1 R_2}}$$

$$Q = \frac{1}{\sqrt{C_3 C_4 R_1 R_2} \left(\frac{1}{C_4}\right) \left(\frac{1}{R_1} + \frac{1}{R_2}\right)}$$

$$\frac{\partial w_0}{\partial C_3} = \frac{-1}{2C_3 \sqrt{C_3 C_4 R_1 R_2}}$$

$$\frac{\partial w_0}{\partial C_3} = \frac{-1}{2C_3 \sqrt{C_3 C_4 R_1 R_2}} = -\frac{w_0}{2C_3}$$

$$S_{C_3}^{w_0} = \frac{\partial w_0}{\partial C_3} \frac{C_3}{w_0} = \underline{\underline{-\frac{1}{2}}}$$

$$\text{clearly } S_{C_3}^{w_0} = S_{C_4}^{w_0} = S_{R_1}^{w_0} = S_{R_2}^{w_0} = \underline{\underline{-\frac{1}{2}}}$$

$$\frac{\partial Q}{\partial C_3} = \frac{-1}{2C_3 \sqrt{C_3 C_4 R_1 R_2} \left(\frac{1}{C_4}\right) \left(\frac{1}{R_1} + \frac{1}{R_2}\right)} = \frac{-Q}{2C_3}$$

$$\therefore S_{C_3}^Q = \underline{\underline{-\frac{1}{2}}}$$

$$\frac{\partial Q}{\partial C_4} = \frac{Q}{2C_4} \Rightarrow S_{C_4}^Q = \underline{\underline{+\frac{1}{2}}}$$

$$\begin{aligned} \frac{\partial Q}{\partial R_1} &= \frac{\frac{1}{\sqrt{R_1}} - \sqrt{R_1}/R_2}{R_1 \left(\frac{1}{\sqrt{R_1}} + \sqrt{R_1}/R_2\right)} \cdot \frac{Q}{2} \\ &= \frac{\sqrt{R_2/R_1} - \sqrt{R_1/R_2}}{R_1 \left(\sqrt{R_2/R_1} + \sqrt{R_1/R_2}\right)} \cdot \frac{Q}{2} \end{aligned}$$

$$\therefore S_{R_1}^Q = \frac{\sqrt{R_2/R_1} - \sqrt{R_1/R_2}}{\sqrt{R_2/R_1} + \sqrt{R_1/R_2}}$$

$$\text{if } R_1 = R_2 \Rightarrow \underline{\underline{S_{R_1}^Q = 0}} \quad \& \quad \underline{\underline{S_{R_2}^Q = 0}}$$

12.66

From table 12.1

$$w_0 = \frac{1}{\sqrt{C_4 C_6 R_1 R_3 R_5 / R_2}}$$

$$Q = R_6 \sqrt{\frac{C_6}{C_4} \frac{R_2}{R_1 R_3 R_5}}$$

$$\frac{\partial w_0}{\partial C_4} = \frac{-w_0}{2C_4}$$

$$\therefore S_{C_4}^{w_0} = \frac{-w_0}{2C_4} \times \frac{C_4}{w_0} = \underline{\underline{-\frac{1}{2}}}$$

$$\text{Similarly } S_{C_6}^{w_0} = S_{R_1}^{w_0} = S_{R_3}^{w_0} = S_{R_5}^{w_0} = \underline{\underline{-\frac{1}{2}}}$$

$$\frac{\partial w_0}{\partial R_2} = \frac{w_0}{2R_2} \Rightarrow S_{R_2}^{w_0} = \underline{\underline{\frac{1}{2}}}$$

Now for  $Q$ :

$$\frac{\partial Q}{\partial R_6} = \frac{Q}{R_6} \Rightarrow S_{R_6}^Q = \frac{\partial Q}{\partial R_6} \frac{R_6}{Q} = \underline{\underline{+1}}$$

CONT.

$$\frac{\partial Q}{\partial C_6} = \frac{Q}{2C_6} \Rightarrow S_{C_6}^Q = S_{R_2}^Q = \underline{\underline{+\frac{1}{2}}}$$

$$\frac{\partial Q}{\partial C_4} = \frac{-Q}{2C_4} \Rightarrow S_{C_4}^Q = S_{R_1, R_3, R_5}^Q = \underline{\underline{-\frac{1}{2}}}$$

12.67

$$R_{eq} = \frac{T_c}{C_1} = \frac{1/100 \times 10^3}{C_1}$$

$$\text{for } 1\text{pF} \rightarrow R_{eq} = 10^{-5}/10^{-12} = \underline{\underline{10\text{M}\Omega}}$$

$$\text{for } 10\text{pF} \rightarrow R_{eq} = 10^{-5}/10 \times 10^{-12} = \underline{\underline{1\text{M}\Omega}}$$

12.68

charge transferred  $\Rightarrow Q = CV$   
 $= 10^{-12}(1)$   
 $= \underline{\underline{1\text{pC}}}$

For  $f_0 = 100\text{kHz}$ , average current is given by:

$$I_{AVE} = \frac{Q}{T} = 1\text{pC} \times \frac{1}{100 \times 10^3}$$

$$= \underline{\underline{0.1\mu\text{A}}}$$

For each clock cycle, the output will change by the same amount as the change in voltage across  $C_2$ !

$$\therefore \Delta V = Q/C_2 = \frac{1\text{pC}}{10\text{pF}} = \underline{\underline{0.1\text{V}}}$$

For  $\Delta V = 0.1\text{V}$  for each clock cycle, the amplifier will saturate in

$$\# \text{cycles} = \frac{10\text{V}}{0.1\text{V}} = \underline{\underline{100 \text{ cycles}}}$$

$$\text{slope} = \frac{\Delta V}{\Delta t} = \frac{10\text{V}}{(100 \text{ cycles}) (1/100 \times 10^3)}$$

$$= \underline{\underline{10^4 \frac{\text{V}}{\text{s}}}}$$

12.69

$$f_c = 400\text{kHz} \quad f_0 = 10\text{kHz} \quad Q = 20$$

$$C_1 = C_2 = 20\text{pF} = C$$

$$C_3 = C_4 = \omega_0 T_c C = 2\pi(10^4) \frac{1}{400 \times 10^3} 20 \times 10^{-12}$$

$$= \underline{\underline{3.14\text{pF}}}$$

$$C_5 = \frac{\omega_0 T_c C}{Q}$$

$$= \frac{C_3}{Q} = \underline{\underline{0.157\text{pF}}}$$

$$C_6 = \frac{\omega_0 T_c C}{Q} \times \text{center frequency gain}$$

$$= \underline{\underline{0.157\text{pF}}}$$

Note that the clock frequency has doubled. Hence the period,  $T_c$ , is halved. Therefore, for the same integrating capacitors, the resistors (switched capacitors) will change by the factor of 2. So compensate for this by changing the switched caps by a factor of 1/2.

12.70

$$\text{Ex 12-31 for } Q = 40 \quad f_c = 200\text{kHz}$$

$$f_0 = 10\text{kHz}$$

$$C_1 = C_2 = 20\text{pF} = C$$

$$C_3 = C_4 = \omega_0 T_c C$$

$$= 2\pi(10^4) \left( \frac{1}{200 \times 10^3} \right) 20 \times 10^{-12}$$

$$= \underline{\underline{6.28\text{pF}}}$$

CONT.

$$C_B = \frac{\omega_0 T_c C}{Q} = \frac{C_3}{Q} = \underline{\underline{0.157 \text{ pF}}}$$

$$C_G = \frac{\omega_0 T_c C}{Q} = C_B = \underline{\underline{0.157 \text{ pF}}}$$

12.71

$$\omega_0 = 10^4, Q = \sqrt{2}, f_c = 100 \text{ kHz}$$


$$\text{DC gain} \Rightarrow \frac{R_4}{R_6} \Rightarrow \frac{C_6}{C_4} = 1$$

$$C_1 = C_2 = 10 \text{ pF}$$

$$\begin{aligned} C_3 = C_4 = C_6 &= \omega_0 T_c C \\ &= 10^4 \left( \frac{1}{100 \times 10^3} \right) 10 \times 10^{-12} \\ &= \underline{\underline{1 \text{ pF}}} \end{aligned}$$

$$C_B = C_4/Q = \underline{\underline{1.41 \text{ pF}}}$$

12.72

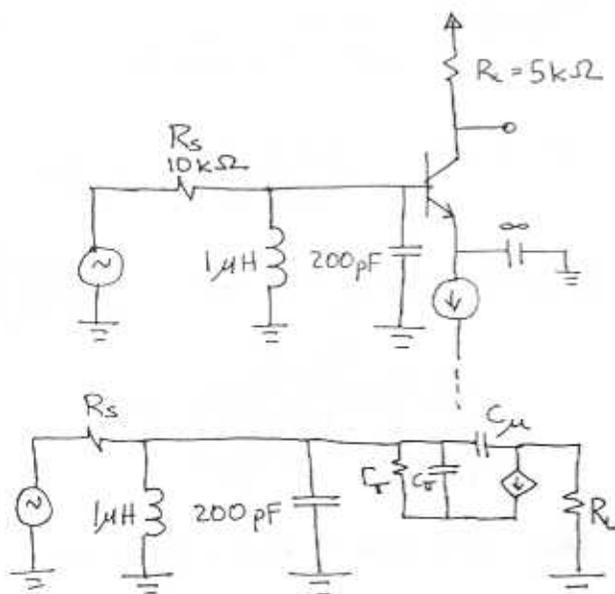

$$r_e = 25 \Omega, C_{\mu} = 1 \text{ pF}, C_{\pi} = 10 \text{ pF}, \beta = 200$$

$$r_{\pi} = (\beta + 1) r_e = 5.025 \text{ k}\Omega$$

From base to collector

$$\frac{V_c}{V_b} = -\frac{\beta}{\beta + 1} \cdot \frac{R_c}{r_e} = -199 = k$$

Total capacitance at base

$$\begin{aligned} C_T &= C_{\pi} + 200 \text{ p} + C_{\mu} (1 - k) \quad \leftarrow \text{Miller Effect} \\ &= 10 + 200 + 1(1 + 199) \\ &= 410 \text{ pF} \end{aligned}$$

$$\begin{aligned} \therefore \omega_0 &= \frac{1}{\sqrt{LC}} \\ &= \frac{1}{\sqrt{10^{-6} \times 410 \times 10^{-12}}} \\ &= \underline{\underline{49.4 \times 10^6 \text{ rad/s}}} \end{aligned}$$

Centre frequency gain =

$$\begin{aligned} &\frac{r_{\pi}}{R_s + r_{\pi}} \cdot k \\ &= \frac{5.025}{10 + 5.025} \times -199 \\ &= \underline{\underline{-66.6 \text{ V/V}}} \end{aligned}$$

$$\begin{aligned} \text{BW} &= \frac{1}{RC} \\ &= \frac{1}{(R_s \parallel r_{\pi}) 410 \text{ pF}} \\ &= \underline{\underline{729 \times 10^3 \frac{\text{rad}}{\text{s}}}} \end{aligned}$$

$$\begin{aligned} Q &= \frac{\omega_0}{\text{BW}} \\ &= 49.4 / 0.7293 \\ &= \underline{\underline{67.7}} \end{aligned}$$

12.73

$$Q_0 = \frac{R_p}{\omega_0 L} \Rightarrow R_p = Q_0 \omega_0 L$$

$$= 200 (2\pi \cdot 10^4) (10 \times 10^{-6})$$

$$= \underline{12.57 \text{ k}\Omega}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow C = \frac{1}{\omega_0^2 L}$$

$$= \frac{1}{(2\pi \cdot 10^4)^2 \cdot 10 \times 10^{-6}}$$

$$= \underline{2.533 \text{ nF}}$$

$$B = \frac{1}{RC} \quad R_r = \frac{1}{(2\pi \times 10 \times 10^3) (2.533 \times 10^{-9})}$$

$$= 6.283 \text{ k}\Omega$$

$$\therefore \frac{1}{R_i} + \frac{1}{R_p} = \frac{1}{R_r}$$


$$\Rightarrow R_i = \underline{12.57 \text{ k}\Omega} \quad \text{i.e. } R_i \parallel R_p = R_r$$

12.74

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$= (2\pi(36 \times 10^{-9}) \cdot 10^{-9})^{-1}$$

$$= \underline{838.8 \text{ kHz}}$$

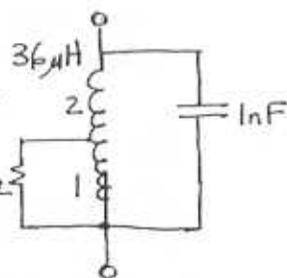

$$R_p = n^2 R$$

$$= 9 (1 \text{ k}\Omega)$$


$$= 9 \text{ k}\Omega$$

$$Q = R_p / \omega_0 L$$

$$= \frac{9 \times 10^3}{2\pi \cdot 838.8 \times 10^3 \times 36 \times 10^{-6}}$$

$$= \underline{47.4}$$

12.75

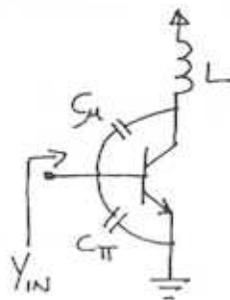for  $\omega C_{\mu} \ll \frac{1}{\omega L}$ 

$$\therefore \omega^2 \ll \frac{1}{LC_{\mu}}$$

ie well below resonance

$$\therefore \text{gain} = -g_m(j\omega L)$$

$$\therefore Y_{in} = \frac{1}{R_{\pi}} + j\omega C_{\pi} + j\omega C_{\mu} (1 + g_m j\omega L)$$

$$= \left( \frac{1}{R_{\pi}} - \omega^2 g_m C_{\mu} L \right) + j\omega (C_{\pi} + C_{\mu})$$

AS REQUIRED!

12.76

From Fig 12.16 (c):

$$T(s) = \frac{a_1 s}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$$T(j\omega) = \frac{j a_1 \omega}{\omega_0^2 - \omega^2 + j \omega \frac{\omega_0}{Q}}$$

$$T(j\omega_0) = \frac{j a_1 \omega_0}{j \omega_0^2 / Q} = \frac{a_1 Q}{\omega_0}$$

$$|T(j\omega)| = a_1 \omega \left[ (\omega_0^2 - \omega^2)^2 + \left( \frac{\omega \omega_0}{Q} \right)^2 \right]^{-1/2}$$

$$= \frac{a_1 \omega \cdot Q / \omega \omega_0}{\sqrt{1 + Q^2 \left( \frac{\omega_0^2 - \omega^2}{\omega_0 \omega} \right)^2}}$$

$$\text{Now } \omega = \omega_0 + \delta \omega, \quad \frac{\delta \omega}{\omega_0} \ll 1$$

$$\text{and } \omega^2 \approx \omega_0^2 \left( 1 + 2 \frac{\delta \omega}{\omega_0} \right)$$

CONT.

$$\text{so } \omega_0^2 - \omega^2 = -2\delta\omega\omega_0$$

$$\therefore |T(j\omega)| \cong \frac{a_1 Q / \omega_0}{\sqrt{1 + Q^2 \left(\frac{2\delta\omega}{\omega}\right)^2}}$$

$$\text{for } Q \gg 1: Q^2 \left(\frac{2\delta\omega}{\omega}\right)^2 \cong Q^2 \left(\frac{2\delta\omega}{\omega_0}\right)^2$$

∴  $\omega \approx \omega_0!$

$$\Rightarrow |T(j\omega)| \cong \frac{|T(j\omega_0)|}{\sqrt{1 + Q^2 \left(\frac{2\delta\omega}{\omega_0}\right)^2}}$$

$$= \frac{|T(j\omega_0)|}{\sqrt{1 + 4Q^2 \frac{\delta\omega^2}{\omega_0^2}}}$$

For  $N$  bandpass sections, synchronously tuned in cascade, half power is given by:

$$\left( \frac{1}{\sqrt{1 + 4Q^2 \left(\frac{\delta\omega}{\omega_0}\right)^2}} \right)^N = \frac{1}{\sqrt{2}}$$

$$\left( 1 + 4Q^2 \left(\frac{\delta\omega}{\omega_0}\right)^2 \right)^N = 2$$

$$4Q^2 \left(\frac{\delta\omega}{\omega_0}\right)^2 = 2^{1/N} - 1$$

$$\delta\omega = \frac{\omega_0}{2Q} \sqrt{2^{1/N} - 1}$$

∴ Bandwidth:

$$B = 2\delta\omega = \frac{\omega_0}{Q} \sqrt{2^{1/N} - 1}$$

12.77

For first order lowpass:

$$T(s) = \frac{\omega_0'}{s + \omega_0'} \quad |T(j\omega)| = \frac{\omega_0'}{\sqrt{\omega^2 + \omega_0'^2}}$$

for a bandpass response around  $\omega_0$  with  $\omega_0' = \frac{\omega_0}{2Q}$ :

$$|T(j\omega)| \cong \frac{\omega_0 / 2Q}{(\delta\omega)^2 + \left(\frac{\omega_0}{2Q}\right)^2}$$

$$= \frac{\omega_0 / 2Q}{\frac{\omega_0}{2Q} \sqrt{\left(\frac{2Q}{\omega_0}\right)^2 (\delta\omega)^2 + 1}}$$

$$= \frac{1}{\sqrt{1 + 4Q^2 \left(\frac{\delta\omega}{\omega_0}\right)^2}}$$

Now at  $\omega = \omega_0$  or  $\delta\omega = 0$   
 $|T(j\omega_0)| = 1$ , then

$$T(j\omega) \cong \frac{|T(j\omega_0)|}{\sqrt{1 + 4Q^2 \left(\frac{\delta\omega}{\omega_0}\right)^2}}$$

Part (b)

For  $N$  synchronously tuned sections in cascade; 3dB bandwidth is given by:

$$\left( \frac{|T|}{|T_0|} \right)^N = \frac{1}{\sqrt{2}}$$

$$\left( \frac{|T|}{|T_0|} \right)^2 = \frac{1}{2^{1/N}} \quad \text{OR}$$

$$1 + 4Q^2 \left(\frac{\delta\omega}{\omega_0}\right)^2 = 2^{1/N} \quad \text{OR}$$

$$2\delta\omega = \frac{\omega_0}{Q} \sqrt{2^{1/N} - 1} \quad (12.110)$$

CONT.

Thus:  $|T(j\omega)|_{\text{overall}} = |T(j\omega)|^N$

$$= \frac{|T(j\omega_0)|_{\text{overall}}}{\left[1 + 4Q^2 \left(\frac{\delta\omega}{\omega_0}\right)^2\right]^{N/2}}$$

NOTE  
 $Q = \frac{\omega_0}{B} \sqrt{2^N - 1}$

$$= \frac{|T(j\omega_0)|_{\text{overall}}}{\left(1 + 4 \frac{\omega_0^2}{B^2} (2^N - 1) \left(\frac{\delta\omega}{\omega_0}\right)^2\right)^{N/2}}$$

$$= \frac{|T(j\omega_0)|_{\text{overall}}}{\left[1 + 4 (2^N - 1) \left(\frac{\delta\omega}{B}\right)^2\right]^{N/2}}$$

Part (c) (i)

for bandwidth = 2B, i.e.  $\delta\omega = \pm B$

$$\text{Att} = -20 \log \left(1 + 4 (2^N - 1) (1)\right)^{N/2}$$

$$= -10N \log (1 + 2^{2+N} - 4)$$

$$= 10N \log (2^{2+N} - 3)$$

N =	1	2	3	4	5
Att (dB)	6.70	8.44	9.28	9.79	10.13

Part (c) (ii)

3dB bandwidth  $\delta\omega = \pm B/2$

30dB bandwidth  $\frac{\delta\omega}{B} = x$

$$-30 = -20 \frac{N}{2} \log (1 + 4 (2^N - 1) x^2)$$

$$3 = N \log (1 + 4 (2^N - 1) x^2)$$

$$x = \left[ \frac{10^{3/N} - 1}{4(2^N - 1)} \right]^{1/2}$$

Ratio of 30dB to 3dB

$$\text{BW} = \frac{2Bx}{B} = 2x$$

N =	1	2	3	4	5
Ratio =	31.6	8.6	5.7		4.5

12.78

See fig 12.48 and Eq 12.115 and 12.116

(a) For the narrowband approximation, variation of  $\Omega$  around 0 is equivalent to  $\delta\omega$  around  $\omega_0$ .

Thus, a low-pass maximally flat filter of bandwidth B/2 and order  $\frac{N-1}{2}$  N for which  $|T| = \left[ \left(1 + \frac{\Omega^2}{(B/2)^2}\right)^{\frac{N-1}{2}} \right]^{-1}$

is transformed to a band-pass maximally flat filter of bandwidth B/2 and order 2N, and centre frequency  $\omega_0$ , for which:

$$|T| = \left(1 + \left(\frac{\delta\omega}{B/2}\right)^{2N}\right)^{-1/2}$$

(b) For bandwidth 2B,  $\delta\omega = B$  &

$$|T| = \left(1 + \left(\frac{B}{B/2}\right)^{2N}\right)^{-1/2}$$

$$= \left(1 + 2^{2N}\right)^{-1/2} \quad \text{thus:}$$

N	1	2	3	4	5
T	0.447	0.242	0.124	0.062	0.031
IT/dB	-6.99	-12.3	-18.1	-24.1	-30.1

For 30 dB bandwidth,  
 $-30 = 20 \log x \Rightarrow x = 10^{-3/2}$   
 $= \frac{1}{31.6}$

$\therefore 1 + \left(\frac{\delta' \omega}{B/2}\right)^{2N} = (31.6)^2$

$\left(\frac{\delta' \omega}{B/2}\right)^{2N} = 999 - 1 = 998$

Now the ratio of 30dB to 3dB bandwidths is

ratio =  $\frac{2\delta' \omega}{B} = \frac{\delta' \omega}{B/2} = 998^{\frac{1}{2N}}$

N	1	2	3	4	5
ratio	31.6	5.62	3.16	2.37	1.99

12.79

$A_{max} = 3dB \Rightarrow \epsilon = \sqrt{10^{A_{max}/10} - 1} \approx 1$

Poles of lowpass prototype are given by FIG 12.10(c)

Poles:  $-\omega_p, \omega_p \left(-\frac{1}{2} \pm j\frac{\sqrt{3}}{2}\right)$

Make  $\omega_p = B/2$

$\Rightarrow$  poles:  $\left\{-\frac{B}{2}, +\frac{B}{2}\left(-\frac{1}{2} \pm j\frac{\sqrt{3}}{2}\right)\right\}$

Using the low-pass to bandpass transformation:

Poles of the bandpass filter:

$-\frac{B}{2} \pm j\omega_0,$

$-\frac{B}{4} \pm j\left(\frac{\sqrt{3}}{4}B + \omega_0\right)$  and

$-\frac{B}{4} \pm j\left(\frac{\sqrt{3}}{4}B - \omega_0\right)$

For the three circuits:

①  $\omega_{01} = \omega_0, B_1 = B, Q_1 = \omega_0/B$

②  $\omega_{02} \cong \frac{\sqrt{3}}{4}B + \omega_0, B_2 = \frac{B}{2}, Q_2 \cong \frac{2\omega_0}{B}$

③  $\omega_{03} \cong \frac{\sqrt{3}}{4}B - \omega_0, B_3 = \frac{B}{2}, Q_3 \cong \frac{2\omega_0}{B}$

