

NAME: KEY

EXAM

EXAM 1 EQUATION SHEET

CHAPTER 15

$$|\vec{F}_e| = k_e \frac{|q_1 q_2|}{r^2} \quad \vec{F}_e = q \vec{E} \quad \vec{F}_{NET} = \vec{F}_1 + \vec{F}_2 + \dots$$

$$|\vec{E}| = k_e \frac{|q|}{r^2} \quad \vec{E}_{NET} = \vec{E}_1 + \vec{E}_2 + \dots \quad k_e = 8.99 \times 10^9 \frac{\text{Nm}^2}{\text{C}^2}$$

CHAPTER 16

$$W = \Delta KE \quad W = -\Delta PE \quad W = qE_x \Delta x \quad \Delta PE = q \Delta V \quad \Delta V = -E_x \Delta x$$

$$V = k_e \frac{q}{r} \quad PE = k_e \frac{q_1 q_2}{r} \quad C = \frac{Q}{\Delta V} = \epsilon_0 \frac{A}{d} \quad \epsilon_0 = 8.85 \times 10^{-12} \frac{\text{C}^2}{\text{Nm}^2}$$

$$\text{ENERGY STORED} = \frac{1}{2} Q \Delta V = \frac{1}{2} C (\Delta V)^2 = \frac{Q^2}{2C}$$

$$C_{NET} = C_1 + C_2 + \dots \text{ (PARALLEL)} \quad \frac{1}{C_{NET}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots \text{ (SERIES)}$$

CHAPTER 17

$$I = \frac{\Delta Q}{\Delta t} \quad \Delta V = IR \quad R = \rho \frac{l}{A} \quad R = R_0 [1 + \alpha (T - T_0)]$$

$$P = I \Delta V = I^2 R = \frac{(\Delta V)^2}{R} \quad \rho = \rho_0 [1 + \alpha (T - T_0)]$$

CHAPTER 18

$$\Delta V = \mathcal{E} - IR$$

$$R_{NET} = R_1 + R_2 + \dots \text{ (SERIES)}$$

$$\frac{1}{R_{NET}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots \text{ (PARALLEL)}$$

$$\tau = R_{NET} C$$

$$q = Q_{MAX} (1 - e^{-t/\tau}) \text{ [CHARGING]}$$

$$q = Q_{MAX} e^{-t/\tau} \text{ [DISCHARGING]}$$

OTHERS

$$\sum F = ma$$

$$1 \text{ W} = 1 \text{ J/s}$$

$$F_g = mg$$

$$1 \Omega = 1 \text{ V/A}$$

$$|e| = 1.6 \times 10^{-19} \text{ C}$$

$$1 \text{ V} = 1 \text{ J/C}$$

$$1 \text{ F} = 1 \text{ C/V}$$

$$1 \text{ A} = 1 \text{ C/s}$$

$$1 \text{ J} = 1 \text{ N} \cdot \text{m}$$

$$A = \pi \frac{d^2}{4} = \pi r^2$$

$$ax^2 + bx + c = 0 \Rightarrow x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$


[1] A special toaster rated at 900 W operates on a 120-V household circuit and a 3.5 m length of platinum wire as its heating element. The operating temperature of this element is 240°C. What is the cross-sectional area of the wire? Use platinum's values of $\rho_0 = 11 \times 10^{-8} \Omega \text{m}$ and $\alpha = 3.92 \times 10^{-3} \text{ } 1/^\circ\text{C}$.

$$P = \frac{(\Delta V)^2}{R} \implies R = \frac{(\Delta V)^2}{P} = \frac{(120 \text{ V})^2}{900 \text{ W}} = 16 \Omega$$


$$R = \rho \frac{l}{A} \implies A = \frac{\rho l}{R} = \frac{\rho_0 [1 + \alpha (T - T_0)] l}{R}$$

$$A = \frac{(11 \times 10^{-8} \Omega \text{m}) [1 + (3.92 \times 10^{-3} \text{ } 1/^\circ\text{C}) (240^\circ\text{C} - 20^\circ\text{C})] (3.5 \text{ m})}{16 \Omega}$$

$$A = \frac{(11 \times 10^{-8} \Omega \text{m}) [1 + 0.862] (3.5 \text{ m})}{16 \Omega}$$

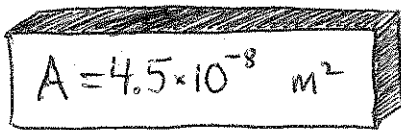
$$A = 4.5 \times 10^{-8} \text{ m}^2$$

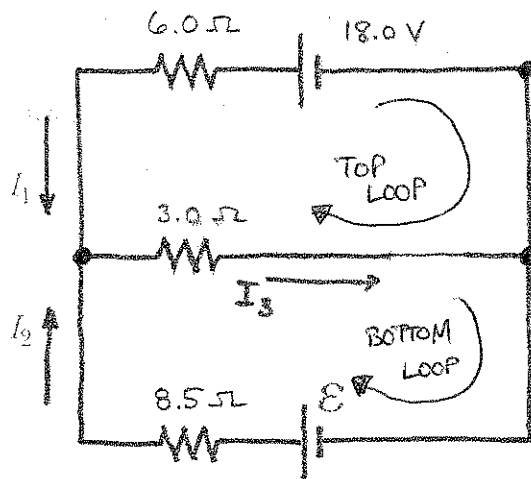[2] If $I_3 = 3.5 \text{ A}$, then find I_1 , I_2 , and \mathcal{E} .



• TOP LOOP, STARTING CLOCKWISE FROM THE TOP RIGHT CORNER:

$$+\Delta V_{3\Omega} + \Delta V_{6\Omega} - 18 \text{ V} = 0$$

$$I_3 R_{3\Omega} + I_1 R_{6\Omega} - 18 \text{ V} = 0$$

$$(3.5 \text{ A})(3\Omega) + I_1(6\Omega) - 18 \text{ V} = 0$$

$$I_1 = \frac{18 \text{ V} - 10.5 \text{ V}}{6\Omega} = 1.25 \text{ A} = I_1$$

• JUNCTION RULE AT LEFT JUNCTION:

$$I_1 + I_2 = I_3 \Rightarrow I_2 = I_3 - I_1 = 3.5 \text{ A} - 1.25 \text{ A} = 2.25 \text{ A} = I_2$$

• BOTTOM LOOP, STARTING CLOCKWISE FROM THE MIDDLE RIGHT JUNCTION:


$$+\mathcal{E} - \Delta V_{8.5\Omega} - \Delta V_{3\Omega} = 0$$

$$+\mathcal{E} - I_2 R_{8.5\Omega} - I_3 R_{3\Omega} = 0$$

$$+\mathcal{E} - (2.25 \text{ A})(8.5\Omega) - (3.5 \text{ A})(3\Omega) = 0$$

$$\mathcal{E} = 19.1 \text{ V} + 10.5 \text{ V} = 29.6 \text{ V} = \mathcal{E}$$

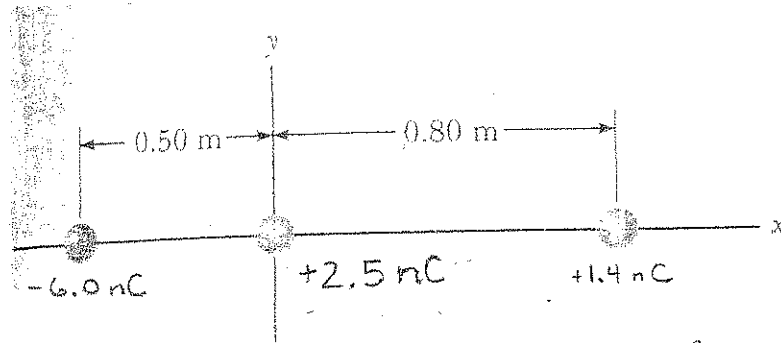[3] Three point charges are aligned along the x-axis as shown. Find the electric field when $x=+3.5\text{m}$ and $y=0$.



$$E_1 = k_e \frac{|q_1|}{r_1^2} = \left(8.99 \times 10^9 \frac{\text{Nm}^2}{\text{C}^2}\right) \frac{|-6.0 \times 10^{-9} \text{C}|}{(4.0 \text{m})^2} = \ominus 3.37 \frac{\text{N}}{\text{C}}$$

$$E_2 = k_e \frac{|q_2|}{r_2^2} = \left(8.99 \times 10^9 \frac{\text{Nm}^2}{\text{C}^2}\right) \frac{|+2.5 \times 10^{-9} \text{C}|}{(3.5 \text{m})^2} = \oplus 1.83 \frac{\text{N}}{\text{C}}$$

$$E_3 = k_e \frac{|q_3|}{r_3^2} = \left(8.99 \times 10^9 \frac{\text{Nm}^2}{\text{C}^2}\right) \frac{|+1.4 \times 10^{-9} \text{C}|}{(2.7 \text{m})^2} = \oplus 1.73 \frac{\text{N}}{\text{C}}$$

$$E_{\text{NET}} = E_1 + E_2 + E_3 = -3.37 \frac{\text{N}}{\text{C}} + 1.83 \frac{\text{N}}{\text{C}} + 1.73 \frac{\text{N}}{\text{C}}$$


$$E_{\text{NET}} = +0.19 \frac{\text{N}}{\text{C}}$$

[4] Two capacitors, $C_1=16\ \mu\text{F}$ and $C_2=24\ \mu\text{F}$, are connected in series, and a 9-V battery is connected across them.

(a) Find the net capacitance and the total energy stored.

$$\frac{1}{C_{\text{NET}}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{16\ \mu\text{F}} + \frac{1}{24\ \mu\text{F}} = \frac{5}{48\ \mu\text{F}}$$

$$C_{\text{NET}} = 9.6\ \mu\text{F}$$

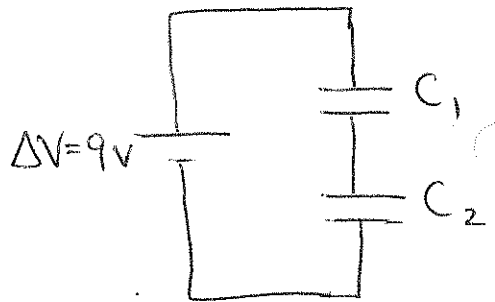

$$\text{ENERGY STORED} = \frac{1}{2} C_{\text{NET}} (\Delta V)^2 = \left(\frac{1}{2}\right)(9.6 \times 10^{-6}\ \text{F})(9\ \text{V})^2 = 3.89 \times 10^{-4}\ \text{J} = E$$


(b) If the same capacitors are connected in parallel, what potential difference would be required across the so that the combination stores the same amount of energy as in part (a)?

$$C_{\text{NET}} = C_1 + C_2 = 16\ \mu\text{F} + 24\ \mu\text{F} = 40\ \mu\text{F}$$

$$E = \frac{1}{2} C_{\text{NET}} (\Delta V)^2$$

$$\Delta V = \sqrt{\frac{2E}{C_{\text{NET}}}} = \sqrt{\frac{(2)(3.89 \times 10^{-4}\ \text{J})}{40 \times 10^{-6}\ \text{F}}}$$

$$\Delta V = 4.41\ \text{V}$$

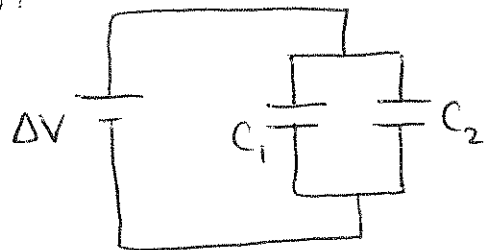

(c) In this new parallel circuit, what is the total energy stored in each capacitor?

$$E = \frac{1}{2} C (\Delta V)^2$$

$$E_{16} = \left(\frac{1}{2}\right)(16 \times 10^{-6}\ \text{F})(4.41\ \text{V})^2 = 1.56 \times 10^{-4}\ \text{J} = E_{16}$$

$$E_{24} = \left(\frac{1}{2}\right)(24 \times 10^{-6}\ \text{F})(4.41\ \text{V})^2 = 2.33 \times 10^{-4}\ \text{J} = E_{24}$$

[5] An uncharged capacitor, $C = 30 \mu\text{F}$, is connected in series to two resistors, $R_1 = 50 \Omega$ and $R_2 = 20 \Omega$, that are connected in parallel as shown.


(a) If this combination is connected to a battery with a terminal voltage of 11.5 V and an internal resistance of $r = 4 \Omega$, then what is the net resistance of the circuit?

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{50 \Omega} + \frac{1}{20 \Omega} = \frac{7}{100 \Omega}$$

$$R_p = 14.3 \Omega$$

$$R_{\text{NET}} = R_p + r = 14.3 \Omega + 4 \Omega$$

$$R_{\text{NET}} = 18.3 \Omega$$

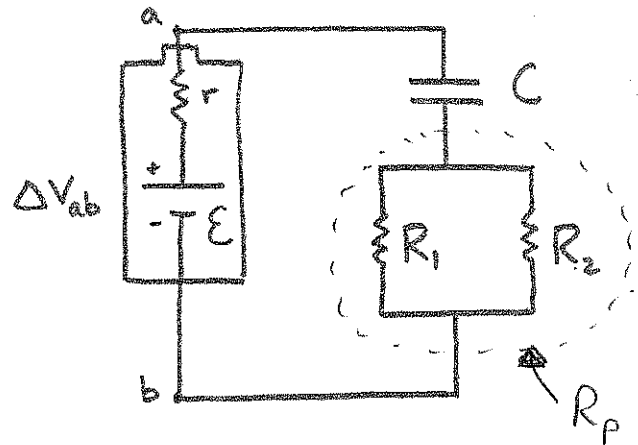

(b) What is the time constant of the circuit?

$$\tau = R_{\text{NET}} C = (18.3 \Omega) (30 \times 10^{-6} \text{ F}) = 5.5 \times 10^{-4} \text{ s} = \tau$$

(c) What is the EMF of the battery?

$$\Delta V = \mathcal{E} - I r \Rightarrow \mathcal{E} = \Delta V + I r$$

$$\Delta V = I R_p \Rightarrow I = \frac{\Delta V}{R_p}$$

$$\therefore \mathcal{E} = \Delta V + \frac{\Delta V}{R_p} \cdot r = 11.5 \text{ V} + \frac{11.5 \text{ V}}{14.3 \Omega} \cdot 4 \Omega = 11.5 \text{ V} + 3.2 \text{ V}$$

$$\mathcal{E} = 14.7 \text{ V}$$

1	2	3	4	5	TOTAL

