
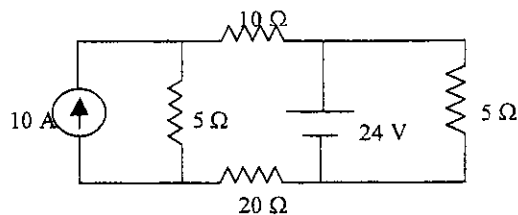


Physics 228
Home Work Chapter II

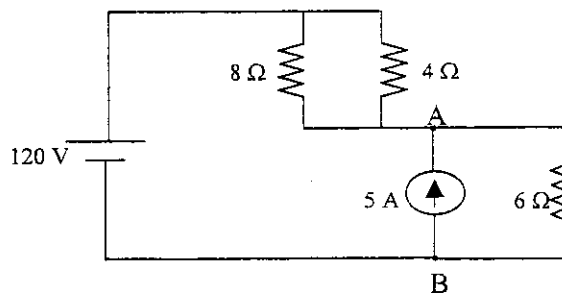
I. Use the superposition to find the current through the 10-Ω resistor.




II. Find the thevenin's equivalent between A and B.



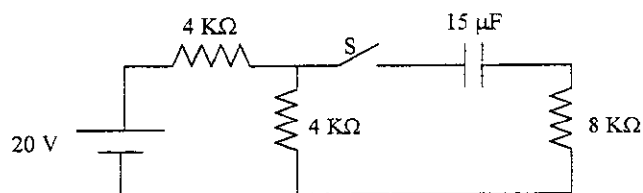III. Find the expression for the current in the 8 kW resistor following the closure of the switch.




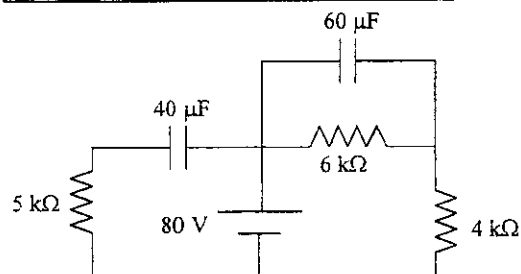IV. Find the voltage across each resistor after the system has reached equilibrium.



V. Capacitor C is charged by closing switch S_1 . After equilibrium is reached, switch S_2 is closed.

- Just before closing S_2 , what is the voltage across C.
- Just after closing S_2 , what is the voltage across C? and the current in the inductor and R_2 ?
- Long after S_2 is closed and equilibrium is reached what are the values of V_C , I_L , and I_2 ?

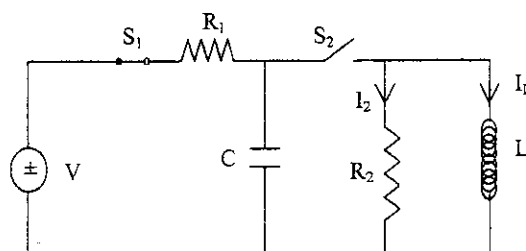


Physics 228
Solution SET II.


S-II 1

N51) Superposition principle

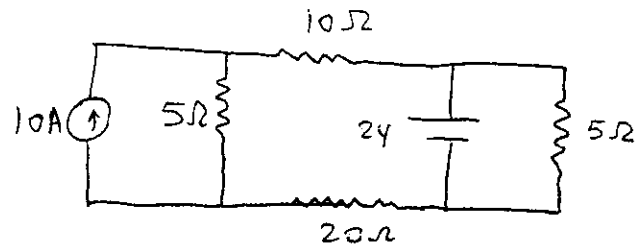Let us first short circuit the voltage source;



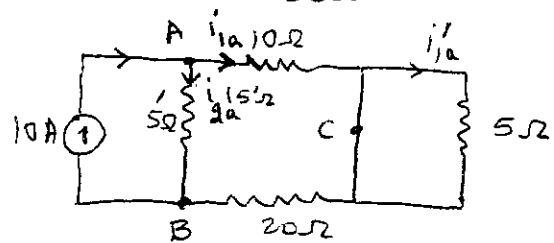Note that No Current will pass through the 5Ω resistor.



$$\Rightarrow i'_{1a}(5\Omega) = 0$$

$$i'_{2a}(5\Omega) = ??$$

Note that $10 = i'_{1a}(10\Omega) + i'_{2a}(5\Omega)$

$$(V_A - V_B) + (V_B - V_C) + (V_C - V_A) = 0 \Rightarrow 5i'_{2a} - 20i'_{1a} - 10i'_{1a} = 0$$

$$\Rightarrow 5i'_{2a} - 30i'_{1a} = 0 \Rightarrow$$

$$5i'_{2a} - 30(10 - i'_{2a}) = 0 \Rightarrow 35i'_{2a} = 300$$

$$\Rightarrow i'_{2a} = \frac{300}{35} = 8.57 \text{ A}$$

$$\Rightarrow i'_{1a} = 1.428 \text{ A}$$

then open circuit the current source

$$i_{2b} = \frac{24 \times 5}{45} = 4.8 \text{ A}$$

$$i_{2b} = \frac{45}{5} = 9 \text{ A} \text{ clockwise}$$

$$i_{1b} = \frac{24 \times 35}{45} = 0.68 \text{ A counter-clockwise}$$

$$i_{1b} = \frac{45}{35} = 1.29 \text{ A counter-clockwise}$$



$$i(5\Omega) = 9 \text{ A clockwise}$$

$$i(10\Omega) = 1.428 - 1.29 = 0.138 \text{ A clockwise}$$

$$1.428 - 0.68 = 0.748 \text{ A}$$

$$i(5\Omega)' = -8.57 - 1.29 = -9.86 \text{ A counter}$$
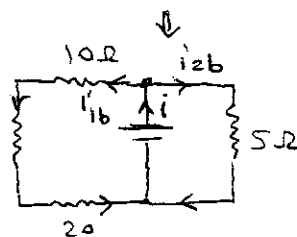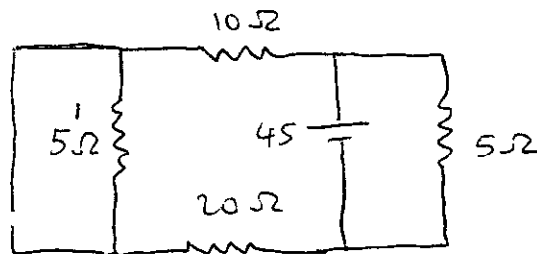
$$-8.57 - 0.68 = -9.25 \text{ A clockwise}$$



N32)

KC Law

$$120 - (6 + \frac{8}{3}) I - 30 = 0$$




$$I = \frac{3 \times 90}{26}$$

$$\Rightarrow V_{Th} = V_A - V_B = 30 + 6 \times \frac{3 \times 90}{26} = 92.3V$$

$$V_{Th} = 92.3V$$

$$R_{Th} = (\frac{8}{3}) \parallel (6\Omega)$$

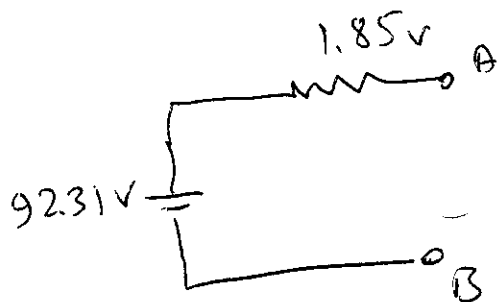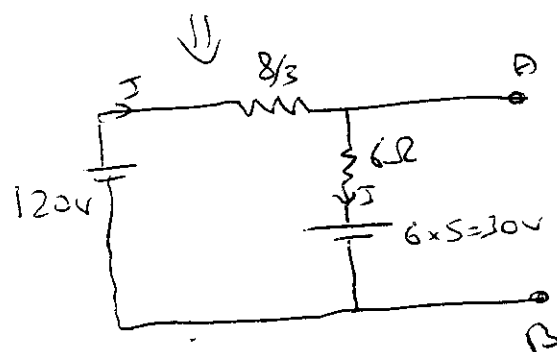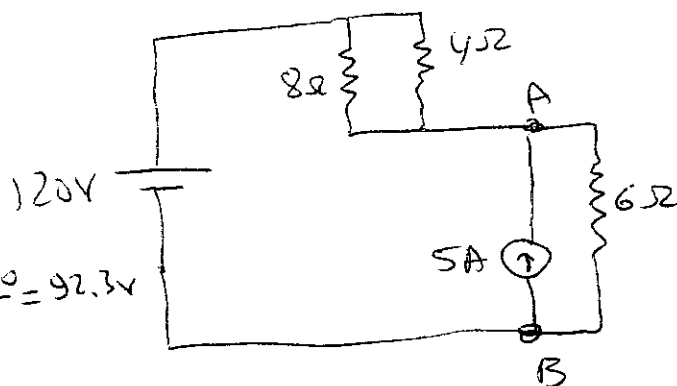
$$\Rightarrow R_{Th} = \frac{24}{13} = 1.85\Omega$$



SET II solution


N33)

Let us use the
Thevenin theorem.

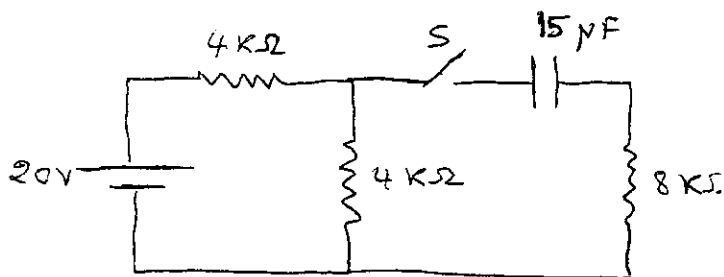



$$V_{Th} = 4 \times \frac{20}{8} = 10V$$
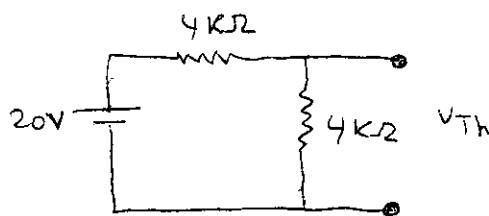
$$R_{Th} = \frac{4 \times 4}{4 + 4} = \frac{16}{8} = 2k\Omega$$



The new circuit will be \Rightarrow

R_{Th} and $8k\Omega$ are in
series. So,

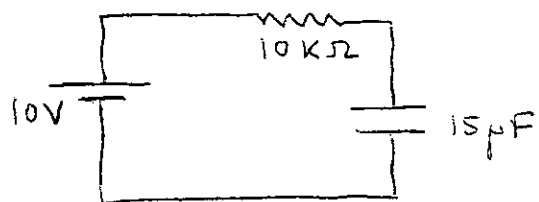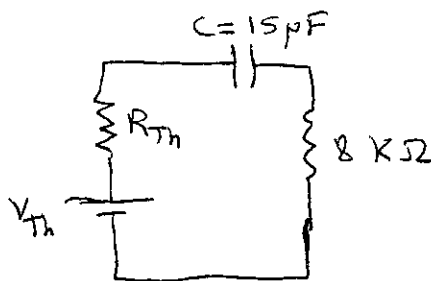

The value of $RC = 10 \times 10^3 \times 15 \times 10^{-6}$



$$RC = 0.15 \text{ seconds.}$$

We know that current will flow to charge C.

$$i(t) = \frac{V_{Th}}{R} e^{-\frac{t}{RC}} = \frac{10}{10 \times 10^3} \cdot e^{-\frac{t}{0.15}} = (1mA) e^{-\frac{t}{0.15}}$$

t is the time in seconds.

Remember that:

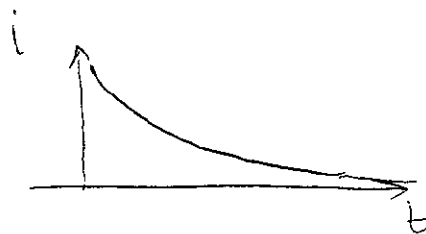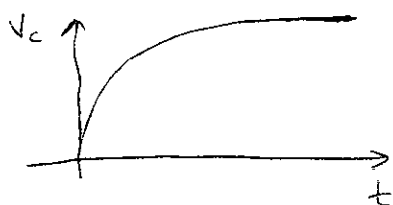


physics 228
Solution Set II.

SII - 4

Ns4)

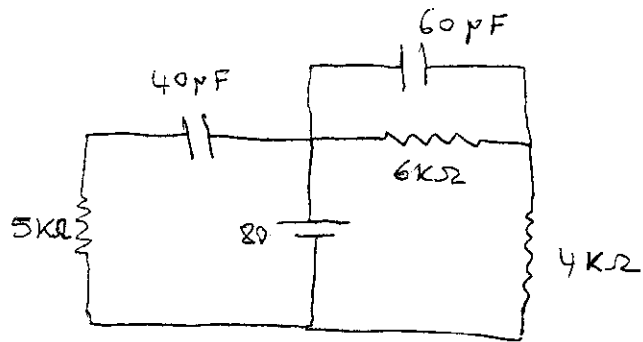When Equilibrium
is reached \Rightarrow
No current from $40\mu\text{F}$
and No current $60\mu\text{F}$.



~~V~~ $V_{\text{Across } 4\text{k}\Omega} = 4 \times \frac{80 \times 10^3}{10 \times 10^3}$

$$V_{\text{Across } 4\text{k}\Omega} = 32\text{V}$$

$$V_{\text{Across } 6\text{k}\Omega} = \frac{6 \times 10^3 \times 80}{10 \times 10^3} = 48\text{V}$$

After Equilibrium is reached,

The voltage Across the $40\mu\text{F}$ capacitor is 80V .


The voltage Across the $60\mu\text{F}$ capacitor is 48V .

\downarrow
Cuz it's with $60\mu\text{F}$

Solution SET II.


5)

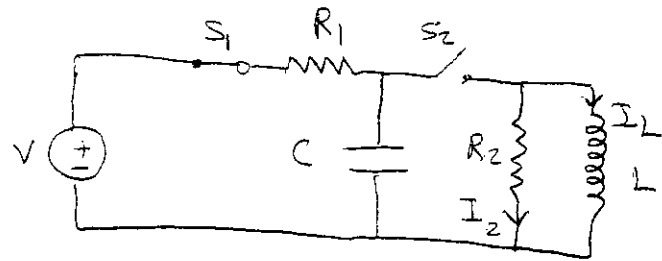a) After closing s_1 , the capacitor C will start charging, until Equilibrium is reached where $V_C = V$




b) Just after closing s_2 ; $V_C = V$, $I_L = 0$, $I_{R_2} = \frac{V}{R_2}$

c) Use of Thevenin's.

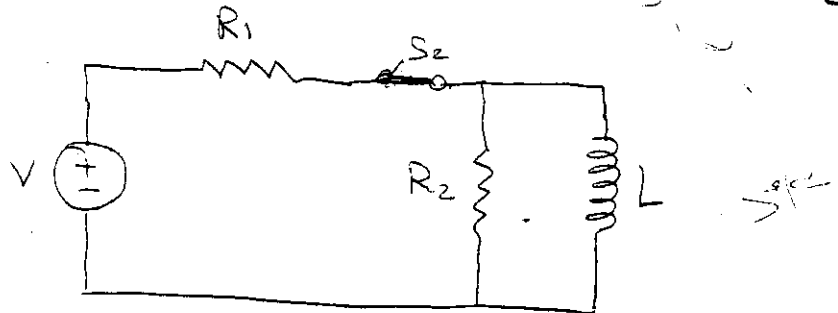


$$V_{Th} = \frac{R_2}{R_1 + R_2} \cdot V$$

$$R_{Th} = \frac{R_1 R_2}{R_1 + R_2}$$

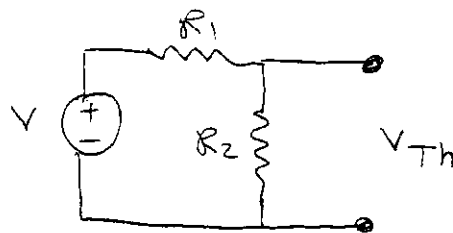

⇒

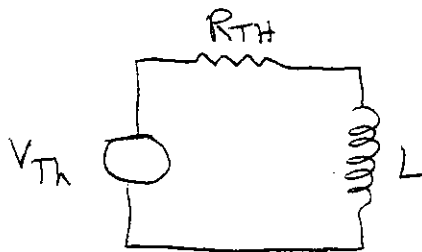

We know that

$$i_L(t) = \frac{V_{Th}}{R_{Th}} \left(1 - e^{-\frac{t R_{Th}}{L}} \right)$$

$$\Rightarrow i_L(t) = \frac{R_2 V}{R_1 + R_2} \times \frac{R_1 + R_2}{R_1 R_2} \left(1 - e^{-\frac{t R_{Th}}{L}} \right)$$

$$i_L(t) = \frac{V}{R_1} \left(1 - e^{-\frac{t R_{Th}}{L}} \right)$$

$$i_2 = 0$$

$$\left\{ \begin{array}{l} \text{at } t=0 \Rightarrow i = 0 \\ t \rightarrow \infty \Rightarrow \frac{V}{R_1} = I_L \end{array} \right.$$