
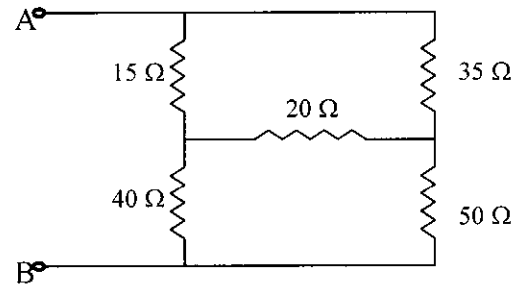


Physics 228  
Home Work Chapter I

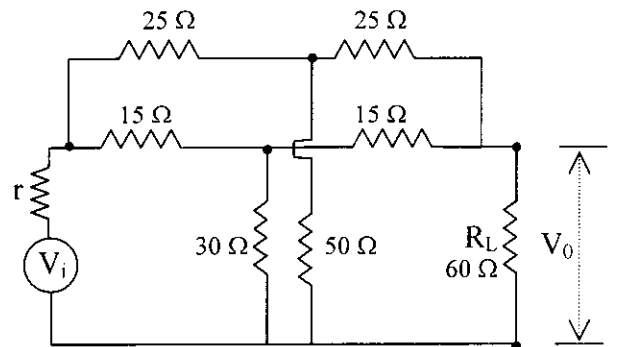
I. Determine the resistance between A and B.




II. The Twin-T circuit is inserted between the power supply with internal resistance  $r = 60\Omega$ . Determine the insertion loss ( $V_0/V_i$ ).



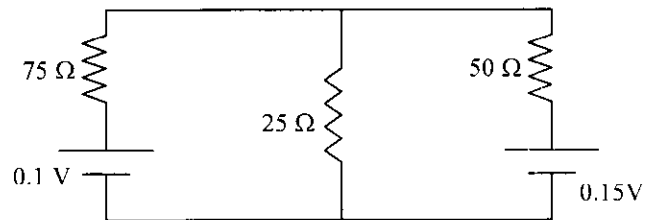
III. Determine the current in each resistor. Calculate the current in the  $25\Omega$  resistor using the principle of superposition.



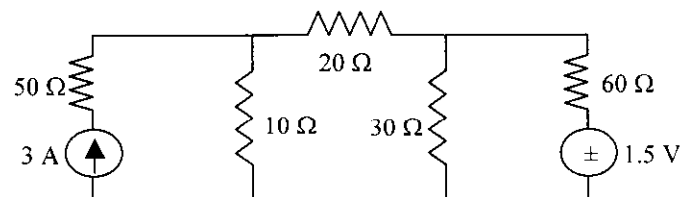IV. Determine the power delivered by each source.





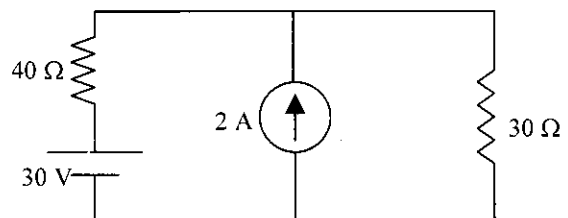V. Determine the power delivered by each source.



Physics 228,  
Solution Set - I.

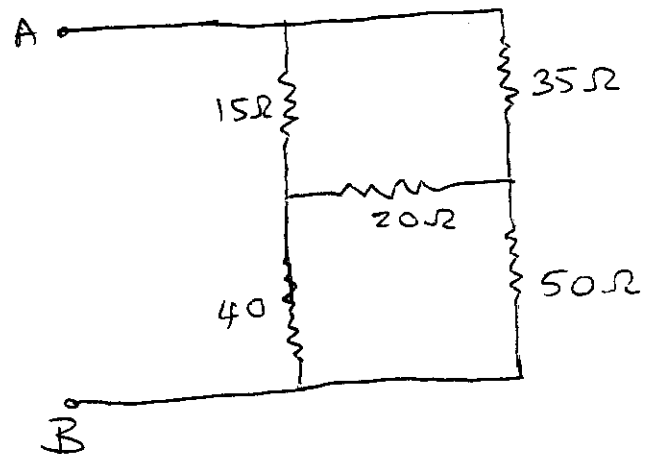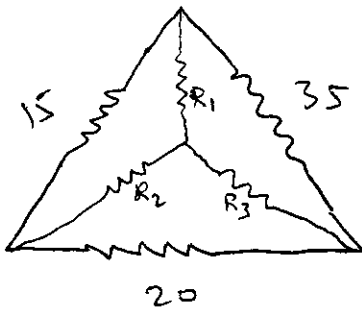I Convert the triangle formed by  $(15, 20, 35) \Omega$  into a star.



$$R_1 = \frac{15 \times 35}{15 + 35 + 20} = \frac{15 \times 35}{70} = 7.5 \Omega$$

$$R_2 = \frac{15 \times 20}{70} = \dots = 4.28 \Omega$$

$$R_3 = \frac{20 \times 35}{70} = \dots = 10 \Omega$$

The circuit becomes as follow:


10 in serie with 50 = 60

4.28 in serie with 40 = 44.28

60 // 44.28  $\Rightarrow$  25.47  $\Omega$

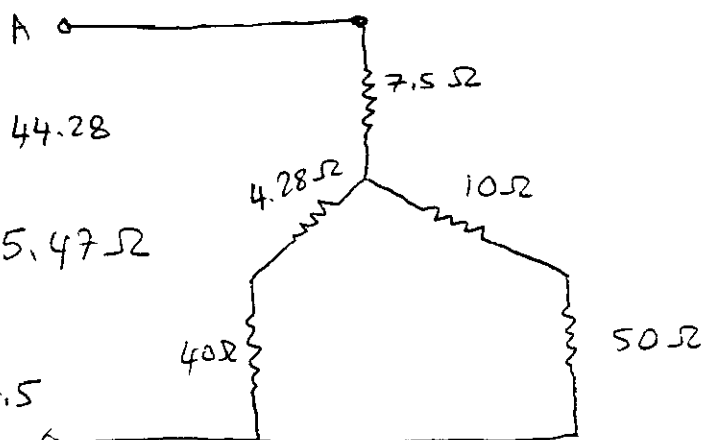25.47 in serie with 7.5

$$\Rightarrow R_{AB} = 25.47 + 7.5 = 33 \Omega$$



## SET I

II - Determine the ratio

$$\left(\frac{V_o}{V_i}\right) = ??$$

Replace the star "Y"  
formed by the  $(30, 15, 15)\Omega$   
resistors by a triangle.

$$R_1 = \frac{15 \times 15 + 15 \times 30 + 15 \times 30}{30} = 37.5 \Omega$$

$$R_2 = \frac{15 \times 15 + 15 \times 30 + 15 \times 30}{15} = 75 \Omega$$

$$R_3 = \frac{15 \times 15 + 15 \times 30 + 15 \times 30}{15} = 75 \Omega$$





Now convert the star "Y"  
formed by the  $(50, 25, 25)$  into a triangle

$$R'_1 = \frac{25 \times 25 + 25 \times 50 + 25 \times 50}{50} = 62.5 \Omega$$

$$R'_2 = \frac{25 \times 25 + 25 \times 50 + 25 \times 50}{25} = 125 \Omega$$

$$R'_3 = \frac{25 \times 25 + 25 \times 50 + 25 \times 50}{25} = 125 \Omega$$


Now we reconstruct our circuit:

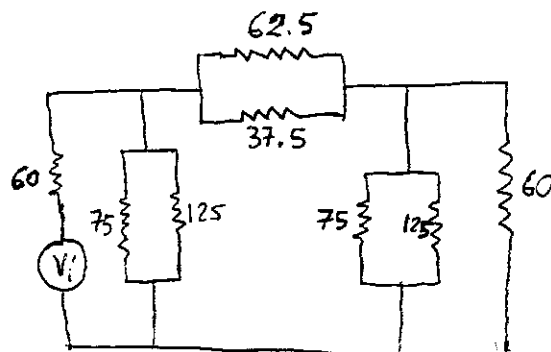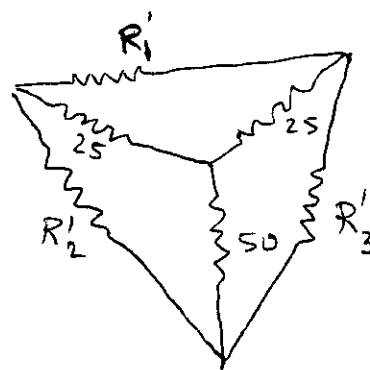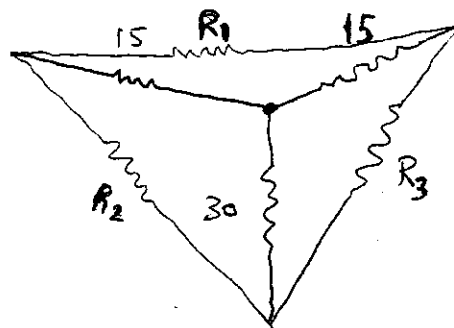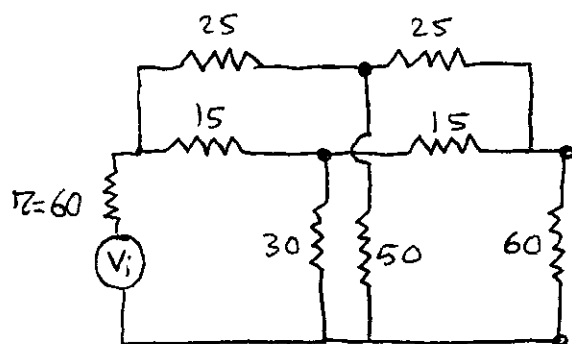

SET I.

One can easily see that the  $\left\{ \begin{array}{l} 62.5 \Omega \parallel 37.5 \Omega \\ 75 \Omega \parallel 125 \Omega \\ 75 \Omega \parallel 125 \Omega. \end{array} \right.$

The Equivalent circuit becomes:

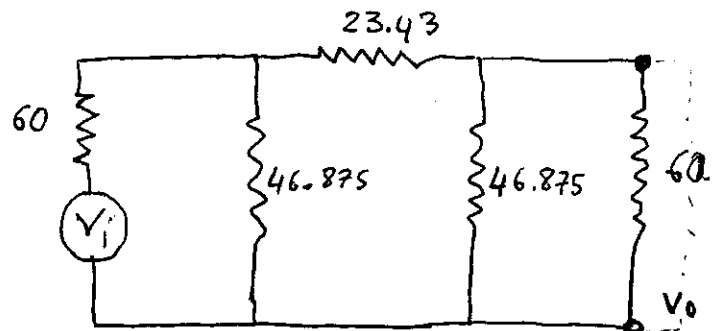


Remember that we need the ratio of  $\left(\frac{V_o}{V_i}\right)$ ; Several methods can lead to this ratio.

I will convert the triangle formed by the  $(46.875, 46.875, 23.43)$  into a star "Y"


$$R_1'' = \frac{23.43 \times 46.875}{46.875 + 46.875 + 23.43} = 9.37$$

$$R_2'' = \frac{23.43 \times 46.875}{46.875 + 46.875 + 23.43} = 9.37$$
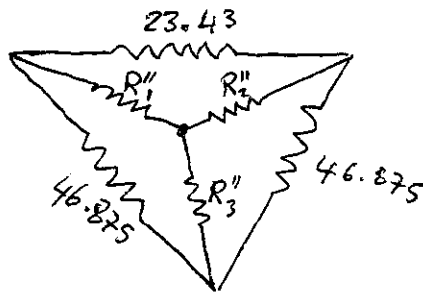
$$R_3'' = \frac{46.875 \times 46.875}{46.875 + 46.875 + 23.43} = 18.75$$




The circuit will become:

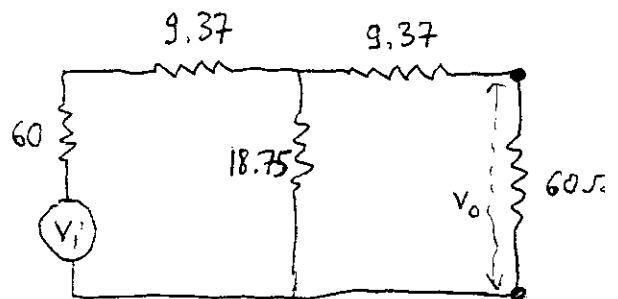

Kirchoff's Law. on the large

Loop:

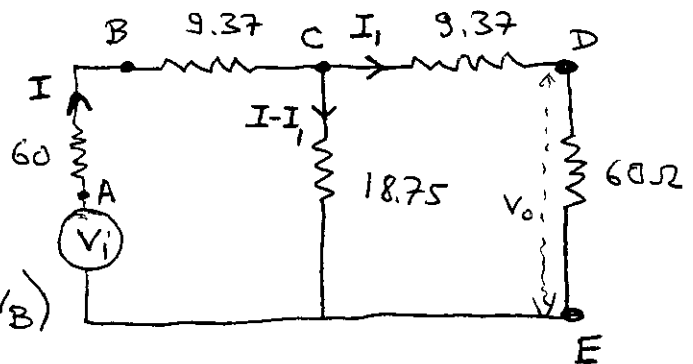

$$(V_A - V_E) + (V_E - V_D) + (V_D - V_C) + (V_C - V_B) + (V_B - V_A) = 0$$

$$V_i - V_o - 9.37 I_1 - 9.37 I - 60 I = 0$$

$$\Rightarrow V_i - V_o - 69.37 I - 9.37 \frac{V_o}{60} = 0 \quad \text{Eq. (B)}$$

The value of  $I$  can be determined as follow:

$$I = \frac{V_i}{R_{Eq}}$$

$60 \Omega$  and  $9.37 \Omega$  in serie  $\Rightarrow 69.37 \Omega$

the  $69.37 \Omega$  in parallel with  $18.75 \Rightarrow \frac{69.37 \times 18.75}{69.37 + 18.75} = 14.7$

the  $14.76$  in serie with  $9.37$  and  $60 \Rightarrow$

$$R_{Eq} = 9.37 + 60 + 14.76 = 84.13 \Omega.$$


$$\Rightarrow I = \frac{V_i}{84.13}$$

$$\text{Eq (B)} \Rightarrow V_i - V_o - V_i \frac{69.37}{84.13} - \frac{9.37}{60} V_o = 0$$

$$\Rightarrow \boxed{\frac{V_o}{V_i} \approx 0.15}$$

SET 1.


III - Superposition principle.

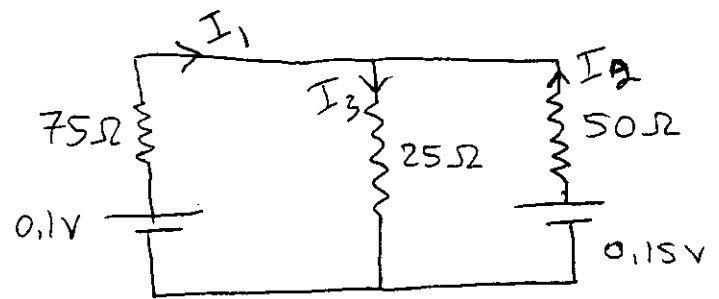

$$I_{1A} = \frac{0.1 \text{ V}}{R_{Eq}}$$

$$R_{Eq} = \frac{50 \times 25}{75} + 75 = \frac{275}{3} \Omega$$

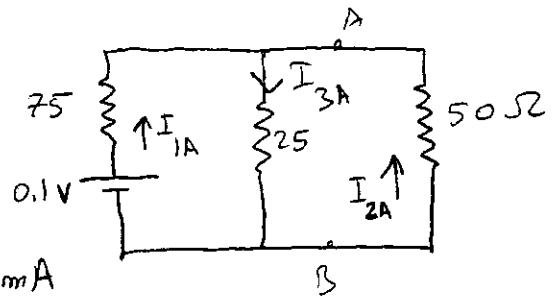
$$\Rightarrow I_{1A} = \frac{0.1 \times 3}{275} = \frac{0.3}{275} \text{ A} = 1.09 \text{ mA}$$



Now 
$$I_{3A} = \frac{0.1 - (0.3 \times 75 / 275)}{25} = \frac{0.1 - 0.9/11}{25} = \frac{0.2}{275} = 0.727 \text{ mA}$$

$$V_A - V_B + V_B - V_A = 0 \Rightarrow 25 I_{3A} + I_{2A} \times 50 = 0 \Rightarrow I_{2A} = -\frac{I_{3A}}{2} = -\frac{0.1}{275} = -0.363 \text{ mA}$$
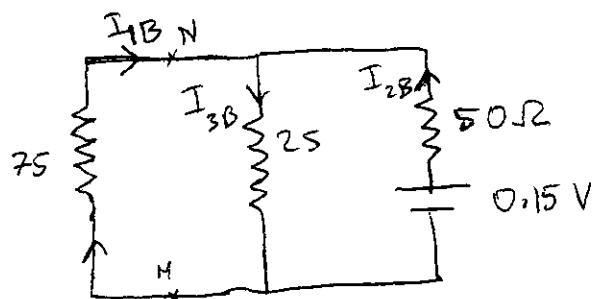
$$\Rightarrow \begin{cases} I_{1A} = \frac{0.3}{275} \\ I_{2A} = -\frac{0.1}{275} \\ I_{3A} = \frac{0.2}{275} \end{cases}$$



$$I_{2B} = \frac{0.15}{\frac{25 \times 75}{100} + 50} = \frac{0.15 \times 4}{275} \Rightarrow I_{2B} = \frac{0.6}{275} \text{ A} = 2.18 \text{ mA}$$

$$I_{3B} = \frac{0.15 - (0.6 \times 50 / 275)}{25} = \frac{0.15 - 1.2/11}{25} = 1.636 \text{ mA}$$


$$I_{1B} = -\frac{25}{75} \times \frac{(0.15 - 1.2/11)}{25} = -\frac{1.65 - 1.2}{11 \times 75} = -\frac{0.45}{11 \times 75} = -0.545 \text{ mA}$$

$$I_{\text{total}} = I_{1A} + I_{1B} = \frac{0.3}{275} + \frac{-0.45}{275} = 0.545 \text{ A}$$

$$\begin{aligned} I_2 &= I_{2A} + I_{2B} = -\frac{0.1}{275} + \frac{0.6}{275} = \frac{0.5}{275} = 1.81 \text{ mA} \\ I_3 &= 2.36 \text{ mA} \end{aligned}$$

III - Another method:

Kirchof's Law:

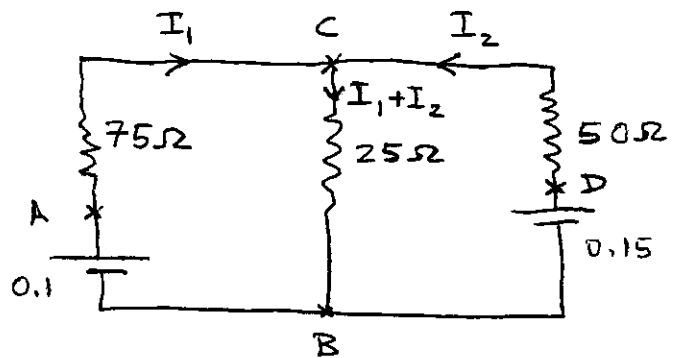

$$(V_A - V_B) + (V_B - V_C) + (V_C - V_A) = 0$$

$$0.1 - 25(I_1 + I_2) - 75I_1 = 0$$

$$(V_D - V_B) + (V_B - V_C) + (V_C - V_D) = 0$$

$$0.15 - 25(I_1 + I_2) - 50I_2 = 0$$

$$\Rightarrow 0.1 - 100I_1 - 25I_2 = 0 \quad (1)$$

$$0.15 - 25I_1 - 75I_2 = 0 \quad (2)$$

$$\text{Eq. (1)} \times -3 \Rightarrow -0.3 + 300I_1 + 75I_2 = 0 \quad (3)$$

$$(3) + (2) \rightarrow -0.15 + 275I_1 = 0 \Rightarrow I_1 = 0.545 \text{ mA}$$


$$(1) \rightarrow 0.1 - 0.0545 - 25I_2 = 0 \Rightarrow I_2 = 1.81 \text{ mA}$$

$$I_3 = I_1 + I_2 = 0.545 + 1.81 = 2.36 \text{ mA} = I_3$$


Physics 228  
Solution SET 1

SI-7

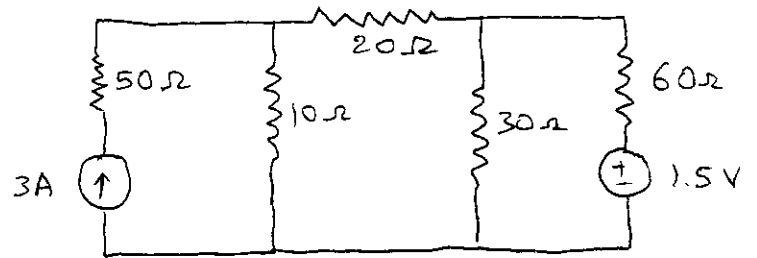IV - Determine the power delivered by each source.



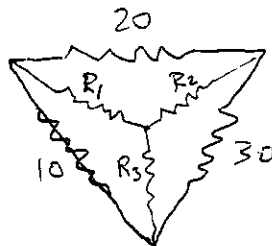First convert the triangle into a star "Y"




$$R_1 = \frac{20 \times 10}{60} = \frac{10}{3} = 3.33 \Omega$$

$$R_2 = \frac{20 \times 30}{60} = 10 \Omega$$


$$R_3 = \frac{10 \times 30}{60} = 5 \Omega$$

The Equivalent circuit

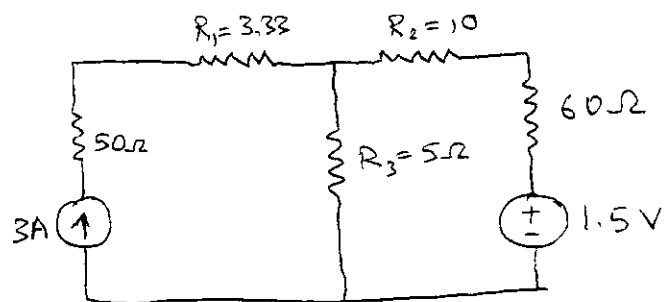

$$I_1 = I_2 + I_3 = 3$$

take the loop formed by (5, 70, 1.5V.)

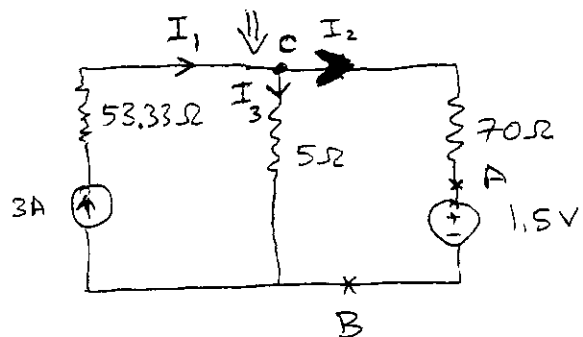

$$V_A - V_B + V_B - V_C + V_C - V_A = 0$$

$$1.5 - 5I_3 + 70I_2 = 0$$

$$I_2 = 3 - I_3$$

$$\Rightarrow 1.5 - 5I_3 + 70(3 - I_3) = 0$$

$$\Rightarrow 1.5 - 75I_3 + 210 = 0 \Rightarrow$$

$$I_3 = \frac{211.5}{75} = 2.82 \text{ A}$$

$$I_2 = 3 - I_3 = 3 - 2.82 = 0.18 \text{ A}$$



## Solution Set I.

IV - Continued.

$$\text{So, } I_1 = 3 \text{ A}$$

$$I_2 = 0.18 \text{ A}$$


$$I_3 = 2.82 \text{ A.}$$

\* the power of the 1.5 V source is  $P = I_2 \times 1.5$

$$\boxed{P = 0.27 \text{ W}} \quad \text{In power}$$

$$* (V_M - V_P) + (V_P - V_N) + (V_N - V_M) = 0$$

$$V_M - V_P - 5I_3 - 53.33 I_1 = 0$$

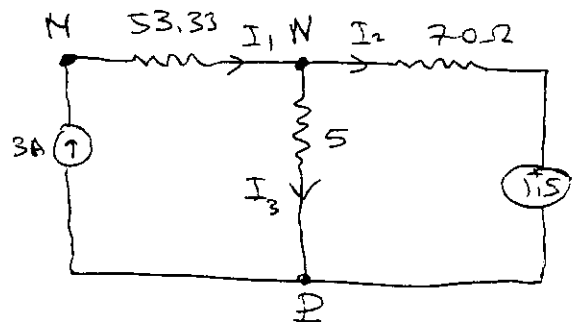

$$\Rightarrow (V_M - V_P) = 5 \times 2.82 + 53.33 \times 3$$

$$= 14.1 + 159.99 = 174 \text{ V}$$

$$\Rightarrow \underset{\text{(3A) source}}{P} = 174 \times 3 = 522.2 \text{ W.}$$

out-power.


please check the conservation of Energy.

Solution SET I.

V.

$$I = I_1 + I_2 = 2 \text{ A}$$
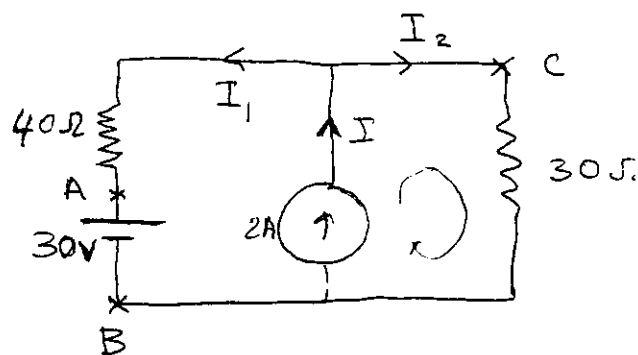
$$(V_A - V_B) + (V_B - V_C) + (V_C - V_A) = 0$$



$$30 - 30I_2 + 40I_1 = 0$$

$$30 - 30(2 - I_1) + 40I_1 = 0 \Rightarrow 30 - 60 + 30I_1 + 40I_1 = 0$$

$$\Rightarrow I_1 = \frac{30}{70} = \frac{3}{7} \text{ A} \Rightarrow I_2 = 2 - \frac{3}{7} = \frac{11}{7} \text{ A}$$

The power of the 30V source is:  $30 \times \frac{3}{7} = 12.86 \text{ W}$   
Absorbed

The power of the (2A) source is:  $30 \times I_2 \times I$   
 $= 30 \times \frac{11}{7} \times 2 = 94.285 \text{ W}$   
delivered

Conservation of Energy:

$$40 \times \frac{9}{49} + 30 \times \frac{121}{49} + 12.86 =$$

$$7.347 + 74.08 + 12.86 = 94.28 \text{ W}$$