

FINAL EXAM
Fall 05-06
Duration 105 minutes

Name : _____

ID: _____


Section: _____

I. (10pts)

In the adjacent figure, given:

$i_a = 3\text{A}$, $i_b = 2\text{A}$ and $i_c = -8\text{A}$, determine

i_1 , i_2 and v .

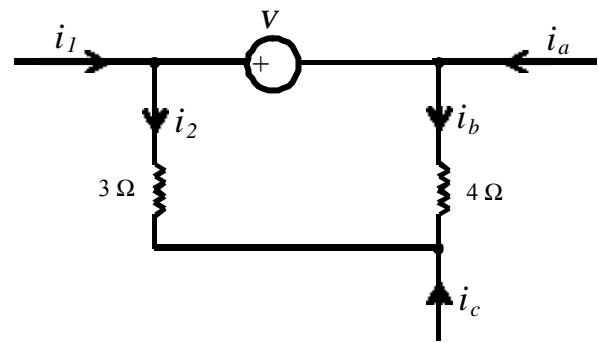

II. (14pts).

Design a regulated power supply using 24 V (rms), center-tapped transformer to supply 10 V at 500 mA, -10 V at 100 mA. What is the minimum current rating of the transformer? (Show your circuit as well as your calculations)

III. (10pts).

a) By use of truth table show that:

$$\overline{A \bullet B} = \overline{A} + \overline{B}$$

$$\overline{A + B} = \overline{A} \bullet \overline{B}$$

b) Draw the circuit for the Boolean expression: $A \bullet B \bullet \overline{C} = \text{OUT}$ using only NOR gates.

IV. (8pts)


Calculate V_o for:

a) $V_i = 1.0 \text{ V}$

b) $V_i = 10 \text{ V}$

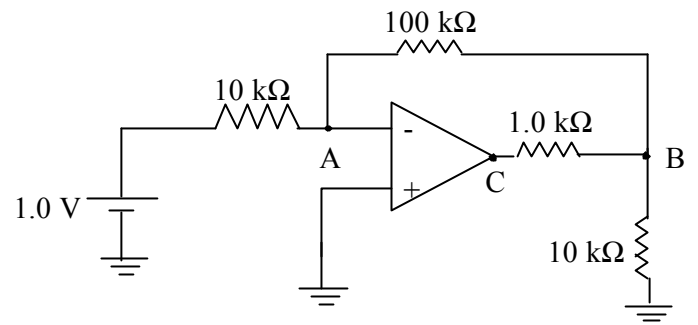V. (12pts)

For the circuit shown, calculate the Voltages at points A, B, and C.



VI. (10pts)

In the adjacent circuit $V_i = V_p \cos(\omega t)$,

At what frequency is the
attenuation 10 db.


VII. (10pts)

Write the Logic relations necessary for comparing two 2-bit binary numbers and indicating with $OUT = 1$ if $A < B$. The case $A \geq B$ should give $OUT = 0$. Design the logic circuit.

VIII. (14pts)

In the adjacent circuit check which of the diodes will be open and determine the current in each branch.

N. B. The diodes are made of Silicon.

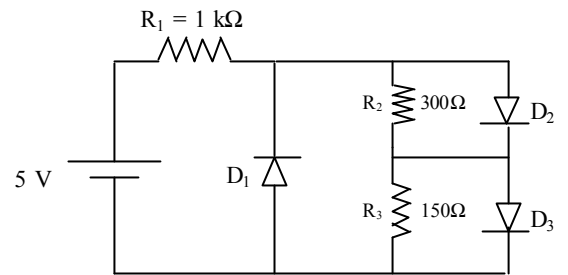

IX. (12 pts)

- a) In the adjacent circuit find the current flowing through the capacitor 0.3 s after the closure of the switch.
- b) what is the voltage across the capacitor long after the switch is closed?