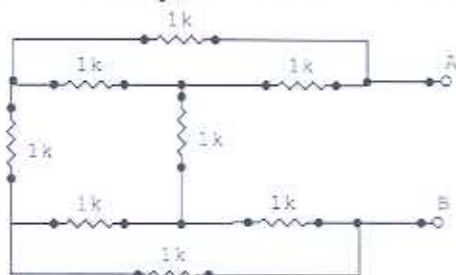



## Physics 228 – Quiz#1 November 2007

All resistances are in Ohms and all voltages are RMS.


1. Find the equivalent resistance between A and B



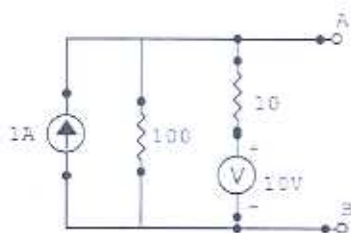
2. Find the Thevenin's equivalent between A and B.





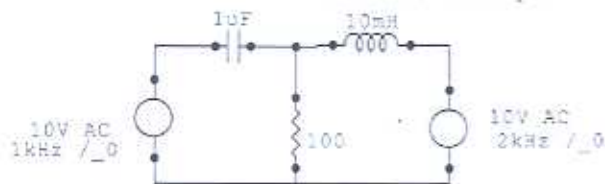
3. Find the current in the resistor and the power delivered to it.



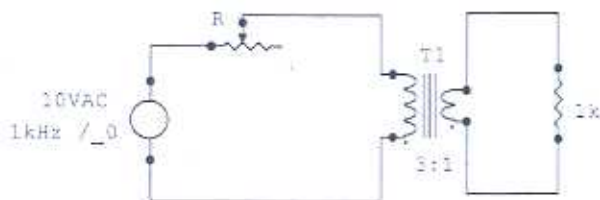4. The resistor in the primary is variable. Find the value of R so that the power delivered to the 1k Ohm load is maximum. In this case, find the power delivered to the load.



# Quiz I

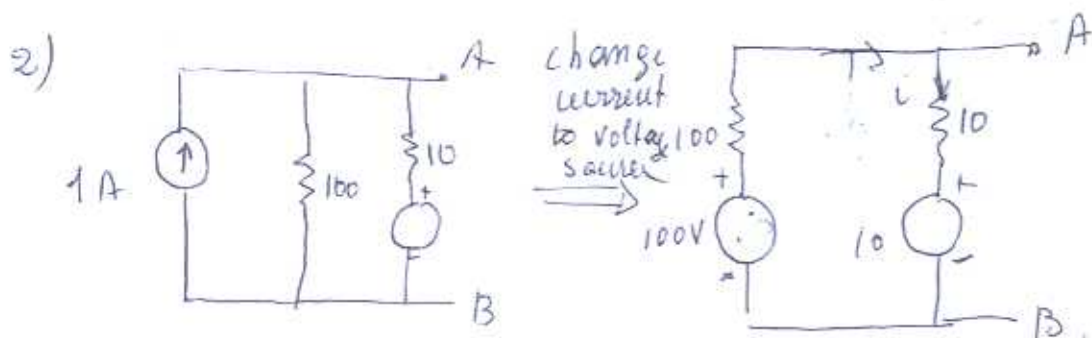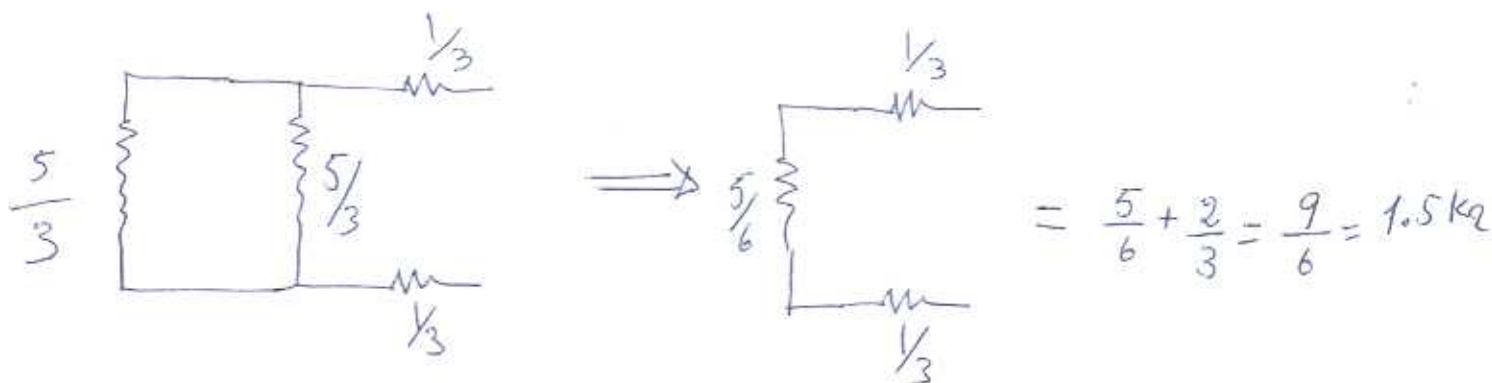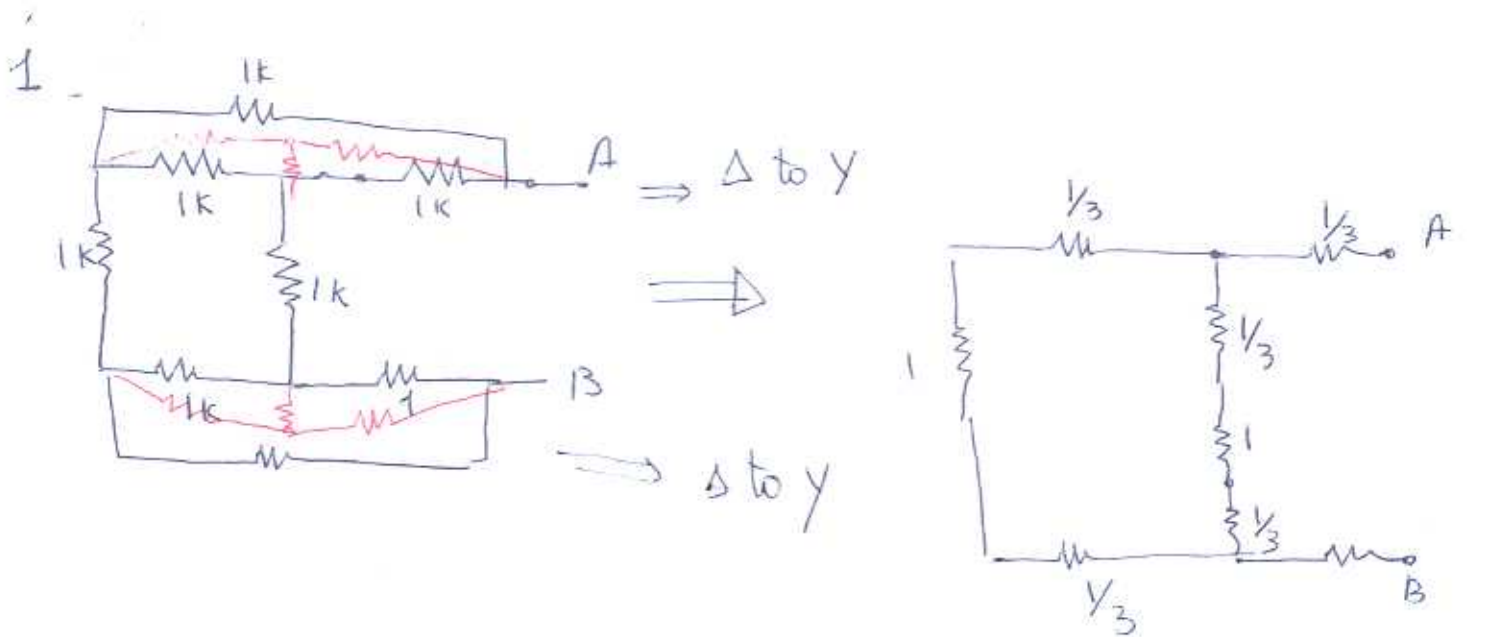


KVL

$$100 - 100i - 10i - 10 = 0 \implies 110i = 90$$

$$i = \frac{9}{11} \text{ A}$$
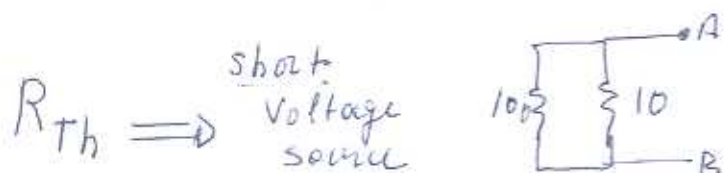
$$V_{AB} = V_{Th} \implies V_A - 10i - 10 = V_B \implies V_A - V_B = \frac{90}{11} + 10 = 18.2 \text{ V}$$



$$R_{Th} = \frac{10 \times 100}{10 + 100} = \frac{1000}{110} = 9.2 \Omega$$

3. a) 1 KHz  $\omega = 6280 \text{ rad/s}$

30

$Z_L = 62.8j$        $Z_C = -159j$


b) 2 KHz  $\omega = 12560 \text{ rad/s}$

$Z_L = 126j$        $Z_C = -79.5j$

1 KHz

$$I_C = \frac{10}{45j + 28.3 - 159j}$$
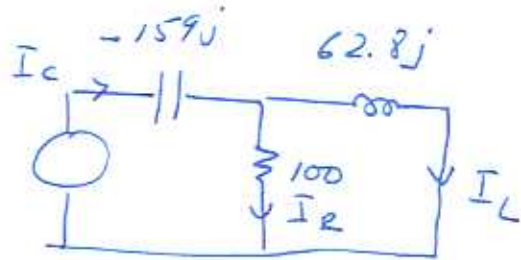
$$= \frac{10}{-114j + 28.3} = \frac{10}{117 \angle -76^\circ}$$



$$I_R = I_C \cdot \frac{62.8j}{100 + 62.8j}$$

$$= \frac{628j}{9989 - 9623j}$$

$$= 0.0453 \angle 134^\circ$$

RMS

$$Z_{||} = \frac{100 \cdot 62.8j}{100 + 62.8j}$$

$$= \frac{62.8j}{1 + 0.628j}$$


$$= 45j + 28.3$$

$$= 53 \angle 58^\circ$$

2 KHz

$$I_L = \frac{10}{126j - 38.7 - 48.7j}$$
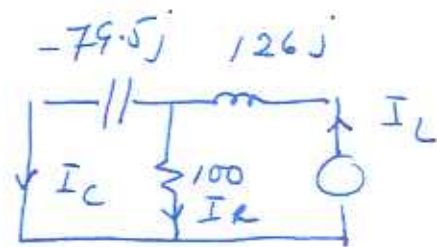
$$= \frac{10}{77.3j - 38.7} = \frac{10}{86 \angle -63.4^\circ}$$



$$I_R = I_L \cdot \frac{-79.5j}{100 - 79.5j}$$

$$= \frac{-795j}{2275 + 10807j}$$

$$= 0.072 \angle -168^\circ$$

RMS

$$Z_{||} = \frac{100(-79.5j)}{100 - 79.5j}$$

$$= \frac{-79.5j}{1 - 0.795j}$$


$$= -48.7j - 38.7$$

$$= 62.2 \angle 51.5^\circ$$


$$i_R = 45.3\sqrt{2} \cos(6280t + 134^\circ) + 72\sqrt{2} \cos(12560t - 168^\circ) \text{ mA}$$

$$\begin{aligned} \text{Power} &= (0.0453)^2 \cdot 100 + (0.072)^2 \cdot 100 \\ &= 0.72 \text{ W.} \end{aligned}$$

4.

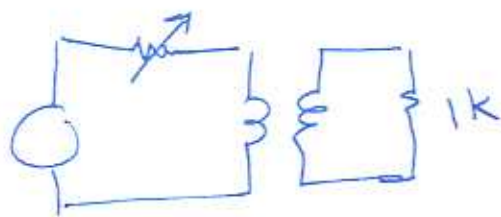

20

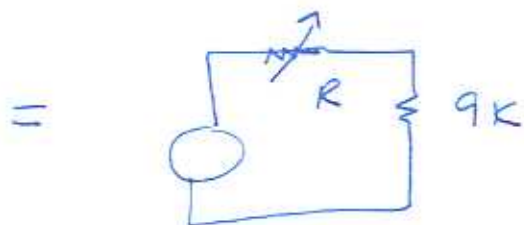

7

Maximum power is delivered to the load when  $R = 0$

7

$$P = \frac{10^2}{9 \times 10^3} = \frac{1}{90} \text{ W} = 11.1 \text{ mW.}$$

6