




# American University of Beirut



## CMPS 255 Final Exam

January 28, 2003

2 hour exam

 


Student Name: \_\_\_\_\_ Student ID: \_\_\_\_\_


Signature: \_\_\_\_\_

- There are **ten** pages, including this one. The test is out of 100 marks, and the value of each question is provided. Please use this information to manage your time effectively.
- Your handwriting should be neat and readable **OR I WILL NOT MARK THE ANSWER!**

Question 1: _____ /10
Question 2: _____ /10
Question 3: _____ /10
Question 4: _____ /30
Question 5: _____ /10
Question 6: _____ /10
Question 7: _____ /10
Question 8: _____ /10
_____ /100

Instructor: *Marcel R. karam*

 

 **Question 1: Multiple Choice [10 points]**


True or false? No explanation required. Each correct answer is worth 1 points, but 1 point will be subtracted for each wrong answer, so answer only if you are reasonably certain.

- 1- **T**    **F**    The SPARC architecture is big-endian, but the Pentium is little-endian.
  
- 2- **T**    **F**    A big-endian file needs to be "byte swapped" before using it on a different architecture (or equivalently, the program needs to know the format of the file and work with it as appropriate for the big/little-endian format.)
  
- 3- **T**    **F**    Multi-byte words are stored as a sequence of bytes, in which the address of the multi-byte word is the same as the byte of the word that has the lowest address.
  
- 4- **T**    **F**    The "control section" of the CPU interprets instructions and effects register transfers.
  
- 5- **T**    **F**    The ARC datapath is made up of the register file and the ALU.
  
- 6- **T**    **F**    Subroutine linkage with a data link area passes parameters in registers.
  
- 7- **T**    **F**    Subroutine linkage with a stack passes parameters in a separate area in memory.
  
- 8- **T**    **F**    A simple register is a register that consists of flip-flops and external gates.
  
- 9- **T**    **F**    In general, a shift register is capable of shifting its stored bits laterally only in one direction.
  
- 10- **T**    **F**    Simultaneous *loading* of bits into a register is not done with a common clock pulse.


 
### Question 2: Bubble Logic [10 points]

Convert the following logic circuit into a circuit that consists of NOR gates and inverters, using the bubble logic.




### Question 3: Control Unit in SPARC CPU [10 points]

Name the five steps that the control unit carries out in executing a program, and describe briefly the role of the Decode the opcode step. (No marks will be given for naming the "decode the opcode" step)


 
### Question 4: State Machines [30 points]

Implement the State Machine that is described by the following state diagram. You can use only D flip-flops and 4:1 multiplexers



- a- Derive the state transition table. For the sake of simplifying the marking process, please follow the Q1 Q0 X, Q1+, Q0+ Z format in your table.
- b- Derive the next state logic equations.
- c- Draw the schematic diagram of the FSM, using D flip-flops and 4:1 multiplexers.





### Question 5: Recognizing Sequences [10 points]

Give the state diagram of a Mealy type finite state machine that has one input X and two outputs Y and Z. The output Y will be 1 whenever the sequence 101 has been detected and the output Z will be 1 when the sequence 011 has been detected. These sequences can be overlapping.

The operation is illustrated in the following example:

X: 00110101100100111011  
Y: 00000101000000000010  
Z: 00010000100000010001







**Question 6: ARC Assembly [10 points]**

The Fibonacci numbers up to 200 are calculated and stored in an array. The following is the java version:

```
int[] fib = new int[20];
int a;
int b = 0;
int c = 1;
fib[0] = b;
fib[1] = c;
int i=2;
while (c<200) {
a = b;
b = c;
c = a + b;
fib[i++] = c;
}
```

Write the above code in the ARC assembly language. The table with some mnemonics and their meanings is provided below.

<b>ld</b>	Load a register from memory
<b>st</b>	Store a register into memory
<b>sethi</b>	Load the 22 most significant bits of a register
<b>andcc</b>	Bitwise logical AND
<b>orcc</b>	Bitwise logical OR
<b>orncc</b>	Bitwise logical NOR
<b>srl</b>	Shift right (logical)
<b>addcc</b>	Add
<b>call</b>	Call subroutine
<b>jmp1</b>	Jump and link (return from subroutine call)
<b>be</b>	Branch if equal
<b>bneg</b>	Branch if negative
<b>bcs</b>	Branch on carry
<b>bvs</b>	Branch on overflow
<b>ba</b>	Branch always



### Question 7: Registers and Mux [10 points]

Implement a system for the following set of Register Transfer Operations. A set of operations needs to be executed during one clock cycle. Only one (or none) of the control signals  $C_a$  or  $C_b$  can be asserted (i.e. "1") at one time. You can draw the registers as block diagrams (no details)

$C_a$ :  $R_0 = R_1$ ;  $R_2 = R_1$ ;  $R_3 = R_0$

$C_b$ :  $R_0 = R_3$ ;  $R_1 = R_2$ ;  $R_3 = R_2$

Draw the logic diagram of the hardware implementation using registers and multiplexers.



**Question 8: Address Instructions [10 points]**

- a) Write the following instruction using 2 and 1 address instruction set:  $A := B - C$
- b) What is the total memory traffic for each instruction?



January 28, 2003

CMPS 255 Final Exam



Instructor: *Marcel R. karam*

12/12