



Fall 2004

??
200

American University of Beirut
Faculty of Arts and Science,
Department of Computer Science

CMPS 255 final exam
Digital Design and Computer Architecture
Exam duration: 2 hours
Prof. G. Beydoun

Name: _____ ID: _____

- a. Students must use this question sheet for their answers
- b. Students can use the back side of each page for rough working

PART I (10 marks): 1 mark for each answer slot. Do not show working.

a) For each of the truth tables shown below write down the function representation in SOP form.

A	B	C	P
0	X	0	1
0	1	1	1
0	1	X	1
1	X	X	0

A	B	C	Q
0	0	X	0
0	1	X	1
0	X	1	1
1	0	1	0
0	1	0	1

P = _____

Q = _____

b) The minterm SOP representation of the function $Y(A, B) = \sim A \sim B$ is:

Y = _____

c) Consider the shown K-map:


CD	00	01	11	10
AB				
00	0	1	1	0
01	X	1	X	1
11	0	X	X	1
10	0	1	0	0

For the shown K-map, write down the following:


In minimal SOP, $F =$ _____

In minimal POS, $F =$ _____

In minimal POS, $\sim F =$ _____

 


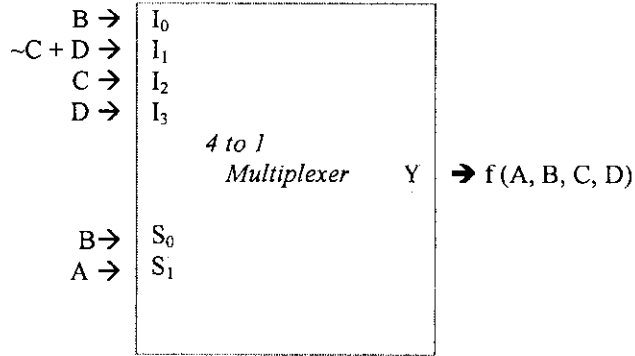d) Write down the expression of the function $f(A, B, C, D)$ implemented by the shown circuit. Note A and B are control inputs (i.e. select lines).



f = _____

 e) R and S are implemented by the following circuits. Note B is the control input (i.e. the select line):



R = _____

S = _____

$$F(R, S) = RS + \sim R \sim S$$

Write down F in terms of A and B:

F(A, B) = _____




PART II (20 marks): Each question in this part is worth 1 mark. Do not show working.

1. $(-29) =$ (_____)
2. $(0110101111) =$ (_____)
3. Interfacing an ALU to data registers can be done with the logic macro (_____)
4. The total number of states that n flip-flops can have is (_____)
5. 4 registers involved in the fetch cycle involve (_____)
6. A device that can have three different output states is said to be (_____)
7. To convert between serial and parallel, the type of register needed is (_____)
8. Number of address bits needed in a 2 byte words addressable machine with 2048 bytes: (_____)

Answer questions 9 to 20 by ticking *True (T)* or *False (F)*:

 9. The number of instruction bytes during the fetch sequence is fixed T _____ F _____
10. Memory organization: 10-bit address, 2048 words, 16 bits per word is possible T _____ F _____
11. The opcode and addressing mode for an instruction is obtained the fetch T _____ F _____
12. PC is incremented during fetch even for branch and jump instructions T _____ F _____
13. Memory organization: 10-bit address, 1024 words, 128 bits per word is not possible T _____ F _____
14. During the execute sequence, one or more additional words containing the operands for the current instruction will always be fetched from memory T _____ F _____
15. The storage capacity for a 256k x 64 memory chip is 16 KBytes T _____ F _____
16. The addressing mode for MOVE d1,#5 for a Pentium CPU is *direct* T _____ F _____
17. Memory organization: 10-bit address, 512 words, 64 bits per word is possible T _____ F _____
18. Using tri-state devices to interface internal buses in CPU to registers reduces complexity of control unit T _____ F _____
19. A Moore sequential network is a network with more output than input. T _____ F _____
20. Memory organization: 10-bit address, 16 words, 8 bits per word is not possible T _____ F _____






Part III (13 marks):

A sequential circuit has one input X and one output Z. If the input X is 1, the circuit counts in the sequence: 011, 001, 110, 010, 111, 100, 101, 011, ... If the input X is 0, the circuit counts in the sequence: 011, 110, 001, 111, 010, 101, 100, 011, ... Each time the count is 100, the circuit outputs 1.

a) Draw the state diagram of the behaviour of the circuit (4 marks)

 b) Give the transition table of the circuit (2 marks)





c) Use K-maps in space provided to give excitation functions for 3 JK flipflops to implement the circuit, and output function Z . Take J_0 and K_0 as the activation for the Flip Flop storing the least significant bit of the state. (7 marks).

$J_0 =$ _____ $K_0 =$ _____

$J_1 =$ _____ $K_1 =$ _____

$J_2 =$ _____ $K_2 =$ _____

$Z =$ _____



Part IV (8 marks):

b) (2 marks) The register transfer steps for *bra #my_proc* are:

d) (6 marks) Translate the following Java expression to assembly language. Use direct addressing mode assuming that $d0 = a$, $d1 = b$, $d2 = c$

```
int a = 0, b = 2, c = 1;
while ( c < (a+b) )
{
    a = c + b;
    if ( a < 5 ) b ++;
    c ++;
}
```