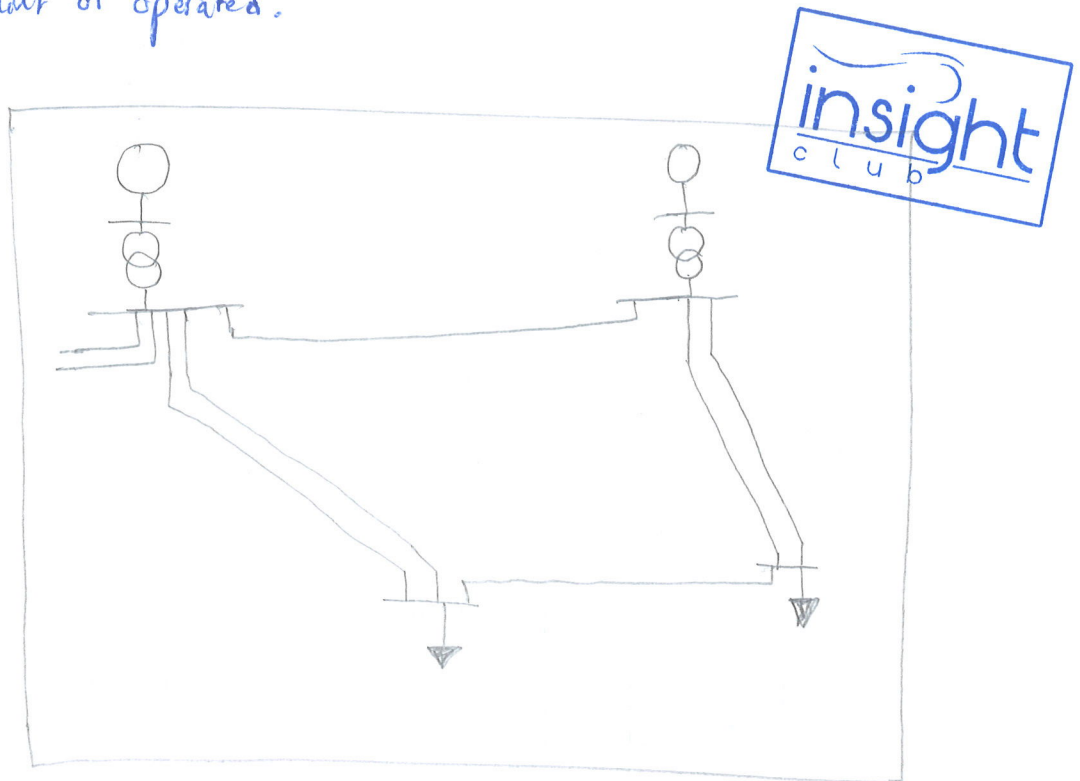


- Calculation tool to assess the operation of a power system that is being built or operated.



• The power flow problem specifies

- system parameters (resistance, reactance, susceptance of TL, transformers).
- Loads (demands of active & reactive power at node).



The active power produced by generators, except for one generator (reference or slack generator).

↳ it cannot be fixed because it compensates for the power losses in the system.

• Outputs:

- Voltages and phase angles
- Line Flows
- Generator Reactive power supply (or absorption)

opt initialization

- planning: used to measure (access) the adequacy of a plan
- Operation: used to assess the effect of possible contingency on network
- Methods of Solutions
  - Gauss Seidel (older method)
  - Newton-Raphson (more modern method), plus its variations

## 6.1: Solution to linear Equations

Example 6.4:  $* 10x_1 + 5x_2 = 6$

$* 2x_1 + 9x_2 = 3$

works for diagonally dominant matrices



$$x_{ii} \gg \sum_{j \in N_i} x_{ij} \quad (\text{sufficient condition for convergence})$$

$N_i$ : set of nodes adjacent to  $i$ .

$x_1 = 0$ , and  $x_2 = 0$  (initialization)

iterations:  $x_1 = \frac{1}{10}(6 - 5x_2) = 0.6$

$x_2 = \frac{1}{9}(3 - 2x_1) = 0.2$

Iterations	0	1	2	...	6
$x_1$	0	0.6	0.5	...	0.4875
$x_2$	0	0.2	0.22	...	0.2250

## Example 6.5: Divergence of Gauss-Seidel


$$\begin{bmatrix} 5 & 10 \\ 9 & 2 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} = \begin{bmatrix} 6 \\ 3 \end{bmatrix}$$

$$x_1 = \frac{1}{5}(6 - 10x_2)$$

$$x_2 = \frac{1}{2}(3 - 9x_1)$$


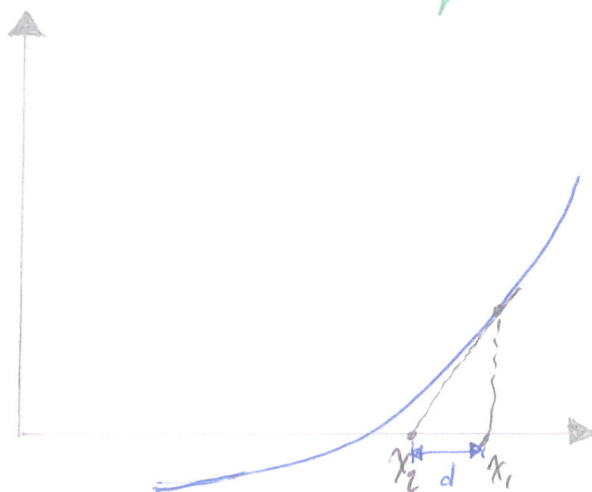
## 6.2: Iterative Solution to Non-linear Equations using Newton-Raphson Method



$$x_2 = x_1 - \frac{f(x_1)}{f'(x_1)}$$

← d →

$$f(x) = f(x_0) + f'(x_0) \cdot (x - x_0) + \frac{f''(x_0)}{2} \cdot (x - x_0)^2 + \dots$$

$$x_1 = v;$$

$$x_{r+1} = x_r + [f'(x_r)]^{-1} \cdot f(x_r)$$

- Sufficient conditions for convergence is the convexity of  $f(x)$  in the neighborhood of solution.

$$f(x) = 0$$

$$x_{r+1} = x_r - [f'(x_r)]^{-1} \cdot f(x_r)$$



$$f'(x) = \begin{bmatrix} \frac{\partial f_1}{\partial x_1} & \frac{\partial f_1}{\partial x_2} & \dots & \frac{\partial f_1}{\partial x_n} \\ \frac{\partial f_2}{\partial x_1} & \frac{\partial f_2}{\partial x_2} & \dots & \frac{\partial f_2}{\partial x_n} \\ \vdots & \vdots & \ddots & \vdots \\ \frac{\partial f_m}{\partial x_1} & \frac{\partial f_m}{\partial x_2} & \dots & \frac{\partial f_m}{\partial x_n} \end{bmatrix}$$

Jacobian Matrix

Ex 6.7

$$x_1 + x_2 = 15$$

$$x_1 \cdot x_2 = 50$$

$$f_1(x_1, x_2) = x_1 + x_2 - 15 = 0$$

$$f_2(x_1, x_2) = x_1 \cdot x_2 - 50 = 0$$

$$x = \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$

$$x_{r+1} = x_r - [f'(x_r)]^{-1} \cdot f(x_r)$$

$$J = f'(x) = \begin{bmatrix} \frac{\partial f_1}{\partial x_1} & \frac{\partial f_1}{\partial x_2} \\ \frac{\partial f_2}{\partial x_1} & \frac{\partial f_2}{\partial x_2} \end{bmatrix} = \begin{bmatrix} 1 & 1 \\ x_2 & x_1 \end{bmatrix}$$

$$x(0) = \begin{bmatrix} 4 \\ 9 \end{bmatrix};$$

i	$x_1(i)$	$x_2(i)$
0	4	9
1	5.2	9.8
2	4.99	10.0089
3	4.99998	10.00002
4	5.0	10.0



# 6.4: The Power Flow Problem

\* Starting point is the single line diagram


\* Input data:

- Active and reactive demands are specified
- Transmission lines & transformer data. (reactances, resistors)
- Parameters of shunt reactors, capacitors or other series elements.

\* Specify active power of all generators except the slack (reference) and voltage magnitude of all generator busses including the slack.
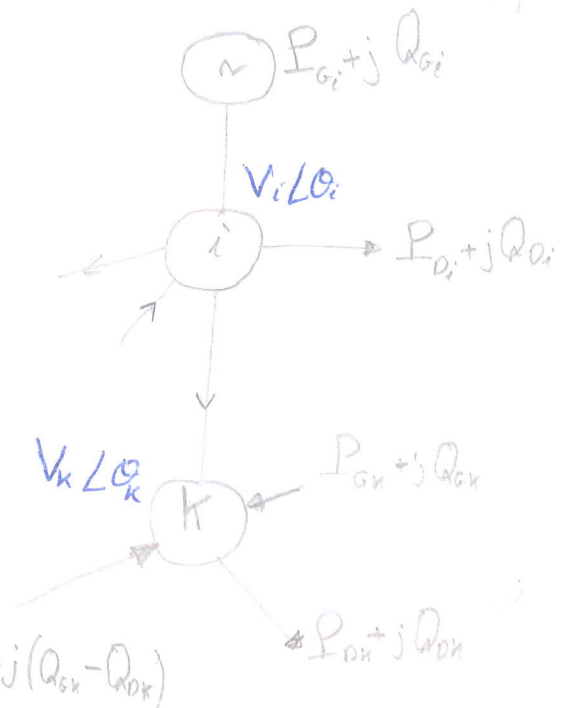
## Output Result

- Voltage magnitudes and phase angles at all nodes (fundamental results)
- Active & reactive power produced by the slack generator (at the slack busbar).
- Active and reactive flows in all TL.
- reactive power produced by generator.



## Alternative Method of Modelling a Generator

- Specify active power and reactive power (Case I)
- Specify voltage magnitudes (Case II)

## \* Nodal Equations:

$$I = Y \cdot V$$

matrix  
All voltage sources are converted to current sources

$$I_n = \sum_{k=1}^N Y_{kn} \cdot V_k =$$

Complex Power delivered to network

$$S_k = P_k + jQ_k = V_k \cdot I_k^* = V_k \cdot \left[ \sum_{n=1}^N Y_{kn}^* \cdot V_n^* \right] \quad \textcircled{1} \text{ power flow going into network}$$

Express in terms of real and imaginary terms:

$$V_k \triangleq |V_k| \angle \delta_k$$

$$V_n \triangleq |V_n| \angle \delta_n = |V_n| \cdot (\cos \delta_n + j \sin \delta_n)$$

$$Y_{kn} = G_{kn} + jB_{kn}$$

$$P_k = V_k \cdot \sum_{n=1}^N V_n \left[ G_{kn} \cdot \cos(\delta_k - \delta_n) + B_{kn} \cdot \sin(\delta_k - \delta_n) \right]$$

$$Q_k = V_k \cdot \sum_{n=1}^N V_n \cdot \left[ G_{kn} \cdot \sin(\delta_k - \delta_n) + B_{kn} \cdot \cos(\delta_k - \delta_n) \right]$$



Nodal Power Equation

$$P_{Gk} - P_{Dk} = P_k \Rightarrow$$

$$\Delta P_k = \underbrace{P_k}_{\text{power going into network}} - \underbrace{P_{Gk} + P_{Dk}}_{\text{specified injection}} = 0$$

active power mismatch at node k

$$\Delta Q_k = Q_k - Q_{Gk} + Q_{Dk} = 0$$

reactive power mismatch

Power Flow Equations

$$\boxed{P_k + jQ_k = V_k^* \cdot \left( \sum_{n=1}^N Y_{kn} \cdot V_n \right)} \quad \textcircled{1}$$


$$S_k + S_D - S_{Gk} = 0 \quad \textcircled{2} \quad k: 2 \rightarrow N \text{ except for } k=1 \text{ (slack node)}$$

$$V_k = |V_k| \cdot e^{j\delta_k}$$

$$Y_{kn} = G_{kn} + jB_{kn}$$

$$P_k = V_k^* \cdot \sum V_n \left( G_{kn} \cdot \cos(\delta_k - \delta_n) + B_{kn} \cdot \sin(\delta_k - \delta_n) \right) \quad \textcircled{3}$$
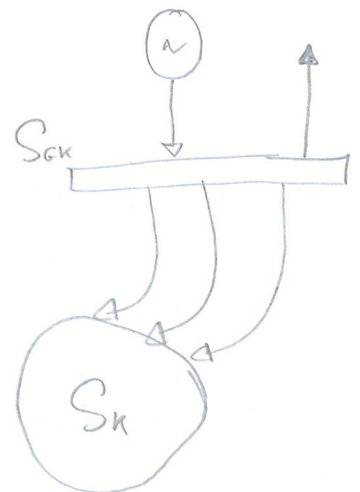
$$Q_k = V_k^* \cdot \sum V_n \left( G_{kn} \cdot \sin(\delta_k - \delta_n) + B_{kn} \cdot \cos(\delta_k - \delta_n) \right) \quad \textcircled{4}$$



## \* Active and Reactive Power Mismatch


$$\Delta P_k = P_k + P_{DK} - P_{GW} = 0 \quad (5)$$

$$\Delta Q_k = Q_k + Q_{DK} - Q_{GW} = 0 \quad (6)$$


- In Gauss Seidel, we solve (2) after replacing  $S_k$  by its value given in (1)
- In NR method, we solve (5) & (6) after replacing  $P_k$  and  $Q_k$  by their values given in (3) & (4)

## 2.4: Network Equations

- Nodal equations of a simple system:

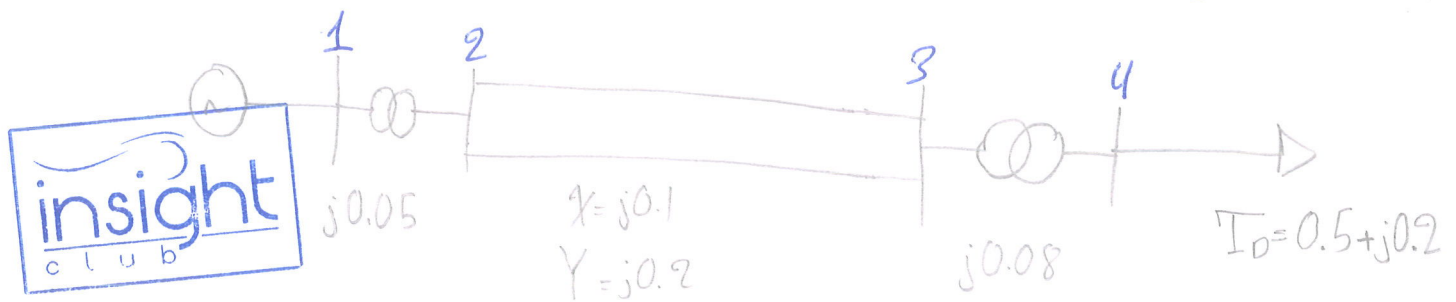

$$I = Y \cdot V$$

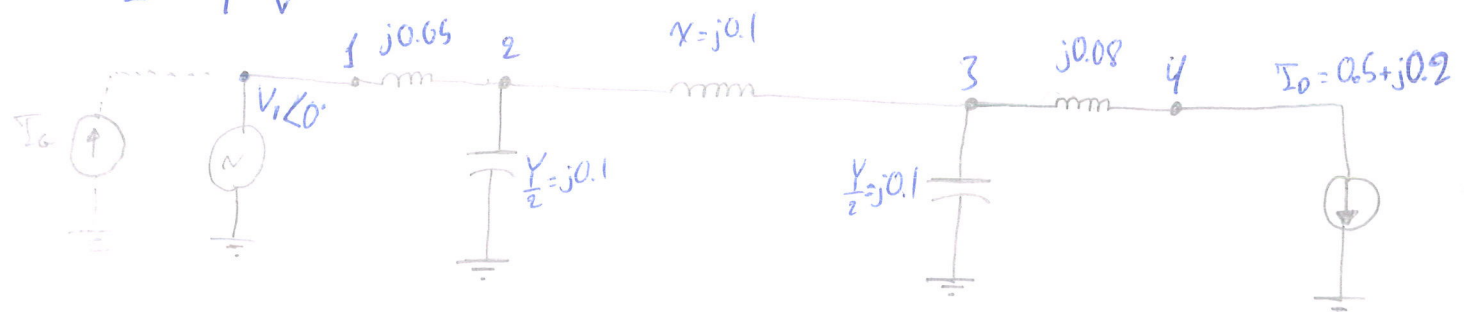

$$1. \frac{V_1 - V_2}{j0.05} = I_G$$

$$2. \frac{V_2 - V_1}{j0.05} + V_2(j0.1) + \frac{V_2 - V_3}{j0.1} = 0$$

$$3. \frac{V_3 - V_2}{j0.1} + V_3(j0.1) + \frac{V_3 - V_4}{j0.08} = 0$$

$$4. \frac{V_4 - V_3}{j0.08} = -(0.5 + j0.2)$$

Rearrange:

equivalent  
to current source of  $\frac{V_1}{j0.05}$

$$+\left(\frac{1}{j0.05} + j0.1 + \frac{1}{j0.1}\right)V_2 + -\frac{1}{j0.1}V_3 + 0 = V_u$$

$$-\frac{1}{j0.1}V_2 + \left(\frac{1}{j0.1} + j0.1 + \frac{1}{j0.08}\right)V_3 + \left(-\frac{1}{j0.08}\right)V_u = 0$$


$$0 = V_2 + \left(-\frac{1}{j0.08}\right)V_3 + \frac{1}{j0.08}V_u = 0$$

	1	2	3	4		
1	X	X	X	X	$V_1$	
2	X	$\frac{1}{j0.05} + j0.1 + \frac{1}{j0.1}$	$-\frac{1}{j0.1}$	0	$V_2$	$\frac{V_1}{j0.05}$
3	X	$-\frac{1}{j0.1}$	$\frac{1}{j0.1} + j0.1 + \frac{1}{j0.08}$	$-\frac{1}{j0.08}$	$V_3$	0
4	X	0	$-\frac{1}{j0.08}$	$\frac{1}{j0.08}$	$V_4$	$-(0.5 + j0.2)$



$$Y \cdot V = I$$

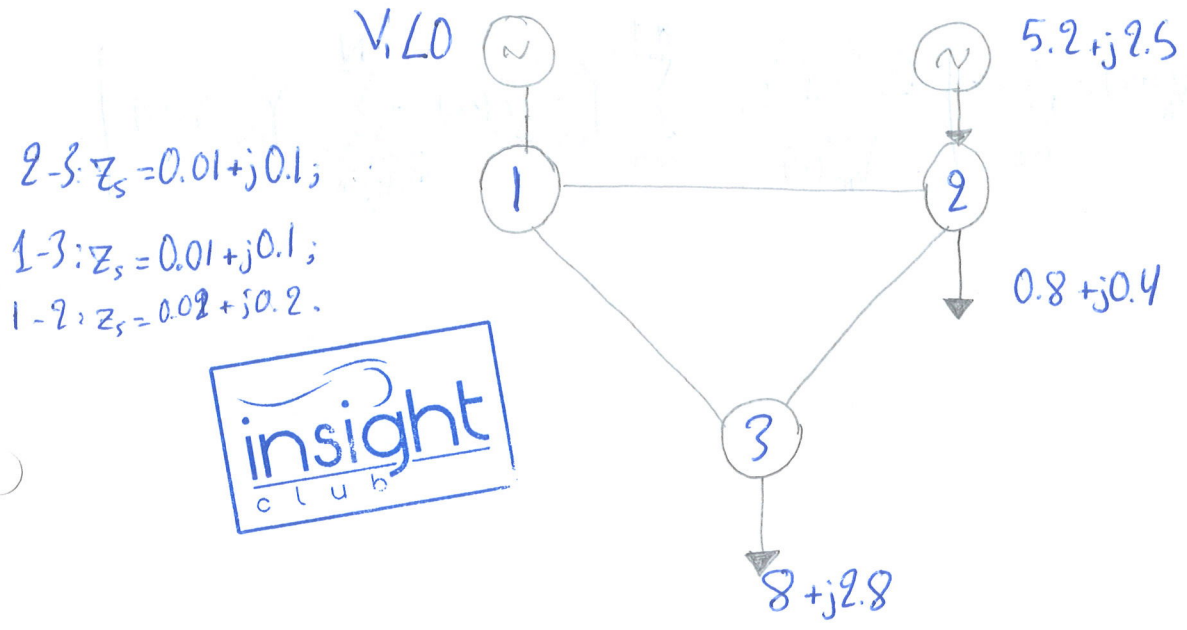Exercise: Write the nodal Equation of the following Network:



# Summary

## Nodal Admittance Matrix:



→ Diagonal Element:  $Y_{ii}$  = the sum of all admittance connected to node  $i$ .


→ off-Diagonal Element:  $Y_{ij}$  = The NEGATIVE of the admittance connecting nodes  $i$  &  $j$

∴  $Y_{ij} = 0$  when there is no connection between  $i$  &  $j$

## 2.5: Power Flow Solution by Gauss Seidel:

$$V_k \cdot \left( \sum_{n=1}^N Y_{kn}^* \cdot V_n^* \right) + S_{Dk} - S_{Gk} = 0$$

$S_k$                        $-S_k^{SP}$

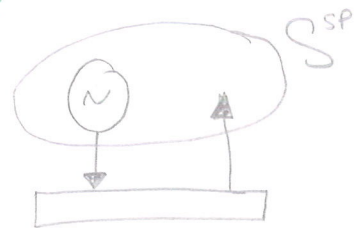

$$\frac{1}{V_k^*} \left[ V_k \cdot Y_{kk}^* \cdot V_k^* + V_k \cdot \sum_{n \neq k} Y_{kn}^* \cdot V_n^* \right] = S_k^{SP} \quad k=2, \dots, N$$



- take conjugates
- divide by  $V_k^*$
- rearrange

$$V_k^{(r+1)} = \frac{1}{Y_{kk}} \left[ \frac{S_k^{SP}}{V_k^*(r)} - \sum_{n \neq k} Y_{kn} \cdot V_n^{(r)} \right] \quad k=2, \dots, N$$

$$V_k^{(r+1)} = \frac{1}{Y_{kk}} \left[ \frac{P_k^{SP} - jQ_k^{SP}}{V_k^*(r)} - \sum_{n=k-1}^k Y_{kn} \cdot V_n^{(r+1)} - \sum_{n=k+1}^N Y_{kn} \cdot V_n^{(r)} \right]$$




Node 1 is slack node!

$$Y_{11} = \frac{1}{0.01 + j0.1} + \frac{1}{0.02 + j0.2} = 1.485 - j14.85$$

$$Y_{12} = -\frac{1}{0.02 + j0.2} = -0.495 + j4.95$$
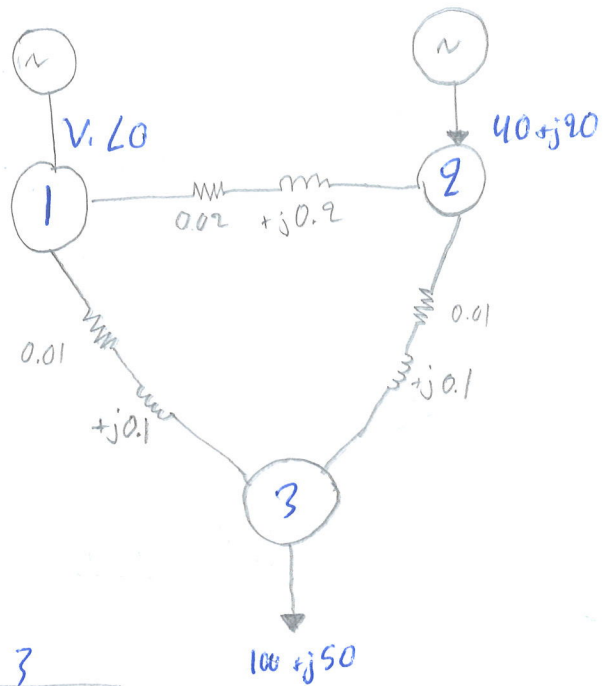
$$Y_{22} = \frac{1}{0.02 + j0.2} + \frac{1}{0.01 + j0.1} = 1.485 - j14.85$$



Y

	1	2	3
Y=1	1.485 -j14.85	-0.495 + j4.95	-0.9901 +j9.901
2	-0.495 +j4.95	1.485 -j14.85	-0.9901 +j9.901
3	-0.9901 +j9.901	-0.99 +j9.901	1.98 -j19.8



Write the Gauss-Seidel Iterative Equations

$$V_k^{(r+1)} = \frac{1}{Y_{kk}} \left[ \frac{P_k^{sp} - jQ^{sp}}{V_k^{*(r)}} - \sum_{n=1}^{k-1} Y_{kn} \cdot V_n^{(r+1)} - \sum_{n=k+1}^N Y_{kn} \cdot V_n^{(r)} \right]$$

$$V_2^{(r+1)} = \frac{1}{Y_{22}} \left[ \frac{0.4 - j0.2}{V_2^{*(r)}} - Y_{21} \cdot V_1 - Y_{23} \cdot V_3^{(r)} \right]$$

$$V_3^{(r+1)} = \frac{1}{Y_{33}} \left[ \frac{(1 - j0.5)}{V_3^{*(r)}} - Y_{31} \cdot V_1 - Y_{32} \cdot V_2^{(r)} \right]$$

Demand



- $V_1 = 1 \angle 0$
- $V_2(0) = 1 \angle 0$
- $V_3(0) = 1 \angle 0$

\* Correction for PV node

$$V_2^{(r+1)} = V_2^{(r)} * \frac{|V_2|}{|\hat{V}_2^{(r)}|}$$

$$\hat{Q}^{sp} = Q = \text{Im} \left( V_2 \cdot \sum_{n=1}^3 Y_{2n}^* \cdot V_n^* \right)$$

$$S_k = P_k + jQ_k = V_k \sum_{n=1}^N Y_{kn}^* \cdot V_n^*$$



Exercise on using G.S for Power Flow Calculation:

• Take the network of H.W #1



• Data given

a) Form Y matrix

b) Write Iterative Equations

• 3 iterative equations

• plug in the numbers

• carry out the first iteration (& 2<sup>nd</sup> iteration)



No generation

No demand

$$V_2^{(r+1)} = \frac{1}{Y_{22}} \left[ \frac{P_2^{sp} + jQ_2^{sp}}{V_2^{(r)}} \dots \right]$$

## 6.6: Power Flow using Newton-Raphson's Method

$$f(x) = 0$$

$$x_{r+1} = x_r - [J'(x_r)]^{-1} \cdot f(x)$$

• When applied to the Power Flow Problem:

$$x = \begin{bmatrix} \delta \\ \vdots \\ v \\ \vdots \\ v \end{bmatrix} \left. \vphantom{\begin{bmatrix} \delta \\ \vdots \\ v \\ \vdots \\ v \end{bmatrix}} \right\} 2(N-1)$$

$$f(x) = \begin{bmatrix} \Delta P(\delta, V) \\ \vdots \\ \Delta Q(\delta, V) \end{bmatrix}$$

insight

$$J = \frac{\partial f}{\partial x} = \begin{bmatrix} \frac{\partial \Delta P_2}{\partial \delta_2} & \frac{\partial \Delta P_2}{\partial \delta_N} & \frac{\partial \Delta P_2}{\partial V_2} & \frac{\partial \Delta P_2}{\partial V_N} \\ \vdots & \vdots & \vdots & \vdots \\ \frac{\partial \Delta P_N}{\partial \delta_2} & \frac{\partial \Delta P_N}{\partial \delta_N} & \frac{\partial \Delta P_N}{\partial V_2} & \frac{\partial \Delta P_N}{\partial V_N} \\ \frac{\partial \Delta Q_2}{\partial \delta_2} & \frac{\partial \Delta Q_2}{\partial \delta_N} & \frac{\partial \Delta Q_2}{\partial V_2} & \frac{\partial \Delta Q_2}{\partial V_N} \\ \vdots & \vdots & \vdots & \vdots \\ \frac{\partial \Delta Q_N}{\partial \delta_2} & \frac{\partial \Delta Q_N}{\partial \delta_N} & \frac{\partial \Delta Q_N}{\partial V_2} & \frac{\partial \Delta Q_N}{\partial V_N} \end{bmatrix}$$

insight club

$$P^{sp} = P_{GK} - P_{DK}$$



$$\Delta P_k = \sum_{n=1}^N V_k \cdot V_n \left[ G_{kn} \cdot \cos(\delta_k - \delta_n) + B_{kn} \cdot \sin(\delta_k - \delta_n) \right] - (P_{GK} - P_{DK}) = 0$$

$P_{\text{going to Network}}$

$$\Delta Q_k = \sum_{n=1}^N V_k \cdot V_n \left[ G_{kn} \cdot \sin(\delta_k - \delta_n) + B_{kn} \cdot \cos(\delta_k - \delta_n) \right] - (Q_{GK} - Q_{DK}) = 0$$

$$\frac{\partial \Delta P_k}{\partial \delta_k} = J_1(k,k) = \sum_{n \neq k} V_k V_n \left[ -G_{kn} \cdot \sin(\delta_k - \delta_n) + B_{kn} \cdot \cos(\delta_k - \delta_n) \right]$$

$n \neq k$  since  $\cos(\delta_k - \delta_n) = 0$   
 $\Delta \sin(\delta_k - \delta_n) = 0$   
 comes from the special form in  $\Delta P_k$  when  $n=k$   
 $V_n^2 G_{kk}$

$$\frac{\partial \Delta P_k}{\partial V_k} = J_2(k,k) = \sum_{n \neq k} V_n \left[ G_{kn} \cdot \cos(\delta_k - \delta_n) + B_{kn} \cdot \sin(\delta_k - \delta_n) \right] + 2 V_k G_{kk}$$

$$\frac{\partial \Delta Q_k}{\partial \delta_n} = J_3(k,k) = \sum_{n \neq k} V_k V_n \left[ G_{kn} \cdot \cos(\delta_k - \delta_n) + B_{kn} \cdot \sin(\delta_k - \delta_n) \right]$$

coming from the special form

$$\frac{\partial \Delta Q_k}{\partial V_k} = J_4(k,k) = \sum_{n \neq k} V_n \left[ G_{kn} \cdot \sin(\delta_k - \delta_n) - B_{kn} \cdot \cos(\delta_k - \delta_n) \right] - 2 V_k \cdot B_{kk}$$


when  $n=k$   
 $(-V_k^2 \cdot B_{kk})$

$$J_1(k,n) = \frac{\partial \Delta P_k}{\partial \delta_n} = V_k V_n \left[ G_{kn} \sin(\delta_k - \delta_n) - B_{kn} \cos(\delta_k - \delta_n) \right]$$

$$J_2(k,n) = \frac{\partial \Delta P_k}{\partial V_n} = V_k \left[ G_{kn} \cos(\delta_k - \delta_n) + B_{kn} \sin(\delta_k - \delta_n) \right]$$

$$J_3(k,n) = \frac{\partial \Delta Q_k}{\partial \delta_n} = -V_k V_n \left[ G_{kn} \cos(\delta_k - \delta_n) + B_{kn} \sin(\delta_k - \delta_n) \right]$$
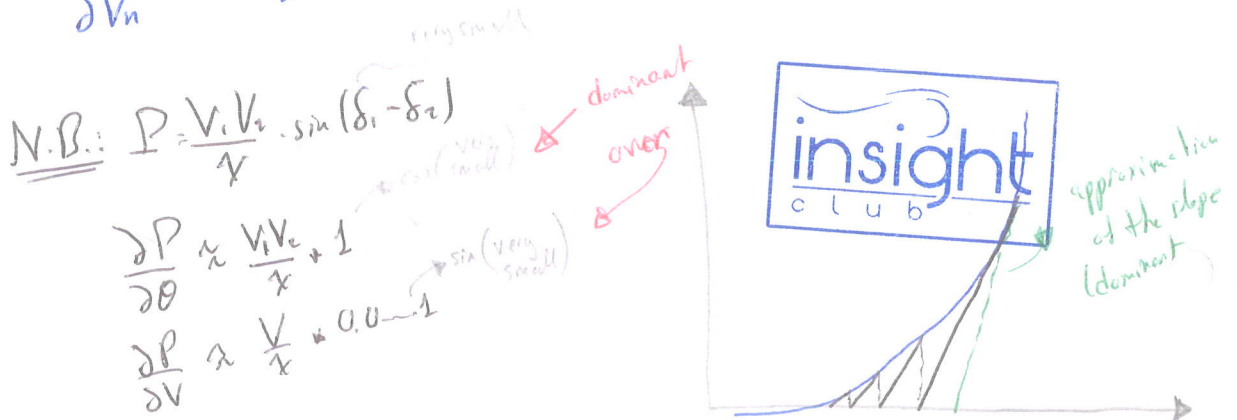
$$J_4(k,n) = \frac{\partial \Delta Q_k}{\partial V_n} = V_k \left[ G_{kn} \sin(\delta_k - \delta_n) - B_{kn} \cos(\delta_k - \delta_n) \right]$$



$$\begin{bmatrix} \theta_{r1} \\ V_{r1} \end{bmatrix} = \begin{bmatrix} \theta_r \\ V_r \end{bmatrix} - \begin{bmatrix} J_1 & J_2 \\ J_3 & J_4 \end{bmatrix}^{-1} \begin{bmatrix} \Delta P(\theta_r, V_r) \\ \Delta Q(\theta_r, V_r) \end{bmatrix}$$

(θ<sub>r</sub>, V<sub>r</sub>)



↑ has to be calculated exactly as given in expressions. Because, they represent KCL at node k

Fast Decoupled Load Flow

Newton-Raphson Power Flow

$$\begin{bmatrix} \theta_{r1} \\ V_{r1} \end{bmatrix} = \begin{bmatrix} \theta_r \\ V_r \end{bmatrix} - \underbrace{\begin{bmatrix} J_1 & J_2 \\ J_3 & J_4 \end{bmatrix}^{-1}}_{\begin{bmatrix} \Delta \theta_r \\ \Delta V_r \end{bmatrix}} \begin{bmatrix} \Delta P(\theta_r, V_r) \\ \Delta Q(\theta_r, V_r) \end{bmatrix}$$

• The calculation matrix  $J$  and its inversion at every iteration is a major computational burden of the method.

• This justifies the approximations sought.

• It was noticed through the computations that  $J_1, J_2, J_3$  significantly vary. (consult example in old note, from Bergen & Kirtley)

• Stott & others tried successfully to keep them constant.

• Also, noticed (conf. example in old notes) that elements of  $J_2$  are much smaller than elements in  $J_1$ , similarly elements in  $J_3$  are much smaller than elements in  $J_1$ !

• The idea occurred to neglect  $J_2$  &  $J_3$ !

$$J_1(k, n) = V_k V_n [G_{kn} \sin(\theta_k - \theta_n) - B_{kn} \cos(\theta_k - \theta_n)]$$

$$J_2(k, n) = V_k (G_{kn} \cos(\theta_k - \theta_n) + B_{kn} \sin(\theta_k - \theta_n))$$

• In a reasonable systems:

$$V_n \approx V_k \approx 1$$

$\theta_k$  &  $\theta_n$  are small  $\therefore \sin(\theta_k - \theta_n) \approx \theta_k - \theta_n$

$$\cos(\theta_k - \theta_n) \approx 1$$

• High  $X/R$  ( $> 5$ )



