


ABCD constants: Two-port network Theory.

5.1: Short and Medium Transmission Lines



Model the transmission line by a two port network

Two Port Network:

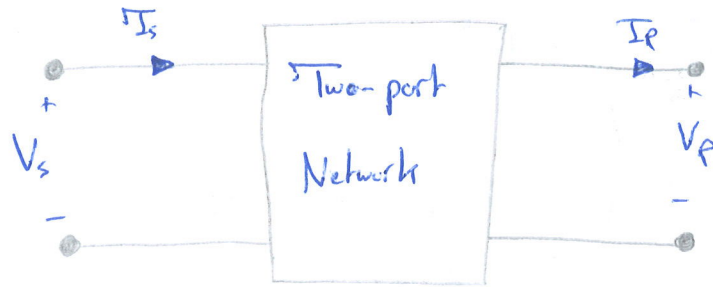

$$V_s = A \cdot V_R + B I_R$$

$$I_s = C \cdot V_R + D I_R$$




$$AD - BC = 1$$

So linear Bilateral Element

Short Line ($l \leq 80 \text{ km} \sim 50 \text{ miles}$)

For such a line, a series model is used

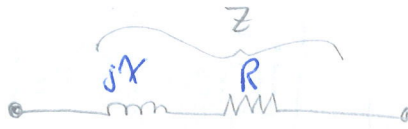

$$X = x \cdot l$$

$\frac{\Omega}{\text{km}}$ $\frac{\Omega}{\text{km}}$

$$R = r \cdot l$$


$\frac{\Omega}{\text{km}}$ $\frac{\Omega}{\text{km}}$

Y is neglected for overhead lines (OHL)

ABCD of a short line:

$$V_s = V_R + Z I_R$$

$$I_s = 0 \cdot V_R + 1 \cdot I_R$$

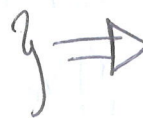

$$A = 1$$

$$B = Z$$

$$C = 0$$

$$D = 1 = A$$

so; $AD - BC = 1 \implies$ this means T^{-1} exists

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$


T : Transmission Matrix



$$\implies \begin{bmatrix} V_R \\ I_R \end{bmatrix} = \begin{bmatrix} T^{-1} \end{bmatrix} \begin{bmatrix} V_s \\ I_s \end{bmatrix}$$

• $S_s = P_s + jQ_s = V_s \cdot I_s^*$ in per unit

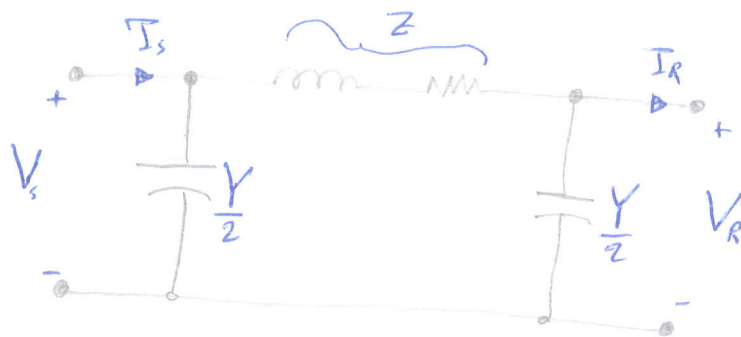• A Medium-Length-Line ($50 \text{ km} < l < 240 \text{ km}$)



π -Equivalent

$$Z = R + jX = (r + ja) \cdot l / Z_{\text{base}}$$

$$Y = jy \cdot l = j\omega CL \quad (* Z_{\text{base}})$$

• ABCD of a medium Line:



$$V_s = V_R + Z \cdot (I_R + V_R \cdot \frac{Y}{2})$$

$$= \underbrace{(1 + \frac{ZY}{2})}_A V_R + \underbrace{Z}_B I_R$$

$$\begin{aligned} I_s &= (I_R + \frac{Y}{2} V_R) + V_s \cdot \frac{Y}{2} \\ &= (I_R + \frac{Y}{2} V_R) + [(1 + \frac{ZY}{2}) V_R + Z I_R] \cdot \frac{Y}{2} \\ &= \underbrace{Y(1 + \frac{ZY}{4})}_C V_R + \underbrace{(1 + \frac{ZY}{2})}_D I_R \end{aligned}$$


$$\implies \begin{cases} A = (1 + \frac{ZY}{2}) \\ B = Z \\ C = Y(1 + \frac{ZY}{4}) \\ D = A = (1 + \frac{ZY}{2}) \end{cases}$$



- A double line $\begin{cases} \cdot Y \text{ is doubled} \\ \cdot Z \text{ is halved} \end{cases}$

• because they are in parallel.

• Simple Transformer Model

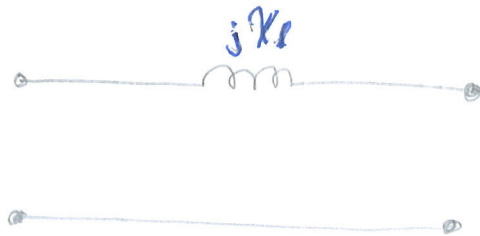

$$R=0$$

$$Y=0$$





$$A = D = 1$$

$$B = Z$$

$$C = 0$$

• System Matrix

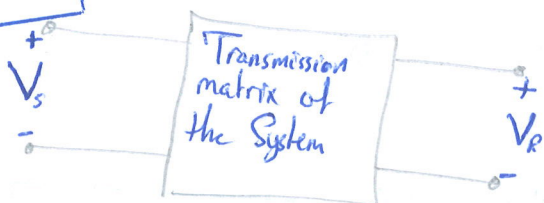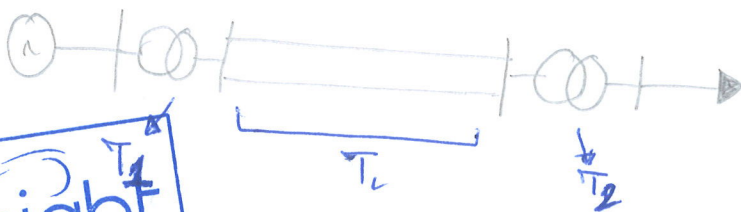

$$T_S = [T_1] \cdot [T_L] \cdot [T_2]$$

• Voltage Regulation

$$VR = \frac{V_{R(\text{no load})} - V_{R(\text{full load})}}{V_{R(\text{full load})}} \times 100$$

at no load:

$$I_R = 0$$

$$V_S = A \cdot V_{R(\text{no load})}$$

$$\rightarrow V_{R(\text{no load})} = \frac{V_S}{A}$$

Exercise: Take data from Assignment 1.

Calculate impedances in P.U.

Form a transmission matrix of the whole system ($T_1 - T_L - T_2$)

Consider the voltage on receiving end is 0.95 p.u. ($V_R = 0.95 \angle 0^\circ$)

For the given load data, Calculate the voltage and current at sending end.

Deduce the active & reactive power delivered by generator.

Example 5.1: ABCD parameters of a medium Line

345 kV, 900 km, 2 * 795000 cmil

$$Z = 0.032 + j0.35 \text{ } \Omega/\text{km}$$

$$Y = j4.2 \times 10^{-6} \text{ S/km}$$

$$Z_{Base} = \frac{345^2}{100} = 1190.25 \text{ } \Omega$$


700 MW @ 0.99 pf loading; $V_R = 0.95$

$$\bullet Z = z l = 70.99 \angle 84.8^\circ \rightarrow Z_{p.u.} = \frac{70.99}{1190.25} \angle 84.8^\circ$$

$$\bullet Y = y l = 840 \times 10^{-6} \angle 90^\circ \rightarrow Y_{p.u.} = 840 \times 10^{-6} \times 1190.25 \angle 90^\circ$$

$$\bullet A = \left(1 + \frac{Y Z}{2}\right) = D = 0.9706 \angle 0.159^\circ$$

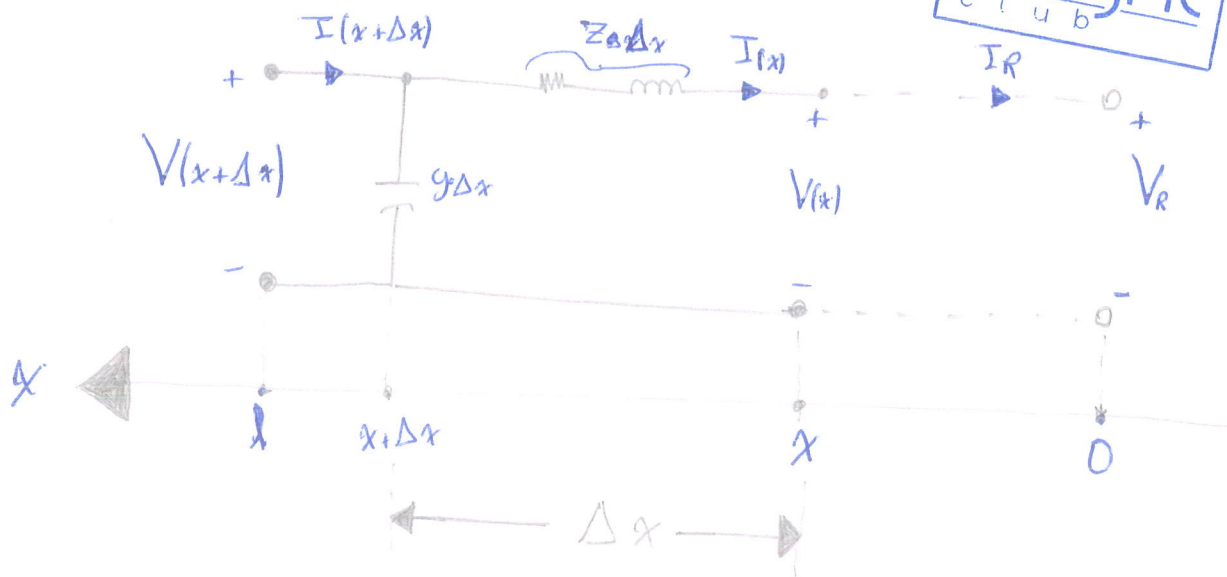5.2: Transmission Line Differential Equations.



$$\bullet Z = r + j\omega l \text{ } \Omega/\text{m} = r + jx \text{ } \Omega/\text{m}$$

$$\bullet Y = j\omega c \text{ S/m}$$

$$\bullet V(x + \Delta x) = V(x) + Z \Delta x \cdot I(x)$$



$$\hookrightarrow \frac{V(x + \Delta x) - V(x)}{\Delta x} = Z \cdot I(x)$$

$$\text{as } \Delta x \rightarrow 0; \boxed{\frac{dV(x)}{dx} = Z I(x)}$$

$$\text{KCL: } I(x+\Delta x) = I(x) + y \cdot \Delta x \cdot V(x+\Delta x)$$

$$\rightarrow \frac{I(x+\Delta x) - I(x)}{\Delta x} = y \cdot V(x+\Delta x)$$

$$\boxed{\frac{dI(x)}{dx} = y \cdot V(x)}$$

$$\frac{d^2 V(x)}{dx^2} = z \cdot \frac{dI(x)}{dx} = z \cdot y \cdot V(x)$$

$$\boxed{\frac{d^2 V(x)}{dx^2} = z \cdot y \cdot V(x)}$$



Solution is an exponential function:

$$V(x) = A_1 \cdot e^{\gamma x} + A_2 \cdot e^{-\gamma x}$$

where $\gamma = \sqrt{yz}$ \rightarrow propagation constant (m^{-1})



$$\gamma = \sqrt{j0.3 \times j3.3 \times 10^{-6}} = \sqrt{j^2 \cdot 0.3 \cdot 3.3 \times 10^{-6}} = j10^{-3} \text{ m}^{-1} = j\beta$$

• Replace $V(x)$ in D.E. of $V(x)$.

$$I(x) = \frac{A_1 \cdot e^{\gamma x} - A_2 \cdot e^{-\gamma x}}{z/\gamma}$$

$$\bullet \frac{z}{\gamma} = \sqrt{\frac{z^2}{\gamma^2 y z}} = \sqrt{\frac{z}{y}} = Z_c \text{ characteristic Impedance}$$

$$\approx \sqrt{\frac{j0.3}{j3.3 \times 10^{-6}}} = \sqrt{0.1 \times 10^6} \approx 300 \Omega$$

KV	Z_c
150	350 Ω
290	310 Ω
275	300 Ω
500	275 Ω
750	250 Ω

$$\left. \begin{aligned} \text{at } x=0; V(x=0) &= V_R \\ V_R &= A_1 + A_2 \\ I_R &= \frac{A_1 - A_2}{Z_c} \end{aligned} \right\} \rightarrow \begin{aligned} A_1 &= \frac{V_R + Z_c I_R}{2} \\ A_2 &= \frac{V_R - Z_c I_R}{2} \end{aligned}$$



$$V(x) = \left(\frac{V_R + Z_c I_R}{2} \cdot e^{\gamma x} \right) + \left(\frac{V_R - Z_c I_R}{2} \cdot e^{-\gamma x} \right)$$

$$\rightarrow V(x) = \left(\frac{e^{\gamma x} + e^{-\gamma x}}{2} \right) \cdot V_R + \left(\frac{e^{\gamma x} - e^{-\gamma x}}{2} \right) \cdot Z_c \cdot I_R$$

\swarrow $\cosh(\gamma x)$ \searrow $\sinh(\gamma x)$

$$\text{So, } I(x) = \frac{1}{Z_c} \cdot \sinh(\gamma x) \cdot V_R + \cosh(\gamma x) \cdot I_R$$



$$V(x) = \overbrace{\cosh(\gamma x)}^A \cdot V_R + \overbrace{Z_c \cdot \sinh(\gamma x)}^B \cdot I_R$$

$$I(x) = \underbrace{\frac{1}{Z_c} \cdot \sinh(\gamma x)}_C \cdot V_R + \underbrace{\cosh(\gamma x)}_D \cdot I_R$$

$$* AD - BC = \cosh^2(\gamma l) - \sinh^2(\gamma l) = 1 \checkmark$$

$$\cosh(\alpha l + j\beta l) = \cosh(\alpha l) \cdot \cos(\beta l) + j \sinh(\alpha l) \cdot \sin(\beta l)$$

$$\sinh(\alpha l + j\beta l) = \sinh(\alpha l) \cdot \cos(\beta l) + j \cosh(\alpha l) \cdot \sin(\beta l)$$

$$V_s = \cosh(\gamma l) \cdot V_R + Z_c \cdot \sinh(\gamma l) \cdot I_R$$

$$I_s = \frac{1}{Z_c} \cdot \sinh(\gamma l) \cdot V_R + \cosh(\gamma l) \cdot I_R$$

$$\gamma = \sqrt{YZ} = \alpha + j\beta \rightarrow \begin{array}{l} \text{phase coefficient} \\ \swarrow \\ \text{loss coefficient} \end{array}$$

(Propagation Constant)

5.3: Equivalent π -Circuits.


$$Z = z \cdot l = (r + jx) \cdot l = R + jX$$

$$Y = y \cdot l = j\omega l C = jB$$



$$V_s = \left(1 + \frac{Y' \cdot Z'}{2}\right) \cdot V_R + Z' \cdot I_R$$
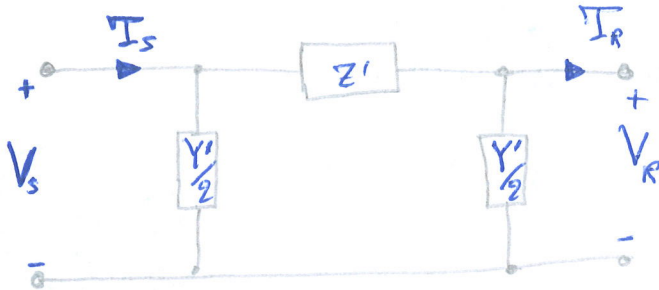
$$I_s = Y' \left(1 + \frac{Y' \cdot Z'}{4}\right) \cdot V_R + \left(1 + \frac{Y' \cdot Z'}{2}\right) \cdot I_R$$




$$\cosh(\gamma l) = 1 + \frac{Y' Z'}{2} \quad ; \quad Z_c \cdot \sinh(\gamma l) = Z'$$

$$Z' = \frac{Z \cdot \sinh(\gamma l)}{\gamma l}$$

$$\frac{Y'}{2} = \frac{Y}{2} \cdot \frac{\tanh(\gamma l/2)}{(\gamma l/2)}$$



Exercise:

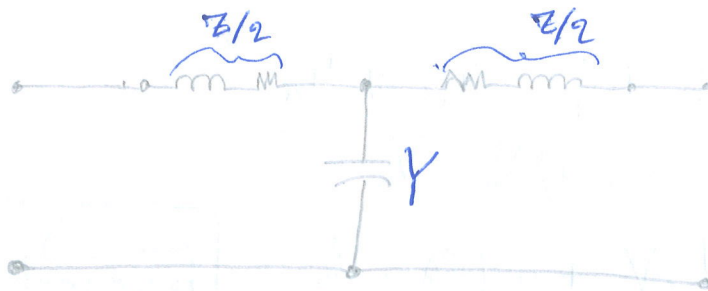

T-Model

Derive the ABCD constants of a T-equivalent in terms of Y & Z

5.4: Loss-less Lines:

$$Z_c = \sqrt{\frac{Z}{y}} = \sqrt{\frac{r + j\omega L}{j\omega C}} = \sqrt{\frac{L}{C}} = \sqrt{\frac{l \times \text{length}}{C \times \text{length}}} = \sqrt{\frac{l}{C}}$$

Surge impedance

$$\gamma = \sqrt{yz} = \sqrt{(j\omega C)(j\omega L)} = j\omega \sqrt{LC} = \alpha + j\beta$$

$$* A = \cosh(\gamma l) = \cosh(j\beta l) = \cos(\beta l) = D$$

$$* B = Z_0 \sinh(\gamma l) = j Z_0 \sin(\beta l)$$


$$* C = \frac{\sinh(\gamma l)}{Z_0} = j \frac{\sin(\beta l)}{Z_0}$$

wavelength: distance to change the angle by 2π

$$\text{So, } \beta \lambda = 2\pi$$

$$\hookrightarrow \lambda = \frac{2\pi}{\beta} = \frac{2\pi}{\omega \sqrt{LC}} = \frac{2\pi}{2\pi f \sqrt{LC}} = \frac{1}{f \sqrt{LC}}$$
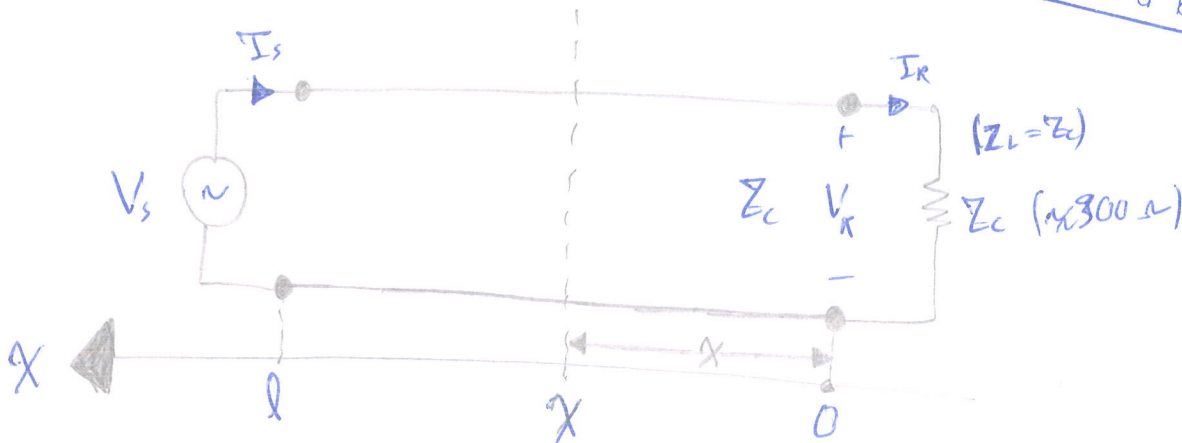
$$\left\{ \begin{array}{l} \text{Q) } f = 50 \text{ Hz ; } \lambda = 6324 \text{ km} \\ \text{Q) } f = 60 \text{ Hz ; } \lambda \approx 5000 \text{ km} \end{array} \right.$$



$$\bullet V(x) = \cos(\beta x) \cdot V_R + j Z_0 \sin(\beta x) \cdot I_R \quad \frac{V_R}{Z_0}$$

$$= (\cos(\beta x) + j \sin(\beta x)) \cdot V_R = V_R \cdot e^{j\beta x}$$

$$\bullet I(x) = j \frac{\sin(\beta x)}{Z_0} \cdot V_R + \cos(\beta x) \cdot \frac{V_R}{Z_0}$$

$$= \frac{V_R}{Z_0} [e^{j\beta x}]$$



• Steady-State Stability Limit,

$$P_{max} = V_s \cdot V_R \cdot P_{SSL} \cdot \frac{\sin(S_{max})}{\sin(\beta l)}$$

5.4

Missey +

97/10/2014

5.5: Maximum Power Flow

$$\bullet V_R = |V_R| \angle 0^\circ$$

$$\bullet V_S = |V_S| \angle \delta$$

$$\bullet S_R = V_R \cdot I_R^*$$

$$\bullet I_R = \frac{V_S - V_R}{Z'}$$

$$P_R = \operatorname{Re}(S_R)$$

$$= \frac{|V_S| \cdot |V_R|}{Z'} \cdot \cos(\theta_Z - \delta) - \frac{|V_R|^2}{Z'} \cdot \cos(\theta_Z)$$



$$Z' = |Z'| \angle \theta_Z \quad (\text{read the rest of solve example})$$

5.6: Line Loadability

- maximum power that can be sent down a transmission line for a specified voltage, and maximum angle.

Example 5.7: (data from Itaipu Project)

3000 MW

500 Km

60 Hz

$\delta_{\max} = 35^\circ$

$V_S = 1$

$V_R = 0.95$

- Determine the number of circuits at 345; 500 and 765 kV capable of transmission of power after one outage.

Solution:

$$Z_c = 297 \Omega @ 345 \text{ kV}$$

$$277 \Omega @ 500 \text{ kV}$$

$$266 \Omega @ 765 \text{ kV}$$



a) At 345 kV

$$P_{\text{SIL}} = \frac{345^2}{297} = 401 \text{ MW}$$

Three gorges

$$\bullet P_{\text{max}} = \frac{1 \cdot 0.95 \cdot 401 \cdot \sin(35^\circ)}{\sin\left(\frac{90^\circ}{5000} \cdot 500 = \frac{180}{\pi}\right)} = 401 \cdot (0.997) \rightarrow \text{able to transmit 92.7\% of the surge impedance}$$

$$= 372 \text{ MW/line}$$

$$\bullet N_{345} = \frac{3000}{372} + 1 = 24.2 + 1 = 25.2 \rightarrow 26 \text{ circuits (25 circuits are not enough)}$$

\hookrightarrow I need 13 towers in Parallel.

b) AL 500 kV

$$P_{STL} = \frac{500^2}{2.77} = 903 \text{ MW}$$

$$P_{max} = 903 \times 0.997 = 837 \text{ MW/line}$$

$$N_{500} = \frac{9000}{837} + 1 = 12$$



c) AL 765 kV


$$P_{STL} = \frac{(765)^2}{9.66} = 2200 \text{ MW}$$

$$P_{max} = 2200 \times 0.927 = 2039 \text{ MW/line}$$

$$N_{765} = \frac{9000}{2039} + 1 = 4.4 + 1 \approx 6$$

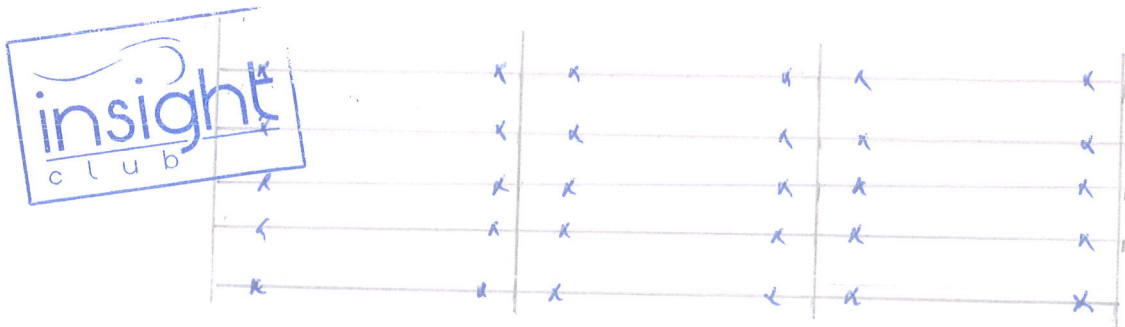Example 5.8:

Can 5 instead of 6 transmit the power if there are two intermediate substations that divide each line into 3 = 167 km sections.



$$X' = 266 \cdot \sin\left(\frac{2\pi}{5000} \times 500\right) = 156.4 \Omega$$

$$X_{eq} = \frac{1}{5} \left(\frac{X'}{3}\right) \times 2 + \frac{1}{4} \cdot \frac{X'}{3} = 33.88 \Omega$$

$$\frac{P}{max} = \frac{V_1 \cdot V_2}{X} \cdot \sin \delta_{max}$$

$$P_{max} = \frac{765 (765 \times 0.96)}{33.88} \cdot \sin(35^\circ)$$

Voltage @ receiving end

$$= 9412 \text{ MW}$$

5.7: Reactive Compensation Techniques.

- Capacitive Shunt Compensation: done at heavy loading when the system experiences low voltage.
- Placed near load.
- Capacitive Series Compensation: Placed in series with the transmission line to increase the line loadability.



Problems: ① High short circuit current, have to be diverted (disconnect the capacitance, short circuit it, should be bypassed).


② Subsynchronous resonance with machines (generators) inductance

③ Series compensation can go up to 75% of X' (series inductance of T.L.).

- Shunt Inductor Compensation: done at low loading when transmission system has an excess of reactive power. It is usually to protect the generator from absorbing too much reactive power.

- Synchronous Condenser (or Capacitor): takes active power from the grid (not operated by prime mover) and supplies reactive power only (or consumes reactive power only).

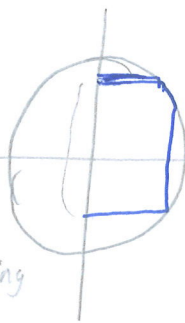machine operating on g-axis only supplying/absorbing reactive power.



It is a synchronous machine, producing zero power (no power to the grid (no-prime mover), gets its real power losses from the grid directly.

Problem: Costly; Cost is higher than static compensation.

Advantage: Controllability of the reactive power, without producing harmonics

