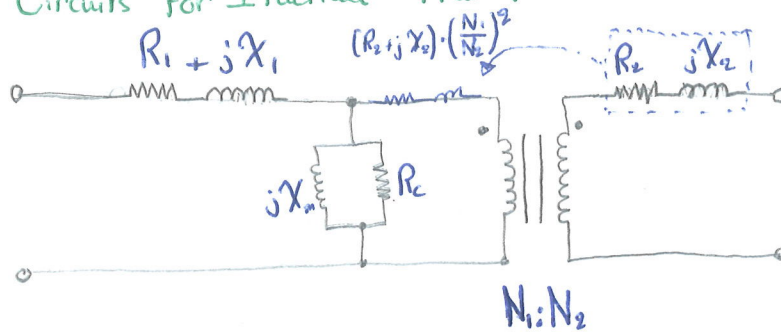



Chapter 3: Power Transformers



3.1: The Ideal Transformer (Self Studying)

3.2: Equivalent Circuits for Practical Transformers



* High level of Approximation: Removing Excitation Branch 
 it becomes only series reactance

Equivalent Circuit #1

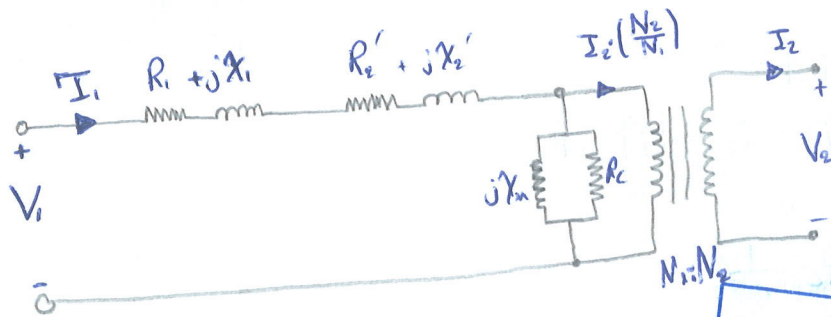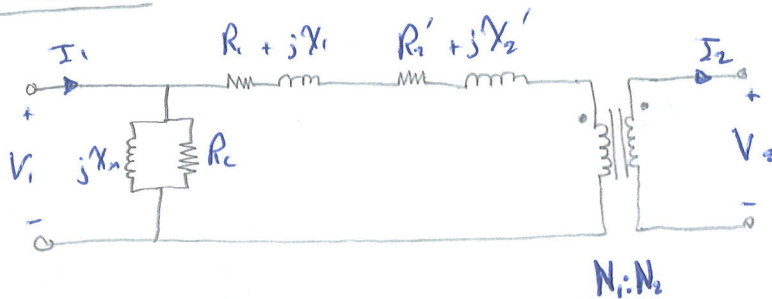

Short Circuit Test


- $V_{sc} \ll V_{rated}$
- $I_{sc} \approx I_{rated}$
- P_{sc}

get $\rightarrow R_{eq} + jX_{eq} = Z_{eq}$

$\rightarrow |Z_{eq}| = \frac{V_{sc}}{I_{sc}}$

$\rightarrow \cos \phi_{sc} = \frac{P_{sc}}{V_{sc} \cdot I_{sc}} \quad j \sin \phi_{sc}$


$\rightarrow R_{eq} + jX_{eq} = |Z_{eq}| * (\cos \phi_{sc} + j \sin \phi_{sc})$

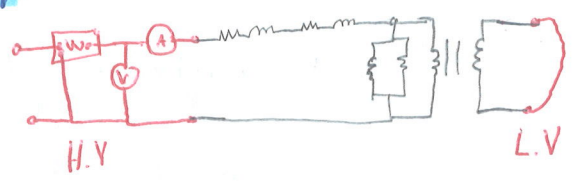

Note: * S.C Test: S.C the L.V side
& measure on H.V side

* O.C Test: O.C the H.V side
& measure on L.V side

Open Circuit Test:

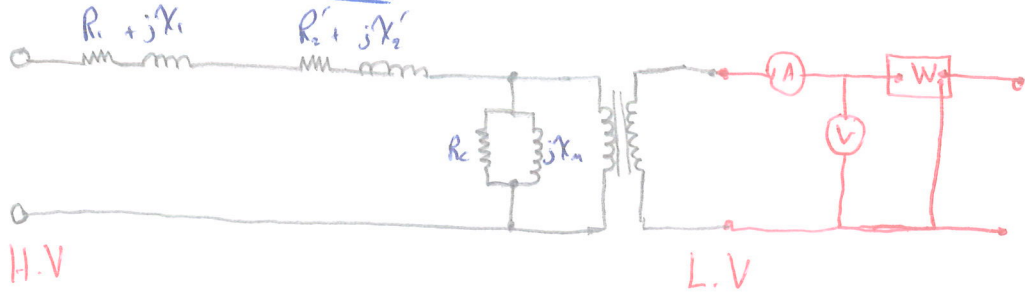

$V_{oc} = V_{rated(L.V)}$
 $I_{oc} \ll I_{rated(L.V)}$
 P_{oc}

$\left. \begin{array}{l} \\ \\ \end{array} \right\} \text{ together } \Rightarrow R_c + jX_m$

$\rightarrow Y = \frac{1}{R_c} + \frac{1}{jX_m}$

$\rightarrow |Y| = \frac{I_{oc}}{V_{oc}}$

$\rightarrow \cos \phi_{oc} = \frac{P_{oc}}{V_{oc} \cdot I_{oc}} ; \sin \phi_{oc}$

$\rightarrow Y = |Y| e^{-j\phi_{oc}}$
 $= \underbrace{|Y| \cos \phi_{oc}}_{G_c} + j \underbrace{|Y| \sin \phi_{oc}}_{B_m}$


$R_c = \frac{1}{G_c}$

$X_m = \frac{1}{B_m}$



* Saturation:

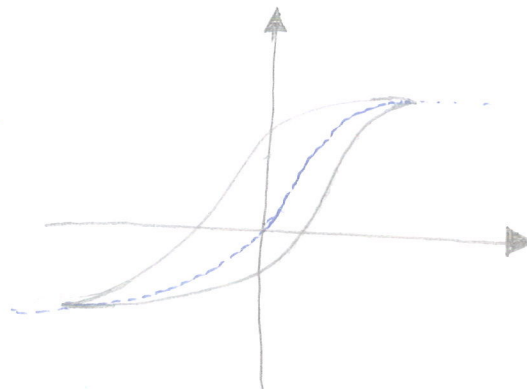- * Saturation lead to Harmonic due to excitation current
- * But its small, its neglected at calculation level but taken into consideration at design level



* Issues not represented in Equivalent Circuit

- 1- Saturation
- 2- Inrush Current
- 3- Non sinusoidal existing current
- 4- Surge phenomena



1- Saturation:

* Due to saturation trend in the BH curve of the laminations.

* This causes changes in the value of μ_r that makes L_m ($a^2 X_m$) dependent on applied voltage.

2- Inrush Current:

* Consider that $B(0)$ is some finite value ($= 1.9 \text{ Wb/m}^2$)
Tesla

* Faraday's law:


$$e = -NA \frac{dB}{dt}$$

when integrated it generates:

$$\int_0^t e dt = -NA \int_0^t dB$$

$$e(t) = -NA (B(t) - B(0))$$

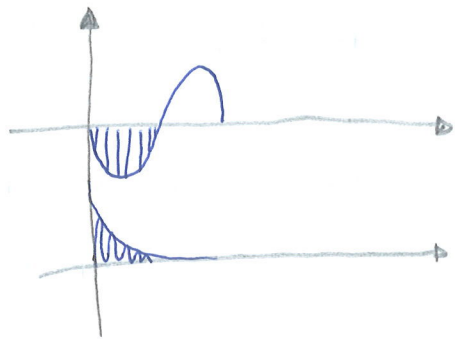
$$\rightarrow B(t) = -\frac{1}{NA} \int_0^t e(t) dt + B(0)$$



* This causes $B(t)$ to be larger than usual, resulting to a very high current flowing - distortion

3- Non sinusoidal exciting current

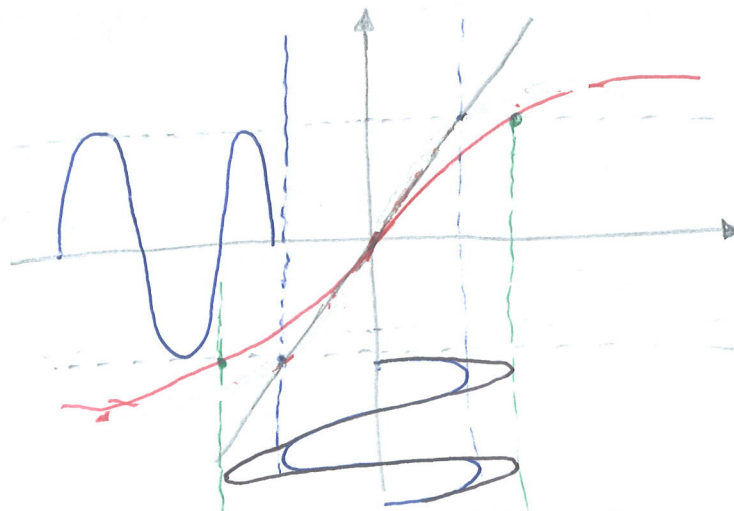
* Non-sinusoidal exciting current contains fundamental and harmonics. The dominant harmonic is the 3rd, with about 40%. This is neglecting in steady state analysis, because the excitation current is a 5% of the rated current.



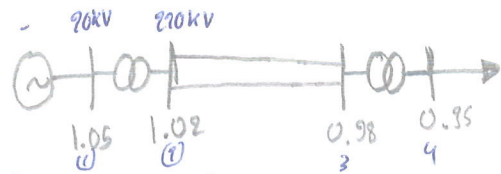
3.3: The Per Unit System

Advantages:

• By proper selection of base quantities, the transformer equivalent circuit is simplified (the ideal transformer disappears)



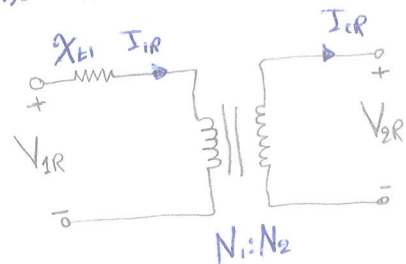Actual voltage (1) = $20kV \cdot 1.05$
 Actual voltage (2) = $220kV \cdot 1.02$
 Actual voltage (3) = $220kV \cdot 0.98$



$$S_R = V_{1R} \cdot I_{1R} = V_{2R} \cdot I_{2R}$$

$$V_{1R} = 11 kV$$

$$V_{2R} = 220 kV$$

$$S_R = 10 MVA \Rightarrow I_{1R} = \frac{10000 kVA}{11 kV} = 909.1 A = 0.909 kA$$

$$I_{2R} = \frac{10000 kVA}{220 kV} = 45.5 A$$

1) Select a scale for power: S_B (arbitrary)
 → usually S_R

2) Select a base for the voltage on one side: V_{B1}
 $V_{B1} = V_{1R}$ (usually selected at rated voltage but it is in general arbitrary)

3) Voltage base on side 2 is selected according to transformer turns rating: $V_{B2} = V_{B1} \cdot \frac{N_2}{N_1}$ (no choice)
 → in this case ($V_{B2} = V_{2R}$)



Per unit Calculations:

$$E_1 (kV) = 10.5 kV$$

$$\hookrightarrow E_1 (pu) = \frac{10.5 kV}{11 kV} = 0.95 pu$$

$$E_2 (kV) = 10.5 \cdot \frac{220}{11}$$

$$\hookrightarrow E_2 (pu) = \left(\frac{10.5 \cdot 220}{11} \right) \cdot \frac{1}{11 \cdot \frac{220}{11}} = \frac{10.5}{11} = 0.95 pu$$

$$I_1 = 500 A$$


$$\hookrightarrow I_1 (pu) = \frac{I_1}{I_{B1}}$$

$$= \frac{500}{909} = 0.55 pu$$

$$I_{B1} = \frac{S_B}{V_{B1}} = \frac{10000 kVA}{11 kV} = 909 A$$

$$I_2 (pu) = \frac{I_2 (A)}{I_{B2}} = \left(I_1 (A) \cdot \frac{N_1}{N_2} \right) \cdot \frac{1}{\left(I_{B1} \cdot \frac{N_1}{N_2} \right)} = \frac{I_1 (A)}{I_{B1}} = I_1 (pu)$$
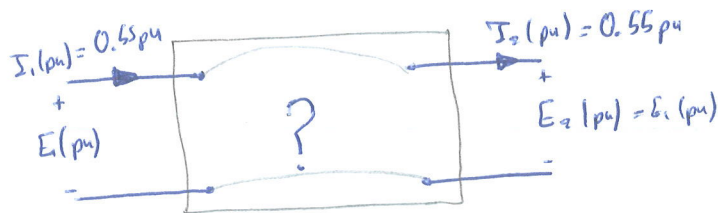
$$\left. \begin{aligned} E_1 (pu) &= E_2 (pu) \\ E_2 (pu) &= \frac{E_2 (kV)}{V_{B2}} \\ &= \left(E_1 (kV) \cdot \frac{N_2}{N_1} \right) \cdot \frac{1}{V_{B1} \cdot \left(\frac{N_2}{N_1} \right)} \\ &= \frac{E_1 (kV)}{V_{B1}} = E_1 (pu) \end{aligned} \right\}$$



$$X_{B1} = X_1 \cdot \frac{V_{B1}}{I_{B1}}$$

$$\rightarrow Z_B = \frac{V_{B1}^2}{S_B}$$

if $S'_B = 2S_B$

$E_1(pu)$ same

$E_2(pu)$ same

$$I'_{B1} = \frac{S'_B}{V_B} ; \neq 2$$

$$\rightarrow I_1(pu) = \frac{I_1(p)}{I'_{B1}} ; \div 2$$

$$\rightarrow I_2(pu) \div 2$$

$$X'_{B1} = \frac{V_{B1}^2}{S'_B} ; \div 2$$

$$\rightarrow X_{B1}(pu) = \frac{X_{B1}}{X'_{B1}} ; \neq 2$$



Per Unit System for 1- ϕ circuits:

S_B selected

V_{B1} selected

$$\rightarrow V_{B2} = V_{B1} \left(\frac{N_2}{N_1} \right) = V_{B1} \left(\frac{V_{R2}}{V_{R1}} \right)$$

$$\rightarrow I_{B1} = \frac{S_B}{V_{B1}}$$

$$\rightarrow I_{B2} = \frac{S_B}{V_{R2}} = I_{B1} \left(\frac{V_{B1}}{V_{R2}} \right) = I_{B1} \cdot \left(\frac{V_{R1}}{V_{R2}} \right)$$

$$\rightarrow Z_{B1} = \frac{V_{B1}}{I_{B1}} = \frac{V_{B1}^2}{S_B}$$

$$\rightarrow Z_{B2} = \frac{V_{B2}^2}{S_B}$$

$$\left. \begin{array}{l} \cdot \frac{Z_{B2}}{Z_{B1}} = \frac{V_{B2}^2}{V_{B1}^2} \\ \cdot Z_{pu} = \frac{Z_{a1}}{Z_{B1}} = \frac{Z_{a2}}{Z_{B2}} \end{array} \right\}$$

N.B: 3 ϕ voltage quoted is the (line-line) voltage

$$Z_{pu} \rightarrow V_{B1} ; S_{B1}$$

$$Z_{pu} \rightarrow V'_{B1} ; S'_{B1} \left\} Z'_{pu} = Z_{pu} \cdot \frac{V_{B1}^2}{S_{B1}} \cdot \frac{S'_{B1}}{V'^2_{B1}}$$

Per Unit System for 3- ϕ circuits

$S_{B(3\phi)}$; selected arbitrary

$V_{B1} = V_{BLL}$; selected arbitrary

$$\rightarrow V_{B2} = V_{B1} \left(\frac{V_{R2}}{V_{R1}} \right)$$

$$\rightarrow I_{B1} = \frac{S_{B(3\phi)}}{3 \cdot \frac{V_{B1}}{\sqrt{3}}} = \frac{S_{B(3\phi)}}{\sqrt{3} V_{B1}}$$

; base value of line current $I_{pu(\Delta)} = I_{pu(Y)}$

$$\rightarrow Z_{B1} = \frac{V_{B1}}{\frac{\sqrt{3} \cdot S_{B(3\phi)}}{\sqrt{3} V_{B1}}} = \frac{V_{B1}^2}{S_{B(3\phi)}}$$

; Z_B in the Y




$$Z_{B1}(\Delta) = \frac{V_{B1}}{I_{B1}(\Delta)}$$

$$I_{B1} = \sqrt{3} I_{B1}(\Delta)$$


$$I_{B1}(\Delta) = \frac{S_B(3\phi)}{3V_{B1}}$$

$$Z_{B1}(\Delta) = \frac{V_{B1}}{I_{B1}(\Delta)} = \frac{V_{B1}}{\frac{S_B(3\phi)}{3V_{B1}}} = \frac{\sqrt{3} V_{B1}(L-N)}{\frac{S_B}{\sqrt{3}}} = 3 Z_{B1} \quad Z_{B1}(\Delta) = 3 Z_{B1}$$

$$\sum_{pu} (Y) = \frac{Z_Y}{Z_{B1}} = \frac{Z_{\Delta}}{3} \cdot \frac{3}{Z_{B1}(\Delta)} = \sum_{pu} (\Delta)$$

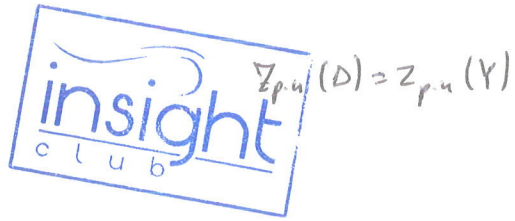

Example 3.23

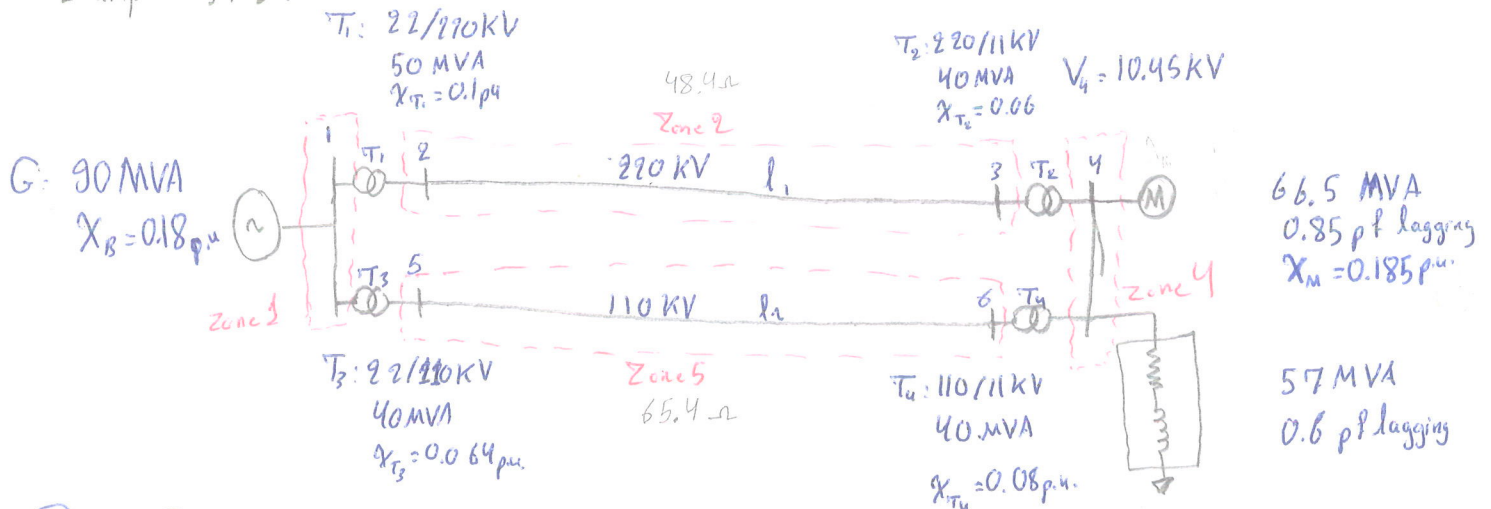

Base Quantities

$$\left. \begin{aligned} S_B &= 100 \text{ MVA} \\ V_{B1} &= 22 \text{ kV} \\ V_{B2} &= 220 \text{ kV} \\ V_{B4} &= 11 \text{ kV} \\ V_{B5} &= 110 \text{ kV} \end{aligned} \right\} \text{ free choices}$$



Z_{Base} for each zone

$$Z_{B1} = \frac{22^2}{100} = 4.84 \Omega$$

$$Z_{B2} = \frac{220^2}{100} = 484 \Omega$$

$$Z_{B4} = \frac{11^2}{100} = 1.21 \Omega$$

$$Z_{B5} = \frac{110^2}{100} = 121 \Omega$$

Impedance in Per Unit

$$X_B(p.u.) = 0.18 \times \frac{1}{S} \times \frac{1}{V^2} = 0.18 \times \frac{1}{90} \times \frac{22^2}{100} = 0.2 \text{ p.u.}$$

$$X_{T1}(p.u.) = 0.1 \times \frac{220^2}{50} \times \frac{1}{220^2} = 0.2 \text{ p.u.} = 0.1 \times \frac{22^2}{50} \times \frac{1}{22^2}$$

referred to 11 kV side

referred to L.V. side


$$X_{T2}(p.u.) = 0.06 \times \frac{220^2}{40} \times \frac{1}{220^2} = 0.15 \text{ p.u.}$$

$$X_{T3}(p.u.) = 0.064 \times \frac{110^2}{40} \times \frac{1}{110^2} = 0.16 \text{ p.u.}$$

- $X_{T_1}(\text{p.u.}) = 0.08 \times \frac{110^2}{40} \cdot \frac{1}{\frac{110^2}{40}} = 0.2 \text{ p.u.}$
- $X_{T_2}(\text{p.u.}) = \frac{48.4}{484} = 0.1 \text{ p.u.}$
- $X_{T_3}(\text{p.u.}) = \frac{65.4}{121} = 0.54 \text{ p.u.}$
- $X_{T_4}(\text{p.u.}) = 0.185 \times \frac{100}{66.5} = 0.277 \text{ p.u.}$

Voltage in p.u. on motor & load (mode 4)
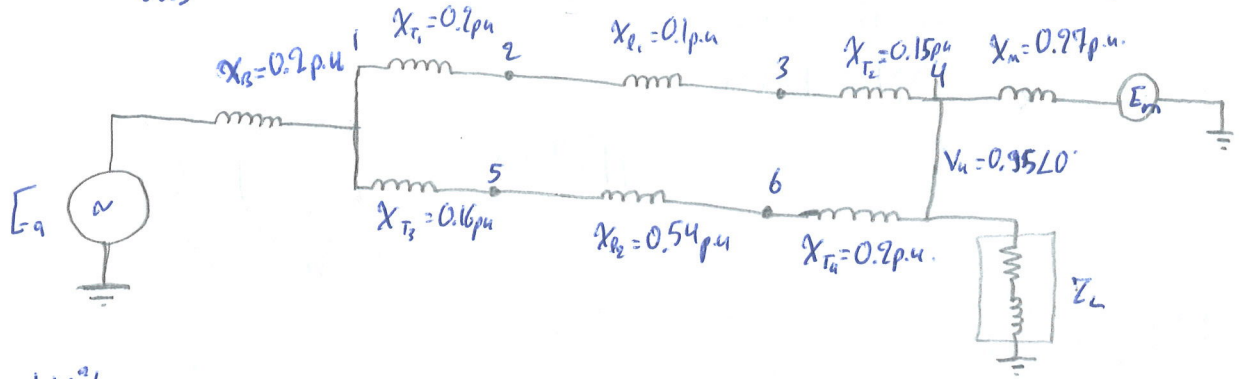
$$V_4 = \frac{10.45}{11} = 0.95 \text{ p.u.}$$



$$Z_L = \frac{|V_u|^2}{S^*} \quad (-L)$$

$$S_L = 5.7 \angle [0.6 + j \sin[\cos^{-1}(0.6)]]$$

$$Z_L = \frac{0.95^2}{0.57(0.6 - j0.8)}$$

→ ? lagging? No → $P + jQ = V \cdot I^*$
 $P - jQ = \frac{V^2}{Z_L}$

$$Z_M = \frac{|V_u|^2}{S_u^*} = \frac{0.95^2}{\frac{66.5}{100} (0.85 - j0.53)}$$

* Calculate Active & Reactive Current delivered by the Generator

$$\begin{aligned} \cdot I_T &= I_M + I_L = I_{T_1} + I_{T_2} = I_G \\ &= \frac{0.95 \cdot \frac{66.5}{100} (0.85 - j0.53)}{0.95^2} + \frac{0.57(0.6 - j0.8)}{0.95} \\ &= 0.955 - j0.851 \end{aligned}$$




$$\begin{aligned} \cdot S_G &= V_1 \cdot I_G^* \\ V_1 &= V_u + \Delta V_B = 0.9 + 0.253 + j0.287 = 1.203 + j0.287 = 1.24 \angle 14^\circ \\ \Delta V_B &= j X_{T(\text{eq})} \cdot I_T = 0.253 + j0.287 \\ X_{T(\text{eq})} &= (X_{T_1} + X_{T_2} + X_{T_3}) // (X_{T_4} + X_{T_5} + X_{T_6}) \\ &= 0.3 \text{ p.u.} \end{aligned}$$

$$\cdot S_G (\text{MVA}) = S_G \cdot S_B$$

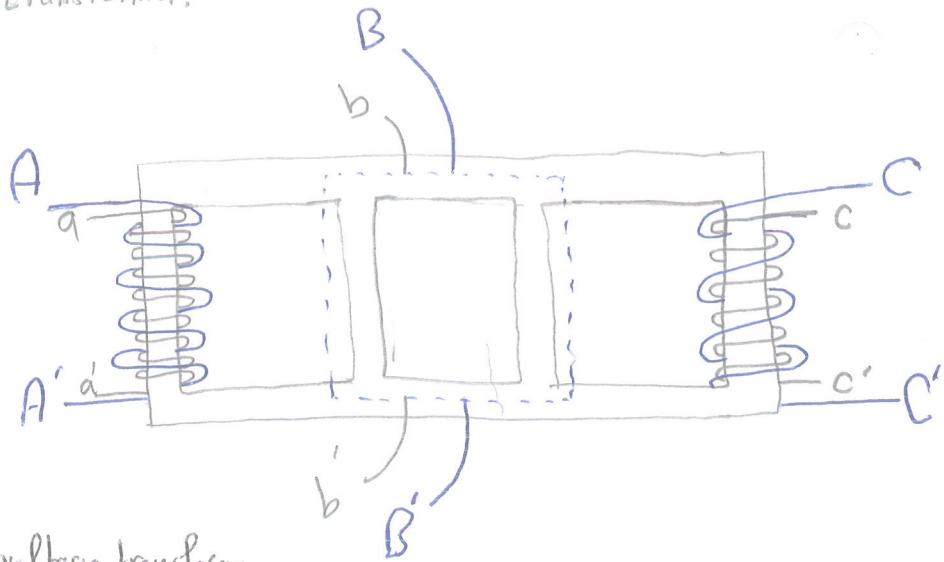
3.4: Three Phase Transformers Connection and Phase Shift

* Four Ways to Connect Transformer:





- Wye - Wye
- Delta - Delta
- Delta - Wye
- Wye - Delta




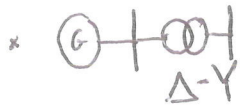N.B: * Y-Y → Too extra High voltage transformer
 → $a = \frac{N_1}{N_2} = \left(\frac{1}{h}\right)$
 → no phase shift





* Δ-Y : Configuration

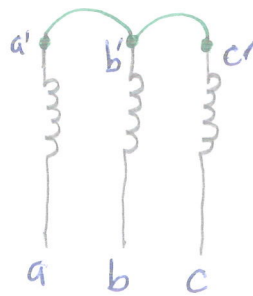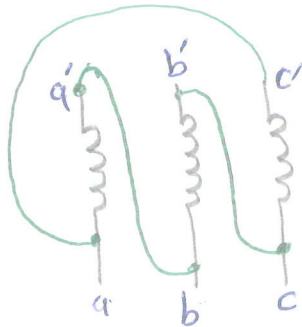
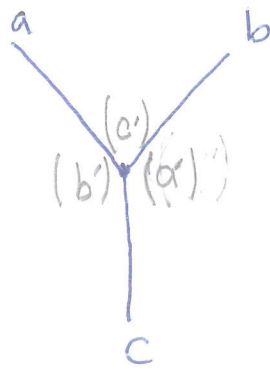
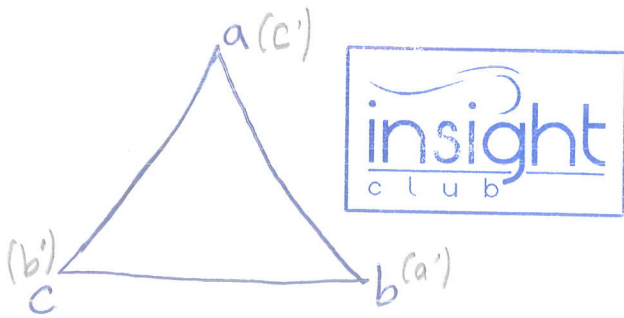


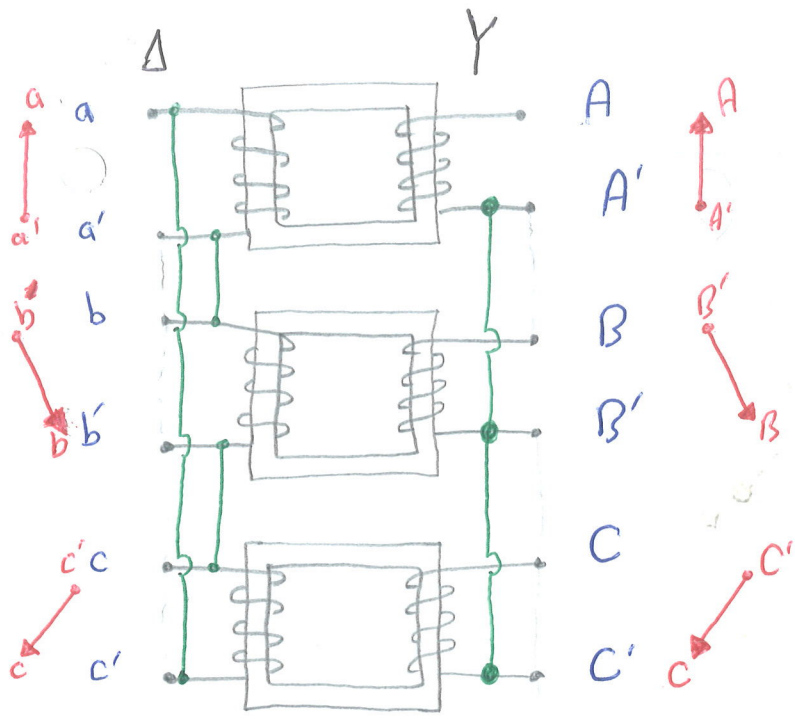


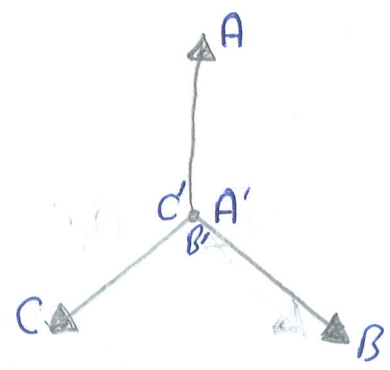
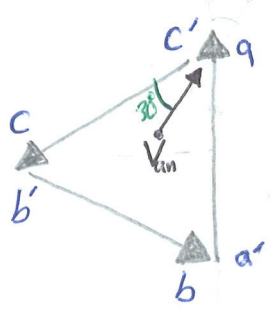
N.B: $c'c$ inphase $C'C$
 $b'b$ inphase $B'B$



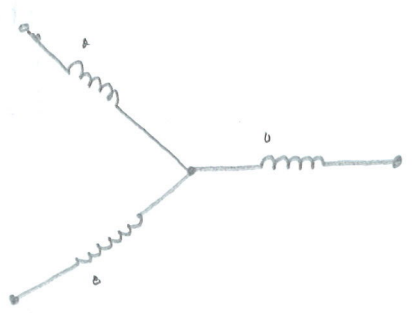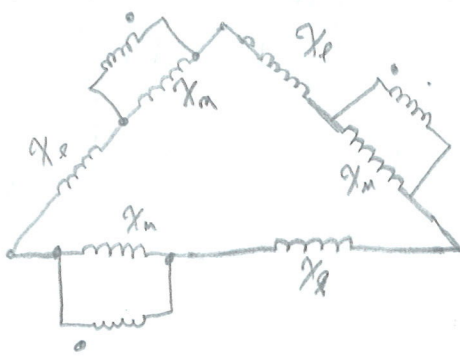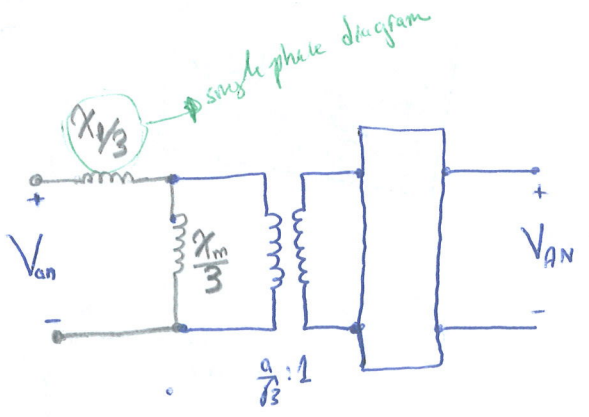N.B.:
 $V_{ab} = a V_{AN}$
 $V_{an} \sqrt{3} e^{j30^\circ} = a V_{AN}$





* Y-Δ : Configuration

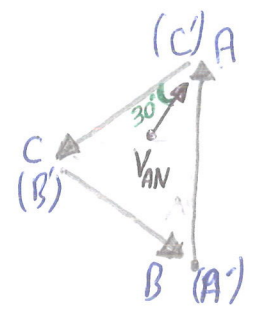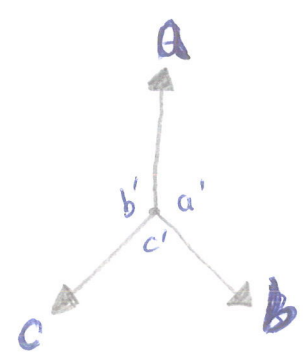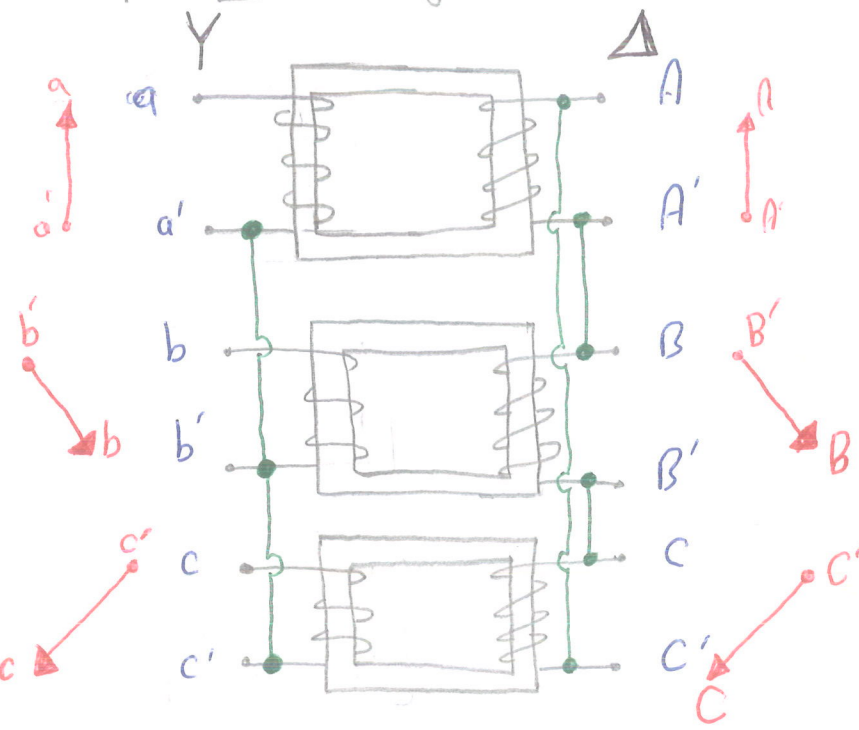

N.B.:

- $V_{ac'} = a V_{AA'}$
- $V_{an} = a V_{AN} \cdot \sqrt{3} e^{j30}$

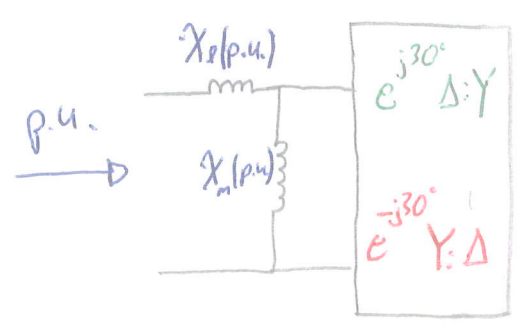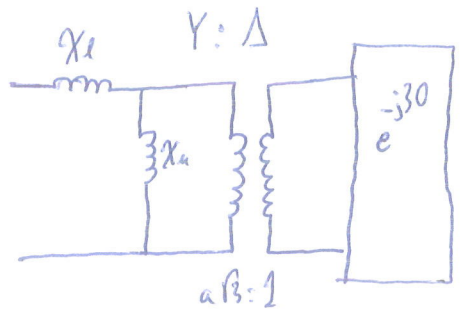• If H.V. side leads L.V. side by 30° , then it's American Standard.



* Three Winding Transformers
used for connection of shunt capacitors and inductors



$$Q = \frac{V^2}{X(\Omega)} \text{ (MVar)}$$



$$= V^2 \cdot Y$$

where Y is admittance. Note: when $V \uparrow$, $Y \downarrow$ then $C \downarrow$



$$N_1 I_1 = N_2 I_2 = N_3 I_3$$
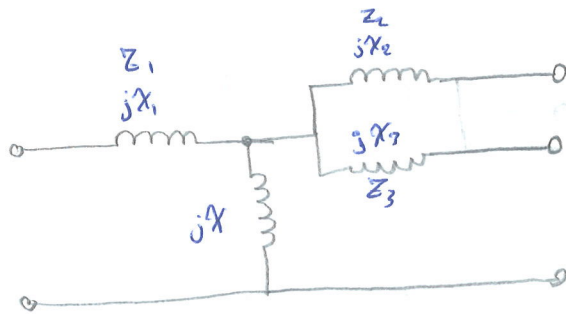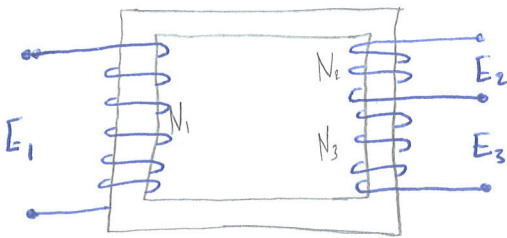
$$\frac{E_1}{N_1} = \frac{E_2}{N_2} = \frac{E_3}{N_3}$$



* Short Circuit Test \rightarrow leakage impedance

$Z_{12} = Z_1 + Z_2$ p.u. leakage impedance
measured from coil w_1 with w_2 shorted
with w_3 opened

$Z_{13} = Z_1 + Z_3$ p.u. leakage impedance
measured from coil w_1 with w_3 shorted
with w_2 opened

$Z_{23} = Z_2 + Z_3$ p.u. leakage impedance
measured from coil w_2 with w_3 shorted
with w_1 opened



$$Z_1 = \frac{1}{2} (Z_{12} + Z_{13} - Z_{23})$$

$$Z_2 = \frac{1}{2} (Z_{12} + Z_{23} - Z_{13})$$

$$Z_3 = \frac{1}{2} (Z_{13} + Z_{23} - Z_{12})$$

Example 3.9: Single Phase 3 winding Transformer

- w 1: 3000 MVA; 13.8 kV
- w 2: 300 MVA; 199.2 kV
- w 3: 50 MVA; 19.92 kV



- $X_{12} = 0.1$ p.u. on 300 MVA; 13.8 kV base
- $X_{13} = 0.16$ p.u. on 50 MVA; 13.8 kV base
- $X_{23} = 0.14$ p.u. on 50 MVA; 199.2 kV base




* Find X_1 ; X_2 ; X_3 referred to $S_B = 300$ MVA

$$\begin{aligned}
 Z_{R(1)} &= \frac{13.8^2}{300} = 0.634 \Omega \\
 Z_{R(2)} &= \frac{13.8^2}{50} = 3.8 \Omega \\
 Z_{R(3)} &= \frac{199.2^2}{50} = 793.6 \Omega
 \end{aligned}
 \quad \left| \quad S_B = 300 \text{ MVA}$$

$$\begin{aligned}
 \rightarrow X_{12} &= 0.16 \cdot \frac{300}{50} = 0.96 & Z'_{R1} &= \frac{13.8^2}{300} = 0.634 \\
 \rightarrow X_{23} &= 0.14 \cdot \frac{300}{50} = 0.84
 \end{aligned}$$




Example 3.10

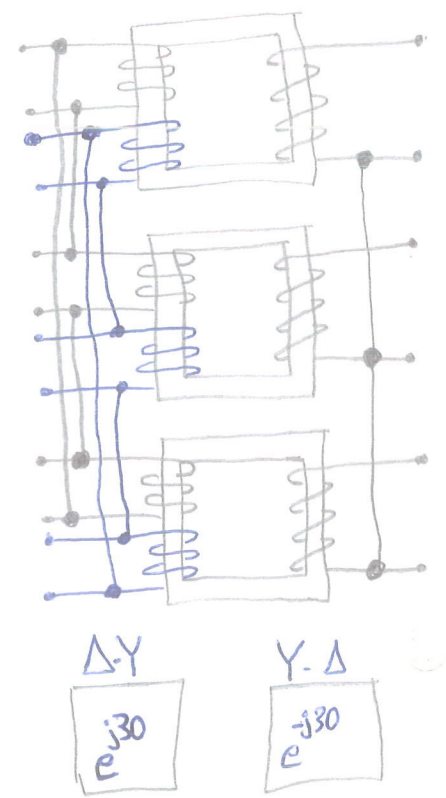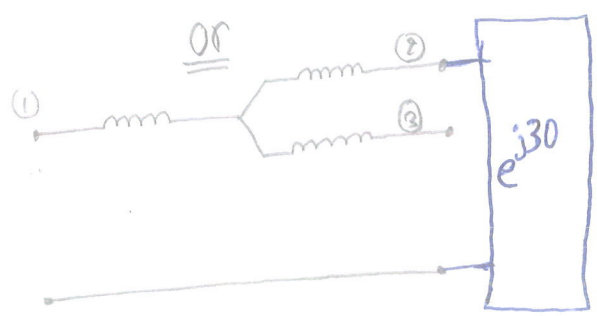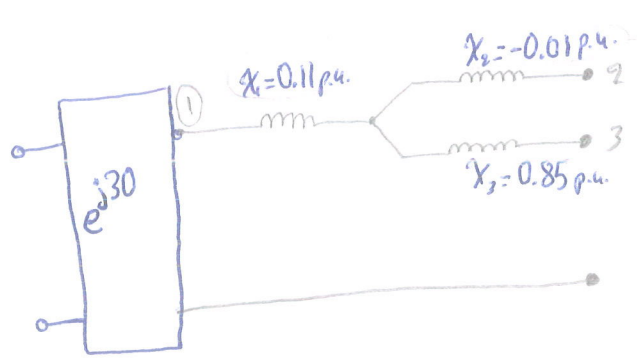- 13.8 kV winding (X): Δ to generator
- 199.2 kV winding (H): Y-grounded connected to 345 kV line (199.2/345)
- 19.92 kV winding (M): Y-grounded to 34.5 kV



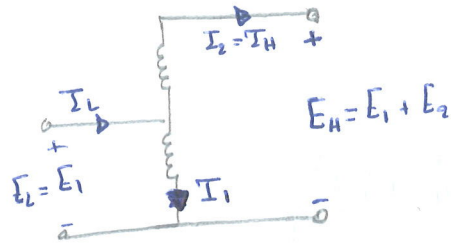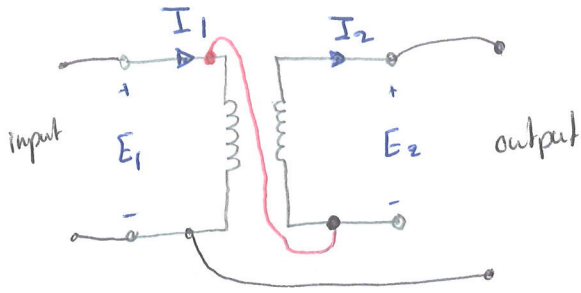
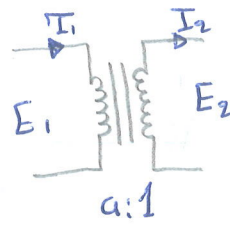
3.7: Auto transformers

$$S_k = E_1 I_1 = E_2 I_2 \quad (\text{rated VA of transformer})$$



$$S_a = E_1 (I_1 + I_2) = E_1 (I_1 + a I_1) = E_1 I_1 (1 + a)$$

$$S_a = S_k (1 + a)$$

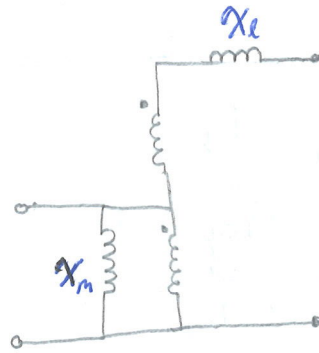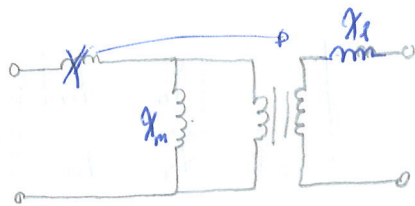

$$X_2(\text{p.u.}) = X_2 \cdot \frac{I_2}{E_2}$$

$$X_2(\text{p.u.}) = X_2 \cdot \frac{I_2}{E_1 + E_2} = \frac{I_2}{E_2(1+a)}$$

$$\frac{E_1}{E_2} = a$$

$$X_m(\text{p.u.}) = X_m \cdot \frac{I_1}{E_1}$$

$$X_m(\text{p.u.}) = X_m \cdot \frac{I_1 (1+a)}{E_1}$$

3.8: Transformers with off-Nominal turns Ratio.

13.8/345 KV (American Standards)





345 KV
348 KV



$$c = \frac{345}{348} = 0.99$$

on-nominal tap ratio

Slickious transformer to raise voltage

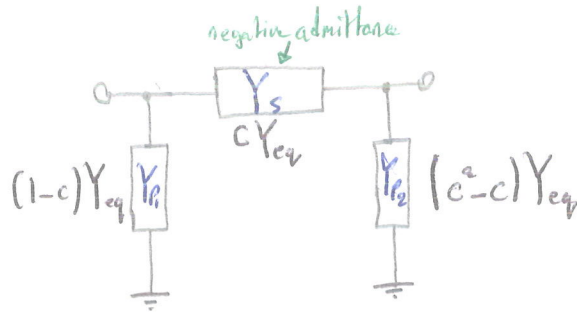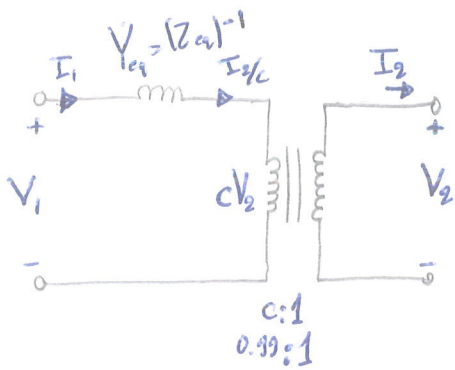

$$\frac{I_2}{c} = (V_1 - cV_2) Y_{eq}$$

$$I_2 = (cV_1 - c^2V_2) Y_{eq}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{eq} & -cY_{eq} \\ cY_{eq} & -c^2Y_{eq} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$



$$Y_{11} = Y_s + Y_{p1} = Y_{eq}$$

$$Y_{12} = Y_{21} = -cY_{eq} = -Y_s$$

$$Y_{22} = Y_s + Y_{p2} = c^2Y_{eq}$$



$$\begin{bmatrix} I_1 \\ -I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ -Y_{21} & -Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$