

Chapter 2: Fundamentals

2.1: Phases


$$v(t) = V_{\max} \cdot \cos(\omega t + \delta)$$

phasor transformation
if all signals have same frequency

$$\frac{V_{\max}}{\sqrt{2}} \cdot e^{j\delta} = \frac{V_{\max}}{\sqrt{2}} \angle \delta$$

$$= \frac{V_{\max}}{\sqrt{2}} (\cos \delta + j \sin \delta)$$
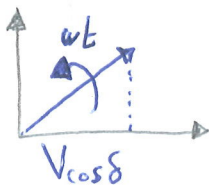
$$v(t) = \sqrt{2} \cdot V \cdot \cos(\omega t + \delta) \quad \xleftarrow{\rho^{-1}}$$



Time domain signal is obtained by rotating phasor at given regular speed ω .




2.2: Instantaneous Power in Single Phase AC circuits


General RLC Loads

$$* v(t) = V_{\max} \cdot \cos(\omega t + \delta)$$
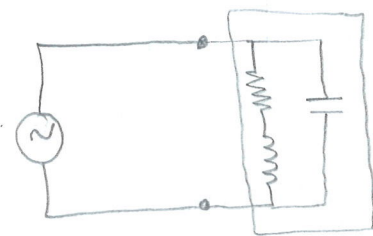
$$* i(t) = I_{\max} \cdot \cos(\omega t + \beta)$$



General RLC Load

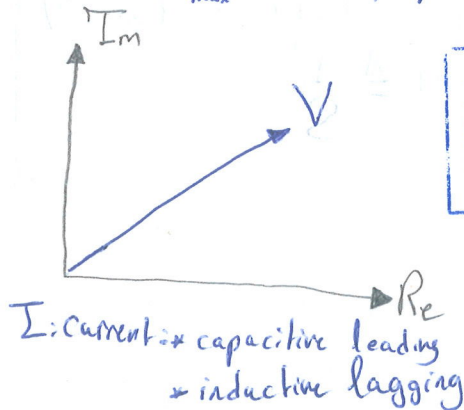

Note: phasor domain should be in "cosine" format

$$* P(t) = v(t) \cdot i(t)$$

$$= \frac{1}{2} V_{\max} \cdot I_{\max} [2 \cos(\omega t + \delta) \cdot \cos(\omega t + \beta)]$$


$$P = V \cdot I \cdot \cos(\delta - \beta) \{ 1 + \cos[2(\omega t + \delta)] \}$$

$$+ V \cdot I \cdot \sin(\delta - \beta) \cdot \sin[2(\omega t + \delta)]$$

$$= P_o [1 + \cos(2(\omega t + \delta))] + Q \cdot \sin(2(\omega t + \delta))$$

$$V = \frac{V_{\max}}{\sqrt{2}}$$

$$I = \frac{I_{\max}}{\sqrt{2}}$$

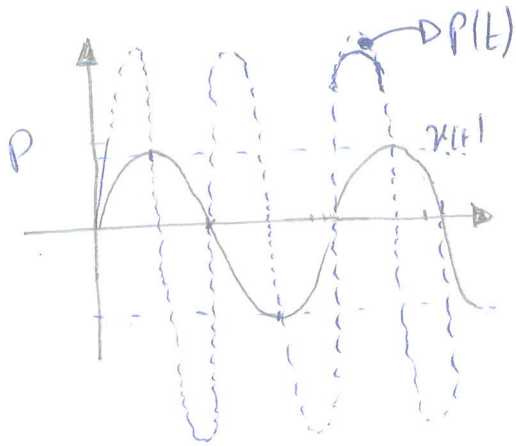

Note: Inductive Load consumes positive reactive power.

* Capacitive Load ^{generate positive} consumes negative reactive power.



2.3: Complex Power

$$\vec{V} = V e^{j\delta}$$

$$\vec{I} = I e^{j\beta}$$

Define Complex power S as :

$$S \triangleq V \cdot I^* = (V e^{j\delta}) (I e^{j\beta})^*$$

$$= V I e^{j(\delta - \beta)}$$

$$= V I [\cos(\delta - \beta) + j \sin(\delta - \beta)]$$

$$= P + jQ$$



$$S = P + jQ$$

$$P(t) = P \cdot [1 + \cos(2\omega t + \delta)]$$

$$+ Q \cdot [\sin(2\omega t + \delta)]$$

$$V \cdot I^* = P + jQ$$

Note: power factor = $\cos(\delta - \beta)$


$$PF \triangleq \frac{P}{S}$$

Example 2.3

* 100 KW at 0.8 pf lagging

* $Q_c = ?$ to make pf = 0.95 lagging


Before Adding Capacitor

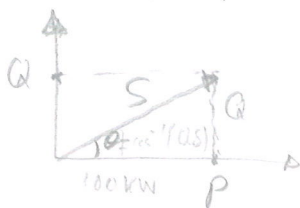

$$\theta_L = \delta - \beta = \cos^{-1}(0.8) = 36.9^\circ$$

$$Q_L = P_L \cdot \tan(\theta_L) = 100 \cdot \tan(36.9) = 75 \text{ KVAR}$$
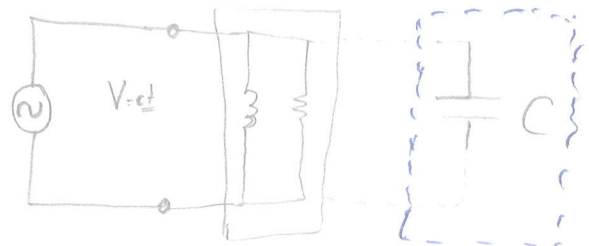
$$S_L = \frac{P}{\cos(\theta_L)} = 125 \text{ KVA}$$





After Adding Capacitor

$$\theta_{\text{system}} = \delta - \beta_s = \cos^{-1}(0.95) = 18.2^\circ$$

$$Q_s = P_L \cdot \tan(\theta_s) = 32.89 \text{ KVAR}$$

$$|S_s| = \frac{P_L}{\cos \theta_s} = 105.3 \text{ KVA}$$
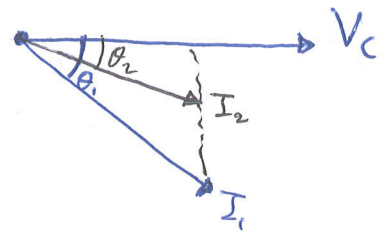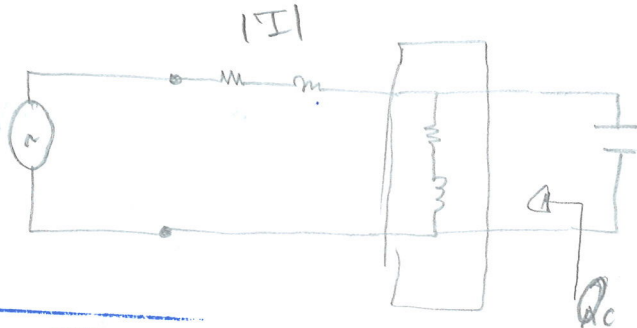
$$Q_c = Q_L - Q_s = 75 - 32.89 = 42.1 \text{ KVAR}$$




$$\times |I_C|^2 R < |I_L|^2 R$$


$$\times P_1 = V_L (I_L \cos \theta_1)$$

$$V_{\text{ref}} \quad P_2 = V_L \cdot I_L \cos \theta_2$$

2.5 Balanced 3-Φ circuits

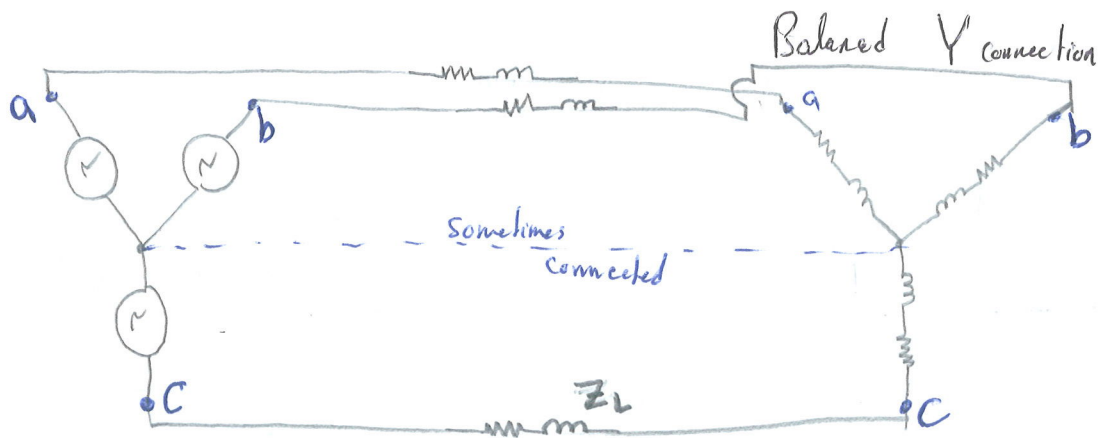
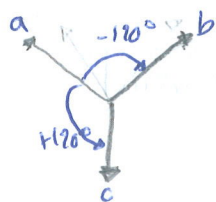
$$\begin{aligned} * E_a &= E \angle 0^\circ \\ * E_b &= E \angle -120^\circ \\ * E_c &= E \angle +120^\circ \end{aligned}$$




$$\left. \begin{aligned} I_a &= \frac{E_a}{Z_L + Z_Y} \\ I_b &= \frac{E_b}{Z_L + Z_Y} \\ I_c &= \frac{E_c}{Z_L + Z_Y} \end{aligned} \right\} \begin{aligned} I_a &= I \angle -\theta_2 \\ I_b &= I \angle -120^\circ - \theta_2 \\ I_c &= I \angle -240^\circ - \theta_2 \end{aligned}$$

example


$$E_{ab} = \sqrt{3} \cdot E_a \cdot e^{j30^\circ} = \sqrt{3} E \angle 30^\circ = E_{an} - E_{bn}$$

$$E_{bc} = \sqrt{3} \cdot E \cdot e^{j(30^\circ - 120^\circ)} = \sqrt{3} E \angle 30^\circ - 120^\circ$$
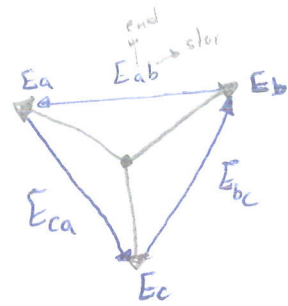
$$E_{ca} = \sqrt{3} E \angle 30^\circ - 240^\circ$$




Balanced Δ Connection

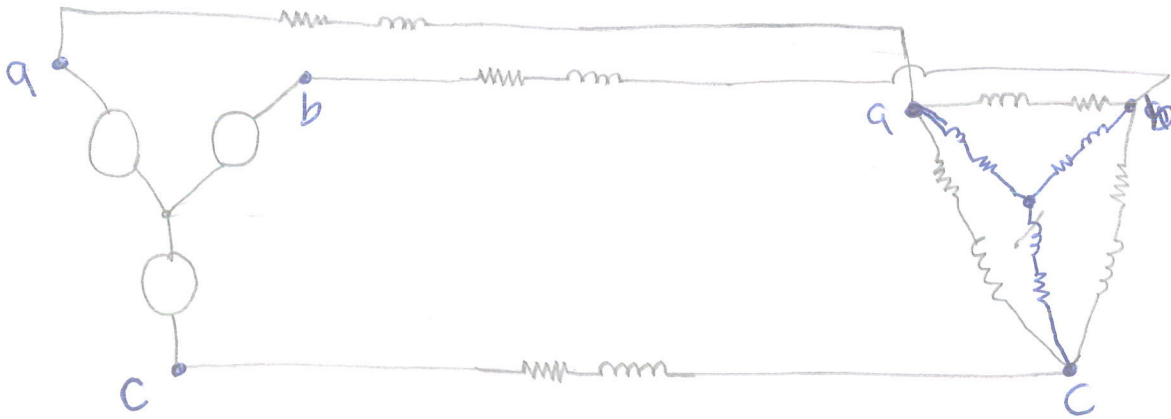

Verify that $I_a + I_b + I_c = 0$ for a Δ -connected Load by considering KCL at Nodes A, B, C at load side

$$I_c = I_{AB} - I_{CA}$$

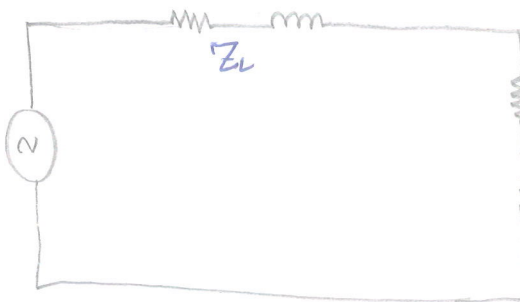

Z_Y or equivalent Z_Y of Δ -load

2.6: Power in Balanced 3- ϕ Circuit



$$V_{an}(t) = \sqrt{2} V_m \cos(\omega t + \delta) \quad \begin{matrix} -120^\circ \\ -240^\circ \end{matrix}$$

$$I_a(t) = \sqrt{2} I_m \cos(\omega t + \beta) \quad \begin{matrix} -120^\circ \\ -240^\circ \end{matrix}$$

$$P(t) = V_{an} i_a + V_{bn} i_b + V_{cn} i_c$$

$$= 3 V_m I_m \cos(\delta - \beta) + V_m I_m \left[\cos(9\omega t + \delta + \beta) + \cos(9\omega t + \delta + \beta - 120^\circ) + \cos(9\omega t + \delta + \beta - 240^\circ) \right]$$

$\rightarrow 0$ $\text{Zero } V_b$

Complex Power

$$V_{an} = V_{en} \angle \delta$$

$$I_a = I_e \angle \beta$$

$$S_a = V_{an} I_a^* = V_{en} I_e \angle \delta - \beta$$

$$S_b = V_{bn} I_b^* = V_{en} I_e \angle \delta - \beta$$


$$S_c = V_{cn} I_c^* = V_{en} I_e \angle \delta - \beta$$

Same on all phases.

Problems

Problem 2.21

a) $Q_c = ?!$

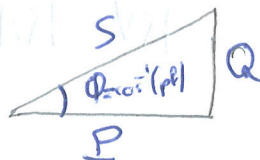


Load

$$\frac{Q_L}{P} = \tan \phi = \tan [\cos^{-1}(0.9)]$$

$$\rightarrow Q_L = 1000 \text{ kW} \times \tan [\cos^{-1}(0.9)] = 1020 \text{ KVAR}$$
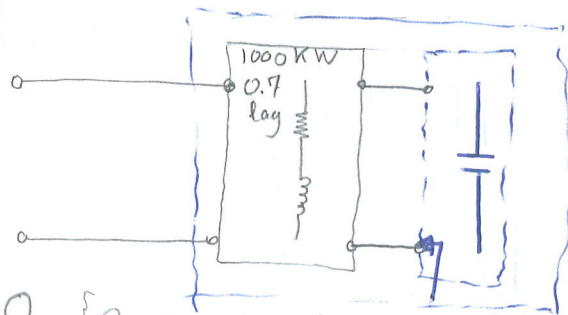
$$Q_s = 1000 \text{ kW} \times \tan [\cos^{-1}(0.9)] = 484 \text{ KVAR}$$



$$Q_c = Q_L - Q_s \quad \{ Q_c + Q_s = Q_L \}$$

$$= 1020 \text{ K} - 484 \text{ K}$$

$$= 536 \text{ KVAR} \quad \text{generated by capacitor}$$

OR

$$Q_c = Q_s - Q_L \quad \{ Q_c + Q_L = Q_s \}$$

$$= 484 \text{ K} - 1020 \text{ K}$$

$$= -536 \text{ KVAR} \quad \text{consumed by capacitor}$$

b) $pf' = ?!$

New System (S.M.)




$$S_o = S_L + S_{S.M.}$$

$$= (1000 \text{ kW} + j1020 \text{ KVAR}) + (746 \text{ K} + j0)$$

$$= (1746 \text{ K} + j1020 \text{ K})$$
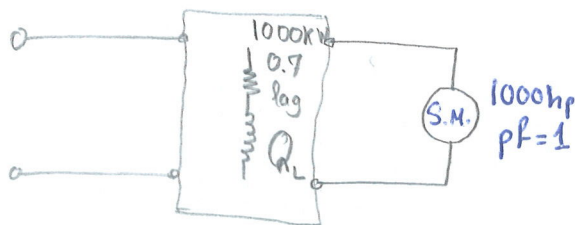
$$\rightarrow pf' = \cos \left[\tan^{-1} \left(\frac{1020}{1746} \right) \right] = 0.864$$



Note: 1000 hp = 746 KW


Problem 2.26:

a) Use Complex Power

$$P + jQ = VI^*$$


$$\rightarrow I = \frac{V_{load}^*}{P_{load} - jQ_{load}} = \frac{480}{120 \text{ K} [1 - j0.6]}$$

$$|I| = 0.294 \text{ KA}$$

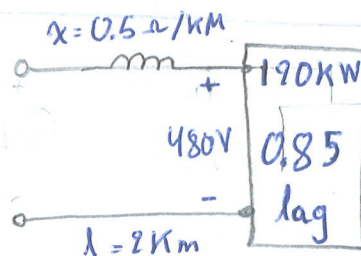

$$\tan [\cos^{-1}(0.85)]$$

$$Z = \frac{|V|^2}{P - jQ}$$

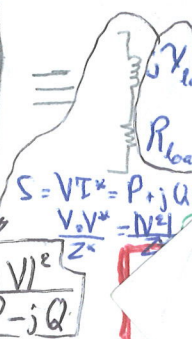

OR

$$VI^* = S \Rightarrow |I| = \frac{|S|}{V} = \frac{120}{\cos \phi} \cdot \frac{1}{480} = 0.294 \text{ kA}$$

$$Q_{\text{line}} = (294)^2 \times 1 = 86436 \\ = 86.436 \text{ KVAR}$$

$$Q_{\text{system}} = Q_{\text{load}} + Q_{\text{line}} = 120 \times 0.62 + 86.436 \\ = 160.8 \text{ KVAR}$$

$$\text{pf} = \frac{P}{S} = \frac{120 \text{ k}}{\sqrt{(120 \text{ k})^2 + (160.8 \text{ k})^2}} = 0.6$$

Note: Consistent set of Unit

V	A	VA	W
KV	KA	MVA	MW

- b)
- $z = \frac{1V}{P-jQ}$
 - Calculate I
 - Calculate $Q_{\text{load}} = I^2 X_{\text{load}}$
 $Q_{\text{line}} = I^2 X_{\text{line}}$
 - $Q_{\text{total}} = Q_{\text{sys}} = Q_{\text{load}} + Q_{\text{line}}$
 - $\text{pf} = \cos \left[\tan^{-1} \left(\frac{Q_s}{P_{\text{load}}} \right) \right]$

