

EECE 471

Final Exam Summer 2010

August 10, 2010

1. As Problem 1 in FE of February 3, 2009.
2. As Problem 2 in FE of February 3, 2009.
- 3.

a) Base impedances at

$$* \text{ Node 1 : } Z_{B1} = 20^2 / 100 = 4 \Omega$$

$$* \text{ Node 2 and 3 : } Z_{B2} = \frac{220^2}{100} = 484 \Omega$$

$$* \text{ Node 4 : } Z_{B4} = \frac{66^2}{100} = 43.56 \Omega$$

$$X'_{d1} = 0.32 \times \frac{100}{250} = 0.128 \text{ p.u.}$$

$$X'_{d1u} = \frac{60}{484} = 0.124 \text{ p.u.}$$

$$X_{T1} = 0.12 \times \frac{100}{250} = 0.048 (= X_{T2})$$

$$X_{T3} = 0.12 \times \frac{100}{125} = 0.096$$

$$X'_{d2} = 0.2 \times \frac{150}{120} = 0.167$$

Total reactance of generator 2 connected to node 4:

$$X_{g2} = X_{T3} + X'_{d2} = 0.263$$

$$Z_{load} = \frac{66^2}{10(30 + j12)} - 12.5 - j5 \Rightarrow Y = 0.069 + j0.0275$$

Admittance Matrix for fault calculations:

$$\begin{array}{c}
 \begin{array}{cccc}
 & 1 & 2 & 3 & 4 \\
 1 & -j28.65 & j20.83 & 0 & 0 \\
 2 & j20.83 & -j36.96 & j16.13 & 0 \\
 3 & 0 & j16.13 & -j36.96 & j20.83 \\
 4 & 0 & 0 & j20.83 & -j24.64
 \end{array}
 \end{array}$$

b)

Z_{kk} is the Thevenin impedance of the positive sequence circuit seen between node k and ground. If the prefault voltage is V_{FK} then the fault current in per unit is given by:

$$I_{FK} = \frac{V_{FK}}{Z_{kk}}$$

Fault currents in per unit and in kA assuming the prefault voltage is 1.0 per unit:

Node	Fault Current (MVA)	Fault Current (kA)
1	965	27.9
2	770	2.02
3	682	1.79
4	687	6.01

c)

$$V_{Fn} - Z_{nk} I_{FK} = E_n$$

$$\text{but } I_{FK} = \frac{V_{FK}}{Z_{FK}}$$

$$\text{Thus } E_n = V_{Fn} - \frac{Z_{nk}}{Z_{FK}} V_{FK}$$

$$\text{With } V_{FK} = V_{Fn} = 1.0 \text{ pu}$$

$$E_n = \left(1 - \frac{Z_{nk}}{Z_{FK}}\right)$$

So for a fault at node 2:

$$E_1 = 1 - \frac{j0.0944}{j0.1298} = 0.273 \quad 27$$

$$E_2 = 0$$

$$E_3 = 1 - \frac{j0.1105}{j0.1298} = 0.149 \quad (86)$$

Fault current from generator:

$$I_{G1} = \frac{E_1 - E_2}{jX_{T1}} = \frac{0.273}{j0.048} = j5.68 \quad \text{pu}$$

$$I_{G2} = \frac{E_3 - E_2}{jX_{L2}} = \frac{0.149}{j\left(\frac{0.124}{2}\right)} = j2.40 \quad \text{pu}$$

$$I_{F2} = I_{G1} + I_{G2} = j8.09$$

d)

The circuit breaker of generator 1 should be picked up from Table I as G32 with the following minimum ratings:

Nominal kV: $> 20 \text{ kV}$

Rated Current (A): $> 7220 \text{ A}$

Breaking Current (kA): $> 28 \text{ kA}$

CB on generator 2 should also be a G32 class with following minimum ratings:

Nominal (kV): $> 15 \text{ kV}$

Rated Current (A): $> 4800 \text{ A}$

Breaking Current (kA): $> 33 \text{ kA}$

CB at the 220kV voltage, should be of type EHV2:

Nominal kV: 230 kV

Rated Current: 1600 A ($> 656 \text{ A}$)

Breaking Current: 31 kA ($> 2.02 \text{ kA}$)

CB at the 66kV voltage (at load) should be HV4 for each feeder:

Rated Current A: 1200 A ($> 87 \text{ A}$)

Breaking Current kA: 19 kA (> 6)