

S. KARAKI

AMERICAN UNIVERSITY OF BEIRUT
FACULTY OF ENGINEERING AND ARCHITECTURE

FALL 2001/2002

MIDTERM

POWER SYSTEMS FUNDAMENTALS (ELEG 071E)

OPEN BOOK (1.5 HOUR)

December 4, 2001

PROGRAMMABLE CALCULATORS ARE NOT ALLOWED

THIS QUESTION SHEET MUST BE RETURNED WITH THE ANSWER BOOKLET.

NAME: _____

ID#: _____

1. Consider the system shown in Fig. 1 below, which has the following data:

$$\begin{aligned} V_1 &= 1 \angle 0^\circ & Z_L &= j 0.2 \\ S_{D1} &= 0.4 + j 0.1 & S_{D2} &= 0.5 + j 0.2 \end{aligned}$$



Fig. 1.

- Determine V_2 when Q_2 is 0. What are the line current I_L and the complex power S_1 supplied by the generator?
 - If $|V_2|$ is to be regulated to 1, what would be in this case the reactive power Q_2 , the line current I_L and the complex power S_1 supplied by the generator?
 - If the line resistance is 0.01, what would be approximately the line losses in parts a) and b) above? Justify your approximation. What additional comments do you have on the complex power supplied by the generator?
 - If you were a system designer in a power company, would you recommend installing a capacitor bank to supply Q_2 ? What arguments would you bring forward to convince management to spend money in order to install the capacitor bank?
2. A 3-phase generator transformer has 3 sets of high voltage (HV) and low voltage (LV) windings rated at 120kV and 12kV, respectively. The transformer rating is 72 MVA. It is to be used in a Δ -Y connection to deliver energy from a generator to a load via a transmission line, as shown in Fig. 2 below.



Fig. 2.

- a) To determine the transformer characteristics, an open circuit and short circuit tests are carried out on one set of the HV/LV windings, with the other windings open circuited. With the HV winding open circuited, rated voltage was applied on the LV winding and the current was measured to be 40A. Then with the LV shorted, 12kV were applied on the HV side to circulate rated current. Find X_l , X_m and $n = V_{HV}/V_{LV}$.
 - b) Draw and identify the parameters of the per-phase equivalent circuit when the transformer is connected as a Δ -Y, with Δ being on the LV side.
 - c) The transmission line series impedance is $15 + j 120 \Omega/\text{phase}$ and the load is such that it consumes 40 MW at 0.85 PF lagging. If the load is modeled by constant impedance and the generator voltage is regulated at 12 kV, determine the voltage at the load end, the current in the transmission line, and the transmission efficiency.
3. It is required to design a 3- Φ 50 Hz transmission line to transmit 400 MW over a distance of 350 miles. The two voltages being considered are 275 kV and 400 kV with typical phase-to-phase spacing of 20 ft and 30 ft, respectively. The typical current density at the prevailing temperature and wind speed conditions 2 A/mm^2 .
 - a) Using data from the table of conductors in your textbook (Table A8.1, pp. 605), select a proper configuration for each of the voltages given. Note that $1 \text{ kmil} = 0.506 \text{ mm}^2$.
 - b) Determine the characteristic impedance and the propagation constant at the two given voltages.
 - c) Which of the voltages would be a better choice if for stability consideration the phase angle difference across the line is to be kept less than 45° ? Justify your answer. Consider that the voltage magnitude at the receiving end is essentially equal to that of the sending end.