

Solution

Introduction to Electrical Engineering

Summer 2014

Test 1

Duration: 60 min

Instructor: Dr. B. Habib


Observations: THE EXAM IS CLOSED-BOOK AND OVER 100.

Name: _____

ID: _____

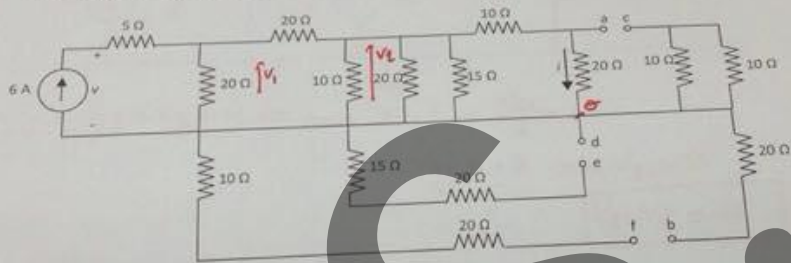Question 1: Network analysis by using series and parallel equivalents. (20 pts)

Find the values of v (Ohm's Law), i and V_{ab} , where a, b, c, d, e and f are open-circuits.



$$R_{eq} = 5 + \left[\left((20+10) \parallel 15 \parallel 20 \parallel 10 \right) + 20 \right] \parallel 20$$

$$\frac{1}{\frac{1}{15} + \frac{1}{20} + \frac{1}{10} + \frac{1}{30}} = 4$$

$$\frac{24}{11} \parallel 20$$

$$\frac{1}{\frac{1}{24} + \frac{1}{20}} = 10,909$$

(8 pt)

$$R_{eq} = 15,909$$

$$V = R_{eq} \cdot i = 15,909 \cdot 6A = 95,4545V \quad (4pt)$$

$$V_{ab} = V_{ac} = i \cdot 20$$

$$V_1 = \frac{10,909}{5+10,909} \cdot V \quad (V-D) = 65,4543V$$

$$V_2 = \frac{4}{4+20} \cdot V_1 = 10,909V$$


$$V_{ab} = \frac{20}{10+20} \cdot V_2 = 7,2727V = V_{ab} \quad (4pt)$$

Ohm's Law

$$i = \frac{V_{ab}}{20} = 0,363A \quad (4pt)$$

Question 2: Node-voltage analysis, (20 pts)

Use the node-voltage technique to solve the value of i_x . Select the location of the reference node to minimize the number of unknown node-voltages.

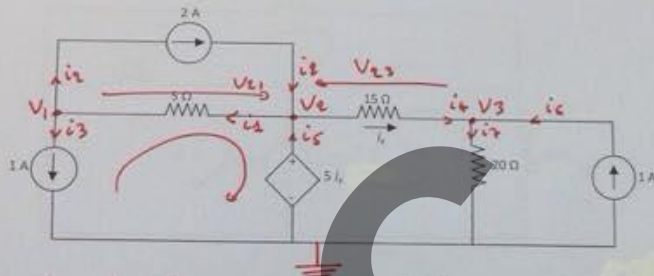

Node 1: $i_2 + i_3 - i_1 = 0 \Rightarrow 2 + 1 - \frac{V_{21}}{5} = 0$
 $-\frac{V_{21}}{5} = -3 \Rightarrow V_{21} = 15$
 $V_2 - V_1 = 15$ (1)


Node 2: $-i_2 + i_2 + i_4 - i_5 = 0$ where $i_x = \frac{V_{23}}{15} = \frac{V_2 - V_3}{15}$
 $-2 + \frac{V_2 - V_1}{5} + \frac{V_2 - V_3}{15} - \frac{5(V_2 - V_3)}{15} = 0$
 $-30 + 3V_2 - 3V_1 + V_2 - V_3 - 5V_2 + 5V_3 = 0$
 $-3V_1 - V_2 + 4V_3 - 30 = 0$ (2)

Node 3: $i_6 + i_4 - i_7 = 0$
 $\frac{V_2 - V_3}{15} + 1 - \frac{V_3}{20} = 0$
 $5 + \frac{V_2 - V_3}{3} - \frac{V_3}{4} = 0 \Rightarrow 5 + \frac{1}{3}V_2 - 0,5833V_3 = 0$ (3)

(1) + (2) + (3) \Rightarrow
 $V_1 = 13,76V$
 $V_2 = 25,02V \Rightarrow i_x = 0,925A$
 $V_3 = 23,76V$
 10pt

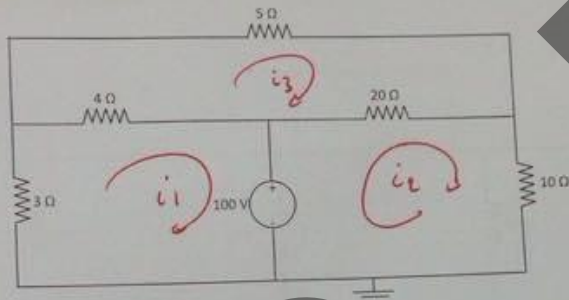Question 3: Mesh-current analysis. (20 pts)

Solve the power delivered by the voltage source using the mesh-current method.



$$\text{Mesh 1: } 3i_1 + 4(i_1 - i_2) + 100 = 0 \quad (1)$$

$$\text{Mesh 2: } -100 + (i_2 - i_3) \cdot 20 + 20i_2 = 0 \quad (2)$$



$$\text{Mesh 3: } 5i_3 + 4(i_3 - i_1) + 20(i_3 - i_2) = 0 \quad (3)$$

$$(1) + (2) + (3) \rightarrow \begin{cases} i_1 = \cancel{13.87} \text{ A} \\ i_2 = \cancel{3.8} \text{ A} \\ i_3 = \cancel{0.711} \text{ A} \end{cases}$$


$$\begin{aligned} P &= V \cdot I \\ &= 100 \cdot (i_2 - i_1) \\ &= \cancel{1767} \text{ W} \end{aligned}$$

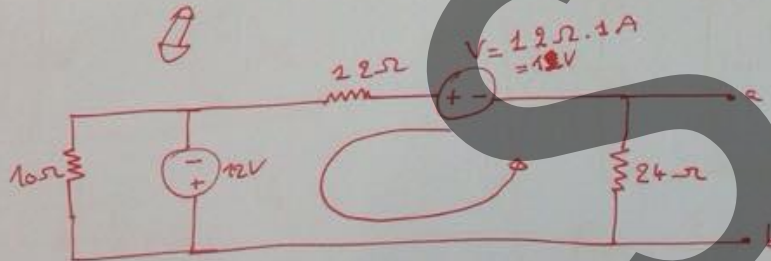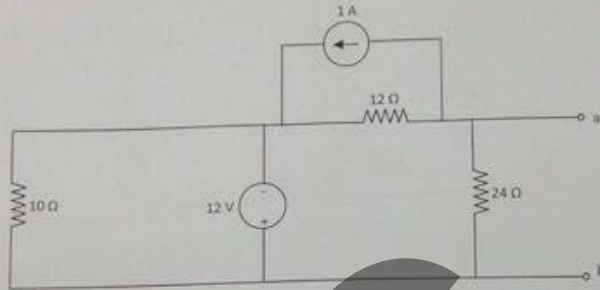Question 4: Thevenin and Norton equivalent circuits. (20 pts)

Find the Thevenin and Norton equivalent circuits. Then calculate the maximum power delivered by the circuit.




Finding R_t :

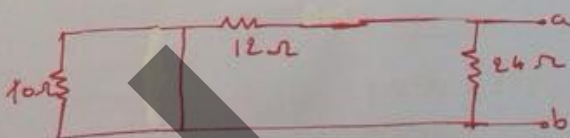

$$R_t = \frac{1}{\frac{1}{12} + \frac{1}{24}} = 8 \Omega$$


Finding $V_{oc} = V_{ab}$:

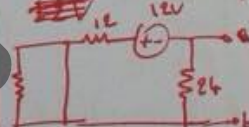Applying ~~the~~ the superposition principle:



$$i_1 = \frac{12}{12+24} = 0,333 \text{ A}$$

$$V_{ab} = 24 \cdot i_1 = 8 \text{ V}$$

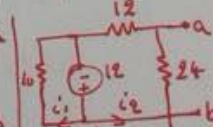


$$R = \frac{1}{\frac{1}{10} + \frac{1}{12+24}} = 7,82 \Omega$$

$$i_2 = \frac{12}{7,82} = 1,53 \text{ A}$$

$$i_2 = 0,3333 \text{ A}$$

$$V_{ab} = i_2 \cdot 24 = 8 \text{ V}$$

$$V_{ab \text{ total}} = 16 \text{ V}$$

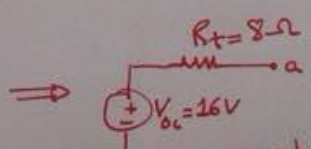


⑤ Thevenin equivalent circuit
 $P_{L \text{ max}} = \frac{V_t^2}{4R_t} = 8 \text{ W}$




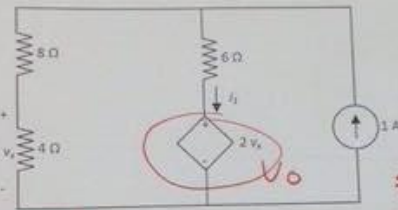Question 5: Superposition Principle, (20 pts)

Use the superposition method to solve i_1 .



step 1

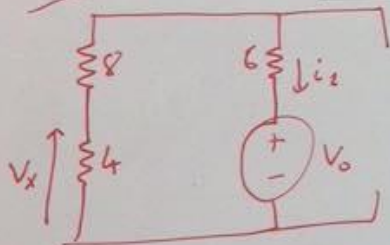

$$V_x = \frac{4}{4+8+6} \cdot V_0$$

$$= 0,2222 \cdot V_0$$

$$i_2 = -\frac{V_0}{18}$$

$$\Rightarrow V_{x \text{ total}} = 0,2222 \cdot 1,3333$$


$$i_2 = 0,6666 - \frac{V_0}{18}$$

$$V_0 = 2V_x \Rightarrow V_x = 0,2222 \cdot 2 \cdot V_x + 1,3333$$

$$= 0,4444V_x + 1,3333$$

$$\Rightarrow \boxed{i_2 = 0,5333 \text{ A}}$$

step 2

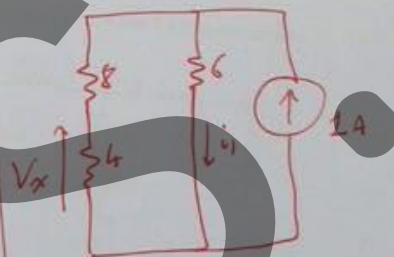

$$R_{eq} = \frac{1}{\frac{1}{6} + \frac{1}{8+4}} = 4$$

$$V = R \cdot I = 4 \text{ V}$$

$$\Rightarrow \Delta V_x = \frac{4}{4+8} \cdot 4 \text{ V}$$

$$= 1,3333 \text{ V}$$

$$i_2 = \frac{8+4}{8+4+6} \cdot 1$$

$$= 0,6666 \text{ A}$$