

• Lab 6: iterative approach:

signal conditioning circuit.

Product dev cycle:

→ include Engg design process

- 1) ideas (Brain storm)
- 2) market survey
- 3) formulate pb statement
- + define CTQ (critical to quality constraints)
- 4) check CBA: Cost Benefit Analysis

(expenditures + gain/revenue)

- 5) Upper mgmt
- 6) Design team

7) Engg design process: end product is a prototype



we need to test it

8) First technical review

Prototype ≠ 9) Pilot

near end products closer to actual finished product

- 10) 2nd technical review
- 11) Manufacturing line dev. → marketing training → inventory building

↓ Normal testing

↓ types of testing / acceptance testing

• Bent Chart: timeline

→ to check milestones + Book resources

→ maybe run tests that might run in parallel

Introd.:

• slow: response time too big


• accurate and precise as correct now

because not repeated experiment

N.B: let's take scenario:

RTD we want to take

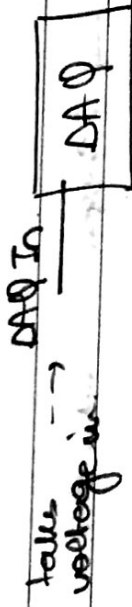→ we want to take resistance of RTD by DAQ



since DAQ analog we need A/D quantization

ex: 0 → 4V

bits

00

01

10

11

0-1V

1-2V

2-3V

3-4V

RTD gives voltage 1-2V

no such precision

⇒ we need signal conditioning circuit

any interface between Sensor and DAQ

FN:

- 1) amplify range
- 2) change from resistance to voltage
- 3) Filtering noise at a sensor
- 4) cold junction for the couple
- 5) excitation circuit for RTD (the biasing)
- 6) for RTD, signal conditioning circuit compensation that makes the curve linear
- 7) Electrical isolation

NB: thermocouple need cold junction compensation

Requirements:

- 0 to 10V
- RTD between Room \rightarrow 40-45C
- Signal Conditioning
- Output for resistance to voltage (0-10V) since at DAQ

2) FN decomposition

1. Resistance to voltage: Transducer Conversion Circuit
2. Range of V from 2 to 10V: Voltage Translat or amplifier circuit

\rightarrow what is design possible?

Voltage divider

A- Transducer Conversion: check of amp.

- RC circuit
- Wheatstone Bridge



put R on feedback and need output



B- Voltage translation circuit:

\rightarrow use of amp

NB:

R_{min} at 25C
 R_{max} at 45C

\rightarrow then use voltage divider to

get original

range before Amplification



How to choose value of this?

measure voltage line



→ R:

our goal is to max V_{min} and V_{max}

$$V_{min} = V_{CC} \times \frac{R_{RTD_{min}}}{R + R_{RTD_{min}}}$$


$$V_{max} = V_{CC} \times \frac{R_{RTD_{max}}}{R + R_{RTD_{max}}}$$

→ we want $V_{max} - V_{min}$ to be largest.


$$\frac{d(V_{max} - V_{min})}{dR} \rightarrow R = \sqrt{R_{RTD_{min}} \times R_{RTD_{max}}}$$

↳ geom average

N.B: Some may use arithmetic mean

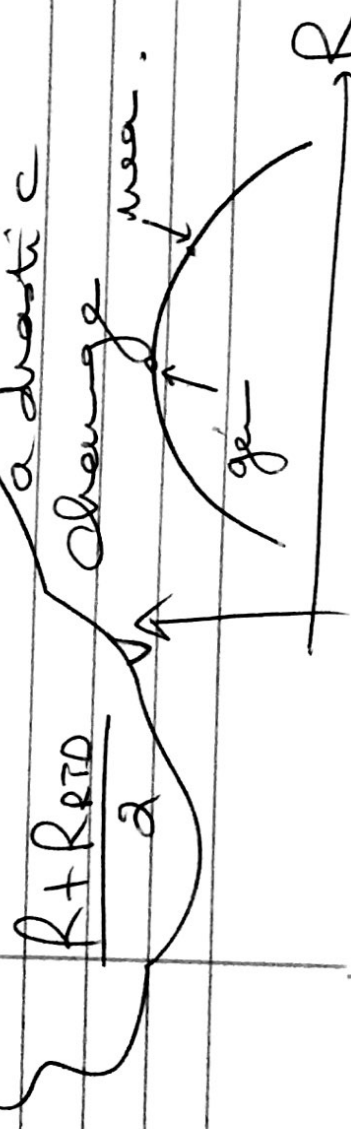

• what V divider:

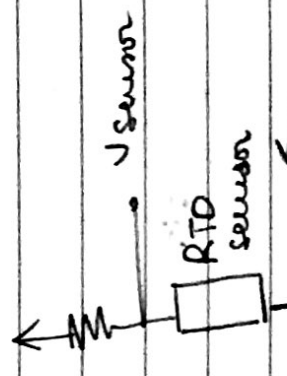

curve of RTD.


$$R = f(T, R_{T0}, \alpha)$$

RTD is a PTC: positive temp coefficient

NTC just like Thermistor: $T \uparrow, R_{NTC} \downarrow, V \uparrow$
it's increase

by using this circuit.

② Translation circuit:

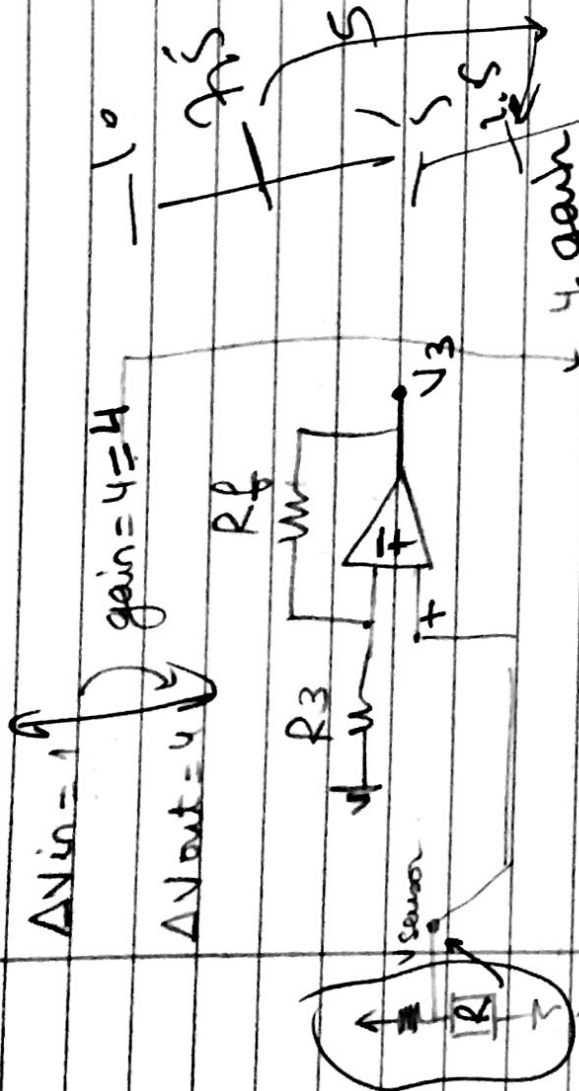


$\Delta V_{in} = 1$
 $\Delta V_{out} = 4$
 gain = 4

$V_3 = V_{sensor} \left(1 + \frac{R_f}{R_3} \right)$ gain


$V_{3min} = 1 \times 4 = 4V$
 $V_{3max} = 2 \times 4 = 8V$
 we need to shift it back
 $4 \rightarrow 18$
 we shift till
 $0 \rightarrow 14V$

we need to fix:

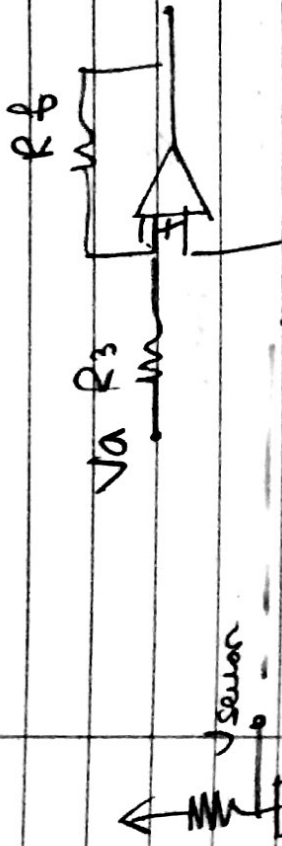

$V_3 = \left(1 + \frac{R_f}{R_3} \right) V_{sensor} = V_a \frac{R_f}{R_3}$
 (derivation) in appendix.

? How to get V_a ? from voltage division

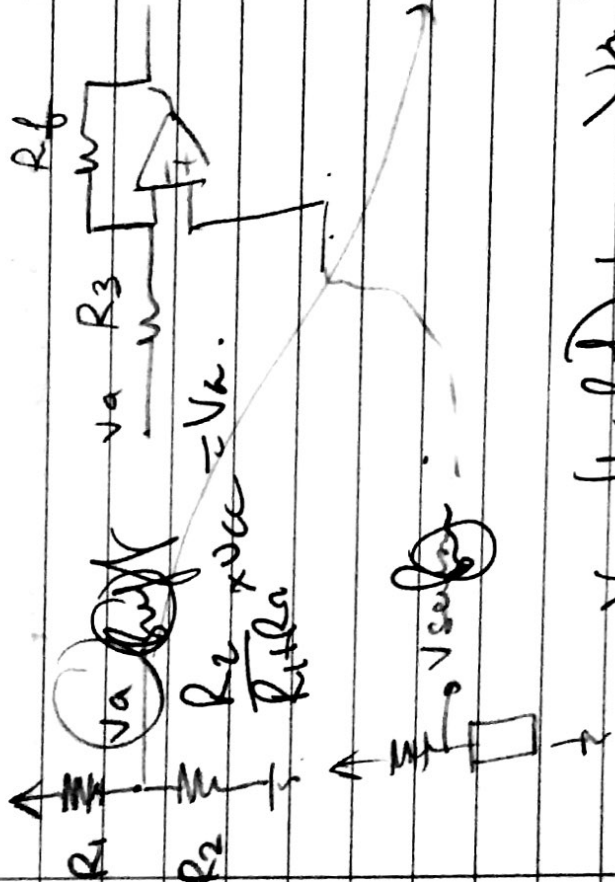

$V_2 = \left(1 + \frac{R_f}{R_3} \right) V_s = V_a \left(\frac{R_f}{R_3} \right)$

lets get V_a : \rightarrow to bias.

at V_{min} :


$$V_3 = 0 = \left(\frac{1+R_1}{R_3} \right) V_{min} - V_a \left(\frac{R_6}{R_3} \right)$$

(assume)

$$\Rightarrow V_a = \left(\frac{1+R_3}{R_6} \right) V_{min}$$


and from this V_a we get values of R_1 and R_2

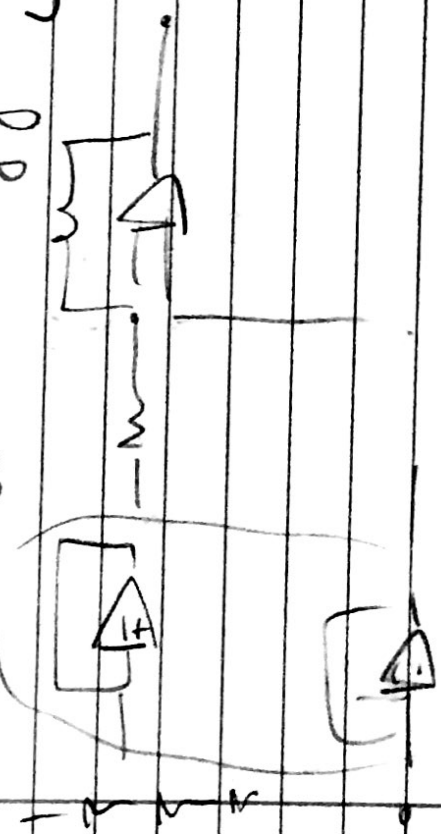• we need to add buffer (unity gain opamp)




Buffers: more than one to 5b on voltage divider.

RTP

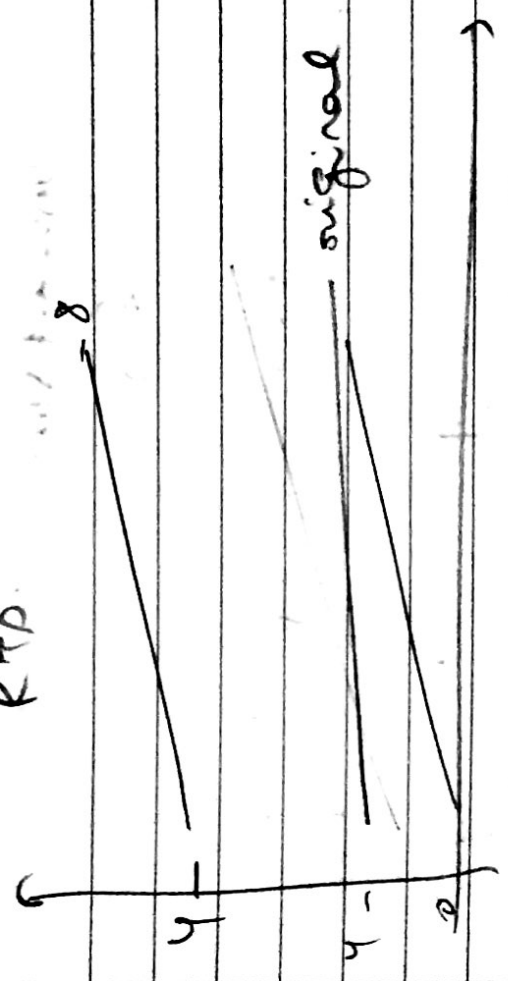

\rightarrow use measured values

~~Vcc used~~
~~= 12V~~

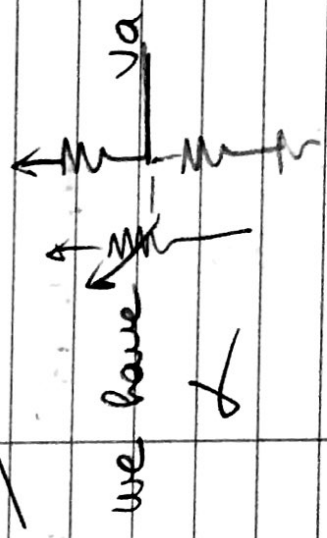

we have V_a we put variable resistor in order to make life easier.

N.B: $V_{cc} = 12V$ because range $0 \rightarrow 10V$
(so about med 5V)
(range not precise, more for low)

$R_{\text{sensor min}} = 1 \text{ k}\Omega$
 $R_{\text{sensor max}} = 1.2 \text{ k}\Omega$ } max 200 RTO

these
 are theoretical:
 measure the resistance
 stimulate
 at 4 degrees
 (instead of
 pellet)


$1.2 \text{ k}\Omega$ $1 \text{ k}\Omega$

$\text{exp} = 1.1889 \text{ k}\Omega$ $\text{exp} = 0.9775 \text{ k}\Omega$



$$\frac{R_1}{R_3} = 16, - \quad \frac{2.2016}{2.2040}$$

$$R_1 = 1.1019$$

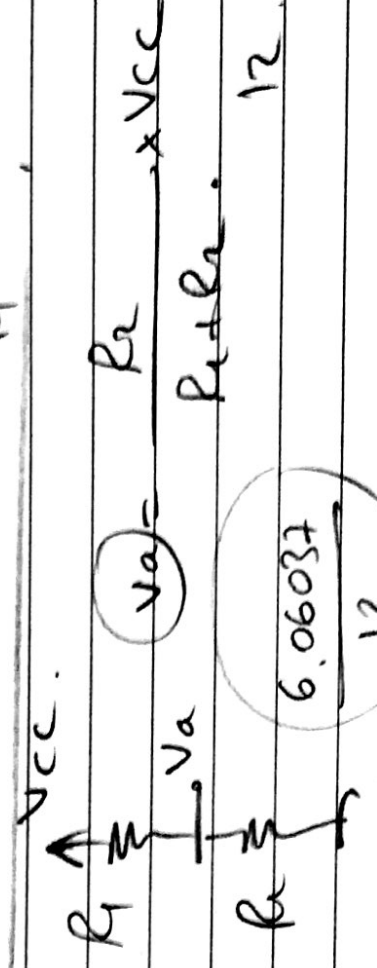

$$\frac{6.06037}{12}$$

$$= 0.505032 \frac{R_2}{R_1 + R_2}$$

$$0.50503 = \frac{1000 + R_2}{1000 + R_2}$$

$$1000 \times 0.50503 = (1000 + R_2) \times 0.50503$$

$$0.4941$$