

Prof. R. Chedid **FACULTY OF ENGINEERING**
R. Jabr **& ARCHITECTURE**
L. Hamandi
S. Khaddaj

SPRING TERM 2011-12

Name:.....


March 23, 2012

(EECE210) ELECTRIC CIRCUITS

CLOSED BOOK (1 ½ HRS)

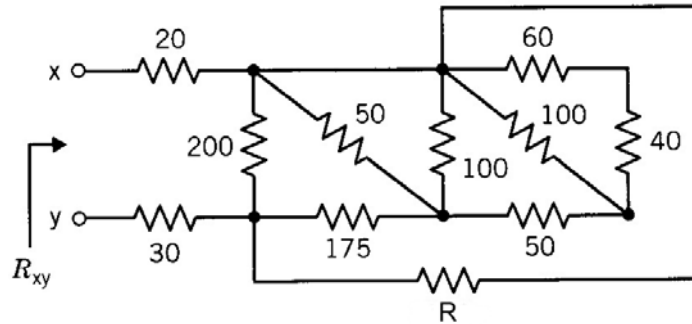Problem 1:


In the circuit shown below, all resistances are in ohms. Determine the equivalent resistance R_{xy} if $R = 100 \Omega$.



- a) 50 Ω
- b) 100 Ω
- c) 200 Ω
- d) 400 Ω
- e) None of the above

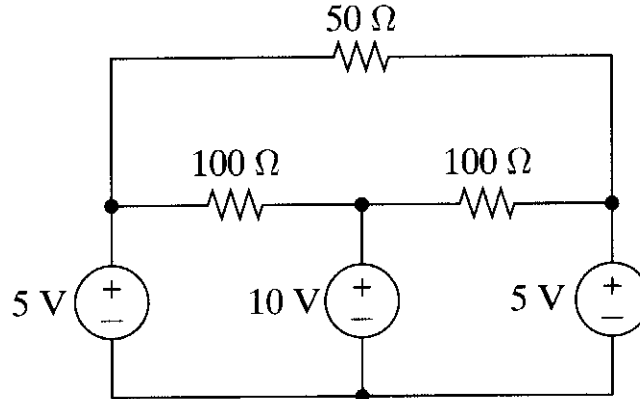Problem 2:


Determine the power developed by the 10 V source in the circuit shown below.



- a) 1 W
- b) 2 W
- c) 3 W
- d) 4 W
- e) None of the above

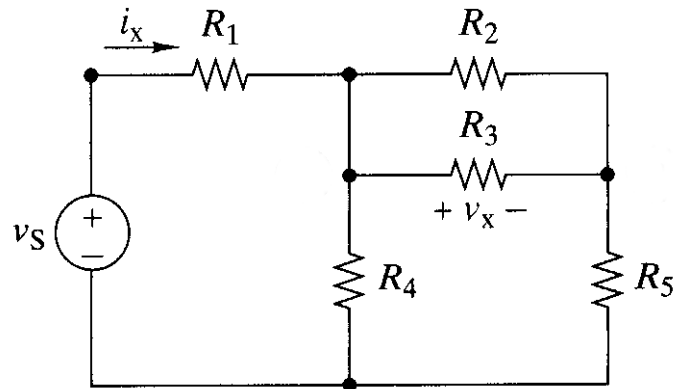Problem 3:


Find v_x in the circuit shown below when $v_s = 12\text{ V}$ and $R_1 = R_2 = R_3 = R_4 = R_5 = 8\text{ k}\Omega$.



- a) 0.5 V
- b) 1.0 V
- c) 1.5 V
- d) 2.0 V
- e) None of the above

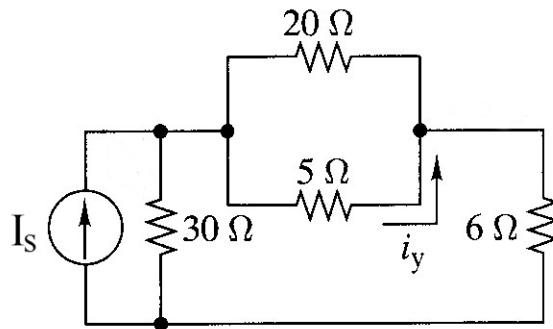Problem 4:


If $i_y = 12\text{ A}$ in the network shown below, find I_s .



- a) 5 A
- b) 10 A
- c) 15 A
- d) 20 A
- e) None of the above

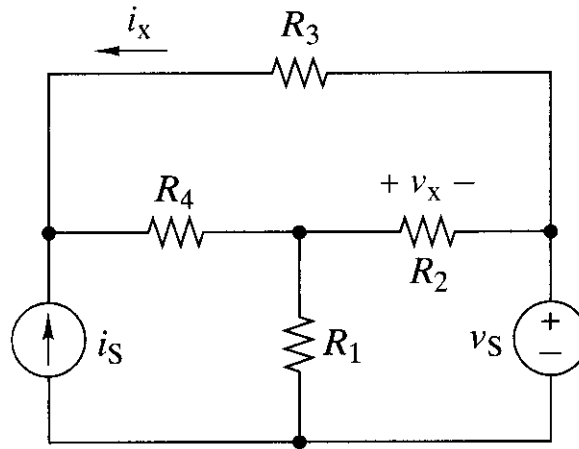Problem 5:


Find i_x in the circuit shown below when $v_s = 30\text{ V}$, $i_s = 4\text{ mA}$, and $R_1 = R_2 = R_3 = R_4 = 10\text{ k}\Omega$.



- a) -0.2 mA
- b) -0.8 mA
- c) -1.2 mA
- d) -1.8 mA
- e) None of the above

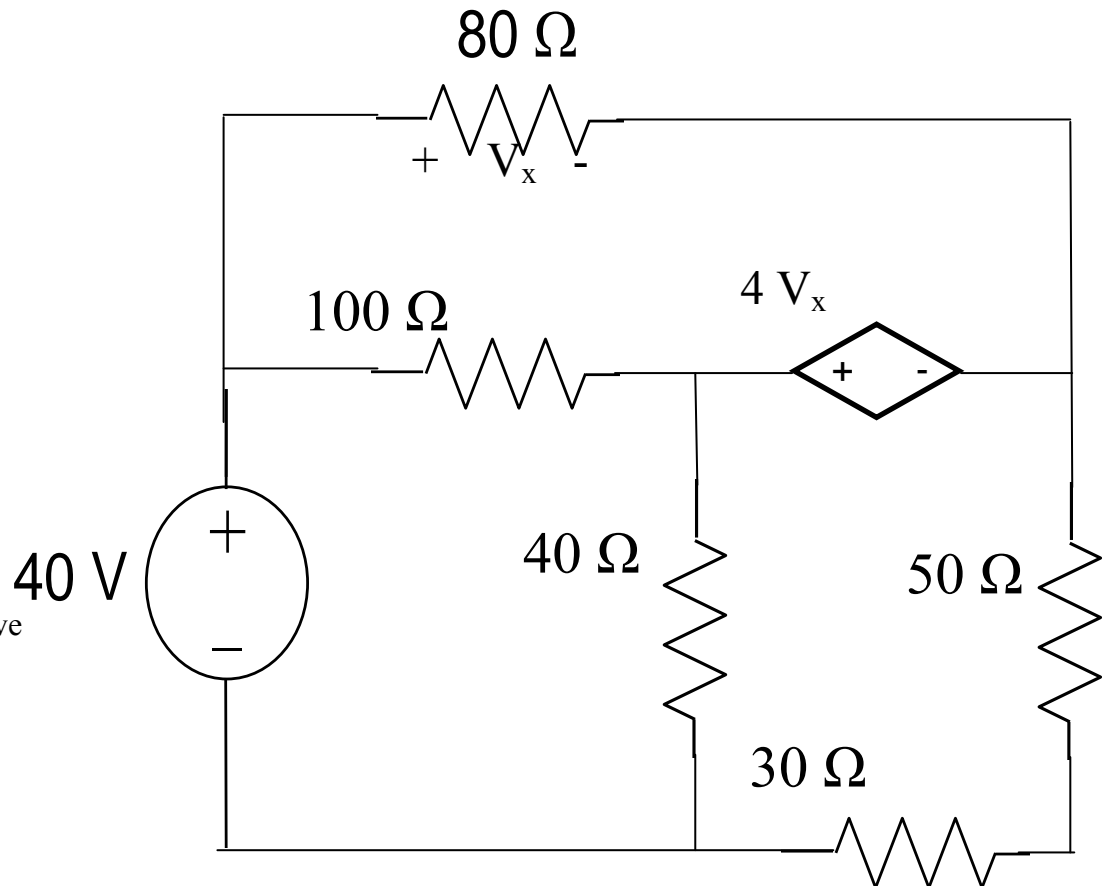Problem 6:


In the following circuit, find V_x in Volts.



- a) -40 V
- b) -18.75 V
- c) -28.125 V
- d) -16.25 V
- e) None of the above

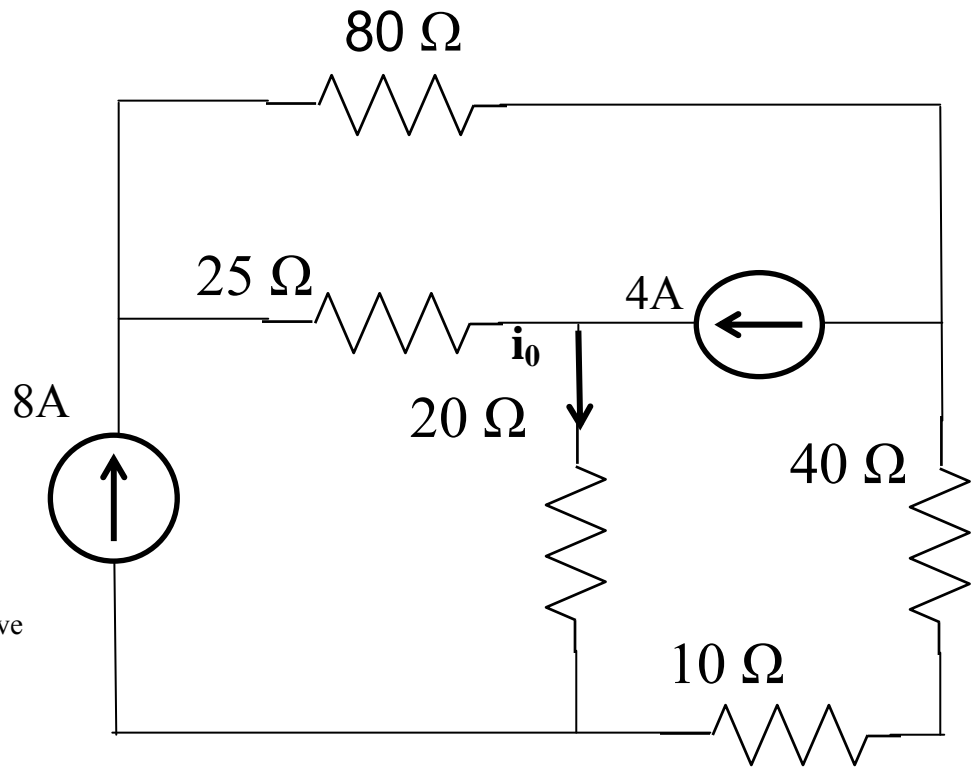Problem 7:


In the circuit below, find i_0 in Amperes.



- a) 0A
- b) 9.83
- c) 8.34
- d) 7.25
- e) None of the above

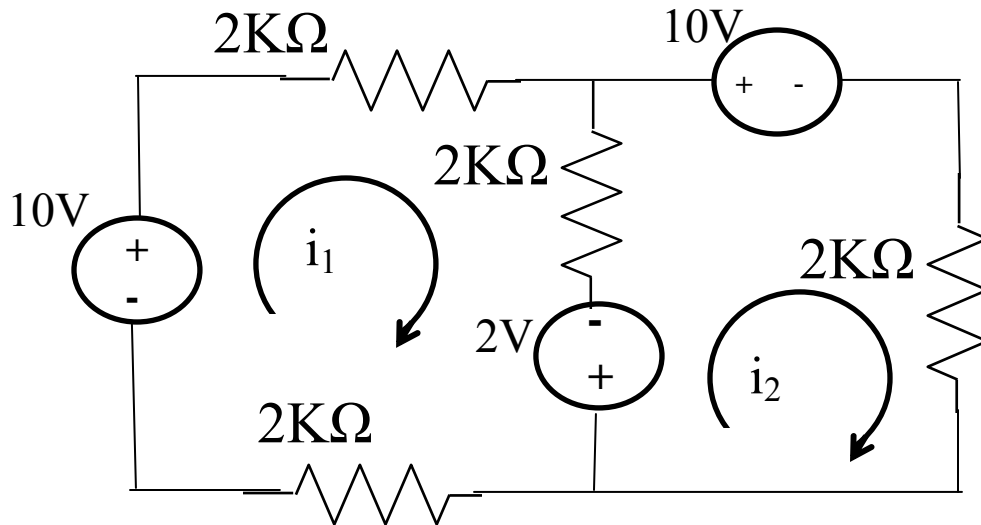Problem 8:


Write the mesh current equations for the circuit shown if the currents are expressed in mA.



- a) $10 - 9i_1 + 2i_2 = 0$ and $12 - 3i_1 + 4i_2 = 0$
- b) $12 - 9i_1 + 3i_2 = 0$ and $12 - 3i_1 + 6i_2 = 0$
- c) $10 - 6i_1 + 3i_2 = 0$ and $10 - 2i_1 + 6i_2 = 0$
- d) $12 - 6i_1 + 2i_2 = 0$ and $12 - 2i_1 + 4i_2 = 0$
- e) None of the above

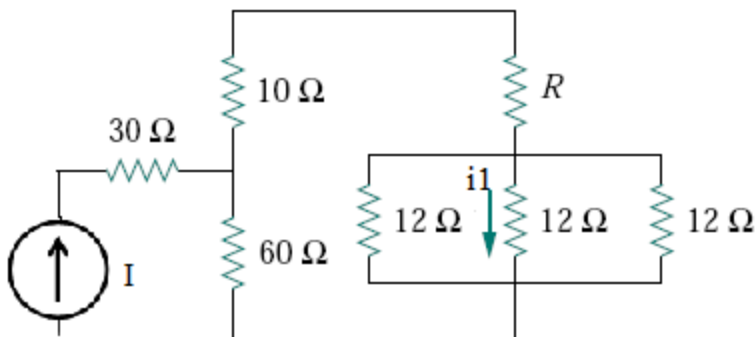Problem 9:


If $R=6$ ohms and $I=2$ A. Find the current i_1 .



- a- 0.5 A
- b- 1A
- c- 0.75A
- d- 0.25A
- e- None of the above

Problem 10:


Find the current i_1 .

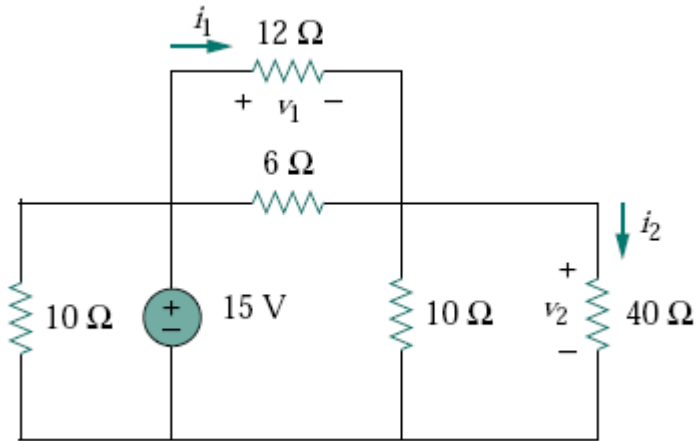

- a- 500 mA
- b- 1A
- c- 833.3 mA
- d- 416.7 mA**
- e- None of the above

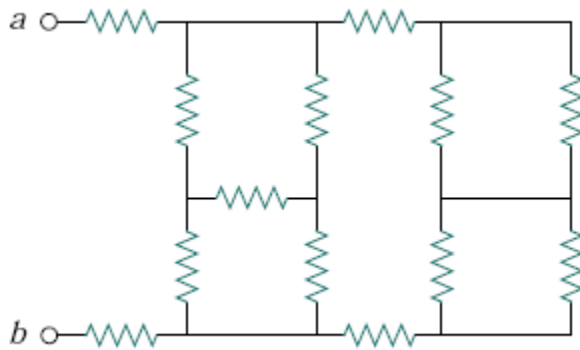Problem 11:


Find R_{eq} as seen from terminals a and b if the value of every resistor is 9 ohms:



- a- 5 ohms
- b- 24.75 ohms**
- c- 25.25 ohms
- d- 27 ohms
- e- None of the above

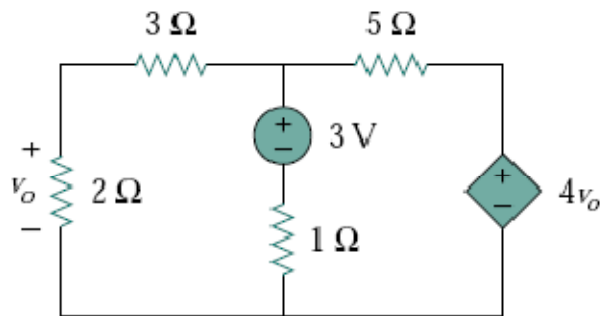Problem 12:

Find the power dissipated in the 2 ohm resistor



- a. 617.3 mW
- b. 1.39 W
- c. 420 mW
- d. 2.4 W
- e. None of the above