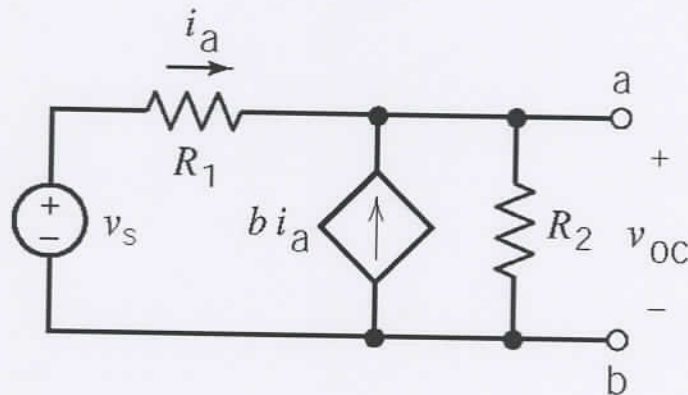


**American University of Beirut**  
**Faculty of Engineering and Architecture**  
**Department of Electrical and Computer Engineering**  
**EECE 210 – Electric Circuits-Spring term 2011**  
**Quiz II – Solution**

**Problem 1**

Find  $V_{Th}$  with respect to the terminals a-b in the circuit shown below when  $v_s = 15\text{ V}$ ,  $R_1 = R_2 = 150\ \Omega$ , and  $b = 1$ .



**Solution**

$$V_s = R_1 i_a + R_2 (1 + b) i_a \Rightarrow i_a = \frac{V_s}{R_1 + R_2 (1 + b)}$$

$$V_{Th} = R_2 (1 + b) i_a = \frac{R_2 (1 + b) V_s}{R_1 + R_2 (1 + b)}$$

**Problem 2**

Find  $R_{Th}$  with respect to the terminals a-b for the circuit in problem 1.


**Solution**

$$i_{sc} = (1 + b) i_a = (1 + b) \frac{V_s}{R_1}$$

$$R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{R_2 (1 + b) V_s}{R_1 + R_2 (1 + b)} * \frac{R_1}{(1 + b) V_s} = \frac{R_1 R_2}{R_1 + R_2 (1 + b)}$$
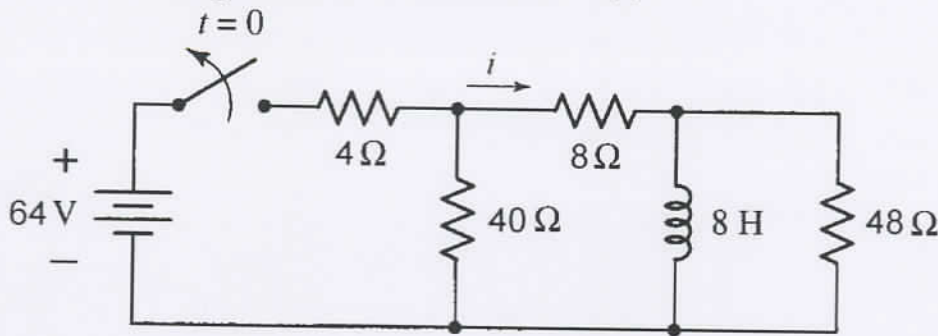
### Problem 3

The switch in the circuit shown below has been closed for a very long time before it opens at  $t = 0$ . Find the energy stored in the inductor at  $t = 0^+$ .



### Solution

As the switch has been closed for a long period of time, the inductor acts as a short circuit. Accordingly, we can remove the  $48\Omega$  resistor and the current in the inductor is the same as the one in the  $8\Omega$  resistor.

$$\text{The total resistance is then given by: } R_T = (8 // 40) + 4 = \frac{8 * 40}{48} + 4 = \frac{20}{3} + 4 = \frac{32}{3} \Omega$$

$$\text{The total current (the current in the } 4\Omega \text{ resistor) is then given by: } I_4 = \frac{64 * 3}{32} = 6\text{ A}$$

$$\text{The current in the } 8\Omega \text{ resistor is then: } I_8 = 6 * \frac{40}{48} = 5\text{ A}$$

$$\text{The total energy stored in the inductor is given by: } W_L = \frac{1}{2} L (I_8)^2 = 4 * 25 = 100\text{ J}$$

### Problem 4

In the circuit of problem 3, Find  $i(t)$  at  $t = 0.333\text{ s}$ .

### Solution


$$R_{eq} = (40 + 8) // 48 = 24\Omega$$

$$\tau = \frac{L}{R} = \frac{8}{24} = 0.33333$$

$$i(t) = \frac{I_0}{2} e^{-\frac{t}{\tau}} \Rightarrow i(0.333) = \frac{5}{2} e^{-1} = 0.92\text{ A}$$

**Problem 5**

Consider the figure shown below, determine the output voltage when  $I = 1 \text{ mA}$

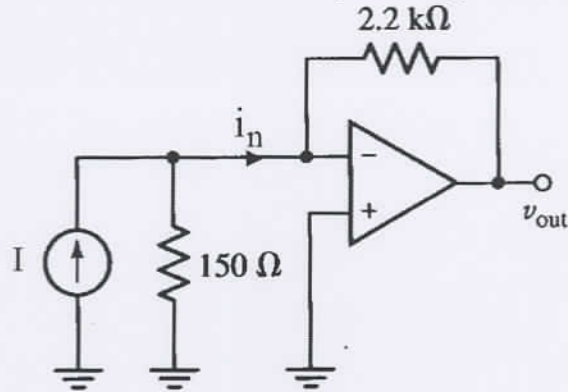
**Solution**

$v_p = 0 \text{ Volts}$ , then  $v_n = 0$  and no currents flow in the  $150 \Omega$  resistor. Accordingly,

$$i_n = I = \frac{0 - v_{out}}{2.2 \times 10^3} \Rightarrow v_{out} = -2200I$$

**Problem 6.**

Consider the Figure shown below, determine the output voltage given that  $v_1 = 1 \text{ volts}$ .

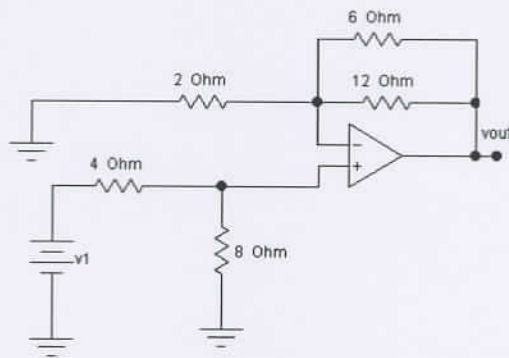**Solution**

Using voltage divider rule,  $v_p = \frac{8}{8+4} v_1 \Rightarrow \frac{2}{3} v_1 = v_p$

Determine  $v_{out}$  as a function of  $v_n$ .


$$i_n = 0 \Rightarrow \frac{v_{out} - v_n}{6} + \frac{v_{out} - v_n}{12} = \frac{v_n}{2}$$

$$\frac{v_{out}}{4} = \frac{3v_n}{4} \Rightarrow v_{out} = 3v_n$$

$$v_n = v_p \Rightarrow v_{out} = 3v_n = 3\left(\frac{2}{3}\right)v_1 \Rightarrow v_{out} = 2v_1$$
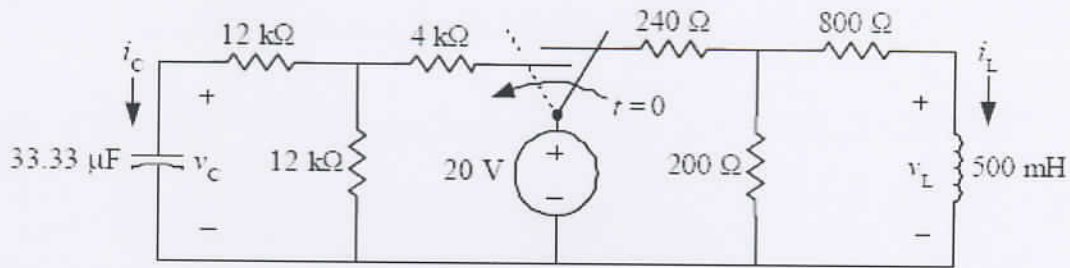
### Problem 7

For the circuit shown below, the switch has been in its position for a long period of time.



What is the value of the current in the inductor  $i_L$  at  $t = 0^-$ ?

### Solution


The inductor, before the switch is open, acts as a short circuit.

$$i_{20} = \frac{20}{240 + (200 // 800)} = 50 \text{ mA}$$

$$i_L = i_{20} \frac{200}{200 + 800} = 10 \text{ mA}$$

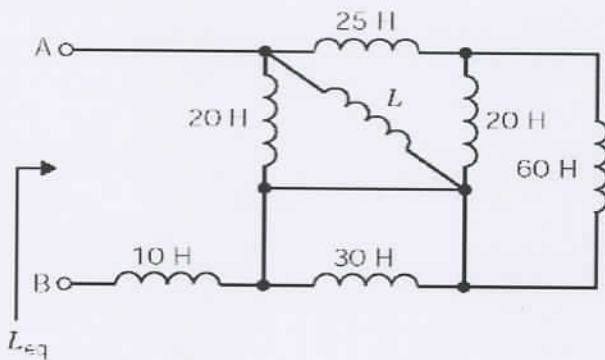
### Problem 8

The figure shown below is equivalent to a single inductor having an equivalent inductance of 15 Henries. Determine  $L$ .


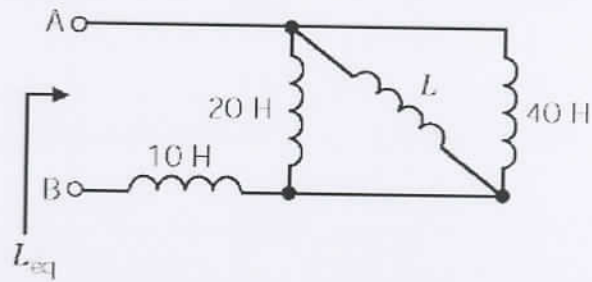
### Solution

The 25 H inductor is in series with a parallel combination of 20H and 60 H inductors. The inductance of the equivalent inductor is:  $25 + ((60 * 20) / (60 + 20)) = 40$  H. The 30 H inductor is in parallel with a short circuit, which is equivalent to a short circuit. After making these simplifications, we have



$$L_{eq} = L_1 + 10, \quad \text{where } \frac{1}{L_1} = \frac{1}{20} + \frac{1}{40} + \frac{1}{L} \Rightarrow L_1 = \frac{40L}{3L + 40}$$


Substituting, we obtain

$$L_{eq} = \frac{40L}{3L + 40} + 10 \Rightarrow 3LL_{eq} + 40L_{eq} = 40L + 30L + 400$$

$$L = \frac{400 - 40L_{eq}}{3L_{eq} - 70}$$
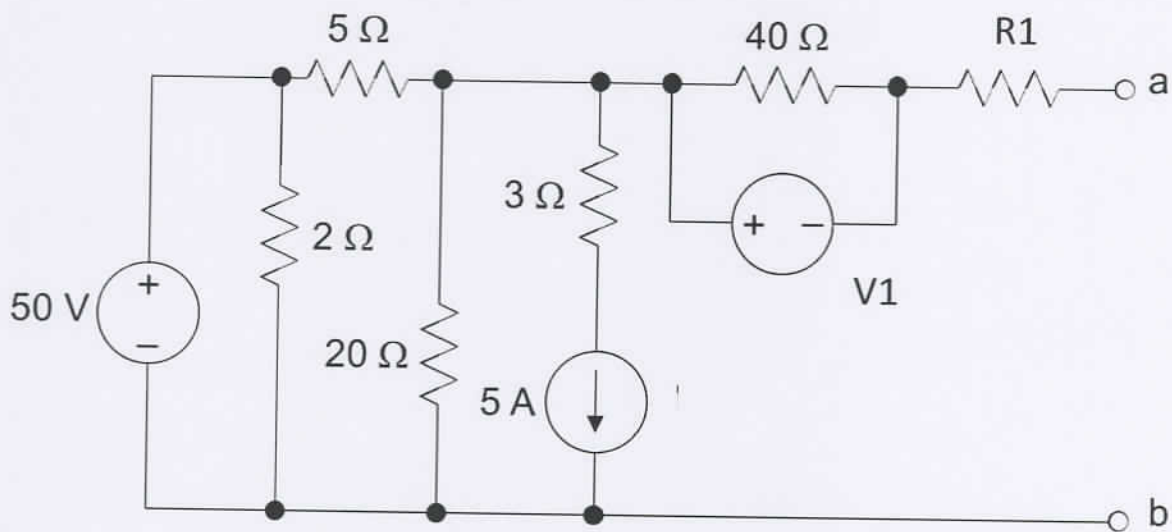
### Problem 9

Find the Thevenin equivalent voltage seen between terminals ab if  $V_1 = 3V$  and  $R_1 = 10\Omega$ .



### Solution

Let  $V_2$  be the node voltage to the left of the  $5\Omega$  resistor and  $V_3$  to the right. Using Nodal

analysis, we have:  $V_2 = 50$  Volts and  $\frac{V_3}{20} + \frac{V_3 - 50}{5} + 5 = 0$

Rearranging the above equation, we obtain


$$V_3 + 4V_3 - 200 + 100 = 0 \Rightarrow 5V_3 = 100 \Rightarrow V_3 = 20 \text{ Volts}$$

$$V_3 - V_{ab} = V_1 \Rightarrow V_{ab} = V_3 - V_1 = 20 - V_1$$



**Problem 10**

The switch was open for a long time before it closes at  $t=0$ . Find the voltage across the capacitor after  $t = 1\tau$  (one time constant after closing the switch) given that  $R = 10\text{ k}\Omega$ .

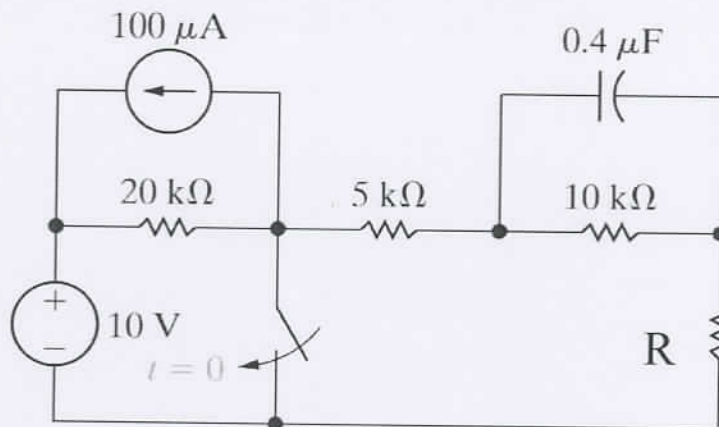**Solution**

First, let us determine the initial voltage across the capacitor when the switch is open.

1. Convert the current source in parallel with the  $20\text{ k}\Omega$  resistor to a voltage source of  $2\text{ V}$  in series with this resistor
2. Combine the two voltage sources into one source of  $8\text{ Volts}$
3. Use voltage divider rule to obtain the voltage across the  $10\text{ k}\Omega$  resistor


$$V_{10} = \frac{8 \cdot 10}{10 + 5 + 20 + R_1} = \frac{80}{35 + R_1} = V_c(0)$$

When the switch is open, the capacitor will discharge through the  $10\text{ k}\Omega$  resistor.

$$V_c(t) = \frac{80}{35 + R_1} e^{-\frac{t}{\tau}} = \frac{80}{35 + R_1} e^{-1}$$

**Problem 11**

The switch was closed for a long time. It opens at  $t=0$ . Find the total energy stored in the capacitors at  $t=0$ , given that  $C = 1\mu\text{F}$ .

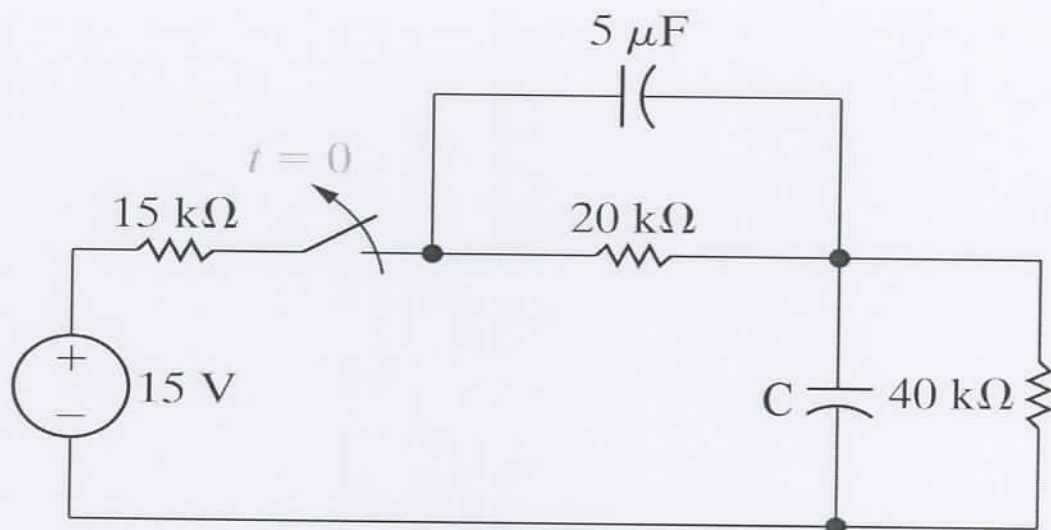**Solution**

When the switch is closed for a very long period of time, both capacitors act as open circuits and the voltage across the  $5\mu\text{F}$  and the capacitor  $C$  are the voltages across the  $20\text{K}\Omega$  and the  $40\text{K}\Omega$  resistors, respectively.

$$V_{40} = \frac{15 * 40}{15 + 20 + 40} = \frac{15 * 40}{75} = 8 \text{ Volts}$$


$$V_{20} = \frac{15 * 20}{15 + 20 + 40} = \frac{15 * 20}{75} = 4 \text{ Volts}$$

Energy stored in the capacitors is given by

$$E = \frac{1}{2}(5 * 10^{-6})(4^2) + \frac{1}{2}(C * 10^{-6})(8^2) \text{ Joules}$$

**Problem 12**

Assume in the following circuit  $L_1=3\text{ H}$ ,  $L_2=2\text{ H}$ ,  $L_3=26\text{ H}$ , and  $M=5\text{ H}$ . Find the mesh equation around  $i_2$ .

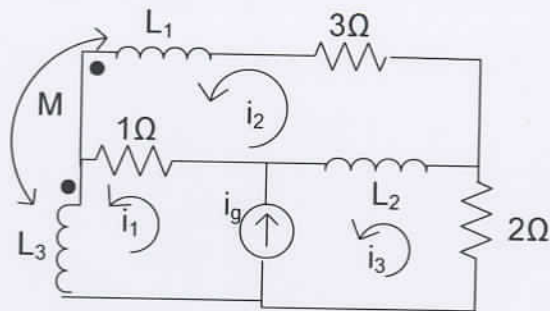**Solution**

$$3i_2 + L_1 \frac{di_2}{dt} - M \frac{di_1}{dt} + 1(i_2 - i_1) + L_2 \frac{d}{dt}(i_2 - i_3) = 0$$


$$i_g = i_1 - i_3$$

$$3i_2 + L_1 \frac{di_2}{dt} - M \frac{di_1}{dt} + 1(i_2 - i_1) + L_2 \frac{d}{dt}(i_2 - i_1 + i_g) = 0$$

$$L_2 \frac{di_g}{dt} + (L_1 + L_2) \frac{di_2}{dt} - (M + L_2) \frac{di_1}{dt} - i_1 + 4i_2 = 0$$

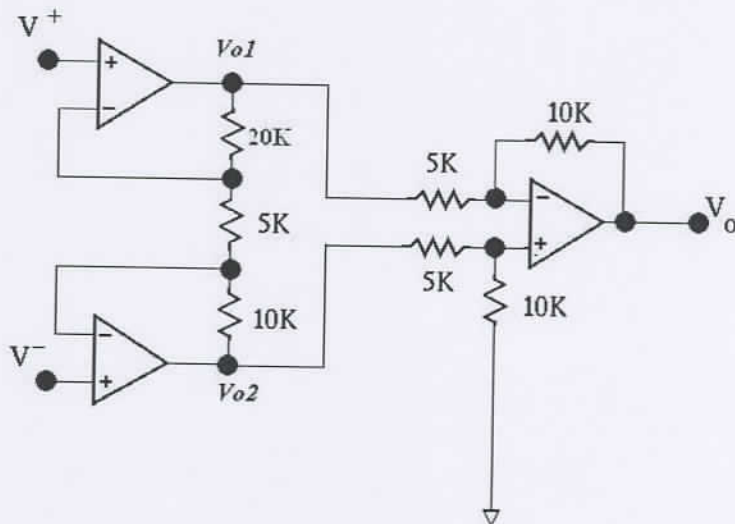
**Problem 13**

In the circuit shown below, find the output voltage  $V_o$  if  $V^+=2\text{ V}$ ,  $V^-=1\text{ V}$  assuming that all operational amplifiers are ideal and operating in their linear region.





### Solution

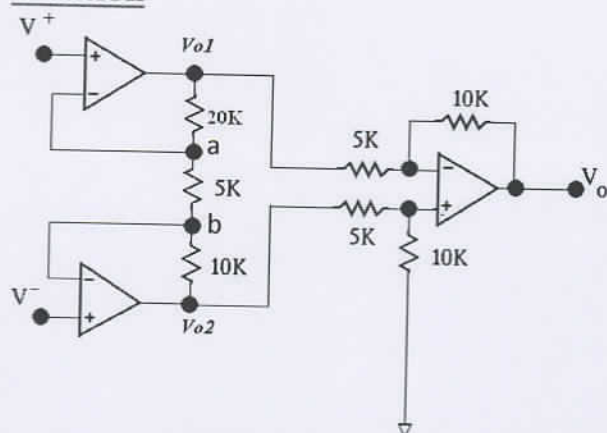

Voltage at node (a) is equal to  $V^+ = 2$  Volts and the voltage at node b is equal to  $V^- = 1$  volts. Therefore, the current in the 5K resistor (which is the same in the 10K and 20K resistors) is given by:

$$v_a - v_b = 5 \times 10^3 * i \Rightarrow i = 0.2 \text{ mA}$$


$$v_{01} - v_a = 20 \times 10^3 * 0.2 \times 10^{-3} \Rightarrow v_{01} = 4 + 2 = 6 \text{ volts}$$

$$v_b - v_{02} = 10 \times 10^3 * 0.2 \times 10^{-3} \Rightarrow v_{02} = 1 - 2 = -1 \text{ volts}$$

$$V_0 = \frac{10}{5} (v_{02} - v_{01}) = 14 \text{ volts}$$

**Problem 14**

In the circuit shown below, calculate the maximum power that can be dissipated by  $R_L$  if  $V_x = 6V$ .

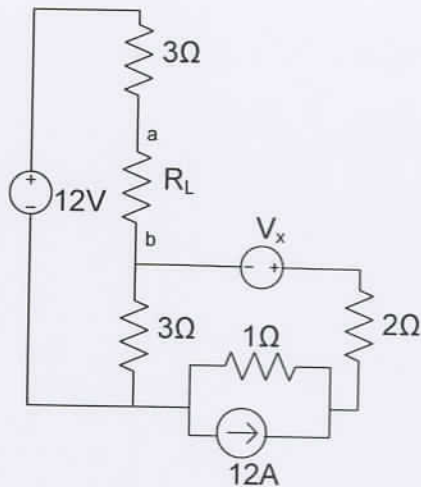**Solution**

Maximum power transfer is obtained when the load is equal to  $R_{TH}$ . Accordingly, we need to determine the Thevenin equivalent

$$R_{Th} = (2 + 1) // 3 + 3 = 4.5\Omega$$

$$V_{Th} = 12 - V_{3\Omega}$$

$V_{3\Omega}$  is the voltage across the  $3\Omega$  resistor which is obtained by converting the current source parallel to a resistor to a voltage source in series with the resistor, add the two voltage sources, and use voltage divider rule.

$$V_{3\Omega} = \frac{(12 - V_x) * 3}{6} = \frac{(12 - V_x)}{2}$$

$$V_{Th} = 12 - \frac{(12 - V_x)}{2} = \frac{12 + V_x}{2}$$

Maximum power transfer is given by:

$$P = \frac{V_{Th}^2}{4R_{Th}} = \frac{(12 + V_x)^2}{4 * 4 * 4.5} = \frac{(12 + V_x)^2}{4 * 18}$$

$$\text{For } V_x = 6 \text{ volts} \Rightarrow P = \frac{(18)^2}{4 * 18} = 4.5 \text{ Watts}$$