
6

Inductance, Capacitance, and Mutual Inductance

Assessment Problems

AP 6.1 [a] $i_g = 8e^{-300t} - 8e^{-1200t}$ A

$$v = L \frac{di_g}{dt} = -9.6e^{-300t} + 38.4e^{-1200t} \text{ V}, \quad t > 0^+$$

$$v(0^+) = -9.6 + 38.4 = 28.8 \text{ V}$$

[b] $v = 0$ when $38.4e^{-1200t} = 9.6e^{-300t}$ or $t = (\ln 4)/900 = 1.54 \text{ ms}$

[c] $p = vi = 384e^{-1500t} - 76.8e^{-600t} - 307.2e^{-2400t}$ W

[d] $\frac{dp}{dt} = 0$ when $e^{1800t} - 12.5e^{900t} + 16 = 0$

Let $x = e^{900t}$ and solve the quadratic $x^2 - 12.5x + 16 = 0$

$$x = 1.45, \quad t = \frac{\ln 1.45}{900} = 411.05 \mu\text{s}$$

$$x = 11.05, \quad t = \frac{\ln 11.05}{900} = 2.67 \text{ ms}$$

p is maximum at $t = 411.05 \mu\text{s}$

[e] $p_{\max} = 384e^{-1.5(0.41105)} - 76.8e^{-0.6(0.41105)} - 307.2e^{-2.4(0.41105)} = 32.72 \text{ W}$

[f] $i_{\max} = 8[e^{-0.3(1.54)} - e^{-1.2(1.54)}] = 3.78 \text{ A}$

$$w_{\max} = (1/2)(4 \times 10^{-3})(3.78)^2 = 28.6 \text{ mJ}$$

[g] W is max when i is max, i is max when di/dt is zero.

When $di/dt = 0$, $v = 0$, therefore $t = 1.54 \text{ ms}$.

$$\begin{aligned} \text{AP 6.2 [a]} \quad i &= C \frac{dv}{dt} = 24 \times 10^{-6} \frac{d}{dt} [e^{-15,000t} \sin 30,000t] \\ &= [0.72 \cos 30,000t - 0.36 \sin 30,000t] e^{-15,000t} \text{ A}, \quad i(0^+) = 0.72 \text{ A} \end{aligned}$$

$$\begin{aligned} \text{[b]} \quad i\left(\frac{\pi}{80} \text{ ms}\right) &= -31.66 \text{ mA}, \quad v\left(\frac{\pi}{80} \text{ ms}\right) = 20.505 \text{ V}, \\ p &= vi = -649.23 \text{ mW} \end{aligned}$$

$$\text{[c]} \quad w = \left(\frac{1}{2}\right) C v^2 = 126.13 \mu\text{J}$$

$$\begin{aligned} \text{AP 6.3 [a]} \quad v &= \left(\frac{1}{C}\right) \int_{0^-}^t i \, dx + v(0^-) \\ &= \frac{1}{0.6 \times 10^{-6}} \int_{0^-}^t 3 \cos 50,000x \, dx = 100 \sin 50,000t \text{ V} \end{aligned}$$

$$\begin{aligned} \text{[b]} \quad p(t) &= vi = [300 \cos 50,000t] \sin 50,000t \\ &= 150 \sin 100,000t \text{ W}, \quad p_{(\text{max})} = 150 \text{ W} \end{aligned}$$

$$\text{[c]} \quad w_{(\text{max})} = \left(\frac{1}{2}\right) C v_{\text{max}}^2 = 0.30(100)^2 = 3000 \mu\text{J} = 3 \text{ mJ}$$

$$\text{AP 6.4 [a]} \quad L_{\text{eq}} = \frac{60(240)}{300} = 48 \text{ mH}$$

$$\text{[b]} \quad i(0^+) = 3 + -5 = -2 \text{ A}$$

$$\text{[c]} \quad i = \frac{125}{6} \int_{0^+}^t (-0.03e^{-5x}) \, dx - 2 = 0.125e^{-5t} - 2.125 \text{ A}$$

$$\text{[d]} \quad i_1 = \frac{50}{3} \int_{0^+}^t (-0.03e^{-5x}) \, dx + 3 = 0.1e^{-5t} + 2.9 \text{ A}$$

$$i_2 = \frac{25}{6} \int_{0^+}^t (-0.03e^{-5x}) \, dx - 5 = 0.025e^{-5t} - 5.025 \text{ A}$$

$$i_1 + i_2 = i$$

$$\text{AP 6.5} \quad v_1 = 0.5 \times 10^6 \int_{0^+}^t 240 \times 10^{-6} e^{-10x} \, dx - 10 = -12e^{-10t} + 2 \text{ V}$$

$$v_2 = 0.125 \times 10^6 \int_{0^+}^t 240 \times 10^{-6} e^{-10x} \, dx - 5 = -3e^{-10t} - 2 \text{ V}$$

$$v_1(\infty) = 2 \text{ V}, \quad v_2(\infty) = -2 \text{ V}$$

$$W = \left[\frac{1}{2}(2)(4) + \frac{1}{2}(8)(4) \right] \times 10^{-6} = 20 \mu\text{J}$$

AP 6.6 [a] Summing the voltages around mesh 1 yields

$$4\frac{di_1}{dt} + 8\frac{d(i_2 + i_g)}{dt} + 20(i_1 - i_2) + 5(i_1 + i_g) = 0$$

or

$$4\frac{di_1}{dt} + 25i_1 + 8\frac{di_2}{dt} - 20i_2 = -\left(5i_g + 8\frac{di_g}{dt}\right)$$

Summing the voltages around mesh 2 yields

$$16\frac{d(i_2 + i_g)}{dt} + 8\frac{di_1}{dt} + 20(i_2 - i_1) + 780i_2 = 0$$

or

$$8\frac{di_1}{dt} - 20i_1 + 16\frac{di_2}{dt} + 800i_2 = -16\frac{di_g}{dt}$$


[b] From the solutions given in part (b)

$$i_1(0) = -0.4 - 11.6 + 12 = 0; \quad i_2(0) = -0.01 - 0.99 + 1 = 0$$

These values agree with zero initial energy in the circuit. At infinity,

$$i_1(\infty) = -0.4\text{A}; \quad i_2(\infty) = -0.01\text{A}$$

When $t = \infty$ the circuit reduces to

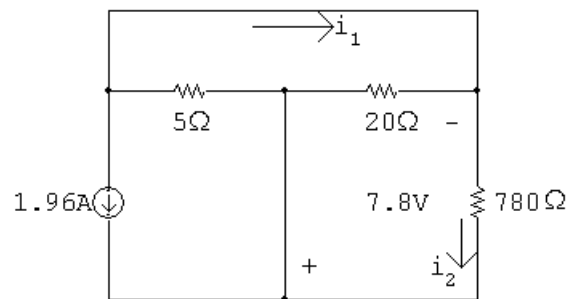

$$\therefore i_1(\infty) = -\left(\frac{7.8}{20} + \frac{7.8}{780}\right) = -0.4\text{A}; \quad i_2(\infty) = -\frac{7.8}{780} = -0.01\text{A}$$

From the solutions for i_1 and i_2 we have

$$\frac{di_1}{dt} = 46.40e^{-4t} - 60e^{-5t}$$

$$\frac{di_2}{dt} = 3.96e^{-4t} - 5e^{-5t}$$

$$\text{Also, } \frac{di_g}{dt} = 7.84e^{-4t}$$

Thus

$$4\frac{di_1}{dt} = 185.60e^{-4t} - 240e^{-5t}$$

$$25i_1 = -10 - 290e^{-4t} + 300e^{-5t}$$

$$8\frac{di_2}{dt} = 31.68e^{-4t} - 40e^{-5t}$$

$$20i_2 = -0.20 - 19.80e^{-4t} + 20e^{-5t}$$

$$5i_g = 9.8 - 9.8e^{-4t}$$

$$8\frac{di_g}{dt} = 62.72e^{-4t}$$

Test:

$$185.60e^{-4t} - 240e^{-5t} - 10 - 290e^{-4t} + 300e^{-5t} + 31.68e^{-4t} - 40e^{-5t}$$

$$+ 0.20 + 19.80e^{-4t} - 20e^{-5t} \stackrel{?}{=} -[9.8 - 9.8e^{-4t} + 62.72e^{-4t}]$$

$$-9.8 + (300 - 240 - 40 - 20)e^{-5t}$$

$$+ (185.60 - 290 + 31.68 + 19.80)e^{-4t} \stackrel{?}{=} -(9.8 + 52.92e^{-4t})$$

$$-9.8 + 0e^{-5t} + (237.08 - 290)e^{-4t} \stackrel{?}{=} -9.8 - 52.92e^{-4t}$$

$$-9.8 - 52.92e^{-4t} = -9.8 - 52.92e^{-4t} \quad (\text{OK})$$

Also,

$$8\frac{di_1}{dt} = 371.20e^{-4t} - 480e^{-5t}$$

$$20i_1 = -8 - 232e^{-4t} + 240e^{-5t}$$

$$16\frac{di_2}{dt} = 63.36e^{-4t} - 80e^{-5t}$$

$$800i_2 = -8 - 792e^{-4t} + 800e^{-5t}$$

$$16\frac{di_g}{dt} = 125.44e^{-4t}$$

Test:

$$371.20e^{-4t} - 480e^{-5t} + 8 + 232e^{-4t} - 240e^{-5t} + 63.36e^{-4t} - 80e^{-5t}$$

$$-8 - 792e^{-4t} + 800e^{-5t} \stackrel{?}{=} -125.44e^{-4t}$$

$$(8 - 8) + (800 - 480 - 240 - 80)e^{-5t}$$

$$+ (371.20 + 232 + 63.36 - 792)e^{-4t} \stackrel{?}{=} -125.44e^{-4t}$$

$$(800 - 800)e^{-5t} + (666.56 - 792)e^{-4t} \stackrel{?}{=} -125.44e^{-4t}$$

$$-125.44e^{-4t} = -125.44e^{-4t} \quad (\text{OK})$$

Problems

P 6.1 [a] $i = 0 \quad t < 0$
 $i = 50t \text{ A} \quad 0 \leq t \leq 5 \text{ ms}$
 $i = 0.5 - 50t \text{ A} \quad 5 \leq t \leq 10 \text{ ms}$
 $i = 0 \quad 10 \text{ ms} < t$

[b] $v = L \frac{di}{dt} = 20 \times 10^{-3}(50) = 1 \text{ V} \quad 0 \leq t \leq 5 \text{ ms}$

$v = 20 \times 10^{-3}(-50) = -1 \text{ V} \quad 5 \leq t \leq 10 \text{ ms}$

$v = 0 \quad t < 0$

$v = 1 \text{ V} \quad 0 < t < 5 \text{ ms}$

$v = -1 \text{ V} \quad 5 < t < 10 \text{ ms}$

$v = 0 \quad 10 \text{ ms} < t$

$p = vi$

$p = 0 \quad t < 0$

$p = (50t)(1) = 50t \text{ W} \quad 0 < t < 5 \text{ ms}$

$p = (0.5 - 50t)(-1) = 50t - 0.5 \text{ W} \quad 5 < t < 10 \text{ ms}$

$p = 0 \quad 10 \text{ ms} < t$

$w = 0 \quad t < 0$

$w = \int_0^t (50x) dx = 50 \frac{x^2}{2} \Big|_0^t = 25t^2 \text{ J} \quad 0 < t < 5 \text{ ms}$

$w = \int_{0.005}^t (50x - 0.5) dx + 0.625 \times 10^{-3}$

$= 25x^2 - 0.5x \Big|_{0.005}^t + 0.625 \times 10^{-3}$

$= 25t^2 - 0.5t + 2.5 \times 10^{-3} \text{ J} \quad 5 < t < 10 \text{ ms}$

$w = 0 \quad 10 \text{ ms} < t$

P 6.14 $i_C = C(dv/dt)$

$0 < t < 0.5 :$


$$v_c = 30t^2 \text{ V}$$

$$i_C = 20 \times 10^{-6}(60)t = 1.2t \text{ mA}$$

$0.5 < t < 1 :$

$$v_c = 30(t - 1)^2 \text{ V}$$
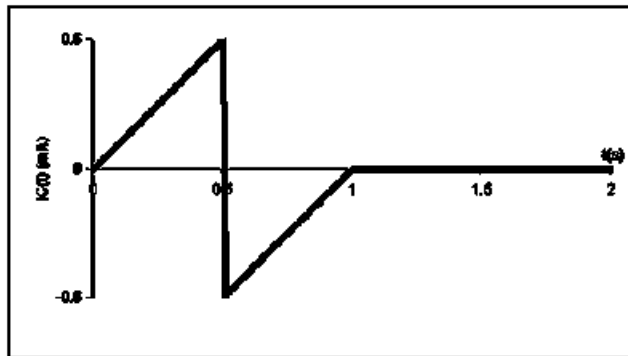
$$i_C = 20 \times 10^{-6}(60)(t - 1) = 1.2(t - 1) \text{ mA}$$



P 6.15 [a] $0 \leq t \leq 5 \mu\text{s}$

$$C = 5 \mu\text{F} \quad \frac{1}{C} = 2 \times 10^5$$

$$v = 2 \times 10^5 \int_0^t 4 dx + 12$$

$$v = 8 \times 10^5 t + 12 \text{ V} \quad 0 \leq t \leq 5 \mu\text{s}$$

$$v(5 \mu\text{s}) = 4 + 12 = 16 \text{ V}$$

[b] $5 \mu\text{s} \leq t \leq 20 \mu\text{s}$

$$v = 2 \times 10^5 \int_{5 \times 10^{-6}}^t -2 dx + 16 = -4 \times 10^5 t + 2 + 16$$

$$v = -4 \times 10^5 t + 18 \text{ V} \quad 5 \leq t \leq 20 \mu\text{s}$$

$$v(20 \mu\text{s}) = -4 \times 10^5(20 \times 10^{-6}) + 18 = 10 \text{ V}$$

[c] $20 \mu\text{s} \leq t \leq 25 \mu\text{s}$

$$v = 2 \times 10^5 \int_{20 \times 10^{-6}}^t 6 dx + 10 = 12 \times 10^5 t - 24 + 10$$

$$v = 12 \times 10^5 t - 14 \text{ V}, \quad 20 \mu\text{s} \leq t \leq 25 \mu\text{s}$$

$$v(25 \mu\text{s}) = 12 \times 10^5 (25 \times 10^{-6}) - 14 = 16 \text{ V}$$

[d] $25 \mu\text{s} \leq t \leq 35 \mu\text{s}$

$$v = 2 \times 10^5 \int_{25 \times 10^{-6}}^t 4 dx + 16 = 8 \times 10^5 t - 20 + 16$$


$$v = 8 \times 10^5 t - 4 \text{ V}, \quad 25 \mu\text{s} \leq t \leq 35 \mu\text{s}$$

$$v(35 \mu\text{s}) = 8 \times 10^5 (35 \times 10^{-6}) - 4 = 24 \text{ V}$$

[e] $35 \mu\text{s} \leq t < \infty$

$$v = 2 \times 10^5 \int_{35 \times 10^{-6}}^t 0 dx + 24 = 24$$
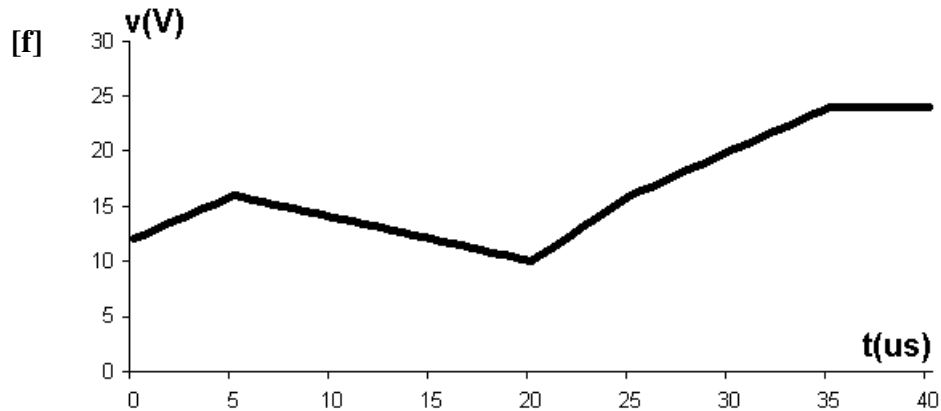
$$v = 24 \text{ V}, \quad 35 \mu\text{s} \leq t < \infty$$



P 6.21 $30 \parallel 20 = 12 \text{ H}$


$$80 \parallel (8 + 12) = 16 \text{ H}$$

$$60 \parallel (14 + 16) = 20 \text{ H}$$

$$15 \parallel (20 + 10) = 20 \text{ H}$$

$$L_{ab} = 5 + 10 = 15 \text{ H}$$

P 6.22 [a]

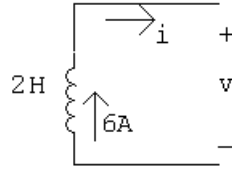

$$i(t) = -\frac{1}{2} \int_0^t 12e^{-x} dx + 6$$

$$= 6e^{-x} \Big|_0^t + 6$$

$$= 6e^{-t} - 6 + 6$$

$$i(t) = 6e^{-t} \text{ A}, \quad t \geq 0$$

$$\text{[b]} \quad i_1(t) = -\frac{1}{3} \int_0^t 12e^{-x} dx + 2$$

$$= 4e^{-x} \Big|_0^t + 2$$

$$= 4(e^{-t} - 1) + 2$$

$$i_1(t) = 4e^{-t} - 2 \text{ A}, \quad t \geq 0$$

$$\text{[c]} \quad i_2(t) = -\frac{1}{6} \int_0^t 12e^{-x} dx + 4$$

$$= 2e^{-x} \Big|_0^t + 4$$

$$= 2(e^{-t} - 1) + 4$$

$$i_2(t) = 2e^{-t} + 2 \text{ A}, \quad t \geq 0$$

$$\text{[d]} \quad p = vi = (12e^{-t})(6e^{-t}) = 72e^{-2t} \text{ W}$$

$$w = \int_0^\infty p dt = \int_0^\infty 72e^{-2t} dt$$

$$= 72 \frac{e^{-2t}}{-2} \Big|_0^\infty$$

$$= 36 \text{ J}$$

$$\text{[e]} \quad w = \frac{1}{2}(3)(2)^2 + \frac{1}{2}(6)(4)^2 = 54 \text{ J}$$

$$\text{[f]} \quad w_{\text{trapped}} = \frac{1}{2}(3)(-2)^2 + \frac{1}{2}(6)(2)^2 = 18 \text{ J}$$

$$w_{\text{trapped}} = 54 - 36 = 18 \text{ J} \quad \text{checks}$$


[g] Yes, they agree.

P 6.26 Work from the right hand side of the circuit, simplifying step by step:

1. $48 \mu\text{F}$ in series with $16 \mu\text{F}$: $1/C = 1/16 \mu + 1/48 \mu \quad \therefore \quad C = 12 \mu\text{F}$
The voltages add in series, so the $12 \mu\text{F}$ capacitor has a voltage of 20 V , negative at the top.
2. Previous $12 \mu\text{F}$ in parallel with $3 \mu\text{F}$: $C = 12 \mu + 3 \mu = 15 \mu\text{F}$
The voltage is 20 V , negative at the top.
3. Previous $15 \mu\text{F}$ in series with $30 \mu\text{F}$:
 $1/C = 1/15 \mu + 1/30 \mu \quad \therefore \quad C = 10 \mu\text{F}$
The voltages add in series, so the $10 \mu\text{F}$ capacitor has a voltage of 10 V , positive at the right.
4. Previous $10 \mu\text{F}$ in parallel with $10 \mu\text{F}$: $C = 10 \mu + 10 \mu = 20 \mu\text{F}$
The voltage is 10 V , negative at the top.
5. Previous $20 \mu\text{F}$ in series with $5 \mu\text{F}$ and $4 \mu\text{F}$:
 $1/C = 1/20 \mu + 1/5 \mu + 1/4 \mu \quad \therefore \quad C = 2 \mu\text{F}$
The voltages in series add: $5\text{V} - 10\text{V} + 30\text{V} = 25\text{V}$ positive at the top.

The equivalent capacitance is $2 \mu\text{F}$ with a voltage of 25 V , positive at the top.

P 6.27 [a]

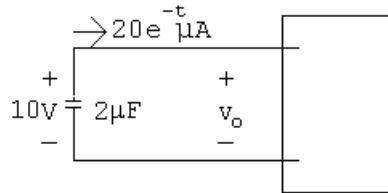

$$\begin{aligned}
 v_o &= -\frac{1}{2 \times 10^{-6}} \int_0^t 20 \times 10^{-6} e^{-x} dx + 10 \\
 &= 10e^{-x} \Big|_0^t + 10 \\
 &= 10e^{-t} \text{ V}, \quad t \geq 0
 \end{aligned}$$

$$\begin{aligned}
 \text{[b]} \quad v_1 &= -\frac{1}{3 \times 10^{-6}} (20 \times 10^{-6}) e^{-x} \Big|_0^t + 4 \\
 &= 6.67e^{-t} - 2.67 \text{ V}, \quad t \geq 0
 \end{aligned}$$

$$\begin{aligned}
 \text{[c]} \quad v_2 &= -\frac{1}{6 \times 10^{-6}} (20 \times 10^{-6}) e^{-x} \Big|_0^t + 6 \\
 &= 3.33e^{-t} + 2.67 \text{ V}, \quad t \geq 0
 \end{aligned}$$

$$\begin{aligned}
 \text{[d]} \quad p &= vi = (10e^{-t})(20 \times 10^{-6})e^{-t} \\
 &= 200 \times 10^{-6} e^{-2t}
 \end{aligned}$$

$$\begin{aligned}
 w &= \int_0^{\infty} 200 \times 10^{-6} e^{-2t} dt \\
 &= 200 \times 10^{-6} \left. \frac{e^{-2t}}{-2} \right|_0^{\infty} \\
 &= -100 \times 10^{-6} (0 - 1) = 100 \mu\text{J}
 \end{aligned}$$

$$\begin{aligned}
 \text{[e]} \quad w &= \frac{1}{2}(3 \times 10^{-6})(4)^2 + \frac{1}{2}(6 \times 10^{-9})(6)^2 \\
 &= 132 \mu\text{J}
 \end{aligned}$$

$$\begin{aligned}
 \text{[f]} \quad w_{\text{trapped}} &= \frac{1}{2}(3 \times 10^{-6})(8/3)^2 + \frac{1}{2}(6 \times 10^{-6})(8/3)^2 \\
 &= 32 \mu\text{J}
 \end{aligned}$$

$$\text{CHECK: } 100 + 32 = 132 \mu\text{J}$$

[g] Yes, they agree.

$$\text{P 6.34 [a]} \quad -2 \frac{di_g}{dt} + 16 \frac{di_2}{dt} + 32i_2 = 0$$

$$16 \frac{di_2}{dt} + 32i_2 = 2 \frac{di_g}{dt}$$

$$\text{[b]} \quad i_2 = e^{-t} - e^{-2t} \text{ A}$$

$$\frac{di_2}{dt} = -e^{-t} + 2e^{-2t} \text{ A/s}$$

$$i_g = 8 - 8e^{-t} \text{ A}$$

$$\frac{di_g}{dt} = 8e^{-t} \text{ A/s}$$

$$\therefore -16e^{-t} + 32e^{-2t} + 32e^{-t} - 32e^{-2t} = 16e^{-t}$$

$$\begin{aligned}
 \text{[c]} \quad v_1 &= 4 \frac{di_g}{dt} - 2 \frac{di_2}{dt} \\
 &= 4(8e^{-t}) - 2(-e^{-t} + 2e^{-2t}) \\
 &= 34e^{-t} - 4e^{-2t} \text{ V}, \quad t > 0
 \end{aligned}$$

$$\text{[d]} \quad v_1(0) = 34 - 4 = 30 \text{ V}; \quad \text{Also}$$

$$\begin{aligned}
 v_1(0) &= 4 \frac{di_g}{dt}(0) - 2 \frac{di_2}{dt}(0) \\
 &= 4(8) - 2(-1 + 2) = 32 - 2 = 30 \text{ V}
 \end{aligned}$$

Yes, the initial value of v_1 is consistent with known circuit behavior.