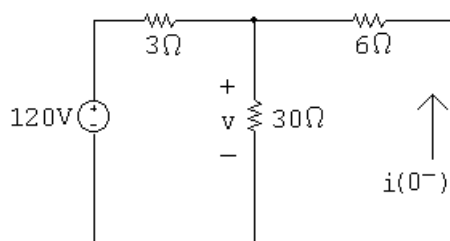


Response of First-Order RL and RC Circuits

Assessment Problems

AP 7.1 [a] The circuit for $t < 0$ is shown below. Note that the inductor behaves like a short circuit, effectively eliminating the $2\ \Omega$ resistor from the circuit.



First combine the $30\ \Omega$ and $6\ \Omega$ resistors in parallel:

$$30 \parallel 6 = 5\ \Omega$$

Use voltage division to find the voltage drop across the parallel resistors:

$$v = \frac{5}{5+3}(120) = 75\ \text{V}$$

Now find the current using Ohm's law:

$$i(0^-) = -\frac{v}{6} = -\frac{75}{6} = -12.5\ \text{A}$$

$$\text{[b]} \quad w(0) = \frac{1}{2}Li^2(0) = \frac{1}{2}(8 \times 10^{-3})(12.5)^2 = 625\ \text{mJ}$$

[c] To find the time constant, we need to find the equivalent resistance seen by the inductor for $t > 0$. When the switch opens, only the $2\ \Omega$ resistor remains connected to the inductor. Thus,


$$\tau = \frac{L}{R} = \frac{8 \times 10^{-3}}{2} = 4\ \text{ms}$$

$$\text{[d]} \quad i(t) = i(0^-)e^{t/\tau} = -12.5e^{-t/0.004} = -12.5e^{-250t}\ \text{A}, \quad t \geq 0$$

$$\text{[e]} \quad i(5\ \text{ms}) = -12.5e^{-250(0.005)} = -12.5e^{-1.25} = -3.58\ \text{A}$$

$$\begin{aligned} \text{So } w(5 \text{ ms}) &= \frac{1}{2}Li^2(5 \text{ ms}) = \frac{1}{2}(8) \times 10^{-3}(3.58)^2 = 51.3 \text{ mJ} \\ w(\text{dis}) &= 625 - 51.3 = 573.7 \text{ mJ} \\ \% \text{ dissipated} &= \left(\frac{573.7}{625}\right) 100 = 91.8\% \end{aligned}$$

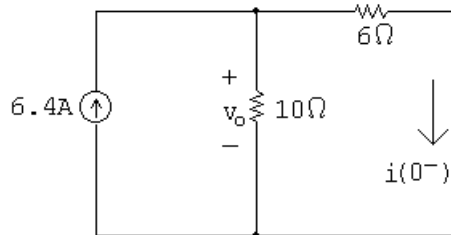
AP 7.2 [a] First, use the circuit for $t < 0$ to find the initial current in the inductor:



Using current division,

$$i(0^-) = \frac{10}{10 + 6}(6.4) = 4 \text{ A}$$

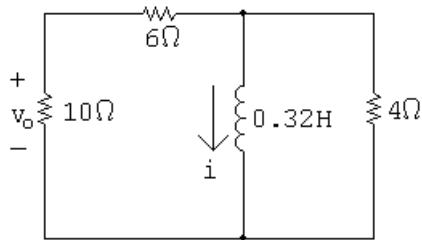Now use the circuit for $t > 0$ to find the equivalent resistance seen by the inductor, and use this value to find the time constant:



$$R_{\text{eq}} = 4 \parallel (6 + 10) = 3.2 \Omega, \quad \therefore \quad \tau = \frac{L}{R_{\text{eq}}} = \frac{0.32}{3.2} = 0.1 \text{ s}$$

Use the initial inductor current and the time constant to find the current in the inductor:

$$i(t) = i(0^-)e^{-t/\tau} = 4e^{-t/0.1} = 4e^{-10t} \text{ A}, \quad t \geq 0$$

Use current division to find the current in the 10Ω resistor:

$$i_o(t) = \frac{4}{4 + 10 + 6}(-i) = \frac{4}{20}(-4e^{-10t}) = -0.8e^{-10t} \text{ A}, \quad t \geq 0^+$$

Finally, use Ohm's law to find the voltage drop across the 10Ω resistor:

$$v_o(t) = 10i_o = 10(-0.8e^{-10t}) = -8e^{-10t} \text{ V}, \quad t \geq 0^+$$

[b] The initial energy stored in the inductor is

$$w(0) = \frac{1}{2}Li^2(0^-) = \frac{1}{2}(0.32)(4)^2 = 2.56 \text{ J}$$

Find the energy dissipated in the 4Ω resistor by integrating the power over all time:

$$v_{4\Omega}(t) = L \frac{di}{dt} = 0.32(-10)(4e^{-10t}) = -12.8e^{-10t} \text{ V}, \quad t \geq 0^+$$


$$p_{4\Omega}(t) = \frac{v_{4\Omega}^2}{4} = 40.96e^{-20t} \text{ W}, \quad t \geq 0^+$$

$$w_{4\Omega}(t) = \int_0^\infty 40.96e^{-20t} dt = 2.048 \text{ J}$$

Find the percentage of the initial energy in the inductor dissipated in the 4Ω resistor:

$$\% \text{ dissipated} = \left(\frac{2.048}{2.56} \right) 100 = 80\%$$

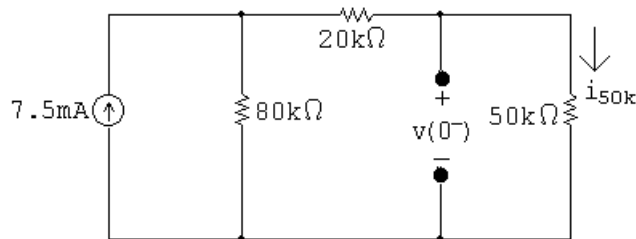AP 7.3 [a] The circuit for $t < 0$ is shown below. Note that the capacitor behaves like an open circuit.



Find the voltage drop across the open circuit by finding the voltage drop across the $50 \text{ k}\Omega$ resistor. First use current division to find the current through the $50 \text{ k}\Omega$ resistor:

$$i_{50\text{k}} = \frac{80 \times 10^3}{80 \times 10^3 + 20 \times 10^3 + 50 \times 10^3} (7.5 \times 10^{-3}) = 4 \text{ mA}$$

Use Ohm's law to find the voltage drop:

$$v(0^-) = (50 \times 10^3) i_{50\text{k}} = (50 \times 10^3)(0.004) = 200 \text{ V}$$

[b] To find the time constant, we need to find the equivalent resistance seen by the capacitor for $t > 0$. When the switch opens, only the $50 \text{ k}\Omega$ resistor remains connected to the capacitor. Thus,

$$\tau = RC = (50 \times 10^3)(0.4 \times 10^{-6}) = 20 \text{ ms}$$

$$\text{[c]} \quad v(t) = v(0^-)e^{-t/\tau} = 200e^{-t/0.02} = 200e^{-50t} \text{ V}, \quad t \geq 0$$


$$\text{[d]} \quad w(0) = \frac{1}{2}Cv^2 = \frac{1}{2}(0.4 \times 10^{-6})(200)^2 = 8 \text{ mJ}$$

$$\text{[e]} \quad w(t) = \frac{1}{2}Cv^2(t) = \frac{1}{2}(0.4 \times 10^{-6})(200e^{-50t})^2 = 8e^{-100t} \text{ mJ}$$

The initial energy is 8 mJ, so when 75% is dissipated, 2 mJ remains:

$$8 \times 10^{-3}e^{-100t} = 2 \times 10^{-3}, \quad e^{100t} = 4, \quad t = (\ln 4)/100 = 13.86 \text{ ms}$$

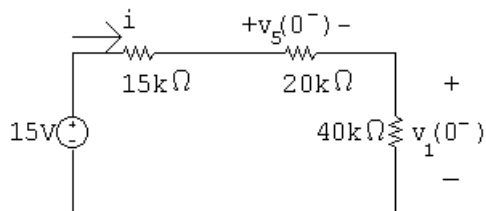AP 7.4 [a] This circuit is actually two RC circuits in series, and the requested voltage, v_o , is the sum of the voltage drops for the two RC circuits. The circuit for $t < 0$ is shown below:



Find the current in the loop and use it to find the initial voltage drops across the two RC circuits:

$$i = \frac{15}{75,000} = 0.2 \text{ mA}, \quad v_5(0^-) = 4 \text{ V}, \quad v_1(0^-) = 8 \text{ V}$$

There are two time constants in the circuit, one for each RC subcircuit. τ_5 is the time constant for the $5 \mu\text{F} - 20 \text{ k}\Omega$ subcircuit, and τ_1 is the time constant for the $1 \mu\text{F} - 40 \text{ k}\Omega$ subcircuit:

$$\tau_5 = (20 \times 10^3)(5 \times 10^{-6}) = 100 \text{ ms}; \quad \tau_1 = (40 \times 10^3)(1 \times 10^{-6}) = 40 \text{ ms}$$

Therefore,

$$v_5(t) = v_5(0^-)e^{-t/\tau_5} = 4e^{-t/0.1} = 4e^{-10t} \text{ V}, \quad t \geq 0$$

$$v_1(t) = v_1(0^-)e^{-t/\tau_1} = 8e^{-t/0.04} = 8e^{-25t} \text{ V}, \quad t \geq 0$$

Finally,

$$v_o(t) = v_1(t) + v_5(t) = [8e^{-25t} + 4e^{-10t}] \text{ V}, \quad t \geq 0$$

[b] Find the value of the voltage at 60 ms for each subcircuit and use the voltage to find the energy at 60 ms:

$$v_1(60 \text{ ms}) = 8e^{-25(0.06)} \cong 1.79 \text{ V}, \quad v_5(60 \text{ ms}) = 4e^{-10(0.06)} \cong 2.20 \text{ V}$$

$$w_1(60 \text{ ms}) = \frac{1}{2}Cv_1^2(60 \text{ ms}) = \frac{1}{2}(1 \times 10^{-6})(1.79)^2 \cong 1.59 \mu\text{J}$$

$$w_5(60 \text{ ms}) = \frac{1}{2}Cv_5^2(60 \text{ ms}) = \frac{1}{2}(5 \times 10^{-6})(2.20)^2 \cong 12.05 \mu\text{J}$$

$$w(60 \text{ ms}) = 1.59 + 12.05 = 13.64 \mu\text{J}$$

Find the initial energy from the initial voltage:


$$w(0) = w_1(0) + w_2(0) = \frac{1}{2}(1 \times 10^{-6})(8)^2 + \frac{1}{2}(5 \times 10^{-6})(4)^2 = 72 \mu\text{J}$$

Now calculate the energy dissipated at 60 ms and compare it to the initial energy:

$$w_{\text{diss}} = w(0) - w(60 \text{ ms}) = 72 - 13.64 = 58.36 \mu\text{J}$$

$$\% \text{ dissipated} = (58.36 \times 10^{-6} / 72 \times 10^{-6})(100) = 81.05 \%$$

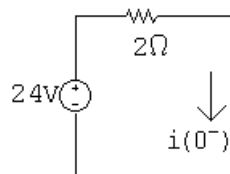
- AP 7.5 [a] Use the circuit at $t < 0$, shown below, to calculate the initial current in the inductor:



$$i(0^-) = 24/2 = 12 \text{ A} = i(0^+)$$

Note that $i(0^-) = i(0^+)$ because the current in an inductor is continuous.

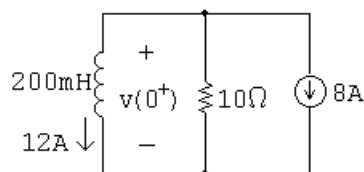- [b] Use the circuit at $t = 0^+$, shown below, to calculate the voltage drop across the inductor at 0^+ . Note that this is the same as the voltage drop across the 10Ω resistor, which has current from two sources — 8 A from the current source and 12 A from the initial current through the inductor.




$$v(0^+) = -10(8 + 12) = -200 \text{ V}$$

- [c] To calculate the time constant we need the equivalent resistance seen by the inductor for $t > 0$. Only the 10Ω resistor is connected to the inductor for $t > 0$. Thus,

$$\tau = L/R = (200 \times 10^{-3}/10) = 20 \text{ ms}$$

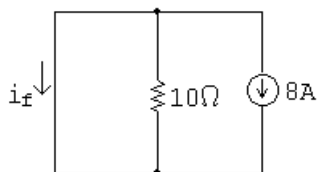- [d] To find $i(t)$, we need to find the final value of the current in the inductor. When the switch has been in position a for a long time, the circuit reduces to the one below:



Note that the inductor behaves as a short circuit and all of the current from the 8 A source flows through the short circuit. Thus,

$$i_f = -8 \text{ A}$$


Now,

$$\begin{aligned} i(t) &= i_f + [i(0^+) - i_f]e^{-t/\tau} = -8 + [12 - (-8)]e^{-t/0.02} \\ &= -8 + 20e^{-50t} \text{ A}, \quad t \geq 0 \end{aligned}$$

- [e] To find $v(t)$, use the relationship between voltage and current for an inductor:

$$v(t) = L \frac{di(t)}{dt} = (200 \times 10^{-3})(-50)(20e^{-50t}) = -200e^{-50t} \text{ V}, \quad t \geq 0^+$$

AP 7.6 [a]

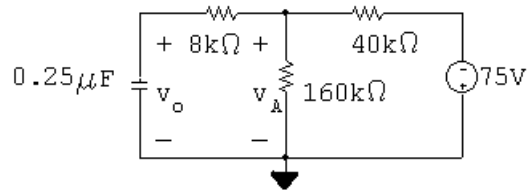

From Example 7.6,

$$v_o(t) = -60 + 90e^{-100t} \text{ V}$$

Write a KVL equation at the top node and use it to find the relationship between v_o and v_A :

$$\frac{v_A - v_o}{8000} + \frac{v_A}{160,000} + \frac{v_A + 75}{40,000} = 0$$

$$20v_A - 20v_o + v_A + 4v_A + 300 = 0$$

$$25v_A = 20v_o - 300$$


$$v_A = 0.8v_o - 12$$

Use the above equation for v_A in terms of v_o to find the expression for v_A :

$$v_A(t) = 0.8(-60 + 90e^{-100t}) - 12 = -60 + 72e^{-100t} \text{ V}, \quad t \geq 0^+$$

[b] $t \geq 0^+$, since there is no requirement that the voltage be continuous in a resistor.

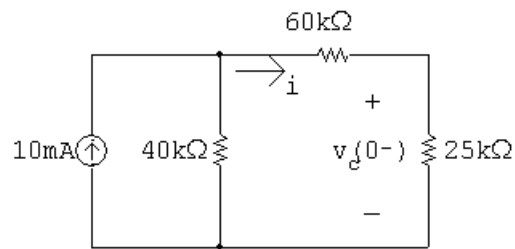
AP 7.7 [a] Use the circuit shown below, for $t < 0$, to calculate the initial voltage drop across the capacitor:



$$i = \left(\frac{40 \times 10^3}{125 \times 10^3} \right) (10 \times 10^{-3}) = 3.2 \text{ mA}$$

$$v_c(0^-) = (3.2 \times 10^{-3})(25 \times 10^3) = 80 \text{ V} \quad \text{so} \quad v_c(0^+) = 80 \text{ V}$$

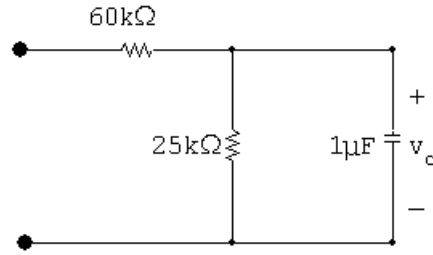Now use the next circuit, valid for $0 \leq t \leq 10$ ms, to calculate $v_c(t)$ for that interval:



For $0 \leq t \leq 100$ ms:


$$\tau = RC = (25 \times 10^3)(1 \times 10^{-6}) = 25 \text{ ms}$$

$$v_c(t) = v_c(0^-)e^{t/\tau} = 80e^{-40t} \text{ V}, \quad 0 \leq t \leq 10 \text{ ms}$$

[b] Calculate the starting capacitor voltage in the interval $t \geq 10$ ms, using the capacitor voltage from the previous interval:

$$v_c(0.01) = 80e^{-40(0.01)} = 53.63 \text{ V}$$

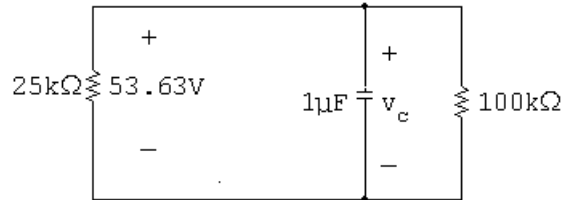Now use the next circuit, valid for $t \geq 10$ ms, to calculate $v_c(t)$ for that interval:



For $t \geq 10$ ms :

$$R_{\text{eq}} = 25 \text{ k}\Omega \parallel 100 \text{ k}\Omega = 20 \text{ k}\Omega$$

$$\tau = R_{\text{eq}}C = (20 \times 10^3)(1 \times 10^{-6}) = 0.02 \text{ s}$$

$$\text{Therefore } v_c(t) = v_c(0.01^+)e^{-(t-0.01)/\tau} = 53.63e^{-50(t-0.01)} \text{ V}, \quad t \geq 0.01 \text{ s}$$

[c] To calculate the energy dissipated in the 25 kΩ resistor, integrate the power absorbed by the resistor over all time. Use the expression $p = v^2/R$ to calculate the power absorbed by the resistor.

$$w_{25 \text{ k}} = \int_0^{0.01} \frac{[80e^{-40t}]^2}{25,000} dt + \int_{0.01}^{\infty} \frac{[53.63e^{-50(t-0.01)}]^2}{25,000} dt = 2.91 \text{ mJ}$$

[d] Repeat the process in part (c), but recognize that the voltage across this resistor is non-zero only for the second interval:

$$w_{100 \text{ k}\Omega} = \int_{0.01}^{\infty} \frac{[53.63e^{-50(t-0.01)}]^2}{100,000} dt = 0.29 \text{ mJ}$$

We can check our answers by calculating the initial energy stored in the capacitor. All of this energy must eventually be dissipated by the 25 kΩ resistor and the 100 kΩ resistor.

$$\text{Check: } w_{\text{stored}} = (1/2)(1 \times 10^{-6})(80)^2 = 3.2 \text{ mJ}$$


$$w_{\text{diss}} = 2.91 + 0.29 = 3.2 \text{ mJ}$$

AP 7.8 [a] Note – the $30\ \Omega$ resistor should be a $3\ \Omega$ resistor; the resistor in parallel with the $8\ \text{A}$ current source should be $9\ \Omega$.

Prior to switch a closing at $t = 0$, there are no sources connected to the inductor; thus, $i(0^-) = 0$.

At the instant A is closed, $i(0^+) = 0$.

For $0 \leq t \leq 1\ \text{s}$,

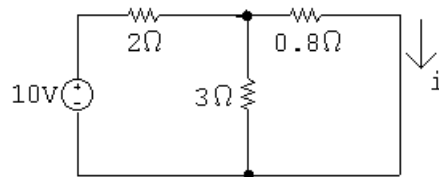

The equivalent resistance seen by the $10\ \text{V}$ source is $2 + (3 \parallel 0.8)$. The current leaving the $10\ \text{V}$ source is

$$\frac{10}{2 + (3 \parallel 0.8)} = 3.8\ \text{A}$$

The final current in the inductor, which is equal to the current in the $0.8\ \Omega$ resistor is

$$i(\infty) = \frac{3}{3 + 0.8}(3.8) = 3\ \text{A}$$

The resistance seen by the inductor is calculated to find the time constant:

$$0.8 + (2 \parallel 3) = 2\ \Omega \quad \tau = \frac{L}{R} = \frac{2}{2} = 1\ \text{s}$$


Therefore,

$$i = i(\infty) + [i(0^+) - i(\infty)]e^{-t/\tau} = 3 - 3e^{-t}\ \text{A}, \quad 0 \leq t \leq 1\ \text{s}$$

For part (b) we need the value of $i(t)$ at $t = 1\ \text{s}$:

$$i(1) = 3 - 3e^{-1} = 1.896\ \text{A}$$

[b] For $t > 1\ \text{s}$

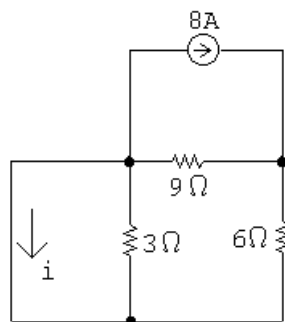

Use current division to find the final value of the current:

$$i = \frac{9}{9 + 6}(-8) = -4.8\ \text{A}$$


The equivalent resistance seen by the inductor is used to calculate the time constant:

$$3 \parallel (9 + 6) = 2.5 \Omega \quad \tau = \frac{L}{R} = \frac{2}{2.5} = 0.8 \text{ s}$$

Therefore,

$$\begin{aligned} i &= i(\infty) + [i(1^+) - i(\infty)]e^{-(t-1)/\tau} \\ &= -4.8 + 6.696e^{-1.25(t-1)} \text{ A}, \quad t \geq 1 \text{ s} \end{aligned}$$

AP 7.9 $0 \leq t \leq 32 \text{ ms}$:

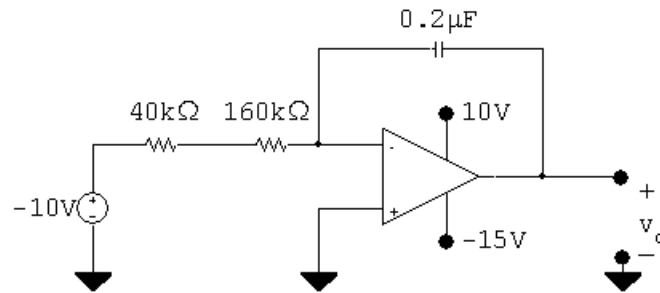


$$v_o = -\frac{1}{RC_f} \int_0^{32 \times 10^{-3}} -10 dt + 0 = -\frac{1}{RC_f} (-10t) \Big|_0^{32 \times 10^{-3}} = -\frac{1}{RC_f} (-320 \times 10^{-3})$$

$$RC_f = (200 \times 10^3)(0.2 \times 10^{-6}) = 40 \times 10^{-3} \quad \text{so} \quad \frac{1}{RC_f} = 25$$

$$v_o = -25(-320 \times 10^{-3}) = 8 \text{ V}$$

$t \geq 32 \text{ ms}$:

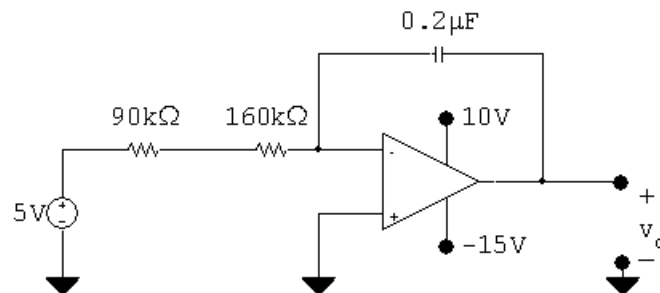

$$v_o = -\frac{1}{RC_f} \int_{32 \times 10^{-3}}^t 5 dy + 8 = -\frac{1}{RC_f} (5y) \Big|_{32 \times 10^{-3}}^t + 8 = -\frac{1}{RC_f} 5(t - 32 \times 10^{-3}) + 8$$

$$RC_f = (250 \times 10^3)(0.2 \times 10^{-6}) = 50 \times 10^{-3} \quad \text{so} \quad \frac{1}{RC_f} = 20$$

$$v_o = -20(5)(t - 32 \times 10^{-3}) + 8 = -100t + 11.2$$

The output will saturate at the negative power supply value:

$$-15 = -100t + 11.2 \quad \therefore \quad t = 262 \text{ ms}$$

AP 7.10 [a] Use RC circuit analysis to determine the expression for the voltage at the non-inverting input:

$$v_p = V_f + [V_o - V_f]e^{-t/\tau} = -2 + (0 + 2)e^{-t/\tau}$$

$$\tau = (160 \times 10^3)(10 \times 10^{-9}) = 10^{-3}; \quad 1/\tau = 625$$

$$v_p = -2 + 2e^{-625t} \text{ V}; \quad v_n = v_p$$

Write a KVL equation at the inverting input, and use it to determine v_o :

$$\frac{v_n}{10,000} + \frac{v_n - v_o}{40,000} = 0$$

$$\therefore v_o = 5v_n = 5v_p = -10 + 10e^{-625t} \text{ V}$$

The output will saturate at the negative power supply value:

$$-10 + 10e^{-625t} = -5; \quad e^{-625t} = 1/2; \quad t = \ln 2/625 = 1.11 \text{ ms}$$

[b] Use RC circuit analysis to determine the expression for the voltage at the non-inverting input:

$$v_p = V_f + [V_o - V_f]e^{-t/\tau} = -2 + (1 + 2)e^{-625t} = -2 + 3e^{-625t} \text{ V}$$


The analysis for v_o is the same as in part (a):

$$v_o = 5v_p = -10 + 15e^{-625t} \text{ V}$$

The output will saturate at the negative power supply value:

$$-10 + 15e^{-625t} = -5; \quad e^{-625t} = 1/3; \quad t = \ln 3/625 = 1.76 \text{ ms}$$

Problems

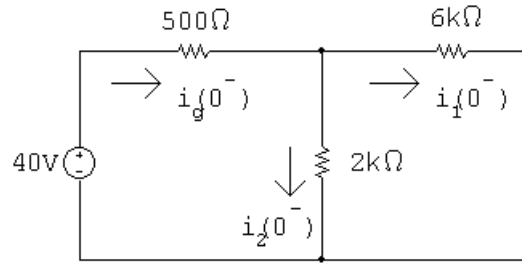P 7.1 [a] $t < 0$ 

$$2\text{ k}\Omega \parallel 6\text{ k}\Omega = 1.5\text{ k}\Omega$$

Find the current from the voltage source by combining the resistors in series and parallel and using Ohm's law:

$$i_g(0^-) = \frac{40}{(1500 + 500)} = 20\text{ mA}$$

Find the branch currents using current division:

$$i_1(0^-) = \frac{2000}{8000}(0.02) = 5\text{ mA}$$

$$i_2(0^-) = \frac{6000}{8000}(0.02) = 15\text{ mA}$$

[b] The current in an inductor is continuous. Therefore,

$$i_1(0^+) = i_1(0^-) = 5\text{ mA}$$

$$i_2(0^+) = -i_1(0^+) = -5\text{ mA} \quad (\text{when switch is open})$$

$$\text{[c]} \quad \tau = \frac{L}{R} = \frac{0.4 \times 10^{-3}}{8 \times 10^3} = 5 \times 10^{-5}\text{ s}; \quad \frac{1}{\tau} = 20,000$$

$$i_1(t) = i_1(0^+)e^{-t/\tau} = 5e^{-20,000t}\text{ mA}, \quad t \geq 0$$

$$\text{[d]} \quad i_2(t) = -i_1(t) \quad \text{when } t \geq 0^+$$

$$\therefore i_2(t) = -5e^{-20,000t}\text{ mA}, \quad t \geq 0^+$$

[e] The current in a resistor can change instantaneously. The switching operation forces $i_2(0^-)$ to equal 15 mA and $i_2(0^+) = -5\text{ mA}$.

P 7.2 [a] $i(0) = 60 \text{ V} / (10 \Omega + 5 \Omega) = 4 \text{ A}$

[b] $\tau = \frac{L}{R} = \frac{4}{45 + 5} = 80 \text{ ms}$

[c] $i = 4e^{-t/0.08} = 4e^{-12.5t} \text{ A}, \quad t \geq 0$

$$v_1 = -45i = -180e^{-12.5t} \text{ V} \quad t \geq 0^+$$

$$v_2 = L \frac{di}{dt} = (4)(-12.5)(4e^{-12.5t}) = -200e^{-12.5t} \text{ V} \quad t \geq 0^+$$

[d] $p_{\text{diss}} = i^2(45) = 720e^{-25t} \text{ W}$

$$w_{\text{diss}} = \int_0^t 720e^{-25x} dx = 720 \frac{e^{-25x}}{-25} \Big|_0^t = 28.8 - 28.8e^{-25t} \text{ J}$$


$$w_{\text{diss}}(40 \text{ ms}) = 28.8 - 28.8e^{-1} = 18.205 \text{ J}$$

$$w(0) = \frac{1}{2}(4)(4)^2 = 32 \text{ J}$$

$$\% \text{ dissipated} = \frac{18.205}{32}(100) = 56.89\%$$

P 7.3 [a] $i_o(0^-) = 0$ since the switch is open for $t < 0$.

[b] For $t = 0^-$ the circuit is:

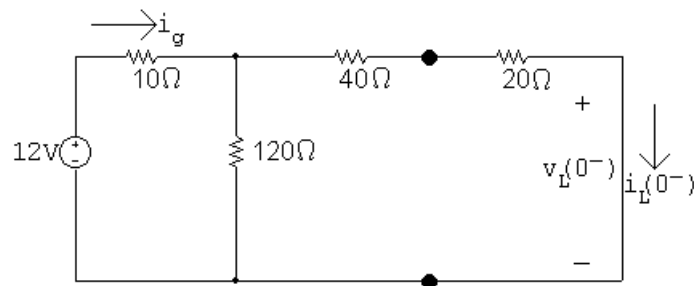


$$120 \Omega \parallel 60 \Omega = 40 \Omega$$

$$\therefore i_g = \frac{12}{10 + 40} = 0.24 \text{ A} = 240 \text{ mA}$$

$$i_L(0^-) = \left(\frac{120}{180} \right) i_g = 160 \text{ mA}$$

[c] For $t = 0^+$ the circuit is:

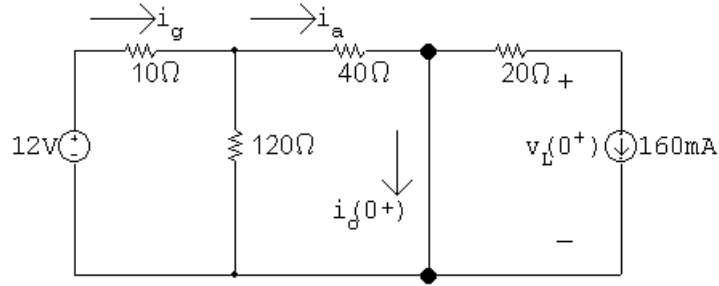

$$120\ \Omega \parallel 40\ \Omega = 30\ \Omega$$

$$\therefore i_g = \frac{12}{10 + 30} = 0.30\ \text{A} = 300\ \text{mA}$$

$$i_a = \left(\frac{120}{160}\right) 300 = 225\ \text{mA}$$

$$\therefore i_o(0^+) = 225 - 160 = 65\ \text{mA}$$

[d] $i_L(0^+) = i_L(0^-) = 160\ \text{mA}$

[e] $i_o(\infty) = i_a = 225\ \text{mA}$

[f] $i_L(\infty) = 0$, since the switch short circuits the branch containing the $20\ \Omega$ resistor and the $100\ \text{mH}$ inductor.

[g] $\tau = \frac{L}{R} = \frac{100 \times 10^{-3}}{20} = 5\ \text{ms}; \quad \frac{1}{\tau} = 200$

$$\therefore i_L = 0 + (160 - 0)e^{-200t} = 160e^{-200t}\ \text{mA}, \quad t \geq 0$$

[h] $v_L(0^-) = 0$ since for $t < 0$ the current in the inductor is constant

[i] Refer to the circuit at $t = 0^+$ and note:

$$20(0.16) + v_L(0^+) = 0; \quad \therefore v_L(0^+) = -3.2\ \text{V}$$


[j] $v_L(\infty) = 0$, since the current in the inductor is a constant at $t = \infty$.

[k] $v_L(t) = 0 + (-3.2 - 0)e^{-200t} = -3.2e^{-200t}\ \text{V}, \quad t \geq 0^+$

[l] $i_o = i_a - i_L = 225 - 160e^{-200t}\ \text{mA}, \quad t \geq 0^+$


P 7.21 [a] $v_1(0^-) = v_1(0^+) = 40 \text{ V}$ $v_2(0^+) = 0$
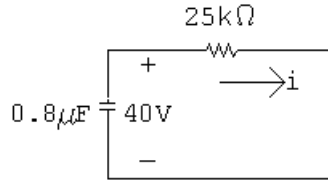
$$C_{\text{eq}} = (1)(4)/5 = 0.8 \mu\text{F}$$



$$\tau = (25 \times 10^3)(0.8 \times 10^{-6}) = 20\text{ms}; \quad \frac{1}{\tau} = 50$$
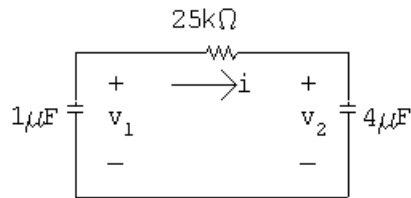
$$i = \frac{40}{25,000} e^{-50t} = 1.6e^{-50t} \text{ mA}, \quad t \geq 0^+$$



$$v_1 = \frac{-1}{10^{-6}} \int_0^t 1.6 \times 10^{-3} e^{-50x} dx + 40 = 32e^{-50t} + 8 \text{ V}, \quad t \geq 0$$

$$v_2 = \frac{1}{4 \times 10^{-6}} \int_0^t 1.6 \times 10^{-3} e^{-50x} dx + 0 = -8e^{-50t} + 8 \text{ V}, \quad t \geq 0$$

[b] $w(0) = \frac{1}{2}(10^{-6})(40)^2 = 800 \mu\text{J}$

[c] $w_{\text{trapped}} = \frac{1}{2}(10^{-6})(8)^2 + \frac{1}{2}(4 \times 10^{-6})(8)^2 = 160 \mu\text{J}.$

The energy dissipated by the 25 kΩ resistor is equal to the energy dissipated by the two capacitors; it is easier to calculate the energy dissipated by the capacitors (final voltage on the equivalent capacitor is zero):

$$w_{\text{diss}} = \frac{1}{2}(0.8 \times 10^{-6})(40)^2 = 640 \mu\text{J}.$$

Check: $w_{\text{trapped}} + w_{\text{diss}} = 160 + 640 = 800 \mu\text{J}; \quad w(0) = 800 \mu\text{J}.$

P 7.22 [a] Calculate the initial voltage drop across the capacitor:

$$v(0) = (2.7 \text{ k} \parallel 3.3 \text{ k})(40 \text{ mA}) = (1485)(40 \times 10^{-3}) = 59.4 \text{ V}$$

The equivalent resistance seen by the capacitor is

$$R_e = 3 \text{ k} \parallel (2.4 \text{ k} + 3.6 \text{ k}) = 3 \text{ k} \parallel 6 \text{ k} = 2 \text{ k}\Omega$$

$$\tau = R_e C = (2000)(0.5) \times 10^{-6} = 1000 \mu\text{s}; \quad \frac{1}{\tau} = 1000$$

$$v = v(0)e^{-t/\tau} = 59.4e^{-1000t} \text{ V} \quad t \geq 0$$

$$i_o = \frac{v}{2.4 \text{ k} + 3.6 \text{ k}} = 9.9e^{-1000t} \text{ mA}, \quad t \geq 0^+$$

$$\mathbf{[b]} \quad w(0) = \frac{1}{2}(0.5 \times 10^{-6})(59.4)^2 = 882.09 \mu\text{J}$$


$$i_{3k} = \frac{59.4e^{-1000t}}{3000} = 19.8e^{-1000t} \text{ mA}$$

$$p_{3k} = [(19.8 \times 10^{-3})e^{-1000t}]^2(3000) = 1.176e^{-2000t}$$

$$w_{3k}(500 \mu\text{s}) = 1.176 \frac{e^{-2000x}}{-2000} \Big|_0^{500 \times 10^{-6}} = \frac{1.176}{-2000}(e^{-1} - 1) = 371.72 \mu\text{J}$$


$$\% = \frac{371.72}{882.09} \times 100 = 42.14\%$$

P 7.33 **[a]** $t < 0$

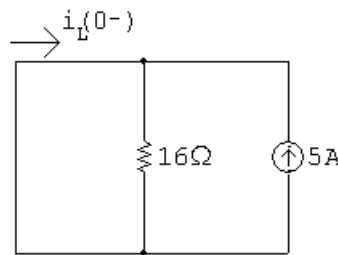

$$i_L(0^-) = -5 \text{ A}$$

$t > 0$

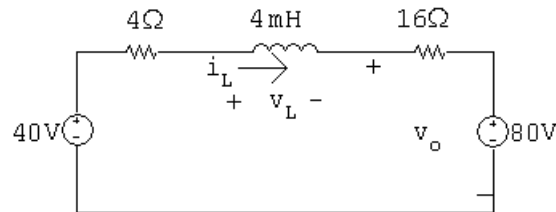

$$i_L(\infty) = \frac{40 - 80}{4 + 16} = -2 \text{ A}$$

$$\tau = \frac{L}{R} = \frac{4 \times 10^{-3}}{4 + 16} = 200 \mu\text{s}; \quad \frac{1}{\tau} = 5000$$

$$i_L = i_L(\infty) + [i_L(0^+) - i_L(\infty)]e^{-t/\tau}$$

$$= -2 + (-5 + 2)e^{-5000t} = -2 - 3e^{-5000t} \text{ A}, \quad t \geq 0$$


$$v_o = 16i_L + 80 = 16(-2 - 3e^{-5000t}) + 80 = 48 - 48e^{-5000t} \text{ V}, \quad t \geq 0^+$$

$$\mathbf{[b]} \quad v_L = L \frac{di_L}{dt} = 4 \times 10^{-3}(-5000)[-3e^{-5000t}] = 60e^{-5000t} \text{ V}, \quad t \geq 0^+$$

$$v_L(0^+) = 60 \text{ V}$$


$$\text{From part (a)} \quad v_o(0^+) = 0 \text{ V}$$

Check: at $t = 0^+$ the circuit is:

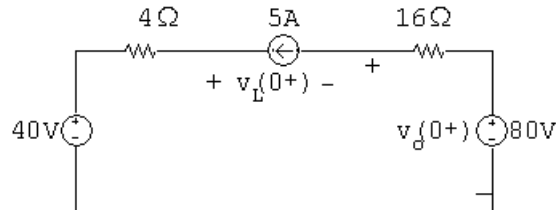

$$v_L(0^+) = 40 + (5 \text{ A})(4 \Omega) = 60 \text{ V}, \quad v_o(0^+) = 80 - (16 \Omega)(5 \text{ A}) = 0 \text{ V}$$

P 7.34 [a] $t < 0$

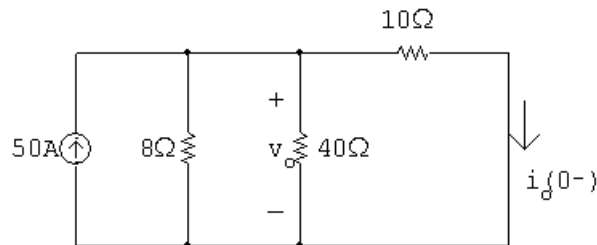

KVL equation at the top node:


$$50 = \frac{v_o}{8} + \frac{v_o}{40} + \frac{v_o}{10}$$

Multiply by 40 and solve:

$$2000 = (5 + 1 + 4)v_o; \quad v_o = 200 \text{ V}$$

$$\therefore i_o(0^-) = \frac{v_o}{10} = 200/10 = 20 \text{ A}$$

$t > 0$

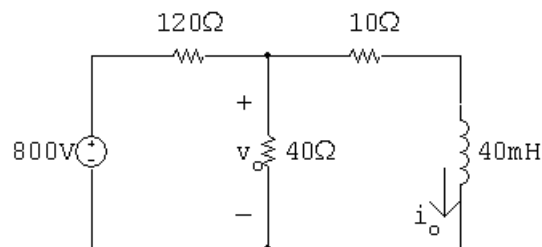


Use voltage division to find the Thévenin voltage:

$$V_{\text{Th}} = v_o = \frac{40}{40 + 120}(800) = 200 \text{ V}$$

Remove the voltage source and make series and parallel combinations of resistors to find the equivalent resistance:

$$R_{\text{Th}} = 10 + 120 \parallel 40 = 10 + 30 = 40 \Omega$$

The simplified circuit is:

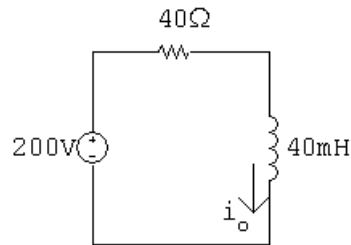


$$\tau = \frac{L}{R} = \frac{40 \times 10^{-3}}{40} = 1 \text{ ms}; \quad \frac{1}{\tau} = 1000$$

$$i_o(\infty) = \frac{200}{40} = 5 \text{ A}$$

$$\begin{aligned} \therefore i_o &= i_o(\infty) + [i_o(0^+) - i_o(\infty)]e^{-t/\tau} \\ &= 5 + (20 - 5)e^{-1000t} = 5 + 15e^{-1000t} \text{ A}, \quad t \geq 0 \end{aligned}$$

$$\begin{aligned} \text{[b]} \quad v_o &= 10i_o + L \frac{di_o}{dt} \\ &= 10(5 + 15e^{-1000t}) + 0.04(-1000)(15e^{-1000t}) \\ &= 50 + 150e^{-1000t} - 600e^{-1000t} \\ v_o &= 50 - 450e^{-1000t} \text{ V}, \quad t \geq 0^+ \end{aligned}$$

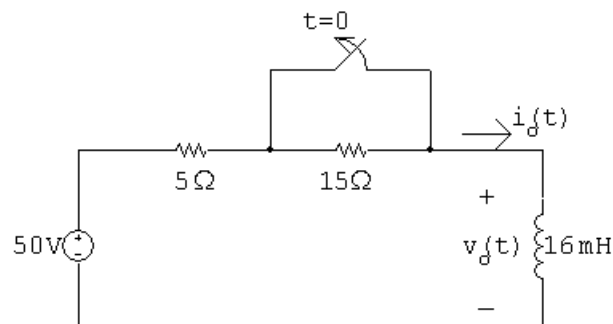P 7.35 After making a Thévenin equivalent we have



For $t < 0$, the 15Ω resistor is bypassed:

$$i_o(0^-) = i_o(0^+) = 50/5 = 10 \text{ A}$$


$$\tau = \frac{L}{R} = \frac{16 \times 10^{-3}}{5 + 15} = 8 \times 10^{-4}; \quad \frac{1}{\tau} = 1250$$

$$i(\infty) = \frac{V}{R_{\text{eq}}} = \frac{50}{5 + 15} = 2.5 \text{ A}$$

$$i_o = i_o(\infty) + [i_o(0^+) - i_o(\infty)]e^{-t/\tau} = 2.5 + (10 - 2.5)e^{-1250t} = 2.5 + 7.5e^{-1250t} \text{ A}, t \geq 0$$

$$v_o = L \frac{di_o}{dt} = 16 \times 10^{-3}(-1250)(7.5e^{-1250t}) = -150e^{-1250t} \text{ V}, t \geq 0^+$$

P 7.47 For $t < 0$

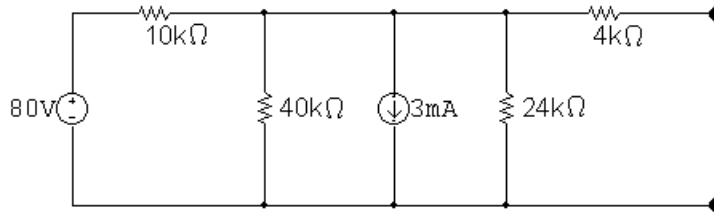


Simplify the circuit:

$$80/10,000 = 8 \text{ mA}, \quad 10 \text{ k}\Omega \parallel 40 \text{ k}\Omega \parallel 24 \text{ k}\Omega = 6 \text{ k}\Omega$$

$$8 \text{ mA} - 3 \text{ mA} = 5 \text{ mA}$$


$$5 \text{ mA} \times 6 \text{ k}\Omega = 30 \text{ V}$$

Thus, for $t < 0$

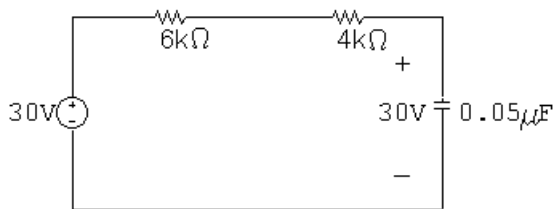

$$\therefore v_o(0^-) = v_o(0^+) = 30 \text{ V}$$

$t > 0$

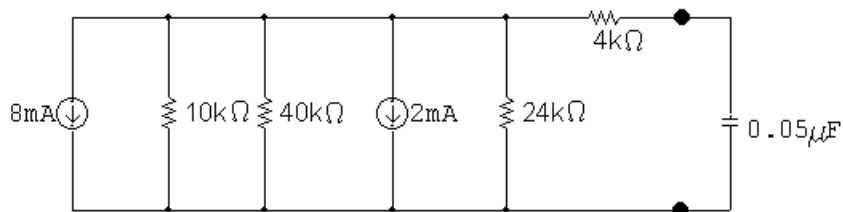


Simplify the circuit:

$$8 \text{ mA} + 2 \text{ mA} = 10 \text{ mA}$$

$$10 \text{ k}\Omega \parallel 40 \text{ k}\Omega \parallel 24 \text{ k}\Omega = 6 \text{ k}\Omega$$

$$(10 \text{ mA})(6 \text{ k}\Omega) = 60 \text{ V}$$

Thus, for $t > 0$

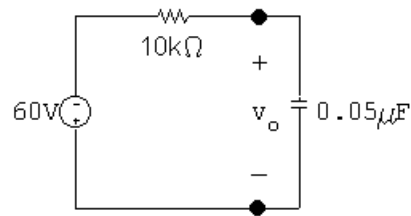


$$v_o(\infty) = -60 \text{ V}$$

$$\tau = RC = (10 \text{ k})(0.05 \mu) = 0.5 \text{ ms}; \quad \frac{1}{\tau} = 2000$$

$$\begin{aligned} v_o &= v_o(\infty) + [v_o(0^+) - v_o(\infty)]e^{-t/\tau} = -60 + [30 - (-60)]e^{-2000t} \\ &= -60 + 90e^{-2000t} \text{ V} \quad t \geq 0 \end{aligned}$$

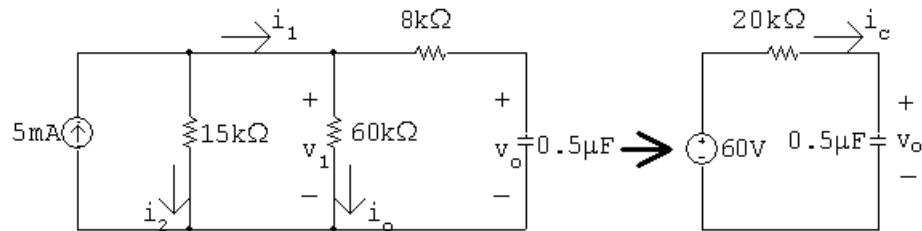P 7.48 [a] Simplify the circuit for $t > 0$ using source transformation:



Since there is no source connected to the capacitor for $t < 0$

$$v_o(0^-) = v_o(0^+) = 0 \text{ V}$$

From the simplified circuit,

$$v_o(\infty) = 60 \text{ V}$$

$$\tau = RC = (20 \times 10^3)(0.5 \times 10^{-6}) = 10 \text{ ms} \quad 1/\tau = 100$$

$$v_o = v_o(\infty) + [v_o(0^+) - v_o(\infty)]e^{-t/\tau} = (60 - 60e^{-100t}) \text{ V}, \quad t \geq 0$$

$$\text{[b]} \quad i_c = C \frac{dv_o}{dt}$$

$$i_c = 0.5 \times 10^{-6}(-100)(-60e^{-100t}) = 3e^{-100t} \text{ mA}$$

$$v_1 = 8000i_c + v_o = (8000)(3 \times 10^{-3})e^{-100t} + (60 - 60e^{-100t}) = 60 - 36e^{-100t} \text{ V}$$

$$i_o = \frac{v_1}{60 \times 10^3} = 1 - 0.6e^{-100t} \text{ mA}, \quad t \geq 0^+$$

$$\text{[c]} \quad i_1(t) = i_o + i_c = 1 + 2.4e^{-100t} \text{ mA} \quad t \geq 0^+$$

$$\text{[d]} \quad i_2(t) = \frac{v_1}{15 \times 10^3} = 4 - 2.4e^{-100t} \text{ mA} \quad t \geq 0^+$$

$$\text{[e]} \quad i_1(0^+) = 1 + 2.4 = 3.4 \text{ mA}$$

At $t = 0^+$:

$$R_e = 15 \text{ k} \parallel 60 \text{ k} \parallel 8 \text{ k} = 4800 \Omega$$

$$v_1(0^+) = (5 \times 10^{-3})(4800) = 24 \text{ V}$$

$$i_1(0^+) = \frac{v_1(0^+)}{60,000} + \frac{v_1(0^+)}{8000} = 0.4 \text{ m} + 3 \text{ m} = 3.4 \text{ mA} \quad (\text{checks})$$

P 7.69 Use voltage division to find the initial voltage:

$$v_o(0) = \frac{60}{40 + 60}(50) = 30 \text{ V}$$

Use Ohm's law to find the final value of voltage:


$$v_o(\infty) = (-5 \text{ mA})(20 \text{ k}\Omega) = -100 \text{ V}$$

$$\tau = RC = (20 \times 10^3)(250 \times 10^{-9}) = 5 \text{ ms}; \quad \frac{1}{\tau} = 200$$

$$v_o = v_o(\infty) + [v_o(0^+) - v_o(\infty)]e^{-t/\tau}$$

$$= -100 + (30 + 100)e^{-200t} = -100 + 130e^{-200t} \text{ V}, \quad t \geq 0$$

P 7.70 [a] $t < 0$:

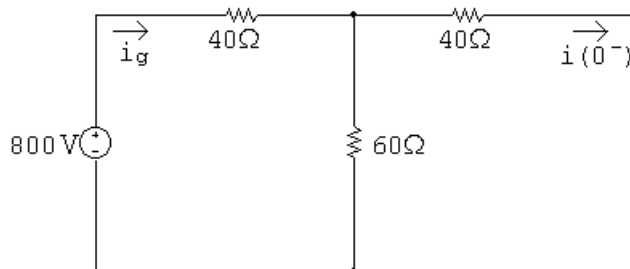

Using Ohm's law,

$$i_g = \frac{800}{40 + 60 \parallel 40} = 12.5 \text{ A}$$

Using current division,

$$i(0^-) = \frac{60}{60 + 40}(12.5) = 7.5 \text{ A} = i(0^+)$$

[b] $0 \leq t \leq 1 \text{ ms}$:

$$i = i(0^+)e^{-t/\tau} = 7.5e^{-t/\tau}$$


$$\frac{1}{\tau} = \frac{R}{L} = \frac{40 + 120 \parallel 60}{80 \times 10^{-3}} = 1000$$

$$i = 7.5e^{-1000t}$$

$$i(200\mu\text{s}) = 7.5e^{-10^3(200 \times 10^{-6})} = 7.5e^{-0.2} = 6.14 \text{ A}$$

[c] $i(1\text{ms}) = 7.5e^{-1} = 2.7591 \text{ A}$

$$1 \text{ ms} \leq t < \infty$$

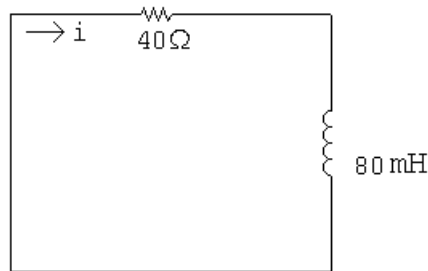

$$\frac{1}{\tau} = \frac{R}{L} = \frac{40}{80 \times 10^{-3}} = 500$$

$$i = i(1 \text{ ms})e^{-(t-1 \text{ ms})/\tau} = 2.7591e^{-500(t-0.001)} \text{ A}$$

$$i(6\text{ms}) = 2.7591e^{-500(0.005)} = 2.7591e^{-2.5} = 226.48 \text{ mA}$$

[d] $0 \leq t \leq 1 \text{ ms}$:

$$i = 7.5e^{-1000t}$$

$$v = L \frac{di}{dt} = (80 \times 10^{-3})(-1000)(7.5e^{-1000t}) = -600e^{-1000t} \text{ V}$$

$$v(1^- \text{ms}) = -600e^{-1} = -220.73 \text{ V}$$

[e] $1 \text{ ms} \leq t \leq \infty$:

$$i = 2.7591e^{-500(t-0.001)}$$

$$v = L \frac{di}{dt} = (80 \times 10^{-3})(-500)(2.591e^{-500(t-0.001)})$$

$$= -110.4e^{-500(t-0.001)} \text{ V}$$

$$v(1^+ \text{ms}) = -110.4 \text{ V}$$

P 7.89 Use voltage division to find the voltage at the non-inverting terminal:

$$v_p = \frac{80}{100}(-45) = -36 \text{ V} = v_n$$

Write a KCL equation at the inverting terminal:

$$\frac{-36 - 14}{80,000} + 2.5 \times 10^{-6} \frac{d}{dt}(-36 - v_o) = 0$$

$$\therefore 2.5 \times 10^{-6} \frac{dv_o}{dt} = \frac{-50}{80,000}$$

Separate the variables and integrate:

$$\frac{dv_o}{dt} = -250 \quad \therefore \quad dv_o = -250 dt$$

$$\int_{v_o(0)}^{v_o(t)} dx = -250 \int_0^t dy \quad \therefore \quad v_o(t) - v_o(0) = -250t$$

$$v_o(0) = -36 + 56 = 20 \text{ V}$$

$$v_o(t) = -250t + 20$$

Find the time when the voltage reaches 0:

$$0 = -250t + 20 \quad \therefore \quad t = \frac{20}{250} = 80 \text{ ms}$$

P 7.90 The equation for an integrating amplifier:

$$v_o = \frac{1}{RC} \int_0^t (v_b - v_a) dy + v_o(0)$$

Find the values and substitute them into the equation:

$$RC = (100 \times 10^3)(0.05 \times 10^{-6}) = 5 \text{ ms}$$

$$\frac{1}{RC} = 200; \quad v_b - v_a = -15 - (-7) = -8 \text{ V}$$

$$v_o(0) = -4 + 12 = 8 \text{ V}$$

$$v_o = 200 \int_0^t -8 dx + 8 = (-1600t + 8) \text{ V}, \quad 0 \leq t \leq t_{\text{sat}}$$

RC circuit analysis for v_2 :

$$v_2(0^+) = -4 \text{ V}; \quad v_2(\infty) = -15 \text{ V}; \quad \tau = RC = (100 \text{ k})(0.05 \mu) = 5 \text{ ms}$$

$$\begin{aligned} v_2 &= v_2(\infty) + [v_2(0^+) - v_2(\infty)]e^{-t/\tau} \\ &= -15 + (-4 + 15)e^{-200t} = -15 + 11e^{-200t} \text{ V}, \quad 0 \leq t \leq t_{\text{sat}} \end{aligned}$$

$$v_f + v_2 = v_o \quad \therefore \quad v_f = v_o - v_2 = 23 - 1600t - 11e^{-200t} \text{ V}, \quad 0 \leq t \leq t_{\text{sat}}$$

Note that

$$-1600t_{\text{sat}} + 8 = -20 \quad \therefore \quad t_{\text{sat}} = \frac{-28}{-1600} = 17.5 \text{ ms}$$

so the op amp operates in its linear region until it saturates at 17.5 ms.