

Natural and Step Responses of *RLC* Circuits

Assessment Problems

AP 8.1 [a] $\frac{1}{(2RC)^2} = \frac{1}{LC}$, therefore $C = 500 \text{ nF}$

[b] $\alpha = 5000 = \frac{1}{2RC}$, therefore $C = 1 \mu\text{F}$

$$s_{1,2} = -5000 \pm \sqrt{25 \times 10^6 - \frac{(10^3)(10^6)}{20}} = (-5000 \pm j5000) \text{ rad/s}$$

[c] $\frac{1}{\sqrt{LC}} = 20,000$, therefore $C = 125 \text{ nF}$

$$s_{1,2} = \left[-40 \pm \sqrt{(40)^2 - 20^2} \right] 10^3,$$

$$s_1 = -5.36 \text{ krad/s}, \quad s_2 = -74.64 \text{ krad/s}$$

AP 8.2 $i_L = \frac{1}{50 \times 10^{-3}} \int_0^t [-14e^{-5000x} + 26e^{-20,000x}] dx + 30 \times 10^{-3}$

$$= 20 \left\{ \frac{-14e^{-5000x}}{-5000} \Big|_0^t + \frac{26e^{-20,000x}}{-20,000} \Big|_0^t \right\} + 30 \times 10^{-3}$$

$$= 56 \times 10^{-3}(e^{-5000t} - 1) - 26 \times 10^{-3}(e^{-20,000t} - 1) + 30 \times 10^{-3}$$

$$= [56e^{-5000t} - 56 - 26e^{-20,000t} + 26 + 30] \text{ mA}$$

$$= 56e^{-5000t} - 26e^{-20,000t} \text{ mA}, \quad t \geq 0$$

AP 8.3 From the given values of R , L , and C , $s_1 = -10 \text{ krad/s}$ and $s_2 = -40 \text{ krad/s}$.

[a] $v(0^-) = v(0^+) = 0$, therefore $i_R(0^+) = 0$

$$[b] i_C(0^+) = -(i_L(0^+) + i_R(0^+)) = -(-4 + 0) = 4 \text{ A}$$

$$[c] C \frac{dv_C(0^+)}{dt} = i_C(0^+) = 4, \quad \text{therefore} \quad \frac{dv_C(0^+)}{dt} = \frac{4}{C} = 4 \times 10^8 \text{ V/s}$$

$$[d] v = [A_1 e^{-10,000t} + A_2 e^{-40,000t}] \text{ V}, \quad t \geq 0^+$$

$$v(0^+) = A_1 + A_2, \quad \frac{dv(0^+)}{dt} = -10,000A_1 - 40,000A_2$$

$$\text{Therefore} \quad A_1 + A_2 = 0, \quad -A_1 - 4A_2 = 40,000; \quad A_1 = 40,000/3 \text{ V}$$

$$[e] A_2 = -40,000/3 \text{ V}$$

$$[f] v = [40,000/3][e^{-10,000t} - e^{-40,000t}] \text{ V}, \quad t \geq 0$$

$$\text{AP 8.4 [a]} \quad \frac{1}{2RC} = 8000, \quad \text{therefore} \quad R = 62.5 \Omega$$

$$[b] i_R(0^+) = \frac{10 \text{ V}}{62.5 \Omega} = 160 \text{ mA}$$

$$i_C(0^+) = -(i_L(0^+) + i_R(0^+)) = -80 - 160 = -240 \text{ mA} = C \frac{dv(0^+)}{dt}$$

$$\text{Therefore} \quad \frac{dv(0^+)}{dt} = \frac{-240 \text{ m}}{C} = -240 \text{ kV/s}$$

$$[c] B_1 = v(0^+) = 10 \text{ V}, \quad \frac{dv_C(0^+)}{dt} = \omega_d B_2 - \alpha B_1$$

$$\text{Therefore} \quad 6000B_2 - 8000B_1 = -240,000, \quad B_2 = (-80/3) \text{ V}$$

$$[d] i_L = -(i_R + i_C); \quad i_R = v/R; \quad i_C = C \frac{dv}{dt}$$

$$v = e^{-8000t} [10 \cos 6000t - \frac{80}{3} \sin 6000t] \text{ V}$$

$$\text{Therefore} \quad i_R = e^{-8000t} [160 \cos 6000t - \frac{1280}{3} \sin 6000t] \text{ mA}$$

$$i_C = e^{-8000t} [-240 \cos 6000t + \frac{460}{3} \sin 6000t] \text{ mA}$$

$$i_L = 10e^{-8000t} [8 \cos 6000t + \frac{82}{3} \sin 6000t] \text{ mA}, \quad t \geq 0$$

$$\text{AP 8.5 [a]} \quad \left(\frac{1}{2RC}\right)^2 = \frac{1}{LC} = \frac{10^6}{4}, \quad \text{therefore} \quad \frac{1}{2RC} = 500, \quad R = 100 \Omega$$

$$[b] 0.5CV_0^2 = 12.5 \times 10^{-3}, \quad \text{therefore} \quad V_0 = 50 \text{ V}$$

$$[c] 0.5LI_0^2 = 12.5 \times 10^{-3}, \quad I_0 = 250 \text{ mA}$$

$$[d] D_2 = v(0^+) = 50, \quad \frac{dv(0^+)}{dt} = D_1 - \alpha D_2$$

$$i_R(0^+) = \frac{50}{100} = 500 \text{ mA}$$

$$\text{Therefore } i_C(0^+) = -(500 + 250) = -750 \text{ mA}$$

$$\text{Therefore } \frac{dv(0^+)}{dt} = -750 \times \frac{10^{-3}}{C} = -75,000 \text{ V/s}$$

$$\text{Therefore } D_1 - \alpha D_2 = -75,000; \quad \alpha = \frac{1}{2RC} = 500, \quad D_1 = -50,000 \text{ V/s}$$

$$[e] v = [50e^{-500t} - 50,000te^{-500t}] \text{ V}$$

$$i_R = \frac{v}{R} = [0.5e^{-500t} - 500te^{-500t}] \text{ A}, \quad t \geq 0^+$$

$$\text{AP 8.6 [a] } i_R(0^+) = \frac{V_0}{R} = \frac{40}{500} = 0.08 \text{ A}$$

$$[b] i_C(0^+) = I - i_R(0^+) - i_L(0^+) = -1 - 0.08 - 0.5 = -1.58 \text{ A}$$

$$[c] \frac{di_L(0^+)}{dt} = \frac{V_o}{L} = \frac{40}{0.64} = 62.5 \text{ A/s}$$

$$[d] \alpha = \frac{1}{2RC} = 1000; \quad \frac{1}{LC} = 1,562,500; \quad s_{1,2} = -1000 \pm j750 \text{ rad/s}$$

$$[e] i_L = i_f + B_1'e^{-\alpha t} \cos \omega_d t + B_2'e^{-\alpha t} \sin \omega_d t, \quad i_f = I = -1 \text{ A}$$

$$i_L(0^+) = 0.5 = i_f + B_1', \quad \text{therefore } B_1' = 1.5 \text{ A}$$

$$\frac{di_L(0^+)}{dt} = 62.5 = -\alpha B_1' + \omega_d B_2', \quad \text{therefore } B_2' = (25/12) \text{ A}$$

$$\text{Therefore } i_L(t) = -1 + e^{-1000t}[1.5 \cos 750t + (25/12) \sin 750t] \text{ A}, \quad t \geq 0$$

$$[f] v(t) = \frac{L di_L}{dt} = 40e^{-1000t}[\cos 750t - (154/3) \sin 750t] \text{ V} \quad t \geq 0$$

$$\text{AP 8.7 [a] } i(0^+) = 0, \text{ since there is no source connected to } L \text{ for } t < 0.$$

$$[b] v_C(0^+) = v_C(0^-) = \left(\frac{15 \text{ k}}{15 \text{ k} + 9 \text{ k}} \right) (80) = 50 \text{ V}$$

$$[c] 50 + 80i(0^+) + L \frac{di(0^+)}{dt} = 100, \quad \frac{di(0^+)}{dt} = 10,000 \text{ A/s}$$

$$[d] \alpha = 8000; \quad \frac{1}{LC} = 100 \times 10^6; \quad s_{1,2} = -8000 \pm j6000 \text{ rad/s}$$

$$[e] i = i_f + e^{-\alpha t}[B_1' \cos \omega_d t + B_2' \sin \omega_d t]; \quad i_f = 0, \quad i(0^+) = 0$$

$$\text{Therefore } B_1' = 0; \quad \frac{di(0^+)}{dt} = 10,000 = -\alpha B_1' + \omega_d B_2'$$

$$\text{Therefore } B_2' = 1.67 \text{ A}; \quad i = 1.67e^{-8000t} \sin 6000t \text{ A}, \quad t \geq 0$$

$$\text{AP 8.8 } v_c(t) = v_f + e^{-\alpha t}[B'_1 \cos \omega_d t + B'_2 \sin \omega_d t], \quad v_f = 100 \text{ V}$$

$$v_c(0^+) = 50 \text{ V}; \quad \frac{dv_c(0^+)}{dt} = 0; \quad \text{therefore } 50 = 100 + B'_1$$

$$B'_1 = -50 \text{ V}; \quad 0 = -\alpha B'_1 + \omega_d B'_2$$

$$\text{Therefore } B'_2 = \frac{\alpha}{\omega_d} B'_1 = \left(\frac{8000}{6000}\right)(-50) = -66.67 \text{ V}$$

$$\text{Therefore } v_c(t) = 100 - e^{-8000t}[50 \cos 6000t + 66.67 \sin 6000t] \text{ V}, \quad t \geq 0$$

Problems

$$\text{P 8.1 [a]} \quad \alpha = \frac{1}{2RC} = \frac{10^9}{(10,000)(8)} = 12,500$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^9}{(1.25)(8)} = 10^8$$

$$s_{1,2} = -12,500 \pm \sqrt{(1.5625 - 1)10^8} = -12,500 \pm 7500$$

$$s_1 = -5000 \text{ rad/s}$$

$$s_2 = -20,000 \text{ rad/s}$$

[b] overdamped

$$\text{[c]} \quad \omega_d = \sqrt{\omega_o^2 - \alpha^2}$$

$$\therefore \alpha^2 = \omega_o^2 - \omega_d^2 = 10^8 - 36 \times 10^6 = 0.64 \times 10^8$$

$$\alpha = 0.8 \times 10^4 = 8000$$

$$\frac{1}{2RC} = 8000; \quad \therefore R = \frac{10^9}{(16,000)(8)} = 7812.5 \Omega$$

$$\text{[d]} \quad s_1 = -8000 + j6000 \text{ rad/s}; \quad s_2 = -8000 - j6000 \text{ rad/s}$$

$$\text{[e]} \quad \alpha = 10^4 = \frac{1}{2RC}; \quad \therefore R = \frac{1}{2C(10^4)} = 6250 \Omega$$

P 8.2 [a] $-\alpha + \sqrt{\alpha^2 - \omega_o^2} = -5000$

$$-\alpha - \sqrt{\alpha^2 - \omega_o^2} = -20,000$$

$$\therefore -2\alpha = -25,000$$

$$\alpha = 12,500 \text{ rad/s}$$

$$\frac{1}{2RC} = \frac{10^6}{2R(0.05)} = 12,500$$

$$R = 800 \Omega$$

$$2\sqrt{\alpha^2 - \omega_o^2} = 15,000$$

$$4(\alpha^2 - \omega_o^2) = 225 \times 10^6$$

$$\therefore \omega_o = 10,000 \text{ rad/s}$$

$$\omega_o^2 = 10^8 = \frac{1}{LC}$$

$$\therefore L = \frac{1}{10^8 C} = 200 \text{ mH}$$

[b] $i_R = \frac{v(t)}{R} = -6.25e^{-5000t} + 25e^{-20,000t} \text{ mA}, \quad t \geq 0^+$

$$i_C = C \frac{dv(t)}{dt} = 1.25e^{-5000t} - 20e^{-20,000t} \text{ mA}, \quad t \geq 0^+$$

$$i_L = -(i_R + i_C) = 5e^{-5000t} - 5e^{-20,000t} \text{ mA}, \quad t \geq 0^+$$

P 8.3 [a] $\alpha = 4000; \quad \omega_d = 3000$

$$\omega_d = \sqrt{\omega_o^2 - \alpha^2}$$

$$\therefore \omega_o^2 = \omega_d^2 + \alpha^2 = 9 \times 10^6 + 16 \times 10^6 = 25 \times 10^6$$

$$\frac{1}{LC} = 25 \times 10^6$$

$$L = \frac{1}{(25 \times 10^6)(50 \times 10^{-9})} = 0.8 \text{ H} = 800 \text{ mH}$$

[b] $\alpha = \frac{1}{2RC}$

$$\therefore R = \frac{1}{2\alpha C} = \frac{10^9}{(8000)(50)} = 2500 \Omega$$

[c] $V_o = v(0) = 125 \text{ V}$

$$[\mathbf{d}] I_o = i_L(0) = -i_R(0) - i_C(0)$$

$$i_R(0) = \frac{V_o}{R} = \frac{125}{2.5} \times 10^{-3} = 50 \text{ mA}$$

$$i_C(0) = C \frac{dv}{dt}(0)$$

$$\begin{aligned} \frac{dv}{dt} &= 125 \{ e^{-4000t} [-3000 \sin 3000t - 6000 \cos 3000t] - \\ &\quad 4000e^{-4000t} [\cos 3000t - 2 \sin 3000t] \} \end{aligned}$$

$$\frac{dv}{dt}(0) = 125 \{ 1(-6000) - 4000 \} = -125 \times 10^4$$

$$C \frac{dv}{dt}(0) = -125 \times 10^4 (50 \times 10^{-9}) = -6250 \times 10^{-5} = -62.5 \text{ mA}$$

$$\therefore I_o = -50 + 62.5 = 12.5 \text{ mA}$$

$$[\mathbf{e}] \frac{dv}{dt} = 125e^{-4000t} [5000 \sin 3000t - 10,000 \cos 3000t]$$

$$= 625 \times 10^3 e^{-4000t} [\sin 3000t - 2 \cos 3000t]$$

$$C \frac{dv}{dt} = 31,250 \times 10^{-6} e^{-4000t} (\sin 3000t - 2 \cos 3000t)$$

$$i_C(t) = 31.25e^{-4000t} (\sin 3000t - 2 \cos 3000t) \text{ mA}$$

$$i_R(t) = 50e^{-4000t} (\cos 3000t - 2 \sin 3000t) \text{ mA}$$

$$i_L(t) = -i_R(t) - i_C(t)$$

$$= e^{-4000t} (12.5 \cos 3000t + 68.75 \sin 3000t) \text{ mA}, \quad t \geq 0$$

CHECK:

$$\begin{aligned} \frac{di_L}{dt} &= \{ -4000e^{-4000t} [12.5 \cos 3000t + 68.75 \sin 3000t] \\ &\quad + e^{-4000t} [-37.5 \times 10^3 \sin 3000t \\ &\quad + 206.25 \times 10^3 \cos 3000t] \} \times 10^{-3} \end{aligned}$$

$$= e^{-4000t} [156.25 \cos 3000t - 312.5 \sin 3000t]$$

$$L \frac{di_L}{dt} = e^{-4000t} [125 \cos 3000t - 250 \sin 3000t]$$

$$= 125e^{-4000t} [\cos 3000t - 2 \sin 3000t] \text{ V}$$

$$\text{P 8.4 [a]} \quad \left(\frac{1}{2RC}\right)^2 = \frac{1}{LC} = (4000)^2$$

$$\therefore C = \frac{1}{(16 \times 10^6)(5)} = 12.5 \text{ nF}$$

$$\frac{1}{2RC} = 4000$$

$$\therefore R = \frac{10^9}{(8000)(12.5)} = 10 \text{ k}\Omega$$

$$v(0) = D_2 = 25 \text{ V}$$

$$i_R(0) = \frac{25}{10} = 2.5 \text{ mA}$$

$$i_C(0) = -2.5 - 5 = -7.5 \text{ mA}$$

$$\frac{dv}{dt}(0) = D_1 - 4000D_2 = \frac{-7.5 \times 10^{-3}}{12.5 \times 10^{-9}} = -6 \times 10^5$$

$$\therefore D_1 = -6 \times 10^5 + 4000(25) = -5 \times 10^5 \text{ V/s}$$

$$\text{[b]} \quad v = -5 \times 10^5 t e^{-4000t} + 25 e^{-4000t}$$

$$\frac{dv}{dt} = [20 \times 10^8 t - 6 \times 10^5] e^{-4000t}$$

$$i_C = C \frac{dv}{dt} = 12.5 \times 10^{-9} [20 \times 10^8 t - 6 \times 10^5] e^{-4000t}$$

$$= (25,000t - 7.5) e^{-4000t} \text{ mA}, \quad t > 0$$

$$\text{P 8.5 [a]} \quad 2\alpha = 200; \quad \alpha = 100 \text{ rad/s}$$

$$2\sqrt{\alpha^2 - \omega_o^2} = 120; \quad \omega_o = 80 \text{ rad/s}$$

$$C = \frac{1}{2\alpha R} = \frac{1}{200(200)} = 25 \mu\text{F}$$

$$L = \frac{1}{\omega_o^2 C} = \frac{10^6}{(80)^2(25)} = 6.25 \text{ H}$$

$$i_C(0^+) = A_1 + A_2 = 15 \text{ mA}$$

$$\frac{di_C}{dt} + \frac{di_L}{dt} + \frac{di_R}{dt} = 0$$

$$\frac{di_C(0)}{dt} = -\frac{di_L(0)}{dt} - \frac{di_R(0)}{dt}$$

$$\frac{di_L(0)}{dt} = \frac{0}{6.25} = 0 \text{ A/s}$$

$$\frac{di_R(0)}{dt} = \frac{1}{R} \frac{dv(0)}{dt} = \frac{1}{R} \frac{i_C(0)}{C} = \frac{15 \times 10^{-3}}{(200)(25 \times 10^{-6})} = 3 \text{ A/s}$$

$$\therefore \frac{di_C(0)}{dt} = -3 \text{ A/s}$$

$$\therefore 160A_1 + 40A_2 = 3$$

$$4A_1 + A_2 = 75 \times 10^{-3}; \quad \therefore A_1 = 20 \text{ mA}; \quad A_2 = -5 \text{ mA}$$

$$\therefore i_C = 20e^{-160t} - 5e^{-40t} \text{ mA}, \quad t \geq 0$$

[b] By hypothesis

$$v = A_3e^{-160t} + A_4e^{-40t}, \quad t \geq 0$$

$$v(0) = A_3 + A_4 = 0$$

$$\frac{dv(0)}{dt} = \frac{15 \times 10^{-3}}{25 \times 10^{-6}} = 600 \text{ V/s}$$

$$-160A_3 - 40A_4 = 600; \quad \therefore A_3 = -5 \text{ V}; \quad A_4 = 5 \text{ V}$$

$$v = -5e^{-160t} + 5e^{-40t} \text{ V}, \quad t \geq 0$$

$$[c] i_R(t) = \frac{v}{200} = -25e^{-160t} + 25e^{-40t} \text{ mA}, \quad t \geq 0^+$$

$$[d] i_L = -i_R - i_C$$

$$i_L = 5e^{-160t} - 20e^{-40t} \text{ mA}, \quad t \geq 0$$

P 8.6 [a] $i_R(0) = \frac{90}{2000} = 45 \text{ mA}$

$$i_L(0) = -30 \text{ mA}$$

$$i_C(0) = -i_L(0) - i_R(0) = 30 - 45 = -15 \text{ mA}$$

$$[b] \alpha = \frac{1}{2RC} = \frac{10^9}{(4000)(10)} = 25,000$$

$$\omega_o^2 = \frac{1}{LC} = \frac{(10^3)(10^9)}{(250)(10)} = 4 \times 10^8$$

$$s_{1,2} = -25,000 \pm \sqrt{6.25 \times 10^8 - 10^8(4)} = -25,000 \pm 15,000$$

$$s_1 = -10,000 \text{ rad/s}; \quad s_2 = -40,000 \text{ rad/s}$$

$$v = A_1e^{-10,000t} + A_2e^{-40,000t}$$

$$v(0) = A_1 + A_2 = 90$$

$$\frac{dv}{dt}(0) = -10^4 A_1 - 4A_2 \times 10^4 = \frac{-15 \times 10^{-3}}{10 \times 10^{-9}} = -1.5 \times 10^6 \text{ V/s}$$

$$-A_1 - 4A_2 = -150$$

$$\therefore -3A_2 = -60; \quad A_2 = 20; \quad A_1 = 70$$

$$v = 70e^{-10,000t} + 20e^{-40,000t} \text{ V}, \quad t \geq 0$$

$$\begin{aligned} \text{[c]} \quad i_C &= C \frac{dv}{dt} \\ &= 10 \times 10^{-9} [-70 \times 10^4 e^{-10,000t} - 80 \times 10^4 e^{-40,000t}] \\ &= -7e^{-10,000t} - 8e^{-40,000t} \text{ mA} \\ i_R &= 35e^{-10,000t} + 10e^{-40,000t} \text{ mA} \\ i_L &= -i_C - i_R = -28e^{-10,000t} - 2e^{-40,000t} \text{ mA}, \quad t \geq 0 \end{aligned}$$

$$\text{P 8.7} \quad \alpha = \frac{1}{2RC} = \frac{10^9}{(5000)(10)} = 2 \times 10^4$$

$$\alpha^2 = 4 \times 10^8; \quad \therefore \alpha^2 = \omega_o^2$$

Critical damping:

$$v = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

$$i_R(0^+) = \frac{90}{2500} = 36 \text{ mA}$$

$$i_C(0^+) = -[i_L(0^+) + i_R(0^+)] = -[-30 + 36] = -6 \text{ mA}$$

$$v(0) = D_2 = 90$$

$$\frac{dv}{dt} = D_1 [t(-\alpha e^{-\alpha t}) + e^{-\alpha t}] - \alpha D_2 e^{-\alpha t}$$

$$\frac{dv}{dt}(0) = D_1 - \alpha D_2 = \frac{i_C(0)}{C} = \frac{-6 \times 10^{-3}}{10 \times 10^{-9}} = -6 \times 10^5$$

$$D_1 = \alpha D_2 - 6 \times 10^5 = (2 \times 10^4)(90) - 6 \times 10^5 = 120 \times 10^4$$

$$v = (120 \times 10^4 t + 90)e^{-20,000t} \text{ V}, \quad t \geq 0$$

$$\text{P 8.8} \quad \frac{1}{2RC} = \frac{3 \times 10^9}{(25,000)(10)} = 12,000$$

$$\frac{1}{LC} = 4 \times 10^8$$

$$s_{1,2} = -12,000 \pm j16,000 \text{ rad/s}$$

\therefore response is underdamped

$$v(t) = B_1 e^{-12,000t} \cos 16,000t + B_2 e^{-12,000t} \sin 16,000t$$

$$v(0^+) = 90 \text{ V} = B_1; \quad i_R(0^+) = \frac{90}{(12,500/3)} = 21.6 \text{ mA}$$

$$i_C(0^+) = [-i_L(0^+) + i_R(0^+)] = -[-30 + 21.6] = 8.4 \text{ mA}$$

$$\frac{dv(0^+)}{dt} = \frac{8.4 \times 10^{-3}}{10 \times 10^{-9}} = 840,000 \text{ V/s}$$

$$\frac{dv(0)}{dt} = -12,000B_1 + 16,000B_2 = 840,000$$

$$\text{or } -3B_1 + 4B_2 = 210; \quad \therefore B_2 = 120 \text{ V}$$

$$v(t) = 90e^{-12,000t} \cos 16,000t + 120e^{-12,000t} \sin 16,000t \text{ V}, \quad t \geq 0$$

$$\text{P 8.9} \quad \alpha = 2000/2 = 1000$$

$$R = \frac{1}{2\alpha C} = \frac{10^6}{(2000)(18)} = 27.78 \Omega$$

$$v(0^+) = -24 \text{ V}$$

$$i_R(0^+) = \frac{-24}{27.78} = -864 \text{ mA}$$

$$\frac{dv}{dt} = 2400e^{-200t} + 21,600e^{-1800t}$$

$$\frac{dv(0^+)}{dt} = 2400 + 21,600 = 24,000 \text{ V/s}$$

$$i_C(0^+) = 18 \times 10^{-6}(24,000) = 432 \text{ mA}$$

$$i_L(0^+) = -[i_R(0^+) + i_C(0^+)] = -[-864 + 432] = 432 \text{ mA}$$

$$\text{P 8.10 [a]} \quad \omega_o^2 = \frac{1}{LC} = \frac{10^9}{40} = 25 \times 10^6$$

$$\omega_o = 5000 \text{ rad/s}$$

$$\frac{1}{2RC} = 5000; \quad R = \frac{1}{10,000C}$$

$$R = \frac{10^9}{8 \times 10^4} = 12.5 \text{ k}\Omega$$

$$\text{[b]} \quad v(t) = D_1 t e^{-5000t} + D_2 e^{-5000t}$$

$$v(0) = -25 \text{ V} = D_2$$

$$\frac{dv}{dt} = (D_1 t - 25)(-5000 e^{-5000t}) + D_1 e^{-5000t}$$

$$\frac{dv}{dt}(0) = 125 \times 10^3 + D_1 = \frac{i_C(0)}{C}$$

$$i_C(0) = -i_R(0) - i_L(0)$$

$$i_R(0) = \frac{-25}{12.5} = -2 \text{ mA}$$

$$\therefore i_C(0) = 2 - (-1) = 3 \text{ mA}$$

$$\therefore \frac{dv}{dt}(0) = \frac{3 \times 10^{-3}}{8 \times 10^{-9}} = 0.375 \times 10^6 = 3.75 \times 10^5$$

$$\therefore 1.25 \times 10^5 + D_1 = 3.75 \times 10^5$$

$$D_1 = 2.5 \times 10^5 = 25 \times 10^4 \text{ V/s}$$

$$\therefore v(t) = (25 \times 10^4 t - 25) e^{-5000t} \text{ V}, \quad t \geq 0$$

$$\text{[c]} \quad i_C(t) = 0 \text{ when } \frac{dv}{dt}(t) = 0$$

$$\frac{dv}{dt} = (25 \times 10^4 t - 25)(-5000) e^{-5000t} + e^{-5000t}(25 \times 10^4)$$

$$= (375,000 - 125 \times 10^7 t) e^{-5000t}$$

$$\frac{dv}{dt} = 0 \text{ when } 125 \times 10^7 t_1 = 375,000; \quad \therefore t_1 = 300 \mu\text{s}$$

$$v(300 \mu\text{s}) = 50 e^{-1.5} = 11.16 \text{ V}$$

$$[d] \quad i_L(300\mu\text{s}) = -i_R(300\mu\text{s}) = \frac{11.16}{12.5} = 0.89 \text{ mA}$$

$$\omega_C(300\mu\text{s}) = 4 \times 10^{-9}(11.16)^2 = 497.87 \text{ nJ}$$

$$\omega_L(300\mu\text{s}) = (2.5)(0.89)^2 \times 10^{-6} = 1991.48 \text{ nJ}$$

$$\omega(300\mu\text{s}) = \omega_C + \omega_L = 2489.35 \text{ nJ}$$

$$\omega(0) = 4 \times 10^{-9}(625) + 2.5(10^{-6}) = 5000 \text{ nJ}$$

$$\% \text{ remaining} = \frac{2489.35}{5000}(100) = 49.79\%$$

$$P 8.11 \quad [a] \quad \alpha = \frac{1}{2RC} = 1 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = 10$$

$$\omega_d = \sqrt{10 - 1} = 3 \text{ rad/s}$$

$$\therefore v = B_1 e^{-t} \cos 3t + B_2 e^{-t} \sin 3t$$

$$v(0) = B_1 = 0; \quad v = B_2 e^{-t} \sin 3t$$

$$i_R(0^+) = 0 \text{ A}; \quad i_C(0^+) = 3 \text{ A}; \quad \frac{dv}{dt}(0^+) = \frac{3}{0.25} = 12 \text{ V/s}$$

$$12 = -\alpha B_1 + \omega_d B_2 = -1(0) + 3B_2$$

$$\therefore B_2 = 4$$

$$\therefore v = 4e^{-t} \sin 3t \text{ V}, \quad t \geq 0$$

$$[b] \quad \frac{dv}{dt} = 4e^{-t}(3 \cos 3t - \sin 3t)$$

$$\frac{dv}{dt} = 0 \quad \text{when} \quad 3 \cos 3t = \sin 3t \quad \text{or} \quad \tan 3t = 3$$

$$\therefore 3t_1 = 1.25, \quad t_1 = 416.35 \text{ ms}$$

$$3t_2 = 1.25 + \pi, \quad t_2 = 1463.55 \text{ ms}$$

$$3t_3 = 1.25 + 2\pi, \quad t_3 = 2510.74 \text{ ms}$$

$$[c] \quad t_3 - t_1 = 2094.40 \text{ ms}; \quad T_d = \frac{2\pi}{\omega_d} = \frac{2\pi}{3} = 2094.40 \text{ ms}$$


$$[d] \quad t_2 - t_1 = 1047.20 \text{ ms}; \quad \frac{T_d}{2} = \frac{2094.40}{2} = 1047.20 \text{ ms}$$

$$[e] \quad v(t_1) = 4e^{-(0.41635)} \sin 3(0.41635) = 2.50 \text{ V}$$

$$v(t_2) = 4e^{-(1.46355)} \sin 3(1.46355) = -0.88 \text{ V}$$

$$v(t_3) = 4e^{-(2.51074)} \sin 3(2.51074) = 0.31 \text{ V}$$

[f]

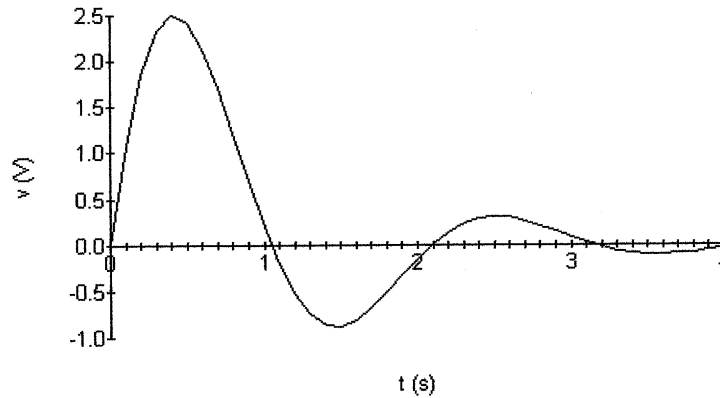

P 8.12 [a] $\alpha = 0$; $\omega_d = \omega_o = \sqrt{10} = 3.16 \text{ rad/s}$

$$v = B_1 \cos \omega_o t + B_2 \sin \omega_o t; \quad v(0) = B_1 = 0; \quad v = B_2 \sin \omega_o t$$

$$C \frac{dv}{dt}(0) = -i_L(0) = 3$$

$$12 = -\alpha B_1 + \omega_d B_2 = -0 + \sqrt{10} B_2$$

$$\therefore B_2 = 12/\sqrt{10} = 3.79 \text{ V}$$

$$v = 3.79 \sin 3.16t \text{ V}, \quad t \geq 0$$

[b] $2\pi f = 3.16$; $f = \frac{3.16}{2\pi} \cong 0.50 \text{ Hz}$

[c] 3.79 V

P 8.13 From the form of the solution we have

$$v(0) = A_1 + A_2$$

$$\frac{dv(0^+)}{dt} = -\alpha(A_1 + A_2) + j\omega_d(A_1 - A_2)$$

We know both $v(0)$ and $dv(0^+)/dt$ will be real numbers. To facilitate the algebra we let these numbers be K_1 and K_2 , respectively. Then our two simultaneous equations are

$$K_1 = A_1 + A_2$$

$$K_2 = (-\alpha + j\omega_d)A_1 + (-\alpha - j\omega_d)A_2$$

The characteristic determinate is

$$\Delta = \begin{vmatrix} 1 & 1 \\ (-\alpha + j\omega_d) & (-\alpha - j\omega_d) \end{vmatrix} = -j2\omega_d$$

The numerator determinates are

$$N_1 = \begin{vmatrix} K_1 & 1 \\ K_2 & (-\alpha - j\omega_d) \end{vmatrix} = -(\alpha + j\omega_d)K_1 - K_2$$

$$\text{and } N_2 = \begin{vmatrix} 1 & K_1 \\ (-\alpha + j\omega_d) & K_2 \end{vmatrix} = K_2 + (\alpha - j\omega_d)K_1$$

$$\text{It follows that } A_1 = \frac{N_1}{\Delta} = \frac{\omega_d K_1 - j(\alpha K_1 + K_2)}{2\omega_d}$$

$$\text{and } A_2 = \frac{N_2}{\Delta} = \frac{\omega_d K_1 + j(\alpha K_1 + K_2)}{2\omega_d}$$

We see from these expressions that $A_1 = A_2^*$

P 8.14 By definition, $B_1 = A_1 + A_2$. From the solution to Problem 8.13 we have

$$A_1 + A_2 = \frac{2\omega_d K_1}{2\omega_d} = K_1$$

But K_1 is $v(0)$, therefore, $B_1 = v(0)$, which is identical to Eq. (8.30).
By definition, $B_2 = j(A_1 - A_2)$. From Problem 8.13 we have

$$B_2 = j(A_1 - A_2) = \frac{j[-2j(\alpha K_1 + K_2)]}{2\omega_d} = \frac{\alpha K_1 + K_2}{\omega_d}$$

It follows that

$$K_2 = -\alpha K_1 + \omega_d B_2, \quad \text{but } K_2 = \frac{dv(0^+)}{dt} \quad \text{and } K_1 = B_1$$

Thus we have

$$\frac{dv}{dt}(0^+) = -\alpha B_1 + \omega_d B_2,$$

which is identical to Eq. (8.31).

P 8.15 [a] $\alpha = \frac{1}{2RC} = 1000\sqrt{2}$, $\omega_o = 10^3$, therefore overdamped

$$s_1 = -414.21, \quad s_2 = -2414.21$$

therefore $v = A_1 e^{-414.21t} + A_2 e^{-2414.21t}$


$$v(0^+) = 0 = A_1 + A_2; \quad \left[\frac{dv(0^+)}{dt} \right] = \frac{i_C(0^+)}{C} = 98,000 \text{ V/s}$$

Therefore $-414.21A_1 - 2414.21A_2 = 98,000$

$$A_1 = 49, \quad A_2 = -49$$

$$v(t) = 49[e^{-414.21t} - e^{-2414.21t}] \text{ V}, \quad t \geq 0$$

[b]

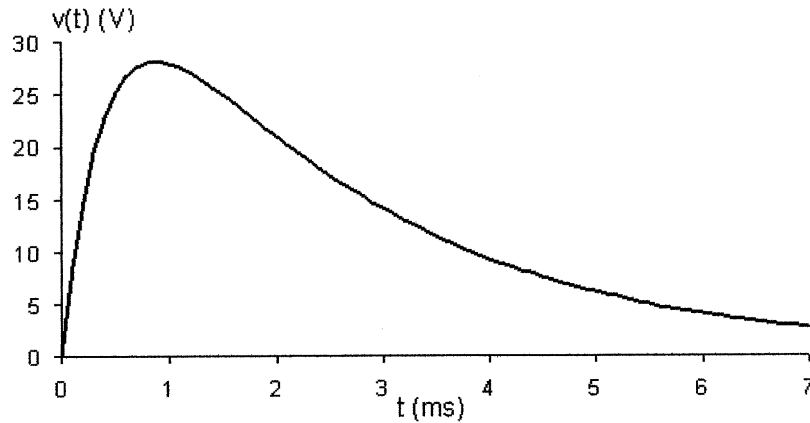


Example 8.4: $v_{\max} \cong 74.1 \text{ V}$ at 1.4 ms

Example 8.5: $v_{\max} \cong 36.1 \text{ V}$ at 1.0 ms

Problem 8.15: $v_{\max} \cong 28.2 \text{ V}$ at 0.9 ms

P 8.16

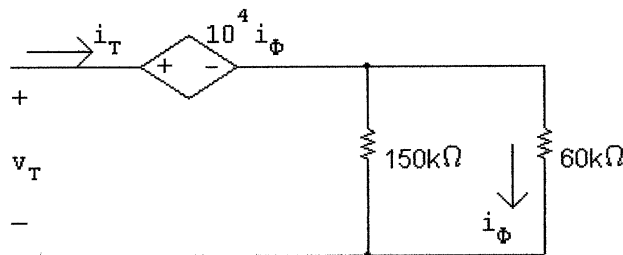

$$v_T = 10^4 \frac{i_T(150 \times 10^3)}{210 \times 10^3} + \frac{(150)(60)10^6}{210 \times 10^3} i_T$$

$$\frac{v_T}{i_T} = \frac{1500 \times 10^3}{210} + \frac{9000 \times 10^3}{210} = \frac{10,500}{210} \times 10^3 = 50 \text{ k}\Omega$$

$$V_o = \frac{75}{10}(6) = 45 \text{ V}; \quad I_o = 0$$

$$i_C(0) = -i_R(0) - i_L(0) = -\frac{45}{50,000} = -0.9 \text{ mA}$$

$$\frac{i_C(0)}{C} = \frac{-0.9}{1.25} \times 10^6 = -720 \times 10^3$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^9}{(8)(1.25)} = 10^8; \quad \omega_o = 10^4 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{10^9}{(2)(50)(1.25) \times 10^3} = 8000 \text{ rad/s}$$

$$\omega_d = \sqrt{(100 - 64) \times 10^6} = 6000 \text{ rad/s}$$

$$v_o = B_1 e^{-8000t} \cos 6000t + B_2 e^{-8000t} \sin 6000t$$


$$v_o(0) = B_1 = 45 \text{ V}$$

$$\frac{dv_o}{dt}(0) = 6000B_2 - 8000B_1 = -720 \times 10^3$$

$$\therefore 6000B_2 = 8000(45) - 720 \times 10^3; \quad \therefore B_2 = -60 \text{ V}$$

$$v_o = 45e^{-8000t} \cos 6000t - 60e^{-8000t} \sin 6000t \text{ V}, \quad t \geq 0$$

P 8.17

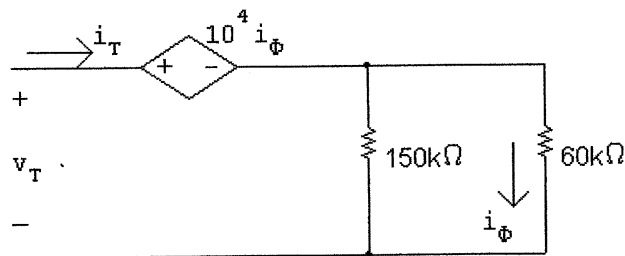

$$v_T = 10^4 \frac{i_T(150 \times 10^3)}{210 \times 10^3} + \frac{(150)(60)10^6}{210 \times 10^3} i_T$$

$$\frac{v_T}{i_T} = \frac{1500 \times 10^3}{210} + \frac{9000 \times 10^3}{210} = \frac{10,500}{210} \times 10^3 = 50 \text{ k}\Omega$$

$$V_o = \frac{75}{10}(6) = 45 \text{ V}; \quad I_o = 0$$

$$i_C(0) = -i_R(0) - i_L(0) = -\frac{45}{50,000} = -0.9 \text{ mA}$$

$$\frac{i_C(0)}{C} = \frac{-0.9 \text{ m}}{10^{-9}} = -900 \times 10^3$$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(10)(10^{-9})} = 10^8; \quad \omega_o = 10,000 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{(2)(50,000)(10^{-9})} = 10,000 \text{ rad/s}$$

$$\alpha^2 = \omega_o^2 \quad \text{so the response is critically damped}$$

$$v_o = D_1 t e^{-10,000t} + D_2 e^{-10,000t}$$


$$v_o(0) = D_2 = 45 \text{ V}$$

$$\frac{dv_o}{dt}(0) = D_1 - \alpha D_2 = -900 \times 10^3$$

$$\therefore D_1 = -900 \times 10^3 + (10,000)(45); \quad \therefore D_1 = -450,000 \text{ V/s}$$

$$v_o = -450,000 t e^{-10,000t} + 45 e^{-10,000t} \text{ V}, \quad t \geq 0$$

P 8.18

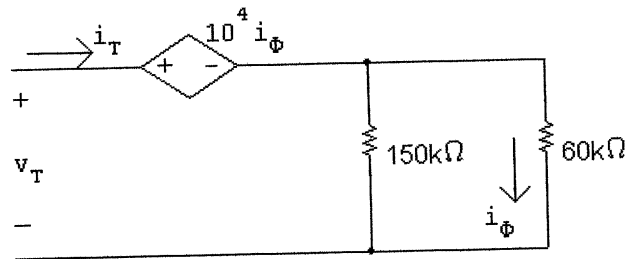

$$v_T = 10^4 \frac{i_T(150 \times 10^3)}{210 \times 10^3} + \frac{(150)(60)10^6}{210 \times 10^3} i_T$$

$$\frac{v_T}{i_T} = \frac{1500 \times 10^3}{210} + \frac{9000 \times 10^3}{210} = \frac{10,500}{210} \times 10^3 = 50 \text{ k}\Omega$$

$$V_o = \frac{75}{10}(6) = 45 \text{ V}; \quad I_o = 0$$

$$i_C(0) = -i_R(0) - i_L(0) = -\frac{45}{50,000} = -0.9 \text{ mA}$$

$$\frac{i_C(0)}{C} = \frac{-0.9}{800 \times 10^{-12}} = -1125 \times 10^3$$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(12.5)(800 \times 10^{-12})} = 10^8; \quad \omega_o = 10,000 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{(2)(50,000)(800 \times 10^{-12})} = 12,500 \text{ rad/s}$$

$\alpha^2 > \omega_o^2$ so the response is overdamped

$$v_o = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_o^2} = -12,500 \pm \sqrt{(12,500)^2 - 10^8} = -12,500 \pm 7500$$


$$\therefore s_{1,2} = -5000 \text{ r/s}, -20,000 \text{ r/s}$$

$$A_1 + A_2 = V_o = 45 \quad \text{and} \quad -5000A_1 - 20,000A_2 = -1125 \times 10^3$$


$$\therefore A_1 = -15, \quad A_2 = 60$$

$$v_o = -15e^{-5000t} + 60e^{-20,000t} \text{ V}, \quad t \geq 0$$

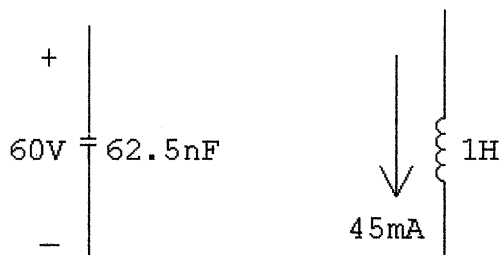P 8.19 $t < 0$: $V_o = 60 \text{ V}$, $I_o = 45 \text{ mA}$



$t > 0$:

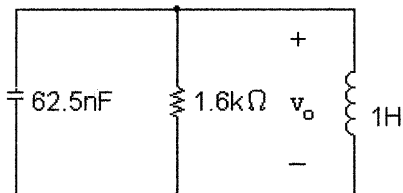

$$i_R(0) = \frac{60}{1600} = 37.5 \text{ mA}; \quad i_L(0) = 45 \text{ mA}$$

$$i_C(0) = -37.5 - 45 = -82.5 \text{ mA}$$

$$\alpha = \frac{1}{2RC} = \frac{10^9}{3200(62.5)} = 5000 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^9}{62.5} = 16 \times 10^6$$

$$s_{1,2} = -5000 \pm \sqrt{25 \times 10^6 - 16 \times 10^6} = -5000 \pm 3000$$

$$s_1 = -2000 \text{ rad/s}; \quad s_2 = -8000 \text{ rad/s}$$

$$\therefore v_o = A_1 e^{-2000t} + A_2 e^{-8000t}$$

$$A_1 + A_2 = v_o(0) = 60$$

$$\frac{dv_o}{dt}(0) = -2000A_1 - 8000A_2 = \frac{-82.5 \times 10^{-3}}{62.5 \times 10^{-9}} = -1320 \times 10^3$$

$$\text{Solving,} \quad A_1 = -140 \text{ V}, \quad A_2 = 200 \text{ V}$$

$$\therefore v_o = -140e^{-2000t} + 200e^{-8000t} \text{ V}, \quad t \geq 0$$

P 8.20 $\omega_o^2 = \frac{1}{LC} = \frac{16 \times 10^6}{0.64} = 25 \times 10^6$

$$\alpha = \frac{1}{2RC} = \frac{16 \times 10^6}{4000} = 4000 \text{ rad/s}; \quad \alpha^2 = 16 \times 10^6$$

$$\omega_d = \sqrt{(25 - 16) \times 10^6} = 3000 \text{ rad/s}$$

$$s_{1,2} = -4000 \pm j3000 \text{ rad/s}$$

$$v_o(t) = B_1 e^{-4000t} \cos 3000t + B_2 e^{-4000t} \sin 3000t$$

$$v_o(0) = B_1 = 60 \text{ V}$$

$$i_R(0) = \frac{60}{2000} = 30 \text{ mA}$$

$$i_L(0) = 45 \text{ mA}$$

$$i_C(0) = -i_R(0) - i_L(0) = -75 \text{ mA}$$

$$\frac{i_C(0)}{C} = (-75 \times 10^{-3})(16 \times 10^6) = -12 \times 10^5$$

$$\frac{dv_o}{dt}(0) = -4000B_1 + 3000B_2 = -12 \times 10^5$$

$$\therefore 3B_2 = 4B_1 - 1200 = 240 - 1200 = -960; \quad \therefore B_2 = -320 \text{ V}$$

$$v_o(t) = 60e^{-4000t} \cos 3000t - 320e^{-4000t} \sin 3000t \text{ V}, \quad t \geq 0$$

$$\text{P 8.21 } \omega_o^2 = \frac{1}{LC} = \frac{16 \times 10^6}{0.16} = 10^8; \quad \omega_o = 10^4$$

$$\alpha = \frac{1}{2RC} = \frac{16 \times 10^6}{1600} = 10^4$$

$$\therefore \alpha^2 = \omega_o^2 \text{ (critical damping)}$$

$$v_o(t) = D_1 t e^{-10,000t} + D_2 e^{-10,000t}$$

$$v_o(0) = D_2 = 60 \text{ V}$$

$$i_R(0) = \frac{60}{800} = 75 \text{ mA}$$

$$i_L(0) = 45 \text{ mA}$$

$$i_C(0) = -120 \text{ mA}$$

$$\frac{dv_o}{dt}(0) = -10,000D_2 + D_1$$

$$\frac{i_C(0)}{C} = (-120 \times 10^{-3})(16 \times 10^6) = -1920 \times 10^3$$

$$D_1 - 10,000D_2 = -1920 \times 10^3; \quad D_1 = -1320 \times 10^3 \text{ V/s}$$

$$v_o(t) = (60 - 132 \times 10^4 t) e^{-10,000t} \text{ V}, \quad t > 0$$

$$\text{P 8.22 [a] } v = L \left(\frac{di_L}{dt} \right) = 16[e^{-20,000t} - e^{-80,000t}] \text{ V}, \quad t \geq 0$$

$$\text{[b] } i_R = \frac{v}{R} = 40[e^{-20,000t} - e^{-80,000t}] \text{ mA}, \quad t \geq 0^+$$

$$\text{[c] } i_C = I - i_L - i_R = [-8e^{-20,000t} + 32e^{-80,000t}] \text{ mA}, \quad t \geq 0^+$$

$$\text{P 8.23 [a]} \quad v = L \left(\frac{di_L}{dt} \right) = 40e^{-32,000t} \sin 24,000t \text{ V}, \quad t \geq 0$$

$$\begin{aligned} \text{[b]} \quad i_C(t) &= I - i_R - i_L = 24 \times 10^{-3} - \frac{v}{625} - i_L \\ &= [24e^{-32,000t} \cos 24,000t - 32e^{-32,000t} \sin 24,000t] \text{ mA}, \quad t \geq 0^+ \end{aligned}$$

$$\text{P 8.24} \quad v = L \left(\frac{di_L}{dt} \right) = 960,000te^{-40,000t} \text{ V}, \quad t \geq 0$$

$$\text{P 8.25} \quad \omega_o^2 = \frac{1}{LC} = \frac{10^6}{(20)(5)} = 10^4; \quad \omega_o = 100 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{10^6}{(1600)(5)} = \frac{10^4}{80} = 125 \text{ rad/s}$$

$$s_{1,2} = -125 \pm \sqrt{(125)^2 - 10^4} = -125 \pm 75$$

$$s_1 = -50 \text{ rad/s}; \quad s_2 = -200 \text{ rad/s}$$

$$I_f = 15 \text{ mA}$$

$$i_L = 15 + A'_1 e^{-50t} + A'_2 e^{-200t}$$

$$\therefore -30 = 15 + A'_1 + A'_2; \quad A'_1 + A'_2 = -45 \times 10^{-3}$$

$$\frac{di_L}{dt} = -50A'_1 - 200A'_2 = \frac{60}{20} = 3$$

$$\text{Solving,} \quad A'_1 = -40 \text{ mA}; \quad A'_2 = -5 \text{ mA}$$

$$i_L = 15 - 40e^{-50t} - 5e^{-200t} \text{ mA}, \quad t \geq 0$$

$$\text{P 8.26} \quad \alpha = \frac{1}{2RC} = \frac{10^6}{(2500)(5)} = 80; \quad \alpha^2 = 6400$$

$$\omega_o^2 = 10^4; \quad \omega_d = \sqrt{10^4 - 6400} = 60 \text{ rad/s}$$

$$s_{1,2} = -\alpha \pm j\omega_d = -80 \pm j60 \text{ rad/s}$$

$$i_L = 15 + B'_1 e^{-80t} \cos 60t + B'_2 e^{-80t} \sin 60t$$

$$-30 = 15 + B'_1 \quad \therefore B'_1 = -45 \text{ mA}$$

$$\frac{di_L}{dt}(0) = -80B'_1 + 60B'_2 = 3$$

$$\therefore B'_2 = -10 \text{ mA}$$

$$i_L = 15 - 45e^{-80t} \cos 60t - 10e^{-80t} \sin 60t \text{ mA}, \quad t \geq 0$$

$$\text{P 8.27 } \alpha = \frac{1}{2RC} = \frac{10^6}{(2000)(5)} = 100$$

$$\alpha^2 = 10^4 = \omega_o^2 \quad \text{critical damping}$$

$$i_L = I_f + D'_1 t e^{-100t} + D'_2 e^{-100t} = 15 + D'_1 t e^{-100t} + D'_2 e^{-100t}$$

$$i_L(0) = -30 = 15 + D'_2; \quad \therefore D'_2 = -45 \text{ mA}$$

$$\frac{di_L}{dt}(0) = -100D'_2 + D'_1 = 3000 \times 10^{-3}$$

$$\therefore D'_1 = 3000 \times 10^{-3} + 100(-45 \times 10^{-3}) = -1500 \times 10^{-3}$$

$$i_L = 15 - 1500t e^{-100t} - 45e^{-100t} \text{ mA}, \quad t \geq 0$$

$$\text{P 8.28 } \alpha = \frac{1}{2RC} = \frac{10^6}{(1600)(6.25)} = 100; \quad \alpha^2 = 10^4$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^6}{(25)(6.25)} = 6400$$

$$s_{1,2} = -100 \pm \sqrt{10^4 - 6400} = -100 \pm 60$$

$$s_1 = -40 \text{ rad/s}; \quad s_2 = -160 \text{ rad/s}$$

$$v_o(\infty) = 0 = V_f$$

$$\therefore v_o = A'_1 e^{-40t} + A'_2 e^{-160t}$$

$$v_o(0) = 30 = A'_1 + A'_2$$

$$\text{Note: } i_C(0^+) = 0$$

$$\therefore \frac{dv_o}{dt}(0) = 0 = -40A'_1 - 160A'_2$$

$$\text{Solving, } A'_1 = 40 \text{ V}, \quad A'_2 = -10 \text{ V}$$

$$v_o(t) = 40e^{-40t} - 10e^{-160t} \text{ V}, \quad t > 0^+$$

P 8.29 [a] $i_o = I_f + A'_1 e^{-40t} + A'_2 e^{-160t}$

$$I_f = \frac{30}{800} = 37.5 \text{ mA}; \quad i_o(0) = 0$$

$$0 = 37.5 \times 10^{-3} + A'_1 + A'_2, \quad \therefore A'_1 + A'_2 = -37.5 \times 10^{-3}$$

$$\frac{di_o}{dt}(0) = \frac{30}{25} = -40A'_1 - 160A'_2$$

Solving, $A'_1 = -40 \text{ mA}; \quad A'_2 = 2.5 \text{ mA}$


$$i_o = 37.5 - 40e^{-40t} + 2.5e^{-160t} \text{ mA}, \quad t \geq 0$$

[b] $\frac{di_o}{dt} = [1600e^{-40t} - 400e^{-160t}] \times 10^{-3}$

$$L \frac{di_o}{dt} = 25(1.6)e^{-40t} - 25(0.4)e^{-160t}$$

$$\therefore v_o = 40e^{-40t} - 10e^{-160t} \text{ V}, \quad t \geq 0$$

P 8.30 For $t > 0$

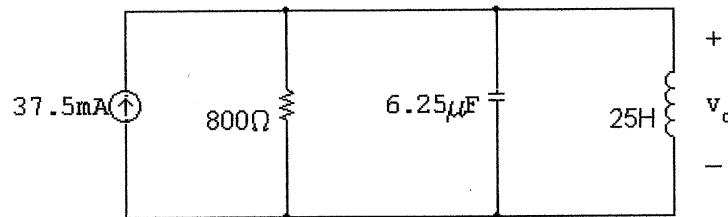

$$\alpha = \frac{1}{2RC} = 100; \quad \frac{1}{LC} = 6400$$

$$s_{1,2} = -100 \pm 60$$

$$s_1 = -40 \text{ rad/s}; \quad s_2 = -160 \text{ rad/s}$$

$$v_o = V_f + A'_1 e^{-40t} + A'_2 e^{-160t}$$

$$V_f = 0; \quad v_o(0^+) = 0; \quad i_C(0^+) = 37.5 \text{ mA}$$

$$\therefore A'_1 + A'_2 = 0$$

$$\frac{dv_o(0^+)}{dt} = \frac{i_C(0^+)}{6.25 \times 10^{-6}} = 6000 \text{ V/s}$$

$$\frac{dv_o(0^+)}{dt} = -40A'_1 - 160A'_2$$

$$-40A'_1 - 160A'_2 = 6000$$

$$A'_1 + 4A'_2 = -150$$

$$A'_1 + A'_2 = 0$$

$$\therefore A'_1 = 50 \text{ V}; \quad A'_2 = -50 \text{ V}$$

$$v_o = 50e^{-40t} - 50e^{-160t} \text{ V}, \quad t \geq 0$$

P 8.31 [a] From the solution to Prob. 8.30 $s_1 = -40 \text{ rad/s}$ and $s_2 = -160 \text{ rad/s}$, therefore

$$i_o = I_f + A'_1 e^{-40t} + A'_2 e^{-160t}$$

$$I_f = 37.5 \text{ mA}; \quad i_o(0^+) = 0; \quad \frac{di_o(0^+)}{dt} = 0$$

$$\therefore 0 = 37.5 + A'_1 + A'_2; \quad -40A'_1 - 160A'_2 = 0$$

It follows that

$$A'_1 = -50 \text{ mA}; \quad A'_2 = 12.5 \text{ mA}$$

$$\therefore i_o = 37.5 - 50e^{-40t} + 12.5e^{-160t} \text{ mA}, \quad t \geq 0$$


$$[b] \frac{di_o}{dt} = 2e^{-40t} - 2e^{-160t}$$

$$v_o = L \frac{di_o}{dt} = 25[2e^{-40t} - 2e^{-160t}]$$

$$v_o = 50e^{-40t} - 50e^{-160t} \text{ V}, \quad t \geq 0$$

P 8.32 $i_L(0^-) = i_L(0^+) = 30 \text{ mA}$

For $t > 0$

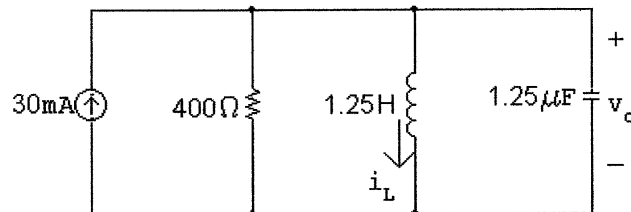

$$i_L(0^-) = i_L(0^+) = 30 \text{ mA}$$

$$\alpha = \frac{1}{2RC} = 1000 \text{ rad/s}; \quad \omega_o^2 = \frac{1}{LC} = 64 \times 10^4$$

$$s_1 = -400 \text{ rad/s} \quad s_2 = -1600 \text{ rad/s}$$

$$v_o(\infty) = 0 = V_f$$

$$v_o = A'_1 e^{-400t} + A'_2 e^{-1600t}$$

$$i_C(0^+) = -30 + 30 + 0 = 0$$

$$\therefore \frac{dv_o}{dt} = 0$$

$$\frac{dv_o}{dt}(0) = -400A'_1 - 1600A'_2$$

$$\therefore A'_1 + 400A'_2 = 0; \quad A'_1 + A'_2 = 0$$

$$\therefore A'_1 = 0; \quad A'_2 = 0$$

$$\therefore v_o = 0 \text{ for } t \geq 0$$


$$\text{Note: } v_o(0) = 0; \quad v_o(\infty) = 0; \quad \frac{dv_o(0)}{dt} = 0$$

Hence the 30 mA current circulates between the current source and the ideal inductor in the equivalent circuit. In the original circuit the 12 V source sustains a current of 30 mA in the inductor. This is an example of a circuit going directly into steady state when the switch is closed. There is no transient period, or interval.

P 8.33 $t < 0$:

$$v_o(0^-) = v_o(0^+) = \frac{1000}{1250}(25) = 20 \text{ V}$$

$$i_L(0^-) = i_L(0^+) = 0$$

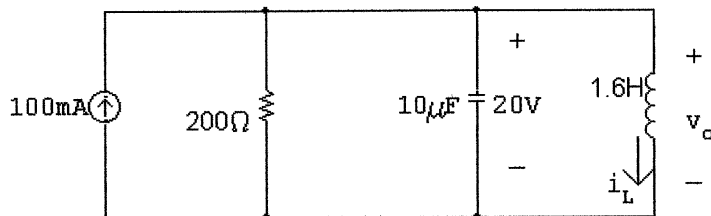$t > 0$ 

$$-100 + \frac{20}{0.2} + i_C(0^+) + 0 = 0; \quad \therefore i_C(0^+) = 0$$

$$\frac{1}{2RC} = \frac{10^6}{(400)(10)} = 250 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^6}{10(1.6)} = 62,500$$

$$\therefore \alpha^2 = \omega_o^2 \text{ critically damped}$$

$$[\mathbf{a}] \quad v_o = V_f + D'_1 t e^{-250t} + D'_2 e^{-250t}$$

$$V_f = 0$$

$$\frac{dv_o(0)}{dt} = -250D'_2 + D'_1 = 0$$

$$v_o(0^+) = 20 = D'_2$$

$$D'_1 = 250D'_2 = 5000 \text{ V/s}$$

$$\therefore v_o = 5000t e^{-250t} + 20e^{-250t} \text{ V}, \quad t \geq 0^+$$

$$[\mathbf{b}] \quad i_L = I_f + D'_3 t e^{-250t} + D'_4 e^{-250t}$$

$$i_L(0^+) = 0; \quad I_f = 100 \text{ mA}; \quad \frac{di_L(0^+)}{dt} = \frac{20}{1.6} = 12.5 \text{ A/s}$$

$$\therefore 0 = 100 + D'_4; \quad D'_4 = -100 \text{ mA};$$

$$-250D'_4 + D'_3 = 12.5; \quad D'_3 = -12.5 \text{ A/s}$$

$$\therefore i_L = 100 - 12,500t e^{-250t} - 100e^{-250t} \text{ mA} \quad t \geq 0$$

$$\text{P 8.34 } [\mathbf{a}] \quad w_L = \int_0^\infty p dt = \int_0^\infty v_o i_L dt$$

$$v_o = 5000t e^{-250t} + 20e^{-250t} \text{ V}$$

$$i_L = 0.1 - 12.5t e^{-250t} - 0.1e^{-250t} \text{ A}$$

$$p = 2e^{-250t} + 500te^{-250t} - 750te^{-500t} - 62,500t^2e^{-500t} - 2e^{-500t} \text{ W}$$

$$\begin{aligned} \frac{w_L}{2} &= \int_0^\infty e^{-250t} dt + 250 \int_0^\infty te^{-250t} dt - 375 \int_0^\infty te^{-500t} dt - \\ &\quad 31,250 \int_0^\infty t^2e^{-500t} dt - \int_0^\infty e^{-500t} dt \\ &= \frac{e^{-250t}}{-250} \Big|_0^\infty + \frac{250}{(250)^2} e^{-250t}(-250t - 1) \Big|_0^\infty - \\ &\quad \frac{375}{(500)^2} e^{-500t}(-500t - 1) \Big|_0^\infty - \\ &\quad \frac{31,250}{(-500)^3} e^{-500t}(500^2t^2 + 1000t + 2) \Big|_0^\infty - \\ &\quad \frac{e^{-500t}}{(-500)} \Big|_0^\infty \end{aligned}$$

All the upper limits evaluate to zero hence

$$\frac{w_L}{2} = \frac{1}{250} + \frac{250}{62,500} - \frac{375}{25 \times 10^4} - \frac{(31,250)(2)}{(5)^3 10^6} - \frac{1}{500}$$

$$w_L = 8 + 8 - 3 - 1 - 4 = 8 \text{ mJ}$$

Note this value corresponds to the final energy stored in the inductor, i.e.

$$w_L(\infty) = \frac{1}{2}(1.6)(0.1)^2 = 8 \text{ mJ.}$$

$$[\text{b}] \quad v = 5000te^{-250t} + 20e^{-250t} \text{ V}$$

$$i_R = \frac{v}{200} = 25te^{-250t} + 0.1e^{-250t} \text{ A}$$

$$p_R = vi_R = 2e^{-500t}[62,500t^2 + 500t + 1]$$

$$w_R = \int_0^\infty p_R dt$$

$$\begin{aligned} \frac{w_R}{2} &= 62,500 \int_0^\infty t^2e^{-500t} dt + 500 \int_0^\infty te^{-500t} dt + \int_0^\infty e^{-500t} dt \\ &= \frac{62,500e^{-500t}}{-125 \times 10^6} [25 \times 10^4 t^2 + 1000t + 2] \Big|_0^\infty + \\ &\quad \frac{500e^{-500t}}{25 \times 10^4} (-500t - 1) \Big|_0^\infty + \frac{e^{-500t}}{(-500)} \Big|_0^\infty \end{aligned}$$

Since all the upper limits evaluate to zero we have

$$\frac{w_R}{2} = \frac{62,500(2)}{125 \times 10^6} + \frac{500}{25 \times 10^4} + \frac{1}{500}$$

$$w_R = 2 + 4 + 4 = 10 \text{ mJ}$$

$$[c] \quad 100 = i_R + i_C + i_L \quad (\text{mA})$$

$$\begin{aligned} i_R + i_L &= 25,000te^{-250t} + 100e^{-250t} + 100 - 12,500te^{-250t} - 100e^{-250t} \text{ mA} \\ &= 100 + 12,500te^{-250t} \text{ mA} \end{aligned}$$

$$\therefore i_C = 100 - (i_R + i_L) = -12,500te^{-250t} \text{ mA} = -12.5te^{-250t} \text{ A}$$

$$\begin{aligned} p_C &= v i_C = [5000te^{-250t} + 20e^{-250t}] [-12.5te^{-250t}] \\ &= -250[250t^2e^{-500t} + te^{-500t}] \end{aligned}$$

$$\frac{w_C}{-250} = 250 \int_0^\infty t^2 e^{-500t} dt + \int_0^\infty te^{-500t} dt$$

$$\frac{w_C}{-250} = \frac{250e^{-500t}}{-125 \times 10^6} [25 \times 10^4 t^2 + 1000t + 2] \Big|_0^\infty + \frac{e^{-500t}}{25 \times 10^4} (-500t - 1) \Big|_0^\infty$$

Since all upper limits evaluate to zero we have

$$w_C = \frac{-250(250)(2)}{125 \times 10^6} - \frac{250(1)}{25 \times 10^4} = -1000 \times 10^{-6} - 10 \times 10^{-4} = -2 \text{ mJ}$$

Note this 2 mJ corresponds to the initial energy stored in the capacitor, i.e.,

$$w_C(0) = \frac{1}{2}(10 \times 10^{-6})(20)^2 = 2 \text{ mJ}.$$

Thus $w_C(\infty) = 0 \text{ mJ}$ which agrees with the final value of $v = 0$.

$$[d] \quad i_s = 100 \text{ mA}$$

$$\begin{aligned} p_s(\text{del}) &= 100v \text{ mW} \\ &= 0.1[5000te^{-250t} + 20e^{-250t}] \end{aligned}$$

$$= 2e^{-250t} + 500te^{-250t} \text{ W}$$

$$\frac{w_s}{2} = \int_0^\infty e^{-250t} dt + \int_0^\infty 250te^{-250t} dt$$

$$= \frac{e^{-250t}}{-250} \Big|_0^\infty + \frac{250e^{-250t}}{62,500} (-250t - 1) \Big|_0^\infty$$

$$= \frac{1}{250} + \frac{1}{250}$$

$$w_s = \frac{2(2)}{250} = \frac{4}{250} = 16 \text{ mJ}$$

$$[e] \quad w_L = 8 \text{ mJ} \quad (\text{absorbed})$$


$$w_R = 10 \text{ mJ} \quad (\text{absorbed})$$

$$w_C = 2 \text{ mJ} \quad (\text{delivered})$$


$$w_S = 16 \text{ mJ} \quad (\text{delivered})$$

$$\sum w_{\text{del}} = w_{\text{abs}} = 18 \text{ mJ}.$$

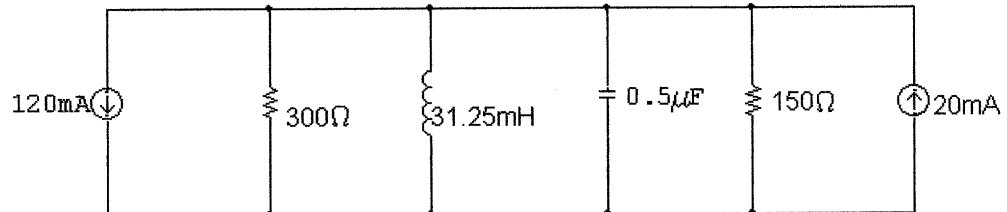P 8.35 $t < 0$: $i_L = 3/150 = 20 \text{ mA}$
 $t > 0$:



$$300 \parallel 150 = 100 \Omega$$

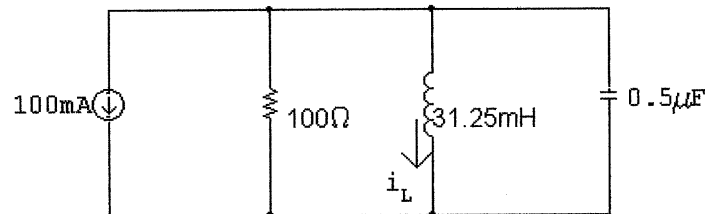

$$i_L(0) = 20 \text{ mA}, \quad i_L(\infty) = -100 \text{ mA}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^9}{(31.25)(0.5)} = 64 \times 10^6; \quad \omega_o = 8000 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{10^6}{(200)(0.5)} = 10^4; \quad \alpha^2 = 100 \times 10^6$$

$$\alpha^2 - \omega_o^2 = (100 - 64)10^6 = 36 \times 10^6$$

$$s_{1,2} = -10,000 \pm 6000$$

$$s_1 = -4000 \text{ rad/s}; \quad s_2 = -16,000 \text{ rad/s}$$

$$i_L = I_f + A'_1 e^{-4000t} + A'_2 e^{-16,000t}$$

$$i_L(\infty) = I_f = -100 \text{ mA}$$

$$i_L(0) = A'_1 + A'_2 + I_f = 20 \text{ mA}$$

$$\therefore A'_1 + A'_2 - 100 = 20 \quad \text{so} \quad A'_1 + A'_2 = 120 \text{ mA}$$

$$\frac{di_L}{dt}(0) = 0 = -4000A_1 - 16,000A'_2$$

$$\text{Solving,} \quad A'_1 = 160 \text{ mA}, \quad A'_2 = -40 \text{ mA}$$

$$i_L = -100 + 160e^{-4000t} - 40e^{-16,000t} \text{ mA}, \quad t \geq 0$$

$$\text{P 8.36} \quad v_C(0^+) = \frac{1}{2}(240) = 120 \text{ V}$$

$$i_L(0^+) = 60 \text{ mA}; \quad i_L(\infty) = \frac{240}{5} \times 10^{-3} = 48 \text{ mA}$$

$$\alpha = \frac{1}{2RC} = \frac{10^6}{2(2500)(5)} = 40$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^6}{400} = 2500$$

$$\alpha^2 = 1600; \quad \alpha^2 < \omega_o^2; \quad \therefore \text{underdamped}$$

$$s_{1,2} = -40 \pm j\sqrt{2500 - 1600} = -40 \pm j30 \text{ rad/s}$$

$$\begin{aligned} i_L &= I_f + B'_1 e^{-\alpha t} \cos \omega_d t + B'_2 e^{-\alpha t} \sin \omega_d t \\ &= 48 + B'_1 e^{-40t} \cos 30t + B'_2 e^{-40t} \sin 30t \end{aligned}$$

$$i_L(0) = 48 + B'_1; \quad B'_1 = 60 - 48 = 12 \text{ mA}$$

$$\frac{di_L}{dt}(0) = 30B'_2 - 40B'_1 = \frac{120}{80} = 1.5 = 1500 \times 10^{-3}$$

$$\therefore 30B'_2 = 40(12) \times 10^{-3} + 1500 \times 10^{-3}; \quad B'_2 = 66 \text{ mA}$$

$$\therefore i_L = 48 + 12e^{-40t} \cos 30t + 66e^{-40t} \sin 30t \text{ mA}, \quad t \geq 0$$

$$\text{P 8.37} \quad [\text{a}] \quad 2\alpha = 5000; \quad \alpha = 2500 \text{ rad/s}$$

$$\sqrt{\alpha^2 - \omega_o^2} = 1500; \quad \omega_o^2 = 4 \times 10^6; \quad \omega_o = 2000 \text{ rad/s}$$

$$\alpha = \frac{R}{2L} = 2500; \quad R = 5000L$$

$$\omega_o^2 = \frac{1}{LC} = 4 \times 10^6; \quad L = \frac{10^9}{4 \times 10^6(50)} = 5 \text{ H}$$

$$R = 25,000 \Omega$$

$$[\mathbf{b}] \quad i(0) = 0$$

$$L \frac{di(0)}{dt} = v_c(0); \quad \frac{1}{2}(50) \times 10^{-9} v_c^2(0) = 90 \times 10^{-6}$$

$$\therefore v_c^2(0) = 3600; \quad v_c(0) = 60 \text{ V}$$

$$\frac{di(0)}{dt} = \frac{60}{5} = 12 \text{ A/s}$$

$$[\mathbf{c}] \quad i(t) = A_1 e^{-1000t} + A_2 e^{-4000t}$$

$$i(0) = A_1 + A_2 = 0$$

$$\frac{di(0)}{dt} = -1000A_1 - 4000A_2 = 12$$

Solving,

$$\therefore A_1 = 4 \text{ mA}; \quad A_2 = -4 \text{ mA}$$

$$i(t) = 4e^{-1000t} - 4e^{-4000t} \text{ mA} \quad t \geq 0$$

$$[\mathbf{d}] \quad \frac{di(t)}{dt} = -4e^{-1000t} + 16e^{-4000t}$$

$$\frac{di}{dt} = 0 \text{ when } 16e^{-4000t} = 4e^{-1000t}$$

$$\text{or } e^{3000t} = 4$$

$$\therefore t = \frac{\ln 4}{3000} \mu\text{s} = 462.10 \mu\text{s}$$

$$[\mathbf{e}] \quad i_{\max} = 4e^{-0.4621} - 4e^{-1.8484} = 1.89 \text{ mA}$$

$$[\mathbf{f}] \quad v_L(t) = 5 \frac{di}{dt} = [-20e^{-1000t} + 80e^{-4000t}] \text{ V}, \quad t \geq 0^+$$

P 8.38 $\alpha = 800 \text{ rad/s}; \quad \omega_d = 600 \text{ rad/s}$


$$\omega_o^2 - \alpha^2 = 36 \times 10^4; \quad \omega_o^2 = 100 \times 10^4; \quad \omega_o = 1000 \text{ rad/s}$$

$$\alpha = \frac{R}{2L} = 800; \quad R = 1600L$$

$$\frac{1}{LC} = 100 \times 10^4; \quad L = \frac{10^6}{(100 \times 10^4)(500)} = 2 \text{ mH}$$

$$\therefore R = 3.2 \Omega$$
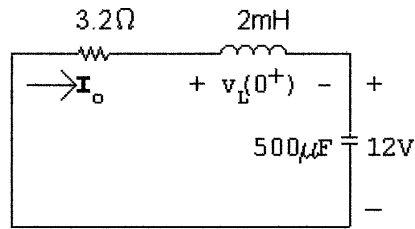
$$i(0^+) = B_1 = 0 \text{ A}; \quad \text{at } t = 0^+$$



$$12 + 0 + v_L(0^+) = 0; \quad v_L(0^+) = -12 \text{ V}$$

$$\frac{di(0^+)}{dt} = \frac{-12}{0.002} = -6000 \text{ A/s}$$

$$\therefore \frac{di(0^+)}{dt} = 600B_2 - 800B_1 = -6000$$

$$\therefore 600B_2 = 800B_1 - 6000; \quad \therefore B_2 = -10 \text{ A}$$

$$\therefore i = -10e^{-800t} \sin 600t \text{ A}, \quad t \geq 0$$

P 8.39 From Prob. 8.38 we know v_c will be of the form

$$v_c = B_3 e^{-800t} \cos 600t + B_4 e^{-800t} \sin 600t$$

From Prob. 8.38 we have

$$v_c(0) = 12 \text{ V} = B_3$$

and

$$\frac{dv_c(0)}{dt} = \frac{i_C(0)}{C} = 0$$

$$\frac{dv_c(0)}{dt} = 600B_4 - 800B_3$$

$$\therefore 600B_4 = 800B_3 + 0; \quad B_4 = 16 \text{ V}$$

$$v_c(t) = 12e^{-800t} \cos 600t + 16e^{-800t} \sin 600t \text{ V} \quad t \geq 0$$

P 8.40 [a] $t < 0$:

$$i_o = \frac{120}{8000} = 15 \text{ mA}; \quad v_o = (5000)(0.015) = 75 \text{ V}$$

$t > 0$:

$$\alpha = \frac{R}{2L} = \frac{5000}{2(1)} = 2500 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^9}{(1)(250)} = 4 \times 10^6 = 400 \times 10^4$$

$$\alpha^2 - \omega_o^2 = 625 \times 10^4 - 400 \times 10^4 = 225 \times 10^4$$

$$\therefore s_{1,2} = -2500 \pm 1500$$

$$s_1 = -1000 \text{ rad/s} \quad s_2 = -4000 \text{ rad/s}$$

$$\therefore i_o(t) = A_1 e^{-1000t} + A_2 e^{-4000t}$$

$$i_o(0) = A_1 + A_2 = 15 \times 10^{-3}$$

$$\frac{di_o}{dt}(0) = -1000A_1 - 4000A_2 = 0$$

$$\text{Solving,} \quad A_1 = 20 \text{ mA}; \quad A_2 = -5 \text{ mA}$$

$$i_o(t) = 20e^{-1000t} - 5e^{-4000t} \text{ mA}, \quad t \geq 0^+$$

$$[\text{b}] v_o(t) = A_1 e^{-1000t} + A_2 e^{-4000t}$$

$$v_o(0) = A_1 + A_2 = 75$$

$$\frac{dv_o}{dt}(0) = -1000A_1 - 4000A_2 = \frac{-15 \times 10^{-3}}{250 \times 10^{-9}}$$

$$\text{Solving,} \quad A_1 = 80 \text{ V}; \quad A_2 = -5 \text{ V}$$

$$v_o(t) = 80e^{-1000t} - 5e^{-4000t} \text{ V}, \quad t \geq 0^+$$

Check:

$$5000i_o + 1 \frac{di_o}{dt} = v_o$$

$$5000i_o = 100e^{-1000t} - 25e^{-4000t}$$

$$\frac{di_o}{dt} = -20e^{-1000t} + 20e^{-4000t}$$

$$\therefore 5000i_o + \frac{di_o}{dt} = 80e^{-1000t} - 5e^{-4000t} \text{ V} \quad (\text{checks})$$

$$\text{P 8.41 [a]} \quad \omega_o^2 = \frac{1}{LC} = \frac{10^9}{(0.25)(160)} = \frac{10^8}{4} = 25 \times 10^6$$

$$\alpha = \frac{R}{2L} = \omega_o = 5000 \text{ rad/s}$$

$$\therefore R = (5000)(2)L = 2500 \Omega$$

$$\text{[b]} \quad i(0) = i_L(0) = 24 \text{ mA}$$

$$v_L(0) = 90 - (0.024)(2500) = 30 \text{ V}$$

$$\frac{di}{dt}(0) = \frac{30}{0.25} = 120 \text{ A/s}$$

$$\text{[c]} \quad v_C = D_1 t e^{-5000t} + D_2 e^{-5000t}$$

$$v_C(0) = D_2 = 90 \text{ V}$$


$$\frac{dv_C}{dt}(0) = D_1 - 5000D_2 = \frac{i_C(0)}{C} = \frac{-i_L(0)}{C}$$

$$D_1 - 450,000 = -\frac{24 \times 10^{-3}}{160 \times 10^{-9}} = -150,000$$

$$\therefore D_1 = 300,000 \text{ V/s}$$

$$v_C = 300,000 t e^{-5000t} + 90 e^{-5000t} \text{ V}, \quad t \geq 0^+$$

P 8.42 [a] For $t > 0$:

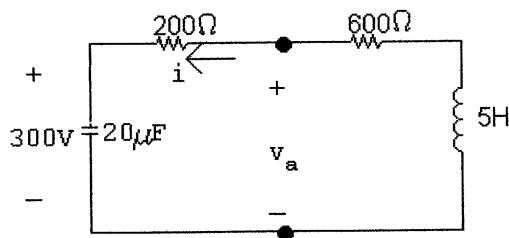

$$\text{Since } i(0^-) = i(0^+) = 0$$

$$v_a(0^+) = 300 \text{ V}$$

$$\text{[b]} \quad v_a = 200i + 5 \times 10^4 \int_0^t i \, dx + 300$$

$$\frac{dv_a}{dt} = 200 \frac{di}{dt} + 5 \times 10^4 i$$

$$\frac{dv_a(0^+)}{dt} = 200 \frac{di(0^+)}{dt} + 5 \times 10^4 i(0^+) = 200 \frac{di(0^+)}{dt}$$

$$-L \frac{di(0^+)}{dt} = 300$$

$$\frac{di(0^+)}{dt} = -0.2(300) = -60 \text{ A/s}$$

$$\therefore \frac{dv_a(0^+)}{dt} = -12,000 \text{ V/s}$$

$$[\text{c}] \alpha = \frac{R}{2L} = \frac{800}{10} = 80 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^6}{(5)(20)} = 10^4$$

$$s_{1,2} = -80 \pm \sqrt{6400 - 10^4} = -80 \pm j60 \text{ rad/s}$$

Underdamped:

$$v_a = B_1 e^{-80t} \cos 60t + B_2 e^{-80t} \sin 60t$$

$$v_a(0) = B_1 = 300 \text{ V}$$

$$\frac{dv_a(0)}{dt} = -80B_1 + 60B_2 = -12,000; \quad \therefore B_2 = 200 \text{ V}$$

$$v_a = 300e^{-80t} \cos 60t + 200e^{-80t} \sin 60t \text{ V}, \quad t \geq 0^+$$

$$\text{P 8.43 } i_L(0^-) = i_L(0^+) = \frac{70}{50 + 200} = 280 \text{ mA}$$

$$v_c(0^-) = v_c(0^+) = 200(0.280) = 56 \text{ V}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(0.100)(200 \times 10^{-9})} = 50 \times 10^6$$

$$\alpha = \frac{R}{2L} = \frac{200}{2(0.100)} = 1000; \quad \alpha^2 = 10^6$$

$$\alpha^2 < \omega_o^2 \quad \therefore \quad \text{underdamped}$$

$$s_{1,2} = -1000 \pm j7000 \text{ rad/s}$$


$$i = B_1 e^{-1000t} \cos 7000t + B_2 e^{-1000t} \sin 7000t$$

$$i(0) = B_1 = 280 \text{ mA}$$

$$\frac{di}{dt}(0) = 7000B_2 - 1000B_1 = 0$$


$$\therefore B_2 = \frac{1}{7}B_1 = 40 \text{ mA}$$

$$i = 280e^{-1000t} \cos 7000t + 40e^{-1000t} \sin 7000t \text{ mA}, \quad t \geq 0^+$$

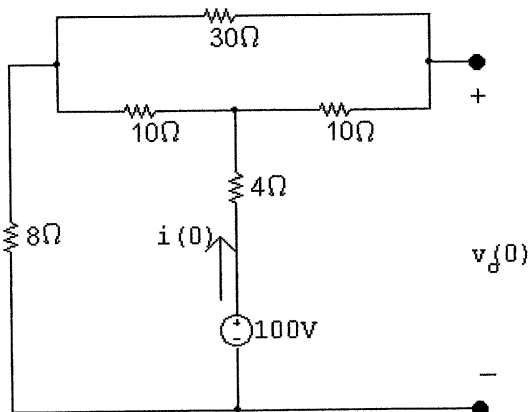P 8.44 $t < 0$:

$$i(0) = \frac{100}{4 + 8 + 8} = \frac{100}{20} = 5 \text{ A}$$

$$v_o(0) = 100 - 5(4) - 10(5) \left(\frac{10}{50}\right) = 70 \text{ V}$$

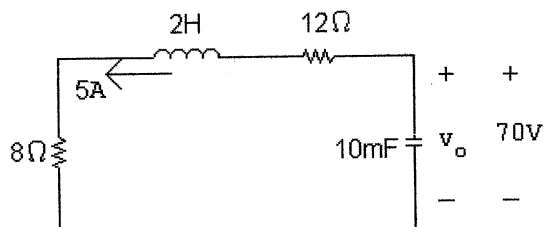 $t > 0$:

$$\alpha = \frac{R}{2L} = \frac{20}{4} = 5, \quad \alpha^2 = 25$$

$$\omega_o^2 = \frac{1}{LC} = \frac{100}{2} = 50$$

$$\omega_o^2 > \alpha^2 \quad \text{underdamped}$$

$$v_o = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t; \quad \omega_d = \sqrt{50 - 25} = 5$$

$$v_o = B_1 e^{-5t} \cos 5t + B_2 e^{-5t} \sin 5t$$

$$v_o(0) = B_1 = 70 \text{ V}$$

$$C \frac{dv_o}{dt}(0) = -5, \quad \frac{dv_o}{dt} = \frac{-5}{10} \times 10^3 = -500 \text{ V/s}$$

$$\frac{dv_o}{dt}(0) = -5B_1 + 5B_2 = -500$$

$$5B_2 = -500 + 5B_1 = -500 + 350; \quad B_2 = -150/5 = -30 \text{ V}$$

$$\therefore v_o = 70e^{-5t} \cos 5t - 30e^{-5t} \sin 5t \text{ V}, \quad t \geq 0$$

$$\text{P 8.45} \quad \alpha = \frac{R}{2L} = 5000 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^9}{20} = 50 \times 10^6$$

$$s_{1,2} = -5000 \pm \sqrt{25 \times 10^6 - 50 \times 10^6} = -5000 \pm j5000 \text{ rad/s}$$

$$v_o = V_f + B'_1 e^{-5000t} \cos 5000t + B'_2 e^{-5000t} \sin 5000t$$

$$v_o(0) = 0 = V_f + B'_1$$

$$v_o(\infty) = 40 \text{ V}; \quad \therefore B'_1 = -40 \text{ V}$$

$$\frac{dv_o(0)}{dt} = 0 = 5000B'_2 - 5000B'_1$$

$$\therefore B'_2 = B'_1 = -40 \text{ V}$$

$$v_o = 40 - 40e^{-5000t} \cos 5000t - 40e^{-5000t} \sin 5000t \text{ V}, \quad t \geq 0$$

$$\text{P 8.46} \quad \alpha = \frac{R}{2L} = 5000 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(0.4)(100 \times 10^{-9})} = 25 \times 10^6 \quad \therefore \omega_o = 5000 \text{ rad/s}$$

The response is therefore critically damped

$$v_o = V_f + D'_1 t e^{-5000t} + D'_2 e^{-5000t}$$

$$v_o(0) = 0 = V_f + D'_2$$

$$v_o(\infty) = 40 \text{ V}; \quad \therefore D'_2 = -40 \text{ V}$$

$$\frac{dv_o(0)}{dt} = 0 = D'_1 - \alpha D'_2$$

$$\therefore D'_1 = (5000)(-40) = -200,000 \text{ V/s}$$

$$v_o = 40 - 200,000 t e^{-5000t} - 40 e^{-5000t} \text{ V}, \quad t \geq 0$$

$$\text{P 8.47 } \alpha = \frac{R}{2L} = 5000 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(0.4)(156.25 \times 10^{-9})} = 16 \times 10^6 \quad \therefore \omega_o = 4000 \text{ rad/s}$$

The response is therefore overdamped

$$s_{1,2} = -5000 \pm \sqrt{5000^2 - 4000^2} = -5000 \pm 3000 = -2000 \text{ rad/s}, -8000 \text{ rad/s},$$

$$v_o = V_f + A'_1 e^{-2000t} + A'_2 e^{-8000t}$$

$$v_o(0) = 0 = V_f + A'_1 + A'_2$$

$$v_o(\infty) = 40 \text{ V}; \quad \therefore A'_1 + A'_2 = -40 \text{ V}$$

$$\frac{dv_o(0)}{dt} = 0 = s_1 A'_1 + s_2 A'_2 = -2000 A'_1 - 8000 A'_2$$

$$\therefore A'_1 = -53.33 \text{ V}, \quad A'_2 = 13.33 \text{ V}$$

$$v_o = 40 - 53.33e^{-2000t} + 13.33e^{-8000t} \text{ V}, \quad t \geq 0$$

P 8.48 [a] Let i be the current in the direction of the voltage drop $v_o(t)$. Then by hypothesis

$$i = i_f + B'_1 e^{-\alpha t} \cos \omega_d t + B'_2 e^{-\alpha t} \sin \omega_d t$$

$$i_f = i(\infty) = 0, \quad i(0) = \frac{V_g}{R} = B'_1$$

$$\text{Therefore } i = B'_1 e^{-\alpha t} \cos \omega_d t + B'_2 e^{-\alpha t} \sin \omega_d t$$

$$L \frac{di(0)}{dt} = 0, \quad \text{therefore } \frac{di(0)}{dt} = 0$$

$$\frac{di}{dt} = [(\omega_d B'_2 - \alpha B'_1) \cos \omega_d t - (\alpha B'_2 + \omega_d B'_1) \sin \omega_d t] e^{-\alpha t}$$

$$\text{Therefore } \omega_d B'_2 - \alpha B'_1 = 0; \quad B'_2 = \frac{\alpha}{\omega_d} B'_1 = \frac{\alpha V_g}{\omega_d R}$$

Therefore

$$\begin{aligned}
 v_o &= L \frac{di}{dt} = - \left\{ L \left(\frac{\alpha^2 V_g}{\omega_d R} + \frac{\omega_d V_g}{R} \right) \sin \omega_d t \right\} e^{-\alpha t} \\
 &= - \left\{ \frac{L V_g}{R} \left(\frac{\alpha^2}{\omega_d} + \omega_d \right) \sin \omega_d t \right\} e^{-\alpha t} \\
 &= - \frac{V_g L}{R} \left(\frac{\alpha^2 + \omega_d^2}{\omega_d} \right) e^{-\alpha t} \sin \omega_d t \\
 &= - \frac{V_g L}{R} \left(\frac{\omega_o^2}{\omega_d} \right) e^{-\alpha t} \sin \omega_d t \\
 &= - \frac{V_g L}{R \omega_d} \left(\frac{1}{LC} \right) e^{-\alpha t} \sin \omega_d t \\
 v_o &= - \frac{V_g}{RC \omega_d} e^{-\alpha t} \sin \omega_d t, \quad t \geq 0^+
 \end{aligned}$$

$$[b] \quad \frac{dv_o}{dt} = - \frac{V_g}{\omega_d RC} \{ \omega_d \cos \omega_d t - \alpha \sin \omega_d t \} e^{-\alpha t}$$

$$\frac{dv_o}{dt} = 0 \quad \text{when} \quad \tan \omega_d t = \frac{\omega_d}{\alpha}$$

Therefore $\omega_d t = \tan^{-1}(\omega_d/\alpha)$ (smallest t)

$$t = \frac{1}{\omega_d} \tan^{-1} \left(\frac{\omega_d}{\alpha} \right)$$

P 8.49 [a] From Problem 8.48 we have

$$v_o = \frac{-V_g}{RC \omega_d} e^{-\alpha t} \sin \omega_d t$$

$$\alpha = \frac{R}{2L} = \frac{120}{0.01} = 12,000 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^{12}}{2500} = 400 \times 10^6$$

$$\omega_d = \sqrt{\omega_o^2 - \alpha^2} = 16 \text{ krad/s}$$

$$\frac{-V_g}{RC \omega_d} = \frac{-(-600)10^9}{(120)(500)(16) \times 10^3} = 625$$

$$\therefore v_o = 625 e^{-12,000t} \sin 16,000t \text{ V}$$

[b] From Problem 8.48

$$t_d = \frac{1}{\omega_d} \tan^{-1} \left(\frac{\omega_d}{\alpha} \right) = \frac{1}{16,000} \tan^{-1} \left(\frac{16,000}{12,000} \right)$$

$$t_d = 57.96 \mu\text{s}$$

[c] $v_{\max} = 625e^{-0.012(57.96)} \sin[(0.016)(57.96)] = 249.42 \text{ V}$

[d] $R = 12 \Omega; \quad \alpha = 1200 \text{ rad/s}$

$$\omega_d = 19,963.97 \text{ rad/s}$$

$$v_o = 5009.02e^{-1200t} \sin 19,963.97t \text{ V}, \quad t \geq 0$$

$$t_d = 75.67 \mu\text{s}$$

$$v_{\max} = 4565.96 \text{ V}$$

P 8.50 $i_C(0) = 0; \quad v_o(0) = 200 \text{ V}$

$$\alpha = \frac{R}{2L} = \frac{4}{2(0.04)} = 50 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^3}{0.4} = 2500$$

$$\therefore \alpha^2 = \omega_o^2; \quad \text{critical damping}$$

$$v_o(t) = V_f + D'_1 t e^{-50t} + D'_2 e^{-50t}$$

$$V_f = 100 \text{ V}$$


$$v_o(0) = 100 + D'_2 = 200; \quad D'_2 = 100 \text{ V}$$

$$\frac{dv_o}{dt}(0) = -50D'_2 + D'_1 = 0$$

$$D'_1 = 50D'_2 = 5000 \text{ V/s}$$

$$v_o = 100 + 5000t e^{-50t} + 100e^{-50t} \text{ V}, \quad t \geq 0$$


P 8.51 [a] $t < 0$:

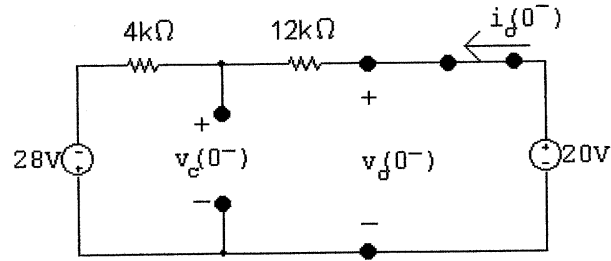

$$i_o(0^-) = \frac{48}{16,000} = 3 \text{ mA}$$

$$v_c(0^-) = 20 - (12,000)(0.003) = -16 \text{ V}$$

$t = 0^+$:

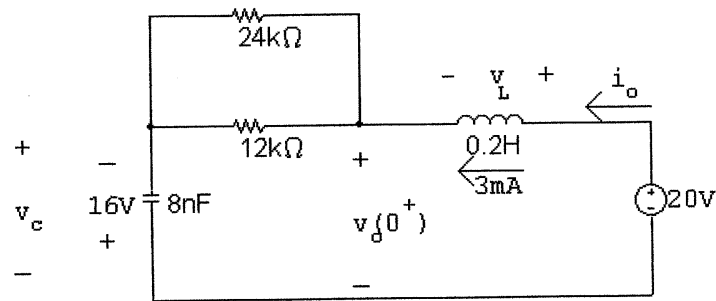

$$12 \text{ k}\Omega \parallel 24 \text{ k}\Omega = 8 \text{ k}\Omega$$

$$\therefore v_o(0^+) = (0.003)(8000) - 16 = 24 - 16 = 8 \text{ V}$$

$$\text{and } v_L(0^+) = 20 - 8 = 12 \text{ V}$$

[b] $v_o(t) = 8000i_o + v_c$

$$\frac{dv_o}{dt}(t) = 8000 \frac{di_o}{dt} + \frac{dv_c}{dt}$$

$$\frac{dv_o}{dt}(0^+) = 8000 \frac{di_o}{dt}(0^+) + \frac{dv_c}{dt}(0^+)$$

$$v_L(0^+) = L \frac{di_o}{dt}(0^+)$$

$$\frac{di_o}{dt}(0^+) = \frac{v_L(0^+)}{L} = \frac{12}{0.2} = 60 \text{ A/s}$$

$$C \frac{dv_c}{dt}(0^+) = i_o(0^+)$$

$$\therefore \frac{dv_c}{dt}(0^+) = \frac{3 \times 10^{-3}}{8 \times 10^{-9}} = 375,000$$

$$\therefore \frac{dv_o}{dt}(0^+) = 8000(60) + 375,000 = 855,000 \text{ V/s}$$

$$[c] \omega_o^2 = \frac{1}{LC} = \frac{10^9}{1.6} = 625 \times 10^6; \quad \omega_o = 25,000 \text{ rad/s}$$

$$\alpha = \frac{R}{2L} = \frac{8000}{0.4} = 20,000 \text{ rad/s}; \quad \alpha^2 = 400 \times 10^6$$

$$\alpha^2 < \omega_o^2 \quad \text{underdamped}$$

$$s_{1,2} = -20,000 \pm j15,000 \text{ rad/s}$$

$$v_o(t) = V_f + B'_1 e^{-20,000t} \cos 15,000t + B'_2 e^{-20,000t} \sin 15,000t$$

$$V_f = v_o(\infty) = 20 \text{ V}$$


$$8 = 20 + B'_1; \quad B'_1 = -12 \text{ V}$$

$$-20,000B'_1 + 15,000B'_2 = 855,000$$

$$\text{Solving,} \quad B'_2 = 41 \text{ V}$$

$$\therefore v_o(t) = 20 - 12e^{-20,000t} \cos 15,000t + 41e^{-20,000t} \sin 15,000t \text{ V}, \quad t \geq 0^+$$


P 8.52 $t < 0$:

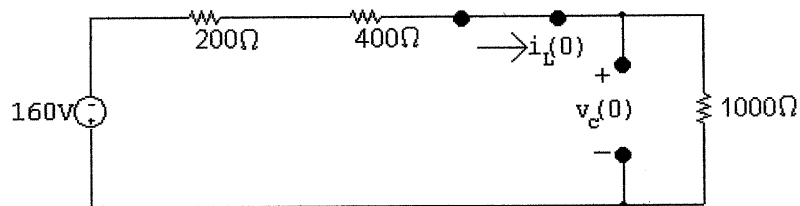

$$i_L(0) = \frac{-160}{1600} = -100 \text{ mA}$$

$$v_C(0) = 1000i_L(0) = -100 \text{ V}$$

$t > 0$:

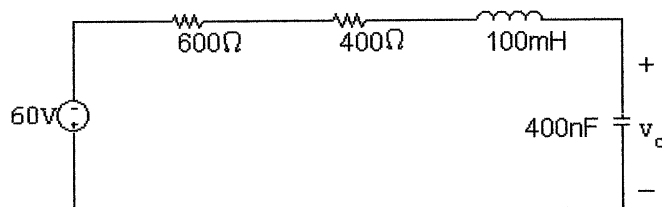

$$\alpha = \frac{R}{2L} = \frac{1000}{200} \times 10^3 = 5000 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{(10^9)(10^3)}{(100)(400)} = \frac{10^8}{4} = 25 \times 10^6$$

$\omega_o = 5000 \text{ rad/s}$ \therefore critical damping

$$v_C(t) = V_f + D'_1 t e^{-5000t} + D'_2 e^{-5000t}$$

$$v_C(0) = -100 \text{ V}; \quad V_f = -60 \text{ V}$$

$$\therefore -100 = -60 + D'_2; \quad D'_2 = -40 \text{ V}$$

$$C \frac{dv_C}{dt}(0) = i_L(0) = -100 \times 10^{-3}$$

$$\frac{dv_C}{dt}(0) = \frac{-100 \times 10^{-3}}{400 \times 10^{-9}} = -250,000 \text{ V/s}$$

$$\therefore D'_1 = 5000(-40) - 250,000 = -450,000$$

$$v_C(t) = -60 - 450,000 t e^{-5000t} - 40 e^{-5000t} \text{ V}, \quad t \geq 0$$

P 8.53 [a] $v_c = V_f + [B'_1 \cos \omega_d t + B'_2 \sin \omega_d t] e^{-\alpha t}$

$$\frac{dv_c}{dt} = [(\omega_d B'_2 - \alpha B'_1) \cos \omega_d t - (\alpha B'_2 + \omega_d B'_1) \sin \omega_d t] e^{-\alpha t}$$

Since the initial stored energy is zero,

$$v_c(0^+) = 0 \quad \text{and} \quad \frac{dv_c(0^+)}{dt} = 0$$

It follows that $B'_1 = -V_f$ and $B'_2 = \frac{\alpha B'_1}{\omega_d}$

When these values are substituted into the expression for $[dv_c/dt]$, we get

$$\frac{dv_c}{dt} = \left(\frac{\alpha^2}{\omega_d} + \omega_d \right) V_f e^{-\alpha t} \sin \omega_d t$$

$$\text{But } V_f = V \quad \text{and} \quad \frac{\alpha^2}{\omega_d} + \omega_d = \frac{\alpha^2 + \omega_d^2}{\omega_d} = \frac{\omega_o^2}{\omega_d}$$

$$\text{Therefore} \quad \frac{dv_c}{dt} = \left(\frac{\omega_o^2}{\omega_d} \right) V e^{-\alpha t} \sin \omega_d t$$

$$\text{[b]} \quad \frac{dv_c}{dt} = 0 \quad \text{when} \quad \sin \omega_d t = 0, \quad \text{or} \quad \omega_d t = n\pi$$

where $n = 1, 2, 3, \dots$

$$\text{Therefore} \quad t = \frac{n\pi}{\omega_d}$$

[c] When $t_n = \frac{n\pi}{\omega_d}$, $\cos \omega_d t_n = \cos n\pi = (-1)^n$

and $\sin \omega_d t_n = \sin n\pi = 0$

Therefore $v_c(t_n) = V[1 - (-1)^n e^{-\alpha n\pi/\omega_d}]$

[d] It follows from [c] that

$$v_c(t_1) = V + Ve^{-(\alpha\pi/\omega_d)} \quad \text{and} \quad v_c(t_3) = V + Ve^{-(3\alpha\pi/\omega_d)}$$

Therefore $\frac{v_c(t_1) - V}{v_c(t_3) - V} = \frac{e^{-(\alpha\pi/\omega_d)}}{e^{-(3\alpha\pi/\omega_d)}} = e^{(2\alpha\pi/\omega_d)}$

But $\frac{2\pi}{\omega_d} = t_3 - t_1 = T_d$, thus $\alpha = \frac{1}{T_d} \ln \frac{[v_c(t_1) - V]}{[v_c(t_3) - V]}$

P 8.54 $\alpha = \frac{1}{T_d} \ln \left\{ \frac{v_c(t_1) - V}{v_c(t_3) - V} \right\}; \quad T_d = t_3 - t_1 = \frac{3\pi}{12} - \frac{\pi}{12} = \frac{2\pi}{12} \text{ ms}$

$$\alpha = \frac{12,000}{2\pi} \ln \left[\frac{13.505}{0.985} \right] = 5000; \quad \omega_d = \frac{2\pi}{T_d} = 12,000 \text{ rad/s}$$

$$\omega_o^2 = \omega_d^2 + \alpha^2 = 144 \times 10^6 + 25 \times 10^6 = 169 \times 10^6$$


$$L = \frac{1}{(169)(0.2)} = 29.6 \text{ mH}; \quad R = 2\alpha L = 295.86 \Omega$$

P 8.55 At $t = 0$ the voltage across each capacitor is zero. It follows that since the operational amplifiers are ideal, the current in the $500 \text{ k}\Omega$ is zero. Therefore there cannot be an instantaneous change in the current in the $1 \mu\text{F}$ capacitor. Since the capacitor current equals $C(dv_o/dt)$, the derivative must be zero.

P 8.56 [a] From Example 8.13 $\frac{d^2 v_o}{dt^2} = 2$

therefore $\frac{dg(t)}{dt} = 2, \quad g(t) = \frac{dv_o}{dt}$
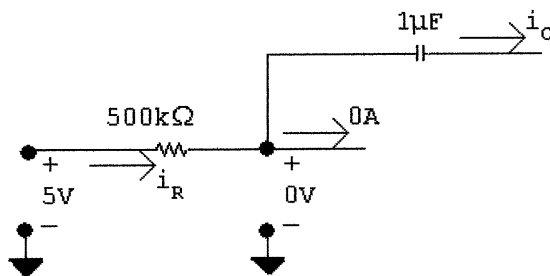
$$g(t) - g(0) = 2t; \quad g(t) = 2t + g(0); \quad g(0) = \frac{dv_o(0)}{dt}$$



$$i_R = \frac{5}{500} \times 10^{-3} = 10 \mu\text{A} = i_C = -C \frac{dv_o(0)}{dt}$$

$$\frac{dv_o(0)}{dt} = \frac{-10 \times 10^{-6}}{1 \times 10^{-6}} = -10 = g(0)$$

$$\frac{dv_o}{dt} = 2t - 10$$

$$dv_o = 2t dt - 10 dt$$

$$v_o - v_o(0) = t^2 - 10t; \quad v_o(0) = 8 \text{ V}$$

$$v_o = t^2 - 10t + 8, \quad 0 \leq t \leq t_{\text{sat}}$$

$$[\text{b}] \quad t^2 - 10t + 8 = -9$$

$$t^2 - 10t + 17 = 0$$

$$t \cong 2.17 \text{ s}$$

P 8.57 Part (1) — Example 8.14, with R_1 and R_2 removed:

$$[\text{a}] \quad R_a = 100 \text{ k}\Omega; \quad C_1 = 0.1 \text{ }\mu\text{F}; \quad R_b = 25 \text{ k}\Omega; \quad C_2 = 1 \text{ }\mu\text{F}$$

$$\frac{d^2 v_o}{dt^2} = \left(\frac{1}{R_a C_1} \right) \left(\frac{1}{R_b C_2} \right) v_g; \quad \frac{1}{R_a C_1} = 100 \quad \frac{1}{R_b C_2} = 40$$

$$v_g = 250 \times 10^{-3}; \quad \text{therefore} \quad \frac{d^2 v_o}{dt^2} = 1000$$

$$[\text{b}] \quad \text{Since } v_o(0) = 0 = \frac{dv_o(0)}{dt}, \quad \text{our solution is } v_o = 500t^2$$

The second op-amp will saturate when

$$v_o = 6 \text{ V}, \quad \text{or} \quad t_{\text{sat}} = \sqrt{6/500} \cong 0.1095 \text{ s}$$

$$[\text{c}] \quad \frac{dv_{o1}}{dt} = -\frac{1}{R_a C_1} v_g = -25$$

$$[\text{d}] \quad \text{Since } v_{o1}(0) = 0, \quad v_{o1} = -25t \text{ V}$$

$$\text{At } t = 0.1095 \text{ s}, \quad v_{o1} \cong -2.74 \text{ V}$$


Therefore the second amplifier saturates before the first amplifier saturates. Our expressions are valid for $0 \leq t \leq 0.1095 \text{ s}$. Once the second op-amp saturates, our linear model is no longer valid.

Part (2) — Example 8.14 with $v_{o1}(0) = -2 \text{ V}$ and $v_o(0) = 4 \text{ V}$:

[\text{a}] Initial conditions will not change the differential equation; hence the equation is the same as Example 8.14.

[b] $v_o = 5 + A'_1 e^{-10t} + A'_2 e^{-20t}$ (from Example 8.14)

$$v_o(0) = 4 = 5 + A'_1 + A'_2$$

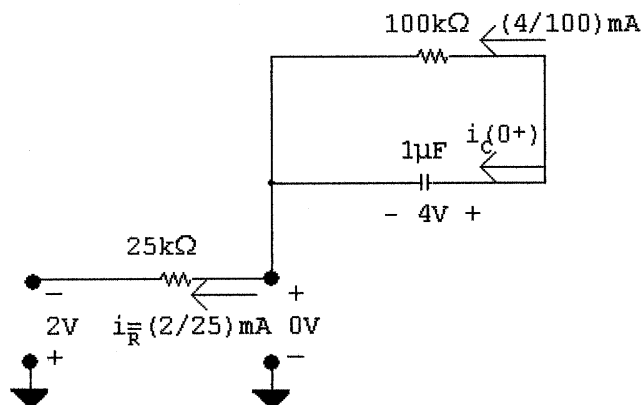

$$\frac{4}{100} + i_C(0^+) - \frac{2}{25} = 0$$

$$i_C(0^+) = \frac{4}{100} \text{ mA} = C \frac{dv_o(0^+)}{dt}$$

$$\frac{dv_o(0^+)}{dt} = \frac{0.04 \times 10^{-3}}{10^{-6}} = 40 \text{ V/s}$$

$$\frac{dv_o}{dt} = -10A'_1 e^{-10t} - 20A'_2 e^{-20t}$$

$$\frac{dv_o}{dt}(0^+) = -10A'_1 - 20A'_2 = 40$$

Therefore $-A'_1 - 2A'_2 = 4$ and $A'_1 + A'_2 = -1$

Thus, $A'_1 = 2$ and $A'_2 = -3$

$$v_o = 5 + 2e^{-10t} - 3e^{-20t} \text{ V}$$

[c] Same as Example 8.14:

$$\frac{dv_{o1}}{dt} + 20v_{o1} = -25$$

[d] From Example 8.14:

$$v_{o1}(\infty) = -1.25 \text{ V}; \quad v_1(0) = -2 \text{ V} \quad (\text{given})$$

Therefore

$$v_{o1} = -1.25 + (-2 + 1.25)e^{-20t} = -1.25 - 0.75e^{-20t} \text{ V}$$

P 8.58 [a] $\frac{d^2 v_o}{dt^2} = \frac{1}{R_1 C_1 R_2 C_2} v_g$

$$\frac{1}{R_1 C_1 R_2 C_2} = \frac{10^{-6}}{(50)(20)(2)(4) \times 10^{-6} \times 10^{-6}} = 125$$

$$\therefore \frac{d^2 v_o}{dt^2} = 125 v_g$$

$$0 \leq t \leq 0.2^-:$$

$$v_g = 400 \text{ mV}$$

$$\frac{d^2 v_o}{dt^2} = 50$$

$$\text{Let } g(t) = \frac{dv_o}{dt}, \quad \text{then } \frac{dg}{dt} = 50 \quad \text{or} \quad dg = 50 dt$$

$$\int_{g(0)}^{g(t)} dx = 50 \int_0^t dy$$

$$g(t) - g(0) = 50t, \quad g(0) = \frac{dv_o}{dt}(0) = 0$$

$$g(t) = \frac{dv_o}{dt} = 50t$$

$$dv_o = 50t dt$$

$$\int_{v_o(0)}^{v_o(t)} dx = 50 \int_0^t x dx; \quad v_o(t) - v_o(0) = 25t^2, \quad v_o(0) = 0$$

$$v_o(t) = 25t^2 \text{ V}, \quad 0 \leq t \leq 0.2^-$$

$$\frac{dv_{o1}}{dt} = -\frac{1}{R_1 C_1} v_g = -10 v_g = -4$$

$$dv_{o1} = -4 dt$$

$$\int_{v_{o1}(0)}^{v_{o1}(t)} dx = -4 \int_0^t dy$$

$$v_{o1}(t) - v_{o1}(0) = -4t, \quad v_{o1}(0) = 0$$

$$v_{o1}(t) = -4t \text{ V}, \quad 0 \leq t \leq 0.2^-$$

$$0.2^+ \leq t \leq t_{\text{sat}}:$$

$$\frac{d^2 v_o}{dt^2} = -12.5, \quad \text{let } g(t) = \frac{dv_o}{dt}$$

$$\frac{dg(t)}{dt} = -12.5; \quad dg(t) = -12.5 dt$$

$$\int_{g(0.2^+)}^{g(t)} dx = -12.5 \int_{0.2}^t dy$$

$$g(t) - g(0.2^+) = -12.5(t - 0.2) = -12.5t + 2.5$$

$$g(0.2^+) = \frac{dv_o(0.2^+)}{dt}$$

$$C \frac{dv_o}{dt}(0.2^+) = \frac{0 - v_{o1}(0.2^+)}{20 \times 10^3}$$

$$v_{o1}(0.2^+) = v_o(0.2^-) = -4(0.2) = -0.80 \text{ V}$$

$$\therefore C \frac{dv_{o1}(0.2^+)}{dt} = \frac{0.80}{20 \times 10^3} = 40 \mu\text{A}$$

$$\frac{dv_{o1}}{dt}(0.2^+) = \frac{40 \times 10^{-6}}{4 \times 10^{-6}} = 10 \text{ V/s}$$

$$\therefore g(t) = -12.5t + 2.5 + 10 = -12.5t + 12.5 = \frac{dv_o}{dt}$$

$$\therefore dv_o = -12.5t dt + 12.5 dt$$

$$\int_{v_o(0.2^+)}^{v_o(t)} dx = \int_{0.2^+}^t -12.5y dy + \int_{0.2^+}^t 12.5 dy$$

$$v_o(t) - v_o(0.2^+) = -6.25y^2 \Big|_{0.2}^t + 12.5y \Big|_{0.2}^t$$

$$v_o(t) = v_o(0.2^+) - 6.25t^2 + 0.25 + 12.5t - 2.5$$

$$v_o(0.2^+) = v_o(0.2^-) = 1 \text{ V}$$

$$\therefore v_o(t) = -6.25t^2 + 12.5t - 1.25 \text{ V}, \quad 0.2^+ \leq t \leq t_{\text{sat}}$$

$$\frac{dv_{o1}}{dt} = -10(-0.1) = 1, \quad 0.2^+ \leq t \leq t_{\text{sat}}$$

$$dv_{o1} = dt; \quad \int_{v_{o1}(0.2^+)}^{v_{o1}(t)} dx = \int_{0.2^+}^t dy$$

$$v_{o1}(t) - v_{o1}(0.2^+) = t - 0.2; \quad v_{o1}(0.2^+) = v_{o1}(0.2^-) = -0.8 \text{ V}$$

$$\therefore v_{o1}(t) = t - 1 \text{ V}, \quad 0.2^+ \leq t \leq t_{\text{sat}}$$

Summary:

$$0 \leq t \leq 0.2^- \text{ s}: \quad v_{o1} = -4t \text{ V}, \quad v_o = 25t^2 \text{ V}$$

$$0.2^+ \text{ s} \leq t \leq t_{\text{sat}}: \quad v_{o1} = t - 1 \text{ V}, \quad v_o = -6.25t^2 + 12.5t - 1.25 \text{ V}$$

$$[\text{b}] -10 = -6.25t_{\text{sat}}^2 + 12.5t_{\text{sat}} - 1.25$$

$$\therefore 6.25t_{\text{sat}}^2 - 12.5t_{\text{sat}} - 8.75 = 0$$

$$t_{\text{sat}}^2 - 2t_{\text{sat}} - 1.4 = 0$$

$$t_{\text{sat}} = 1 \pm \sqrt{2 + 1.4} = 1 \pm 1.844$$

$$\therefore t_{\text{sat}} = 2.844 \text{ sec}$$

$$v_{o1}(t_{\text{sat}}) = 1.844 - 1 = 0.844 \text{ V}$$

$$P\ 8.59 \quad \tau_1 = (0.25 \times 10^6)(2 \times 10^{-6}) = 0.50\text{ s}$$

$$\frac{1}{\tau_1} = 2; \quad \tau_2 = (0.25 \times 10^6)(4 \times 10^{-6}) = 1\text{ s}; \quad \therefore \frac{1}{\tau_2} = 1$$

$$\therefore \frac{d^2 v_o}{dt^2} + 3 \frac{dv_o}{dt} + 2v_o = 50$$

$$s^2 + 3s + 2 = 0$$

$$(s+1)(s+2) = 0; \quad s_1 = -1, \quad s_2 = -2$$

$$v_o = V_f + A'_1 e^{-t} + A'_2 e^{-2t}; \quad V_f = \frac{50}{2} = 25\text{ V}$$

$$v_o = 25 + A'_1 e^{-t} + A'_2 e^{-2t}$$

$$v_o(0) = 0 = 25 + A'_1 + A'_2; \quad \frac{dv_o}{dt}(0) = 0 = -A'_1 - 2A'_2$$

$$\therefore A'_1 = -50, \quad A'_2 = 25\text{ V}$$


$$v_o(t) = 25 - 50e^{-t} + 25e^{-2t}\text{ V}, \quad 0 \leq t \leq 0.2\text{ s}$$

$$\frac{dv_{o1}}{dt} + 2v_{o1} = -4; \quad \therefore v_{o1} = -2 + 2e^{-2t}\text{ V}, \quad 0 \leq t \leq 0.2\text{ s}$$

$$v_o(0.2) = 25 - 50e^{-0.2} + 25e^{-0.4} = 0.8215\text{ V}$$

$$v_{o1}(0.2) = -2 + 2e^{-0.4} = -0.6594\text{ V}$$

At $t = 0.2\text{ s}$

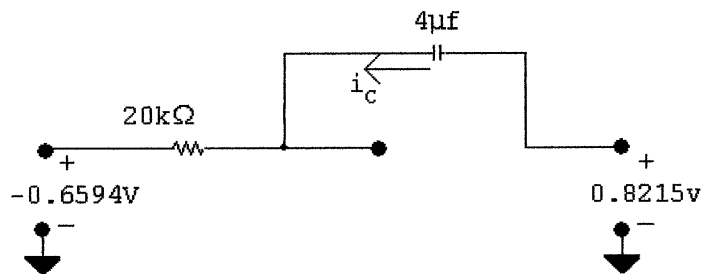

$$i_C = \frac{0 + 0.6594}{20 \times 10^3} = 32.97\ \mu\text{A}$$

$$C \frac{dv_o}{dt} = 32.97 \mu\text{A}; \quad \frac{dv_o}{dt} = \frac{32.97}{4} = 8.24 \text{ V/s}$$

$$0.2 \text{ s} \leq t < \infty:$$

$$\frac{d^2v_o}{dt^2} + 3 \frac{dv_o}{dt} + 2 = -12.5$$

$$v_o(\infty) = -6.25$$

$$\therefore v_o = -6.25 + A'_1 e^{-(t-0.2)} + A'_2 e^{-2(t-0.2)}$$

$$0.8215 = -6.25 + A'_1 + A'_2$$

$$\frac{dv_o}{dt}(0.2) = 8.24 = -A'_1 - 2A'_2$$

$$\therefore A'_1 + A'_2 = 7.07; \quad -A'_1 - 2A'_2 = 8.24$$


$$A'_1 = 22.38; \quad A'_2 = -15.31$$

$$\therefore v_o = -6.25 + 22.38e^{-(t-0.2)} - 15.31e^{-2(t-0.2)} \text{ V}, \quad 0.2 \leq t < \infty$$

$$\frac{dv_{o1}}{dt} + 2v_{o1} = 1$$

$$\therefore v_{o1} = 0.5 + (-0.6594 - 1)e^{-2(t-0.2)} = 0.5 - 1.66e^{-2(t-0.2)} \text{ V}, \quad 0.2 \leq t < \infty$$

P 8.60 [a]

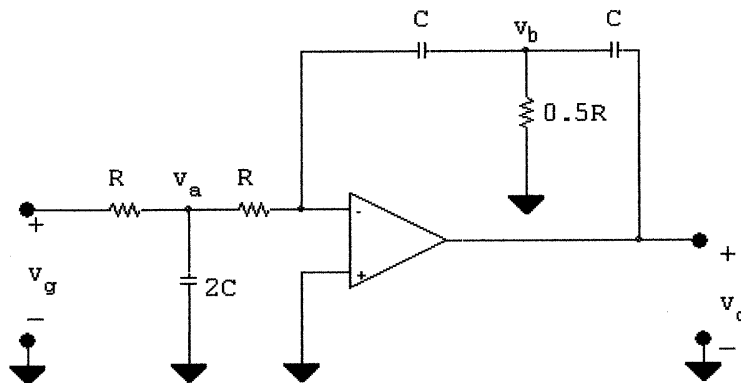

$$2C \frac{dv_a}{dt} + \frac{v_a - v_g}{R} + \frac{v_a}{R} = 0$$

$$(1) \text{ Therefore } \frac{dv_a}{dt} + \frac{v_a}{RC} = \frac{v_g}{2RC}; \quad \frac{0 - v_a}{R} + C \frac{d(0 - v_b)}{dt} = 0$$

(2) Therefore $\frac{dv_b}{dt} + \frac{v_a}{RC} = 0, \quad v_a = -RC \frac{dv_b}{dt}$

$$\frac{2v_b}{R} + C \frac{dv_b}{dt} + C \frac{d(v_b - v_o)}{dt} = 0$$

(3) Therefore $\frac{dv_b}{dt} + \frac{v_b}{RC} = \frac{1}{2} \frac{dv_o}{dt}$

From (2) we have $\frac{dv_a}{dt} = -RC \frac{d^2v_b}{dt^2}$ and $v_a = -RC \frac{dv_b}{dt}$

When these are substituted into (1) we get

(4) $-RC \frac{d^2v_b}{dt^2} - \frac{dv_b}{dt} = \frac{v_g}{2RC}$

Now differentiate (3) to get

(5) $\frac{d^2v_b}{dt^2} + \frac{1}{RC} \frac{dv_b}{dt} = \frac{1}{2} \frac{d^2v_o}{dt^2}$

But from (4) we have

(6) $\frac{d^2v_b}{dt^2} + \frac{1}{RC} \frac{dv_b}{dt} = -\frac{v_g}{2R^2C^2}$

Now substitute (6) into (5)

$$\frac{d^2v_o}{dt^2} = -\frac{v_g}{R^2C^2}$$

[b] When $R_1C_1 = R_2C_2 = RC : \quad \frac{d^2v_o}{dt^2} = \frac{v_g}{R^2C^2}$

The two equations are the same except for a reversal in algebraic sign.

[c] Two integrations of the input signal with one operational amplifier.

P 8.61 [a] $f(t) =$ inertial force + frictional force + spring force

$$= M[d^2x/dt^2] + D[dx/dt] + Kx$$

[b] $\frac{d^2x}{dt^2} = \frac{f}{M} - \left(\frac{D}{M}\right) \left(\frac{dx}{dt}\right) - \left(\frac{K}{M}\right) x$

Given $v_A = \frac{d^2x}{dt^2}$, then

$$v_B = -\frac{1}{R_1C_1} \int_0^t \left(\frac{d^2x}{dy^2}\right) dy = -\frac{1}{R_1C_1} \frac{dx}{dt}$$

$$v_C = -\frac{1}{R_2C_2} \int_0^t v_B dy = \frac{1}{R_1R_2C_1C_2} x$$

$$v_D = -\frac{R_3}{R_4} \cdot v_B = \frac{R_3}{R_4 R_1 C_1} \frac{dx}{dt}$$

$$v_E = \left[\frac{R_5 + R_6}{R_6} \right] v_C = \left[\frac{R_5 + R_6}{R_6} \right] \cdot \frac{1}{R_1 R_2 C_1 C_2} \cdot x$$

$$v_F = \left[\frac{-R_8}{R_7} \right] f(t), \quad v_A = -(v_D + v_E + v_F)$$

$$\text{Therefore } \frac{d^2 x}{dt^2} = \left[\frac{R_8}{R_7} \right] f(t) - \left[\frac{R_3}{R_4 R_1 C_1} \right] \frac{dx}{dt} - \left[\frac{R_5 + R_6}{R_6 R_1 R_2 C_1 C_2} \right] x$$

$$\text{Therefore } M = \frac{R_7}{R_8}, \quad D = \frac{R_3 R_7}{R_8 R_4 R_1 C_1} \quad \text{and} \quad K = \frac{R_7 (R_5 + R_6)}{R_8 R_6 R_1 R_2 C_1 C_2}$$

Box Number	Function
1	inverting and scaling
2	inverting and scaling
3	integrating and scaling
4	integrating and scaling
5	inverting and scaling
6	noninverting and scaling

P 8.62 [a] Given that the current response is underdamped we know i will be of the form

$$i = I_f + [B'_1 \cos \omega_d t + B'_2 \sin \omega_d t] e^{-\alpha t}$$

$$\text{where } \alpha = \frac{R}{2L}$$

$$\text{and } \omega_d = \sqrt{\omega_o^2 - \alpha^2} = \sqrt{\frac{1}{LC} - \alpha^2}$$

The capacitor will force the final value of i to be zero, therefore $I_f = 0$.

By hypothesis $i(0^+) = V_{dc}/R$ therefore $B'_1 = V_{dc}/R$.

At $t = 0^+$ the voltage across the primary winding is zero hence $di(0^+)/dt = 0$.

From our equation for i we have

$$\frac{di}{dt} = [(\omega_d B'_2 - \alpha B'_1) \cos \omega_d t - (\omega_d B'_1 + \alpha B'_2) \sin \omega_d t] e^{-\alpha t}$$

Hence

$$\frac{di(0^+)}{dt} = \omega_d B'_2 - \alpha B'_1 = 0$$

Thus

$$B'_2 = \frac{\alpha}{\omega_d} B'_1 = \frac{\alpha V_{dc}}{\omega_d R}$$

It follows directly that

$$i = \frac{V_{dc}}{R} \left[\cos \omega_d t + \frac{\alpha}{\omega_d} \sin \omega_d t \right] e^{-\alpha t}$$

[b] Since $\omega_d B'_1 - \alpha B'_2 = 0$ it follows that

$$\frac{di}{dt} = -(\omega_d B'_1 + \alpha B'_2) e^{-\alpha t} \sin \omega_d t$$

$$\text{But } \alpha B'_2 = \frac{\alpha^2 V_{dc}}{\omega_d R} \quad \text{and} \quad \omega_d B'_1 = \frac{\omega_d V_{dc}}{R}$$

Therefore

$$\omega_d B'_1 + \alpha B'_2 = \frac{\omega_d V_{dc}}{R} + \frac{\alpha^2 V_{dc}}{\omega_d R} = \frac{V_{dc}}{R} \left[\frac{\omega_d^2 + \alpha^2}{\omega_d} \right]$$

$$\text{But } \omega_d^2 + \alpha^2 = \omega_o^2 = \frac{1}{LC}$$

Hence

$$\omega_d B'_1 + \alpha B'_2 = \frac{V_{dc}}{\omega_d RLC}$$

Now since $v_1 = L \frac{di}{dt}$ we get

$$v_1 = -L \frac{V_{dc}}{\omega_d RLC} e^{-\alpha t} \sin \omega_d t = -\frac{V_{dc}}{\omega_d RC} e^{-\alpha t} \sin \omega_d t$$

[c] $v_c = V_{dc} - iR - L \frac{di}{dt}$

$$iR = V_{dc} \left(\cos \omega_d t + \frac{\alpha}{\omega_d} \sin \omega_d t \right) e^{-\alpha t}$$

$$v_c = V_{dc} - V_{dc} \left(\cos \omega_d t + \frac{\alpha}{\omega_d} \sin \omega_d t \right) e^{-\alpha t} + \frac{V_{dc}}{\omega_d RC} e^{-\alpha t} \sin \omega_d t$$

$$= V_{dc} - V_{dc} e^{-\alpha t} \cos \omega_d t + \left(\frac{V_{dc}}{\omega_d RC} - \frac{\alpha V_{dc}}{\omega_d} \right) e^{-\alpha t} \sin \omega_d t$$

$$= V_{dc} \left[1 - e^{-\alpha t} \cos \omega_d t + \frac{1}{\omega_d} \left(\frac{1}{RC} - \alpha \right) e^{-\alpha t} \sin \omega_d t \right]$$

$$= V_{dc} [1 - e^{-\alpha t} \cos \omega_d t + K e^{-\alpha t} \sin \omega_d t]$$

$$\text{P 8.63 } v_{sp} = V_{dc} \left[1 - \frac{a}{\omega_d RC} e^{-\alpha t} \sin \omega_d t \right]$$

$$\begin{aligned} \frac{dv_{sp}}{dt} &= \frac{-aV_{dc}}{\omega_d RC} \frac{d}{dt} [e^{-\alpha t} \sin \omega_d t] \\ &= \frac{-aV_{dc}}{\omega_d RC} [-\alpha e^{-\alpha t} \sin \omega_d t + \omega_d \cos \omega_d t e^{-\alpha t}] \\ &= \frac{aV_{dc} e^{-\alpha t}}{\omega_d RC} [\alpha \sin \omega_d t - \omega_d \cos \omega_d t] \end{aligned}$$

$$\frac{dv_{sp}}{dt} = 0 \quad \text{when} \quad \alpha \sin \omega_d t = \omega_d \cos \omega_d t$$

$$\text{or} \quad \tan \omega_d t = \frac{\omega_d}{\alpha}; \quad \omega_d t = \tan^{-1} \left(\frac{\omega_d}{\alpha} \right)$$

$$\therefore t_{\max} = \frac{1}{\omega_d} \tan^{-1} \left(\frac{\omega_d}{\alpha} \right)$$

Note that because $\tan \theta$ is periodic, i.e., $\tan \theta = \tan(\theta \pm n\pi)$, where n is an integer, there are an infinite number of solutions for t where $dv_{sp}/dt = 0$, that is

$$t = \frac{\tan^{-1}(\omega_d/\alpha) \pm n\pi}{\omega_d}$$

Because of $e^{-\alpha t}$ in the expression for v_{sp} and knowing $t \geq 0$ we know v_{sp} will be maximum when t has its smallest positive value. Hence

$$t_{\max} = \frac{\tan^{-1}(\omega_d/\alpha)}{\omega_d}.$$

$$\text{P 8.64 } [\mathbf{a}] v_c = V_{dc} [1 - e^{-\alpha t} \cos \omega_d t + K e^{-\alpha t} \sin \omega_d t]$$

$$\begin{aligned} \frac{dv_c}{dt} &= V_{dc} \frac{d}{dt} [1 + e^{-\alpha t} (K \sin \omega_d t - \cos \omega_d t)] \\ &= V_{dc} \{ (-\alpha e^{-\alpha t}) (K \sin \omega_d t - \cos \omega_d t) + \\ &\quad e^{-\alpha t} [\omega_d K \cos \omega_d t + \omega_d \sin \omega_d t] \} \\ &= V_{dc} e^{-\alpha t} [(\omega_d - \alpha K) \sin \omega_d t + (\alpha + \omega_d K) \cos \omega_d t] \end{aligned}$$

$$\frac{dv_c}{dt} = 0 \quad \text{when} \quad (\omega_d - \alpha K) \sin \omega_d t = -(\alpha + \omega_d K) \cos \omega_d t$$

$$\text{or } \tan \omega_d t = \left[\frac{\alpha + \omega_d K}{\alpha K - \omega_d} \right]$$

$$\therefore \omega_d t \pm n\pi = \tan^{-1} \left[\frac{\alpha + \omega_d K}{\alpha K - \omega_d} \right]$$

$$t_c = \frac{1}{\omega_d} \left\{ \tan^{-1} \left(\frac{\alpha + \omega_d K}{\alpha K - \omega_d} \right) \pm n\pi \right\}$$

$$\alpha = \frac{R}{2L} = \frac{4 \times 10^3}{6} = 666.67 \text{ rad/s}$$

$$\omega_d = \sqrt{\frac{10^9}{1.2} - (666.67)^2} = 28,859.81 \text{ rad/s}$$

$$K = \frac{1}{\omega_d} \left(\frac{1}{RC} - \alpha \right) = 21.63$$

$$t_c = \frac{1}{\omega_d} \left\{ \tan^{-1}(-43.29) + n\pi \right\} = \frac{1}{\omega_d} \{-1.55 + n\pi\}$$

The smallest positive value of t occurs when $n = 1$, therefore

$$t_{c \max} = 55.23 \mu\text{s}$$

$$\begin{aligned} \text{[b]} \quad v_c(t_{c \max}) &= 12[1 - e^{-\alpha t_{c \max}} \cos \omega_d t_{c \max} + K e^{-\alpha t_{c \max}} \sin \omega_d t_{c \max}] \\ &= 262.42 \text{ V} \end{aligned}$$

[c] From the text example the voltage across the spark plug reaches its maximum value in $53.63 \mu\text{s}$. If the spark plug does not fire the capacitor voltage peaks in $55.23 \mu\text{s}$. When v_{sp} is maximum the voltage across the capacitor is 262.15 V . If the spark plug does not fire the capacitor voltage reaches 262.42 V .

$$\text{P 8.65 [a]} \quad w = \frac{1}{2} L [i(0^+)]^2 = \frac{1}{2} (5)(16) \times 10^{-3} = 40 \text{ mJ}$$

$$\text{[b]} \quad \alpha = \frac{R}{2L} = \frac{3 \times 10^3}{10} = 300 \text{ rad/s}$$

$$\omega_d = \sqrt{\frac{10^9}{1.25} - (300)^2} = 28,282.68 \text{ rad/s}$$

$$\frac{1}{Rc} = \frac{10^6}{0.75} = \frac{4 \times 10^6}{3}$$

$$t_{\max} = \frac{1}{\omega_d} \tan^{-1} \left(\frac{\omega_d}{\alpha} \right) = 55.16 \mu\text{s}$$

$$v_{sp}(t_{\max}) = 12 - \frac{12(50)(4 \times 10^6)}{3(28,282.68)} e^{-\alpha t_{\max}} \sin \omega_d t_{\max} = -27,808.04 \text{ V}$$

$$[\mathbf{c}] \quad v_c(t_{\max}) = 12[1 - e^{-\alpha t_{\max}} \cos \omega_d t_{\max} + K e^{-\alpha t_{\max}} \sin \omega_d t_{\max}]$$

$$K = \frac{1}{\omega_d} \left[\frac{1}{RC} - \alpha \right] = 47.13$$

$$v_c(t_{\max}) = 568.15 \text{ V}$$