
Sinusoidal Steady State Analysis

Assessment Problems

AP 9.1 [a] $\mathbf{V} = 170/\underline{-40^\circ}$ V

[b] $10 \sin(1000t + 20^\circ) = 10 \cos(1000t - 70^\circ)$

$\therefore \mathbf{I} = 10/\underline{-70^\circ}$ A

[c] $\mathbf{I} = 5/\underline{36.87^\circ} + 10/\underline{-53.13^\circ}$

$= 4 + j3 + 6 - j8 = 10 - j5 = 11.18/\underline{-26.57^\circ}$ A

[d] $\sin(20,000\pi t + 30^\circ) = \cos(20,000\pi t - 60^\circ)$

Thus,

$\mathbf{V} = 300/\underline{45^\circ} - 100/\underline{-60^\circ} = 212.13 + j212.13 - (50 - j86.60)$

$= 162.13 + j298.73 = 339.90/\underline{61.51^\circ}$ mV

AP 9.2 [a] $v = 18.6 \cos(\omega t - 54^\circ)$ V

[b] $\mathbf{I} = 20/\underline{45^\circ} - 50/\underline{-30^\circ} = 14.14 + j14.14 - 43.3 + j25$

$= -29.16 + j39.14 = 48.81/\underline{126.68^\circ}$

Therefore $i = 48.81 \cos(\omega t + 126.68^\circ)$ mA

[c] $\mathbf{V} = 20 + j80 - 30/\underline{15^\circ} = 20 + j80 - 28.98 - j7.76$

$= -8.98 + j72.24 = 72.79/\underline{97.08^\circ}$

$v = 72.79 \cos(\omega t + 97.08^\circ)$ V

AP 9.3 [a] $\omega L = (10^4)(20 \times 10^{-3}) = 200 \Omega$

[b] $Z_L = j\omega L = j200 \Omega$

[c] $\mathbf{V}_L = \mathbf{I}Z_L = (10/\underline{30^\circ})(200/\underline{90^\circ}) \times 10^{-3} = 2/\underline{120^\circ} \text{ V}$

[d] $v_L = 2 \cos(10,000t + 120^\circ) \text{ V}$

AP 9.4 [a] $X_C = \frac{-1}{\omega C} = \frac{-1}{4000(5 \times 10^{-6})} = -50 \Omega$

[b] $Z_C = jX_C = -j50 \Omega$

[c] $\mathbf{I} = \frac{\mathbf{V}}{Z_C} = \frac{30/\underline{25^\circ}}{50/\underline{-90^\circ}} = 0.6/\underline{115^\circ} \text{ A}$

[d] $i = 0.6 \cos(4000t + 115^\circ) \text{ A}$

AP 9.5 $\mathbf{I}_1 = 100/\underline{25^\circ} = 90.63 + j42.26$

$\mathbf{I}_2 = 100/\underline{145^\circ} = -81.92 + j57.36$

$\mathbf{I}_3 = 100/\underline{-95^\circ} = -8.72 - j99.62$

$\mathbf{I}_4 = -(\mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3) = (0 + j0) \text{ A}, \quad \text{therefore } i_4 = 0 \text{ A}$

AP 9.6 [a] $\mathbf{I} = \frac{125/\underline{-60^\circ}}{|Z|/\underline{\theta_z}} = \frac{125}{|Z|}/\underline{(-60 - \theta_z)^\circ}$

But $-60 - \theta_z = -105^\circ \quad \therefore \theta_z = 45^\circ$


$Z = 90 + j160 + jX_C$

$\therefore X_C = -70 \Omega; \quad X_C = -\frac{1}{\omega C} = -70$

$\therefore C = \frac{1}{(70)(5000)} = 2.86 \mu\text{F}$

[b] $\mathbf{I} = \frac{\mathbf{V}_s}{Z} = \frac{125/\underline{-60^\circ}}{(90 + j90)} = 0.982/\underline{-105^\circ} \text{ A}; \quad \therefore |\mathbf{I}| = 0.982 \text{ A}$

AP 9.7 [a]

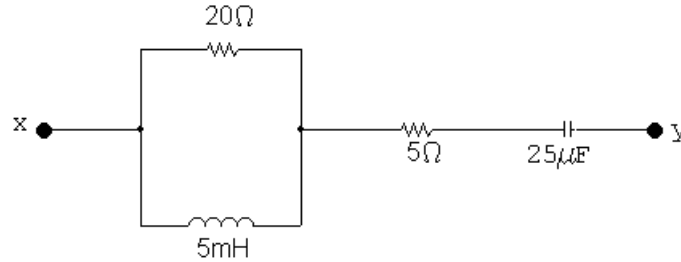

$$\omega = 2000 \text{ rad/s}$$

$$\omega L = 10 \Omega, \quad \frac{-1}{\omega C} = -20 \Omega$$

$$\begin{aligned} Z_{xy} &= 20 \parallel j10 + 5 + j20 = \frac{20(j10)}{(20 + j10)} + 5 - j20 \\ &= 4 + j8 + 5 - j20 = (9 - j12) \Omega \end{aligned}$$

$$\text{[b]} \quad \omega L = 40 \Omega, \quad \frac{-1}{\omega C} = -5 \Omega$$

$$\begin{aligned} Z_{xy} &= 5 - j5 + 20 \parallel j40 = 5 - j5 + \left[\frac{(20)(j40)}{20 + j40} \right] \\ &= 5 - j5 + 16 + j8 = (21 + j3) \Omega \end{aligned}$$

$$\begin{aligned} \text{[c]} \quad Z_{xy} &= \left[\frac{20(j\omega L)}{20 + j\omega L} \right] + \left(5 - \frac{j10^6}{25\omega} \right) \\ &= \frac{20\omega^2 L^2}{400 + \omega^2 L^2} + \frac{j400\omega L}{400 + \omega^2 L^2} + 5 - \frac{j10^6}{25\omega} \end{aligned}$$

The impedance will be purely resistive when the j terms cancel, i.e.,

$$\frac{400\omega L}{400 + \omega^2 L^2} = \frac{10^6}{25\omega}$$

Solving for ω yields $\omega = 4000 \text{ rad/s}$.

$$\text{[d]} \quad Z_{xy} = \frac{20\omega^2 L^2}{400 + \omega^2 L^2} + 5 = 10 + 5 = 15 \Omega$$

AP 9.8 The frequency 4000 rad/s was found to give $Z_{xy} = 15 \Omega$ in Assessment Problem 9.7. Thus,


$$\mathbf{V} = 150 \angle 0^\circ, \quad \mathbf{I}_s = \frac{\mathbf{V}}{Z_{xy}} = \frac{150 \angle 0^\circ}{15} = 10 \angle 0^\circ \text{ A}$$

Using current division,

$$\mathbf{I}_L = \frac{20}{20 + j20} (10) = 5 - j5 = 7.07 \angle -45^\circ \text{ A}$$

$$i_L = 7.07 \cos(4000t - 45^\circ) \text{ A}, \quad I_m = 7.07 \text{ A}$$

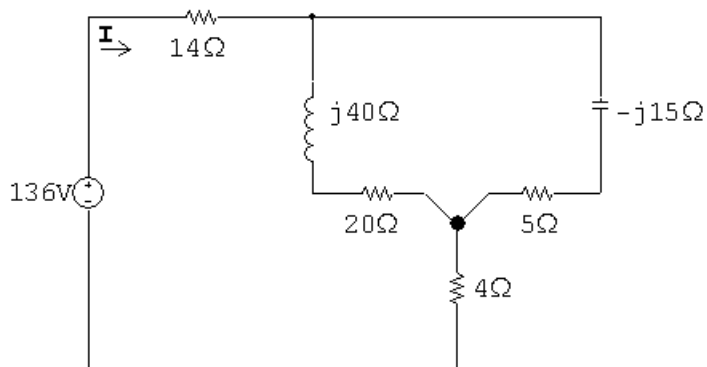AP 9.9 After replacing the delta made up of the $50\ \Omega$, $40\ \Omega$, and $10\ \Omega$ resistors with its equivalent wye, the circuit becomes



The circuit is further simplified by combining the parallel branches,

$$(20 + j40) \parallel (5 - j15) = (12 - j16)\ \Omega$$

$$\text{Therefore } \mathbf{I} = \frac{136/0^\circ}{14 + 12 - j16 + 4} = 4/28.07^\circ\ \text{A}$$

AP 9.10 $\mathbf{V}_1 = 240/53.13^\circ = 144 + j192\ \text{V}$

$$\mathbf{V}_2 = 96/-90^\circ = -j96\ \text{V}$$


$$j\omega L = j(4000)(15 \times 10^{-3}) = j60\ \Omega$$

$$\frac{1}{j\omega C} = -j \frac{6 \times 10^6}{(4000)(25)} = -j60\ \Omega$$

Perform source transformations:

$$\frac{\mathbf{V}_1}{j60} = \frac{144 + j192}{j60} = 3.2 - j2.4\ \text{A}$$

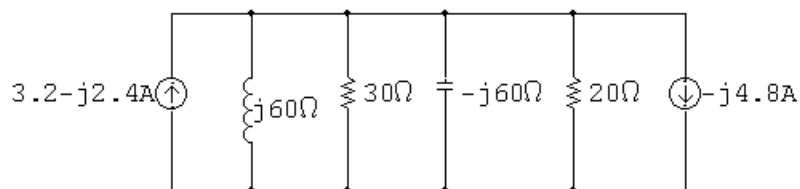
$$\frac{\mathbf{V}_2}{20} = -j \frac{96}{20} = -j4.8\ \text{A}$$



Combine the parallel impedances:

$$Y = \frac{1}{j60} + \frac{1}{30} + \frac{1}{-j60} + \frac{1}{20} = \frac{j5}{j60} = \frac{1}{12}$$

$$Z = \frac{1}{Y} = 12 \Omega$$

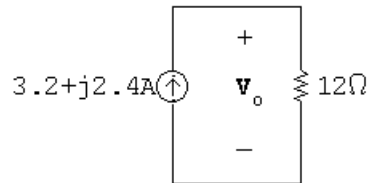

$$\mathbf{V}_o = 12(3.2 + j2.4) = 38.4 + j28.8 \text{ V} = 48 \angle 36.87^\circ \text{ V}$$

$$v_o = 48 \cos(4000t + 36.87^\circ) \text{ V}$$


AP 9.11 Use the lower node as the reference node. Let \mathbf{V}_1 = node voltage across the 20Ω resistor and \mathbf{V}_{Th} = node voltage across the capacitor. Writing the node voltage equations gives us

$$\frac{\mathbf{V}_1}{20} - 2 \angle 45^\circ + \frac{\mathbf{V}_1 - 10\mathbf{I}_x}{j10} = 0 \quad \text{and} \quad \mathbf{V}_{\text{Th}} = \frac{-j10}{10 - j10}(10\mathbf{I}_x)$$

We also have

$$\mathbf{I}_x = \frac{\mathbf{V}_1}{20}$$

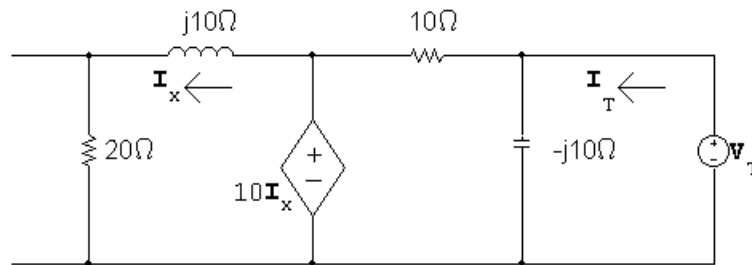Solving these equations for \mathbf{V}_{Th} gives $\mathbf{V}_{\text{Th}} = 10 \angle 45^\circ \text{ V}$. To find the Thévenin impedance, we remove the independent current source and apply a test voltage source at the terminals a, b. Thus



It follows from the circuit that


$$10\mathbf{I}_x = (20 + j10)\mathbf{I}_x$$

Therefore

$$\mathbf{I}_x = 0 \quad \text{and} \quad \mathbf{I}_T = \frac{\mathbf{V}_T}{-j10} + \frac{\mathbf{V}_T}{10}$$

$$Z_{\text{Th}} = \frac{\mathbf{V}_T}{\mathbf{I}_T}, \quad \text{therefore} \quad Z_{\text{Th}} = (5 - j5) \Omega$$

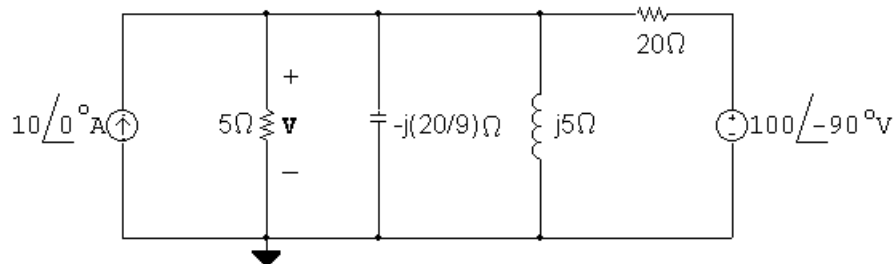AP 9.12 The phasor domain circuit is as shown in the following diagram:



The node voltage equation is

$$-10 + \frac{\mathbf{V}}{5} + \frac{\mathbf{V}}{-j(20/9)} + \frac{\mathbf{V}}{j5} + \frac{\mathbf{V} - 100\angle-90^\circ}{20} = 0$$

$$\text{Therefore} \quad \mathbf{V} = 10 - j30 = 31.62\angle-71.57^\circ$$

$$\text{Therefore} \quad v = 31.62 \cos(50,000t - 71.57^\circ) \text{ V}$$

AP 9.13 Let \mathbf{I}_a , \mathbf{I}_b , and \mathbf{I}_c be the three clockwise mesh currents going from left to right. Summing the voltages around meshes a and b gives

$$33.8 = (1 + j2)\mathbf{I}_a + (3 - j5)(\mathbf{I}_a - \mathbf{I}_b)$$

and

$$0 = (3 - j5)(\mathbf{I}_b - \mathbf{I}_a) + 2(\mathbf{I}_b - \mathbf{I}_c).$$

But

$$\mathbf{V}_x = -j5(\mathbf{I}_a - \mathbf{I}_b),$$

therefore

$$\mathbf{I}_c = -0.75[-j5(\mathbf{I}_a - \mathbf{I}_b)].$$

$$\text{Solving for } \mathbf{I} = \mathbf{I}_a = 29 + j2 = 29.07\angle3.95^\circ \text{ A.}$$

AP 9.14 [a] $M = 0.4\sqrt{0.0625} = 0.1 \text{ H}, \quad \omega M = 80 \Omega$

$$Z_{22} = 40 + j800(0.125) + 360 + j800(0.25) = (400 + j300) \Omega$$

Therefore $|Z_{22}| = 500 \Omega, \quad Z_{22}^* = (400 - j300) \Omega$

$$Z_r = \left(\frac{80}{500}\right)^2 (400 - j300) = (10.24 - j7.68) \Omega$$

[b] $\mathbf{I}_1 = \frac{245.20}{184 + 100 + j400 + Z_r} = 0.50 \angle -53.13^\circ \text{ A}$

$$i_1 = 0.5 \cos(800t - 53.13^\circ) \text{ A}$$

[c] $\mathbf{I}_2 = \left(\frac{j\omega M}{Z_{22}}\right) \mathbf{I}_1 = \frac{j80}{500 \angle 36.87^\circ} (0.5 \angle -53.13^\circ) = 0.08 \angle 0^\circ \text{ A}$

$$i_2 = 80 \cos 800t \text{ mA}$$

AP 9.15 $\mathbf{I}_1 = \frac{\mathbf{V}_s}{Z_1 + Z_2/a^2} = \frac{25 \times 10^3 \angle 0^\circ}{1500 + j6000 + (25)^2(4 - j14.4)}$

$$= 4 + j3 = 5 \angle 36.87^\circ \text{ A}$$

$$\mathbf{V}_1 = \mathbf{V}_s - Z_1 \mathbf{I}_1 = 25,000 \angle 0^\circ - (4 + j3)(1500 + j6000)$$

$$= 37,000 - j28,500$$

$$\mathbf{V}_2 = -\frac{1}{25} \mathbf{V}_1 = -1480 + j1140 = 1868.15 \angle 142.39^\circ \text{ V}$$

$$\mathbf{I}_2 = \frac{\mathbf{V}_2}{Z_2} = \frac{1868.15 \angle 142.39^\circ}{4 - j14.4} = 125 \angle -143.13^\circ \text{ A}$$

Also, $I_2 = -25I_1$

Problems

P 9.12 [a] 1000Hz

[b] $\theta_v = 0^\circ$

[c] $\mathbf{I} = \frac{200/0^\circ}{j\omega L} = \frac{200}{\omega L} \angle -90^\circ = 25 \angle -90^\circ; \quad \theta_i = -90^\circ$

[d] $\frac{200}{\omega L} = 25; \quad \omega L = \frac{200}{25} = 8 \Omega$

[e] $L = \frac{8}{2\pi(1000)} = 1.27 \text{ mH}$

[f] $Z_L = j\omega L = j8 \Omega$

P 9.13 [a] $\omega = 2\pi f = 314,159.27 \text{ rad/s}$

[b] $\mathbf{I} = \frac{\mathbf{V}}{Z_C} = \frac{10 \times 10^{-3} / 0^\circ}{1/j\omega C} = j\omega C (10 \times 10^{-3}) / 0^\circ = 10 \times 10^{-3} \omega C / 90^\circ$

$\therefore \theta_i = 90^\circ$

[c] $628.32 \times 10^{-6} = 10 \times 10^{-3} \omega C$

$\frac{1}{\omega C} = \frac{10 \times 10^{-3}}{628.32 \times 10^{-6}} = 15.92 \Omega, \quad \therefore X_C = -15.92 \Omega$


[d] $C = \frac{1}{15.92(\omega)} = \frac{1}{(15.92)(100\pi \times 10^3)}$

$C = 0.2 \mu\text{F}$

[e] $Z_c = j \left(\frac{-1}{\omega C} \right) = -j15.92 \Omega$

P 9.14 [a] $j\omega L = j(2 \times 10^4)(300 \times 10^{-6}) = j6 \Omega$

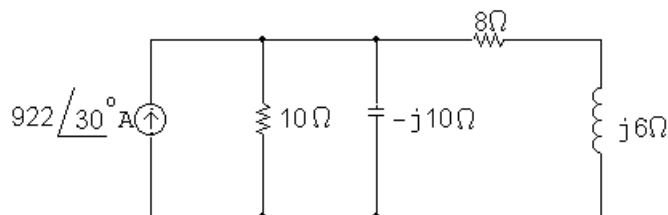$\frac{1}{j\omega C} = -j \frac{1}{(2 \times 10^4)(5 \times 10^{-6})} = -j10 \Omega; \quad \mathbf{I}_g = 922 \angle 30^\circ \text{ A}$



$$\text{[b]} \mathbf{V}_o = 922/30^\circ Z_e$$

$$Z_e = \frac{1}{Y_e}; \quad Y_e = \frac{1}{10} + j\frac{1}{10} + \frac{1}{8 + j6}$$

$$Y_e = 0.18 + j0.04 \text{ S}$$


$$Z_e = \frac{1}{0.18 + j0.04} = 5.42/-12.53^\circ \Omega$$

$$\mathbf{V}_o = (922/30^\circ)(5.42/-12.53^\circ) = 5000.25/17.47^\circ \text{ V}$$

$$\text{[c]} v_o = 5000.25 \cos(2 \times 10^4 t + 17.47^\circ) \text{ V}$$

$$\text{P 9.15 [a]} Z_L = j(8000)(5 \times 10^{-3}) = j40 \Omega$$
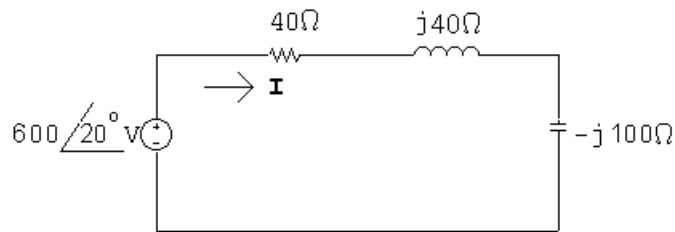
$$Z_C = \frac{-j}{(8000)(1.25 \times 10^{-6})} = -j100 \Omega$$



$$\text{[b]} \mathbf{I} = \frac{600/20^\circ}{40 + j40 - j100} = 8.32/76.31^\circ \text{ A}$$

$$\text{[c]} i = 8.32 \cos(8000t + 76.31^\circ) \text{ A}$$

$$\text{P 9.16} \quad Z = 4 + j(50)(0.24) - j\frac{1}{(50)(0.0025)} = 4 + j4 = 5.66/45^\circ \Omega$$

$$\mathbf{I}_o = \frac{\mathbf{V}}{Z} = \frac{0.1/-90^\circ}{5.66/45^\circ} = 17.68/-135^\circ \text{ mA}$$

$$i_o(t) = 17.68 \cos(50t - 135^\circ) \text{ mA}$$

$$\begin{aligned}
 \text{P 9.17 [a]} \quad Y &= \frac{1}{3 + j4} + \frac{1}{16 - j12} + \frac{1}{-j4} \\
 &= 0.12 - j0.16 + 0.04 + j0.03 + j0.25 \\
 &= 0.16 + j0.12 = 200/\underline{36.87^\circ} \text{ mS}
 \end{aligned}$$

$$\text{[b]} \quad G = 160 \text{ mS}$$

$$\text{[c]} \quad B = 120 \text{ mS}$$

$$\text{[d]} \quad \mathbf{I} = 8/\underline{0^\circ} \text{ A}, \quad \mathbf{V} = \frac{\mathbf{I}}{Y} = \frac{8}{0.2/\underline{36.87^\circ}} = 40/\underline{-36.87^\circ} \text{ V}$$


$$\mathbf{I}_C = \frac{\mathbf{V}}{Z_C} = \frac{40/\underline{-36.87^\circ}}{4/\underline{-90^\circ}} = 10/\underline{53.13^\circ} \text{ A}$$

$$i_C = 10 \cos(\omega t + 53.13^\circ) \text{ A}, \quad I_m = 10 \text{ A}$$

$$\text{P 9.18} \quad Z_L = j(2000)(60 \times 10^{-3}) = j120 \Omega$$

$$Z_C = \frac{-j}{(2000)(12.5 \times 10^{-6})} = -j40 \Omega$$

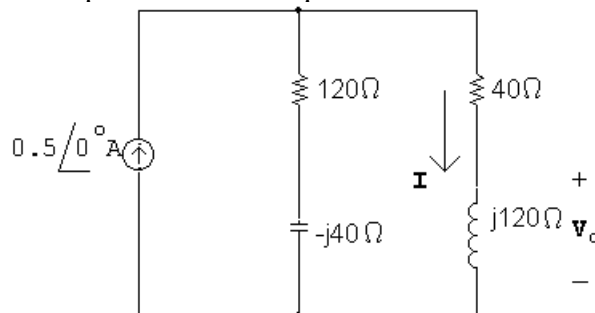Construct the phasor domain equivalent circuit:



Using current division:

$$\mathbf{I} = \frac{(120 - j40)}{120 - j40 + 40 + j120}(0.5) = 0.25 - j0.25 \text{ A}$$

$$\mathbf{V}_o = j120\mathbf{I} = 30 + j30 = 42.43/\underline{45^\circ} \text{ V}$$

$$v_o = 42.43 \cos(2000t + 45^\circ) \text{ V}$$

P 9.19 [a] $\mathbf{V}_g = 300\angle 78^\circ$; $\mathbf{I}_g = 6\angle 33^\circ$

$$\therefore Z = \frac{\mathbf{V}_g}{\mathbf{I}_g} = \frac{300\angle 78^\circ}{6\angle 33^\circ} = 50\angle 45^\circ \Omega$$

[b] i_g lags v_g by 45° :


$$2\pi f = 5000\pi; \quad f = 2500 \text{ Hz}; \quad T = 1/f = 400 \mu\text{s}$$

$$\therefore i_g \text{ lags } v_g \text{ by } \frac{45^\circ}{360^\circ}(400 \mu\text{s}) = 50 \mu\text{s}$$

P 9.20 $\frac{1}{j\omega C} = \frac{1}{(1 \times 10^{-6})(50 \times 10^3)} = -j20 \Omega$

$$j\omega L = j50 \times 10^3(1.2 \times 10^{-3}) = j60 \Omega$$
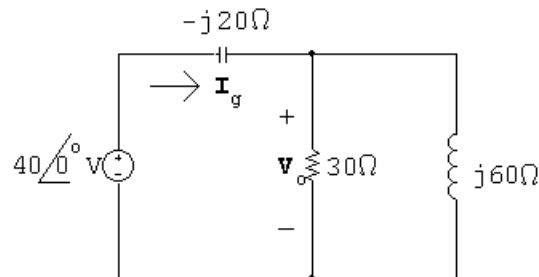
$$\mathbf{V}_g = 40\angle 0^\circ \text{ V}$$



$$Z_e = -j20 + 30\|j60 = 24 - j8 \Omega$$

$$\mathbf{I}_g = \frac{40\angle 0^\circ}{24 - j8} = 1.5 + j0.5 \text{ mA}$$


$$\mathbf{V}_o = (30\|j60)\mathbf{I}_g = \frac{30(j60)}{30 + j60}(1.5 + j0.5) = 30 + j30 = 42.43\angle 45^\circ \text{ V}$$

$$v_o = 42.43 \cos(50,000t + 45^\circ) \text{ V}$$

P 9.35 Simplify the top triangle using series and parallel combinations:

$$(1 + j1) \parallel (1 - j1) = 1 \Omega$$

Convert the lower left delta to a wye:

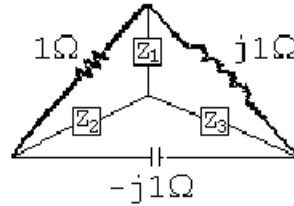


$$Z_1 = \frac{(j1)(1)}{1 + j1 - j1} = j1 \Omega$$

$$Z_2 = \frac{(-j1)(1)}{1 + j1 - j1} = -j1 \Omega$$

$$Z_3 = \frac{(j1)(-j1)}{1 + j1 - j1} = 1 \Omega$$

Convert the lower right delta to a wye:

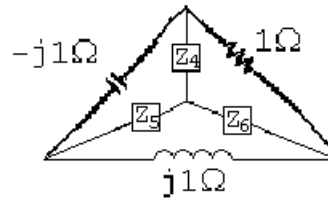


$$Z_4 = \frac{(-j1)(1)}{1 + j1 - j1} = -j1 \Omega$$

$$Z_5 = \frac{(-j1)(j1)}{1 + j1 - j1} = 1 \Omega$$

$$Z_6 = \frac{(j1)(1)}{1 + j1 - j1} = j1 \Omega$$

The resulting circuit is shown below:

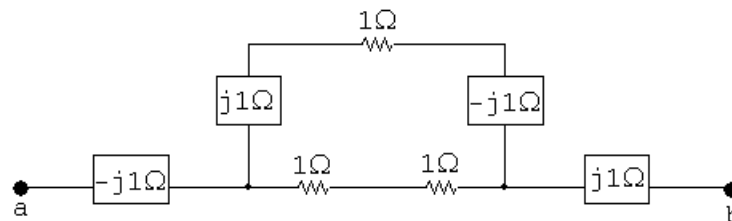

Simplify the middle portion of the circuit by making series and parallel combinations:

$$(1 + j1 - j1) \parallel (1 + 1) = 1 \parallel 2 = 2/3 \Omega$$


$$Z_{ab} = -j1 + 2/3 + j1 = 2/3 \Omega$$

P 9.39 $\mathbf{I}_s = 3\angle 0^\circ \text{ mA}$

$$\frac{1}{j\omega C} = -j0.4 \Omega$$

$$j\omega L = j0.4 \Omega$$

After source transformation we have

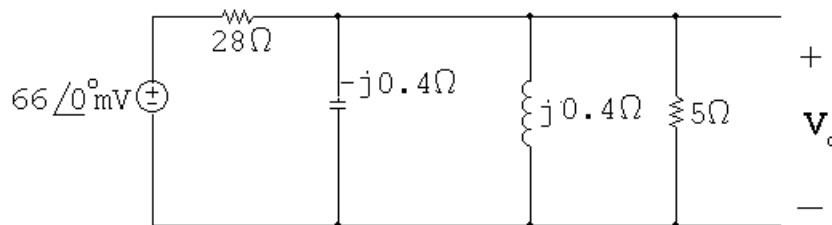

$$\mathbf{V}_o = \frac{-j0.4 \parallel j0.4 \parallel 5}{28 + -j0.4 \parallel j0.4 \parallel 5} (66 \times 10^{-3}) = 10 \text{ mV}$$

$$v_o = 10 \cos 200t \text{ mV}$$


P 9.42 Using voltage division:

$$\mathbf{V}_{Th} = \frac{36}{36 + j60 - j48} (240) = 216 - j72 = 227.68 \angle -18.43^\circ \text{ V}$$

Remove the source and combine impedances in series and in parallel:

$$Z_{Th} = 36 \parallel (j60 - j48) = 3.6 + j10.8 \Omega$$

P 9.43 Open circuit voltage:

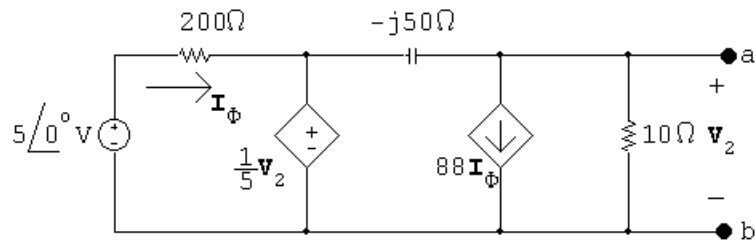


$$\frac{V_2}{10} + 88I_\phi + \frac{V_2 - \frac{1}{5}V_2}{-j50} = 0$$

$$I_\phi = \frac{5 - (V_2/5)}{200}$$

Solving,

$$V_2 = -66 + j88 = 110/\underline{126.87^\circ} \text{ V} = V_{Th}$$

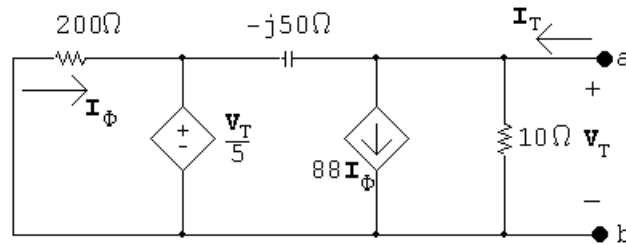Find the Thévenin equivalent impedance using a test source:



$$I_T = \frac{V_T}{10} + 88I_\phi + \frac{0.8V_T}{-j50}$$


$$I_\phi = \frac{-V_T/5}{200}$$

$$I_T = V_T \left(\frac{1}{10} - 88 \frac{1/5}{200} + \frac{0.8}{-j50} \right)$$


$$\therefore \frac{V_T}{I_T} = 30 - j40 = Z_{Th}$$

$$I_N = \frac{V_{Th}}{Z_{Th}} = \frac{-66 + j88}{30 - j40} = -2.2 + j0 \text{ A} = 2.2/\underline{180^\circ} \text{ A}$$

The Norton equivalent circuit:

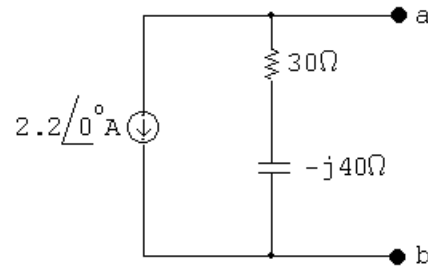

P 9.51

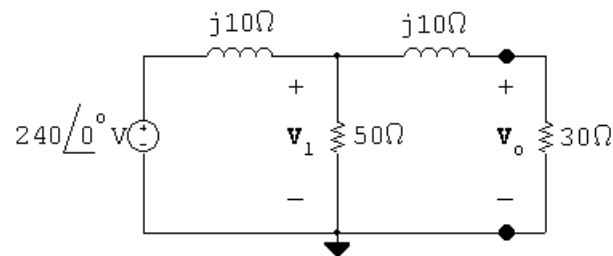


$$\frac{V_1 - 240}{j10} + \frac{V_1}{50} + \frac{V_1}{30 + j10} = 0$$

Solving for V_1 yields

$$V_1 = 198.63\angle -24.44^\circ \text{ V}$$

$$V_o = \frac{30}{30 + j10}(V_1) = 188.43\angle -42.88^\circ \text{ V}$$

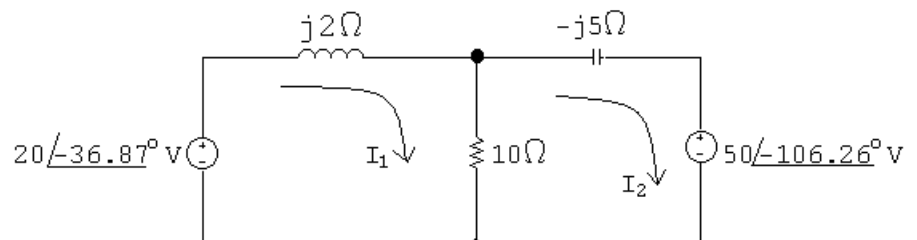P 9.54 The circuit with the mesh currents identified is shown below:



The mesh current equations are:

$$-20/\underline{-36.87^\circ} + j2\mathbf{I}_1 + 10(\mathbf{I}_1 - \mathbf{I}_2) = 0$$

$$50/\underline{-106.26^\circ} + 10(\mathbf{I}_2 - \mathbf{I}_1) - j5\mathbf{I}_2 = 0$$

In standard form:

$$\mathbf{I}_1(10 + j2) + \mathbf{I}_2(-10) = 20/\underline{-36.87^\circ}$$

$$\mathbf{I}_1(-10) + \mathbf{I}_2(10 - j5) = -50/\underline{-106.26^\circ} = 50/\underline{73.74^\circ}$$

Solving on a calculator yields:

$$\mathbf{I}_1 = -6 + j10\text{A}; \quad \mathbf{I}_2 = -9.6 + j10\text{A}$$

Thus,

$$\mathbf{V}_o = 10(\mathbf{I}_1 - \mathbf{I}_2) = 36\text{V}$$

and

$$v_o(t) = 36 \cos 2000t\text{V}$$

P 9.56 Write a KCL equation at the top node:

$$\frac{\mathbf{V}_o}{-j8} + \frac{\mathbf{V}_o - 2.4\mathbf{I}_\Delta}{j4} + \frac{\mathbf{V}_o}{5} - (10 + j10) = 0$$


The constraint equation is:

$$\mathbf{I}_\Delta = \frac{\mathbf{V}_o}{-j8}$$

Solving,

$$\mathbf{V}_o = j80 = 80/\underline{90^\circ}\text{V}$$

P 9.59

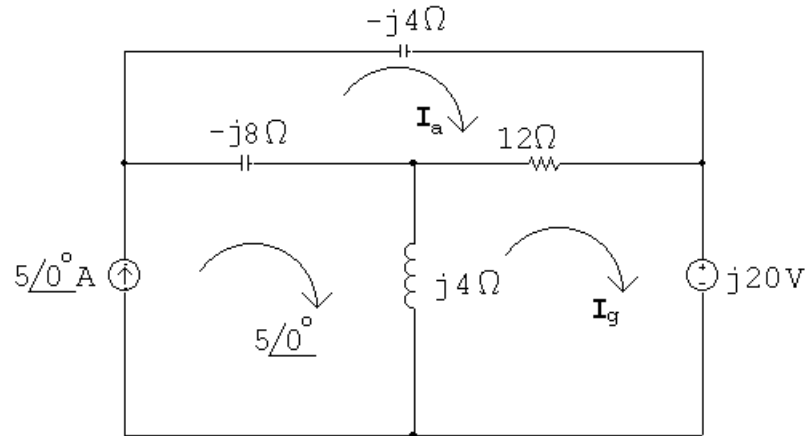

$$(12 - j12)\mathbf{I}_a - 12\mathbf{I}_g - 5(-j8) = 0$$

$$-12\mathbf{I}_a + (12 + j4)\mathbf{I}_g + j20 - 5(j4) = 0$$


Solving,

$$\mathbf{I}_g = 4 - j2 = 4.47/\underline{-26.57^\circ} \text{ A}$$

 P 9.66 [a] $j\omega L_1 = j(5000)(2 \times 10^{-3}) = j10 \Omega$

$$j\omega L_2 = j(5000)(8 \times 10^{-3}) = j40 \Omega$$

$$j\omega M = j10 \Omega$$

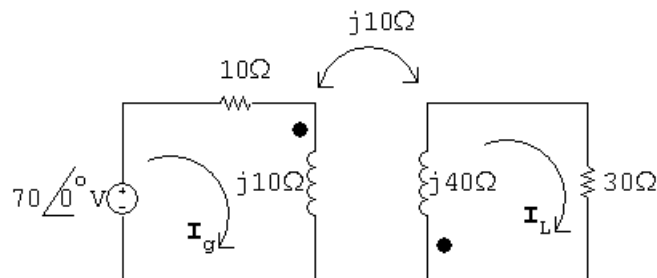

$$70 = (10 + j10)\mathbf{I}_g + j10\mathbf{I}_L$$

$$0 = j10\mathbf{I}_g + (30 + j40)\mathbf{I}_L$$

Solving,

$$\mathbf{I}_g = 4 - j3 \text{ A}; \quad \mathbf{I}_L = -1 \text{ A}$$

$$i_g = 5 \cos(5000t - 36.87^\circ) \text{ A}$$

$$i_L = 1 \cos(5000t - 180^\circ) \text{ A}$$

$$\text{[b]} \quad k = \frac{M}{\sqrt{L_1 L_2}} = \frac{2}{\sqrt{16}} = 0.5$$

[c] When $t = 100\pi \mu\text{s}$,

$$5000t = (5000)(100\pi) \times 10^{-6} = 0.5\pi = \pi/2 \text{ rad} = 90^\circ$$

$$i_g(100\pi \mu\text{s}) = 5 \cos(53.13^\circ) = 3 \text{ A}$$

$$i_L(100\pi \mu\text{s}) = 1 \cos(-90^\circ) = 0 \text{ A}$$

$$w = \frac{1}{2}L_1 i_1^2 + \frac{1}{2}L_2 i_2^2 + M i_1 i_2 = \frac{1}{2}(2 \times 10^{-3})(9) + 0 + 0 = 9 \text{ mJ}$$

When $t = 200\pi \mu\text{s}$,

$$5000t = \pi \text{ rad} = 180^\circ$$

$$i_g(200\pi \mu\text{s}) = 5 \cos(180^\circ - 36.87^\circ) = -4 \text{ A}$$

$$i_L(200\pi \mu\text{s}) = 1 \cos(180^\circ - 180^\circ) = 1 \text{ A}$$


$$w = \frac{1}{2}(2 \times 10^{-3})(16) + \frac{1}{2}(8 \times 10^{-3})(1) + 2 \times 10^{-3}(-4)(1) = 12 \text{ mJ}$$

P 9.67 Remove the voltage source to find the equivalent impedance:


$$Z_{\text{Th}} = 45 + j125 + \left(\frac{20}{|5 + j5|} \right)^2 (5 - j5) = 85 + j85 \Omega$$

Using voltage division:
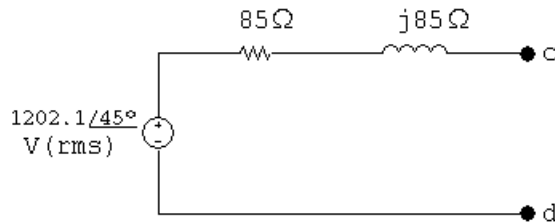
$$\mathbf{V}_{\text{Th}} = \mathbf{V}_{\text{cd}} = j20\mathbf{I}_1 = j20 \left(\frac{425}{5 + j5} \right) = 850 + j850 \text{ V} = 1202.1 \angle 45^\circ \text{ V}$$



P 9.71

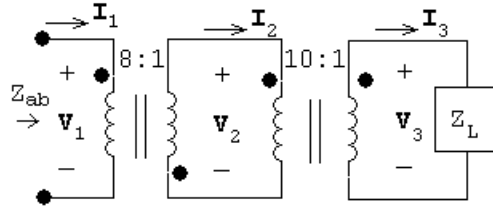

$$Z_L = \frac{\mathbf{V}_3}{\mathbf{I}_3} = 80\angle 60^\circ \Omega$$

$$\frac{\mathbf{V}_2}{10} = \frac{\mathbf{V}_3}{1}; \quad 10\mathbf{I}_2 = 1\mathbf{I}_3$$

$$\frac{\mathbf{V}_1}{8} = -\frac{\mathbf{V}_2}{1}; \quad 8\mathbf{I}_1 = -1\mathbf{I}_2$$

$$Z_{ab} = \frac{\mathbf{V}_1}{\mathbf{I}_1}$$

Substituting,

$$\begin{aligned} Z_{ab} &= \frac{\mathbf{V}_1}{\mathbf{I}_1} = \frac{-8\mathbf{V}_2}{-\mathbf{I}_2/8} = \frac{8^2\mathbf{V}_2}{\mathbf{I}_2} \\ &= \frac{8^2(10\mathbf{V}_3)}{\mathbf{I}_3/10} = \frac{(8)^2(10)^2\mathbf{V}_3}{\mathbf{I}_3} = (8)^2(10)^2 Z_L = 512,000\angle 60^\circ \Omega \end{aligned}$$