

---

# Sinusoidal Steady State Analysis

---

## Assessment Problems

AP 9.1 [a]  $\mathbf{V} = 170/\underline{-40^\circ}$  V

[b]  $10 \sin(1000t + 20^\circ) = 10 \cos(1000t - 70^\circ)$

$\therefore \mathbf{I} = 10/\underline{-70^\circ}$  A

[c]  $\mathbf{I} = 5/\underline{36.87^\circ} + 10/\underline{-53.13^\circ}$

$= 4 + j3 + 6 - j8 = 10 - j5 = 11.18/\underline{-26.57^\circ}$  A

[d]  $\sin(20,000\pi t + 30^\circ) = \cos(20,000\pi t - 60^\circ)$

Thus,

$\mathbf{V} = 300/\underline{45^\circ} - 100/\underline{-60^\circ} = 212.13 + j212.13 - (50 - j86.60)$

$= 162.13 + j298.73 = 339.90/\underline{61.51^\circ}$  mV

AP 9.2 [a]  $v = 18.6 \cos(\omega t - 54^\circ)$  V

[b]  $\mathbf{I} = 20/\underline{45^\circ} - 50/\underline{-30^\circ} = 14.14 + j14.14 - 43.3 + j25$

$= -29.16 + j39.14 = 48.81/\underline{126.68^\circ}$

Therefore  $i = 48.81 \cos(\omega t + 126.68^\circ)$  mA

[c]  $\mathbf{V} = 20 + j80 - 30/\underline{15^\circ} = 20 + j80 - 28.98 - j7.76$

$= -8.98 + j72.24 = 72.79/\underline{97.08^\circ}$

$v = 72.79 \cos(\omega t + 97.08^\circ)$  V

AP 9.3 [a]  $\omega L = (10^4)(20 \times 10^{-3}) = 200 \Omega$

[b]  $Z_L = j\omega L = j200 \Omega$

$$[c] \mathbf{V}_L = \mathbf{I}Z_L = (10/30^\circ)(200/90^\circ) \times 10^{-3} = 2/\underline{120^\circ} \text{ V}$$

$$[d] v_L = 2 \cos(10,000t + 120^\circ) \text{ V}$$

$$\text{AP 9.4 [a]} X_C = \frac{-1}{\omega C} = \frac{-1}{4000(5 \times 10^{-6})} = -50 \Omega$$

$$[b] Z_C = jX_C = -j50 \Omega$$

$$[c] \mathbf{I} = \frac{\mathbf{V}}{Z_C} = \frac{30/25^\circ}{50/-90^\circ} = 0.6/115^\circ \text{ A}$$

$$[d] i = 0.6 \cos(4000t + 115^\circ) \text{ A}$$

$$\text{AP 9.5 } \mathbf{I}_1 = 100/25^\circ = 90.63 + j42.26$$

$$\mathbf{I}_2 = 100/145^\circ = -81.92 + j57.36$$

$$\mathbf{I}_3 = 100/-95^\circ = -8.71 - j99.62$$

$$\mathbf{I}_4 = -(\mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3) = (0 + j0) \text{ A,} \quad \text{therefore } i_4 = 0 \text{ A}$$

$$\text{AP 9.6 [a]} \mathbf{I} = \frac{125/-60^\circ}{|Z|/\theta_z} = \frac{125}{|Z|}/(-60 - \theta_z)^\circ$$

$$\text{But } -60 - \theta_z = -105^\circ \quad \therefore \theta_z = 45^\circ$$


$$Z = 90 + j160 + jX_C$$

$$\therefore X_C = -70 \Omega; \quad X_C = -\frac{1}{\omega C} = -70$$

$$\therefore C = \frac{1}{(70)(5000)} = 2.86 \mu\text{F}$$

$$[b] \mathbf{I} = \frac{\mathbf{V}_s}{Z} = \frac{125/-60^\circ}{(90 + j90)} = 0.982/-105^\circ \text{ A;} \quad \therefore |\mathbf{I}| = 0.982 \text{ A}$$

AP 9.7 [a]

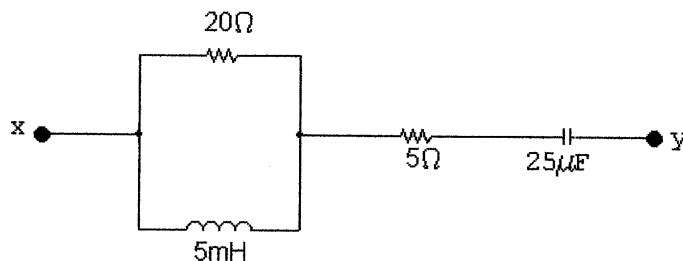

$$\omega = 2000 \text{ rad/s}$$

$$\omega L = 10 \Omega, \quad \frac{-1}{\omega C} = -20 \Omega$$

$$Z_{xy} = 20 \parallel j10 + 5 + j20 = \frac{20(j10)}{(20 + j10)} + 5 - j20$$

$$= 4 + j8 + 5 - j20 = (9 - j12) \Omega$$

$$[b] \quad \omega L = 40 \Omega, \quad \frac{-1}{\omega C} = -5 \Omega$$

$$\begin{aligned} Z_{xy} &= 5 - j5 + 20 \parallel j40 = 5 - j5 + \left[ \frac{(20)(j40)}{20 + j40} \right] \\ &= 5 - j5 + 16 + j8 = (21 + j3) \Omega \end{aligned}$$

$$\begin{aligned} [c] \quad Z_{xy} &= \left[ \frac{20(j\omega L)}{20 + j\omega L} \right] + \left( 5 - \frac{j10^6}{25\omega} \right) \\ &= \frac{20\omega^2 L^2}{400 + \omega^2 L^2} + \frac{j400\omega L}{400 + \omega^2 L^2} + 5 - \frac{j10^6}{25\omega} \end{aligned}$$

The impedance will be purely resistive when the  $j$  terms cancel, i.e.,

$$\frac{400\omega L}{400 + \omega^2 L^2} = \frac{10^6}{25\omega}$$

Solving for  $\omega$  yields  $\omega = 4000$  rad/s.

$$[d] \quad Z_{xy} = \frac{20\omega^2 L^2}{400 + \omega^2 L^2} + 5 = 10 + 5 = 15 \Omega$$

AP 9.8 The frequency 4000 rad/s was found to give  $Z_{xy} = 15 \Omega$  in Assessment Problem 9.7. Thus,


$$\mathbf{V} = 150 \angle 0^\circ, \quad \mathbf{I}_s = \frac{\mathbf{V}}{Z_{xy}} = \frac{150 \angle 0^\circ}{15} = 10 \angle 0^\circ \text{ A}$$

Using current division,

$$\mathbf{I}_L = \frac{20}{20 + j20} (10) = 5 - j5 = 7.07 \angle -45^\circ \text{ A}$$

$$i_L = 7.07 \cos(4000t - 45^\circ) \text{ A}, \quad I_m = 7.07 \text{ A}$$

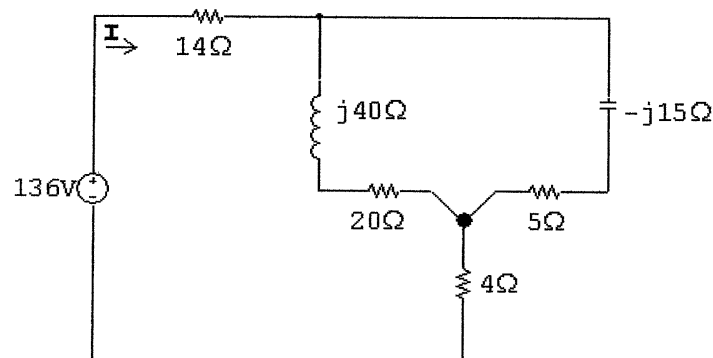AP 9.9 After replacing the delta made up of the  $50 \Omega$ ,  $40 \Omega$ , and  $10 \Omega$  resistors with its equivalent wye, the circuit becomes



The circuit is further simplified by combining the parallel branches,

$$(20 + j40) \parallel (5 - j15) = (12 - j16) \Omega$$

$$\text{Therefore } \mathbf{I} = \frac{136/0^\circ}{14 + 12 - j16 + 4} = 4/\underline{28.07^\circ} \text{ A}$$

AP 9.10

$$\mathbf{V}_1 = 240/\underline{53.13^\circ} = 144 + j192 \text{ V}$$

$$\mathbf{V}_2 = 96/\underline{-90^\circ} = -j96 \text{ V}$$


$$j\omega L = j(4000)(15 \times 10^{-3}) = j60 \Omega$$

$$\frac{1}{j\omega C} = -j \frac{6 \times 10^6}{(4000)(25)} = -j60 \Omega$$

Perform a source transformation:

$$\frac{\mathbf{V}_1}{j60} = \frac{144 + j192}{j60} = 3.2 - j2.4 \text{ A}$$

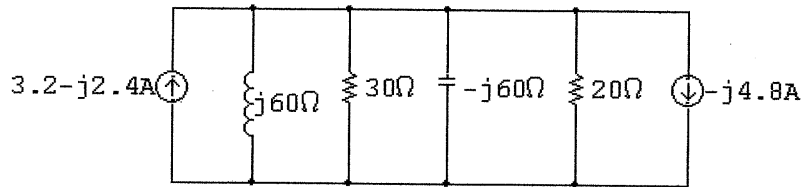
$$\frac{\mathbf{V}_2}{20} = -j \frac{96}{20} = -j4.8 \text{ A}$$



Combine the parallel impedances:

$$Y = \frac{1}{j60} + \frac{1}{30} + \frac{1}{-j60} + \frac{1}{20} = \frac{j5}{j60} = \frac{1}{12}$$

$$Z = \frac{1}{Y} = 12 \Omega$$

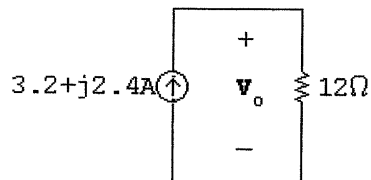

$$\mathbf{V}_o = 12(3.2 + j2.4) = 38.4 + j28.8 \text{ V} = 48/\underline{36.87^\circ} \text{ V}$$

$$v_o = 48 \cos(4000t + 36.87^\circ) \text{ V}$$


AP 9.11 Use the lower node as the reference node. Let  $V_1 =$  node voltage across the  $20\Omega$  resistor and  $V_{Th} =$  node voltage across the capacitor. Writing the node voltage equations gives us

$$\frac{V_1}{20} - 2/\underline{45^\circ} + \frac{V_1 - 10I_x}{j10} = 0 \quad \text{and} \quad V_{Th} = \frac{-j10}{10 - j10}(10I_x)$$

We also have

$$I_x = \frac{V_1}{20}$$

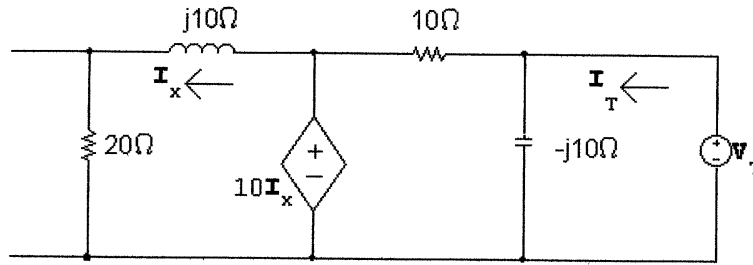Solving these equations for  $V_{Th}$  gives  $V_{Th} = 10/\underline{45^\circ}V$ . To find the Thévenin impedance, we remove the independent current source and apply a test voltage source at the terminals a, b. Thus



It follows from the circuit that


$$10I_x = (20 + j10)I_x$$

Therefore

$$I_x = 0 \quad \text{and} \quad I_T = \frac{V_T}{-j10} + \frac{V_T}{10}$$

$$Z_{Th} = \frac{V_T}{I_T}, \quad \text{therefore} \quad Z_{Th} = (5 - j5)\Omega$$

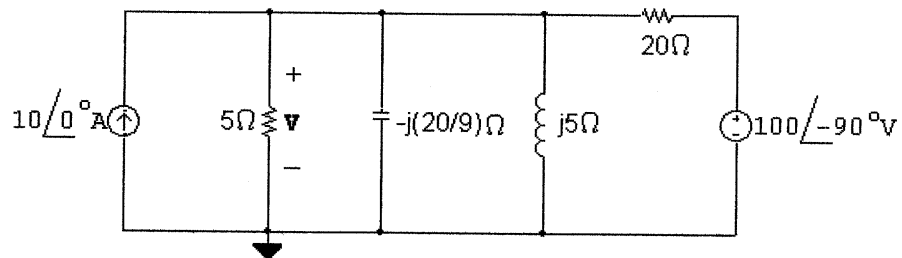AP 9.12 The phasor domain circuit is as shown in the following diagram:



The node voltage equation is

$$-10 + \frac{\mathbf{V}}{5} + \frac{\mathbf{V}}{-j(20/9)} + \frac{\mathbf{V}}{j5} + \frac{\mathbf{V} - 100/\underline{-90^\circ}}{20} = 0$$

Therefore  $\mathbf{V} = 10 - j30 = 31.62/\underline{-71.57^\circ}$

Therefore  $v = 31.62 \cos(50,000t - 71.57^\circ) \text{ V}$

AP 9.13 Let  $\mathbf{I}_a$ ,  $\mathbf{I}_b$ , and  $\mathbf{I}_c$  be the three clockwise mesh currents going from left to right. Summing the voltages around meshes a and b gives

$$33.8 = (1 + j2)\mathbf{I}_a + (3 - j5)(\mathbf{I}_a - \mathbf{I}_b)$$

and

$$0 = (3 - j5)(\mathbf{I}_b - \mathbf{I}_a) + 2(\mathbf{I}_b - \mathbf{I}_c).$$

But

$$\mathbf{V}_x = -j5(\mathbf{I}_a - \mathbf{I}_b),$$

therefore

$$\mathbf{I}_c = -0.75[-j5(\mathbf{I}_a - \mathbf{I}_b)].$$

Solving for  $\mathbf{I} = \mathbf{I}_a = 29 + j2 = 29.07/\underline{3.95^\circ} \text{ A}$ .

AP 9.14 [a]  $M = 0.4\sqrt{0.0625} = 0.1 \text{ H}$ ,  $\omega M = 80 \Omega$

$$Z_{22} = 40 + j800(0.125) + 360 + j800(0.25) = (400 + j300) \Omega$$

Therefore  $|Z_{22}| = 500 \Omega$ ,  $Z_{22}^* = (400 - j300) \Omega$

$$Z_\tau = \left(\frac{80}{500}\right)^2 (400 - j300) = (10.24 - j7.68) \Omega$$

[b]  $\mathbf{I}_1 = \frac{245.20}{184 + 100 + j400 + Z_\tau} = 0.50/\underline{-53.13^\circ} \text{ A}$

$$i_1 = 0.5 \cos(800t - 53.13^\circ) \text{ A}$$

[c]  $\mathbf{I}_2 = \left(\frac{j\omega M}{Z_{22}}\right) \mathbf{I}_1 = \frac{j80}{500/\underline{36.87^\circ}} (0.5/\underline{-53.13^\circ}) = 0.08/\underline{0^\circ} \text{ A}$

$$i_2 = 80 \cos 800t \text{ mA}$$

AP 9.15

$$\mathbf{I}_1 = \frac{\mathbf{V}_s}{Z_1 + 2s^2 Z_2} = \frac{25 \times 10^3 / 0^\circ}{1500 + j6000 + (25)^2(4 - j14.4)}$$

$$= 4 + j3 = 5 / \underline{36.87^\circ} \text{ A}$$

$$\mathbf{V}_1 = \mathbf{V}_s - Z_1 \mathbf{I}_1 = 25,000 / 0^\circ - (4 + j3)(1500 + j6000)$$

$$= 37,000 - j28,500$$

$$\mathbf{V}_2 = -\frac{1}{25} \mathbf{V}_1 = -1480 + j1140 = 1868.15 / \underline{142.39^\circ} \text{ V}$$


$$\mathbf{I}_2 = \frac{\mathbf{V}_2}{Z_2} = \frac{1868.15 / \underline{142.39^\circ}}{4 - j14.4} = 125 / \underline{216.87^\circ} \text{ A}$$

## Problems

- P 9.1 [a]  $\omega = 2\pi f = 240\pi \text{ rad/s}$ ,  $f = \frac{\omega}{2\pi} = 120 \text{ Hz}$   
 [b]  $T = 1/f = 8.33 \text{ ms}$   
 [c]  $V_m = 100 \text{ V}$   
 [d]  $v(0) = 100 \cos(45^\circ) = 70.71 \text{ V}$   
 [e]  $\phi = 45^\circ$ ;  $\phi = \frac{45^\circ(2\pi)}{360^\circ} = \frac{\pi}{4} = 0.7854 \text{ rad}$   
 [f]  $V = 0$  when  $240\pi t + 45^\circ = 90^\circ$ . Now resolve the units:  

$$(240\pi \text{ rad/s})t = \frac{45^\circ}{57.3^\circ/\text{rad}} = \frac{\pi}{4} \text{ rad}, \quad t = 1.042 \text{ ms}$$
  
 [g]  $(dv/dt) = (-100)240\pi \sin(240\pi t + 45^\circ)$   
 $(dv/dt) = 0$  when  $240\pi t + 45^\circ = 180^\circ$   
 or  $240\pi t = \frac{135^\circ}{57.3^\circ/\text{rad}} = \frac{3\pi}{4} \text{ rad}$   
 Therefore  $t = 3.125 \text{ ms}$

P 9.2

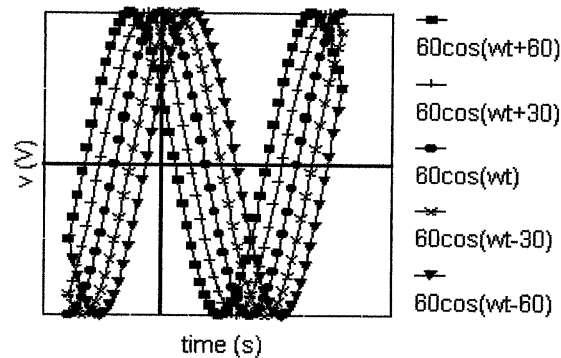

- [a] Left as  $\phi$  becomes more positive  
 [b] Right

- P 9.3 [a]  $\frac{T}{2} = \frac{1250}{6} + \frac{250}{6} = 250 \mu\text{s}$ ;  $T = 500 \mu\text{s}$   

$$f = \frac{1}{T} = \frac{10^6}{500} = 2000 \text{ Hz}$$



$$[\mathbf{b}] \quad v = V_m \sin(\omega t + \theta)$$

$$\omega = 2\pi f = 4000\pi \text{ rad/s}$$

$$4000\pi \left( \frac{-250}{6} \times 10^{-6} \right) + \theta = 0; \quad \therefore \theta = \frac{\pi}{6} \text{ rad} = 30^\circ$$

$$v = V_m \sin[4000\pi t + 30^\circ]$$

$$75 = V_m \sin 30^\circ; \quad V_m = 150 \text{ V}$$

$$v = 150 \sin[4000\pi t + 30^\circ] = 150 \cos[4000\pi t - 60^\circ] \text{ V}$$

P 9.4 [a] By hypothesis

$$i = 10 \cos(\omega t + \theta)$$

$$\frac{di}{dt} = -10\omega \sin(\omega t + \theta)$$

$$\therefore 10\omega = 20,000\pi; \quad \omega = 2000\pi \text{ rad/s}$$

$$[\mathbf{b}] \quad f = \frac{\omega}{2\pi} = 1000 \text{ Hz}; \quad T = \frac{1}{f} = 1 \text{ ms} = 1000 \mu\text{s}$$

$$\frac{150}{1000} = \frac{3}{20}, \quad \therefore \theta = -90 - \frac{3}{20}(360) = -144^\circ$$

$$\therefore i = 10 \cos(2000\pi t - 144^\circ) \text{ A}$$

P 9.5 [a] 170 V

$$[\mathbf{b}] \quad 2\pi f = 120\pi; \quad f = 60 \text{ Hz}$$

$$[\mathbf{c}] \quad \omega = 120\pi = 376.99 \text{ rad/s}$$

$$[\mathbf{d}] \quad \theta(\text{rad}) = \frac{-\pi}{180}(60) = \frac{-\pi}{3} = -1.05 \text{ rad}$$

$$[\mathbf{e}] \quad \theta = -60^\circ$$

$$[\mathbf{f}] \quad T = \frac{1}{f} = \frac{1}{60} = 16.67 \text{ ms}$$

$$[\mathbf{g}] \quad 120\pi t - \frac{\pi}{3} = 0; \quad \therefore t = \frac{1}{360} = 2.78 \text{ ms}$$

$$\begin{aligned}
 [\mathbf{h}] \quad v &= 170 \cos \left[ 120\pi \left( t + \frac{0.125}{18} \right) - \frac{\pi}{3} \right] \\
 &= 170 \cos[120\pi t + (15\pi/18) - (\pi/3)] \\
 &= 170 \cos[120\pi t + (\pi/2)] \\
 &= -170 \sin 120\pi t \text{ V}
 \end{aligned}$$

$$[i] \quad 120\pi(t - t_o) - (\pi/3) = 120\pi t - (\pi/2)$$

$$\therefore 120\pi t_o = \frac{\pi}{6}; \quad t_o = \frac{25}{18} \text{ ms}$$

$$[j] \quad 120\pi(t - t_o) - (\pi/3) = 120\pi t$$

$$\therefore 120\pi t_o = \frac{\pi}{3}; \quad t_o = \frac{25}{9} \text{ ms}$$

$$\begin{aligned} \text{P 9.6} \quad u &= \int_{t_o}^{t_o+T} V_m^2 \cos^2(\omega t + \phi) dt \\ &= V_m^2 \int_{t_o}^{t_o+T} \frac{1}{2} + \frac{1}{2} \cos(2\omega t + 2\phi) dt \\ &= \frac{V_m^2}{2} \left\{ \int_{t_o}^{t_o+T} dt + \int_{t_o}^{t_o+T} \cos(2\omega t + 2\phi) dt \right\} \\ &= \frac{V_m^2}{2} \left\{ T + \frac{1}{2\omega} [\sin(2\omega t + 2\phi)]_{t_o}^{t_o+T} \right\} \\ &= \frac{V_m^2}{2} \left\{ T + \frac{1}{2\omega} [\sin(2\omega t_o + 4\pi + 2\phi) - \sin(2\omega t_o + 2\phi)] \right\} \\ &= V_m^2 \left( \frac{T}{2} \right) + \frac{1}{2\omega} (0) = V_m^2 \left( \frac{T}{2} \right) \end{aligned}$$

$$\text{P 9.7} \quad V_m = \sqrt{2} V_{\text{rms}} = \sqrt{2}(120) = 169.71 \text{ V}$$

$$\text{P 9.8} \quad V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^{T/2} V_m^2 \sin^2 \frac{2\pi}{T} t dt}$$

$$\int_0^{T/2} V_m^2 \sin^2 \left( \frac{2\pi}{T} t \right) dt = \frac{V_m^2}{2} \int_0^{T/2} \left( 1 - \cos \frac{4\pi}{T} t \right) dt = \frac{V_m^2 T}{4}$$

$$\text{Therefore} \quad V_{\text{rms}} = \sqrt{\frac{1}{T} \frac{V_m^2 T}{4}} = \frac{V_m}{2}$$

P 9.9 [a] The numerical values of the terms in Eq. 9.8 are

$$V_m = 100, \quad R/L = 533.33, \quad \omega L = 30$$

$$\sqrt{R^2 + \omega^2 L^2} = 50$$

$$\phi = 60^\circ, \quad \theta = \tan^{-1} 30/40, \quad \theta = 36.87^\circ$$

$$i = \left[ -1.84e^{-533.33t} + 2 \cos(400t + 23.13^\circ) \right] \text{ A}, \quad t \geq 0$$

[b] Transient component =  $-1.84e^{-533.33t}$  A

Steady-state component =  $2 \cos(400t + 23.13^\circ)$  A

[c] By direct substitution into Eq 9.9,  $i(1.875 \text{ ms}) = 133.61 \text{ mA}$

[d] 2 A, 400 rad/s, 23.13°

[e] The current lags the voltage by 36.87°.

P 9.10 [a] From Eq. 9.9 we have

$$L \frac{di}{dt} = \frac{V_m R \cos(\phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} e^{-(R/L)t} - \frac{\omega L V_m \sin(\omega t + \phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}}$$

$$Ri = \frac{-V_m R \cos(\phi - \theta) e^{-(R/L)t}}{\sqrt{R^2 + \omega^2 L^2}} + \frac{V_m R \cos(\omega t + \phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}}$$

$$L \frac{di}{dt} + Ri = V_m \left[ \frac{R \cos(\omega t + \phi - \theta) - \omega L \sin(\omega t + \phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} \right]$$

But

$$\frac{R}{\sqrt{R^2 + \omega^2 L^2}} = \cos \theta \quad \text{and} \quad \frac{\omega L}{\sqrt{R^2 + \omega^2 L^2}} = \sin \theta$$

Therefore the right-hand side reduces to

$$V_m \cos(\omega t + \phi)$$

At  $t = 0$ , Eq. 9.9 reduces to

$$i(0) = \frac{-V_m \cos(\phi - \theta)}{\sqrt{R^2 - \omega^2 L^2}} + \frac{V_m \cos(\phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} = 0$$

$$[b] \quad i_{ss} = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$$

Therefore

$$L \frac{di_{ss}}{dt} = \frac{-\omega L V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin(\omega t + \phi - \theta)$$

and

$$Ri_{ss} = \frac{V_m R}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$$

$$L \frac{di_{ss}}{dt} + Ri_{ss} = V_m \left[ \frac{R \cos(\omega t + \phi - \theta) - \omega L \sin(\omega t + \phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} \right]$$

$$= V_m \cos(\omega t + \phi)$$

P 9.11 [a]  $\mathbf{Y} = 100/45^\circ + 500/-60^\circ = 483.86/-48.48^\circ$

$$y = 483.86 \cos(300t - 48.48^\circ)$$

[b]  $\mathbf{Y} = 250/30^\circ - 150/50^\circ = 120.51/4.8^\circ$

$$y = 120.51 \cos(377t + 4.8^\circ)$$

$$[c] \mathbf{Y} = 60/\underline{60^\circ} - 120/\underline{-215^\circ} + 100/\underline{90^\circ} = 152.88/\underline{32.94^\circ}$$

$$y = 152.88 \cos(100t + 32.94^\circ)$$

$$[d] \mathbf{Y} = 100/\underline{40^\circ} + 100/\underline{160^\circ} + 100/\underline{-80^\circ} = 0$$

$$y = 0$$

P 9.12 [a] 50Hz

$$[b] \theta_v = 0^\circ$$

$$\mathbf{I} = \frac{340/\underline{0^\circ}}{j\omega L} = \frac{340}{\omega L} \underline{-90^\circ} = 8.5 \underline{-90^\circ}; \quad \theta_i = -90^\circ$$

$$[c] \frac{340}{\omega L} = 8.5; \quad \omega L = 40 \Omega$$

$$[d] L = \frac{40}{100\pi} = \frac{400}{\pi} \text{ mH} = 127.32 \text{ mH}$$

$$[e] Z_L = j\omega L = j40 \Omega$$

P 9.13 [a]  $\omega = 2\pi f = 80\pi \times 10^3 = 251.33 \text{ krad/s} = 251,327.41 \text{ rad/s}$

$$[b] \mathbf{I} = \frac{2.5 \times 10^{-3} \underline{0^\circ}}{1/j\omega C} = j\omega C(2.5 \times 10^{-3}) \underline{0^\circ} = 2.5 \times 10^{-3} \omega C \underline{90^\circ}$$

$$\therefore \theta_i = 90^\circ$$

$$[c] 125.66 \times 10^{-6} = 2.5 \times 10^{-3} \omega C$$

$$\frac{1}{\omega C} = \frac{2.5 \times 10^{-3}}{125.66 \times 10^{-6}} = 19.89 \Omega, \quad \therefore X_C = -19.89 \Omega$$

$$[d] C = \frac{1}{19.89(\omega)} = \frac{1}{(19.89)(80\pi \times 10^3)}$$

$$C = 0.2 \times 10^{-6} = 0.2 \mu\text{F}$$

$$[e] Z_c = j \left( \frac{-1}{\omega C} \right) = -j19.89 \Omega$$

P 9.14 [a]  $\mathbf{V}_g = 150/\underline{20^\circ}; \quad \mathbf{I}_g = 30/\underline{-52^\circ}$

$$\therefore Z = \frac{\mathbf{V}_g}{\mathbf{I}_g} = 5/\underline{72^\circ} \Omega$$


[b]  $i_g$  lags  $v_g$  by  $72^\circ$ :

$$2\pi f = 8000\pi; \quad f = 4000 \text{ Hz}; \quad T = 1/f = 250 \mu\text{s}$$

$$\therefore i_g \text{ lags } v_g \text{ by } \frac{72}{360}(250) = 50 \mu\text{s}$$

P 9.15 [a]  $j\omega L = j(5 \times 10^4)(40 \times 10^{-6}) = j2\Omega$
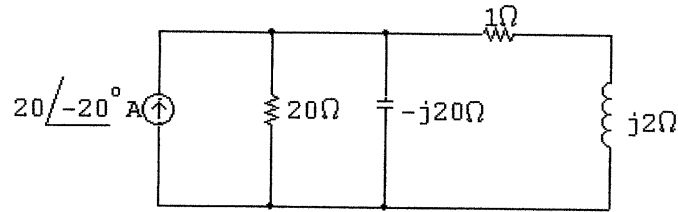
$$\frac{1}{j\omega C} = -j\frac{10^6}{5 \times 10^4} = -j20\Omega; \quad \mathbf{I}_g = 20/\underline{-20^\circ} \text{ A}$$



[b]  $\mathbf{V}_o = 20/\underline{-20^\circ} Z_e$

$$Z_e = \frac{1}{Y_e}; \quad Y_e = \frac{1}{20} + j\frac{1}{20} + \frac{1}{1+j2}$$


$$Y_e = 0.05 + j0.05 + 0.20 - j0.40 = 0.25 - j0.35 \text{ S}$$

$$Z_e = \frac{1}{0.25 - j0.35} = 2.32/\underline{54.46^\circ} \Omega$$

$$\mathbf{V}_o = (20/\underline{-20^\circ})(2.32/\underline{54.46^\circ}) = 46.4/\underline{34.46^\circ} \text{ V}$$

[c]  $v_o = 46.4 \cos(5 \times 10^4 t + 34.46^\circ) \text{ V}$

P 9.16 [a]

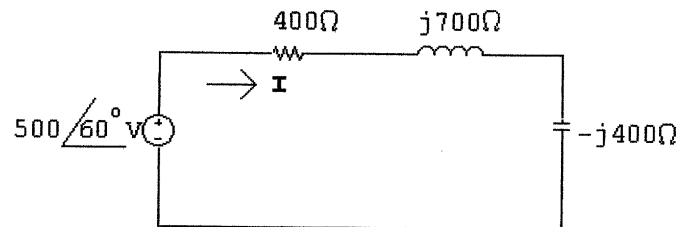

[b]  $\mathbf{I} = \frac{500/\underline{60^\circ}}{400 + j700 - j400} = 1/\underline{23.13^\circ} \text{ A}$

[c]  $i = 1 \cos(8000t + 23.13^\circ) \text{ A}$

P 9.17 [a]  $Z_1 = R_1 - j\frac{1}{\omega C_1}$

$$Z_2 = \frac{R_2/j\omega C_2}{R_2 + (1/j\omega C_2)} = \frac{R_2}{1 + j\omega R_2 C_2} = \frac{R_2 - j\omega R_2^2 C_2}{1 + \omega^2 R_2^2 C_2^2}$$

$$Z_1 = Z_2 \quad \text{when} \quad R_1 = \frac{R_2}{1 + \omega^2 R_2^2 C_2^2} \quad \text{and}$$

$$\frac{1}{\omega C_1} = \frac{\omega R_2^2 C_2}{1 + \omega^2 R_2^2 C_2^2} \quad \text{or} \quad C_1 = \frac{1 + \omega^2 R_2^2 C_2^2}{\omega^2 R_2^2 C_2}$$

$$[b] R_1 = \frac{500}{1 + (64 \times 10^8)(25 \times 10^4)(625 \times 10^{-18})} = 250 \Omega$$

$$C_1 = \frac{2}{(64 \times 10^8)(25 \times 10^4)(25 \times 10^{-9})} = 50 \text{ nF}$$

P 9.18 [a]  $Y_2 = \frac{1}{R_2} + j\omega C_2$

$$Y_1 = \frac{1}{R_1 + (1/j\omega C_1)} = \frac{j\omega C_1}{1 + j\omega R_1 C_1} = \frac{\omega^2 R_1 C_1^2 + j\omega C_1}{1 + \omega^2 R_1^2 C_1^2}$$

Therefore  $Y_1 = Y_2$  when

$$R_2 = \frac{1 + \omega^2 R_1^2 C_1^2}{\omega^2 R_1 C_1^2} \quad \text{and} \quad C_2 = \frac{C_1}{1 + \omega^2 R_1^2 C_1^2}$$

[b]  $R_2 = \frac{1 + (4 \times 10^8)(4 \times 10^6)(2500 \times 10^{-18})}{(4 \times 10^8)(2 \times 10^3)(2500 \times 10^{-18})} = 2500 = 2.5 \text{ k}\Omega$

$$C_2 = \frac{50 \times 10^{-9}}{5} = 10 \text{ nF}$$

P 9.19 [a]  $Z_1 = R_1 + j\omega L_1$

$$Z_2 = \frac{R_2(j\omega L_2)}{R_2 + j\omega L_2} = \frac{\omega^2 L_2^2 R_2 + j\omega L_2 R_2^2}{R_2^2 + \omega^2 L_2^2}$$

$$Z_1 = Z_2 \quad \text{when} \quad R_1 = \frac{\omega^2 L_2^2 R_2}{R_2^2 + \omega^2 L_2^2} \quad \text{and} \quad L_1 = \frac{R_2^2 L_2}{R_2^2 + \omega^2 L_2^2}$$

[b]  $R_1 = \frac{(4 \times 10^8)(6.25)(5 \times 10^4)}{25 \times 10^8 + (4 \times 10^8)(6.25)} = 2.5 \times 10^4$

$$\therefore R_1 = 25 \text{ k}\Omega$$

$$L_1 = \frac{(25 \times 10^8)2.5}{50 \times 10^8} = 1.25 \text{ H}$$

P 9.20 [a]  $Y_2 = \frac{1}{R_2} - \frac{j}{\omega L_2}$

$$Y_1 = \frac{1}{R_1 + j\omega L_1} = \frac{R_1 - j\omega L_1}{R_1^2 + \omega^2 L_1^2}$$

Therefore  $Y_2 = Y_1$  when

$$R_2 = \frac{R_1^2 + \omega^2 L_1^2}{R_1} \quad \text{and} \quad L_2 = \frac{R_1^2 + \omega^2 L_1^2}{\omega^2 L_1}$$

$$[\text{b}] R_2 = \frac{25 \times 10^6 + 10^8(0.25)}{5 \times 10^3} = 10 \times 10^3$$

$$\therefore R_2 = 10 \text{ k}\Omega$$

$$L_2 = \frac{50 \times 10^6}{10^8(0.5)} = 1 \text{ H}$$

$$\begin{aligned} \text{P 9.21 } [\text{a}] Y &= \frac{1}{4 - j3} + \frac{1}{16 + j12} + \frac{1}{-j100} \\ &= 0.16 + j0.12 + 0.04 - j0.03 + j0.01 \\ &= 0.2 + j0.1 = 223.6/26.57^\circ \text{ mS} \end{aligned}$$

$$[\text{b}] G = 200 \text{ mS}$$

$$[\text{c}] B = 100 \text{ mS}$$

$$[\text{d}] \mathbf{I} = 50/0^\circ \text{ A}, \quad \mathbf{V} = \frac{\mathbf{I}}{Y} = \frac{50}{0.223/26.57^\circ} = 223.61/-26.57^\circ \text{ V}$$

$$\mathbf{I}_C = \frac{\mathbf{V}}{Z_C} = \frac{223.6/-26.57^\circ}{100/-90^\circ} = 2.24/63.43^\circ \text{ A}$$

$$i_C = 2.24 \cos(\omega t + 63.43^\circ) \text{ A}, \quad I_m = 2.24 \text{ A}$$

$$\begin{aligned} \text{P 9.22 } [\text{a}] Z_{ab} &= j5\omega + \frac{(4000)(10^9/j\omega 625)}{4000 + (10^9/j\omega 625)} \\ &= j5\omega + \frac{4 \times 10^{12}}{25 \times 10^5 j\omega + 10^9} \\ &= j5\omega + \frac{4 \times 10^7}{10^4 + j25\omega} \\ &= j5\omega + \frac{4 \times 10^{11}}{10^8 + 625\omega^2} - j \frac{100 \times 10^7 \omega}{10^8 + 625\omega^2} \\ \therefore 5 &= \frac{10^9}{10^8 + 625\omega^2} \end{aligned}$$

$$5 \times 10^8 + 3125\omega^2 = 10^9$$

$$\omega = 4 \times 10^2 = 400 \text{ rad/s}$$

$$[\text{b}] Z_{ab}(400) = j2000 + \frac{(4000)(-j4000)}{4000 - j4000} = 2 \text{ k}\Omega$$

$$\text{P 9.23 } Z_1 = 10 - j40 \Omega$$

$$Z_2 = \frac{(5 - j10)(10 + j30)}{15 + j20} = 10 - j10 \Omega$$

$$Z_3 = \frac{20(j20)}{20 + j20} = 10 + j10\Omega$$

$$\therefore Z_{ab} = Z_1 + Z_2 + Z_3 = 30 - j40\Omega = 50/\underline{-53.13^\circ}\Omega$$

P 9.24 First find the admittance of the parallel branches

$$Y_p = \frac{1}{6 - j2} + \frac{1}{4 + j12} + \frac{1}{5} + \frac{1}{j10} = 0.375 - j0.125\text{ S}$$

$$Z_p = \frac{1}{Y_p} = \frac{1}{0.375 - j0.125} = 2.4 + j0.8\Omega$$

$$Z_{ab} = -j12.8 + 2.4 + j0.8 + 13.6 = 16 - j12\Omega$$

$$Y_{ab} = \frac{1}{Z_{ab}} = \frac{1}{16 - j12} = 0.04 + j0.03\text{ S}$$

$$= 40 + j30\text{ mS} = 50/\underline{36.87^\circ}\text{ mS}$$

P 9.25  $Z = 400 + j(5)(40) - j\frac{1000}{(5)(0.4)} = 500/\underline{-36.87^\circ}\Omega$

$$I_o = \frac{750/0^\circ \times 10^{-3}}{500/\underline{-36.87^\circ}} = 1.5/\underline{36.87^\circ}\text{ mA}$$

$$i_o(t) = 1.5 \cos(5000t + 36.87^\circ)\text{ mA}$$

P 9.26  $V_g = 50/\underline{-45^\circ}\text{ V}; \quad I_g = 100/\underline{-8.13^\circ}\text{ mA}$

$$Z = \frac{V_g}{I_g} = 500/\underline{-36.87^\circ}\Omega = 400 - j300\Omega$$

$$Z = 400 + j\left(0.04\omega - \frac{2.5 \times 10^6}{\omega}\right)$$

$$\therefore 0.04\omega - \frac{2.5 \times 10^6}{\omega} = -300$$

$$\therefore \omega^2 + 7500\omega - 62.5 \times 10^6 = 0$$

$$\therefore \omega = -3750 \pm \sqrt{(3750)^2 + 62.5 \times 10^6} = -3750 \pm 8750$$


$$\omega > 0, \quad \therefore \omega = 5000\text{ rad/s}$$



$$P\ 9.27 \quad Z_L = j(5000)(48 \times 10^{-3}) = j240\ \Omega$$

$$Z_C = \frac{-j}{(5000)(2.5 \times 10^{-6})} = -j80\ \Omega$$

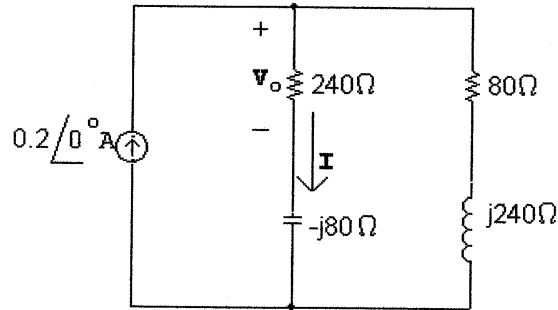Construct the phasor domain equivalent circuit:



Using current division:

$$\mathbf{I} = \frac{(80 + j240)}{240 - j80 + 80 + j240}(0.2) = 0.1 + j0.1\ \text{A}$$


$$\mathbf{V}_o = 240\mathbf{I} = 24 + j24 = 33.94/45^\circ$$

$$v_o = 33.94 \cos(5000t + 45^\circ)\ \text{V}$$

$$P\ 9.28 \quad \frac{1}{j\omega C} = \frac{10^9}{(31.25)(8000)} = -j4000\ \Omega$$

$$j\omega L = j8000(500)10^{-3} = j4000\ \Omega$$

$$\mathbf{V}_g = 64/0^\circ\ \text{V}$$

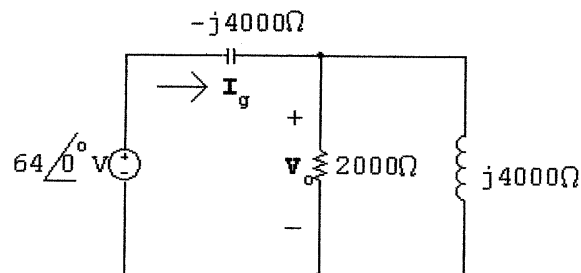

$$Z_e = \frac{(2000)(j4000)}{2000 + j4000} = 1600 + j800\ \Omega$$


$$Z_T = 1600 + j800 - j4000 = 1600 - j3200\ \Omega$$

$$\mathbf{I}_g = \frac{64/0^\circ}{1600 - j3200} = 8 + j16 \text{ mA}$$

$$\mathbf{V}_o = \mathbf{Z}_e \mathbf{I}_g = (1600 + j800)(0.008 + j0.016) = j32 = 32/90^\circ \text{ V}$$

$$v_o = 32 \cos(8000t + 90^\circ) \text{ V}$$

P 9.29 [a]

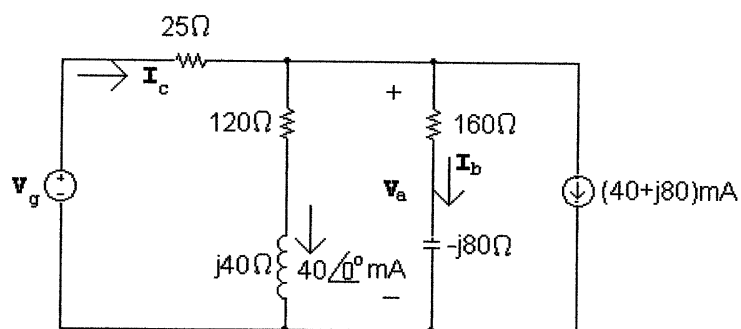

$$\mathbf{V}_a = (120 + j40)(0.04/0^\circ) = 4.8 + j1.6 \text{ V}$$

$$\mathbf{I}_b = \frac{4.8 + j1.6}{160 - j80} = 20 + j20 \text{ mA}$$

$$\mathbf{I}_c = 40/0^\circ + (20 + j20) + (40 + j80) \text{ mA} = 100 + j100 \text{ mA}$$

$$\mathbf{V}_g = 25\mathbf{I}_c + \mathbf{V}_a = 25(0.100 + j0.100) + 4.8 + j1.6 = 7.3 + j4.1 \text{ V}$$

[b]  $i_b = 28.28 \cos(800t + 45^\circ) \text{ mA}$

$$i_c = 141.42 \cos(800t + 45^\circ) \text{ mA}$$

$$v_g = 8.37 \cos(800t + 29.32^\circ) \text{ V}$$


P 9.30 [a]  $\frac{1}{j\omega C} = \frac{10^9}{j8 \times 10^5(125)} = -j10 \Omega$

$$j\omega L = j8 \times 10^5(25 \times 10^{-6}) = j20 \Omega$$

$$\mathbf{Z}_e = \frac{(-j10)(20)}{20 - j10} = 4 - j8 \Omega$$

$$\mathbf{I}_g = 5/0^\circ$$
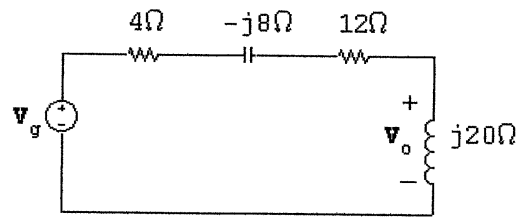
$$\mathbf{V}_g = \mathbf{I}_g \mathbf{Z}_e = 5(4 - j8) = 20 - j40 \text{ V}$$



$$\mathbf{V}_o = \frac{(20 - j40)(j20)}{(16 + j12)} = 44 - j8 = 44.72 \angle -10.30^\circ \text{ V}$$

$$v_o = 44.72 \cos(8 \times 10^5 t - 10.30^\circ) \text{ V}$$

$$[\text{b}] \quad \omega = 2\pi f = 8 \times 10^5; \quad f = \frac{4 \times 10^5}{\pi}$$

$$T = \frac{1}{f} = \frac{\pi}{4 \times 10^5} = 2.5\pi \mu\text{s}$$

$$\therefore \frac{10.30}{360}(2.5\pi) = 224.82 \text{ ns}$$


$$\therefore v_o \text{ lags } i_g \text{ by } 224.82 \text{ ns}$$

P 9.31  $\mathbf{I}_s = 15 \angle 0^\circ \text{ mA}$

$$\frac{1}{j\omega C} = \frac{10^6}{j0.05(8000)} = -j2500 \Omega$$

$$j\omega L = j8000(1.25) = j10,000 \Omega$$

After two source transformations we have

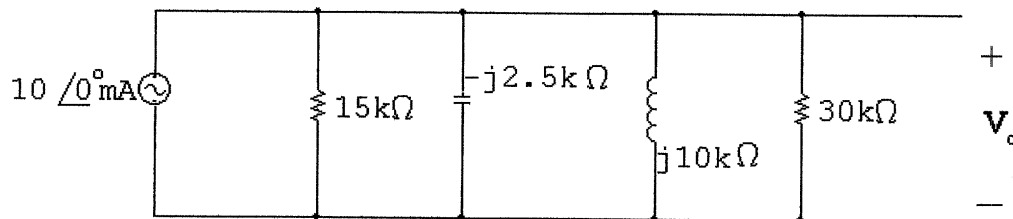

$$15 \text{ k}\Omega \parallel 30 \text{ k}\Omega = 10 \text{ k}\Omega$$


$$Y_o = \frac{10^{-3}}{10} + \frac{1}{-j2500} + \frac{1}{j10^4} = 10^{-4}(1 + j3)$$

$$Z_o = \frac{10^4}{1 + j3} = (1 - j3) \text{ k}\Omega$$

$$\mathbf{V}_o = \mathbf{I}_s Z_o = (10)(1 - j3) = 10 - j30 = 31.62 \angle -71.57^\circ \text{ V}$$

$$v_o = 31.62 \cos(8000t - 71.57^\circ) \text{ V}$$

P 9.32

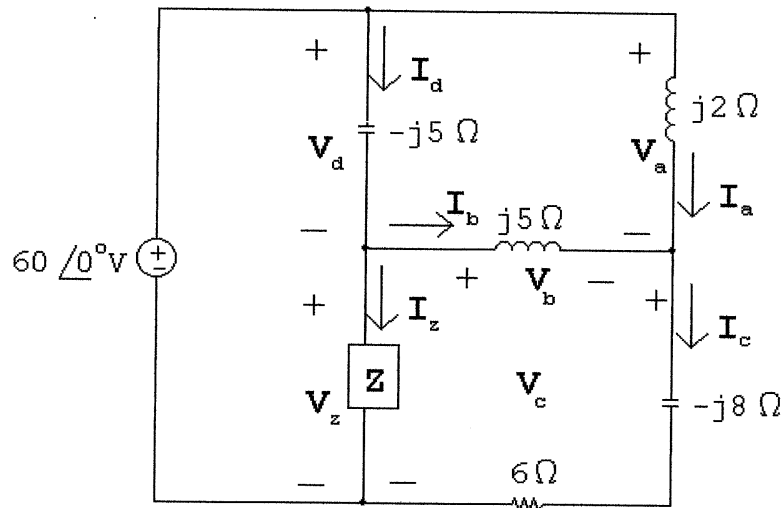

$$\mathbf{V}_a = j2\mathbf{I}_a = j2(-j5) = 10\angle 0^\circ \text{ V}$$

$$\mathbf{V}_c = 60\angle 0^\circ - \mathbf{V}_a = 50\angle 0^\circ \text{ V}$$

$$\mathbf{I}_c = \frac{\mathbf{V}_c}{6 - j8} = \frac{50\angle 0^\circ}{10\angle -53.13^\circ} = 5\angle 53.13^\circ = 3 + j4 \text{ A}$$

$$\mathbf{I}_b = \mathbf{I}_c - \mathbf{I}_a = 3 + j4 - (-j5) = 3 + j9 \text{ A} = 9.49\angle 71.57^\circ \text{ A}$$

$$\mathbf{V}_b = \mathbf{I}_b(j5) = (3 + j9)(j5) = -45 + j15 \text{ V}$$

$$\mathbf{V}_z = \mathbf{V}_b + \mathbf{V}_c = -45 + j15 + 50 + j0 = 5 + j15 \text{ V}$$

$$\mathbf{V}_d + \mathbf{V}_z = 60\angle 0^\circ; \quad \therefore \mathbf{V}_d = 60 - 5 - j15 = 55 - j15 \text{ V}$$

$$\mathbf{I}_d = \frac{\mathbf{V}_d}{-j5} = 3 + j11 \text{ A}$$

$$\mathbf{I}_z = \mathbf{I}_d - \mathbf{I}_b = 3 + j11 - 3 - j9 = j2 \text{ A}$$

$$\mathbf{Z} = \frac{\mathbf{V}_z}{\mathbf{I}_z} = \frac{5 + j15}{j2} = 7.5 - j2.5 \Omega$$

 P 9.33  $\mathbf{V}_2$  is the voltage across the  $-j10\Omega$  impedance.

$$\frac{\mathbf{V}_1 - \mathbf{V}_g}{20} + \frac{\mathbf{V}_1}{j5} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{Z} = 0$$

$$\frac{(40 + j30) - (100 - j50)}{20} + \frac{40 + j30}{j5} + \frac{(40 + j30) - \mathbf{V}_2}{Z} = 0$$

$$\therefore \mathbf{V}_2 = 40 + j30 + (3 - j4)Z$$

$$\frac{\mathbf{V}_2 - \mathbf{V}_1}{Z} + \frac{\mathbf{V}_L}{-j10} - \mathbf{I}_g + \frac{\mathbf{V}_2 - \mathbf{V}_g}{3 + j1} = 0$$

$$\frac{\mathbf{V}_2 - (40 + j30)}{Z} + \frac{\mathbf{V}_2}{-j10} - (20 + j30) + \frac{\mathbf{V}_2 - (100 - j50)}{3 + j1} = 0$$


Substituting the expression for  $\mathbf{V}_2$  found at the start and simplifying yields

$$Z = 12 + j16 \Omega$$

P 9.34 Simplify the top triangle using series and parallel combinations:

$$(1 + j1) \parallel (1 - j1) = 1 \Omega$$

Convert the lower left delta to a wye:

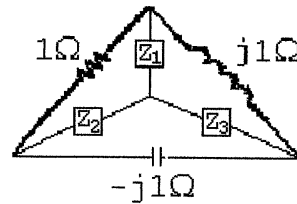


$$Z_1 = \frac{(j1)(1)}{1 + j1 - j1} = j1 \Omega$$

$$Z_2 = \frac{(-j1)(1)}{1 + j1 - j1} = -j1 \Omega$$

$$Z_3 = \frac{(j1)(-j1)}{1 + j1 - j1} = 1 \Omega$$

Convert the lower right delta to a wye:

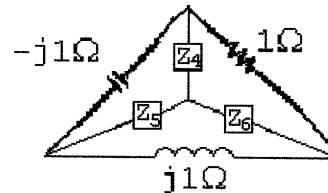


$$Z_4 = \frac{(-j1)(1)}{1 + j1 - j1} = -j1 \Omega$$

$$Z_5 = \frac{(-j1)(j1)}{1 + j1 - j1} = 1 \Omega$$

$$Z_6 = \frac{(j1)(1)}{1 + j1 - j1} = j1 \Omega$$

The resulting circuit is shown below:

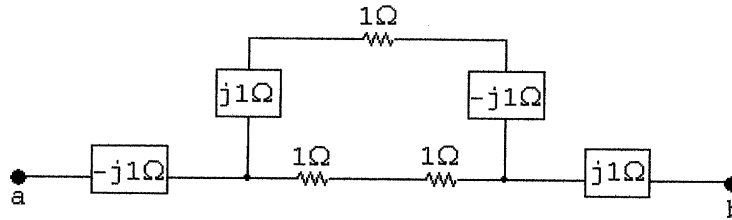

Simplify the middle portion of the circuit by making series and parallel combinations:

$$(1 + j1 - j1) \parallel (1 + 1) = 1 \parallel 2 = 2/3 \Omega$$

$$Z_{ab} = -j1 + 2/3 + j1 = 2/3 \Omega$$

P 9.35 [a] 
$$Y_p = \frac{1}{10 + j2\omega} + j4 \times 10^{-3}\omega$$

$$= \frac{10 - j2\omega}{100 + 4\omega^2} + j4 \times 10^{-3}\omega$$

$$= \frac{10}{100 + 4\omega^2} - \frac{j2\omega}{100 + 4\omega^2} + j4 \times 10^{-3}\omega$$

$Y_p$  is real when

$$4 \times 10^{-3}\omega = \frac{2\omega}{100 + 4\omega^2}$$

or  $\omega^2 = 100$ ;  $\omega = 10$  rad/s;  $f = 5/\pi = 1.59$  Hz

[b] 
$$Y_p(10 \text{ rad/s}) = \frac{10}{500} = 20 \text{ mS}$$

$$Z_p(10 \text{ rad/s}) = \frac{10^3}{20} = 50 \Omega$$

$$Z(10 \text{ rad/s}) = 50 + 150 = 200 \Omega$$

$$I_o = \frac{V_g}{200} \text{ A} = \frac{10/0^\circ}{200} = 50/0^\circ \text{ mA}$$

$$i_o = 50 \cos 10t \text{ mA}$$

$$\begin{aligned}
 \text{P 9.36 [a]} \quad Z_g &= 4000 - j\frac{10^9}{25\omega} + \frac{10^4(j2\omega)}{10^4 + j2\omega} \\
 &= 4000 - j\frac{10^9}{25\omega} + \frac{2 \times 10^4 j\omega(10^4 - j2\omega)}{10^8 + 4\omega^2} \\
 &= 4000 - j\frac{10^9}{25\omega} + \frac{4 \times 10^4 \omega^2}{10^8 + 4\omega^2} + j\frac{2 \times 10^8 \omega}{10^8 + 4\omega^2}
 \end{aligned}$$

$$\therefore \frac{10^9}{25\omega} = \frac{0.2 \times 10^9 \omega}{10^8 + 4\omega^2}$$

$$10^8 + 4\omega^2 = 5\omega^2$$

$$\omega^2 = 10^8; \quad \omega = 10,000 \text{ rad/s}$$

[b] When  $\omega = 10,000 \text{ rad/s}$

$$Z_g = 4000 + \frac{4 \times 10^4 (10^4)^2}{10^8 + 4(10^4)^2} = 12,000 \Omega$$

$$\therefore I_g = \frac{45/0^\circ}{12,000} = 3.75/0^\circ \text{ mA}$$

$$V_o = V_g - I_g Z_1$$

$$Z_1 = 4000 - j\frac{10^9}{25 \times 10^4} = 4000 - j4000 \Omega$$

$$\begin{aligned}
 V_o &= 45/0^\circ - (3.75 \times 10^{-3})(4000 - j4000) = 45 - (15 - j15) \\
 &= 30 + j15 = 33.54/26.57^\circ \text{ V}
 \end{aligned}$$

$$v_o = 33.54 \cos(10,000t + 26.57^\circ) \text{ V}$$

$$\text{P 9.37 [a]} \quad Y_1 = \frac{1}{5000} = 0.2 \times 10^{-3} \text{ S}$$

$$\begin{aligned}
 Y_2 &= \frac{1}{1200 + j0.2\omega} \\
 &= \frac{1200}{1.44 \times 10^6 + 0.04\omega^2} - j\frac{0.2\omega}{1.44 \times 10^6 + 0.04\omega^2}
 \end{aligned}$$

$$Y_3 = j\omega 50 \times 10^{-9}$$

$$Y_T = Y_1 + Y_2 + Y_3$$

For  $i_g$  and  $v_o$  to be in phase the  $j$  component of  $Y_T$  must be zero; thus,

$$\omega 50 \times 10^{-9} = \frac{0.2\omega}{1.44 \times 10^6 + 0.04\omega^2}$$

or

$$0.04\omega^2 + 1.44 \times 10^6 = \frac{0.2 \times 10^9}{50} = 4 \times 10^6$$

$$\therefore 0.04\omega^2 = 2.56 \times 10^6 \quad \therefore \omega = 8000 \text{ rad/s} = 8 \text{ krad/s}$$

$$[\text{b}] Y_T = 0.2 \times 10^{-3} + \frac{1200}{1.44 \times 10^6 + 0.04(64) \times 10^6} = 0.5 \times 10^{-3} \text{ S}$$

$$\therefore Z_T = 2000 \Omega$$

$$\mathbf{V}_o = (2.5 \times 10^{-3} \angle 0^\circ)(2000) = 5 \angle 0^\circ$$

$$v_o = 5 \cos 8000t \text{ V}$$

$$\text{P 9.38 } [\text{a}] Z_p = \frac{\frac{R}{j\omega C}}{R + (1/j\omega C)} = \frac{R}{1 + j\omega RC}$$

$$= \frac{12,500}{1 + j(1000)(12,500)C} = \frac{12,500}{1 + j12.5 \times 10^6 C}$$

$$= \frac{12,500(1 - j12.5 \times 10^6 C)}{1 + 156.25 \times 10^{12} C^2}$$

$$= \frac{12,500}{1 + 156.25 \times 10^{12} C^2} - j \frac{156.25 \times 10^9 C}{1 + 156.25 \times 10^{12} C^2}$$

$$j\omega L = j1000(5) = j5000$$

$$\therefore 5000 = \frac{156.25 \times 10^9 C}{1 + 156.25 \times 10^{12} C^2}$$

$$\therefore 781.25 \times 10^{15} C^2 - 156.25 \times 10^9 C + 5000 = 0$$

$$\therefore C^2 - 20 \times 10^{-8} C + 64 \times 10^{-16} = 0$$

$$\therefore C_{1,2} = 10 \times 10^{-8} \pm \sqrt{100 \times 10^{-16} - 64 \times 10^{-16}}$$

$$C_1 = 10 \times 10^{-8} + 6 \times 10^{-8} = 16 \times 10^{-8} = 0.16 \mu\text{F}$$

$$C_2 = 10 \times 10^{-8} - 6 \times 10^{-8} = 4 \times 10^{-8} = 0.04 \mu\text{F}$$

$$[\text{b}] R_e = \frac{12,500}{1 + 156.25 \times 10^{12} C^2}$$

$$\text{When } C = 160 \text{ nF} \quad R_e = 2500 \Omega;$$

$$\mathbf{I}_g = \frac{250 \angle 0^\circ}{2500} = 0.1 \angle 0^\circ \text{ A}; \quad i_g = 100 \cos 1000t \text{ mA}$$

$$\text{When } C = 40 \text{ nF} \quad R_e = 10,000 \Omega;$$

$$\mathbf{I}_g = \frac{250 \angle 0^\circ}{10,000} = 0.025 \angle 0^\circ \text{ A}; \quad i_g = 25 \cos 1000t \text{ mA}$$



$$\text{P 9.39 [a]} \quad Z_1 = 1600 - j \frac{10^9}{10^4(62.5)} = 1600 - j1600 \Omega$$

$$Z_1 = \frac{4000(j10^4L)}{4000 + j10^4L} = \frac{4 \times 10^5 L^2 + j16 \times 10^4 L}{16 + 100L^2}$$

$$Z_T = Z_1 + Z_2 = 1600 + \frac{4 \times 10^5 L^2}{16 + 100L^2} - j1600 + j \frac{16 \times 10^4 L}{16 + 100L^2}$$

$Z_T$  is resistive when

$$\frac{16 \times 10^4 L}{16 + 100L^2} = 1600 \quad \text{or}$$

$$L^2 - L + 0.16 = 0$$

Solving,  $L_1 = 0.8$  H and  $L_2 = 0.2$  H.

[b] When  $L = 0.8$  H:

$$Z_T = 1600 + \frac{4 \times 10^5(0.64)}{16 + 64} = 4800 \Omega$$

$$\mathbf{I}_g = \frac{96/0^\circ}{4.8} \times 10^{-3} = 20/0^\circ \text{ mA}$$

$$i_g = 20 \cos 10,000t \text{ mA}$$

When  $L = 0.2$  H:

$$Z_T = 1600 + \frac{4 \times 10^5(0.04)}{16 + 4} = 2400 \Omega$$

$$i_g = 40 \cos 10,000t \text{ mA}$$

P 9.40 Step 1 to Step 2:





$$\frac{75/0^\circ}{j18} = -j4.167 = 4.167/-90^\circ \text{ A}$$

Step 2 to Step 3:

$$(j18) \parallel 24 = \frac{(j18)(24)}{24 + j18} = 8.64 + j11.52 \Omega$$

Step 3 to Step 4:
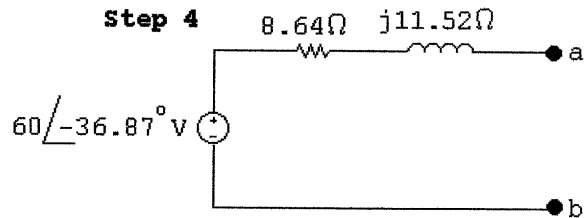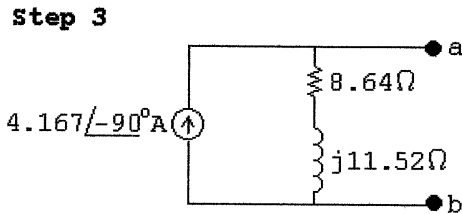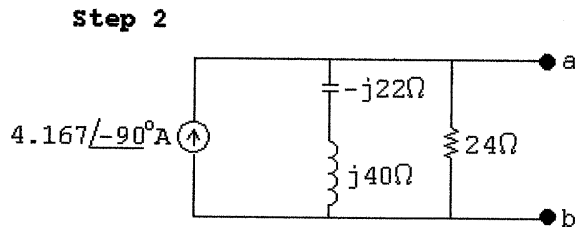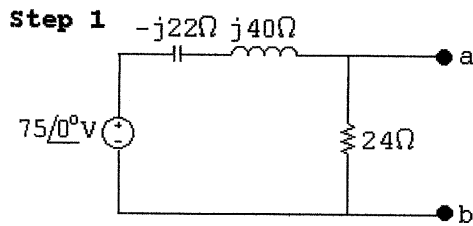
$$(4.167/-90^\circ)(8.64 + j11.52) = 60/-36.87^\circ \text{ V}$$



P 9.41 Step 1 to Step 2:

$$(16/0^\circ)(25) = 400/0^\circ \text{ V}$$

Step 2 to Step 3:






$$25 + 15 + j30 = (40 + j30) \Omega$$

Step 3 to Step 4:

$$\frac{400/0^\circ}{(40 + j30)} = 8/-36.87^\circ \text{ A}$$


Step 4 to Step 5:
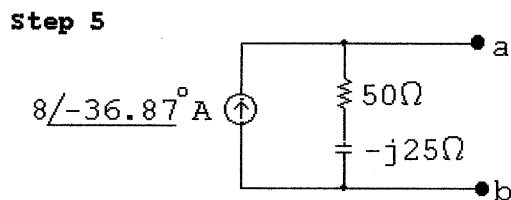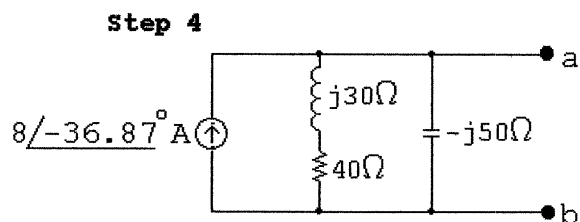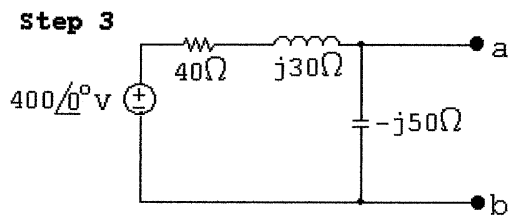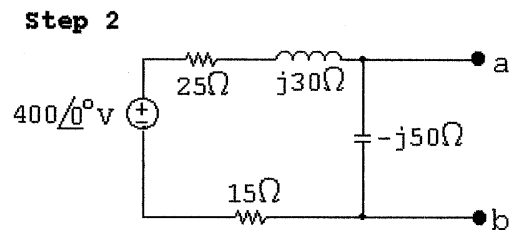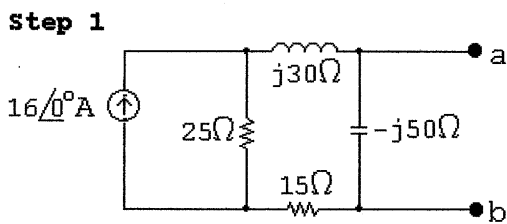
$$(40 + j30 \parallel -j50) = \frac{(-j50)(40 + j30)}{40 + j30 - j50} = 50 - j25 \Omega$$



P 9.42 [a]  $j\omega L = j(5000)(50) \times 10^{-3} = j250 \Omega$
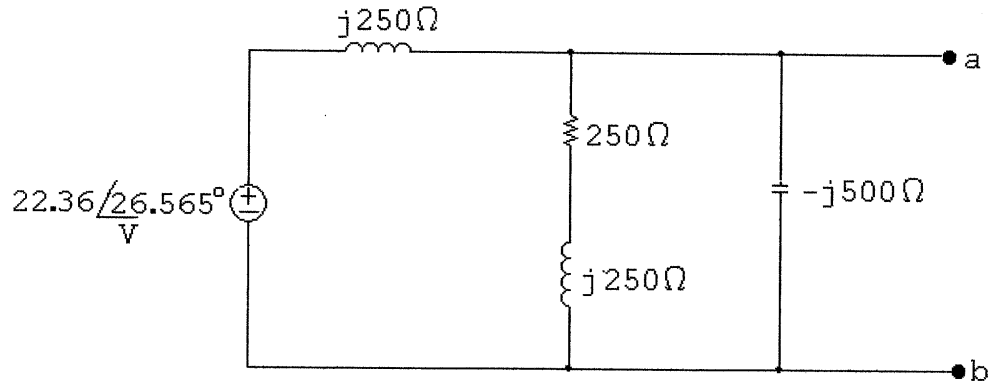
$$\frac{1}{j\omega C} = -j \frac{1}{(5000)(400 \times 10^{-9})} = -j500 \Omega$$



Using voltage division,

$$\mathbf{V}_{ab} = \frac{(250 + j250) \parallel (-j500)}{j250 + (250 + j250) \parallel (-j500)} (23.36 / 26.565^\circ) = 20 / 0^\circ$$

$$\mathbf{V}_{Th} = \mathbf{V}_{ab} = 20 / 0^\circ \text{ V}$$


[b] Remove the voltage source and combine impedances in parallel to find

$$Z_{Th} = Z_{ab}:$$


$$Y_{ab} = \frac{1}{j250} + \frac{1}{250 + j250} + \frac{1}{-j500} = 2 - j4 \text{ mS}$$

$$Z_{Th} = Z_{ab} = \frac{1}{Y_{ab}} = 100 + j200 \Omega$$

[c]

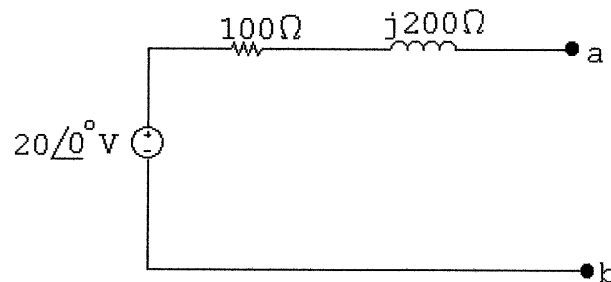

P 9.43

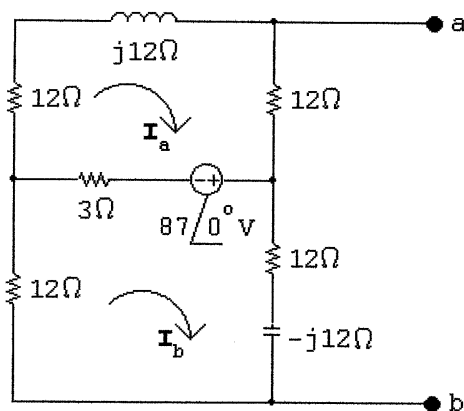

$$(27 + j12)\mathbf{I}_a - 3\mathbf{I}_b = -87\angle 0^\circ$$


$$-3\mathbf{I}_a + (27 - j12)\mathbf{I}_b = 87\angle 0^\circ$$

Solving,

$$\mathbf{I}_a = -2.4167 + j1.21; \quad \mathbf{I}_b = 2.4167 + j1.21$$

$$\mathbf{V}_{Th} = 12\mathbf{I}_a + (12 - j12)\mathbf{I}_b = 14.5\angle 0^\circ \text{ V}$$

Short Circuit Test:

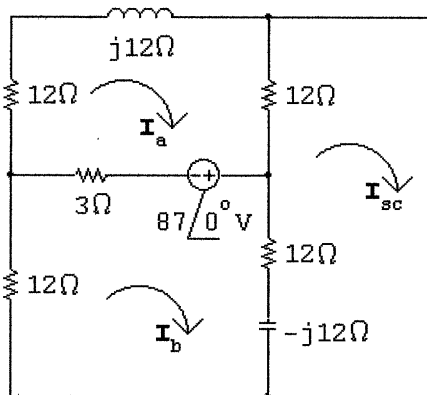

$$(27 + j12)\mathbf{I}_a - 3\mathbf{I}_b - 12\mathbf{I}_{sc} = -87$$

$$-3\mathbf{I}_a + (27 - j12)\mathbf{I}_b - (12 - j12)\mathbf{I}_{sc} = 87$$


$$-12\mathbf{I}_a - (12 - j12)\mathbf{I}_b + (24 - j12)\mathbf{I}_{sc} = 0$$

Solving,

$$\mathbf{I}_{sc} = 1\angle 0^\circ$$

$$Z_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{14.5/0^\circ}{1/0^\circ} = 14.5 \Omega$$

Alternate calculation for  $Z_{Th}$ :

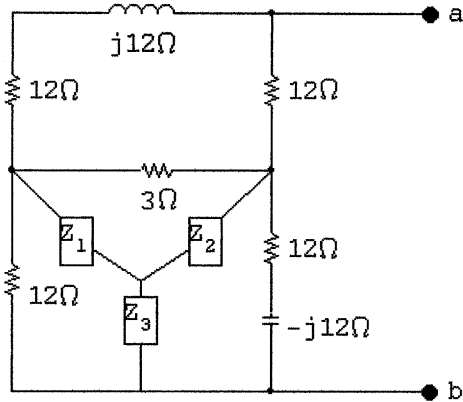


$$\sum Z = 12 + 3 + 12 - j12 = 27 - j12$$

$$Z_1 = \frac{36}{27 - j12} = \frac{12}{9 - j4}$$

$$Z_2 = \frac{36 - j36}{27 - j12} = \frac{12 - j12}{9 - j4}$$
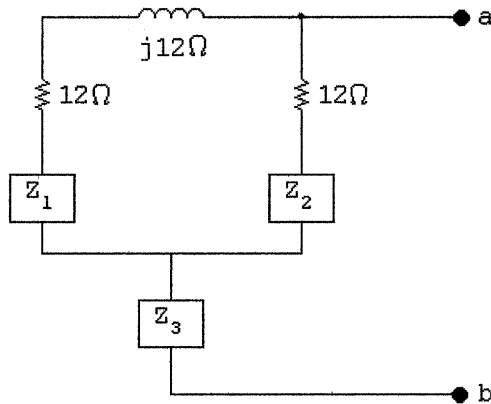
$$Z_3 = \frac{12(12 - j12)}{27 - j12} = \frac{48 - j48}{9 - j4}$$




$$Z_a = 12 + j12 + \frac{12}{9 - j4} = \frac{12(14 + j5)}{9 - j4}$$

$$Z_b = 12 + \frac{12 - j12}{9 - j4} = \frac{12(10 - j5)}{9 - j4}$$


$$Z_a \parallel Z_b = \frac{165 - j20}{18 - j8}$$

$$Z_3 + Z_a \parallel Z_b = \frac{48 - j48}{9 - j4} + \frac{165 - j20}{18 - j8} = 14.5 \Omega$$

P 9.44

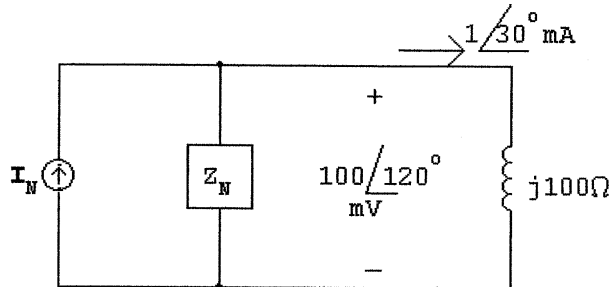
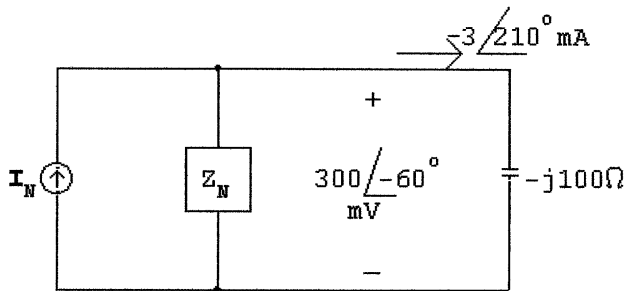
$$I_N = \frac{0.1 \angle 120^\circ}{Z_N} + 1 \angle 30^\circ \text{ mA}, \quad Z_N \text{ in k}\Omega$$




$$I_N = \frac{0.3 \angle -60^\circ}{Z_N} + (-3 \angle 210^\circ) \text{ mA}, \quad Z_N \text{ in k}\Omega$$

$$\frac{0.1 \angle 120^\circ}{Z_N} + 1 \angle 30^\circ = \frac{0.3 \angle -60^\circ}{Z_N} + (-3 \angle 210^\circ)$$

$$\frac{0.3 \angle -60^\circ - 0.1 \angle 120^\circ}{Z_N} = 1 \angle 30^\circ + 3 \angle 210^\circ$$


$$Z_N = \frac{0.3 \angle -60^\circ - 0.1 \angle 120^\circ}{1 \angle 30^\circ + 3 \angle 210^\circ} = 0.2 \angle 90^\circ = j0.2 \text{ k}\Omega$$
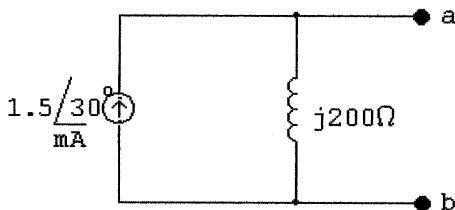
$$I_N = \frac{0.1 \angle 120^\circ}{0.2 \angle 90^\circ} + 1 \angle 30^\circ = 1.5 \angle 30^\circ \text{ mA}$$



$$P\ 9.45 \quad j\omega L = j1.6 \times 10^6(25 \times 10^{-6}) = j40\ \Omega$$
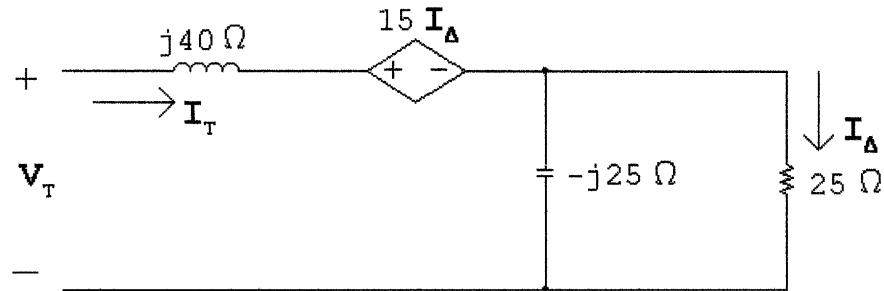
$$\frac{1}{j\omega C} = \frac{10^{-6} \times 10^9}{j1.6(25)} = -j25\ \Omega$$



$$V_T = j40I_T + 15I_\Delta + 25I_\Delta$$


$$I_\Delta = \frac{I_T(-j25)}{25 - j25} = \frac{-jI_T}{1 - j1}$$

$$V_T = j40I_T + 40 \frac{(-jI_T)}{1 - j1}$$

$$\frac{V_T}{I_T} = Z_{ab} = j40 + 20(-j)(1 + j) = 20 + j20\ \Omega = 28.28/\underline{45^\circ}\ \Omega$$

$$P\ 9.46 \quad \frac{1}{\omega C_1} = \frac{(10^{-3})(10^9)}{25(10/3)} = 12\ \text{k}\Omega$$

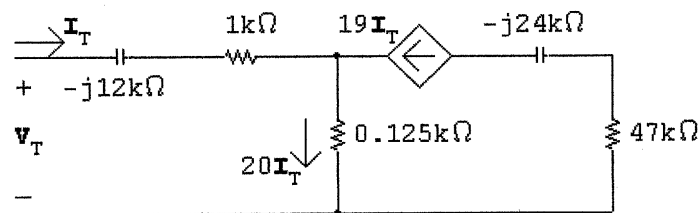
$$\frac{1}{\omega C_2} = \frac{(10^{-3})(10^9)}{25(5/3)} = 24\ \text{k}\Omega$$



$$V_T = (1 - j12)I_T + 20I_T(0.125)$$

$$Z_{Th} = \frac{V_T}{I_T} = 3.5 - j12\ \text{k}\Omega$$

P 9.47 Short circuit current

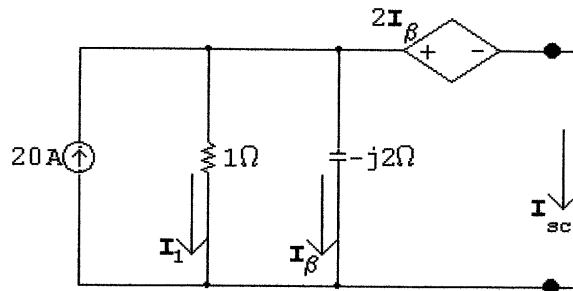


$$I_{\beta} = \frac{2I_{\beta}}{-j2}$$

$$-j2I_{\beta} = 2I_{\beta}; \quad \therefore I_{\beta} = 0$$

$$I_1 = 0; \quad \therefore I_{sc} = 20 \text{ A} = I_N$$

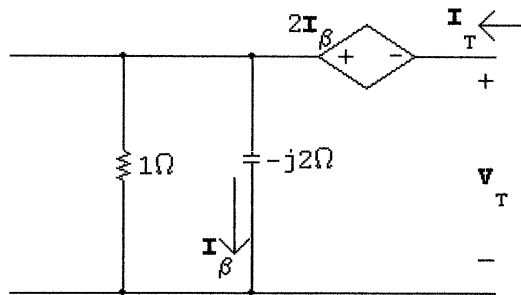
The Norton impedance is the same as the Thévenin impedance. Find it using a test source



$$V_T = -2I_{\beta} - j2I_{\beta} = (-2 - j2)I_{\beta}, \quad I_{\beta} = \frac{1}{1 - j2}I_T$$

$$Z_{Th} = \frac{V_T}{I_T} = \frac{(-2 - j2)I_{\beta}}{[(1 - j2)/1]I_{\beta}} = \frac{-2 - j2}{1 - j2} = 0.4 - j1.2 \Omega$$

P 9.48

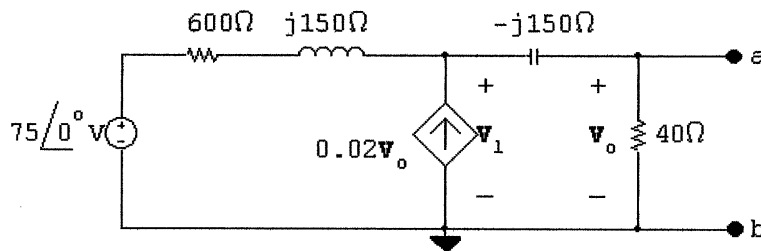

$$\frac{V_1 - 75}{150(4 + j1)} - \frac{0.02V_1(40)}{40 - j150} + \frac{V_1}{40 - j150} = 0$$




$$\therefore \mathbf{V}_1 = \frac{75(4 - j15)}{16 - j12}$$


$$\begin{aligned} \mathbf{V}_{\text{Th}} &= \frac{40\mathbf{V}_1}{40 - j150} = \frac{4}{4 - j15} \cdot \frac{75(4 - j15)}{16 - j12} \\ &= \frac{75}{4 - j3} = 15/\underline{36.87^\circ} \text{ V} \end{aligned}$$

$$\mathbf{I}_{\text{sc}} = \frac{75}{600} = \frac{1}{8} \text{ A}$$
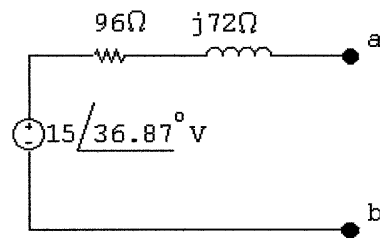
$$\mathbf{Z}_{\text{Th}} = \frac{\mathbf{V}_{\text{Th}}}{\mathbf{I}_{\text{sc}}} = 120/\underline{36.87^\circ} = 96 + j72 \Omega$$



P 9.49

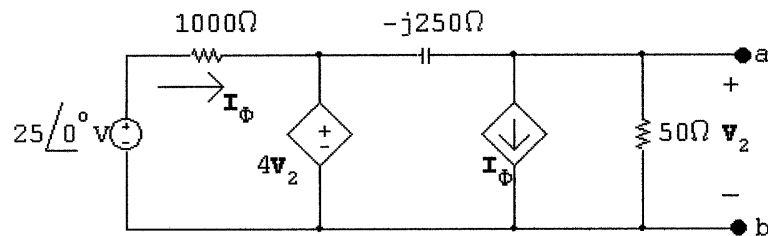

$$\frac{\mathbf{V}_2}{50} + \frac{25 - 4\mathbf{V}_2}{1000} + \frac{\mathbf{V}_2 - 4\mathbf{V}_2}{-j250} = 0$$

Solving,


$$\mathbf{V}_2 = -1 - j0.75 \text{ V} = 1.25/\underline{216.87^\circ} \text{ V}$$

$$\mathbf{I}_{\text{sc}} = -\mathbf{I}_\phi = \frac{-25/0^\circ}{1000} = -25/0^\circ \text{ mA}$$


$$\mathbf{Z}_{\text{Th}} = \frac{1.25/\underline{216.87^\circ}}{-25 \times 10^{-3}/0^\circ} = 50/\underline{36.87^\circ} \Omega = 40 + j30 \Omega$$

$$\mathbf{I}_N = \mathbf{I}_{\text{sc}} = -25/0^\circ \text{ mA}$$
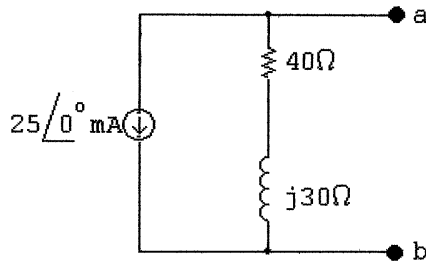
$$Z_N = Z_{Th} = 50/\underline{36.87^\circ} = 40 + j30 \Omega$$



P 9.50 [a]

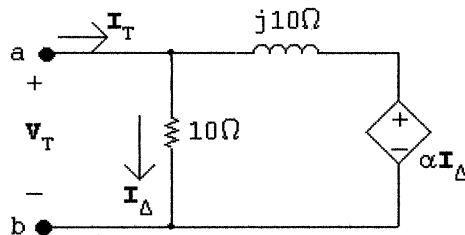

$$I_T = \frac{V_T}{10} + \frac{V_T - \alpha V_T/10}{j10}$$

$$\frac{I_T}{V_T} = \frac{1}{10} + \frac{(1 - \alpha/10)}{j10} = \frac{(10 - \alpha) + j10}{j100}$$

$$\therefore Z_{Th} = \frac{V_T}{I_T} = \frac{1000 + j100(10 - \alpha)}{(10 - \alpha)^2 + 100}$$

 $Z_{Th}$  is real when  $\alpha = 10$ .

[b]  $Z_{Th} = \frac{1000}{100} = 10 \Omega$

[c]  $Z_{Th} = 5 + j5$

$$\frac{1000}{(10 - \alpha)^2 + 100} = 5; \quad (10 - \alpha)^2 = 100$$


$$\therefore 10 - \alpha = \pm 10; \quad \alpha = 10 \mp 10$$

$$\alpha = 0; \quad \alpha = 20$$

 But the  $j$  term can only equal the real term with  $\alpha = 0$ . Thus,  $\alpha = 0$ .

[d]  $Z_{Th}$  will be inductive when  $\alpha < 10$ .

P 9.51

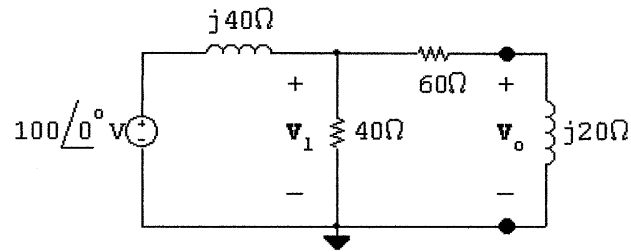

$$\frac{V_1 - 100}{j40} + \frac{V_1}{40} + \frac{V_1}{60 + j20} = 0$$

 Solving for  $V_1$  yields

$$V_1 = 30 - j40 \text{ V}$$

$$V_o = \frac{V_1}{60 + j20}(j20) = \left(\frac{j}{3 + j}\right) V_1$$


$$V_o = 15 + j5 \text{ V} = 15.81/18.43^\circ \text{ V}$$

 P 9.52  $j\omega L = j(5000)(0.4 \times 10^{-3}) = j2 \Omega$ 

$$\frac{1}{j\omega C} = -j \frac{10^6}{(5000)(50)} = -j4 \Omega$$

$$V_{g1} = 10/53.13^\circ = 6 + j8 \text{ V}$$

$$V_{g2} = 8/-90^\circ = -j8 \text{ V}$$

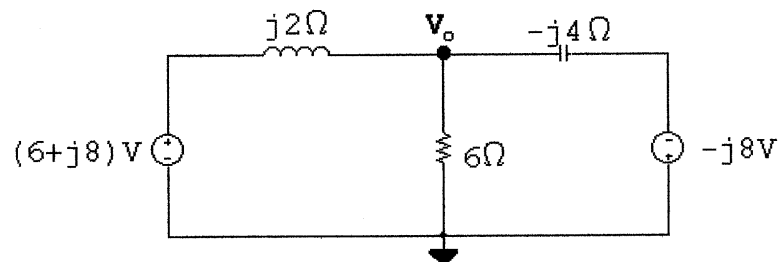

$$\frac{V_o - 6 - j8}{j2} + \frac{V_o}{6} + \frac{V_o + (-j8)}{-j4} = 0$$

Solving,

$$V_o = 12/0^\circ$$

$$v_o(t) = 12 \cos 5000t \text{ V}$$




$$P\ 9.53 \quad j\omega L = j10^4(1.2 \times 10^{-3}) = j12\ \Omega$$

$$\frac{1}{j\omega C} = \frac{-j10^6}{5 \times 10^4} = -j20\ \Omega$$

$$\mathbf{V}_a = 100/\underline{-90^\circ} = -j100\ \text{V}$$
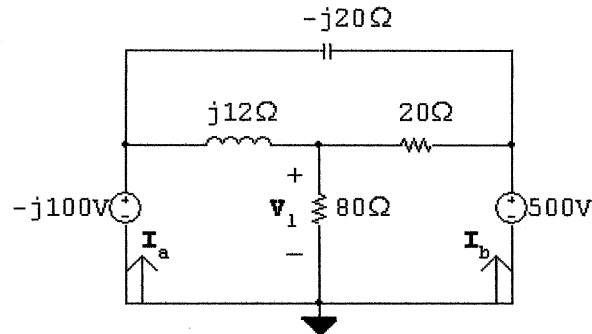
$$\mathbf{V}_b = 500/\underline{0^\circ} = 500\ \text{V}$$



$$\frac{\mathbf{V}_1}{80} + \frac{\mathbf{V}_1 - 500}{20} + \frac{\mathbf{V}_1 + j100}{j12} = 0$$

Solving,

$$\mathbf{V}_1 = 160/\underline{53.13^\circ}\ \text{V} = 96 + j128\ \text{V}$$


$$\begin{aligned} \mathbf{I}_a &= \frac{-j100 - 96 - j128}{j12} + \frac{-j100 - 500}{-j20} \\ &= -14 - j17 = 22.02/\underline{-129.47^\circ}\ \text{A} \end{aligned}$$

$$i_a = 22.02 \cos(10,000t - 129.47^\circ)\ \text{A}$$

$$\begin{aligned} \mathbf{I}_b &= \frac{500 - 96 - j128}{20} + \frac{500 + j100}{-j20} \\ &= 15.2 + j18.6 = 24.02/\underline{50.74^\circ}\ \text{A} \end{aligned}$$

$$i_b = 24.02 \cos(10,000t + 50.74^\circ)\ \text{A}$$

P 9.54

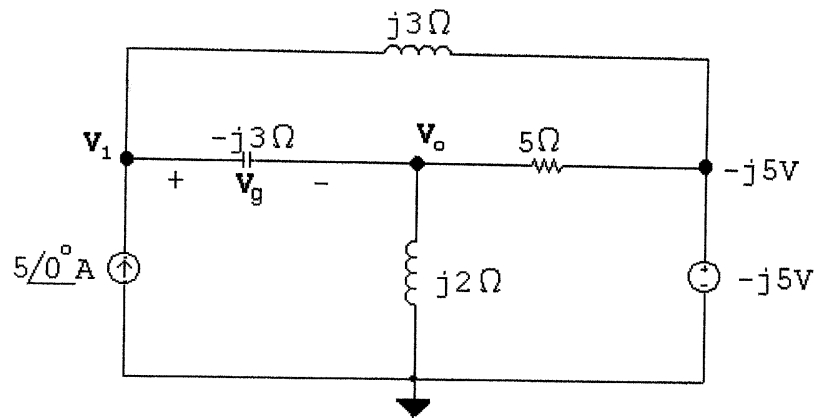

$$\frac{V_o}{j2} + \frac{V_o + j5}{5} + \frac{V_o - V_1}{-j3} = 0$$


$$(5 + j6)V_o + 10V_1 = 30$$

$$-5 + \frac{V_1 - V_o}{-j3} + \frac{V_1 + j5}{j3} = 0$$

$$V_o = j10; \quad V_1 = 9 - j5$$

$$V_g = V_1 - V_o = 9 - j5 - j10 = 9 - j15 = 17.49 \angle -59.04^\circ \text{ V}$$

P 9.55

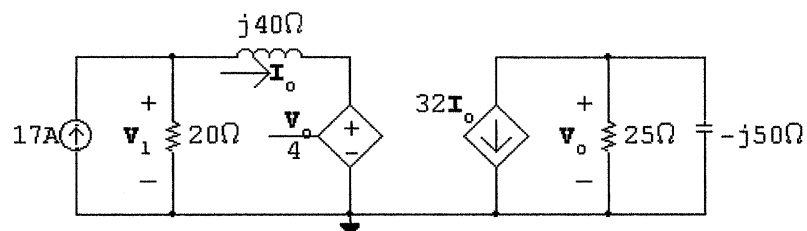

$$\frac{V_o}{25} + \frac{V_o}{-j50} + 32I_o = 0$$

$$(2 + j)V_o = -1600I_o$$

$$V_o = (-640 + j320)I_o$$

$$I_o = \frac{V_1 - (V_o/4)}{j40}$$

$$\therefore V_1 = (-160 + j120)I_o$$



$$17 = \frac{\mathbf{V}_1}{20} + \mathbf{I}_o = (-8 + j6)\mathbf{I}_o + \mathbf{I}_o = (-7 + j6)\mathbf{I}_o$$

$$\therefore \mathbf{I}_o = \frac{17}{(-7 + j6)} = -1.4 - j1.2 \text{ A} = 1.84 / -139.40^\circ \text{ A}$$

$$\mathbf{V}_o = (-640 + j320)\mathbf{I}_o = 1280 + j320 = 1319.39 / 14.04^\circ \text{ V}$$

P 9.56  $-15 / 0^\circ + \frac{\mathbf{V}_o}{8} + \frac{\mathbf{V}_o - 2.5\mathbf{I}_\Delta}{j5} + \frac{\mathbf{V}_o}{-j10} = 0$

$$\mathbf{I}_\Delta = \frac{\mathbf{V}_o}{-j10}$$


Solving,

$$\mathbf{V}_o = 72 + j96 = 120 / 53.13^\circ \text{ V}$$

P 9.57  $\mathbf{V}_a = 60 / 0^\circ \text{ V}; \quad \mathbf{V}_b = 90 / 90^\circ \text{ V}$

$$j\omega L = j(4 \times 10^4)(125 \times 10^{-6}) = j5 \Omega$$
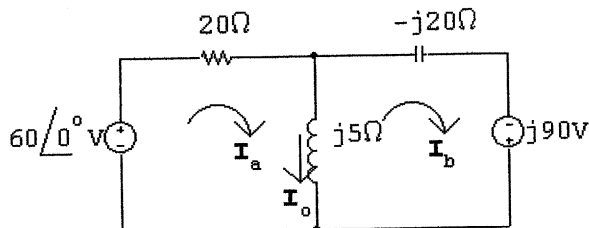
$$\frac{-j}{\omega C} = \frac{-j10^6}{40,000(1.25)} = -j20 \Omega$$



$$60 = (20 + j5)\mathbf{I}_a - j5\mathbf{I}_b$$

$$j90 = -j5\mathbf{I}_a - j15\mathbf{I}_b$$

Solving,


$$\mathbf{I}_a = 2.25 - j2.25 \text{ A}; \quad \mathbf{I}_b = -6.75 + j0.75 \text{ A}$$

$$\mathbf{I}_o = \mathbf{I}_a - \mathbf{I}_b = 9 - j3 = 9.49 / -18.43^\circ \text{ A}$$

$$i_o(t) = 9.49 \cos(40,000t - 18.43^\circ) \text{ A}$$



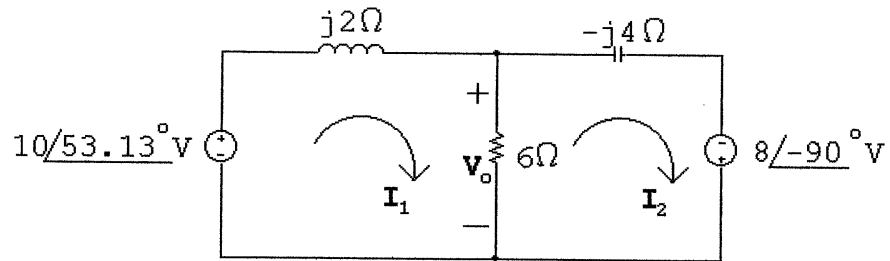P 9.58 From the solution to Problem 9.52 the phasor-domain circuit is



$$10/53.13^\circ = (6 + j2)\mathbf{I}_1 - 6\mathbf{I}_2$$

$$8/-90^\circ = -6\mathbf{I}_1 + (6 - j4)\mathbf{I}_2$$


$$\mathbf{V}_o = (\mathbf{I}_1 - \mathbf{I}_2)6$$

Solving,

$$\mathbf{V}_o = 12/0^\circ \text{ V}$$

$$v_o(t) = 12 \cos 5000t \text{ V}$$

P 9.59

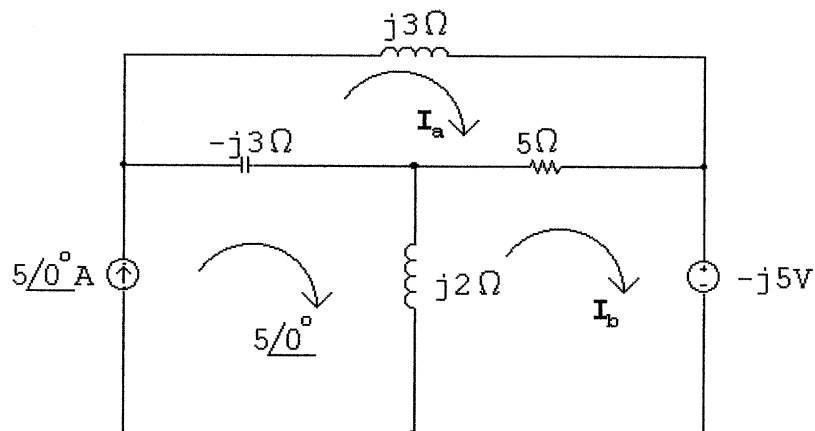


$$j3\mathbf{I}_a + 5(\mathbf{I}_a - \mathbf{I}_b) - j3(\mathbf{I}_a - 5) = 0$$

$$j2(\mathbf{I}_b - 5) + 5(\mathbf{I}_b - \mathbf{I}_a) - j5 = 0$$

Solving,

$$\mathbf{I}_a = -j3; \quad \mathbf{I}_b = -j3 = 3/-90^\circ \text{ A}$$

P 9.60

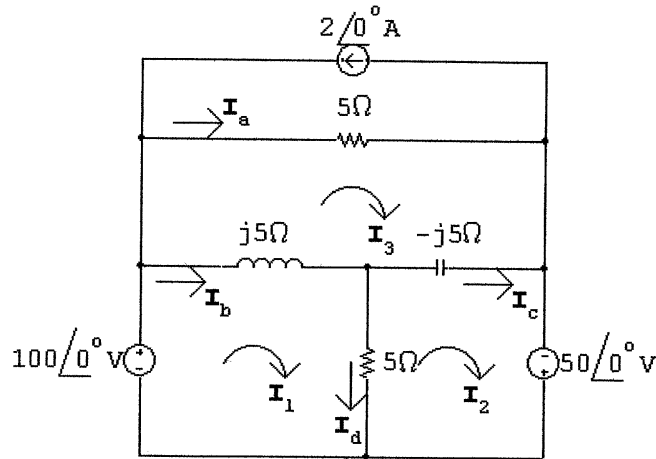

$$100\angle 0^\circ = (5 + j5)\mathbf{I}_1 - 5\mathbf{I}_2 - j5\mathbf{I}_3$$

$$50\angle 0^\circ = -5\mathbf{I}_1 + (5 - j5)\mathbf{I}_2 + j5\mathbf{I}_3$$

$$-10\angle 0^\circ = -j5\mathbf{I}_1 + j5\mathbf{I}_2 + 5\mathbf{I}_3$$

Solving,

$$\mathbf{I}_1 = 58 - j20 \text{ A}; \quad \mathbf{I}_2 = 58 + j10 \text{ A}; \quad \mathbf{I}_3 = 28 + j0 \text{ A}$$

$$\mathbf{I}_a = \mathbf{I}_3 + 2 = 30 + j0 \text{ A}$$


$$\mathbf{I}_b = \mathbf{I}_1 - \mathbf{I}_3 = 58 - j20 - 28 = 30 - j20 \text{ A}$$

$$\mathbf{I}_c = \mathbf{I}_2 - \mathbf{I}_3 = 58 + j10 - 28 = 30 + j10 \text{ A}$$

$$\mathbf{I}_d = \mathbf{I}_1 - \mathbf{I}_2 = 58 - j20 - 58 - j10 = -j30 \text{ A}$$

P 9.61  $j\omega L = j5000(14 \times 10^{-3}) = j70 \Omega$
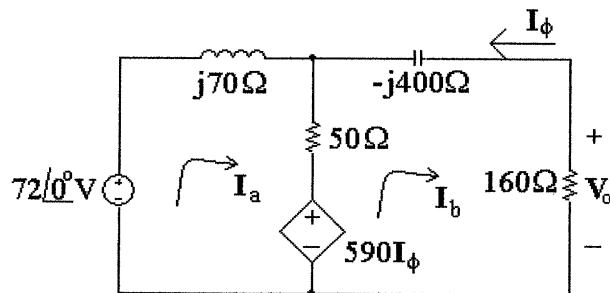
$$\frac{1}{j\omega C} = \frac{-j}{(5000)(0.5 \times 10^{-6})} = -j400 \Omega$$



$$72\angle 0^\circ = (50 + j70)\mathbf{I}_a - 50\mathbf{I}_b + 590(-\mathbf{I}_b)$$

$$0 = -50\mathbf{I}_a - 590(-\mathbf{I}_b) + (210 - j400)\mathbf{I}_b$$

Solving,

$$\mathbf{I}_b = (50 - j50) \text{ mA}$$

$$\mathbf{V}_o = 160\mathbf{I}_b = 8 - j8 = 11.31/\underline{-45^\circ}$$

$$v_o = 11.31 \cos(5000t - 45^\circ) \text{ V}$$

$$\text{P 9.62 } Z_o = 600 - j \frac{10^6}{(5000)(0.25)} = 600 - j800 \Omega$$

$$Z_T = 300 + j2000 + 600 - j800 = 900 + j1200 \Omega = 1500/\underline{53.13^\circ} \Omega$$

$$\mathbf{V}_o = \mathbf{V}_g \frac{Z_o}{Z_T} = \frac{(75/\underline{0^\circ})(1000/\underline{-53.13^\circ})}{1500/\underline{53.13^\circ}} = 50/\underline{-106.26^\circ} \text{ V}$$

$$v_o = 50 \cos(5000t - 106.26^\circ) \text{ V}$$

$$\text{P 9.63 } \frac{1}{j\omega C} = -j \frac{10^6}{10^4} = -j100 \Omega$$

$$j\omega L = j(500)(1) = j500 \Omega$$

$$\text{Let } Z_1 = 50 - j100 \Omega; \quad Z_2 = 250 + j500 \Omega$$

$$\mathbf{I}_g = 125/\underline{0^\circ} \text{ mA}$$

$$\begin{aligned} \mathbf{I}_o &= \frac{\mathbf{I}_g Z_1}{Z_1 + Z_2} = \frac{125/\underline{0^\circ}(50 - j100)}{(300 + j400)} \\ &= -12.5 - j25 \text{ mA} = 27.95/\underline{-116.57^\circ} \text{ mA} \end{aligned}$$

$$i_o = 27.95 \cos(500t - 116.57^\circ) \text{ mA}$$

$$\text{P 9.64 } \mathbf{V}_g = 1.2/\underline{0^\circ} \text{ V}; \quad \frac{1}{j\omega C} = \frac{10^6}{j100} = -j10 \text{ k}\Omega$$

Let  $\mathbf{V}_a$  = voltage across  $1 \mu\text{F}$  capacitor, positive at upper terminal  
Then:


$$\frac{\mathbf{V}_a - 1.2/\underline{0^\circ}}{10} + \frac{\mathbf{V}_a}{-j10} + \frac{\mathbf{V}_a}{10} = 0; \quad \therefore \mathbf{V}_a = (0.48 - j0.24) \text{ V}$$

$$\frac{0 - \mathbf{V}_a}{10} + \frac{0 - \mathbf{V}_o}{200} = 0; \quad \mathbf{V}_o = -20\mathbf{V}_a$$

$$\therefore \mathbf{V}_o = -9.6 + j4.8 = 10.73/\underline{153.43^\circ} \text{ V}$$

$$v_o = 10.73 \cos(100t + 153.43^\circ) \text{ V}$$

P 9.65 [a]

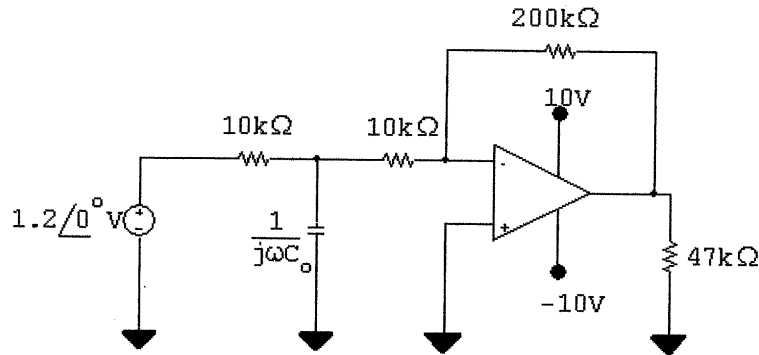

$$\frac{V_a - 1.2/0^\circ}{10,000} + j\omega C_o V_a + \frac{V_a}{10,000} = 0$$

$$V_a = \frac{1.2}{2 + j10^4 \omega C_o}$$

$$V_o = -20V_a \quad (\text{see solution to Prob. 9.73})$$

$$V_o = \frac{-24}{2 + j10^6 C_o} = \frac{24/180^\circ}{2 + j10^6 C_o}$$

$$\therefore \text{denominator angle} = 60^\circ$$

$$\tan 60^\circ = \sqrt{3}$$

$$\frac{10^6 C_o}{2} = \sqrt{3}$$

$$\text{or } C_o = \frac{2\sqrt{3}}{10^6} = 2\sqrt{3} \mu\text{F} = 3.46 \mu\text{F}$$

$$[\text{b}] V_o = \frac{24/180^\circ}{2 + j2\sqrt{3}} = 6/120^\circ \text{ V}$$

$$v_o = 6 \cos(100t + 120^\circ) \text{ V}$$

P 9.66 [a]  $V_g = 2/0^\circ \text{ V}$ 

$$V_p = \frac{80}{100} V_g = 1.6/0^\circ; \quad V_n = V_p = 1.6/0^\circ \text{ V}$$

$$\frac{1.6}{160} + \frac{1.6 - V_o}{Z_p} = 0$$

$$Z_p = \frac{(200)(1/j\omega C)}{200 + (1/j\omega C)}$$

$$\frac{1}{j\omega C} = \frac{10^9}{j10^5(0.1)} = -j10^5 = -j100 \text{ k}\Omega$$

$$Z_p = \frac{200(-j100)}{200 - j100} = 40 - j80 \text{ k}\Omega$$

$$\mathbf{V}_o = 1.6 + \frac{Z_p}{100} = 2 - j0.8 = 2.15 / -21.80^\circ$$

$$v_o = 2.15 \cos(10^5 t - 21.80^\circ) \text{ V}$$

[b]  $\mathbf{V}_p = 0.8V_m / 0^\circ$ ;  $\mathbf{V}_n = \mathbf{V}_p = 0.8V_m / 0^\circ$

$$\frac{0.8V_m}{160} + \frac{0.8V_m - \mathbf{V}_o}{40 - j80} = 0$$


$$\therefore \mathbf{V}_o = 0.8V_m + \frac{40 - j80}{160} V_m (0.8) = 0.8V_m (1.25 - j0.5)$$

$$\therefore |0.8V_m (1.25 - j0.5)| \leq 5$$

$$\therefore V_m \leq 4.64 \text{ V}$$

P 9.67  $\frac{1}{j\omega C_1} = \frac{10^{12}}{j10^6(100)} = -j10 \text{ k}\Omega$
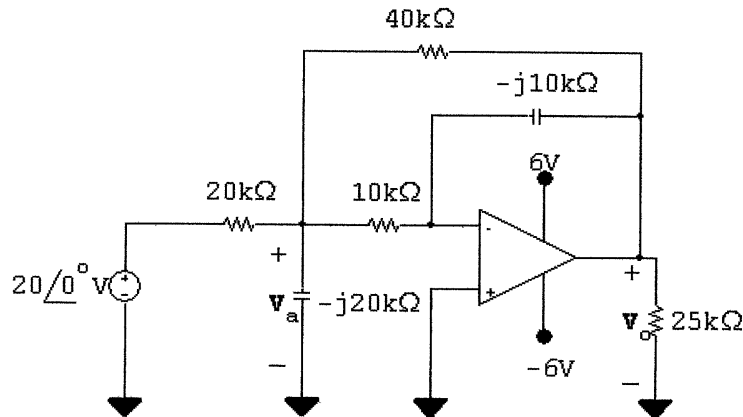
$$\frac{1}{j\omega C_2} = \frac{10^{12}}{j(10^6)(50)} = -j20 \text{ k}\Omega$$



$$\frac{\mathbf{V}_a}{-j20} + \frac{\mathbf{V}_a - 20}{20} + \frac{\mathbf{V}_a - \mathbf{V}_o}{40} + \frac{\mathbf{V}_a}{10} = 0$$

$$\therefore (-2 + j7)\mathbf{V}_a - j\mathbf{V}_o = j40$$

$$\frac{0 - \mathbf{V}_a}{10} + \frac{0 - \mathbf{V}_o}{-j10} = 0; \quad \therefore \mathbf{V}_a = -j\mathbf{V}_o$$

$$\therefore (7 + j)\mathbf{V}_o = j40$$

$$\mathbf{V}_o = \frac{j40}{7+j} = 0.8 + j5.6 = 5.657/81.87^\circ \text{ V}$$

$$v_o(t) = 5.657 \cos(10^6 t + 81.87^\circ) \text{ V}$$

P 9.68 [a]  $\frac{1}{j\omega C} = \frac{-j10^9}{(2 \times 10^5)(12.5)} = -j400 \Omega$

$$\frac{\mathbf{V}_n}{200} + \frac{\mathbf{V}_n - \mathbf{V}_o}{-j400} = 0$$

$$\frac{\mathbf{V}_o}{-j400} = \frac{\mathbf{V}_n}{200} + \frac{\mathbf{V}_n}{-j400}$$

$$\mathbf{V}_o = \mathbf{V}_n - j2\mathbf{V}_n = (1 - j2)\mathbf{V}_n$$

$$\mathbf{V}_p = \frac{\mathbf{V}_g(1/j\omega C_o)}{500 + (1/j\omega C_o)} = \frac{\mathbf{V}_g}{1 + j(500)(2 \times 10^5)C_o}$$

$$\mathbf{V}_g = 10/0^\circ \text{ V}$$

$$\mathbf{V}_p = \frac{10/0^\circ}{1 + j10^8 C_o} = \mathbf{V}_n$$

$$\therefore \mathbf{V}_o = \frac{(1 - j2)10/0^\circ}{1 + j10^8 C_o}$$

$$|\mathbf{V}_o| = \frac{\sqrt{5}(10)}{\sqrt{1 + 10^{16} C_o^2}} = 10$$


Solving,

$$C_o = 20 \text{ nF}$$

[b]  $\mathbf{V}_o = \frac{10(1 - j2)}{1 + j2} = 10/-126.87^\circ$

$$v_o = 10 \cos(2 \times 10^5 t - 126.87^\circ) \text{ V}$$

P 9.69 [a]

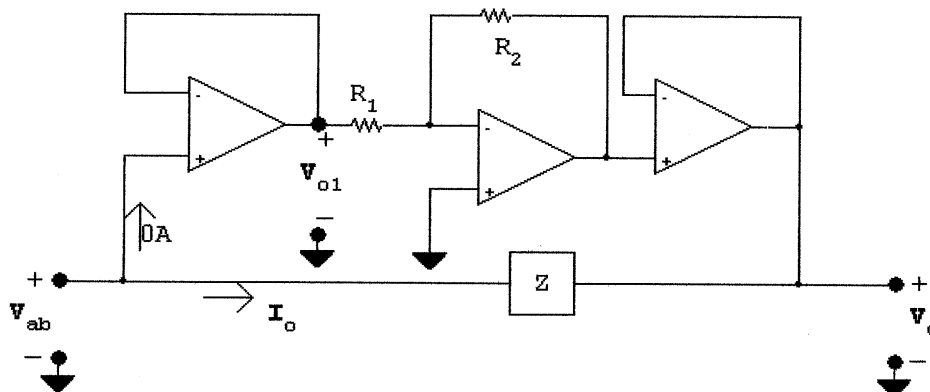

Because the op-amps are ideal  $I_{in} = I_o$ , thus

$$Z_{ab} = \frac{V_{ab}}{I_{in}} = \frac{V_{ab}}{I_o}; \quad I_o = \frac{V_{ab} - V_o}{Z}$$

$$V_{o1} = V_{ab}; \quad V_{o2} = -\left(\frac{R_2}{R_1}\right)V_{o1} = -KV_{o1} = -KV_{ab}$$

$$V_o = V_{o2} = -KV_{ab}$$


$$\therefore I_o = \frac{V_{ab} - (-KV_{ab})}{Z} = \frac{(1+K)V_{ab}}{Z}$$

$$\therefore Z_{ab} = \frac{V_{ab}}{(1+K)V_{ab}}Z = \frac{Z}{(1+K)}$$

$$[b] \quad Z = \frac{1}{j\omega C}; \quad Z_{ab} = \frac{1}{j\omega C(1+K)}; \quad \therefore C_{ab} = C(1+K)$$

P 9.70 [a] Superposition must be used because the frequencies of the two sources are different.

[b] For  $\omega = 80,000$  rad/s:

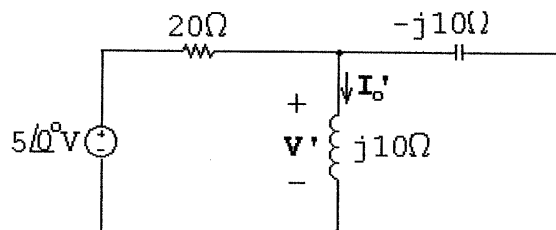


$$\frac{V_o' - 5}{20} + \frac{V_o'}{j10} + \frac{V_o'}{-j10} = 0$$

$$V_o' \left( \frac{1}{20} + \frac{1}{j10} + \frac{1}{-j10} \right) = \frac{5}{20}$$

$$\therefore V_o' = 5/0^\circ \text{ V}$$

$$I_o' = \frac{V_o'}{j10} = -j0.5 = 500/-90^\circ \text{ mA}$$

For  $\omega = 320,000$  rad/s:

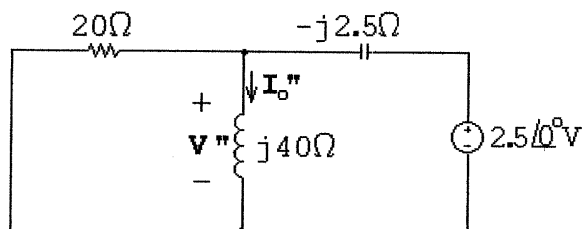

$$20 \parallel j40 = 16 + j8 \Omega$$

$$\mathbf{V}'' = \frac{16 + j8}{16 + j8 - j2.5} (2.5/0^\circ) = 2.643/7.59^\circ \text{ V}$$


$$\therefore \mathbf{I}_o'' = \frac{\mathbf{V}''}{j40} = 66.08/-82.4^\circ \text{ mA}$$

Thus,

$$i_o(t) = [500 \sin 80,000t + 66.08 \cos(320,000t - 82.4^\circ)] \text{ mA}, \quad t \geq 0$$


P 9.71 [a] Superposition must be used because the frequencies of the two sources are different.

[b] For  $\omega = 2000 \text{ rad/s}$ :

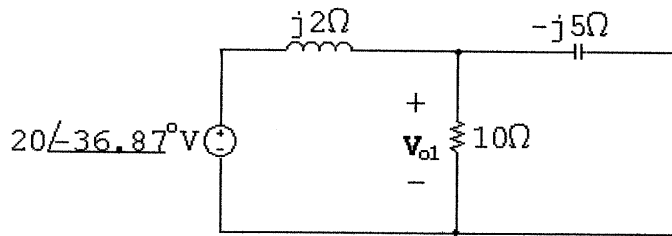

$$10 \parallel -j5 = 2 - j4 \Omega \quad \text{so} \quad \mathbf{V}_{o1} = \frac{2 - j4}{2 - j4 + j2} (20/-36.87^\circ) = 31.62/-55.3^\circ \text{ V}$$

For  $\omega = 5000 \text{ rad/s}$ :

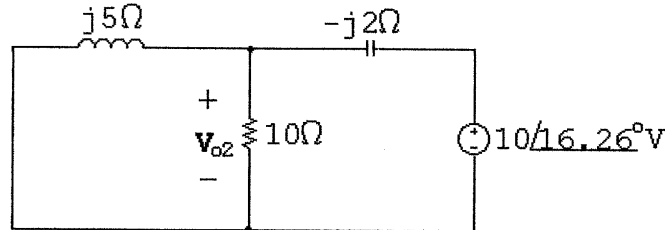

$$j5 \parallel 10 = 2 + j4 \Omega$$

$$\mathbf{V}_{o2} = \frac{2 + j4}{2 + j4 - j2} (10/16.26^\circ) = 15.81/34.69^\circ \text{ V}$$


Thus,

$$v_o(t) = [31.62 \cos(2000t - 55.3^\circ) + 15.81 \cos(5000t + 34.69^\circ)] \text{ V}, \quad t \geq 0$$

P 9.72 [a]  $j\omega L_1 = j\omega L_2 = j(10,000)(1 \times 10^{-3}) = j10 \Omega$
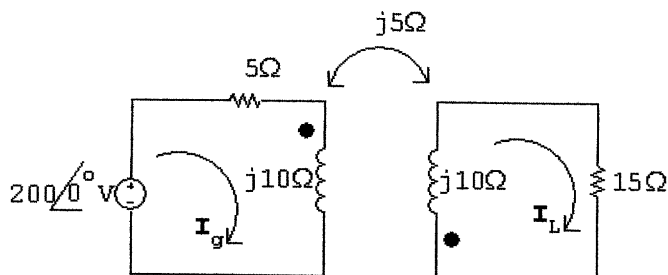
$$j\omega M = j(10,000)(0.5 \times 10^{-3}) = j5 \Omega$$





$$200 = (5 + j10)\mathbf{I}_g + j5\mathbf{I}_L$$

$$0 = j5\mathbf{I}_g + (15 + j10)\mathbf{I}_L$$

Solving,

$$\mathbf{I}_g = 10 - j15 \text{ A}; \quad \mathbf{I}_L = -5 \text{ A}$$

$$i_g = 18.03 \cos(10,000t - 56.31^\circ) \text{ A}$$

$$i_L = 5 \cos(10,000t - 180^\circ) \text{ A}$$

$$[\text{b}] \quad k = \frac{M}{\sqrt{L_1 L_2}} = \frac{0.5}{\sqrt{1}} = 0.5$$

[c] When  $t = 50\pi \mu\text{s}$ ,

$$10,000t = (10,000)(50\pi) \times 10^{-6} = 0.5\pi = \pi/2 \text{ rad} = 90^\circ$$

$$i_g(50\pi \mu\text{s}) = 18.03 \cos(90 - 56.31^\circ) = 15 \text{ A}$$

$$i_L(50\pi \mu\text{s}) = 5 \cos(90 + 180^\circ) = 0 \text{ A}$$

$$w = \frac{1}{2}L_1 i_1^2 + \frac{1}{2}L_2 i_2^2 + M i_1 i_2 = \frac{1}{2}(1 \times 10^{-3})(15)^2 + 0 + 0 = 112.5 \text{ mJ}$$

When  $t = 100\pi \mu\text{s}$ ,

$$10,000t = \pi \text{ rad} = 180^\circ$$

$$i_g(100\pi \mu\text{s}) = -10 \text{ A}$$

$$i_L(100\pi \mu\text{s}) = 5 \text{ A}$$

$$w = \frac{1}{2}(1 \times 10^{-3})(10)^2 + \frac{1}{2}(1 \times 10^{-3})(5)^2 + 0.5 \times 10^{-3}(-10)(5) = 37.5 \text{ mJ}$$

P 9.73 [a]  $j\omega L_1 = j(50)(5) = j250 \Omega$

$$j\omega L_2 = j(50)(20) = j1000 \Omega$$

$$\frac{1}{j\omega C} = \frac{10^9}{j(50 \times 10^3)(40)} = -j500 \Omega$$

$$\therefore Z_{22} = 75 + 300 + j1000 - j500 = 375 + j500 \Omega$$

$$\therefore Z_{22}^* = 375 - j500 \Omega$$

$$M = k\sqrt{L_1 L_2} = 10k \times 10^{-3}$$

$$\omega M = (50)(10k) = 500k$$

$$Z_r = \left[ \frac{500k}{625} \right]^2 (375 - j500) = k^2(240 - j320) \Omega$$

$$Z_{in} = 120 + j250 + 240k^2 - j320k^2$$

$$|Z_{in}| = [(120 + 240k^2)^2 + (250 - 320k^2)^2]^{\frac{1}{2}}$$

$$\frac{d|Z_{in}|}{dk} = \frac{1}{2}[(120 + 240k^2)^2 + (250 - 320k^2)^2]^{-\frac{1}{2}} \times$$

$$[2(120 + 240k^2)480k + 2(250 - 320k^2)(-640k)]$$

$$\frac{d|Z_{in}|}{dk} = 0 \text{ when}$$

$$960k(120 + 240k^2) - 1280k(250 - 320k^2) = 0$$

$$\therefore k^2 = 0.32; \quad \therefore k = \sqrt{0.32} = 0.5657$$

$$\begin{aligned} \text{[b]} \quad Z_{in}(\text{min}) &= 120 + 240(0.32) + j[250 - 0.32(320)] \\ &= 196.8 + j147.6 = 246/\underline{36.87^\circ} \Omega \end{aligned}$$

$$I_1(\text{max}) = \frac{369/\underline{0^\circ}}{246/\underline{36.87^\circ}} = 1.5/\underline{-36.87^\circ} \text{ A}$$

$$\therefore i_1(\text{peak}) = 1.5 \text{ A}$$

Note — You can test that the  $k$  value obtained from setting  $d|Z_{in}|/dt = 0$  leads to a minimum by noting  $0 \leq k \leq 1$ . If  $k = 1$ ,

$$Z_{in} = 360 - j70 = 366.74/\underline{-11^\circ} \Omega$$

Thus,

$$|Z_{in}|_{k=1} > |Z_{in}|_{k=\sqrt{0.32}}$$

If  $k = 0$ ,


$$Z_{in} = 120 + j250 = 277.31/\underline{64.36^\circ} \Omega$$

Thus,

$$|Z_{in}|_{k=0} > |Z_{in}|_{k=\sqrt{0.32}}$$

$$P\ 9.74\ Z_{Th} = 30 + j200 + (50/25)^2(15 - j20) = 90 + j120\ \Omega$$
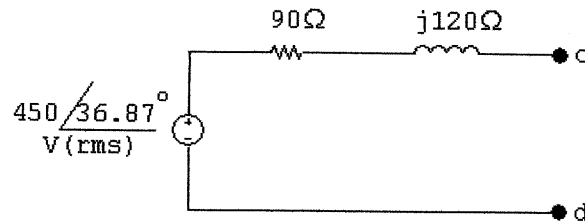
$$V_{Th} = \frac{225/0^\circ}{15 + j20}(j50) = 450/36.87^\circ\text{ V}$$



$$P\ 9.75\ j\omega L_1 = j(25 \times 10^3)(3.2 \times 10^{-3}) = j80\ \Omega$$

$$j\omega L_2 = j(25 \times 10^3)(12.8 \times 10^{-3}) = j320\ \Omega$$

$$\frac{1}{j\omega C} = \frac{10^9}{j(25 \times 10^3)(250)} = -j160\ \Omega$$

$$j\omega M = j(25 \times 10^3)k\sqrt{(3.2)(12.8)} \times 10^{-3} = j160k\ \Omega$$

$$Z_{22} = 40 + j320 - j160 = 40 + j160\ \Omega$$

$$Z_{22}^* = 40 - j160\ \Omega$$

$$Z_r = \left[ \frac{160k}{|40 + j160|} \right]^2 (40 - j160) = 37.647k^2 - j150.588k^2$$

$$Z_{ab} = 10 + j80 + 37.647k^2 - j150.588k^2 = (10 + 37.647k^2) + j(80 - 150.588k^2)$$

$Z_{ab}$  is resistive when

$$80 - 150.588k^2 = 0 \quad \text{or} \quad k^2 = 0.53125$$

$$\therefore Z_{ab} = 10 + (37.647)(0.53125) = 30\ \Omega$$

$$P\ 9.76\ [a]\ j\omega L_2 = j(500)10^3(500)10^{-6} = j250\ \Omega$$

$$\frac{1}{j\omega C} = \frac{10^9}{j(500 \times 10^3)(20)} = -j100\ \Omega$$

$$Z_{22} = 150 + 50 + j250 - j100 = 200 + j150\ \Omega$$

$$Z_{22}^* = 200 - j150\ \Omega$$

$$\omega M = (500 \times 10^3)(100 \times 10^{-6}) = 50\ \Omega$$


$$Z_r = \left( \frac{50}{250} \right)^2 [200 - j150] = 8 - j6\ \Omega$$

$$[b] Z_{ab} = R_1 + j\omega L_1 + 8 - j6$$

$$j\omega L_1 = j(500 \times 10^3)(80 \times 10^{-6}) = j40 \Omega$$

$$Z_{ab} = 20 + j34 \Omega$$

P 9.77

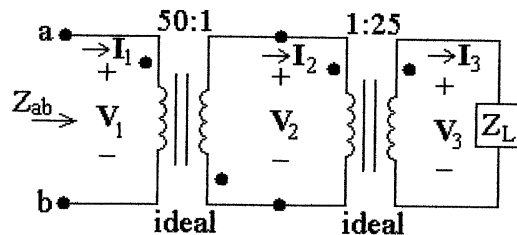

$$Z_{ab} = \frac{V_1}{I_1}$$

$$\frac{V_1}{50} = -\frac{V_2}{1}; \quad 50I_1 = -I_2$$

$$\therefore Z_{ab} = \frac{-50V_2}{-I_2/50} = 2500 \frac{V_2}{I_2}$$

$$\frac{V_2}{1} = \frac{V_3}{25}; \quad I_2 = 25I_3$$

$$\therefore Z_{ab} = 2500 \frac{V_3/25}{25I_3} = \frac{2500}{625} \frac{V_3}{I_3}$$

$$= 4Z_L = 4(200 + j150) = (800 + j600) \Omega$$

P 9.78 In Eq. 9.69 replace  $\omega^2 M^2$  with  $k^2 \omega^2 L_1 L_2$  and then write  $X_{ab}$  as

$$\begin{aligned} X_{ab} &= \omega L_1 - \frac{k^2 \omega^2 L_1 L_2 (\omega L_2 + \omega L_L)}{R_{22}^2 + (\omega L_2 + \omega L_L)^2} \\ &= \omega L_1 \left\{ 1 - \frac{k^2 \omega L_2 (\omega L_2 + \omega L_L)}{R_{22}^2 + (\omega L_2 + \omega L_L)^2} \right\} \end{aligned}$$

For  $X_{ab}$  to be negative requires

$$R_{22}^2 + (\omega L_2 + \omega L_L)^2 < k^2 \omega L_2 (\omega L_2 + \omega L_L)$$

or


$$R_{22}^2 + (\omega L_2 + \omega L_L)^2 - k^2 \omega L_2 (\omega L_2 + \omega L_L) < 0$$

which reduces to

$$R_{22}^2 + \omega^2 L_2^2(1 - k^2) + \omega L_2 \omega L_L(2 - k^2) + \omega^2 L_L^2 < 0$$

But  $k \leq 1$  hence it is impossible to satisfy the inequality. Therefore  $X_{ab}$  can never be negative if  $X_L$  is an inductive reactance.

P 9.79 [a]

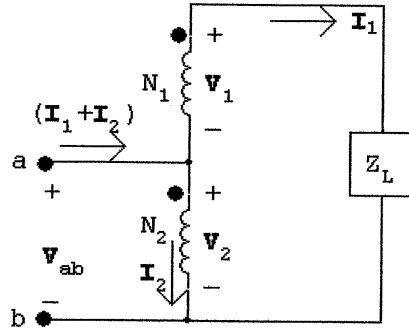

$$Z_{ab} = \frac{V_{ab}}{I_1 + I_2} = \frac{V_2}{I_1 + I_2} = \frac{V_2}{(1 + N_1/N_2)I_1}$$

$$N_1 I_1 = N_2 I_2, \quad I_2 = \frac{N_1}{N_2} I_1$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}, \quad V_1 = \frac{N_1}{N_2} V_2$$

$$V_1 + V_2 = Z_L I_1 = \left( \frac{N_1}{N_2} + 1 \right) V_2$$

$$Z_{ab} = \frac{I_1 Z_L}{(N_1/N_2 + 1)(1 + N_1/N_2)I_1}$$

$$\therefore Z_{ab} = \frac{Z_L}{[1 + (N_1/N_2)]^2} \quad \text{Q.E.D.}$$

[b] Assume dot on the  $N_2$  coil is moved to the lower terminal. Then

$$V_1 = -\frac{N_1}{N_2} V_2 \quad \text{and} \quad I_2 = -\frac{N_1}{N_2} I_1$$


As before

$$Z_{ab} = \frac{V_2}{I_1 + I_2} \quad \text{and} \quad V_1 + V_2 = Z_L I_1$$

$$\therefore Z_{ab} = \frac{V_2}{(1 - N_1/N_2)I_1} = \frac{Z_L I_1}{[1 - (N_1/N_2)]^2 I_1}$$

$$Z_{ab} = \frac{Z_L}{[1 - (N_1/N_2)]^2} \quad \text{Q.E.D.}$$

P 9.80 [a]

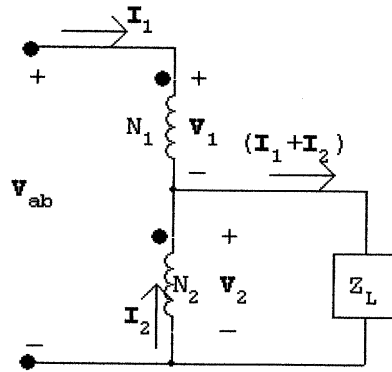

$$Z_{ab} = \frac{V_{ab}}{I_1} = \frac{V_1 + V_2}{I_1}$$

$$\frac{V_1}{N_1} = \frac{V_2}{N_2}, \quad V_2 = \frac{N_2}{N_1} V_1$$

$$N_1 I_1 = N_2 I_2, \quad I_2 = \frac{N_1}{N_2} I_1$$

$$V_2 = (I_1 + I_2) Z_L = I_1 \left(1 + \frac{N_1}{N_2}\right) Z_L$$

$$V_1 + V_2 = \left(\frac{N_1}{N_2} + 1\right) V_2 = \left(1 + \frac{N_1}{N_2}\right)^2 Z_L I_1$$

$$\therefore Z_{ab} = \frac{(1 + N_1/N_2)^2 Z_L I_1}{I_1}$$

$$Z_{ab} = \left(1 + \frac{N_1}{N_2}\right)^2 Z_L \quad \text{Q.E.D.}$$

[b] Assume dot on  $N_2$  is moved to the lower terminal, then

$$\frac{V_1}{N_1} = \frac{-V_2}{N_2}, \quad V_1 = \frac{-N_1}{N_2} V_2$$

$$N_1 I_1 = -N_2 I_2, \quad I_2 = \frac{-N_1}{N_2} I_1$$

As in part [a]

$$V_2 = (I_2 + I_1) Z_L \quad \text{and} \quad Z_{ab} = \frac{V_1 + V_2}{I_1}$$

$$Z_{ab} = \frac{(1 - N_1/N_2) V_2}{I_1} = \frac{(1 - N_1/N_2)(1 - N_1/N_2) Z_L I_1}{I_1}$$

$$Z_{ab} = [1 - (N_1/N_2)]^2 Z_L \quad \text{Q.E.D.}$$

P 9.81 [a]  $\mathbf{I} = \frac{240}{24} + \frac{240}{j32} = (10 - j7.5) \text{ A}$

$$\mathbf{V}_s = 240/0^\circ + (0.1 + j0.8)(10 - j7.5) = 247 + j7.25 = 247.11/1.68^\circ \text{ V}$$

[b] Use the capacitor to eliminate the  $j$  component of  $\mathbf{I}$ , therefore

$$\mathbf{I}_c = j7.5 \text{ A}, \quad Z_c = \frac{240}{j7.5} = -j32 \Omega$$

$$\mathbf{V}_s = 240 + (0.1 + j0.8)10 = 241 + j8 = 241.13/1.90^\circ \text{ V}$$

[c] Let  $I_c$  denote the magnitude of the current in the capacitor branch. Then

$$\mathbf{I} = (10 - j7.5 + jI_c) = 10 + j(I_c - 7.5) \text{ A}$$

$$\begin{aligned} \mathbf{V}_s &= 240/\alpha = 240 + (0.1 + j0.8)[10 + j(I_c - 7.5)] \\ &= (247 - 0.8I_c) + j(7.25 + 0.1I_c) \end{aligned}$$

It follows that

$$240 \cos \alpha = (247 - 0.8I_c) \quad \text{and} \quad 240 \sin \alpha = (7.25 + 0.1I_c)$$


Now square each term and then add to generate the quadratic equation

$$I_c^2 - 605.77I_c + 5325.48 = 0; \quad I_c = 302.88 \pm 293.96$$

Therefore


$$I_c = 8.92 \text{ A (smallest value)} \quad \text{and} \quad Z_c = 240/j8.92 = -j26.90 \Omega.$$

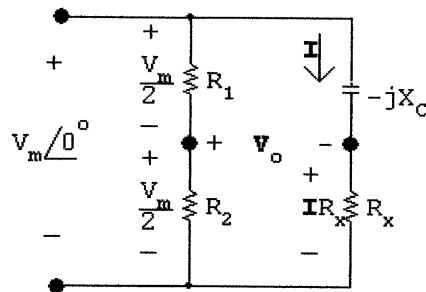P 9.82 The phasor domain equivalent circuit is




$$V_o = \frac{V_m}{2} - \mathbf{I}R_x; \quad \mathbf{I} = \frac{V_m}{R_x - jX_C}$$

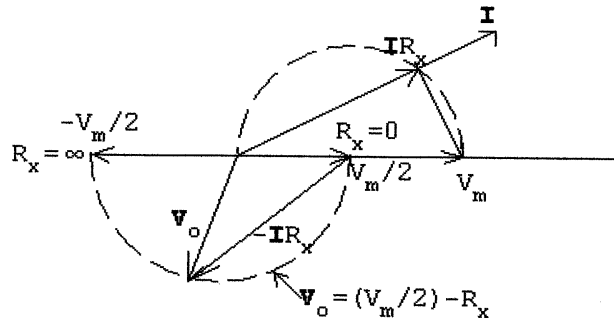As  $R_x$  varies from 0 to  $\infty$ , the amplitude of  $v_o$  remains constant and its phase angle increases from  $0^\circ$  to  $-180^\circ$ , as shown in the following phasor diagram:



P 9.83 [a]

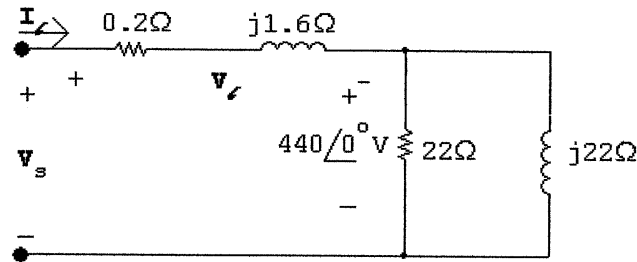


$$I_l = \frac{440}{22} + \frac{440}{j22} = 20 - j20 \text{ A}$$

$$V_l = (0.2 + j1.6)(20 - j20) = 36 + j28 = 45.61/37.87^\circ \text{ V(rms)}$$

$$V_s = 440/0^\circ + V_l = 476 + j28 = 476.82/3.37^\circ \text{ V}$$


[b]

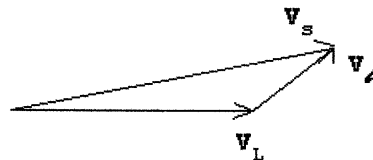

$$[c] I_l = \frac{440}{22} + \frac{440}{j22} + \frac{440}{-j22} = 20 + j0 \text{ A}$$

$$V_l = (0.2 + j1.6)(20 + j0) = 4 + j32 = 32.25/82.87^\circ$$
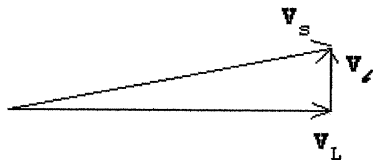
$$V_s = 440 + V_l = 444 + j32 = 445.15/4.12^\circ$$





$$\text{P 9.84 [a] } \mathbf{I}_1 = \frac{120}{24} + \frac{240}{8.4 + j6.3} = 23.29 - j13.71 = 27.02/\underline{-30.5^\circ} \text{ A}$$

$$\mathbf{I}_2 = \frac{120}{12} - \frac{120}{24} = 5/\underline{0^\circ} \text{ A}$$

$$\mathbf{I}_3 = \frac{120}{12} + \frac{240}{8.4 + j6.3} = 28.29 - j13.71 = 31.44/\underline{-25.87^\circ} \text{ A}$$

$$\mathbf{I}_4 = \frac{120}{24} = 5/\underline{0^\circ} \text{ A}; \quad \mathbf{I}_5 = \frac{120}{12} = 10/\underline{0^\circ} \text{ A}$$

$$\mathbf{I}_6 = \frac{240}{8.4 + j6.3} = 18.29 - j13.71 = 22.86/\underline{-36.87^\circ} \text{ A}$$

[b] When fuse A is interrupted,

$$\mathbf{I}_1 = 0 \qquad \mathbf{I}_3 = 15 \text{ A} \qquad \mathbf{I}_5 = 10 \text{ A}$$


$$\mathbf{I}_2 = 10 + 5 = 15 \text{ A} \qquad \mathbf{I}_4 = -5 \text{ A} \qquad \mathbf{I}_6 = 5 \text{ A}$$

[c] The clock and television set were fed from the uninterrupted side of the circuit, that is, the  $12\ \Omega$  load includes the clock and the TV set.

[d] No, the motor current drops to 5 A, well below its normal running value of 22.86 A.

[e] After fuse A opens, the current in fuse B is only 15 A.

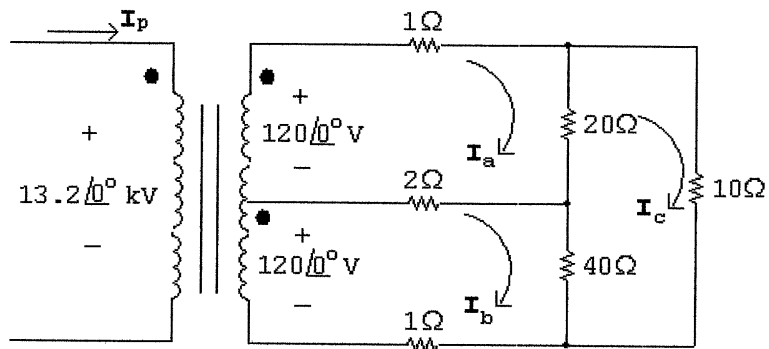P 9.85 [a] The circuit is redrawn, with mesh currents identified:



The mesh current equations are:

$$120/\underline{0^\circ} = 23\mathbf{I}_a - 2\mathbf{I}_b - 20\mathbf{I}_c$$

$$120/\underline{0^\circ} = -2\mathbf{I}_a + 43\mathbf{I}_b - 40\mathbf{I}_c$$

$$0 = -20\mathbf{I}_a - 40\mathbf{I}_b + 70\mathbf{I}_c$$

Solving,

$$\mathbf{I}_a = 24/\underline{0^\circ} \text{ A}$$

$$\mathbf{I}_b = 21.96/\underline{0^\circ} \text{ A}$$

$$\mathbf{I}_c = 19.40/\underline{0^\circ} \text{ A}$$

The branch currents are:

$$\mathbf{I}_1 = \mathbf{I}_a = 24/0^\circ \text{ A}$$

$$\mathbf{I}_2 = \mathbf{I}_a - \mathbf{I}_b = 2.04/0^\circ \text{ A}$$

$$\mathbf{I}_3 = \mathbf{I}_b = 21.96/0^\circ \text{ A}$$

$$\mathbf{I}_4 = \mathbf{I}_c = 19.40/0^\circ \text{ A}$$

$$\mathbf{I}_5 = \mathbf{I}_a - \mathbf{I}_c = 4.6/0^\circ \text{ A}$$

$$\mathbf{I}_6 = \mathbf{I}_b - \mathbf{I}_c = 2.55/0^\circ \text{ A}$$

[b] Let  $N_1$  be the number of turns on the primary winding; because the secondary winding is center-tapped, let  $2N_2$  be the total turns on the secondary. From Fig. 9.58,

$$\frac{13,200}{N_1} = \frac{240}{2N_2} \quad \text{or} \quad \frac{N_2}{N_1} = \frac{1}{110}$$


The ampere turn balance requires

$$N_1 \mathbf{I}_p = N_2 \mathbf{I}_1 + N_2 \mathbf{I}_3$$

Therefore,

$$\mathbf{I}_p = \frac{N_2}{N_1} (\mathbf{I}_1 + \mathbf{I}_3) = \frac{1}{110} (24 + 21.96) = 0.42/0^\circ \text{ A}$$

P 9.86 [a]

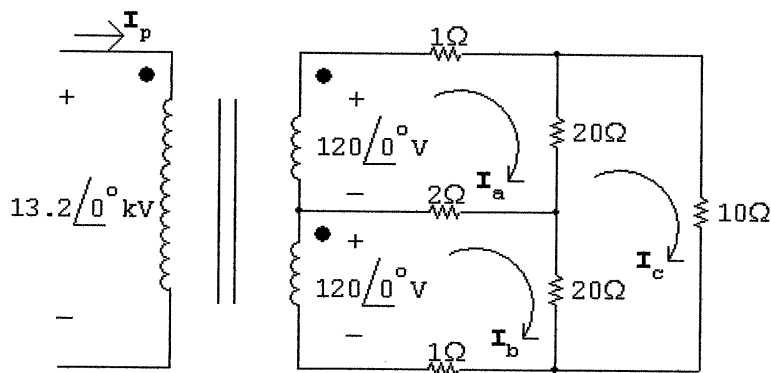

The three mesh current equations are

$$120/0^\circ = 23\mathbf{I}_a - 2\mathbf{I}_b - 20\mathbf{I}_c$$

$$120/0^\circ = -2\mathbf{I}_a + 23\mathbf{I}_b - 20\mathbf{I}_c$$

$$0 = -20\mathbf{I}_a - 20\mathbf{I}_b + 50\mathbf{I}_c$$

Solving,


$$\mathbf{I}_a = 24/0^\circ \text{ A}; \quad \mathbf{I}_b = 24/0^\circ \text{ A}; \quad \mathbf{I}_c = 19.2/0^\circ \text{ A}$$

$$\therefore \mathbf{I}_2 = \mathbf{I}_a - \mathbf{I}_b = 0 \text{ A}$$

$$\begin{aligned}
 \text{[b]} \quad I_p &= \frac{N_2}{N_1}(I_1 + I_3) = \frac{N_2}{N_1}(I_a + I_b) \\
 &= \frac{1}{110}(24 + 24) = 0.436 \text{ A}
 \end{aligned}$$

[c] When the two loads are equal, more current is drawn from the primary.

P 9.87 [a]

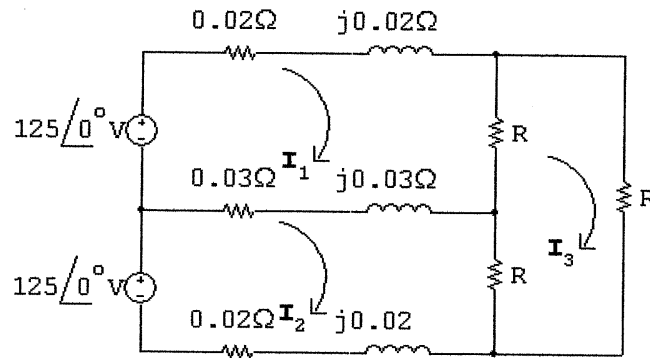

$$125 = (R + 0.05 + j0.05)I_1 - (0.03 + j0.03)I_2 - RI_3$$

$$125 = -(0.03 + j0.03)I_1 + (R + 0.05 + j0.05)I_2 - RI_3$$

Subtracting the above two equations gives


$$0 = (R + 0.08 + j0.08)I_1 - (R + 0.08 + j0.08)I_2$$

$$\therefore I_1 = I_2 \quad \text{so} \quad I_n = I_1 - I_2 = 0 \text{ A}$$

$$\text{[b]} \quad V_1 = R(I_1 - I_3); \quad V_2 = R(I_2 - I_3)$$

Since  $I_1 = I_2$  (from part [a])  $V_1 = V_2$

[c]

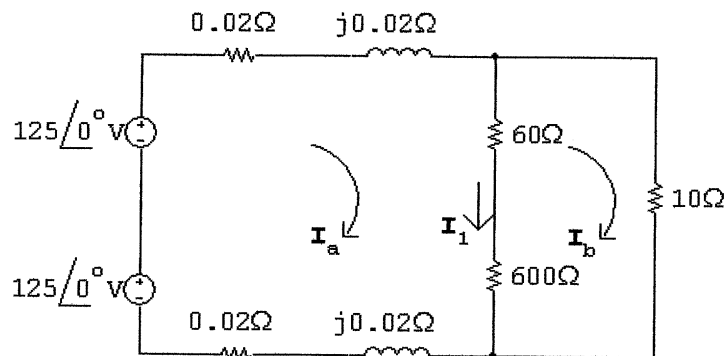

$$250 = (660.04 + j0.04)I_a - 660I_b$$

$$0 = -660I_a + 670I_b$$

Solving,

$$\mathbf{I}_a = 25.275945 / -0.231714^\circ = 25.275738 - j0.10222 \text{ A}$$


$$\mathbf{I}_b = 24.898692 / -0.231713^\circ = 24.898488 - j0.100694 \text{ A}$$

$$\mathbf{I}_1 = \mathbf{I}_a - \mathbf{I}_b = 0.37725 - j0.001526 \text{ A}$$

$$\mathbf{V}_1 = 60\mathbf{I}_1 = 22.635 - j0.09156 = 22.635185 / -0.231764^\circ \text{ V}$$

$$\mathbf{V}_2 = 600\mathbf{I}_1 = 226.35 - j0.9156 = 226.35185 / -0.231764^\circ \text{ V}$$

[d]

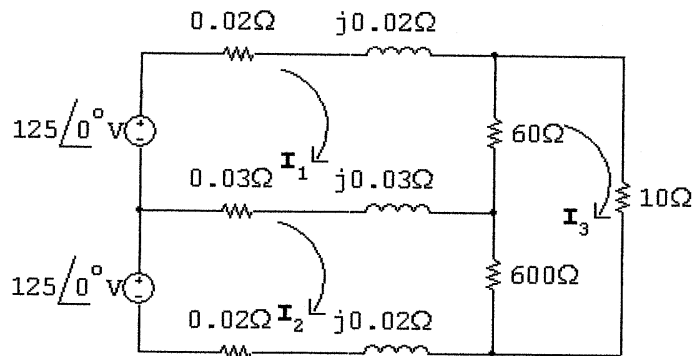

$$125 = (60.05 + j0.05)\mathbf{I}_1 - (0.03 + j0.03)\mathbf{I}_2 - 60\mathbf{I}_3$$

$$125 = -(0.03 + j0.03)\mathbf{I}_1 + (600.05 + j0.05)\mathbf{I}_2 - 600\mathbf{I}_3$$

$$0 = -60\mathbf{I}_1 - 600\mathbf{I}_2 + 670\mathbf{I}_3$$

Solving,

$$\mathbf{I}_1 = 26.97 / -0.24^\circ = 26.97 - j0.113 \text{ A}$$

$$\mathbf{I}_2 = 25.10 / -0.24^\circ = 25.10 - j0.104 \text{ A}$$

$$\mathbf{I}_3 = 24.90 / -0.24^\circ = 24.90 - j0.104 \text{ A}$$

$$\mathbf{V}_1 = 60(\mathbf{I}_1 - \mathbf{I}_3) = 124.4 / -0.27^\circ \text{ V}$$

$$\mathbf{V}_2 = 600(\mathbf{I}_2 - \mathbf{I}_3) = 124.6 / -0.20^\circ \text{ V}$$

[e] Because an open neutral can result in severely unbalanced voltages across the 125 V loads.

P 9.88 [a] Let  $N_1$  = primary winding turns and  $2N_2$  = secondary winding turns.  
Then

$$\frac{14,000}{N_1} = \frac{250}{2N_2}; \quad \therefore \frac{N_2}{N_1} = \frac{1}{112} = a$$

In part c),

$$\mathbf{I}_p = 2a\mathbf{I}_a$$

$$\begin{aligned} \therefore \mathbf{I}_p &= \frac{2N_2\mathbf{I}_a}{N_1} = \frac{1}{56}\mathbf{I}_a \\ &= \frac{1}{56}(25.28 - j0.10) \end{aligned}$$

$$\mathbf{I}_p = 451.4 - j1.8 \text{ mA}$$

In part d),

$$\mathbf{I}_p N_1 = \mathbf{I}_1 N_2 + \mathbf{I}_2 N_2$$

$$\begin{aligned} \therefore \mathbf{I}_p &= \frac{N_2}{N_1}(\mathbf{I}_1 + \mathbf{I}_2) \\ &= \frac{1}{112}(26.97 - j0.11 + 25.10 - j0.10) \\ &= \frac{1}{112}(52.07 - j0.22) \end{aligned}$$

$$\mathbf{I}_p = 464.9 - j1.9 \text{ mA}$$

- [b] Yes, because the neutral conductor carries non-zero current whenever the load is not balanced.