
Sinusoidal Steady State Power Calculations

Assessment Problems

AP 10.1 [a] $\mathbf{V} = 100/\underline{-45^\circ} \text{ V}$, $\mathbf{I} = 20/\underline{15^\circ} \text{ A}$

Therefore

$$P = \frac{1}{2}(100)(20) \cos[-45 - (15)] = 500 \text{ W}, \quad \text{A} \rightarrow \text{B}$$

$$Q = 1000 \sin -60^\circ = -866.03 \text{ VAR}, \quad \text{B} \rightarrow \text{A}$$

[b] $\mathbf{V} = 100/\underline{-45^\circ}$, $\mathbf{I} = 20/\underline{165^\circ}$

$$P = 1000 \cos(-210^\circ) = -866.03 \text{ W}, \quad \text{B} \rightarrow \text{A}$$

$$Q = 1000 \sin(-210^\circ) = 500 \text{ VAR}, \quad \text{A} \rightarrow \text{B}$$

[c] $\mathbf{V} = 100/\underline{-45^\circ}$, $\mathbf{I} = 20/\underline{-105^\circ}$

$$P = 1000 \cos(60^\circ) = 500 \text{ W}, \quad \text{A} \rightarrow \text{B}$$

$$Q = 1000 \sin(60^\circ) = 866.03 \text{ VAR}, \quad \text{A} \rightarrow \text{B}$$

[d] $\mathbf{V} = 100/\underline{0^\circ}$, $\mathbf{I} = 20/\underline{120^\circ}$

$$P = 1000 \cos(-120^\circ) = -500 \text{ W}, \quad \text{B} \rightarrow \text{A}$$

$$Q = 1000 \sin(-120^\circ) = -866.03 \text{ VAR}, \quad \text{B} \rightarrow \text{A}$$

AP 10.2 $\text{pf} = \cos(\theta_v - \theta_i) = \cos[15 - (75)] = \cos(-60^\circ) = 0.5$ leading

$$\text{rf} = \sin(\theta_v - \theta_i) = \sin(-60^\circ) = -0.866$$

AP 10.3 From Ex. 9.4 $I_{\text{eff}} = \frac{I_\rho}{\sqrt{3}} = \frac{0.18}{\sqrt{3}} \text{ A}$

$$P = I_{\text{eff}}^2 R = \left(\frac{0.0324}{3}\right)(5000) = 54 \text{ W}$$

AP 10.4 [a] $Z = (39 + j26) \parallel (-j52) = 48 - j20 = 52 / \underline{-22.62^\circ} \Omega$

$$\text{Therefore } \mathbf{I}_\ell = \frac{250 / 0^\circ}{48 - j20 + 1 + j4} = 4.85 / \underline{18.08^\circ} \text{ A(rms)}$$

$$\mathbf{V}_L = Z\mathbf{I}_\ell = (52 / \underline{-22.62^\circ})(4.85 / \underline{18.08^\circ}) = 252.20 / \underline{-4.54^\circ} \text{ V(rms)}$$

$$\mathbf{I}_L = \frac{\mathbf{V}_L}{39 + j26} = 5.38 / \underline{-38.23^\circ} \text{ A(rms)}$$

[b] $S_L = \mathbf{V}_L \mathbf{I}_L^* = (252.20 / \underline{-4.54^\circ})(5.38 / \underline{+38.23^\circ}) = 1357 / \underline{33.69^\circ}$
 $= (1129.09 + j752.73) \text{ VA}$

$$P_L = 1129.09 \text{ W}; \quad Q_L = 752.73 \text{ VAR}$$

[c] $P_\ell = |\mathbf{I}_\ell|^2 1 = (4.85)^2 \cdot 1 = 23.52 \text{ W}; \quad Q_\ell = |\mathbf{I}_\ell|^2 4 = 94.09 \text{ VAR}$

[d] $S_g(\text{delivering}) = 250 \mathbf{I}_\ell^* = (1152.62 - j376.36) \text{ VA}$

Therefore the source is delivering 1152.62 W and absorbing 376.36 magnetizing VAR.

[e] $Q_{\text{cap}} = \frac{|\mathbf{V}_L|^2}{-52} = \frac{(252.20)^2}{-52} = -1223.18 \text{ VAR}$

Therefore the capacitor is delivering 1223.18 magnetizing VAR.

Check: $94.09 + 752.73 + 376.36 = 1223.18 \text{ VAR}$ and

$$1129.09 + 23.52 = 1152.62 \text{ W}$$

AP 10.5 Series circuit derivation:

$$S = 250\mathbf{I}^* = (40,000 - j30,000)$$

$$\text{Therefore } \mathbf{I}^* = 160 - j120 = 200/\underline{-36.87^\circ} \text{ A(rms)}$$

$$\mathbf{I} = 200/\underline{36.87^\circ} \text{ A(rms)}$$

$$Z = \frac{\mathbf{V}}{\mathbf{I}} = \frac{250}{200/\underline{36.87^\circ}} = 1.25/\underline{-36.87^\circ} = (1 - j0.75) \Omega$$

$$\text{Therefore } R = 1 \Omega, \quad X_C = -0.75 \Omega$$

Parallel circuit derivation:

$$P = \frac{(250)^2}{R}; \quad \text{therefore } R = \frac{(250)^2}{40,000} = 1.5625 \Omega$$

$$Q = \frac{(250)^2}{X_C}; \quad \text{therefore } X_C = \frac{(250)^2}{-30,000} = -2.083 \Omega$$

$$\text{AP 10.6 } S_1 = 15,000(0.6) + j15,000(0.8) = 9000 + j12,000 \text{ VA}$$

$$S_2 = 6000(0.8) + j6000(0.6) = 4800 - j3600 \text{ VA}$$


$$S_T = S_1 + S_2 = 13,800 + j8400 \text{ VA}$$

$$S_T = 200\mathbf{I}^*; \quad \text{therefore } \mathbf{I}^* = 69 + j42 \quad \mathbf{I} = 69 - j42 \text{ A}$$


$$\mathbf{V}_s = 200 + j\mathbf{I} = 200 + j69 + 42 = 242 + j69 = 251.64/\underline{15.91^\circ} \text{ V(rms)}$$

AP 10.7 [a] The phasor domain equivalent circuit and the Thévenin equivalent are shown below:

Phasor domain equivalent circuit:

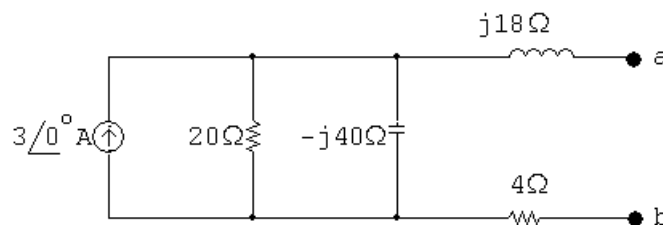

Thévenin equivalent:

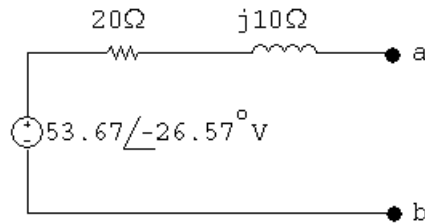

$$\mathbf{V}_{Th} = 3 \frac{-j800}{20 - j40} = 48 - j24 = 53.67 \angle -26.57^\circ \text{ V}$$

$$\mathbf{Z}_{Th} = 4 + j18 + \frac{-j800}{20 - j40} = 20 + j10 = 22.36 \angle 26.57^\circ \Omega$$

For maximum power transfer, $\mathbf{Z}_L = (20 - j10) \Omega$

$$\text{[b] } \mathbf{I} = \frac{53.67 \angle -26.57^\circ}{40} = 1.34 \angle -26.57^\circ \text{ A}$$


$$\text{Therefore } P = \left(\frac{1.34}{\sqrt{2}} \right)^2 20 = 18 \text{ W}$$

$$\text{[c] } R_L = |Z_{Th}| = 22.36 \Omega$$

$$\text{[d] } \mathbf{I} = \frac{53.67 \angle -26.57^\circ}{42.36 + j10} = 1.23 \angle -39.85^\circ \text{ A}$$

$$\text{Therefore } P = \left(\frac{1.23}{\sqrt{2}} \right)^2 (22.36) = 17 \text{ W}$$

AP 10.8

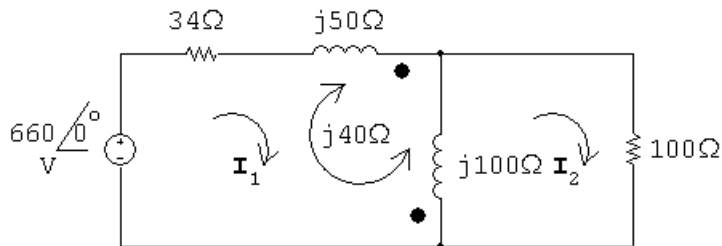

Mesh current equations:

$$660 = (34 + j50)\mathbf{I}_1 + j100(\mathbf{I}_1 - \mathbf{I}_2) + j40\mathbf{I}_1 + j40(\mathbf{I}_1 - \mathbf{I}_2)$$


$$0 = j100(\mathbf{I}_2 - \mathbf{I}_1) - j40\mathbf{I}_1 + 100\mathbf{I}_2$$

Solving,

$$\mathbf{I}_1 = 3.536 \angle -45^\circ \text{ A,}$$

$$\mathbf{I}_2 = 3.5 \angle 0^\circ \text{ A; } \quad \therefore P = \frac{1}{2}(3.5)^2(100) = 612.50 \text{ W}$$

AP 10.9 [a]

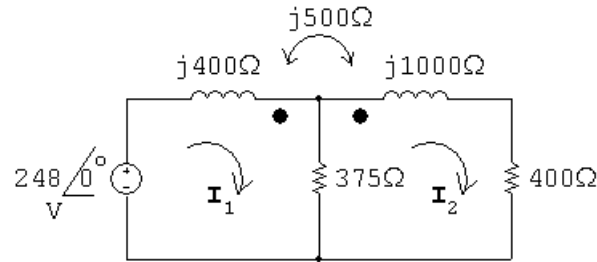

$$248 = j400\mathbf{I}_1 - j500\mathbf{I}_2 + 375(\mathbf{I}_1 - \mathbf{I}_2)$$

$$0 = 375(\mathbf{I}_2 - \mathbf{I}_1) + j1000\mathbf{I}_2 - j500\mathbf{I}_1 + 400\mathbf{I}_2$$

Solving,

$$\mathbf{I}_1 = 0.80 - j0.62 \text{ A}; \quad \mathbf{I}_2 = 0.4 - j0.3 = 0.5/\underline{-36.87^\circ} \text{ A}$$

$$\therefore P = \frac{1}{2}(0.25)(400) = 50 \text{ W}$$

[b] $\mathbf{I}_1 - \mathbf{I}_2 = 0.4 - j0.32 \text{ A}$

$$P_{375} = \frac{1}{2}|\mathbf{I}_1 - \mathbf{I}_2|^2(375) = 49.20 \text{ W}$$

[c] $P_g = \frac{1}{2}(248)(0.8) = 99.20 \text{ W}$

$$\sum P_{\text{abs}} = 50 + 49.2 = 99.20 \text{ W} \quad (\text{checks})$$

AP 10.10 **[a]** $V_{\text{Th}} = 210/\underline{0^\circ} \text{ V}; \quad \mathbf{V}_2 = \frac{1}{4}\mathbf{V}_1; \quad \mathbf{I}_1 = \frac{1}{4}\mathbf{I}_2$

Short circuit equations:

$$840 = 80\mathbf{I}_1 - 20\mathbf{I}_2 + \mathbf{V}_1$$

$$0 = 20(\mathbf{I}_2 - \mathbf{I}_1) - \mathbf{V}_2$$

$$\therefore \mathbf{I}_2 = 14 \text{ A}; \quad R_{\text{Th}} = \frac{210}{14} = 15 \Omega$$

[b] $P_{\text{max}} = \left(\frac{210}{30}\right)^2 15 = 735 \text{ W}$

AP 10.11 **[a]** $\mathbf{V}_{\text{Th}} = -4(146/\underline{0^\circ}) = -584/\underline{0^\circ} \text{ V(rms)} = 584/\underline{180^\circ} \text{ V(rms)}$

$$\mathbf{V}_2 = 4\mathbf{V}_1; \quad \mathbf{I}_1 = -4\mathbf{I}_2$$

Short circuit equations:

$$146/\underline{0^\circ} = 80\mathbf{I}_1 - 20\mathbf{I}_2 + \mathbf{V}_1$$

$$0 = 20(\mathbf{I}_2 - \mathbf{I}_1) + \mathbf{V}_2$$

$$\therefore \mathbf{I}_2 = -146/365 = -0.40 \text{ A}; \quad R_{\text{Th}} = \frac{-584}{-0.4} = 1460 \Omega$$

[b] $P = \left(\frac{-584}{2920}\right)^2 1460 = 58.40 \text{ W}$

Problems

P 10.1 [a] $P = \frac{1}{2}(100)(10) \cos(50 - 15) = 500 \cos 35^\circ = 409.58 \text{ W}$ (abs)

$$Q = 500 \sin 35^\circ = 286.79 \text{ VAR} \quad (\text{abs})$$

[b] $P = \frac{1}{2}(40)(20) \cos(-15 - 60) = 400 \cos(-75^\circ) = 103.53 \text{ W}$ (abs)

$$Q = 400 \sin(-75^\circ) = -386.37 \text{ VAR} \quad (\text{del})$$

[c] $P = \frac{1}{2}(400)(10) \cos(30 - 150) = 2000 \cos(-120^\circ) = -1000 \text{ W}$ (del)

$$Q = 2000 \sin(-120^\circ) = -1732.05 \text{ VAR} \quad (\text{del})$$

[d] $P = \frac{1}{2}(200)(5) \cos(160 - 40) = 500 \cos(120^\circ) = -250 \text{ W}$ (del)

$$Q = 500 \sin(120^\circ) = 433.01 \text{ VAR} \quad (\text{abs})$$

P 10.6 [a] Area under one cycle of v_g^2 :

$$\begin{aligned} A &= (5^2)(2)(30 \times 10^{-6}) + 2^2(2)(37.5 \times 10^{-6}) \\ &= 1800 \times 10^{-6} \end{aligned}$$

Mean value of v_g^2 :

$$\text{M.V.} = \frac{A}{200 \times 10^{-6}} = \frac{1800 \times 10^{-6}}{200 \times 10^{-6}} = 9$$

$$\therefore V_{\text{rms}} = \sqrt{9} = 3 \text{ V(rms)}$$

[b] $P = \frac{V_{\text{rms}}^2}{R} = \frac{3^2}{2.25} = 4 \text{ W}$

P 10.14 [a] $P = \frac{1}{2} \frac{(240)^2}{480} = 60 \text{ W}$

$$-\frac{1}{\omega C} = \frac{-9 \times 10^6}{(5000)(5)} = -360 \Omega$$

$$Q = \frac{1}{2} \frac{(240)^2}{(-360)} = -80 \text{ VAR}$$

$$p_{\text{max}} = P + \sqrt{P^2 + Q^2} = 60 + \sqrt{(60)^2 + (80)^2} = 160 \text{ W (del)}$$

[b] $p_{\text{min}} = 60 - \sqrt{60^2 + 80^2} = -40 \text{ W (abs)}$

[c] $P = 60 \text{ W}$ from (a)

[d] $Q = -80 \text{ VAR}$ from (a)

[e] generate, because $Q < 0$


[f] $\text{pf} = \cos(\theta_v - \theta_i)$

$$\mathbf{I} = \frac{240}{480} + \frac{240}{-j360} = 0.5 + j0.67 = 0.83 \angle 53.13^\circ \text{ A}$$

$$\therefore \text{pf} = \cos(0 - 53.13^\circ) = 0.6 \text{ leading}$$

[g] $\text{rf} = \sin(-53.13^\circ) = -0.8$

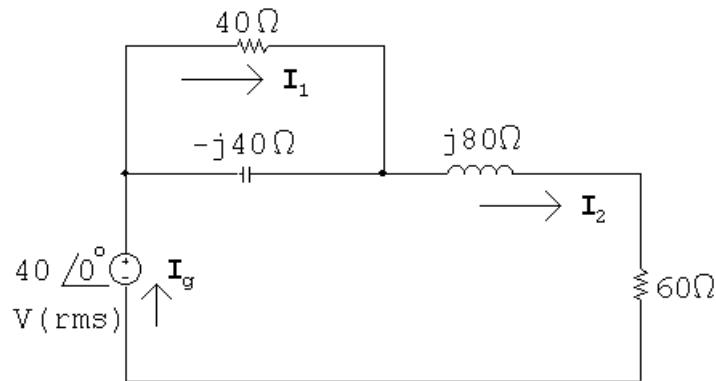P 10.16 [a] $\frac{1}{j\omega C} = -j40 \Omega$; $j\omega L = j80 \Omega$



$$Z_{\text{eq}} = 40 \parallel -j40 + j80 + 60 = 80 + j60 \Omega$$

$$\mathbf{I}_g = \frac{40 \angle 0^\circ}{80 + j60} = 0.32 - j0.24 \text{ A}$$

$$S_g = -\frac{1}{2} \mathbf{V}_g \mathbf{I}_g^* = -\frac{1}{2} 40(0.32 + j0.24) = -6.4 - j4.8 \text{ VA}$$

$$P = 6.4 \text{ W (del)}; \quad Q = 4.8 \text{ VAR (del)}$$

$$|S| = |S_g| = 8 \text{ VA}$$

[b] $\mathbf{I}_1 = \frac{-j40}{40 - j40} \mathbf{I}_g = 0.04 - j0.28 \text{ A}$

$$P_{40\Omega} = \frac{1}{2} |\mathbf{I}_1|^2 (40) = 1.6 \text{ W}$$

$$P_{60\Omega} = \frac{1}{2} |\mathbf{I}_g|^2 (60) = 4.8 \text{ W}$$

$$\sum P_{\text{diss}} = 1.6 + 4.8 = 6.4 \text{ W} = \sum P_{\text{dev}}$$

$$\text{[c]} \mathbf{I}_{-j40\Omega} = \mathbf{I}_g - \mathbf{I}_1 = 0.28 + j0.04 \text{ A}$$

$$Q_{-j40\Omega} = \frac{1}{2} |\mathbf{I}_{-j40\Omega}|^2 (-40) = -1.6 \text{ VAR (del)}$$

$$Q_{j80\Omega} = \frac{1}{2} |\mathbf{I}_g|^2 (80) = 6.4 \text{ VAR (abs)}$$

$$\sum Q_{\text{abs}} = 6.4 - 1.6 = 4.8 \text{ VAR} = \sum Q_{\text{dev}}$$

$$\text{P 10.18 [a]} S_1 = 16 + j18 \text{ kVA}; \quad S_2 = 6 - j8 \text{ kVA}; \quad S_3 = 8 + j0 \text{ kVA}$$

$$S_T = S_1 + S_2 + S_3 = 30 + j10 \text{ kVA}$$

$$250\mathbf{I}^* = (30 + j10) \times 10^3; \quad \therefore \mathbf{I} = 120 - j40 \text{ A}$$


$$Z = \frac{250}{120 - j40} = 1.875 + j0.625 \Omega = 1.98 \angle 18.43^\circ \Omega$$

$$\text{[b]} \text{pf} = \cos(18.43^\circ) = 0.9487 \text{ lagging}$$

$$\text{P 10.33 [a]} Z_{\text{Th}} = j40 \parallel 40 - j40 = 20 - j20$$

$$\therefore Z_L = Z_{\text{Th}}^* = 20 + j20 \Omega$$
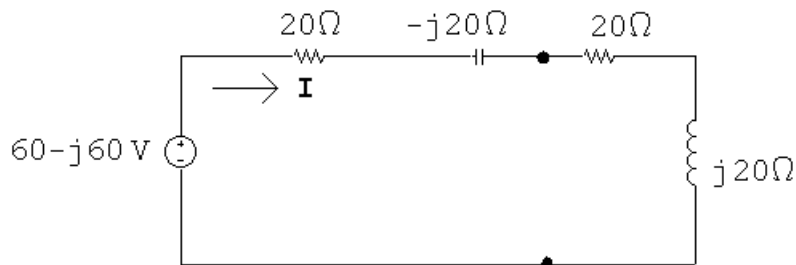
$$\text{[b]} \mathbf{V}_{\text{Th}} = \frac{40}{40 + j40} (120) = 60 - j60 \text{ V}$$



$$\mathbf{I} = \frac{60 - j60}{40} = 1.5 - j1.5 \text{ A}$$

$$P_{\text{load}} = \frac{1}{2} |\mathbf{I}|^2 (20) = 45 \text{ W}$$


$$\text{P 10.38 [a]} \text{ First find the Thévenin equivalent:}$$

$$j\omega L = j3000 \Omega$$

$$Z_{\text{Th}} = 6000 \parallel 12,000 + j3000 = 4000 + j3000 \Omega$$

$$\mathbf{V}_{\text{Th}} = \frac{12,000}{6000 + 12,000} (180) = 120 \angle 0^\circ \text{ V}$$

$$\frac{-j}{\omega C} = -j1000 \Omega$$

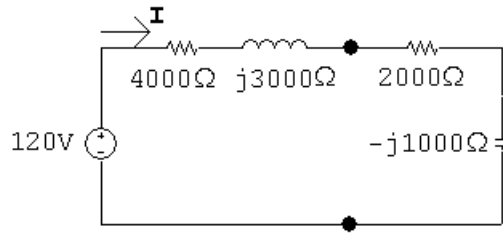

$$\mathbf{I} = \frac{120}{6000 + j2000} = 18 - j6 \text{ mA}$$

$$P = \frac{1}{2} |\mathbf{I}|^2 (2000) = 360 \text{ mW}$$

- [b]** Set $C_o = 0.1 \mu\text{F}$ so $-j/\omega C = -j2000 \Omega$ $j3000 - j2000 = j1000 \Omega$
Set R_o as close as possible to

$$R_o = \sqrt{4000^2 + 1000^2} = 4123.1 \Omega$$

$$\therefore R_o = 4000 \Omega$$

[c] $\mathbf{I} = \frac{120}{8000 + j1000} = 14.77 - j1.85 \text{ mA}$

$$P = \frac{1}{2} |\mathbf{I}|^2 (4000) = 443.1 \text{ mW}$$

Yes; $443.1 \text{ mW} > 360 \text{ mW}$

[d] $\mathbf{I} = \frac{120}{8000} = 15 \text{ mA}$

$$P = \frac{1}{2} (0.015)^2 (4000) = 450 \text{ mW}$$

[e] $R_o = 4000 \Omega$; $C_o = 66.67 \text{ nF}$

[f] Yes; $450 \text{ mW} > 443.1 \text{ mW}$

P 10.39 **[a]** Set $C_o = 0.1 \mu\text{F}$, so $-j/\omega C = -j2000 \Omega$; also set $R_o = 4123.1 \Omega$


$$\mathbf{I} = \frac{120}{8123.1 + j1000} = 14.55 - j1.79 \text{ mA}$$

$$P = \frac{1}{2} |\mathbf{I}|^2 (4123.1) = 443.18 \text{ mW}$$

[b] Yes; $443.18 \text{ mW} > 360 \text{ mW}$

[c] Yes; $443.18 \text{ mW} < 450 \text{ mW}$

P 10.43 [a]

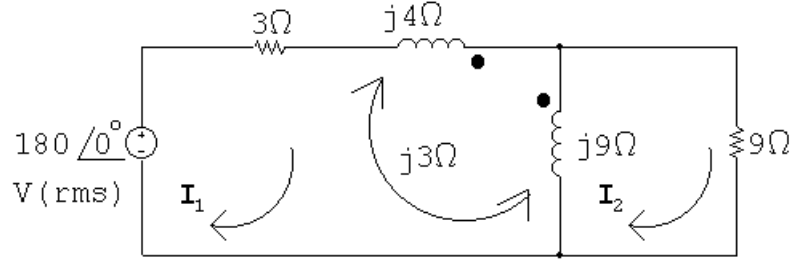

$$180 = 3\mathbf{I}_1 + j4\mathbf{I}_1 + j3(\mathbf{I}_2 - \mathbf{I}_1) + j9(\mathbf{I}_1 - \mathbf{I}_2) - j3\mathbf{I}_1$$

$$0 = 9\mathbf{I}_2 + j9(\mathbf{I}_2 - \mathbf{I}_1) + j3\mathbf{I}_1$$

Solving,

$$\mathbf{I}_1 = 18 - j18 \text{ A(rms)}; \quad \mathbf{I}_2 = 12\angle 0^\circ \text{ A(rms)}$$


$$\therefore \mathbf{V}_o = (12)(9) = 108\angle 0^\circ \text{ V(rms)}$$

$$\text{[b]} P = (12)^2(9) = 1296 \text{ W}$$

$$\text{[c]} S_g = -(180)(18 + j18) = -3240 - j3240 \text{ VA} \quad \therefore P_g = -3240 \text{ W}$$

$$\% \text{ delivered} = \frac{1296}{3240}(100) = 40\%$$

P 10.44 [a] Open circuit voltage:

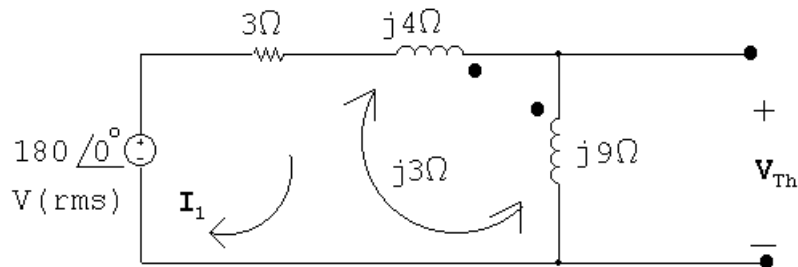


$$180 = 3\mathbf{I}_1 + j4\mathbf{I}_1 - j3\mathbf{I}_1 + j9\mathbf{I}_1 - j3\mathbf{I}_1$$

$$\therefore \mathbf{I}_1 = \frac{180}{3 + j7} = 9.31 - j21.72 \text{ A(rms)}$$

$$\mathbf{V}_{\text{Th}} = j9\mathbf{I}_1 - j3\mathbf{I}_1 = j6\mathbf{I}_1 = 130.34 + j55.86 \text{ V} = 141.81\angle 23.20^\circ \text{ V(rms)}$$

Short circuit current:

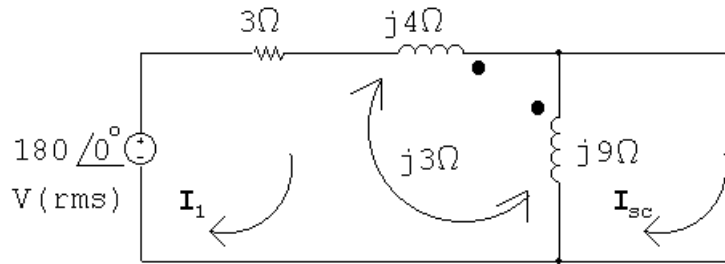


$$180 = 3\mathbf{I}_1 + j4\mathbf{I}_1 + j3(\mathbf{I}_{sc} - \mathbf{I}_1) + j9(\mathbf{I}_1 - \mathbf{I}_{sc}) - j3\mathbf{I}_1$$

$$0 = j9(\mathbf{I}_{sc} - \mathbf{I}_1) + j3\mathbf{I}_1$$

Solving,

$$\mathbf{I}_{sc} = 20 - j20 \text{ A} \quad \mathbf{I}_1 = 30 - j20 \text{ A}$$
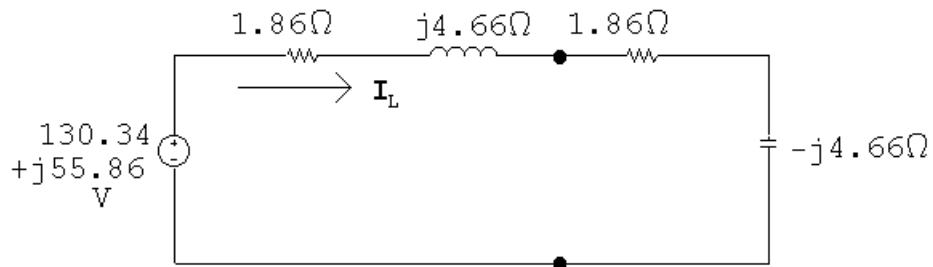
$$Z_{Th} = \frac{\mathbf{V}_{Th}}{\mathbf{I}_{sc}} = \frac{130.34 + j55.86}{20 - j20} = 1.86 + j4.66 \Omega$$




$$\mathbf{I}_L = \frac{130.34 + j55.86}{3.72} = 35 + j15 = 38.08 \angle 23.20^\circ \text{ A}$$

$$P_L = (38.12)^2(1.86) = 2700 \text{ W}$$

[b] $\mathbf{I}_1 = \frac{Z_o + j9}{j6} \mathbf{I}_2 = \frac{1.86 - j4.66 + j9}{j6} (35 + j15) = 30 \angle 0^\circ \text{ A (rms)}$

$$P_{dev} = (180)(30) = 5400 \text{ W}$$

P 10.55 **[a]**

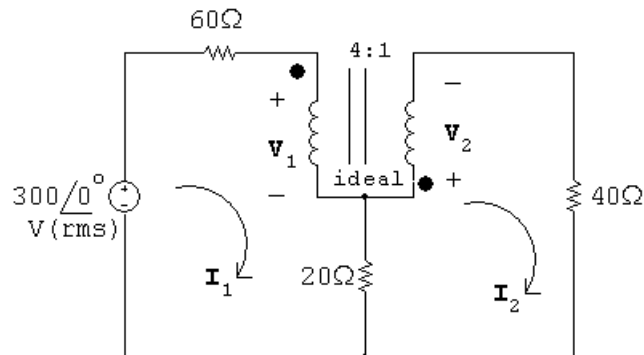

$$300 = 60\mathbf{I}_1 + \mathbf{V}_1 + 20(\mathbf{I}_1 - \mathbf{I}_2)$$

$$0 = 20(\mathbf{I}_2 - \mathbf{I}_1) + \mathbf{V}_2 + 40\mathbf{I}_2$$

$$\mathbf{V}_2 = \frac{1}{4}\mathbf{V}_1; \quad \mathbf{I}_2 = -4\mathbf{I}_1$$

Solving,

$$\mathbf{V}_1 = 260 \text{ V(rms)}; \quad \mathbf{V}_2 = 65 \text{ V(rms)}$$

$$\mathbf{I}_1 = 0.25 \text{ A(rms)}; \quad \mathbf{I}_2 = -1.0 \text{ A(rms)}$$

$$\mathbf{V}_{5A} = \mathbf{V}_1 + 20(\mathbf{I}_1 - \mathbf{I}_2) = 285 \text{ V(rms)}$$


$$\therefore P = -(285)(5) = -1425 \text{ W}$$

Thus 1425 W is delivered by the current source to the circuit.

[b] $\mathbf{I}_{20\Omega} = \mathbf{I}_1 - \mathbf{I}_2 = 1.25 \text{ A(rms)}$

$$\therefore P_{20\Omega} = (1.25)^2(20) = 31.25 \text{ W}$$

P 10.56

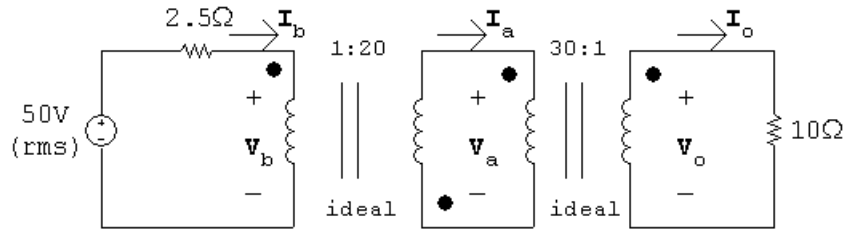

$$30\mathbf{V}_o = \mathbf{V}_a; \quad \frac{\mathbf{I}_o}{30} = \mathbf{I}_a; \quad \mathbf{V}_o = 10\mathbf{I}_o \quad \text{therefore} \quad \frac{\mathbf{V}_a}{\mathbf{I}_a} = 9 \text{ k}\Omega$$

$$\frac{\mathbf{V}_b}{1} = \frac{-\mathbf{V}_a}{20}; \quad \mathbf{I}_b = -20\mathbf{I}_a; \quad \text{therefore} \quad \frac{\mathbf{V}_b}{\mathbf{I}_b} = \frac{9000}{400} = 22.5 \Omega$$

Therefore $\mathbf{I}_b = [50/(2.5 + 22.5)] = 2 \text{ A (rms)}$; since the ideal transformers are lossless, $P_{10\Omega} = P_{22.5\Omega}$, and the power delivered to the 22.5Ω resistor is $2^2(22.5)$ or 90 W .

P 10.57 **[a]** $\frac{\mathbf{V}_b}{\mathbf{I}_b} = \frac{a^2 10}{400} = 2.5 \Omega;$ therefore $a^2 = 100,$ $a = 10$

[b] $\mathbf{I}_b = \frac{50}{5} = 10 \text{ A}; \quad P = (100)(2.5) = 250 \text{ W}$