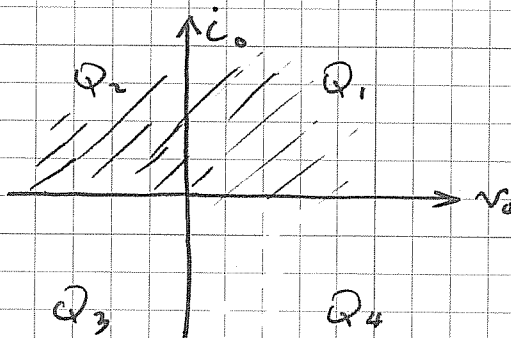


Problem 1:

- a) When T_1 is triggered T_2 is reverse biased and I_o circulates in source and T_1 . The output voltage v_o is nearly equal to the supply voltage. When T_2 is triggered in the negative half-cycle T_1 becomes reverse biased and turns off the current. I_o circulates in T_2 and v_o is ≈ 0 . When $\alpha < 90^\circ$ $V_o > 0$ and the converter operates as a controlled rectifier and when $\alpha > 90^\circ$ the converter operates in inverter mode with $V_o < 0$. The operating quadrants are Q_1 and Q_2 as shown below.



- b) See plots on Question sheet. (attached)


$$c) \quad I_1 = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\pi+\alpha} I_o^2 dt} = \frac{I_o}{\sqrt{2}} \quad V_o = \frac{1}{2\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t dt$$

$$d) \quad PF = \frac{V_s I_{s1} \cos \phi_1}{V_s I_s} = \frac{V_m \cos \alpha}{\pi}$$


$$I_s = \frac{I_o}{\sqrt{2}} \quad \text{and} \quad I_{s1} = \frac{4I_o}{2\sqrt{2}\pi} \quad \text{from Fourier Series Analysis}$$

$$\phi_1 = \alpha \quad \therefore \quad PF = \frac{2}{\pi} \cos \alpha$$




PLOT SHEET 1

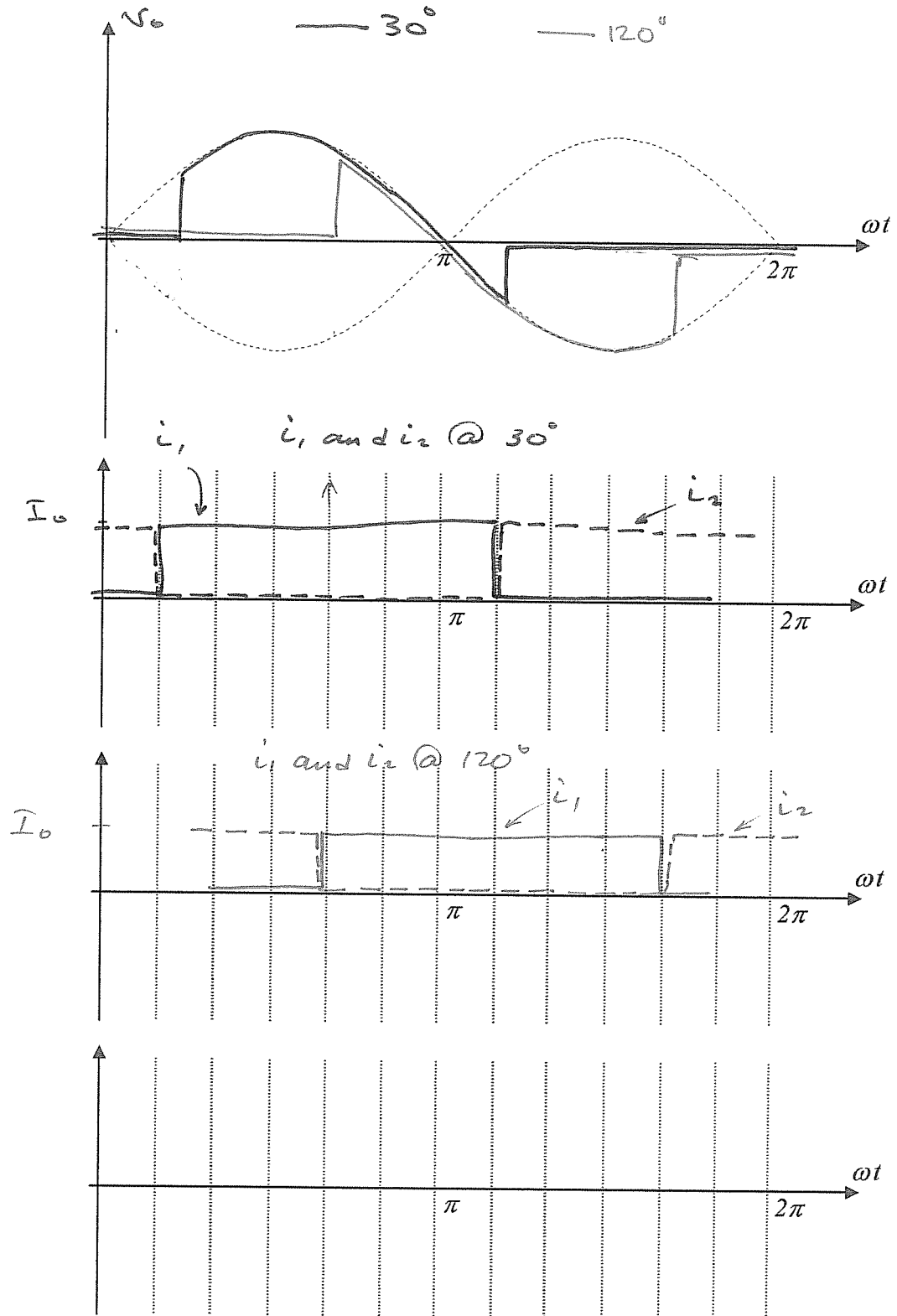

Problem 2.

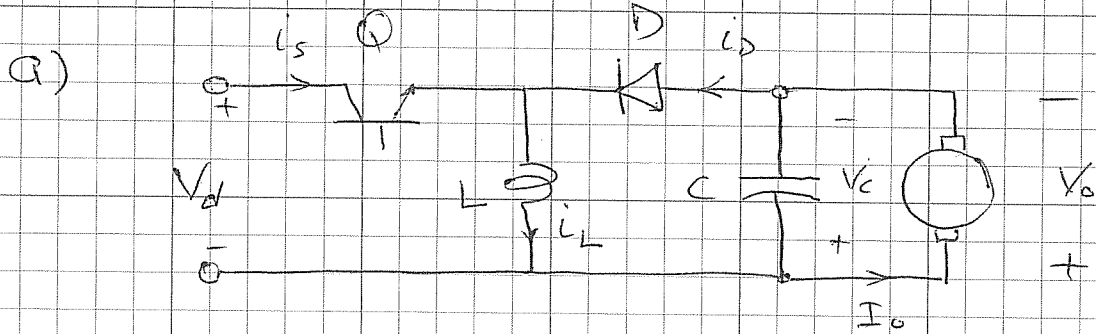

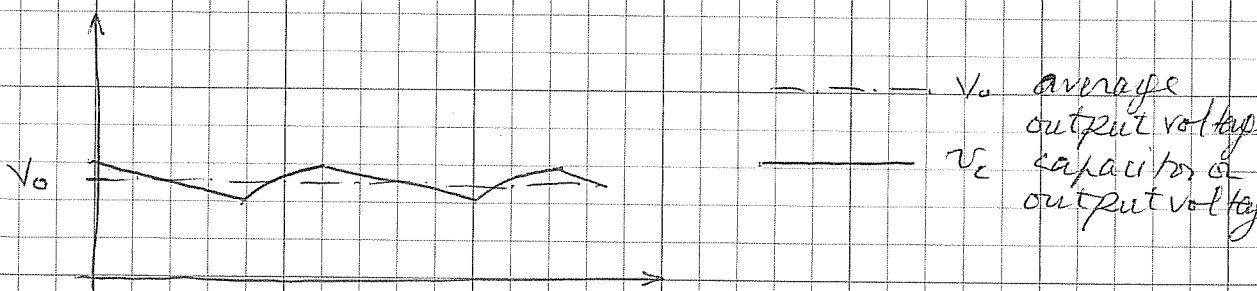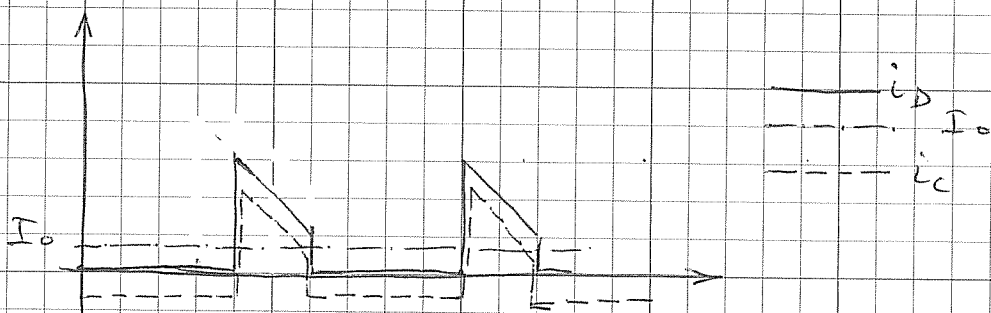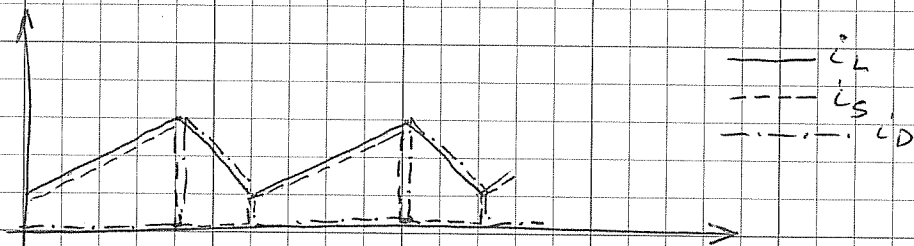Two modes of operation: Mode M₁, the transistor Q is on, L is charged at a rate V_d/L and the energy in C is discharge to the load. In mode M₂, Q is off and energy in L charges capacitor and load.



$$c) \quad I_{LB} = I_s + I_o$$

$$\text{but } I_s = I_o \frac{D}{1-D}$$

$$\text{at } D_1 = 0.33 \Rightarrow I_s = 7.39 \text{ A}$$

$$D_2 = 0.6 \Rightarrow I_s = 22.5 \text{ A}$$

$\therefore I_{LB1}$ calculated at $D_1 = 0.33$ is 22.4 A

I_{LB2} calculated at $D_2 = 0.6$ is 37.5 A.

$$L > \frac{V_d D_1}{2f_s I_{LB1}} = 14.1 \mu\text{H}$$

$$L > \frac{V_d D_2}{2f_s I_{LB2}} = 15.4 \mu\text{H}$$

Select $L = 20 \mu\text{H}$.

$$C = \frac{I_o D}{f_s \Delta V_o} = \frac{15 \times 0.6}{25 \times 10^3 \times 0.1} = 3600 \mu\text{F}$$

d) Peak transistor current is $I_2 = I_L + \frac{D I_o}{2}$

$$I_L = I_o + I_s = \frac{I_o}{1-D} \Rightarrow I_2 = \frac{I_o}{1-D} + \frac{V_d D}{2f_s L} \Rightarrow$$

$$D = 0.33 \Rightarrow I_2 = \frac{15}{0.67} + \frac{48 \times 0.33}{2 \times 25 \times 10^3 \times 20 \times 10^{-6}} = 38.23 \text{ A}$$

$$D = 0.6 \Rightarrow I_2 = \frac{15}{0.4} + 48 \times 0.6 = \underline{\underline{66.3 \text{ A}}}$$


b) Buck-boost regulator is needed because output voltage can be higher or lower than supply V_d .

$$V_o = \frac{D V_d}{1-D} \Rightarrow V_o = 24 \text{ V} \Rightarrow D = 0.33$$

$$\text{and at } V_o = 72 \text{ V} \Rightarrow D = 0.6$$

The peak transistor current is mainly determined by the load current and the maximum duty cycle allowed. The higher the duty cycle, the higher the peak transistor current. The effect of frequency on the peak transistor current is secondary in comparison, but a higher frequency will allow a smaller inductance L , which makes it easier to construct.

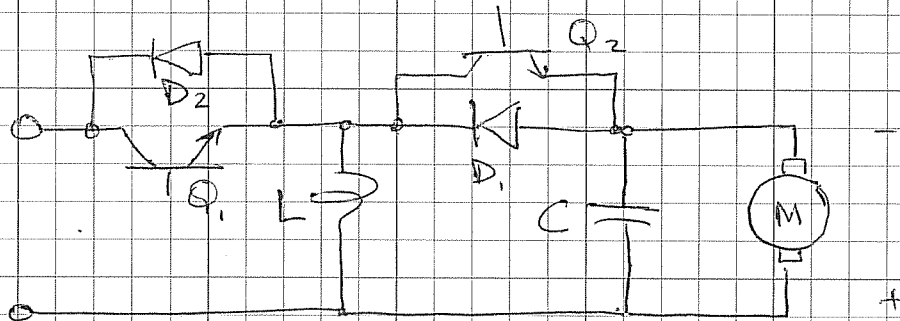e) A diode and transistor are added as shown:



To drive the motor Q_2 is turned off and Q_1 is switched (on-off) with a variable duty cycle. To br. the motor, Q_1 is turned off and Q_2 is switched on-off.

Date: June 6, 2005

Name: Final Exam 2005


Course: EECE 473

ON MY HONOR, I WILL NOT GIVE OR RECEIVE ANY ASSISTANCE ON THIS QUIZ OR EXAM.

Signature: _____

Problem 3:

a)

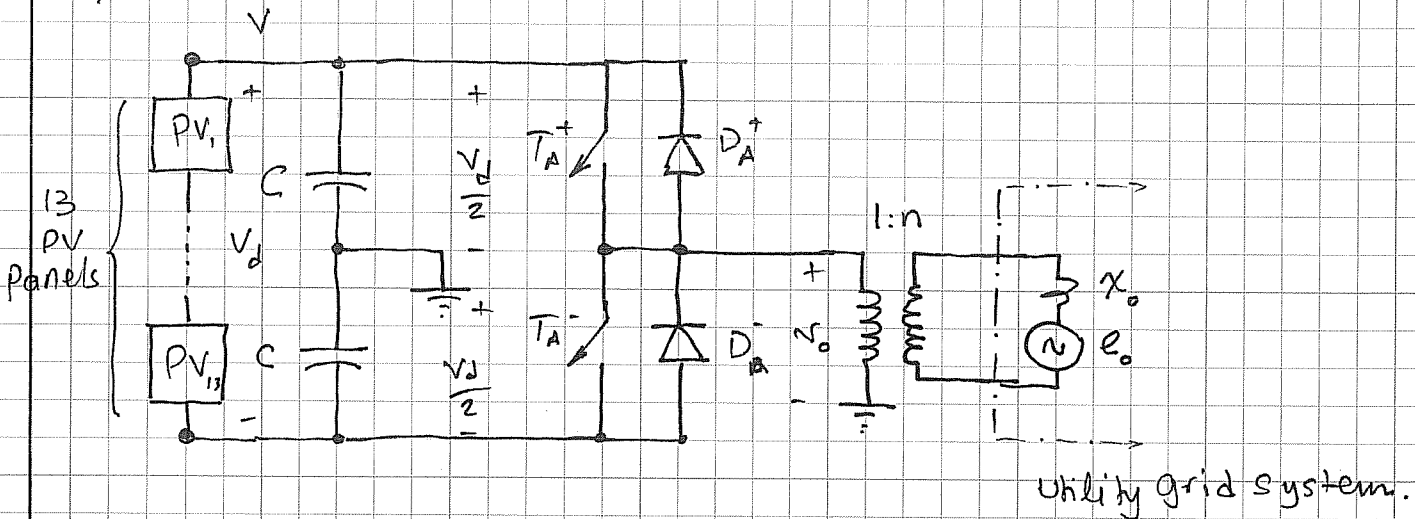

The connection diagram is as shown above. The switches T_A⁺ and T_A⁻ are turned on and off in a complementary way using a trigger signal derived from the comparison of a control signal (V_c) and a triangular signal (V_t) as shown on the plot sheet (2). When V_c > V_t T_A⁺ is on (T_A⁻ is off) and vice versa when V_c < V_t T_A⁺ is off and T_A⁻ is on. When T_A⁺ is on V_o is $\frac{V_d}{2}$ and when T_A⁻ is on V_o = $-\frac{V_d}{2}$.

b) Let us try the middle end transformer, i.e. 1:3 (= 1:n)
The output voltage inverter (fundamental component) is given by:

$$\hat{V}_{o1} = \frac{\sqrt{2} E_o}{n}$$

For the half-bridge inverter:

$$\hat{V}_{o1} = m_a \frac{V_d}{2}$$

$$\text{where } V_d = \{ 13 \times 18 = 234 \text{V}; 13 \times 9 \text{V} = 117 \text{V} \}$$

As V_d varies m_a will be varied to match the fundamental of the inverter output with that of the utility:

$$m_a = \frac{2\hat{V}_{o1}}{V_d}$$

$$\text{For } V_d = 117 \text{V} \quad m_a = 1.77$$


$$V_d = 234 \text{V} \quad m_a = 0.886$$

Since $m_a > \frac{4}{\pi} = 1.273$ we need to go to a higher n .

$$\text{At } n=4 \quad \hat{V}_{o1} = 77.77 \text{V} \quad m_a = \{ 1.329; 0.665 \}$$

$$m_a > 1.273$$

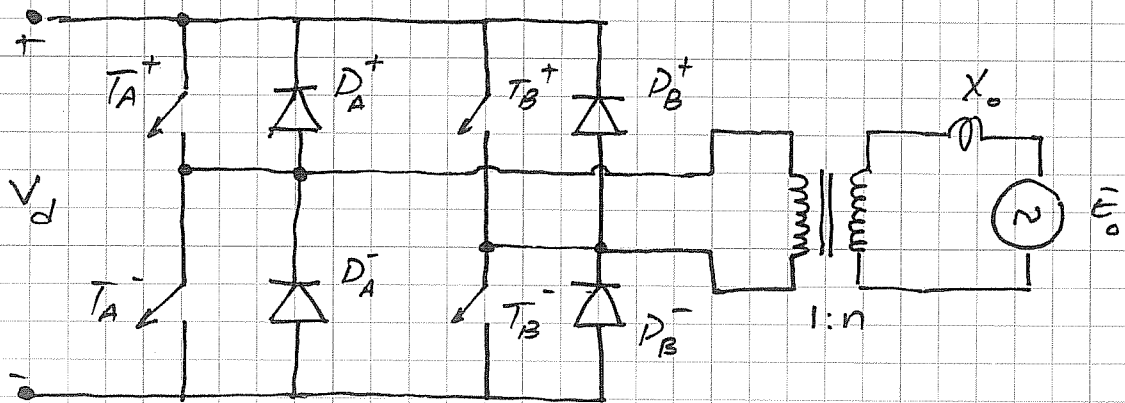Discussion: If m_a is limited to 1.0, for the purpose of controlling the harmonics, then the minimum voltage that can be accommodated is $V_d = 2\hat{V}_{o1}/m_a = 155.5 \text{V}$ or 11.96V (155.5V per panel). If the full range is strictly needed then a full bridge inverter can be used as follows:



In this case with $n=3$ as transformer ratio:

$$\hat{V}_{o1} = m_a V_d \Rightarrow m_a = \frac{\hat{V}_{o1}}{V_d}$$

$$\text{but } \hat{V}_{o1} = \frac{\sqrt{2} \cdot 220}{3} = \frac{311.1}{3} = 103.7 \text{ V}$$

In this case as V_d changes from 117 to 234V, the range of m_a is $\{0.886; 0.443\}$. The system in this case would be able to sustain a lower voltage per panel for a $m_a=1$: $V_d = 103.7 = 13 \times 7.8 \text{ V}$.

So the inverter would be able to supply power now to a lower panel voltage of 7.8V.

c) The five most dominant harmonics are at: (for $\frac{1}{2}$ bridge).

$$f_1, m_f, f_1(m_f+2), f_1(m_f-2), f_1(2m_f+1), f_1(2m_f-1)$$


$$f_{21} = 1050, f_{23} = 1150, f_{19} = 950, f_{43} = 2150, f_{41} = 2050 \text{ rad/s}$$

The corresponding harmonic voltages at $m_a=1$ are:

$$V_{on} = \frac{1}{\sqrt{2}} \frac{V_d}{2} \left(\frac{\hat{V}_{on}}{V_d/2} \right) = \frac{1}{\sqrt{2}} \frac{155.5}{2} \left(\frac{\hat{V}_{on}}{V_d/2} \right) = 55 \left(\frac{\hat{V}_{on}}{V_d/2} \right)$$

d) Equivalent circuits

* At fundamental frequency:

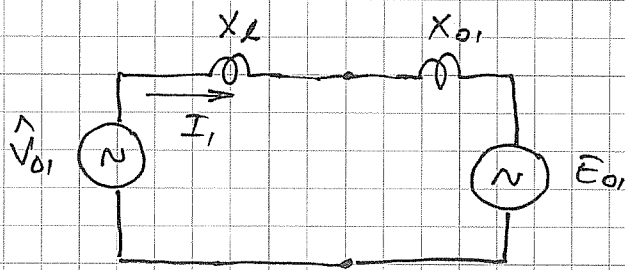

X_{o1} and E_{o1} are the reflected values of X_o and E_o .


$$X_{o1} = \frac{1}{n^2} X_o = \frac{1}{4^2} \times 1.4 \times 10^{-3} \times 314 = 0.0275 \Omega$$

$$E_{o1} = \frac{1}{n} E_o = \frac{220}{4} = 55 \text{ V rms.} \Rightarrow \hat{E}_{o1} = 55 \times \sqrt{2} = 77.8 \text{ V.}$$

$$\hat{V}_{o1} = 77.8 \text{ V.}$$

$$X_L = \frac{1 \times 10^{-3} \times 314}{4^2} = 0.196 \Omega$$

* At the harmonic frequencies:

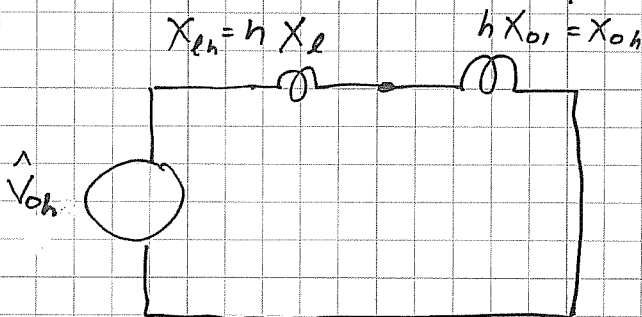


As illustrated in the plots of Plot sheet 2, the maximum current ripple occurs around the zero crossing of the fundamental. Using the ripple integral, the peak-to-peak current ripple ΔI_r is given by:

$$\Delta I_r \approx \frac{1}{L} \int_{t_1}^{t_2} V_d dt = \frac{V_d}{L} (t_2 - t_1) = \frac{V_d}{L} \Delta t$$


$\Delta t = t_2 - t_1$, is nearly equal to about a period of the triangular carrier wave: $\Delta t = \frac{T_s}{2} = \frac{1}{2f_s} = \frac{1}{2 \times m_f \times f_i} = \frac{1}{2 \times 21 \times 50} = 4.76 \times 10^{-4}$

$$\therefore \Delta I_r = \frac{155.5}{\frac{(10+1.4)}{4^2}} \times 4.76 \times 10^{-4} = 0.104 \text{ A}$$

e) phasor diagram and Power:

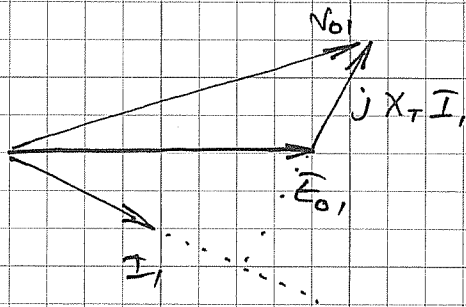

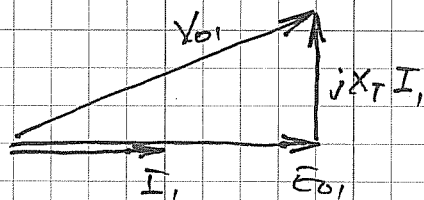This is the phasor diagram of the fundamental inductor



Phasor diagram when current is in phase with utility voltage.

Consider the cell operating at rated insulation i.e. providing a power of $120 \text{ W} \times 13 = 1560 \text{ W}$. About 15% is lost in the inverter-transformer set-up, so 1326 W is reach the utility. Therefore the rms of the current $I_1 = \frac{1326}{55} = 24$

From the phasor diagram: $E_{o1}^2 + (X_T I_1)^2 = V_{o1}^2 \Rightarrow$

